

# EE247

## Lecture 18



### ADC Converters

- Sampling switch charge injection
  - Bottom plate sampling
  - Flip around track & hold
  - Sample and hold including gain
  - Sample and hold including offset cancellation
- Impact of ESD protection on converters
- ADC architectures

### Sampling Switch Charge Injection Summary


- Extra charge injected onto sampling capacitor @ switch device turn-off
  - Charge sharing with  $C_{ov}$
  - Channel charge transfer
- Issues:
  - DC offset
  - Input dependant error voltage → distortion
- Solutions:
  - Complementary switch → only cancels offset, does not address input signal dependant error
  - Addition of dummy switches → cancels charge injection to 1<sup>st</sup> order but not fully
  - Bottom-plate sampling?
  
## Switch Charge Injection Bottom Plate Sampling




- Switches M2A @ B are opened slightly earlier compared to M1A & B  
 → Injected charge by the opening of M2AB is constant & eliminated when used differentially
- Since bottom plate of  $C_s$  is open when M1A & B are opened → no charge injected on  $C_s$

## Flip-Around T/H

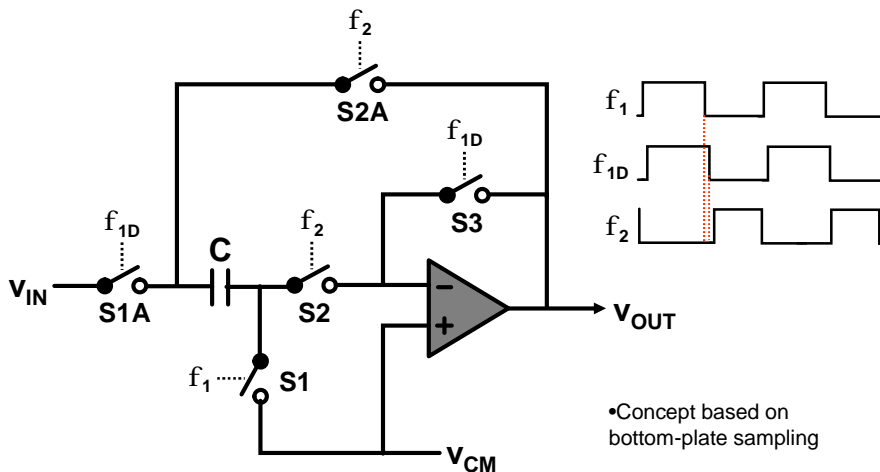


- Concept based on bottom-plate sampling


# Flip-Around T/H

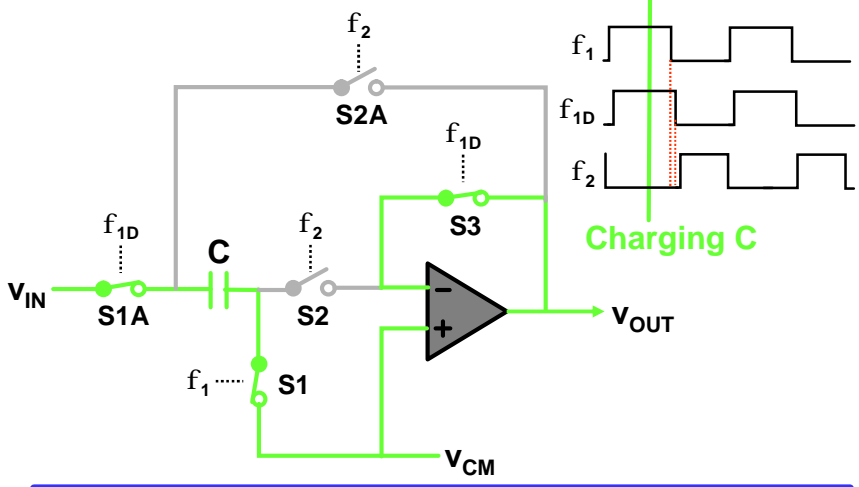

# Flip-Around T/H

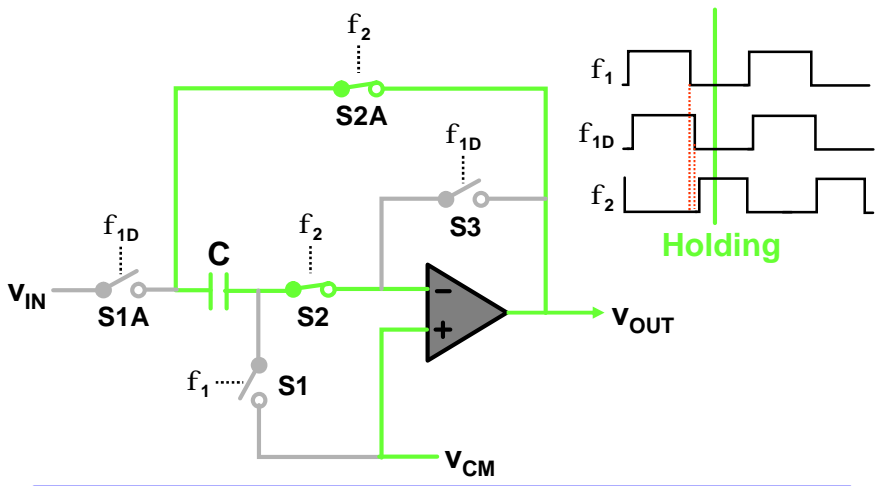


## Flip-Around T/H - Timing

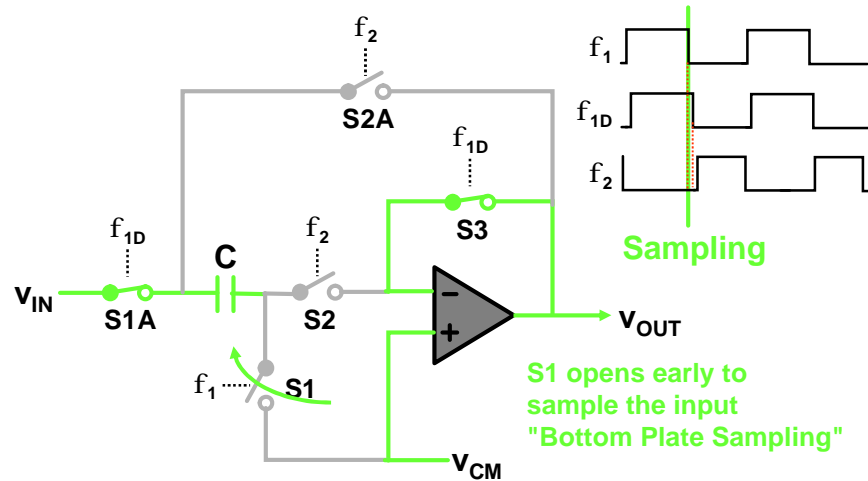


## Charge Injection

- At the instant of sampling, some of the charge stored in sampling switch S1 is dumped onto C
- With "Bottom Plate Sampling", charge injection comes only from S1 and is to first-order independent of  $v_{IN}$ 
  - Only a dc offset is added to the input signal
  - This dc offset can be removed with a differential architecture

# Flip-Around T/H

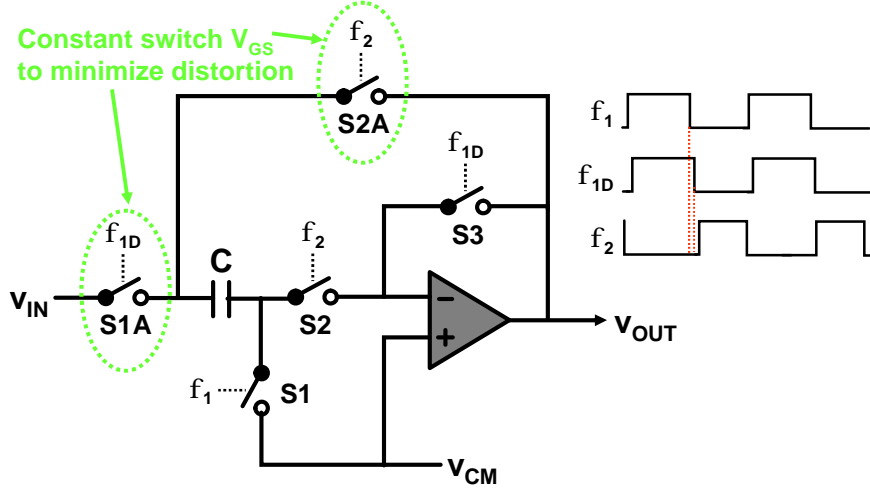


# Flip-Around T/H

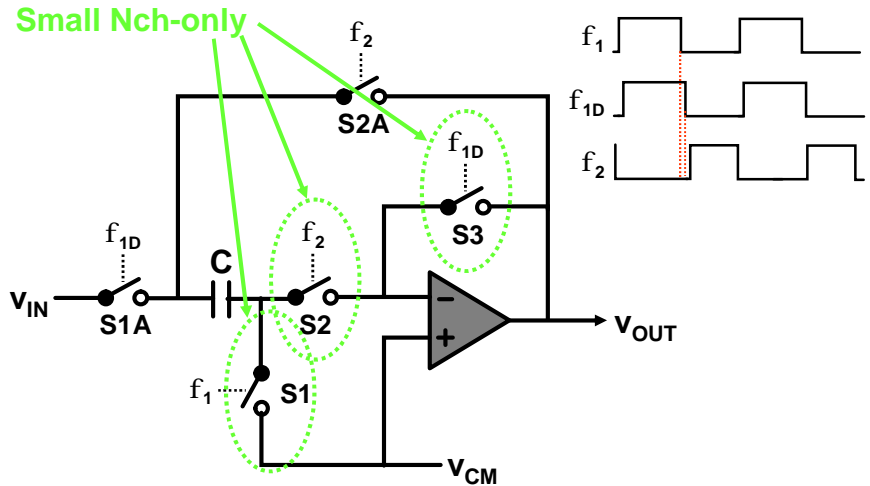

## Flip-Around T/H

- S1 is an n-channel MOSFET
- Since it always switches the same voltage, its on-resistance,  $R_{S1}$ , is signal-independent (to first order)
- Choosing  $R_{S1} \gg R_{S1A}$  minimizes the non-linear component of  $R = R_{S1A} + R_{S1}$ 
  - S1A is a wide (much lower resistance than S1) constant  $V_{GS}$  switch
  - In practice size of S1A is limited by the (nonlinear) S/D capacitance that also adds distortion
  - If S1A's resistance is negligible  $\rightarrow$  delay depends only on S1 resistance
  - S1 resistance is independent of  $v_{IN}$   $\rightarrow$  delay is independent of  $v_{IN}$



## Differential Flip-Around T/H

 

Offset voltage associated with charge injection of S11 & S12 cancelled by differential nature of the circuit



Ref: W. Yang, et al. "A 3-V 340-mW 14-b 75-Msample/s CMOS ADC With 85-dB SFDR at Nyquist Input," IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 36, NO. 12, DECEMBER 2001 1931

# Differential Flip-Around T/H

  

- Gain=1
- Feedback factor=1
- $\Delta V_{in-cm} = V_{out-cm} - V_{sig-com}$   
 $\rightarrow$  Amplifier needs to have large input common-mode compliance

  
# Differential Flip-Around T/H Choice of Sampling Switch Size



- THD simulated w/o sampling switch boosted clock  $\rightarrow$  -45dB
- THD simulated with sampling switch boosted clock (see figure)


Ref: K. Vleugels et al. "A 2.5-V Sigma-Delta Modulator for Broadband Communications Applications"  
 IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 36, NO. 12, DECEMBER 2001, pp. 1887

# Input Common-Mode Cancellation

 

Ref: R. Yen, et al. "A MOS Switched-Capacitor Instrumentation Amplifier,"  
IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. SC-17, NO. 6., DECEMBER 1982 1008

# Input Common-Mode Cancellation

 


Track mode ( $\phi$  high)  
 $V_{C1}=V_{I1}$  ,  $V_{C2}=V_{I2}$   
 $V_{O1}=V_{O2}=0$

Hold mode ( $\phi$  low)  
 $V_{O1}+V_{O2} = 0$   
 $V_{O1}-V_{O2} = -(V_{I1}-V_{I2})(C_1/(C_1+C_3))$

→ Input common-mode level removed



## S/H + Charge Redistribution Amplifier

 

Track mode (S1, S3 → on S2 → off)

$$V_{C1} = V_{OS} - V_{IN}, V_{C2} = 0$$

$$V_o = V_{OS}$$

## S/H + Charge Redistribution Amplifier Cont'd

$$V_{C1} \rightarrow V_{OS}$$


$$\Delta V_{C1} = V_{OS} - (V_{OS} - V_{IN}) = V_{IN}$$

$$\Delta Q_1 = C_1 \Delta V_{C1} = C_1 V_{IN}$$

$$\Delta Q_2 = C_2 \Delta V_{C2} = \Delta Q_1$$

$$\Delta V_{C2} = \left(\frac{C_1}{C_2}\right) V_{C1} = V_{C2}$$
 
$$V_o = V_{C2} + V_{OS} = \left(\frac{C_1}{C_2}\right) V_{IN} + V_{OS}$$





Hold/amplify mode (S1, S3 → off S2 → on)

→ Offset NOT cancelled, but not amplified

→ Input-referred offset =  $(C_2/C_1) \times V_{OS}$ , &  $C_2 < C_1$

## S/H & Input Difference Amplifier

  

Sample mode (S1, S3 → on S2 → off)  
 $V_{C1} = V_{os} - V_{11}$ ,  $V_{C2} = 0$   
 $V_o = V_{os}$

## Input Difference Amplifier Cont'd


Subtract/Amplify mode (S1, S3 → off S2 → on)  
 During previous phase:  
 $V_{C1} = V_{os} - V_{11}$ ,  $V_{C2} = 0$   
 $V_o = V_{os}$

$$V_{C1} = V_{os} - V_{12}$$

$$\Delta V_{C1} = (V_{os} - V_{12}) - (V_{os} - V_{11}) = V_{11} - V_{12}$$


$$\Delta V_{C2} = \left(\frac{C_1}{C_2}\right) \Delta V_{C1} = \left(\frac{C_1}{C_2}\right) (V_{11} - V_{12})$$
 
$$V_o = \left(\frac{C_1}{C_2}\right) (V_{11} - V_{12}) + V_{os}$$




→ Offset NOT cancelled, but not amplified  
 → Input-referred offset =  $(C_2/C_1) \times V_{os}$ , &  $C_2 < C_1$

## S/H & Summing Amplifier

 


## S/H & Summing Amplifier Cont'd

 

Sample mode (S1, S3, S5 → on, S2, S4 → off)  
 $V_{C1} = V_{OS} - V_{11}$ ,  $V_{C2} = V_{OS} - V_{13}$ ,  $V_{C3} = 0$   
 $V_O = V_{OS}$
 
## S/H & Summing Amplifier Cont'd

Amplify mode (S1, S3, S5 → off, S2, S4 → on)



$$V_{C1} = V_{OB} - V_{I2} \Rightarrow \Delta V_{C1} = V_{I1} - V_{I2}$$


$$V_{C2} = V_{OB} - V_{I4} \Rightarrow \Delta V_{C2} = V_{I3} - V_{I4}$$

$$\Delta Q_3 = \Delta Q_1 + \Delta Q_2 = C_1 \Delta V_{C1} + C_2 \Delta V_{C2}$$

$$\Delta V_{C3} = \frac{\Delta Q_3}{C_3} = \left(\frac{C_1}{C_3}\right)(V_{I1} - V_{I2}) + \left(\frac{C_2}{C_3}\right)(V_{I3} - V_{I4})$$


$$V_O = \left(\frac{C_1}{C_3}\right)(V_{I1} - V_{I2}) + \left(\frac{C_2}{C_3}\right)(V_{I3} - V_{I4}) + V_{OB}$$
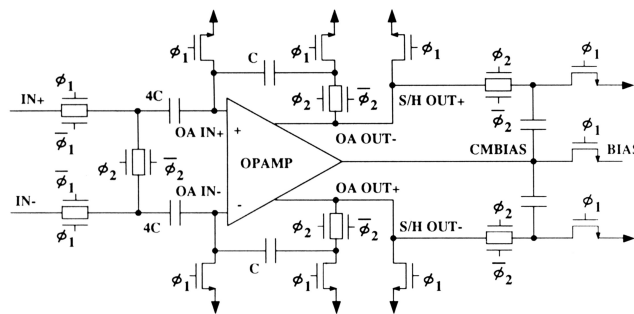
## Differential S/H Combined with Gain Stage




Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987
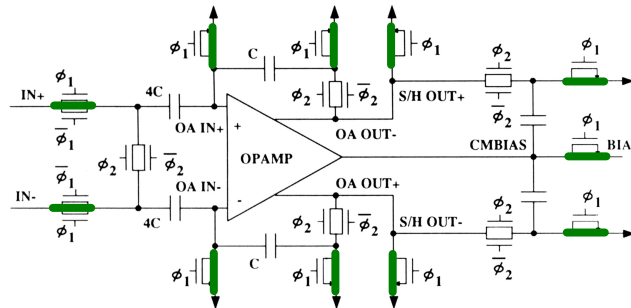
## Differential S/H Combined with Gain Stage



Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987

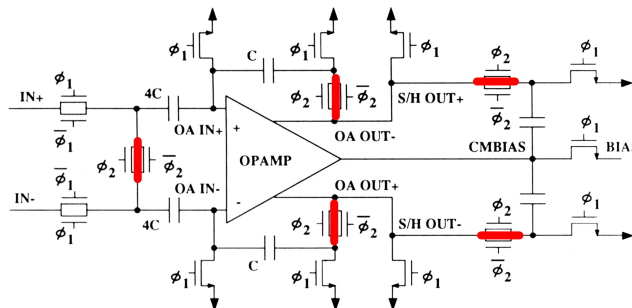
## Differential S/H Combined with Gain Stage



- $Gain = 4C/C = 4$
- $Feedback\ factor = 1/(1+G) = 0.2$
- *Input common-mode level removed*
- *Amplifier offset not removed*

Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987
 
## Differential S/H Including Offset Cancellation




- Operation during offset cancellation shown
- Auxiliary inputs added with  $A_{\text{main}}/A_{\text{aux}}=10$
- During offset cancellation phase AZ and S1 closed  $\rightarrow$  main amplifier offset stored on  $C_{AZ}$
- Auxiliary amp chosen to have lower gain so that aux. amp offset & charge injection associated with opening of switch AZ  $\rightarrow$  reduced by  $A_{\text{aux}}/A_{\text{main}}=1/10$
- Requires an extra auto-zero clock phase

Ref: H. Ohara, et al., "A CMOS programmable self-calibrating 13-bit eight-channel data acquisition peripheral," *IEEE Journal of Solid-State Circuits*, vol. 22, pp. 930 - 938, December 1987.
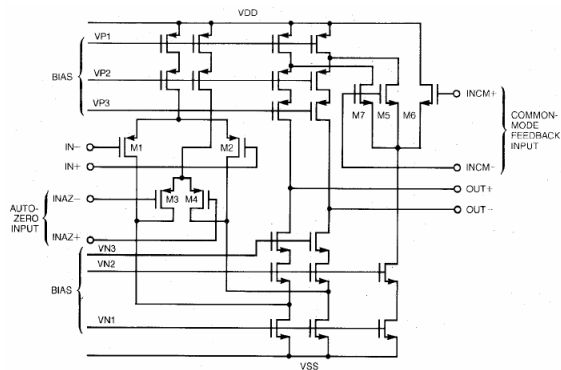
## Differential S/H Including Offset Cancellation Operational Amplifier

- Operational amplifier  $\rightarrow$  dual input folded-cascode opamp
- M3,4 auxiliary input, M1,2 main input
- To achieve 1/10 gain ratio  $W_{M3,4} = 1/10 \times W_{M1,2}$  & current sources are scaled by 1/10
- M5,6,7  $\rightarrow$  common-mode control
- Output stage  $\rightarrow$  dual cascode  $\rightarrow$  high DC gain



Ref: H. Ohara, et al., "A CMOS programmable self-calibrating 13-bit eight-channel data acquisition peripheral," *IEEE Journal of Solid-State Circuits*, vol. 22, pp. 930 - 938, December 1987.

## ESD Protection ADC Architectures

## What is ESD?

- Electrostatic discharge
- Example: Charge built up on human body while walking on carpet...
- Charged objects near or touching IC pins can discharge through on-chip devices
- Without dedicated protection circuitry, ESD events are destructive



# Model and Protection Circuit


 


Figure 1. Human Body Model for ESD testing.

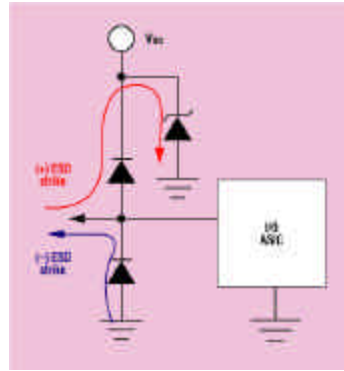

[<http://www.ce-mag.com/archive/03/ARG/dunniho.html>]

# Equivalent Circuit

 



Fig. 1. Equivalent input circuit.

[I. E. Opris, "Bootstrapped pad protection structure," IEEE J. Solid-State Circuits, pp. 300, Feb. 1998.]

- Nonlinear capacitance causes distortion
- Distortion increases with frequency
  - Today's converters: High frequency, low distortion!



# ESD Circuit Distortion

 


[I. E. Opris, "Bootstrapped pad protection structure," IEEE J. Solid-State Circuits, pp. 300, Feb. 1998.]

**$C(V_{in}) = 2..4\text{pF}$**   
**for  $V_{in} = 2..0\text{V}$**

 
# ESD Circuit Distortion

- Analysis:
  - Model nonlinear cap & run SPICE
  - Hand calculations using Volterra Series
- Example:



$R = 25\Omega$   
 $C_{jo} = 1\text{pF}$   
 $C_L = 5\text{pF}$   
 $V_{i\text{peak}} = 0.5\text{V}$

# ESD Circuit Distortion

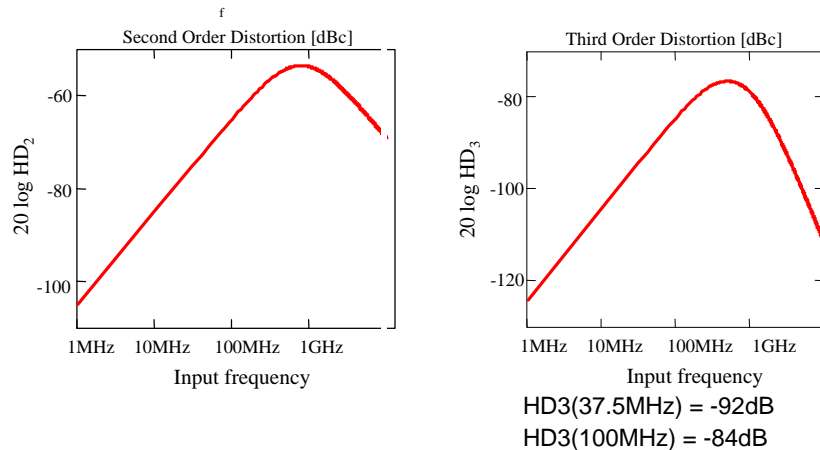


# ESD Circuit Distortion

- Distortion from ESD circuits approaches state of-the-art ADC performance!
- If you are working on a new, record breaking ADC, better think about ESD now...
- Ref.: A. Wang, "Recent developments in ESD protection for RF IC," *Proc. DAC Conference*, Jan. 2003
- Solutions still pre-mature
- Lots of company IP

# ADC Architectures


- Slope Converters
- Successive approximation
- Flash
- Folding
- Time-interleaved / parallel converter
- Residue type ADCs
  - Two-step
  - Pipeline
  - Algorithmic
  - ...
- Oversampled ADCs

# Single Slope ADC

 

- Low complexity
- Hard to generate precise ramp
- Better: Dual Slope, Multi-Slope


# Dual Slope ADC

 

[http://www.maxim-ic.com/appnotes.cfm/appnote\\_number/1041](http://www.maxim-ic.com/appnotes.cfm/appnote_number/1041)

- Integrate  $V_{in}$  for fixed time, de-Integrate with  $V_{ref}$  applied  $\rightarrow T_{De-Int} \sim V_{in}/V_{ref}$
- Insensitive to most linear error sources


# Successive Approximation

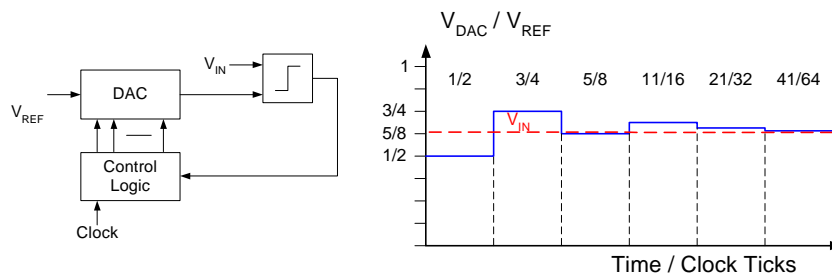


- Binary search over DAC output
- High accuracy achievable (16+ Bits)
- Moderate speed proportional to B (MHz range)
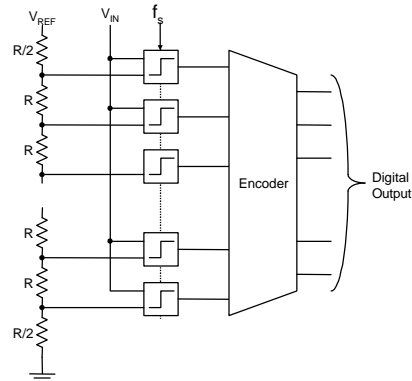
# Flash Converter

- Very fast: only 1 clock cycle per conversion
- High complexity:  $2^B - 1$  comparators
- High input capacitance




# Folding Converter

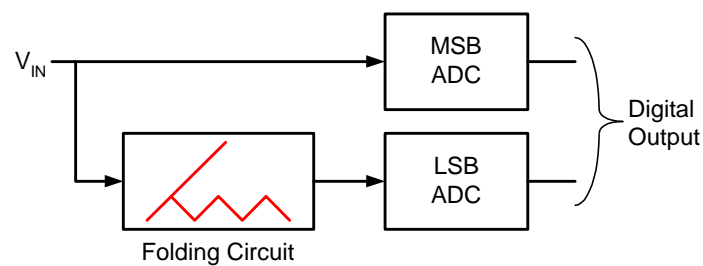


- Significantly fewer comparators than flash
- Fast
- Nonidealities in folder limit resolution to  $\sim 10$ Bits
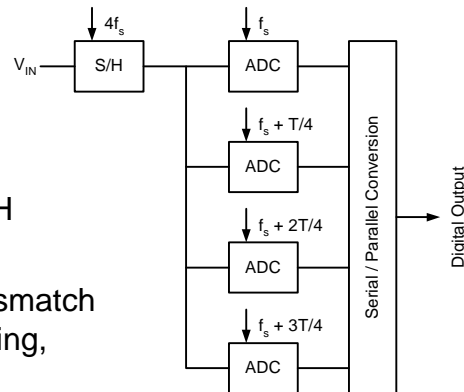
# Time Interleaved Converter

- Extremely fast:  
Limited by speed of S/H
- Accuracy limited by mismatch in individual ADCs (timing, offset, gain, ...)




# Residue Type ADC

 


- Quantization error output (“residuum”) enables cascading for higher resolution
- Great flexibility for stages: flash, oversampling ADC, ...
- Optional S/H enables parallelism (pipelining)
- Fast: one clock per conversion (with S/H), latency

# Pipelined ADC

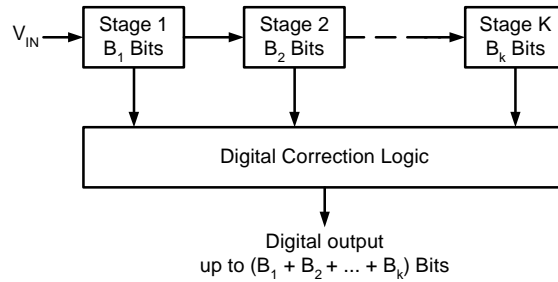


- Approaches speed of flash, but much lower complexity
- One clock per conversion, but K clocks latency
- Efficient digital calibration possible
- Versatile: from 16Bits / 1MS/s to 14Bits / 100MS/s

# Algorithmic ADC

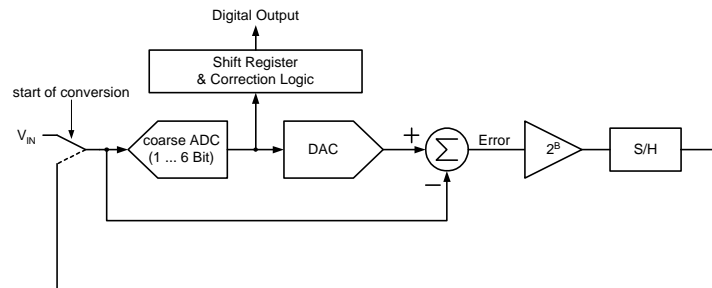


- Essentially same as pipeline, but a single stage is used for all partial conversions
- K clocks per conversion

# Oversampled ADC

 

- Hard to comprehend ... “easy” to build
- Input is oversampled ( $M$  times faster than output rate)
- Reduces Anti-Aliasing filter requirements and capacitor size
- Accuracy independent of component matching
- Very high resolution achievable ( $> 20$  Bits)

# Throughput Rate Comparison

 



# Speed-Resolution Map

