

# EE247

## Lecture 24

- Administrative
  - EE247 Final exam:
    - Date: Wed. Dec. 15<sup>th</sup>
    - Time: -12:30pm-3:30pm-
    - Location: 289 Cory
  - Closed book/course notes
  - No calculators/cell phones/PDAs/Computers
  - Bring one 8x11 paper with your own notes
  - Final exam covers the entire course material

# EE247

## Lecture 24

- Oversampled ADCs
  - 2<sup>nd</sup> order  $\Sigma\Delta$  modulator
    - Practical implementation
      - Effect of various nonidealities on the  $\Sigma\Delta$  performance
- Higher order  $\Sigma\Delta$  modulators
  - Cascaded modulators (multi-stage)
  - Single-loop single-quantizer modulators with multi-order filtering in the forward path


# Oversampled ADCs

## Last Lecture

- Oversampled ADCs
  - 1<sup>st</sup> order  $\Sigma\Delta$  modulator
    - Quantization error
    - SQNR analysis
    - Limit cycle oscillation
  - 2<sup>nd</sup> order  $\Sigma\Delta$  modulator
    - Dynamic range
    - Practical implementation
      - Effect of various nonidealities on the  $\Sigma\Delta$  performance

### 2<sup>nd</sup> Order $\Sigma\Delta$

#### Effect of Integrator Finite DC Gain


 


$$H(z)_{ideal} = \frac{Cs}{CI} \times \frac{z^{-1}}{1-z^{-1}}$$

$$H(z)_{Finite\ DC\ Gain} = \frac{Cs}{CI} \times \frac{\left( \frac{a}{1+a+\frac{Cs}{CI}} \right) z^{-1}}{1 - \left( \frac{1+a}{1+a+\frac{Cs}{CI}} \right) z^{-1}}$$

## 2<sup>nd</sup> Order $\Sigma\Delta$


### Effect of Integrator Finite DC Gain

  

- Low integrator DC gain  $\rightarrow$  degrades noise performance
- If  $a > M$  (oversampling ratio)  $\rightarrow$  Insignificant degradation in SNR
- Normally DC gain designed to be  $\gg M$  in order to suppress nonlinearities

## 2<sup>nd</sup> Order $\Sigma\Delta$


### Effect of Integrator Finite DC Gain

 

- Simulation results
- $H_0 = a \rightarrow$  finite DC gain
- $a > M \rightarrow$  no degradation in SNR


Ref: B.E. Boser and B.A. Wooley, "The Design of Sigma-Delta Modulation A/D Converters," IEEE J. Solid-State Circuits, vol. 23, no. 6, pp. 1298-1308, Dec. 1988.
 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Effect of Integrator Overall Integrator Gain Inaccuracy



- Gain of  $\frac{1}{2}$  in front of integrators is a function of  $C1/C2$  of the integrator
- The effect of  $C1/C2$  inaccuracy inspected by simulation
 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Effect of Integrator Overall Gain Inaccuracy




- Simulation show gain can vary by 20% w/o loss in performance  
→ Confirms insensitivity of  $\Sigma\Delta$  to component variations
- Note that for gain  $>0.65$  system becomes unstable & SNR drops rapidly

Ref: B.E. Boser and B.A. Wooley, "The Design of Sigma-Delta Modulation A/D Converters," IEEE J. Solid-State Circuits, vol. 23, no. 6, pp. 1298-1308, Dec. 1988.


 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Effect of Integrator Nonlinearities




with nonlinearity

$$v(kT + T) = u(kT) + \alpha_1[u(kT)]^2 + \alpha_2[u(kT)]^3 + \dots$$

$$+ v(kT) + \beta_1[v(kT)]^2 + \beta_2[v(kT)]^3 + \dots$$

Ref: B.E. Boser and B.A. Wooley, "The Design of Sigma-Delta Modulation A/D Converters," IEEE J. Solid-State Circuits, vol. 23, no. 6, pp. 1298-1308, Dec. 1988.

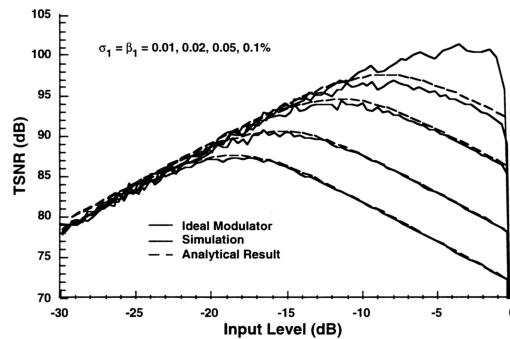
## 2<sup>nd</sup> Order $\Sigma\Delta$ Effect of Integrator Nonlinearities



- Simulation for single-ended topology
- Even order nonlinearities can be significantly attenuated by using differential circuit topologies

Ref: B.E. Boser and B.A. Wooley, "The Design of Sigma-Delta Modulation A/D Converters," IEEE J. Solid-State Circuits, vol. 23, no. 6, pp. 1298-1308, Dec. 1988.

 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Effect of Integrator Nonlinearities



- Simulation for single-ended topology
- Odd order nonlinearities (3<sup>rd</sup> in this case)

Ref: B.E. Boser and B.A. Wooley, "The Design of Sigma-Delta Modulation A/D Converters," IEEE J. Solid-State Circuits, vol. 23, no. 6, pp. 1298-1308, Dec. 1988.
 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Effect of $KT/C$ noise



$$\overline{v_n^2} = 2 \frac{kT}{C_s}$$

$$\overline{v_n^2} / f = 2 \frac{kT}{C_s} \times \frac{1}{f_s/2} = 4 \frac{kT}{C_s \times f_s}$$



Total in-band noise:

$$\overline{v_{n\text{input}}^2} = 4 \frac{kT}{C_s \times f_s} \times B$$

$$= \frac{2kT}{C_s \times M}$$


- For the example of digital audio with 16-bit (100dB) &  $M=256$ 
  - $C_s=1\text{pF} \rightarrow 6\mu\text{V}_{\text{rms}}$  noise
  - If  $FS=4V_{\text{p-p-d}}$  then noise is -107dB → almost no degradation in overall SNR
  - $C_s=1\text{pF}, C_I=2\text{pF} \rightarrow$  small cap area compared to Nyquist ADC caps
  - Since thermal noise provides some level of dithering → better not choose much larger capacitors!
  
## 2<sup>nd</sup> Order $\Sigma\Delta$ Effect of Finite Opamp Bandwidth




Assumption-  
Opamp  $\rightarrow$  does not slew  
Opamp has only one pole  $\rightarrow$  exponential settling
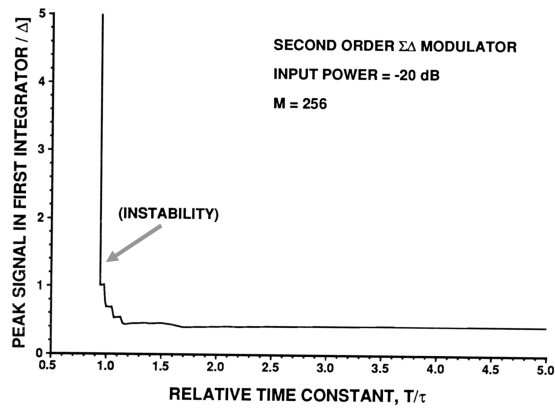
## 2<sup>nd</sup> Order $\Sigma\Delta$ Effect of Finite Opamp Bandwidth




$\rightarrow$   $\Sigma\Delta$  does not require high opamp bandwidth  $f_u > 2f_s$  adequate
 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Effect of Slew Limited Settling



 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Effect of Slew Limited Settling



- Assumption-
- Opamp settling  $\rightarrow$  slew limited
  - $\rightarrow$  Minimum slew rate of 1.2 ( $\Delta \times f_s$ ) required
  - $\rightarrow$  Low slew rate degrade SNR rapidly

 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Effect of Comparator Non-Idealities on SD Performance



1-bit A/D  $\rightarrow$  Single comparator


- Speed must be adequate for the operating sampling rate
- Input referred noise- same as offset
- Input referred offset- feedback loop suppresses the effect  $\rightarrow$   
 $\Sigma\Delta$  performance not sensitive to input referred offset
- Hysteresis= Minimum overdrive required to change the output
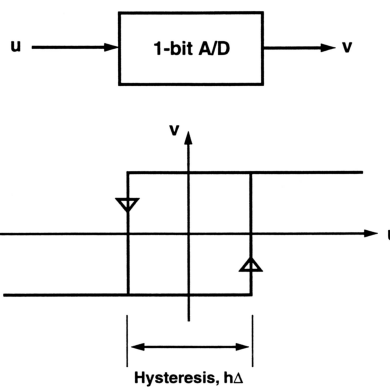
## 2<sup>nd</sup> Order $\Sigma\Delta$ Comparator Hysteresis



Hysteresis=  
Minimum overdrive  
required to change  
the output
 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Comparator Hysteresis




- Comparator hysteresis  $< \Delta/40$  does not affect SNR
- E.g.  $\Delta=1V$ , comparator hysteresis up to 25mV tolerable

## Design Phase Simulations


- Design of oversampled ADCs requires simulation of extremely long data traces
- SPICE type simulators normally used to test for gross circuit errors only
- SPICE type simulators too slow and not accurate enough for performance verification
- Typically, behavioral modeling is used in MATLAB-like environments
- Circuit non-idealities either computed or found by using SPICE at subcircuit level
- Non-idealities introduced in the behavioral model one-by-one first to fully understand the effect of each individually
- Next step is to add as many of the non-idealities as possible simultaneously to verify whether there are interaction among non-idealities
 
# Modulator Testing

- Should make provisions for testing the modulator (AFE) separate from the decimator (digital back-end)
- Data acquisition board used to collect 1-bit digital output at  $f_s$  rate
- Analyze data in a PC or dedicated test equipment in manufacturing environments can be used
- Need run DFT on the data and also make provisions to perform the function of digital decimation filter in software
- Typically, at this stage, parts of the design phase behavioral modeling effort can be utilized
- Good testing strategy vital for debugging/improving challenging designs


 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Implementation Example: Digital Audio Application



- 5V supply,  $\Delta=4V_{p-p-d}$
- Minimum capacitor values computed based on noise -107dB wrt maximum signal
- Max. inband  $KT/C$  noise =  $7mV_{rms}$
- $C1=(2kT)/(M v_n^2)=1pF$      $C2=2C1$

Ref: B. P. Brandt, D. E. Wingard, and B. A. Wooley, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.

## 2<sup>nd</sup> Order $\Sigma\Delta$ Implementation Example: Digital Audio Applications


### Summary of Measured Performance

<b>Dynamic Range</b>	<b>98 dB (16 bits)</b>
<b>Peak SNDR</b>	<b>94 dB (0.002% THD)</b>
<b>Nyquist rate</b>	<b>50 kHz</b>
<b>Sampling rate</b>	<b>12.8 MHz</b>
<b>Oversampling Ratio</b>	<b>256</b>
<b>Differential input range</b>	<b>4 V</b>
<b>Supply voltage</b>	<b>5 V</b>
<b>Supply rejection</b>	<b>60 dB</b>
<b>Power dissipation</b>	<b>13.8 mW</b>
<b>Active Area</b>	<b>0.39 mm<sup>2</sup></b>
<b>Technology</b>	<b>1-<math>\mu</math>m CMOS</b>

Ref: B. P. Brandt, D. E. Wingard, and B. A. Wooley, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.

## 2<sup>nd</sup> Order $\Sigma\Delta$ Implementation Example: Digital Audio Applications


### Measured SNDR

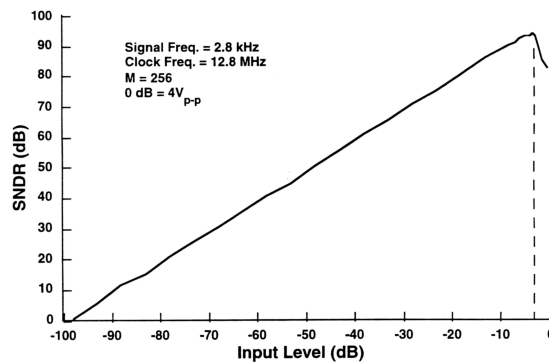

Ref: B. P. Brandt, D. E. Wingard, and B. A. Wooley, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.



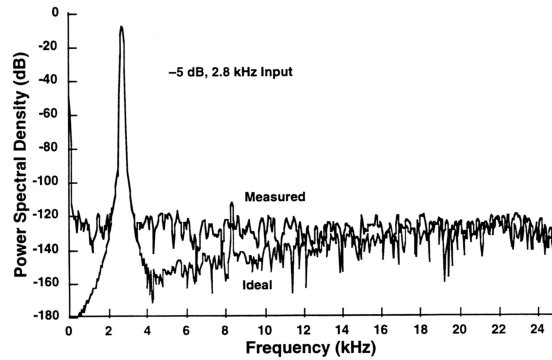
## 2<sup>nd</sup> Order $\Sigma\Delta$ Implementation Example: Digital Audio Applications



Ref: B. P. Brandt, D. E. Wingard, and B. A. Wooley, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.

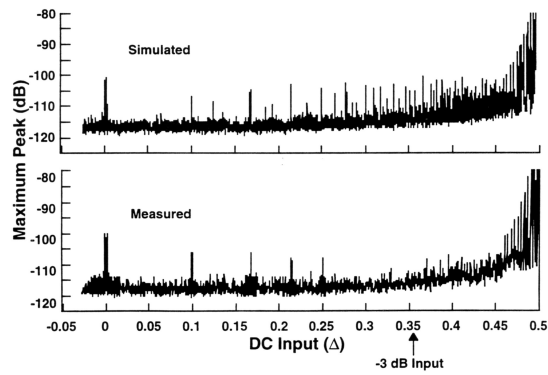
## 2<sup>nd</sup> Order $\Sigma\Delta$ Implementation Example: Digital Audio Applications



→ Measured & simulated noise tone performance as a function of DC input signal  
→ Sampling rate=12.8MHz, M=256

Ref: B. P. Brandt, D. E. Wingard, and B. A. Wooley, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.

 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Implementation Example: Digital Audio Applications



- Measured & simulated noise tone performance for near zero DC input
- Sampling rate=12.8MHz, M=256

Ref: B. P. Brandt, D. E. Wingard, and B. A. Wooley, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.
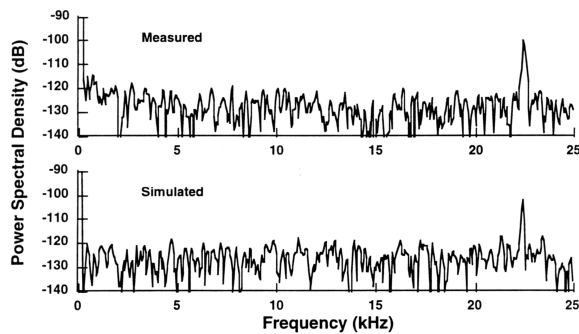
## 2<sup>nd</sup> Order $\Sigma\Delta$ Implementation Example: Digital Audio Applications



- Measured & simulated worst-case noise tone @ DC input of 0.00088Δ
- Sampling rate=12.8MHz, M=256

Ref: B. P. Brandt, D. E. Wingard, and B. A. Wooley, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.

## 2<sup>nd</sup> Order $\Sigma\Delta$ Implementation Example: Integrator Opamp

- Class A/B opamp + S.C. common-mode feedback  
→ high slew-rate


- Input referred noise (both thermal and 1/f) should be much smaller compared to in-band quantization noise

- Minimum required DC gain  $M=256$ , usually DC gain designed to be much higher to suppress nonlinearities

- Minimum required slew rate of  $1.2(\Delta fs) \rightarrow 65V/\mu\text{sec}$

- Minimum opamp settling time constant  $\rightarrow 1/2fs \sim 30\text{nsec}$

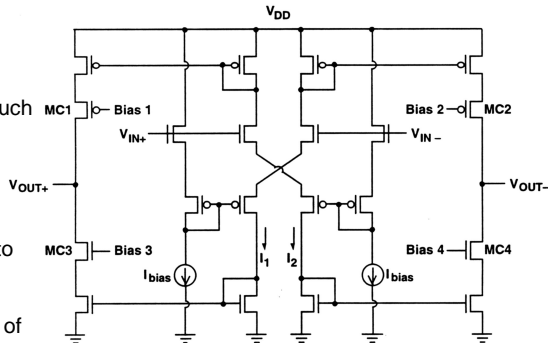
Ref: B. P. Brandt, D. E. Wingard, and B. A. Wooley, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.


 
## 2<sup>nd</sup> Order $\Sigma\Delta$ Implementation Example: Comparator

- Comparator  $\rightarrow$  simple design

- Minimum acceptable hysteresis or offset  $\rightarrow \Delta/40 \sim 100\text{mV}$



Ref: B. P. Brandt, D. E. Wingard, and B. A. Wooley, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.

## 2<sup>nd</sup> Order $\Sigma\Delta$ Implementation Example: Subcircuit Performance


Subcircuit Performance		<u>Our computed</u> <u>minimum required</u>	<u>Over-Design Factor</u>
<b>Operational Amplifier</b>			
DC gain	<b>67 dB</b>	DC Gain 48dB	x8
Unity-gain frequency	<b>50 MHz</b>	Unity-gain freq =2fs=25MHz	x2
Slew rate	<b>350 V/<math>\mu</math>sec</b>	Slew rate = 65V/usec	x5
Linear output range	<b>6 V</b>	Output range 1.7 $\Delta$ =6.8V!	X0.9
Sampling rate	<b>12.8 MHz</b>		
<b>Integrator</b>			
Settling time constant	<b>7.25 nsec</b>	Settling time constant= 30nsec	x4
<b>Comparator</b>			
Offset	<b>13 mV</b>	Comparator offset 100mV	x7

Ref: B. P. Brandt, D. E. Wingard, and B. A. Wooley, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.

## Higher Order $\Sigma\Delta$ Modulators

- Two different architectural approaches used to implement  $\Sigma\Delta$  modulators of order  $>2$ 
  - Cascaded modulators (multi-stage)
  - Single-loop single-quantizer modulators with multi-order filtering in the forward path
 
## Higher Order $\Sigma\Delta$ Modulators Multi-Stage Filter



$$Y(z) = \frac{H(z)}{1+H(z)}X(z) + \frac{1}{1+H(z)}E(z)$$


$$NTF = \frac{Y(z)}{E(z)} = \frac{1}{1+H(z)}$$

- Zeros of NTF (poles of  $A(z)$ ) can be positioned to flatten baseband noise spectrum
- Main issue  $\rightarrow$  Loop stability for 3<sup>rd</sup> and higher orders

## Higher Order $\Sigma\Delta$ Modulators Cascaded Modulators


- Cascade two or more stable SD stages
- Quantization error of each stage is quantized by the succeeding stage and subtracted digitally
- Order of noise shaping equals sum of the orders of the stages
- Quantization noise cancellation depends on the precision of analog signal paths
- Typically, no potential instability
 
## 2-Stage Cascaded $\Sigma\Delta$ Modulators



- Main  $\Sigma\Delta$  quantizes the signal
- The quantization error is then quantized by the 2<sup>nd</sup> quantizer
- The quantized error is then subtracted from the results in the digital domain
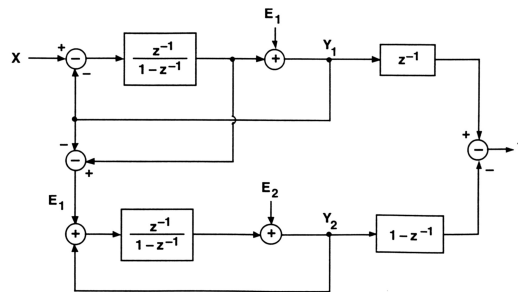
## 2<sup>nd</sup> Order (1-1) Cascaded $\Sigma\Delta$ Modulators



$$Y_1(z) = z^{-1}X(z) + (1 - z^{-1})E_1(z)$$

$$Y_2(z) = z^{-1}E_1(z) + (1 - z^{-1})E_2(z)$$


$$Y(z) = z^{-1}Y_1(z) - (1 - z^{-1})Y_2(z)$$

$$= z^{-2}X(z) + z^{-1}(1 - z^{-1})E_1(z) - z^{-1}(1 - z^{-1})E_1(z) - (1 - z^{-1})^2E_2(z)$$

$$Y(z) = z^{-2}X(z) - (1 - z^{-1})^2E_2(z) \quad \leftarrow \text{2<sup>nd</sup> order noise shaping}$$
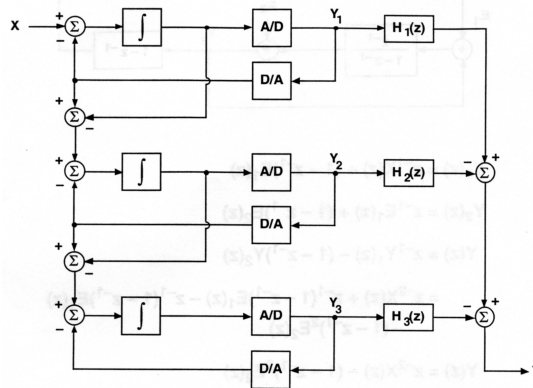
### 3<sup>rd</sup> Order Cascaded $\Sigma\Delta$ Modulators


- Can implement 3<sup>rd</sup> order noise shaping with 1-1-1
- This is also called MASH


 
### 3rd Order (2-1) Cascaded $\Sigma\Delta$ Modulators

Advantages of 2-1 cascade:

- Low sensitivity to precision of analog paths
- Low spurious noise tones
- No potential instability



$$Y_1(z) = z^{-2}X(z) + (1 - z^{-1})^2E_1(z)$$

$$Y_2(z) = z^{-1}E_1(z) + (1 - z^{-1})E_2(z)$$


$$Y(z) = z^{-1}Y_1(z) - (1 - z^{-1})^2Y_2(z)$$

$$= z^{-3}X(z) + z^{-1}(1 - z^{-1})^2E_1(z) - z^{-1}(1 - z^{-1})^2E_1(z) - (1 - z^{-1})^3E_2(z)$$


3rd order noise shaping  $\implies$

$$Y(z) = z^{-3}X(z) - (1 - z^{-1})^3E_2(z)$$
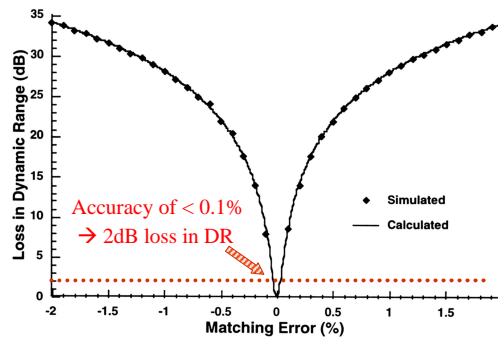
### Sensitivity of (1-1-1) Cascaded $\Sigma\Delta$ Modulators to Matching of Analog & Digital Gains


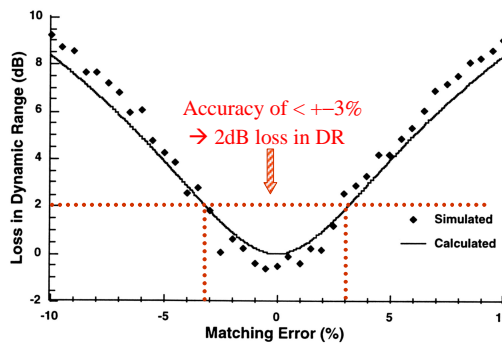
### Sensitivity of (2-1) Cascaded $\Sigma\Delta$ Modulators to Matching Error




Main advantage of 2-1 cascade compared to 1-1-1 topology:

- Low sensitivity to precision of analog paths (over one order of magnitude!)



 
## 2-1 Cascaded $\Sigma\Delta$ Modulators



Ref: L. A. Williams III and B. A. Wooley, "A third-order sigma-delta modulator with extended dynamic range," *IEEE Journal of Solid-State Circuits*, vol. 29, pp. 193 - 202, March 1994.
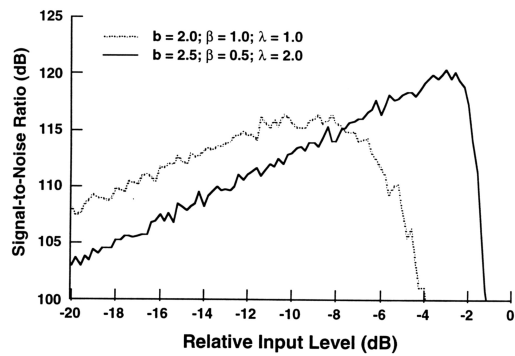
## 2-1 Cascaded $\Sigma\Delta$ Modulators




Effect of gain parameters on signal-to-noise ratio

## Comparison of 2<sup>nd</sup> order & Cascaded (2-1) $\Sigma\Delta$ Modulator

Digital Audio Application, $F_N=50\text{kHz}$		
Reference	Brandt, JSSC 4/91	Williams, JSSC 3/94
Architecture	2 <sup>nd</sup> order	(2+1) Order
Dynamic Range	98dB (16-bits)	104dB (17-bits)
Peak SNDR	94dB	98dB
Oversampling rate	256	128
Differential input range	4Vppd 5V supply	8Vppd 5V supply
Power Dissipation	13.8mW	47.2mW
Active Area	0.39mm <sup>2</sup>	5.2mm <sup>2</sup>
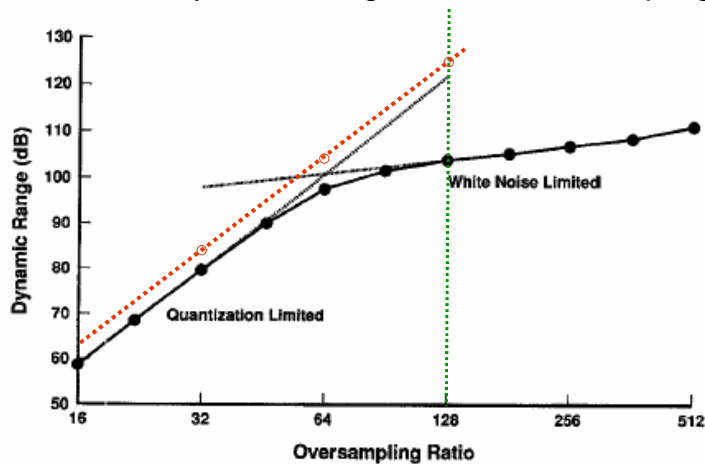
## 2-1 Cascaded $\Sigma\Delta$ Modulators Measured Dynamic Range Versus Oversampling Ratio



Ref: L. A. Williams III and B. A. Wooley, "A third-order sigma-delta modulator with extended dynamic range," *IEEE Journal of Solid-State Circuits*, vol. 29, pp. 193 - 202, March 1994.

# Summary

- Oversampled ADCs decouple SQNR from circuit complexity and accuracy
- If a 1-Bit DAC is used, the converter is inherently linear—independent of component matching
- Typically, used for high resolution & low frequency applications – e.g. digital audio
- 2<sup>nd</sup> order  $\Sigma\Delta$  used extensively due to lower levels of limit cycle related spurious tones
- $\Sigma\Delta$  modulators of order greater than 2:
  - Single-loop, single-quantizer modulators with multi-order filtering in the forward path
  - Cascaded (multi-stage) modulators

Refs:

J. C. Candy and G. C. Temes, "Oversampling Methods for A/D and D/A Conversion", Oversampling Delta-Sigma Data Converters: Theory, Design, and Simulation, 1992, pp. 1-25.

S. R. Norsworthy, R. Schreier, and G. C. Temes, "Delta-Sigma Data Converters, Theory, Design, and Simulation," IEEE Press, 1997.