

EE247

Lecture 7


- Summary last lecture
- Continuous-time filters
 - Bandpass filters
 - Example Gm-C BP filter using simple diff. pair
 - Linearity
 - Noise
 - Various Gm-C Filter implementations
 - Comparison of continuous-time filter topologies

Summary last lecture

- Automatic on-chip filter tuning
 - Continuous tuning
 - Master-slave tuning
 - Periodic off-line tuning
 - Systems where filter is followed by ADC & DSP, existing hardware can be used to periodically update filter freq. response


Master-Slave Frequency Tuning Reference Voltage-Controlled-Oscillator (VCO)

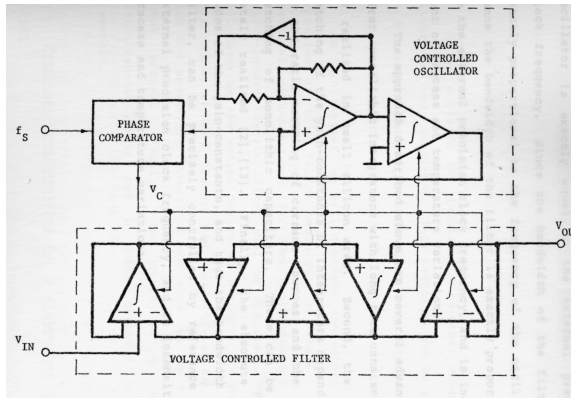- Instead of VCF a voltage-controlled-oscillator (VCO) is used
- VCO made or replica integrators
- Tuning circuit operates exactly as a conventional phase-locked loop (PLL)
- Tuning signal used to tune main filter




Ref: K.S. Tan and P.R. Gray, "Fully integrated analog filters using bipolar FET technology," IEEE, J. Solid-State Circuits, vol. SC-13, no.6, pp. 814-821, December 1978..

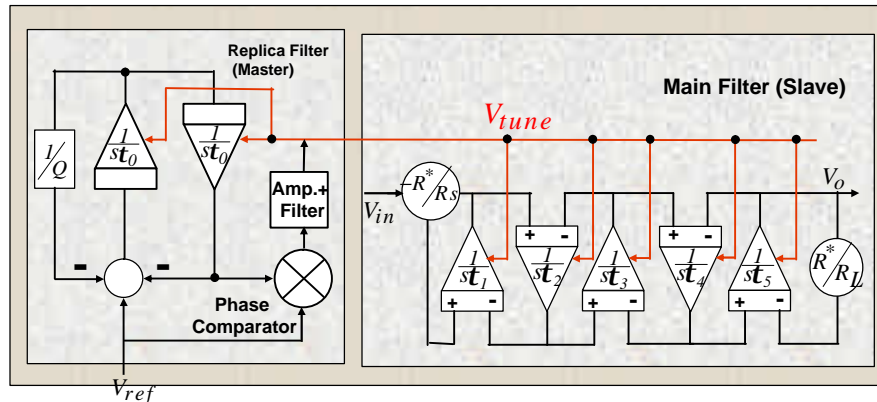Master-Slave Frequency Tuning Reference Filter (VCF)




Ref: H. Khorrabadi and P.R. Gray, "High Frequency CMOS continuous-time filters," IEEE Journal of Solid-State Circuits, Vol.-SC-19, No. 6, pp.939-948, Dec. 1984.


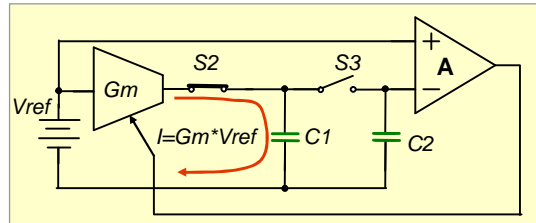
Reference C/Gm Locked to Ref. Frequency P2 high → S2 closed



Charge C1 with $I = Gm \times Vref$

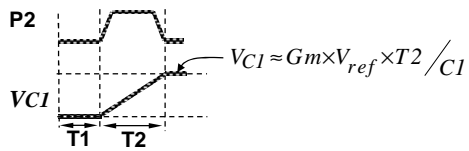

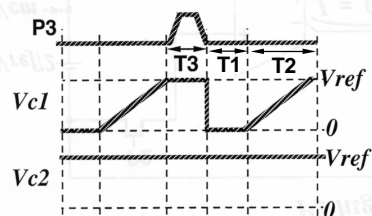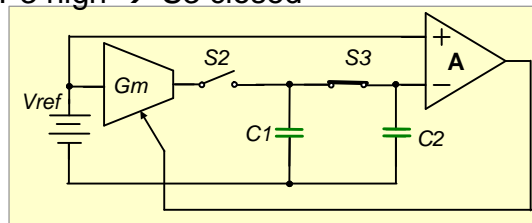Reference C/Gm Locked to Ref. Frequency P3 high → S3 closed



Charge on C1 shared with C2
Feedback forces Gm to assume a value:


$$V_{C1} = V_{C2} = V_{ref}$$

$$\text{since: } V_{C1} = Gm \times V_{ref} \times T2 / C1$$


$$\text{then: } V_{ref} = Gm \times V_{ref} \times T2 / C1$$

$$\text{or: } \boxed{C1 / Gm = T2 = N / fclk}$$

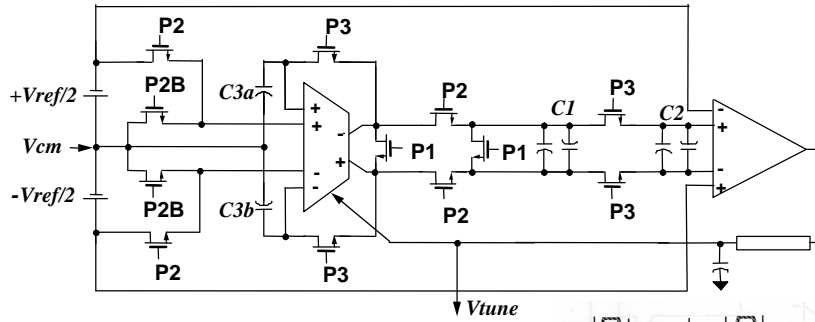Reference C/Gm Locked to Ref. Frequency Incorporating Offset Cancellation



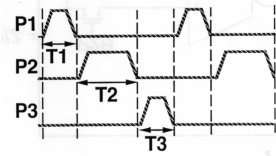Gm-cell → two sets of input pairs
Aux. input pair + C3a,b → Offset cancellation
Same clock timing




DC Tuning of Resistive Timing Element

R_{ext} used to lock Gm or on-chip R


Feedback forces $G_m = I/R_{ext}$

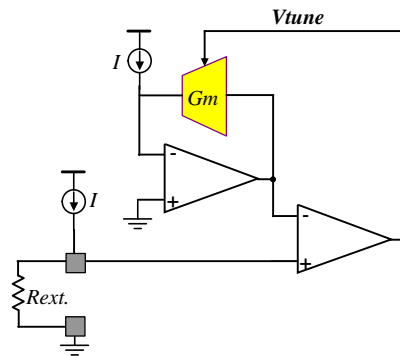Account for Cap. variations in the gm-C implementation by trimming




Ref: C. Laber and Gray, "A 20MHz 6th Order BiCOM Parasitic Insensitive Continuous-time Filter and Second Order Equalizer Optimized for Disk Drive Read Channels," *IEEE Journal of Solid State Circuits*, Vol. 28, pp. 462-470, April 1993

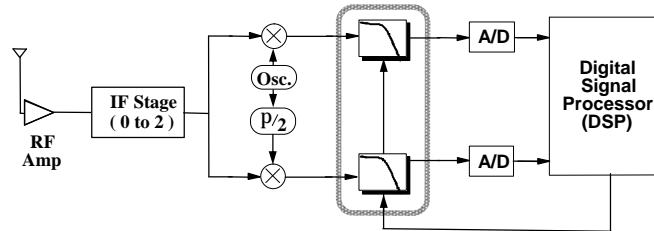Off-line Frequency Tuning Example: Wireless Receiver Baseband Filters



- Systems where filter is followed by ADC & DSP
 - Take advantage of existing digital signal processor to periodically update the filter critical frequency
 - Filter tuned only at the outset of each data transmission session (off-line tuning)

Offline Filter Tuning Concept

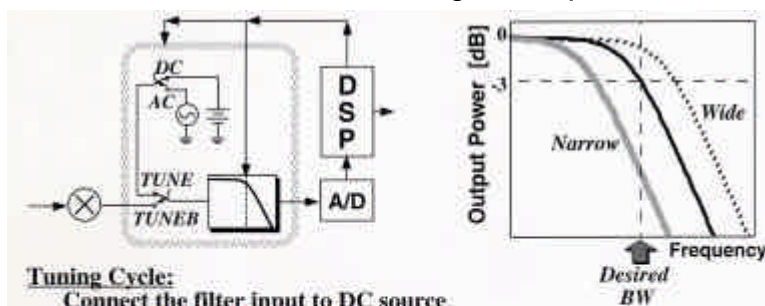

Tuning Cycle:

Connect the filter input to DC source
 DSP measures the DC power level
 Connect the filter input to AC source (freq. \rightarrow desired -3dB freq.)
 DSP measures the AC signal power level
 If $DC = 4 * AC$

Then filter is tuned

Else If $DC > 4 * AC$

Then widen the filter bandwidth & repeat



Else narrow the filter bandwidth & repeat

Summary Filter Frequency Tuning


- Trimming
 - Expensive
 - Does not account for variations associated with temperature and supply etc...
- Automatic frequency tuning
 - Continuous tuning
 - Master VCF used in tuning loop
 - Tuning quite accurate
 - Issue → reference signal feedthrough to the filter output
 - Master VCO used in tuning loop
 - Design of reliable & stable VCO challenging
 - Issue → reference signal feedthrough
 - Single integrator in negative feedback loop forces time-constant to be a function of accurate clock frequency
 - More flexibility in choice of reference frequency → less feedthrough issues
 - Locking a replica of the Gm-cell to an external resistor
 - DC offset issues
 - Does not account for integrating capacitor variations
 - Periodic tuning
 - Requires digital capability + minimal additional hardware
 - Advantage of no reference signal feedthrough since tuning performed off-line

Bandpass Filters

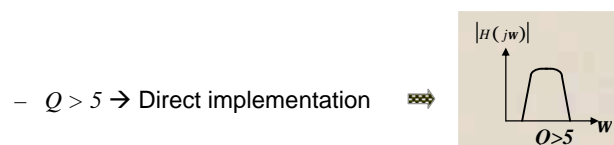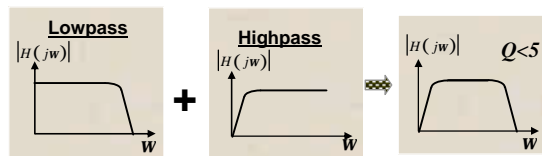- Bandpass Filters:
 - $Q < 5 \rightarrow$ Combination of lowpass & highpass



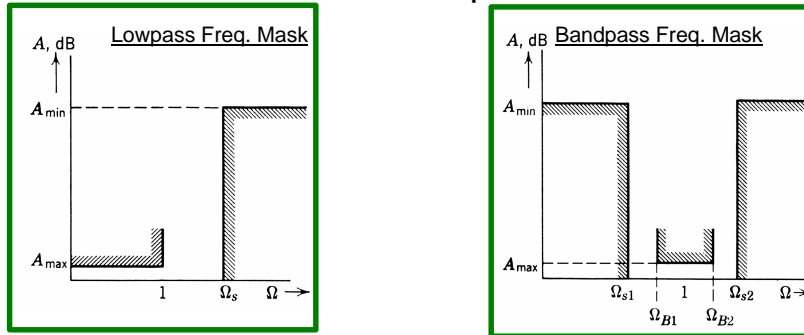
Direct Implementation Narrow Band Bandpass Filters



$$s \Rightarrow = Q \times \left[\frac{s + W_C}{W_C} + \frac{W_C}{s} \right] \quad \frac{\Omega_S}{\Omega_C} = \frac{\Omega_{S2} - \Omega_{S1}}{\Omega_{B2} - \Omega_{B1}}$$

- Design based on lowpass prototype for narrow band filters
- Same lowpass tables used

Lowpass to Bandpass Transformation

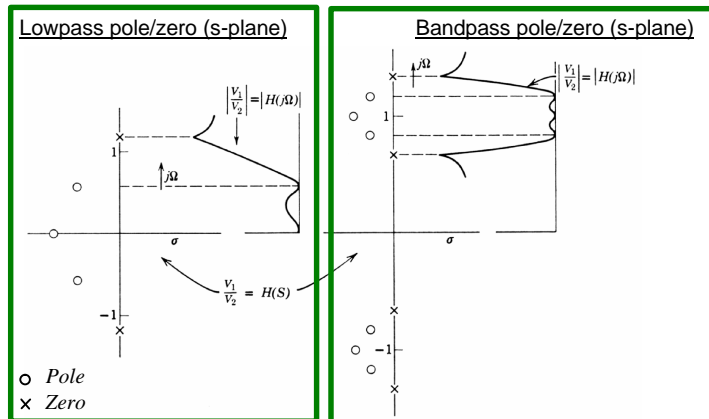

From: Zverev, *Handbook of filter synthesis*, Wiley, 1967- p.156.

Lowpass to Bandpass Transformation Table

$$a = (\Omega_{B2} - \Omega_{B1})^{-1}$$


$$a = Q_{filter}$$

From:
Zverev,
Handbook of filter synthesis,
Wiley, 1967- p.157.

LP	BP Schematic	BP Values
		$C = aC' \frac{1}{R_r \omega_r}$ $L = \frac{1}{aC'} \frac{R_r}{\omega_r}$
		$L = aL' \frac{R_r}{\omega_r}$ $C = \frac{1}{aL'} \frac{1}{R_r \omega_r}$ <i>L, C are unnormalized BP values</i>
		$c_+ = \frac{1}{L} = aC'(1 + \Omega_s^2)$ $c_- = \frac{1}{L} = aC'(1 + \Omega_s^2)$ $l_+ = \frac{1}{C} = aL'(1 + \Omega_s^2)$ $l_- = \frac{1}{C} = aL'(1 + \Omega_s^2)$ where $\Omega_s = \sqrt{1 + \left(\frac{\Omega_s}{2a}\right)^2} \pm \frac{\Omega_s}{2a}$ $L_+ + L_- = \frac{1}{aC'}$ <i>c₊, l₊, c₋, and l₋ are normalized BP values</i>

C and L' are normalized LP values

Lowpass to Bandpass Transformation

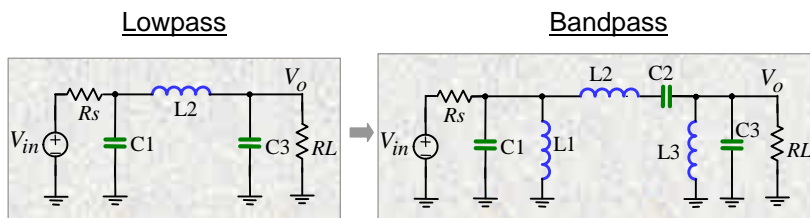

- Each capacitor replaced by parallel L & C
- Each inductor replaced by series L & C

Lowpass to Bandpass Transformation

$$C_1 = QC_1' \times \frac{1}{Rw_0}$$


$$L_1 = \frac{1}{QC_1'} \times \frac{R}{w_0}$$

$$C_2 = \frac{1}{QL_2'} \times \frac{1}{Rw_0}$$

$$L_2 = QL_2' \times \frac{R}{w_0}$$

$$C_3 = QC_3' \times \frac{1}{Rw_0}$$
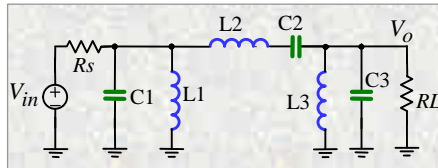
$$L_3 = \frac{1}{QC_3'} \times \frac{R}{w_0}$$





Where:

C_1' , L_2' , C_3' , \rightarrow normalized lowpass values

$Q \rightarrow$ bandpass filter quality factor &

$w_0 \rightarrow$ filter center frequency

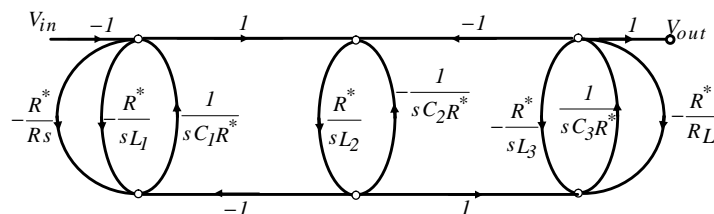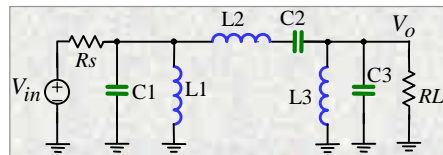Signal Flowgraph 6th Order Bandpass Filter




Note each C & L in the original lowpass prototype \rightarrow replaced by a resonator

Substituting the bandpass L1, C1,..... by their normalized lowpass equivalent previous page


The resulting SFG is:

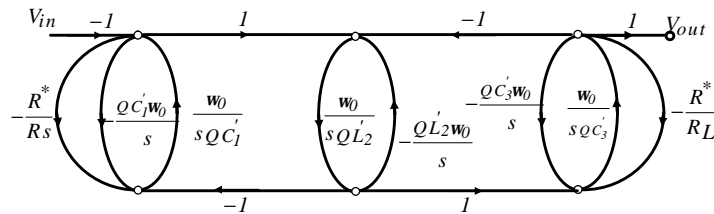Signal Flowgraph 6th Order Bandpass Filter




- Note the integrators have different time constants
 - Ratio of time constants for each resonator $\sim 1/Q^2$
 - typically, requires high component ratios
 - poor matching
- Desirable to convert SFG so that all integrators have equal time constants for optimum matching.
 - Scale nodes to obtain equal integrator time constant

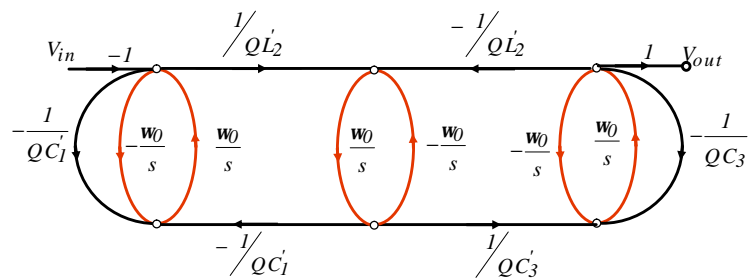Signal Flowgraph 6th Order Bandpass Filter



- Note: Three resonators
- All integrator time-constants are equal
- Let us try to build this bandpass filter using the simple Gm-C structure

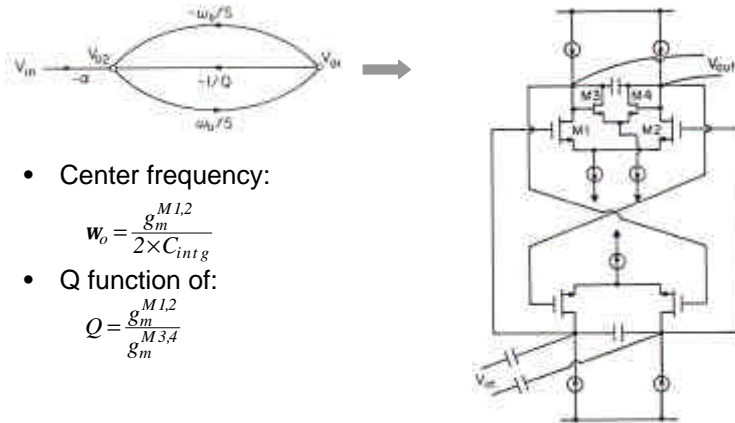Second Order Gm-C Filter Using Simple Source-Couple Pair Gm-Cell



- Center frequency:


$$\omega_0 = \frac{g_m^{M1,2}}{2 \times C_{int} g}$$

- Q function of:

$$Q = \frac{g_m^{M1,2}}{g_m^{M3,4}}$$

To use this structure it is easier to couple resonators through capacitive coupling

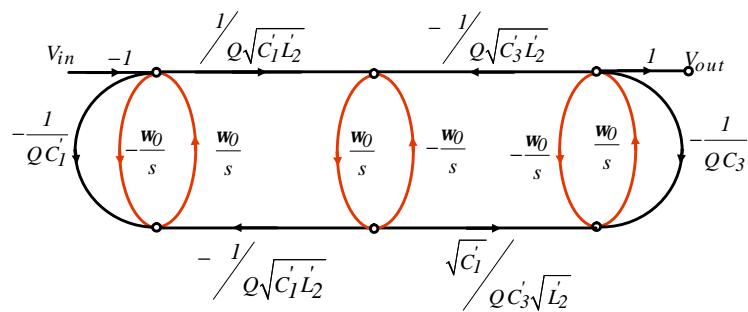
Signal Flowgraph 6th Order Bandpass Filter



Modified signal flowgraph to have equal coupling between resonators

- In most filter cases $C_1' = C_3'$
- Example: For a butterworth lowpass filter $C_1' = C_3' = 1$ & $L_2' = 2$
- Assume overall bandpass filter $Q=10$

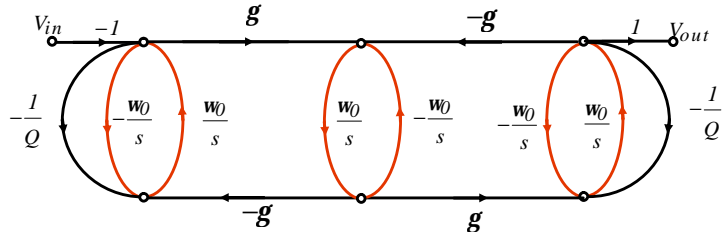Sixth Order Bandpass Filter Signal Flowgraph




•Where for a Butterworth shape $g = \frac{1}{Q\sqrt{2}}$

•Since $Q=10$ then: $g \approx \frac{1}{14}$

Sixth Order Bandpass Filter Signal Flowgraph

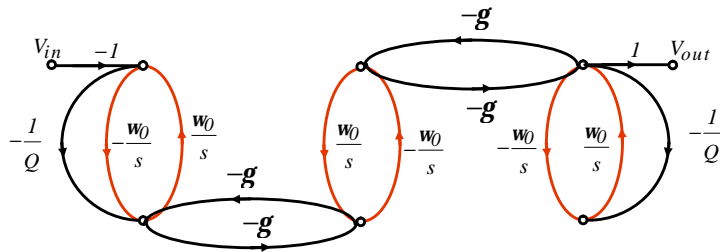For narrow band filters (high Q) where frequencies within the passband are close to ω_0 narrow-band approximation can be used:
The resulting SFG:




Sixth Order Gm-C Bandpass Filter Utilizing Simple Source-Coupled Pair Gm-Cell

$$g = \frac{C_k}{2 \times C_{int} g}$$


$$g = 1/14$$

$$\rightarrow C_k = \frac{I}{7 \times C_{int} g}$$

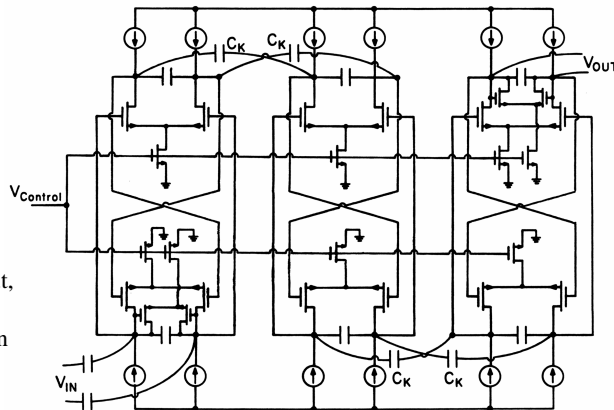Parasitic C at
integrator output,
if unaccounted
for, will result in
inaccuracy in g



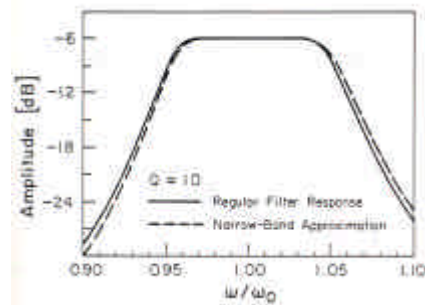Sixth Order Gm-C Bandpass Filter Frequency Response Simulation




Simplest Form of CMOS Gm-Cell Nonidealities

- DC gain (integrator Q)

$$a = \frac{g_m^{M1,2}}{g_0^{M1,2} + g_{load}}$$
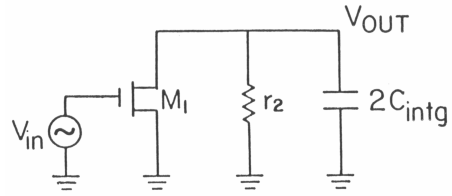
$$a = \frac{2L}{q(V_{gs} - V_{th})_{M1,2}}$$



Small Signal Differential Mode Half-Circuit


- Where θ is related to channel length modulation by:

$$I = \frac{q}{L}$$

- Seems no extra poles!

CMOS Gm-Cell High-Frequency Poles

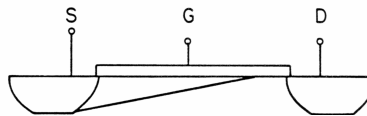Cross section view of a MOS transistor operating in saturation



Distributed channel resistance & gate capacitance


- Distributed nature of gate capacitance & channel resistance results in infinite no. of high-frequency poles

CMOS Gm-Cell High-Frequency Poles

$$P_2^{effective} = \frac{1}{\sum_{i=2}^{\infty} \frac{1}{P_i}}$$

$$P_2^{effective} \approx 2.5 w_t^{M1,2}$$
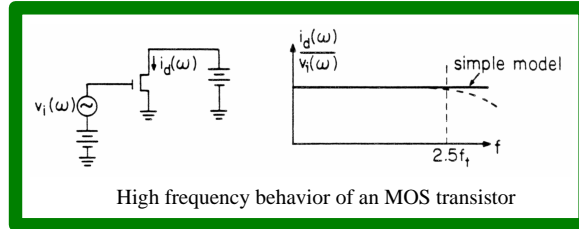
$$w_t^{M1,2} = \frac{g_m^{M1,2}}{C_{ox}WL} = \frac{3}{2} \frac{m(V_{gs} - V_{th})_{M1,2}}{L^2}$$



- Distributed nature of gate capacitance & channel resistance results in an effective pole at 2.5 times input device cut-off frequency

CMOS Gm-Cell Quality Factor

$$a = \frac{2L}{q(V_{gs} - V_{th})_{M1,2}}$$

$$P_2^{effective} = \frac{15}{4} \frac{m(V_{gs} - V_{th})_{M1,2}}{L^2}$$


$$Q_{real}^{intg.} \approx \frac{1}{\frac{1}{a} - w_0 \sum_{i=2}^{\infty} \frac{1}{P_i}}$$

$$\frac{1}{Q_{real}^{intg.}} \approx \frac{q(V_{gs} - V_{th})_{M1,2}}{2L} - \frac{4}{15} \frac{w_0 L^2}{m(V_{gs} - V_{th})_{M1,2}}$$

- Note that the phase lead associated with DC gain is inversely prop. to L
 - The phase lag due to high-freq. poles directly prop. to L
- For a given ω_0 there exists an optimum L which cancel the lead/lag phase error resulting in high integrator Q



CMOS Gm Cell Channel Length for Optimum Quality Factor
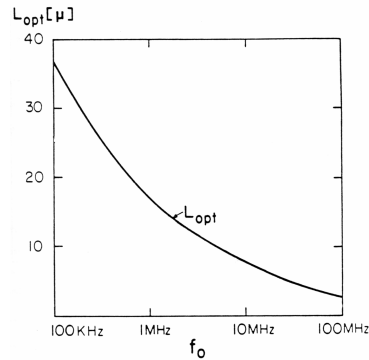
$$L_{opt} \approx \left[\frac{15}{4} \frac{qm(V_{gs} - V_{th})^2 M_{1,2}}{w_o} \right]^{1/3}$$




- Optimum channel length computed based on process parameters

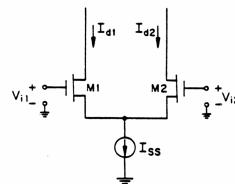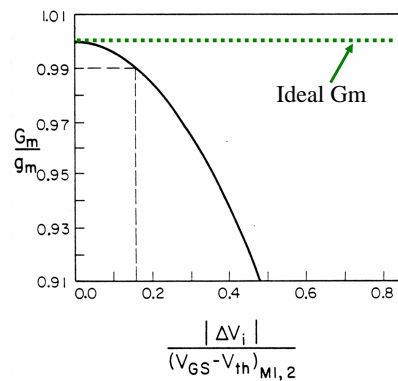Linearity of the Source-Coupled Pair CMOS Gm-Cell



- Large signal Gm drops as input voltage increases
→ Gives rise to filter nonlinearity

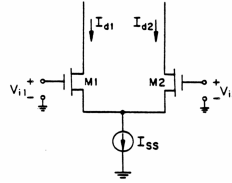Source-Coupled Pair CMOS Gm-Cell Linearity




$$\Delta I_d = I_{ss} \left[\frac{\Delta v_i}{(V_{gs} - V_{th})_{M1,2}} \right] \left\{ 1 - \frac{1}{4} \left[\frac{\Delta v_i}{(V_{gs} - V_{th})_{M1,2}} \right]^2 \right\}^{1/2} \quad (1)$$

$$\Delta I_d = a_1 \times \Delta v_i + a_2 \times \Delta v_i^2 + a_3 \times \Delta v_i^3 + \dots$$

Series expansion used in (1)

Measure of Linearity
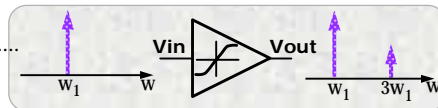
$$V_{out} = a_1 V_{in} + a_2 V_{in}^2 + a_3 V_{in}^3 + \dots$$



$$HD3 = \frac{\text{amplitude 3rd harmonic dist. comp.}}{\text{amplitude fundamental}}$$

$$= \frac{1}{4} \frac{a_3}{a_1} V_{in}^2 + \dots$$

$$IM_3 = \frac{\text{amplitude 3rd order IM comp.}}{\text{amplitude fundamental}}$$

$$= \frac{3}{4} \frac{a_3}{a_1} V_{in}^2 + \frac{25}{8} \frac{a_5}{a_1} V_{in}^4 + \dots$$




Linearity of the Source-Coupled Pair CMOS Gm-Cell

$$a_1 = \frac{I_{SS}}{(V_{GS} - V_{th})} \quad a_2 = 0$$

$$a_3 = -\frac{I_{SS}}{8(V_{GS} - V_{th})^3} \quad a_4 = 0$$
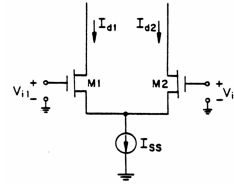
$$a_5 = -\frac{I_{SS}}{128(V_{GS} - V_{th})^5} \quad a_6 = 0$$



$$IM_3 \approx \frac{3}{4} \frac{a_3}{a_1} \hat{v}_i^2 + \frac{25}{8} \frac{a_5}{a_1} \hat{v}_i^4 + \dots$$

$$\hat{v}_{i \max} \approx 4(V_{GS} - V_{th}) \left[\frac{2}{3} IM_3 \right]^{1/2}$$

$$IM_3 = 1\% \text{ \& } (V_{GS} - V_{th}) = 1V \Rightarrow \hat{V}_{in}^{rms} \approx 230mV$$

- Key point: Max. signal handling capability function of gate-overdrive

Simplest Form of CMOS Gm Cell Disadvantages

- Max. signal handling capability function of gate-overdrive


$$IM_3 \propto (V_{GS} - V_{th})^{-2}$$

- Critical freq. function of gate-overdrive too

$$w_o = \frac{g_m^{M1,2}}{2 \times C_{intg}}$$

$$\text{since } g_m = \mu C_{ox} \frac{W}{L} (V_{gs} - V_{th})$$

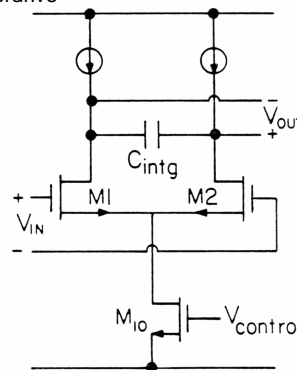
$$\text{then } w_o \propto (V_{gs} - V_{th})$$



→ Filter tuning affects max. signal handling capability!

Simplest Form of CMOS Gm Cell Removing Dependence of Maximum Signal Handling Capability on Tuning

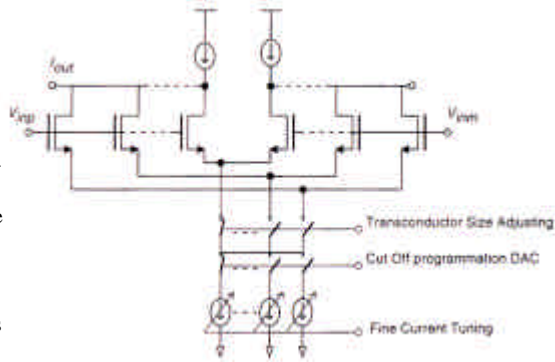- Can overcome problem of max. signal handling capability a function of tuning by providing tuning through :
 - Coarse tuning via switching in/out binary-weighted cross-coupled pairs → Try to keep gate overdrive voltage constant
 - Fine tuning through varying current sources



→ Dynamic range dependence on tuning removed (to 1st order)

Ref: R.Castello, I.Bietti, F. Svelto, "High-Frequency Analog Filters in Deep Submicron Technology", *International Solid State Circuits Conference*, pp 74-75, 1999.

Dynamic Range for Source-Coupled Pair Based Filter

$$IM_3 = 1\% \quad \& \quad (V_{GS} - V_{th}) = 1V \quad \Rightarrow \quad V_{in}^{rms} \approx 230mV$$

- It can be shown for the 6th order Butterworth bandpass filter noise is given by:


$$\sqrt{v_o^2} \approx \sqrt{3Q \frac{kT}{C_{intg}}}$$

Assuming $Q=10$ $C_{intg}=5pF$

$$v_{noise}^{rms} \approx 160mV$$

since $v_{max}^{rms} = 230mV$

Dynamic Range $\approx 63dB$

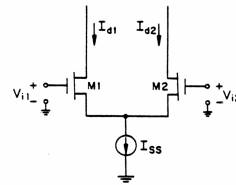


Improving the Max. Signal Handling Capability of the Source-Coupled Pair Gm-Cell



- 2nd source-coupled pair added to subtract current from the main SCP

$$\frac{I_{SS1}}{I_{SS3}} = b \text{ and } \frac{(V_{GS} - V_{th})_{M1,2}}{(V_{GS} - V_{th})_{M3,4}} = a \text{ and thus}$$
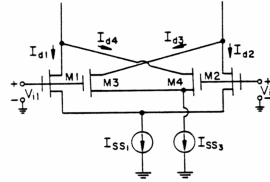
$$\left(\frac{W}{L}\right)_{M1,2} = \frac{b}{a^2} \left(\frac{W}{L}\right)_{M3,4}$$




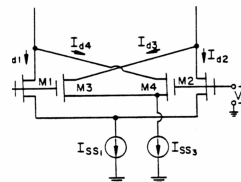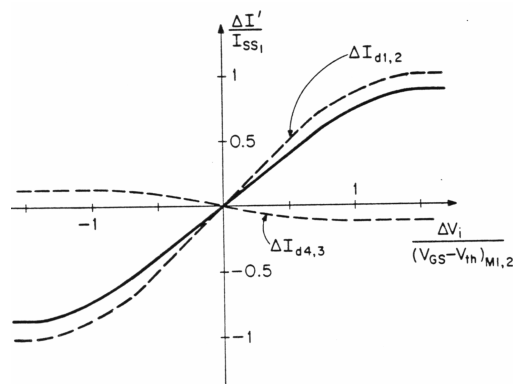Improving the Max. Signal Handling Capability of the Source-Coupled Pair Gm



Ref: H. Khorramabadi, "High-Frequency CMOS Continuous-Time Filters," U. C. Berkeley, Department of Electrical Engineering, Ph.D. Thesis, February 1985 (ERL Memorandum No. UCB/ERL M85/19).

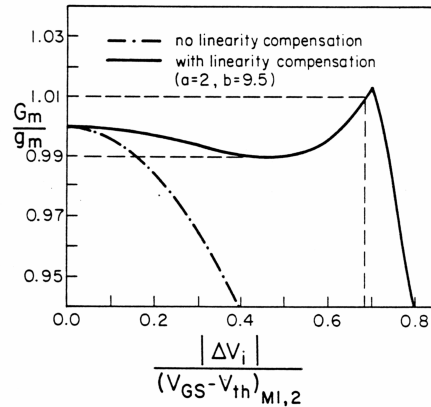
Improving the Max. Signal Handling Capability of the Source-Coupled Pair Gm



- Improves maximum signal handling capability by about 12dB
 -> Dynamic range theoretically improved to $63+12=75\text{dB}$

Simplest Form of CMOS Gm-Cell

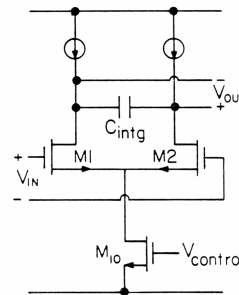- Pros
 - Capable of very high frequency performance (highest?)
 - Simple design
- Cons
 - Tuning affects power dissipation
 - Tuning affects max. signal handling capability (can overcome)
 - Limited linearity (possible to improve)



Ref: H. Khorramabadi and P.R. Gray, "High Frequency CMOS continuous-time filters," *IEEE Journal of Solid-State Circuits*, Vol.-SC-19, No. 6, pp.939-948, Dec. 1984.

BiCMOS Gm-Cell

- MOSFET in triode mode:

$$I_d = \frac{mC_{ox}W}{2L} [2(V_{gs} - V_{th})V_{ds} - V_{ds}^2]$$

- Note that if V_{ds} is kept constant:


$$g_m = \frac{\partial I_d}{\partial V_{gs}} = mC_{ox} \frac{W}{L} V_{ds}$$

- Linearity performance function of how constant V_{ds} can be held

- Gain @ Node X must be minimized

$$A_x = g_m^{M1} / g_m^{B1}$$

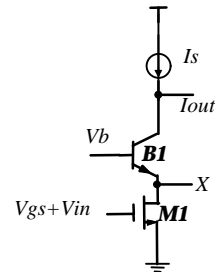
- Since for a given current, g_m of BJT is larger compared to MOS preferable to have BJT
- Extra pole at node X



g_m can be varied by changing V_b and thus V_{ds}


CMOS Alternative Gm-Cell

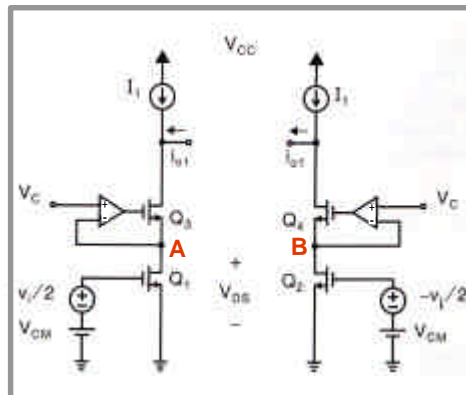- BJT replaced by a MOS transistor with boosted g_m
- Lower frequency of operation compared to the BiCMOS version due to more parasitic capacitance at node A & B




BiCMOS Gm-C Integrator

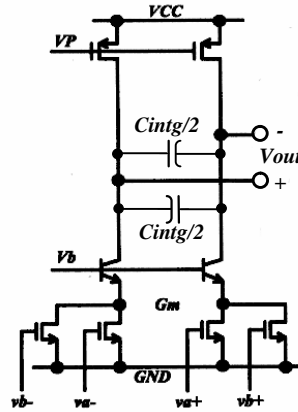- Differential- needs common-mode feedback ckt
- Freq. tuned by varying V_b
- Design tradeoffs:
 - Extra poles at the input device drain junctions
 - Input devices have to be small to minimize parasitic poles
 - Results in high input-referred offset voltage \rightarrow could drive ckt into non-linear region
 - Small devices \rightarrow high $1/f$ noise




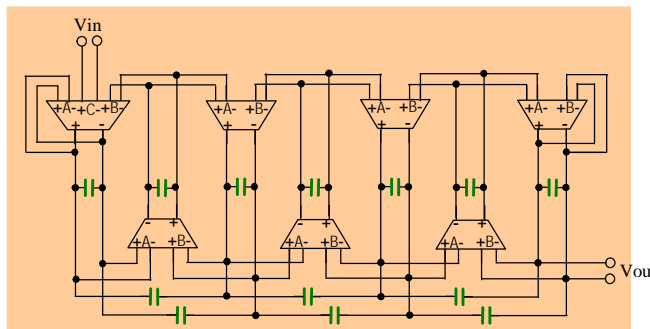
7th Order Elliptic Gm-C LPF For CDMA RX Baseband Application



- Gm-Cell in previous page used to build a 7th order elliptic filter for CDMA baseband applications (650kHz corner frequency)
- In-band dynamic range of <50dB achieved


Comparison of 7th Order Gm-C versus Opamp-RC LPF

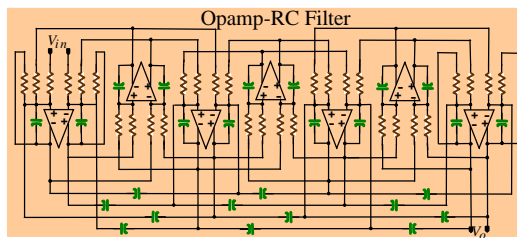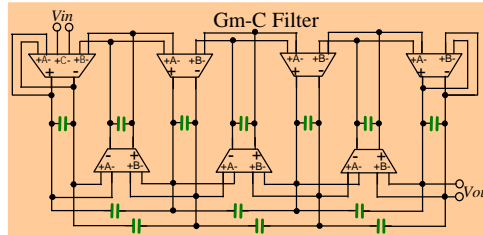- Gm-C filter requires 4 times less intg. cap. area compared to Opamp-RC
 → For low-noise applications where filter area is dominated by cap. area could make a significant difference in the total area
- Opamp-RC linearity superior compared to Gm-C
- Power dissipation tends to be lower for Gm-C since output is high impedance and thus no need for buffering




BiCMOS Gm-OTA-C Integrator

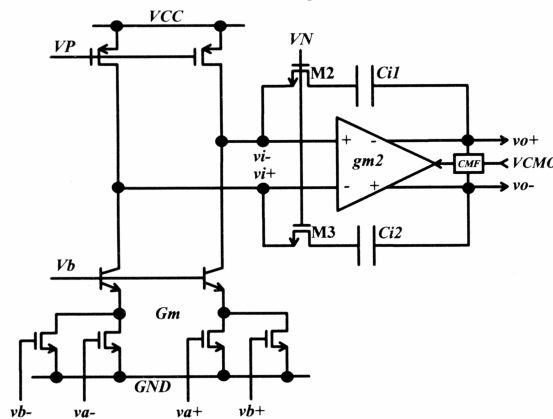- Used to build filter for disk-drive applications
- Since high frequency of operation, time-constant sensitivity to parasitic caps significant.
 → Opamp used
- M2 & M3 added to compensate for phase lag (provides phase lead)



Ref: C. Laber and P.Gray, "A 20MHz 6th Order BiCMOS Parasitic Insensitive Continuous-time Filter & Second Order Equalizer Optimized for Disk Drive Read Channels," *IEEE Journal of Solid State Circuits*, Vol. 28, pp. 462-470, April 1993.

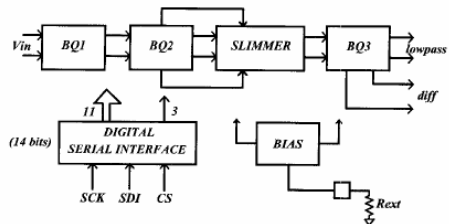
6th Order BiCMOS Continuous-time Filter & Second Order Equalizer for Disk Drive Read Channels



- Gm-C-opamp of the previous page used to build a 6th order filter for Disk Drive
- Filter consists of 3 Biquad with max. Q of 2 each
- Performance in the order of 40dB SNDR achieved for up to 20MHz corner frequency

Ref: C. Laber and P.Gray, "A 20MHz 6th Order BiCMOS Parasitic Insensitive Continuous-time Filter & Second Order Equalizer Optimized for Disk Drive Read Channels," *IEEE Journal of Solid State Circuits*, Vol. 28, pp. 462-470, April 1993.

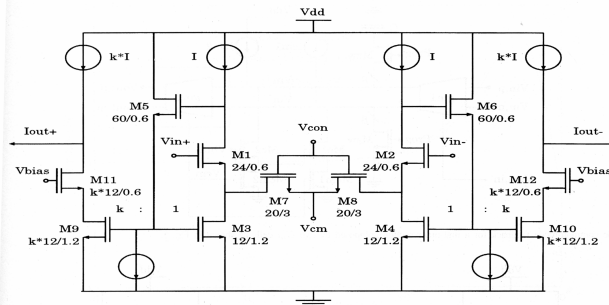
Gm-Cell Source-Coupled Pair with Degeneration



- Gm-cell intended for low Q disk drive filter

Ref: I.Mehr and D.R.Welland, "A CMOS Continuous-Time Gm-C Filter for PRML Read Channel Applications at 150 Mb/s and Beyond", *IEEE Journal of Solid-State Circuits*, April 1997, Vol.32, No.4, pp. 499-513.

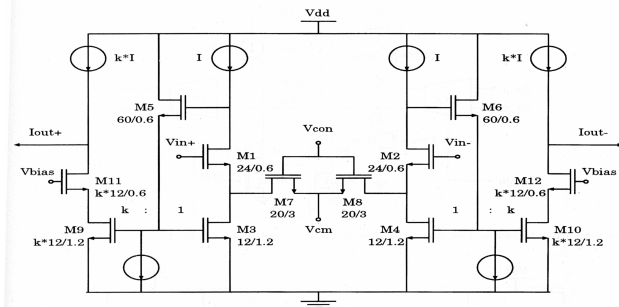
Gm-Cell Source-Coupled Pair with Degeneration



- M7,8 operating in triode mode determine the g_m of the cell
- Feedback provided by M5,6 maintains the gate-source voltage of M1,2 constant by forcing their current to be constant \rightarrow helps linearize r_{ds} of M7,8
- Current mirrored to the output via M9,10 with a factor of k
- Performance level of about 50dB SNDR at corner of 25MHz achieved


BiCMOS Gm-C Integrator

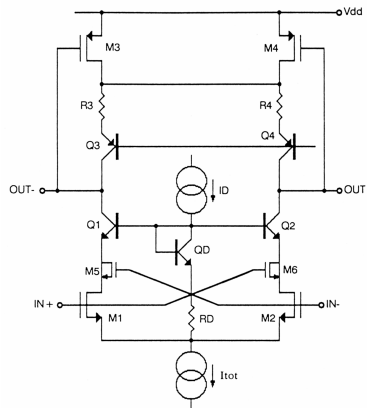- Needs higher supply voltage compared to the previous design
- M5 & M6 configured as capacitors added to compensate for RHP zero due to C_{gd} of M1 & M2 (moves it to LHP) size of M5-6 is 1/3 of M1-2
- Current I_D used to tune filter critical frequency
- M3, M4 operate in triode mode and added to provide CMFB



Ref: R. Alini, A. Baschiroto, and R. Castello, "Tunable BiCMOS Continuous-Time Filter for High-Frequency Applications," *IEEE Journal of Solid State Circuits*, Vol. 27, No. 12, pp. 1905-1915, Dec. 1992.

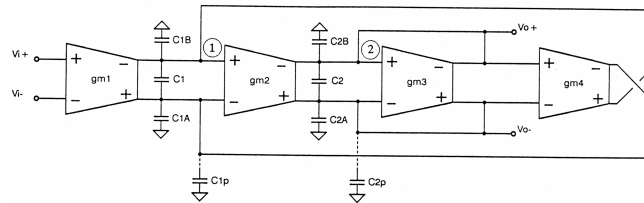BiCMOS Gm-C Filter For Disk-Drive Application



- Using the integrators shown in the previous page
- Biquad filter for disk drives
- $gm1 = gm2 = gm4 = 2gm3$
- $Q=2$
- Tunable from 8MHz to 32MHz

Ref: R. Alini, A. Baschiroto, and R. Castello, "Tunable BiCMOS Continuous-Time Filter for High-Frequency Applications," *IEEE Journal of Solid State Circuits*, Vol. 27, No. 12, pp. 1905-1915, Dec. 1992.

Summary Continuous-Time Filters

- Opamp RC filters
 - Good linearity → High dynamic range (60-90dB)
 - Only discrete tuning possible
 - Medium usable signal bandwidth (<10MHz)
- Opamp MOSFET-C
 - Linearity compromised (typical dynamic range 40-60dB)
 - Continuous tuning possible
 - Low usable signal bandwidth (<5MHz)
- Opamp MOSFET-RC
 - Improved linearity compared to Opamp MOSFET-C (D.R. 50-90dB)
 - Continuous tuning possible
 - Low usable signal bandwidth (<5MHz)
- Gm-C
 - Highest frequency performance (at least an order of magnitude higher compared to the rest <100MHz)
 - Dynamic range not as high as Opamp RC but better than Opamp MOSFET-C (40-70dB)