
 

 
## Linear Feedback Shift Registers (LFSRs)


- These are n-bit counters exhibiting *pseudo-random* behavior.
- Built from simple shift-registers with a small number of xor gates.
- Used for:
  - random number generation
  - counters
  - error checking and correction
- Advantages:
  - very little hardware
  - high speed operation
- Example 4-bit LFSR:


 
## 4-bit LFSR



- Circuit counts through  $2^4 - 1$  different non-zero bit patterns.
- Leftmost bit decides whether the "10011" xor pattern is used to compute the next value or if the register just shifts left.
- Can build a similar circuit with any number of FFs, may need more xor gates.
- In general, with n flip-flops,  $2^n - 1$  different non-zero bit patterns.
- (Intuitively, this is a counter that *wraps around* many times and in a strange way.)



## Applications of LFSRs

- Performance:
  - In general, xors are only ever 2-input and never connect in series.
  - Therefore the minimum clock period for these circuits is:  
 $T > T_{2\text{-input-xor}} + \text{clock overhead}$
  - Very little latency, and independent of  $n!$
- This can be used as a fast counter, if the particular sequence of count values is not important.
  - Example: micro-code micro-pc
- Can be used as a random number generator.
  - Sequence is a pseudo-random sequence:
    - numbers appear in a random sequence
    - repeats every  $2^n - 1$  patterns
  - Random numbers useful in:
    - computer graphics
    - cryptography
    - automatic testing
- Used for error detection and correction
  - CRC (cyclic redundancy codes)
  - ethernet uses them

## Galois Fields - the theory behind LFSRs

- LFSR circuits performs multiplication on a *field*.
- A field is defined as a *set* with the following:
  - two operations defined on it:
    - “addition” and “multiplication”
  - closed under these operations
  - associative and distributive laws hold
  - additive and multiplicative identity elements
  - additive inverse for every element
  - multiplicative inverse for every non-zero element
- Example fields:
  - set of rational numbers
  - set of real numbers
  - set of integers is *not* a field (why?)
- Finite fields are called *Galois* fields.
- Example:
  - Binary numbers 0,1 with XOR as “addition” and AND as “multiplication”.
  - Called GF(2).

## Galois Fields - The theory behind LFSRs

- Consider *polynomials* whose coefficients come from GF(2).
- Each term of the form  $x^n$  is either present or absent.
- Examples:  $0$ ,  $1$ ,  $x$ ,  $x^2$ , and  $x^7 + x^6 + 1$   

$$= 1 \cdot x^7 + 1 \cdot x^6 + 0 \cdot x^5 + 0 \cdot x^4 + 0 \cdot x^3 + 0 \cdot x^2 + 0 \cdot x^1 + 1 \cdot x^0$$

- With addition and multiplication these form a field:
- “Add”: XOR each element individually with no carry:

$$\begin{array}{r} x^4 + x^3 + \quad + x + 1 \\ + \quad x^4 + \quad + x^2 + x \\ \hline x^3 + x^2 + \quad + 1 \end{array}$$

- “Multiply”: multiplying by  $x^n$  is like shifting to the left.

$$\begin{array}{r} x^2 + x + 1 \\ \times \quad x + 1 \\ \hline x^2 + x + 1 \\ x^3 + x^2 + x \\ \hline x^3 + \quad + 1 \end{array}$$

## Galois Fields - The theory behind LFSRs

- These polynomials form a *Galois (finite) field* if we take the results of this multiplication modulo a prime polynomial  $p(x)$ .
  - A prime polynomial is one that cannot be written as the product of two non-trivial polynomials  $q(x)r(x)$
  - Perform modulo operation by subtracting a (polynomial) multiple of  $p(x)$  from the result. If the multiple is 1, this corresponds to XOR-ing the result with  $p(x)$ .
- For any degree, there exists at least one prime polynomial.
- With it we can form  $GF(2^n)$
- Additionally, ...
- Every Galois field has a primitive element,  $\alpha$ , such that all non-zero elements of the field can be expressed as a power of  $\alpha$ . By raising  $\alpha$  to powers (modulo  $p(x)$ ), all non-zero field elements can be formed.
- Certain choices of  $p(x)$  make the simple polynomial  $x$  the primitive element. These polynomials are called *primitive*, and one exists for every degree.
- For example,  $x^4 + x + 1$  is primitive. So  $\alpha = x$  is a primitive element and successive powers of  $\alpha$  will generate all non-zero elements of GF(16). *Example on next slide.*

## Galois Fields - The theory behind LFSRs

$$\begin{aligned}
 \alpha^0 &= 1 \\
 \alpha^1 &= x \\
 \alpha^2 &= x^2 \\
 \alpha^3 &= x^3 \\
 \alpha^4 &= x + 1 \\
 \alpha^5 &= x^2 + x \\
 \alpha^6 &= x^3 + x^2 \\
 \alpha^7 &= x^3 + x + 1 \\
 \alpha^8 &= x^2 + 1 \\
 \alpha^9 &= x^3 + x \\
 \alpha^{10} &= x^2 + x + 1 \\
 \alpha^{11} &= x^3 + x^2 + x \\
 \alpha^{12} &= x^3 + x^2 + x + 1 \\
 \alpha^{13} &= x^3 + x^2 + 1 \\
 \alpha^{14} &= x^3 + 1 \\
 \alpha^{15} &= 1
 \end{aligned}$$

- Note this pattern of coefficients matches the bits from our 4-bit LFSR example.

$$\begin{aligned}
 \alpha^4 &= x^4 \bmod x^4 + x + 1 \\
 &= x^4 \text{ xor } x^4 + x + 1 \\
 &= x + 1
 \end{aligned}$$

- In general finding primitive polynomials is difficult. Most people just look them up in a table, such as:

## Primitive Polynomials

|                             |                                 |                                |
|-----------------------------|---------------------------------|--------------------------------|
| $x^2 + x + 1$               | $x^{12} + x^6 + x^4 + x + 1$    | $x^{22} + x + 1$               |
| $x^3 + x + 1$               | $x^{13} + x^4 + x^3 + x + 1$    | $x^{23} + x^5 + 1$             |
| $x^4 + x + 1$               | $x^{14} + x^{10} + x^6 + x + 1$ | $x^{24} + x^7 + x^2 + x + 1$   |
| $x^5 + x^2 + 1$             | $x^{15} + x + 1$                | $x^{25} + x^3 + 1$             |
| $x^6 + x + 1$               | $x^{16} + x^{12} + x^3 + x + 1$ | $x^{26} + x^6 + x^2 + x + 1$   |
| $x^7 + x^3 + 1$             | $x^{17} + x^3 + 1$              | $x^{27} + x^5 + x^2 + x + 1$   |
| $x^8 + x^4 + x^3 + x^2 + 1$ | $x^{18} + x^7 + 1$              | $x^{28} + x^3 + 1$             |
| $x^9 + x^4 + 1$             | $x^{19} + x^5 + x^2 + x + 1$    | $x^{29} + x + 1$               |
| $x^{10} + x^3 + 1$          | $x^{20} + x^3 + 1$              | $x^{30} + x^6 + x^4 + x + 1$   |
| $x^{11} + x^2 + 1$          | $x^{21} + x^2 + 1$              | $x^{31} + x^3 + 1$             |
|                             |                                 | $x^{32} + x^7 + x^6 + x^2 + 1$ |

### Galois Field

Multiplication by  $x$

⇔ shift left

Taking the result mod  $p(x)$

⇔ XOR-ing with the coefficients of  $p(x)$  when the most significant coefficient is 1.

Obtaining all  $2^n - 1$  non-zero elements by evaluating  $x^k$

⇔ Shifting and XOR-ing  $2^n - 1$  times.


for  $k = 1, \dots, 2^n - 1$

## Building an LFSR from a Primitive Polynomial


- For  $k$ -bit LFSR number the flip-flops with FF1 on the right.
- The feedback path comes from the Q output of the leftmost FF.
- Find the primitive polynomial of the form  $x^k + \dots + 1$ .
- The  $x^0 = 1$  term corresponds to connecting the feedback directly to the D input of FF 1.
- Each term of the form  $x^n$  corresponds to connecting an xor between FF  $n$  and  $n+1$ .

- 4-bit example, uses  $x^4 + x + 1$

 
- $x^4 \Leftrightarrow$  FF4's Q output
- $x \Leftrightarrow$  xor between FF1 and FF2
- $1 \Leftrightarrow$  FF1's D input



 - To build an 8-bit LFSR, use the primitive polynomial  $x^8 + x^4 + x^3 + x^2 + 1$  and connect xors between FF2 and FF3, FF3 and FF4, and FF4 and FF5.



## Error Correction with LFSRs

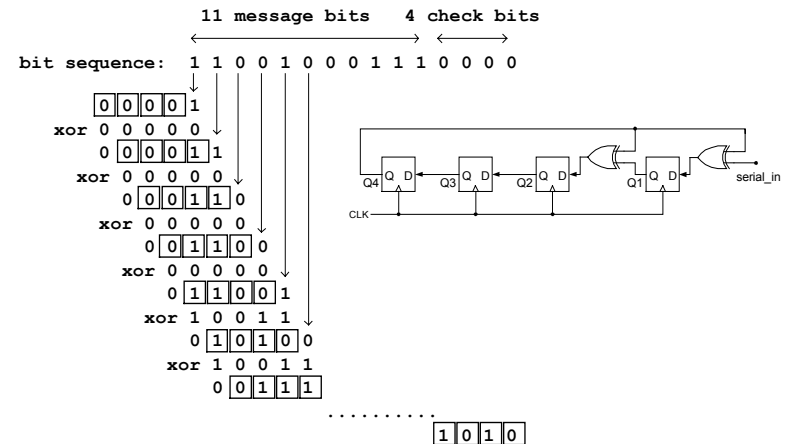

## Error Correction with LFSRs

- XOR Q4 with incoming bit sequence. Now values of shift-register don't follow a fixed pattern. Dependent on input sequence.
- Look at the value of the register after 15 cycles: "1010"
- Note the length of the input sequence is  $2^4 - 1 = 15$  (same as the number of different nonzero patterns for the original LFSR)
- Binary message occupies only 11 bits, the remaining 4 bits are "0000".
  - They would be replaced by the final result of our LFSR: "1010"
  - If we run the sequence back through the LFSR with the replaced bits, we would get "0000" for the final result.
  - 4 parity bits, "neutralize" the sequence with respect to the LFSR.
    - $11001000111\ 0000 \Rightarrow 1010$
    - $11001000111\ 1010 \Rightarrow 0000$
- If parity bits not all zero, an error occurred in transmission.
- If number of parity bits = log total number of bits, then single bit errors can be corrected.
- Using more parity bits allows more errors to be detected.
- Ethernet uses 32 parity bits per frame (packet) with 16-bit LFSR.


## Division

$$\begin{array}{r}
 \text{Divisor } 1000 \quad \overline{) 1001010} \quad \begin{array}{l} \text{Quotient} \\ \text{Dividend} \end{array} \\
 \underline{-1000} \\
 10 \\
 \underline{101} \\
 1010 \\
 \underline{-1000} \\
 10 \quad \text{Remainder (or Modulo result)}
 \end{array}$$

- See how big a number can be subtracted, creating quotient bit on each step
  - Binary  $\Rightarrow 1 * \text{divisor}$  or  $0 * \text{divisor}$
- Dividend = Quotient x Divisor + Remainder
  - $\text{sizeof}(\text{dividend}) = \text{sizeof}(\text{quotient}) + \text{sizeof}(\text{divisor})$
- 3 versions of divide, successive refinement
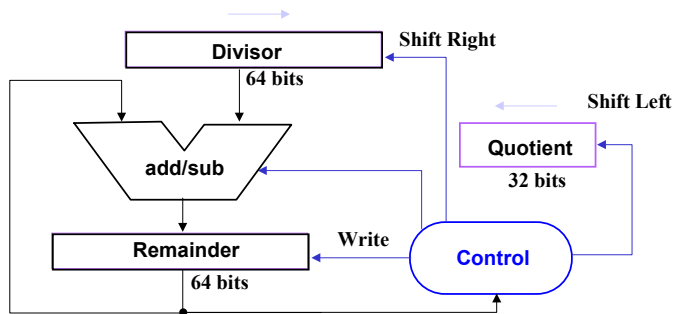
## DIVIDE HARDWARE Version 1

- 64-bit Divisor register, 64-bit adder/subtractor, 64-bit Remainder register, 32-bit Quotient register




## Divide Algorithm Version 1

Start: Place Dividend in Remainder

Takes  $n+1$  steps for  $n$ -bit Quotient & Rem

|           |          |          |
|-----------|----------|----------|
| Remainder | Quotient | Divisor  |
| 00000111  | 0000     | 00100000 |
| $7_{10}$  |          | $2_{10}$ |

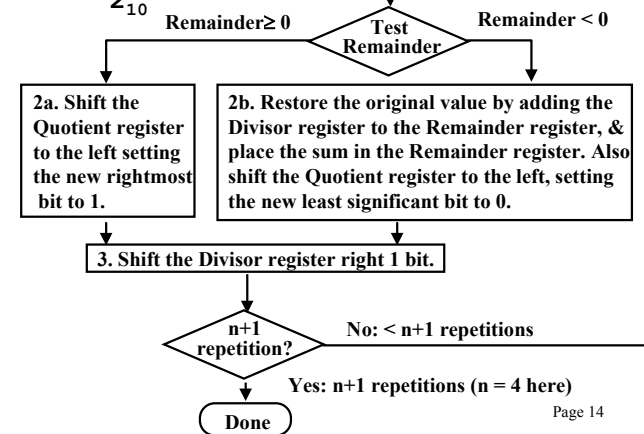1. Subtract the Divisor register from the Remainder register, and place the result in the Remainder register.



### Version 1 Division Example 7/2

| Iteration step                | quotient | divisor   | remainder |
|-------------------------------|----------|-----------|-----------|
| 0 Initial values              | 0000     | 0010 0000 | 0000 0111 |
| 1 1: rem=rem-div              | 0000     | 0010 0000 | 1110 0111 |
| 2b: rem<0 ⇒ +div, sll Q, Q0=0 | 0000     | 0010 0000 | 0000 0111 |
| 3: shift div right            | 0000     | 0001 0000 | 0000 0111 |
| 2 1: rem=rem-div              | 0000     | 0001 0000 | 1111 0111 |
| 2b: rem<0 ⇒ +div, sll Q, Q0=0 | 0000     | 0001 0000 | 0000 0111 |
| 3: shift div right            | 0000     | 0000 1000 | 0000 0111 |
| 3 1: rem=rem-div              | 0000     | 0000 1000 | 1111 1111 |
| 2b: rem<0 ⇒ +div, sll Q, Q0=0 | 0000     | 0000 1000 | 0000 0111 |
| 3: shift div right            | 0000     | 0000 0100 | 0000 0111 |
| 4 1: rem=rem-div              | 0000     | 0000 0100 | 0000 0011 |
| 2a: rem≥0 ⇒ sll Q, Q0=1       | 0001     | 0000 0100 | 0000 0011 |
| 3: shift div right            | 0001     | 0000 0010 | 0000 0011 |
| 5 1: rem=rem-div              | 0001     | 0000 0010 | 0000 0001 |
| 2a: rem≥0 ⇒ sll Q, Q0=1       | 0011     | 0000 0010 | 0000 0001 |
| 3: shift div right            | 0011     | 0000 0001 | 0000 0001 |


### Observations on Divide Version 1

- 1/2 bits in divisor always 0  
⇒ 1/2 of 64-bit adder is wasted  
⇒ 1/2 of divisor is wasted
- Instead of shifting divisor to right, shift remainder to left?
- 1<sup>st</sup> step cannot produce a 1 in quotient bit (otherwise quotient  $\geq 2^n$ )  
⇒ switch order to shift first and then subtract, can save 1 iteration



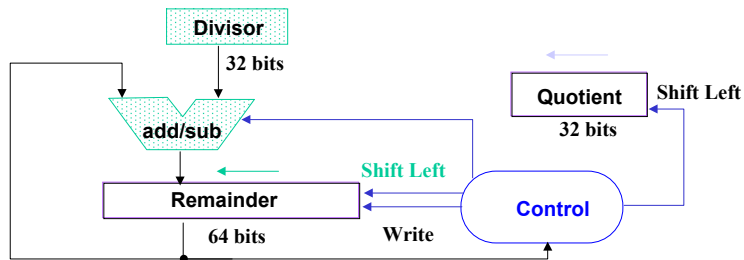
## DIVIDE HARDWARE Version 2

- 32-bit Divisor register, 32-bit ALU, 64-bit Remainder register, 32-bit Quotient register


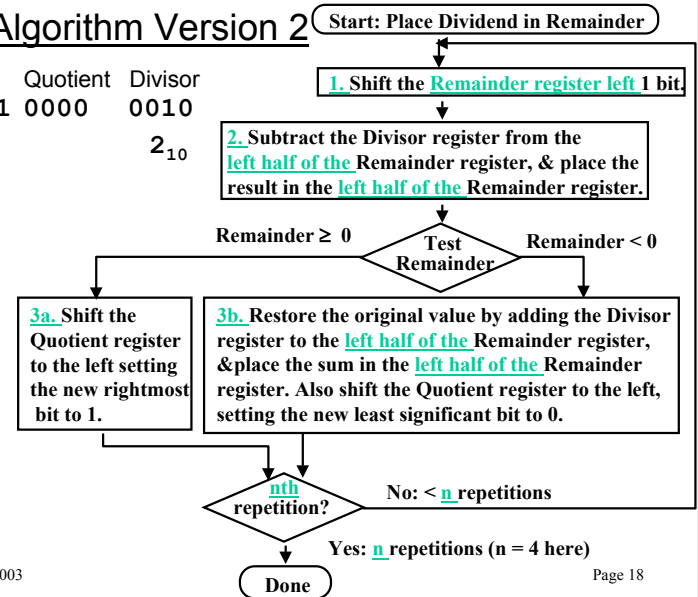
## Divide Algorithm Version 2

Remainder    Quotient    Divisor  
 00000111    0000    0010  
 $7_{10}$                      $2_{10}$





## Observations on Divide Version 2

- Eliminate Quotient register by combining with Remainder as shifted left.
  - Start by shifting the Remainder left as before.
  - Thereafter loop contains only two steps because the shifting of the Remainder register shifts both the remainder in the left half and the quotient in the right half
  - The consequence of combining the two registers together and the new order of the operations in the loop is that the remainder will shifted left one time too many.
  - Thus the final correction step must shift back only the remainder in the left half of the register
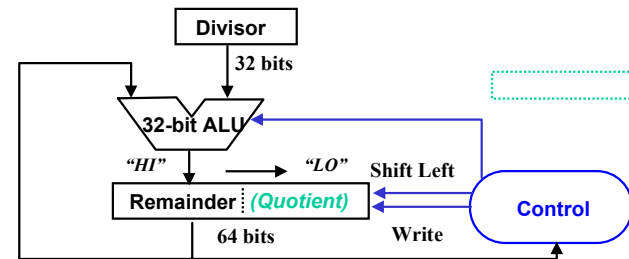
## DIVIDE HARDWARE Version 3

- 32-bit Divisor register, 32-bit adder/subtractor, 64-bit Remainder register, (Q-bit Quotient reg)



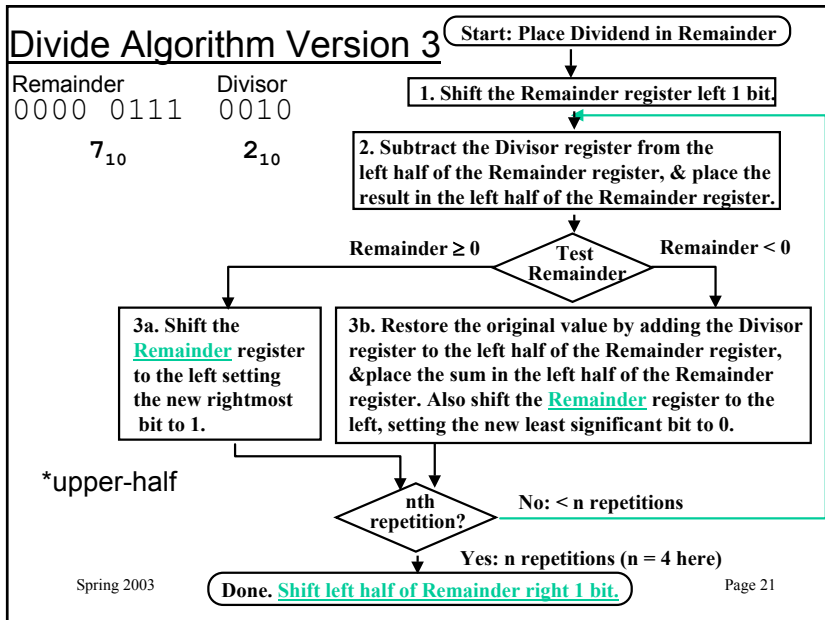

### Observations on Divide Version 3

- Same Hardware as shift and add multiplier: just 63-bit register to shift left or shift right
- Signed divides: Simplest is to remember signs, make positive, and complement quotient and remainder if necessary
  - Note: Dividend and Remainder must have same sign
  - Note: Quotient negated if Divisor sign & Dividend sign disagree e.g.,  $-7 \div 2 = -3$ , remainder =  $-1$
- Possible for quotient to be too large: if divide 64-bit integer by 1, quotient is 64 bits (“called saturation”)