

University of California at Berkeley
College of Engineering
Department of Electrical Engineering and Computer Science

EECS 150
 Spring 2004

R. H. Katz

Problem Set # 2 (Assigned 29 January, Due 6 February)

1. Given the following expressions using the laws and theorems of Boolean Algebra:
 - (i) $W(A,B,C) = A' B' C' + A' B C' + A B' C' + A B C'$
 - (ii) $X(A,B,C) = A' B' C' + A' B' C + A B' C + A B C$
 - (iii) $Y(A,B,C,D) = A' B' C' D + A' B' C D' + A' B' C D + A' B C D + A B' C' D' + A B' C D$
 - (iv) $Z(A,B,C,D) = A' B' C' D + A' B' C D + A' B C' D + A' B C D + A B' C' D' + A B' C D' + A B C' D' + A B C D'$

Use K-maps on the expressions (i)-(iv) to answer the following. Show your work in K-map form:

 - (a) Find the minimized sum of products form.
 - (b) Find the minimized product of sums form.
 - (c) Find the minimized sum of products form of the function's complement.
 - (d) Find the minimized product of sums form of the function's complement.
2. Using the same four functions as described in Problem 1, do the following:
 - (a) Show how to implement each function with a Decoder and an OR gate.
 - (b) Show how to implement (i) and (ii) with a 4:1 multiplexer and (iii) and (iv) with an 8:1 multiplexer.
3. Consider the following multilevel Boolean expressions:
 - (i) $W(A,B) = AB$
 - (ii) $X(A,B) = A' B + A B'$
 - (iii) $Y(X,C) = X' C + X C'$
 - (iv) $Z(C,X,W) = X C + W$

Answer the following questions, showing your work:

 - (a) What is the complexity of Y and Z in terms of gate, wire, and literal counts?
 - (b) Expand Y and Z into two level networks, and repeat (a) on the result.
 - (c) Find the two level canonical Sum of Products form for Y and Z.
 - (d) Find the two level canonical Products of Sums form for Y and Z.
 - (e) Which of your answers to (b), (c), (d) yields the "simplest" implementation of Y and Z.
4. How would you implement the functions Y(A,B,C) and Z(A,B,C) in Problem 3 using multiplexer logic? How does the complexity in terms of gates and wires compare with your answer to 3(e)?
5. Develop a minimized Boolean implementation of a multifunctional circuit that works as follows. The subsystem has four binary inputs A, B, C, D, and generates a single output bit, X. X is A if C and D are both 0, B if C and D are both 1, A + B if C is 0 and D is 1, and A B if C is 1 and D is 0.
 - (a) Draw the truth table for X (A, B, C, D).
 - (b) Minimize the function X using a 4-variable K-map. Write down the Boolean expressions for the minimized Sum of Products form of X.
 - (c) Repeat the minimization process, this time deriving Product of Sums form.
 - (d) Now implement X using an 8:1 multiplexer and no other logic other than literals. How does its complexity in terms of gates and wires compare with your answers to parts (b) and (c)?
6. Consider a combinational logic subsystem that performs a 2 x 2 multiplication function (this was presented in Lecture 2). It has two 2-bit inputs A B and C D representing binary magnitude numbers in the range 0-3, and forms the 4-bit product W X Y Z in the range 0-9. Show how to implement WXYZ using one 8:1 multiplexer for each of W, X, Y, and Z. How does the complexity in terms of gates and wires compare with the minimized answers derived in the course notes?