

CS150 Spring 2004

Problem Set #3 Solutions

1) a)

I_3	I_2	I_1	O_1	O_0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1

c)

I_1	$I_3 I_2$	O_1	O_0
0	00	0	0
1	01	0	1
0	10	1	0
1	11	1	1

I_1	$I_3 I_2$	O_0
0	00	0
1	01	0
0	10	0
1	11	1



$$O_1 = I_2 \bar{I}_1 + I_3 \bar{I}_1$$

$$= (I_2 + I_3) \bar{I}_1$$

$$O_0 = (I_3 + I_1)(\bar{I}_2 + I_1)$$

$$= I_1 + I_3 \bar{I}_2$$

b) Attached

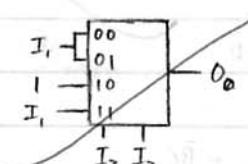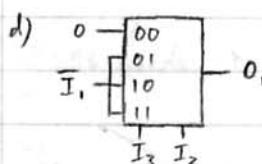


e) The ROM would have to be 8 words by 2 bits/word because there are 8 different input combinations and the output is 2 bits.

f) The answer from (c) is simpler than the answer from (d). The answer from (c) uses a total of four 2-input gates. The muxes in (d) use a total of eight 2-input gates and two 4-input gates.

2) a)

	A	B	C	D	S1	S2	S3	S4	S5	S6	S7
0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	0	1	0
2	0	0	1	0	0	0	1	0	0	1	0
3	0	0	1	1	1	0	1	0	0	1	0
4	0	1	0	0	1	1	1	0	0	1	0
5	0	1	0	1	1	1	1	0	1	1	0
6	0	1	1	0	1	1	1	1	1	1	0
7	0	1	1	1	1	1	1	1	1	1	1
8	1	0	0	0	1	1	1	1	0	1	1
9	1	0	0	1	1	1	1	0	0	1	1
A	1	0	1	0	1	0	1	0	0	1	1
B	1	0	1	1	0	0	1	0	0	1	1
C	1	1	0	0	0	0	0	0	0	1	1
D	1	1	0	1	0	0	0	0	0	0	1
E	1	1	1	0	0	0	0	1	0	0	1
F	1	1	1	1	0	0	0	1	0	1	1

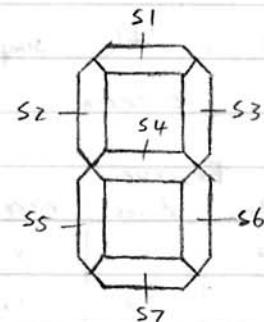

b) Attached

c)

	AB	00	01	11	10	S1
CD	00	0	1	0	1	
00	0	1	0	1		
01	0	1	0	1		
11	1	1	0	0		
10	0	1	0	1		

	AB	00	01	11	10	S2
CD	00	0	1	0	1	
00	0	1	0	1		
01	0	1	0	1		
11	0	1	0	0		
10	0	1	0	0		

	AB	00	01	11	10	S3
CD	00	0	1	0	1	
00	0	1	0	1		
01	0	1	0	1		
11	1	1	1	0		
10	1	1	1	0		

\backslash	AB	00	01	11	10
CD	00	0	0	0	1
00	00	0	0	0	0
01	00	0	1	0	0
11	00	0	1	0	0
10	00	1	1	0	0

\backslash	AB	00	01	11	10
CD	00	0	0	0	0
00	00	0	0	0	0
01	00	0	1	0	0
11	00	0	1	0	0
10	00	1	0	0	0

\backslash	AB	00	01	11	10
CD	00	0	1	1	1
00	00	0	1	1	1
01	00	1	1	0	1
11	00	1	1	0	1
10	00	1	0	0	1

\backslash	AB	00	01	11	10
CD	00	0	0	1	1
00	00	0	0	1	1
01	00	0	1	1	1
11	00	0	1	1	1
10	00	0	1	1	1

$$\begin{aligned}
 S1 &= \bar{A}\bar{B} + A\bar{B}\bar{C} + A\bar{B}\bar{D} + \bar{A}CD \\
 S2 &= \bar{A}\bar{B} + A\bar{B}\bar{C} \\
 S3 &= \bar{A}C + \bar{A}\bar{B} + A\bar{B} \\
 S4 &= BC + A\bar{B}\bar{C}\bar{D} \\
 S5 &= \bar{A}\bar{B}D + \bar{A}\bar{B}C \\
 S6 &= \bar{A}\bar{D} + \bar{A}\bar{C} + CD + \bar{A}\bar{B} + A\bar{B} + B\bar{C}\bar{D} \\
 S7 &= A + BCD
 \end{aligned}$$

(16 different terms)

d)

$$S1 = \bar{A}\bar{B} + \bar{A}CD + A\bar{B}\bar{C} + A\bar{B}\bar{D}$$

$$S2 = \bar{A}\bar{B} + A\bar{B}\bar{C}$$

$$S3 = \bar{A}\bar{B} + \bar{A}\bar{B} + \bar{B}\bar{C}$$

$$S4 = \bar{A}\bar{B}\bar{C}$$

$$S5 = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{D}$$

$$S6 = A\bar{B} + BCD + \bar{A}\bar{B}$$

$$S7 = A\bar{B} + BCD + A$$

(14 different terms)

e) (d) is a little simpler when using the number of different terms as the criteria.

3) a)

Reservoir			Output		
quarters	dimes	nickels	quarters	dimes	nickels
4+	x	x	4	0	0
3	2+	1+	3	2	1
3	x	0	no change		
3	1	3+	3	1	3
3	0	5+	3	0	5
3-	0	0	no change		
2	5+	x	2	5	0
2	4+	2+	2	4	2
2	2+	6+	2	2	6
2	0	10+	2	0	10
1	x	0	no change		
1	7+	1+	1	7	1
1	6+	5+	1	6	5
1	5+	7+	1	5	7
1	4+	9+	1	4	9
1	2+	11+	1	2	11
1	1	13+	1	1	13
1	0	15+	1	0	15


(continued)

0	10+	x	0	10
1	9	z	1	9
2	8	4+	2	8
3	7	6+	3	7
4	6	8+	4	6
5	5	10+	5	10
6	4	12+	6	12
7	3	14+	7	14
8	2	16	8	16
9	1	z	9	1

27 Unique ways

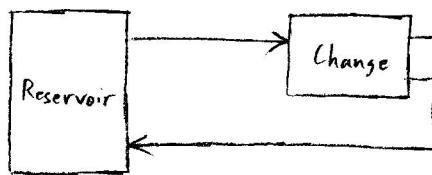b) Inputs: number of quarters/dimes/nickels in reservoir
bit to indicate that a user has inserted a dollar bill

Outputs: number of quarters/dimes/nickels to output
"no change" light on or off



c) 4096 words by 12 bits word

The range for... quarters is 0 to 4 (3 bits). (Above 5 quarters is just like having 4)
... dimes is 0 to 10 (4 bits).
... nickels is 0 to 16 (5 bits).

So the input signal and resulting output are 12 bits wide. The
number of words = $2^{\# \text{ of input bits}}$.

d) Attached

```

1 // Problem 1, part b
2
3 module lowBit (I, O);
4     input [3:1] I;
5     output [1:0] O;
6     reg [1:0] O;
7
8     assign O[1] = (I[3] | I[2]) & (~I[1]);
9     assign O[0] = I[1] | (I[3] & ~I[2]);
10 endmodule
11
12
13
14 // Problem 2, part b
15
16 module toMartian (in, led);
17     input [3:0] in;
18     output [7:1] led;
19     reg [7:1] led;
20
21     assign led[7] = in[3] | (in[2] & in[1] & in[0]);
22     assign led[6] = (~in[3] & in[2]) | (in[3] & ~in[2]) | (in[2] & ~in[1] & ~in[0])
23         | (~in[3] & in[0]) | (~in[3] & in[1]) | (in[1] & in[0]);
24     assign led[5] = (~in[3] & in[2] & in[0]) | (~in[3] & in[2] & in[1]);
25     assign led[4] = (in[2] & in[1]) | (in[3] & ~in[2] & ~in[1] & ~in[0]);
26     assign led[3] = (~in[3] & in[2]) | (in[3] & ~in[2] & in[1]);
27     assign led[2] = (~in[3] & in[2]) | (in[3] & ~in[2] & ~in[1]);
28     assign led[1] = (~in[3] & in[2]) | (in[3] & ~in[2] & ~in[1]) | (in[3] & ~in[2] & ~in
29         [0])
30         | (~in[3] & in[1] & in[0]);
31 endmodule
32
33
34 // Problem 3, part d
35
36 module changeMe (inq, ind, inn, outq, outd, outn, nc, go);
37     input [2:0] inq;
38     input [3:0] ind;
39     input [4:0] inn;
40     input go;
41     output [2:0] out1;
42     output [3:0] outd;
43     output [4:0] outn;
44     output nc;
45     reg [2:0] outq, q;
46     reg [3:0] outd, d;
47     reg [4:0] outn, n;
48     reg nc;
49
50     integer i, j, k;
51
52     always @ (inq or ind or inn) begin
53         begin : find_change
54             for (i = inq; i >= 0; i = i - 1) begin
55                 for (j = ind; j >= 0; j = j - 1) begin
56                     for (k = inn; k >= 0; k = k - 1) begin
57                         if ((inq*25) + (ind*10) + (inn*5) == 100) begin
58                             nc <= 1b'0;
59                             q <= i; d <= j; n <= k;
60                             disable find_change;

```

```
61           end
62           end
63       end
64   end
65   end
66 end
67
68 always @ (posedge go) begin
69     outq <= q;
70     outd <= d;
71     outn <= n;
72 end
73 endmodule
```

