

EECS150 - Digital Design
Lecture 22 - Arithmetic and Logic Circuits
Part 3


April 14, 2005
 John Wawrzynek

Multiplication

$$\begin{array}{r}
 \begin{array}{cccc}
 a_3 & a_2 & a_1 & a_0 \leftarrow \text{Multiplicand} \\
 b_3 & b_2 & b_1 & b_0 \leftarrow \text{Multiplier} \\
 \hline
 & X & a_3b_0 & a_2b_0 & a_1b_0 & a_0b_0 \\
 & & a_3b_1 & a_2b_1 & a_1b_1 & a_0b_1 \\
 & & a_3b_2 & a_2b_2 & a_1b_2 & a_0b_2 \\
 a_3b_3 & a_2b_3 & a_1b_3 & a_0b_3 & & \\
 \hline
 & & \dots & a_1b_0+a_0b_1 & a_0b_0 & \leftarrow \text{Product}
 \end{array}
 \end{array}
 \left. \vphantom{\begin{array}{r} a_3b_0 \\ a_3b_1 \\ a_3b_2 \\ a_3b_3 \end{array}} \right\} \text{Partial products}$$

*Many different circuits exist for multiplication.
 Each one has a different balance between
 speed (performance) and amount of logic (cost).*

“Shift and Add” Multiplier

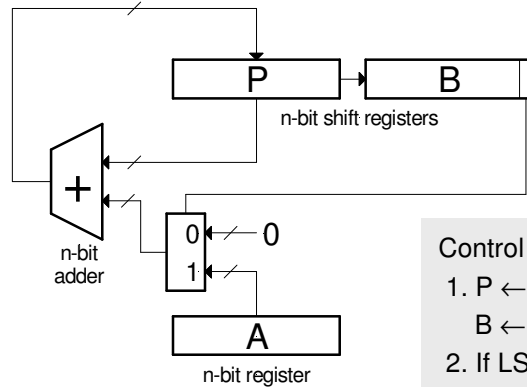

- Sums each partial product, one at a time.
- In binary, each partial product is shifted versions of A or 0.

Control Algorithm:

1. $P \leftarrow 0$, $A \leftarrow$ multiplicand, $B \leftarrow$ multiplier
2. If LSB of $B == 1$ then add A to P
else add 0
3. Shift $[P][B]$ right 1
4. Repeat steps 2 and 3 $n-1$ times.
5. $[P][B]$ has product.

- Cost $\propto n$, $T = n$ clock cycles.
- What is the critical path for determining the min clock period?

Spring 2005

EECS150 - Lec22-alc3

Page 3

“Shift and Add” Multiplier

Signed Multiplication:

Remember for 2's complement numbers MSB has negative weight:

$$X = \sum_{i=0}^{N-2} x_i 2^i - x_{n-1} 2^{n-1}$$

$$\begin{aligned} \text{ex: } -6 &= 11010_2 = 0 \cdot 2^0 + 1 \cdot 2^1 + 0 \cdot 2^2 + 1 \cdot 2^3 - 1 \cdot 2^4 \\ &= 0 + 2 + 0 + 8 - 16 = -6 \end{aligned}$$

- Therefore for multiplication:
 - a) subtract final partial product
 - b) sign-extend partial products
- Modifications to shift & add circuit:
 - a) adder/subtractor
 - b) sign-extender on P shifter register


Spring 2005

EECS150 - Lec22-alc3

Page 4

Array Multiplier

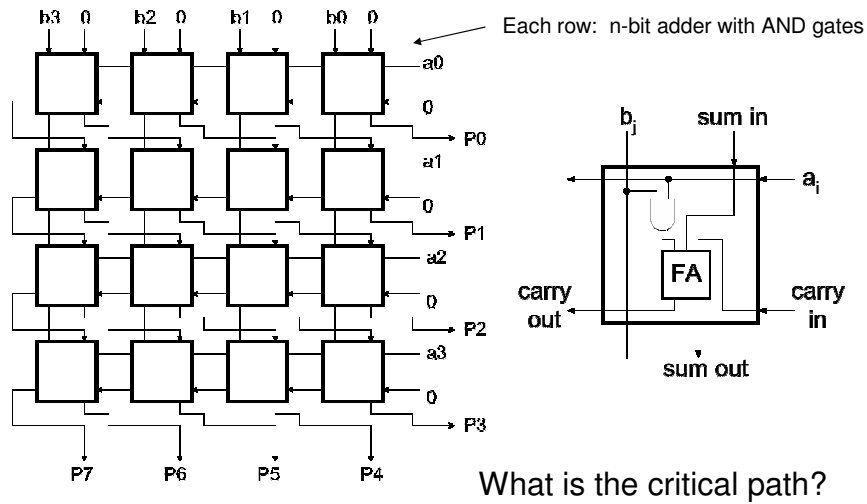Generates all n partial products simultaneously.



Carry-save Addition


- Speeding up multiplication is a matter of speeding up the summing of the partial products.
- “Carry-save” addition can help.
- Carry-save addition passes (saves) the carries to the output, rather than propagating them.
- Example: sum three numbers, $3_{10} = 0011$, $2_{10} = 0010$, $3_{10} = 0011$

$$\begin{array}{r}
 3_{10} \ 0011 \\
 + 2_{10} \ 0010 \\
 \hline
 c \ 0100 = 4_{10} \\
 s \ 0001 = 1_{10} \\
 \hline
 \text{carry-save add} \left\{ \begin{array}{l} 3_{10} \ 0011 \\ c \ 0010 = 2_{10} \\ s \ 0110 = 6_{10} \\ \hline 1000 = 8_{10} \end{array} \right.
 \end{array}$$

carry-propagate add

- In general, *carry-save* addition takes in 3 numbers and produces 2.
- Whereas, *carry-propagate* takes 2 and produces 1.
- With this technique, we can avoid carry propagation until final addition

Carry-save Circuits

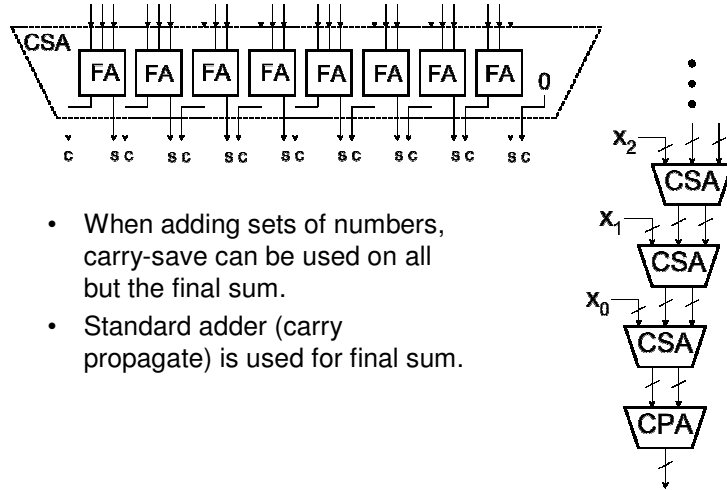


- When adding sets of numbers, carry-save can be used on all but the final sum.
- Standard adder (carry propagate) is used for final sum.

Spring 2005

EECS150 - Lec22-alc3

Page 7

Array Multiplier using Carry-save Addition

 

Spring 2005


EECS150 - Lec22-alc3

Page 8

Carry-save Addition

CSA is associative and commutative. For example:
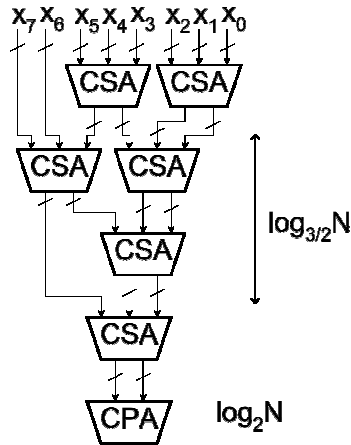
$$(((X_0 + X_1) + X_2) + X_3) = ((X_0 + X_1) + (X_2 + X_3))$$



- A balanced tree can be used to reduce the logic delay.
- This structure is the basis of the **Wallace Tree Multiplier**.
- Partial products are summed with the CSA tree. Fast CPA (ex: CLA) is used for final sum.
- Multiplier delay $\propto \log_{3/2} N + \log_2 N$

Spring 2005

EECS150 - Lec22-alc3

Page 9

Division

```

          1001  Quotient
Divisor 1000 | 1001010  Dividend
          -1000
          ---
           10
           101
           1010
           -1000
           ---
            10  Remainder (or Modulo result)
    
```

- See how big a number can be subtracted, creating quotient bit on each step
Binary $\Rightarrow 1 * \text{divisor}$ or $0 * \text{divisor}$
- Dividend = Quotient x Divisor + Remainder
sizeof(dividend) = sizeof(quotient) + sizeof(divisor)
- 3 versions of divide, "successive refinement"


Spring 2005

EECS150 - Lec22-alc3

Page 10

DIVIDE HARDWARE Version 1

- 64-bit Divisor register, 64-bit adder/subtractor, 64-bit Remainder register, 32-bit Quotient register

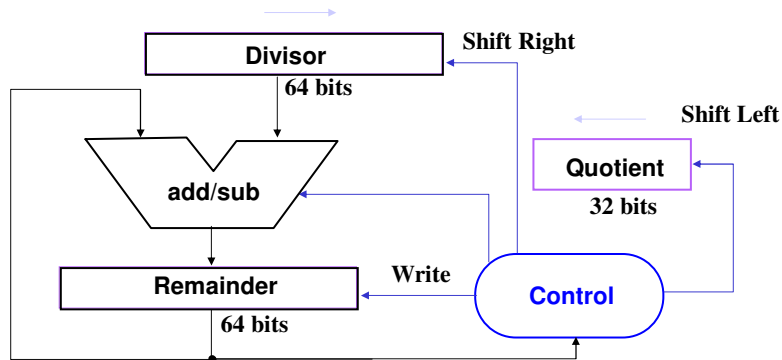

Spring 2005

EECS150 - Lec22-alc3


Page 11

Divide Algorithm Version 1 (Start: Place Dividend in Remainder)

Takes $n+1$ steps for n -bit Quotient & Rem

Remainder	Quotient	Divisor
00000111	0000	00100000
7_{10}	2_{10}	

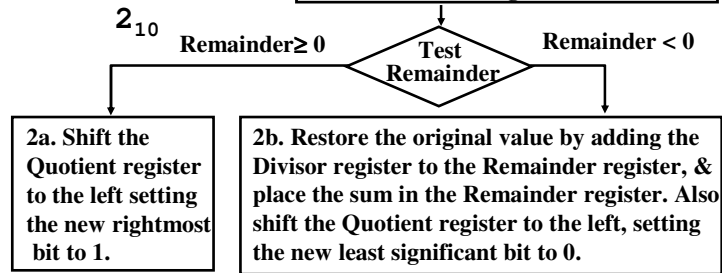1. Subtract the Divisor register from the Remainder register, and place the result in the Remainder register.



$n+1$ repetition? No: $< n+1$ repetitions

Yes: $n+1$ repetitions ($n = 4$ here)

Done

Spring 2005

Page 12

Version 1 Division Example 7/2


Iteration step	quotient	divisor	remainder
0 Initial values	0000	0010 0000	0000 0111
1 1: rem=rem-div	0000	0010 0000	1110 0111
2b: rem<0 ⇒ +div, sll Q, Q0=0	0000	0010 0000	0000 0111
3: shift div right	0000	0001 0000	0000 0111
2 1: rem=rem-div	0000	0001 0000	1111 0111
2b: rem<0 ⇒ +div, sll Q, Q0=0	0000	0001 0000	0000 0111
3: shift div right	0000	0000 1000	0000 0111
3 1: rem=rem-div	0000	0000 1000	1111 1111
2b: rem<0 ⇒ +div, sll Q, Q0=0	0000	0000 1000	0000 0111
3: shift div right	0000	0000 0100	0000 0111
4 1: rem=rem-div	0000	0000 0100	0000 0011
2a: rem≥0 ⇒ sll Q, Q0=1	0001	0000 0100	0000 0011
3: shift div right	0001	0000 0010	0000 0011
5 1: rem=rem-div	0001	0000 0010	0000 0001
2a: rem≥0 ⇒ sll Q, Q0=1	0011	0000 0010	0000 0001
3: shift div right	0011	0000 0001	0000 0001

Observations on Divide Version 1

- 1/2 bits in divisor always 0
 - ⇒ 1/2 of 64-bit adder is wasted
 - ⇒ 1/2 of divisor is wasted
- Instead of shifting divisor to right, shift remainder to left?
- 1st step cannot produce a 1 in quotient bit (otherwise quotient $\geq 2^n$)
 - ⇒ switch order to shift first and then subtract, can save 1 iteration

DIVIDE HARDWARE Version 2

- 32-bit Divisor register, 32-bit ALU, 64-bit Remainder register, 32-bit Quotient register

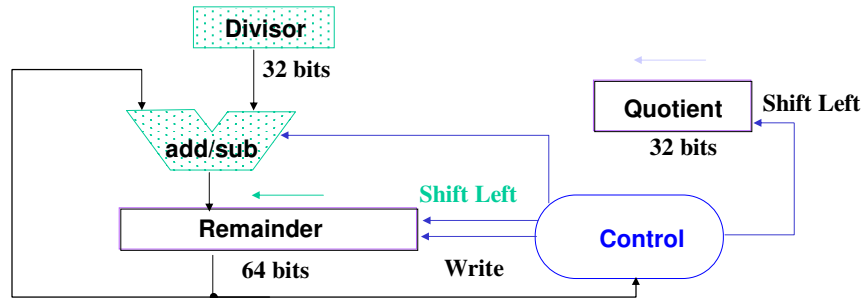

Spring 2005

EECS150 - Lec22-alc3

Page 15

Divide Algorithm Version 2

Remainder	Quotient	Divisor
00000111	0000	0010
7_{10}		2_{10}

Start: Place Dividend in Remainder

1. Shift the Remainder register left 1 bit.

2. Subtract the Divisor register from the left half of the Remainder register, & place the result in the left half of the Remainder register.

Test
Remainder

Remainder ≥ 0 Remainder < 0

3a. Shift the Quotient register to the left setting the new rightmost bit to 1.

3b. Restore the original value by adding the Divisor register to the left half of the Remainder register, & place the sum in the left half of the Remainder register. Also shift the Quotient register to the left, setting the new least significant bit to 0.

nth repetition?

No: $< n$ repetitions

Yes: n repetitions ($n = 4$ here)

Done

Spring 2005

Page 16

Observations on Divide Version 2

- Eliminate Quotient register by combining with Remainder as shifted left.
 - Start by shifting the Remainder left as before.
 - Thereafter loop contains only two steps because the shifting of the Remainder register shifts both the remainder in the left half and the quotient in the right half
 - The consequence of combining the two registers together and the new order of the operations in the loop is that the remainder will shifted left one time too many.
 - Thus the final correction step must shift back only the remainder in the left half of the register


Spring 2005

EECS150 - Lec22-alc3

Page 17

DIVIDE HARDWARE Version 3


- 32-bit Divisor register, 32-bit adder/subtractor, 64-bit Remainder register, (0-bit Quotient reg)

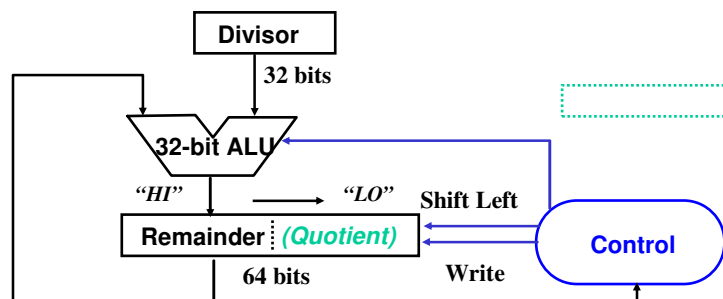

Spring 2005

EECS150 - Lec22-alc3

Page 18

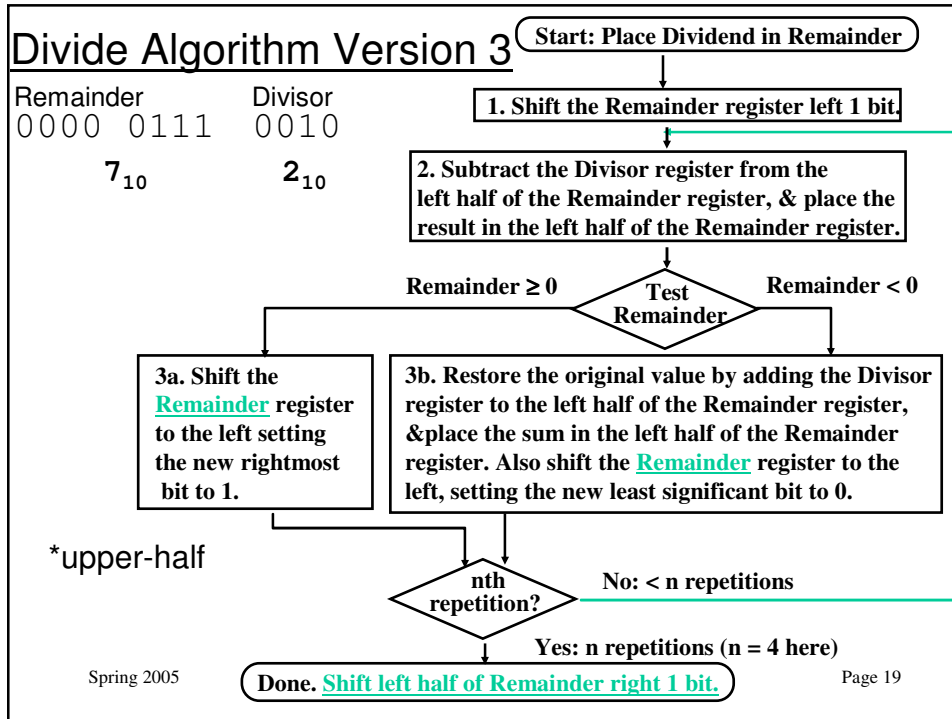

Observations on Divide Version 3

- Same Hardware as shift and add multiplier: just 63-bit register to shift left or shift right
- Signed divides: Simplest is to remember signs, make positive, and complement quotient and remainder if necessary
 - Note: Dividend and Remainder must have same sign
 - Note: Quotient negated if Divisor sign & Dividend sign disagree e.g., $-7 \div 2 = -3$, remainder = -1
- Possible for quotient to be too large: if divide 64-bit integer by 1, quotient is 64 bits (“called saturation”)