

EECS150 - Digital Design

Lecture 7- MIPS CPU


Microarchitecture

Feb 4, 2012
John Wawrzynek

Key 61c Concept: “Stored Program”

- Instructions and data stored in memory.
- Only difference between two applications (for example, a text editor and a video game), is the sequence of instructions.
- To run a new program:
 - No rewiring required
 - Simply store new program in memory
 - The processor hardware executes the program:
 - fetches (reads) the instructions from memory in sequence
 - performs the specified operation
- The program counter (PC) keeps track of the current instruction.

Assembly Code	Machine Code
lw \$t2, 32(\$0)	0x8C0A0020
add \$s0, \$s1, \$s2	0x02328020
addi \$t0, \$s3, -12	0x2268FFF4
sub \$t0, \$t3, \$t5	0x016D4022

 

Key 61c Concept:

High-level languages help productivity.

High-level code

```
// add the numbers from 0 to 9
int sum = 0;
int i;


for (i=0; i!=10; i = i+1) {
    sum = sum + i;
}
```

MIPS assembly code

```
# $s0 = i, $s1 = sum
addi $s1, $0, 0
add $s0, $0, $0
addi $t0, $0, 10
for: beq $s0, $t0, done
      add $s1, $s1, $s0
      addi $s0, $s0, 1
      j for
done:
```

Therefore with the help of a compiler (and assembler), to run applications all we need is a means to interpret (or “execute”) machine instructions. Usually the application calls on the operating system and libraries to provide special functions.

Abstraction Layers

 

- **Architecture:** the programmer's view of the computer
 - Defined by instructions (operations) and operand locations
- **Microarchitecture:** how to implement an architecture in hardware (covered in great detail later)
- The microarchitecture is built out of "logic" circuits and memory elements (this semester).
- All logic circuits and memory elements are implemented in the physical world with transistors.

Interpreting Machine Code

- Start with opcode
- Opcode tells how to parse the remaining bits
- If opcode is all 0's
 - R-type instruction
 - Function bits tell what instruction it is
- Otherwise
 - opcode tells what instruction it is

	Machine Code				Field Values				Assembly Code				
(0x2237FFF1)	op 001000	rs 10001	rt 10111	imm 111111110001		op 8	rs 17	rt 23	imm -15	addi \$s7, \$s1, -15			
	2 2	2 3	3 7	F F	F F								
(0x02F34022)	op 000000	rs 10111	rt 10011	rd 01000	shamt 00000	funct 100010	op 0	rs 23	rt 19	rd 8	shamt 0	funct 34	sub \$t0, \$s7, \$s3
	0 2	2 F	F 3	4 3	0 2	2 2							


A processor is a machine code interpreter build in hardware!

Processor Microarchitecture Introduction

Microarchitecture: how to implement an architecture in hardware

Good examples of how to put principles of digital design to practice.

Introduction to final project.

 


MIPS Processor Architecture

- For now we consider a subset of MIPS instructions:
 - R-type instructions: `and`, `or`, `add`, `sub`, `slt`
 - Memory instructions: `lw`, `sw`
 - Branch instructions: `beq`
- Later we'll add `addi` and `j`

MIPS Micrarchitecture Organization

Datapath + Controller + External Memory

 

How to Design a Processor: step-by-step

1. Analyze instruction set architecture (ISA) \Rightarrow datapath requirements
 - meaning of each instruction is given by the ***data transfers (register transfers)***
 - datapath must include storage element for ISA registers
 - datapath must support each data transfer
2. Select set of datapath components and establish clocking methodology
3. Assemble datapath meeting requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the data transfer.
5. Assemble the control logic.

Review: The MIPS Instruction

	31	26	21	16	11	6	0
R-type		op	rs	rt	rd	shamt	funct
	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	0
I-type	31	26	21	16			0
	op	rs	rt				address/immediate
	6 bits	5 bits	5 bits				16 bits
J-type	31	26					0
	op						target address
	6 bits						26 bits

The different fields are:

op: operation ("opcode") of the instruction

rs, **rt**, **rd**: the source and destination register specifiers

shamt: shift amount

funct: selects the variant of the operation in the "op" field


address / immediate: address offset or immediate value

target address: target address of jump instruction

Subset for Lecture


add, sub, or, slt

- addu rd,rs,rt
- subu rd,rs,rt

 


lw, sw

- lw rt,rs,imm16
- sw rt,rs,imm16

 

beq

- beq rs,rt,imm16

 

Register Transfer Descriptions

All start with instruction fetch:

{op , rs , rt , rd , shamt , funct} \leftarrow IMEM[PC] OR
{op , rs , rt , Imm16} \leftarrow IMEM[PC] THEN

inst Register Transfers

add	$R[rd] \leftarrow R[rs] + R[rt];$	$PC \leftarrow PC + 4$
sub	$R[rd] \leftarrow R[rs] - R[rt];$	$PC \leftarrow PC + 4$
or	$R[rd] \leftarrow R[rs] R[rt];$	$PC \leftarrow PC + 4$
slt	$R[rd] \leftarrow (R[rs] < R[rt]) ? 1 : 0;$	$PC \leftarrow PC + 4$
lw	$R[rt] \leftarrow DMEM[R[rs] + \text{sign_ext(Imm16)}];$	$PC \leftarrow PC + 4$
sw	$DMEM[R[rs] + \text{sign_ext(Imm16)}] \leftarrow R[rt];$	$PC \leftarrow PC + 4$
beq	if (R[rs] == R[rt]) then $PC \leftarrow PC + 4 + \{\text{sign_ext(Imm16)}, 00\}$ else $PC \leftarrow PC + 4$	


Microarchitecture

Multiple implementations for a single architecture:

- Single-cycle
 - Each instruction executes in a single clock cycle.
- Multicycle
 - Each instruction is broken up into a series of shorter steps with one step per clock cycle.
- Pipelined (variant on "multicycle")
 - Each instruction is broken up into a series of steps with one step per clock cycle
 - Multiple instructions execute at once.


CPU clocking (1/2)

 - Single Cycle CPU: All stages of an instruction are completed within one *long* clock cycle.
 - The clock cycle is made sufficient long to allow each instruction to complete all stages without interruption and within one cycle.



CPU clocking [2/2]

 
- Multiple-cycle CPU: Only one stage of instruction per clock cycle.
 - The clock is made as long as the slowest stage.



Several significant advantages over single cycle execution: Unused stages in a particular instruction can be skipped OR instructions can be pipelined (overlapped).

MIPS State Elements

 - Determines everything about the execution status of a processor:
 - PC register
 - 32 registers
 - Memory




Note: for these state elements, clock is used for write but not for read (asynchronous read, synchronous write).

Single-Cycle Datapath: lw fetch

- First consider executing `lw`

$$R[rt] \leftarrow DMEM[R[rs] + \text{sign_ext}(Imm16)]$$


- STEP 1: Fetch instruction

 

Single-Cycle Datapath: lw register read

$$R[rt] \leftarrow DMEM[R[rs] + \text{sign_ext}(Imm16)]$$

 
- STEP 2: Read source operands from register file



Single-Cycle Datapath: lw immediate

$$R[rt] \leftarrow DMEM[R[rs] + \text{sign_ext}(Imm16)]$$


- STEP 3: Sign-extend the immediate

 

Single-Cycle Datapath: lw address

$$R[rt] \leftarrow DMEM[R[rs] + \text{sign_ext}(Imm16)]$$


- STEP 4: Compute the memory address

 

Single-Cycle Datapath: lw memory read

$$R[rt] \leftarrow DMEM[R[rs] + \text{sign_ext}(Imm16)]$$

 
- STEP 5: Read data from memory and write it back to register file



Single-Cycle Datapath: 1w PC increment

- STEP 6: Determine the address of the next instruction


$$\text{PC} \leftarrow \text{PC} + 4$$

 

Single-Cycle Datapath: sw


$DMEM[R[rs] + \text{sign_ext}(Imm16)] \leftarrow R[rt]$

- Write data in rt to memory

 

Single-Cycle Datapath: R-type instructions

 - Read from **rs** and **rt** $R[rd] \leftarrow R[rs] \text{ op } R[rt]$
- Write *ALUResult* to register file
- Write to **rd** (instead of **rt**)




Single-Cycle Datapath: `beq`


`if (R[rs] == R[rt]) then PC \leftarrow PC + 4 + {sign_ext(Imm16), 00}`

- Determine whether values in `rs` and `rt` are equal
- Calculate branch target address:

 
$$\text{BTA} = (\text{sign-extended immediate} \ll 2) + (\text{PC}+4)$$



Complete Single-Cycle Processor

 


Review: ALU

 

$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \sim B$
110	$A - B$
111	SLT

Control Unit

 


Control Unit: ALU Decoder

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	XXXXXX	010 [Add]
X1	XXXXXX	110 [Subtract]
1X	100000 (add)	010 [Add]
1X	100010 (sub)	110 [Subtract]
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)


Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000							
lw	100011							
sw	101011							
beq	000100							

 


Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

 


Single-Cycle Datapath Example: or

 

Extended Functionality: addi

- No change to datapath

 


Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000							

Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000	1	0	1	0	0	0	00

Extended Functionality: j

 

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000100								

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	0	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	0	0
sw	101011	0	X	1	0	1	X	0	0
beq	100	0	X	0	1	0	X	1	0
j	100	0	X	X	X	0	X	XX	1


Review: Processor Performance

Program Execution Time

$$\begin{aligned} &= (\# \text{ instructions})(\text{cycles/instruction})(\text{seconds/cycle}) \\ &= \# \text{ instructions} \times \text{CPI} \times T_C \end{aligned}$$

Single-Cycle Performance

 - T_C is limited by the critical path (**lw**)



Single-Cycle Performance

- Single-cycle critical path:

$$T_c = t_{pcq_PC} + t_{\text{mem}} + \max(t_{RF\text{read}}, t_{\text{sext}} + t_{\text{mux}}) + t_{\text{ALU}} + t_{\text{mem}} + t_{\text{mux}} + t_{RF\text{setup}}$$

- In most implementations, limiting paths are:
 - memory, ALU, register file.
 - $T_c = t_{pcq_PC} + 2t_{\text{mem}} + t_{RF\text{read}} + t_{\text{mux}} + t_{\text{ALU}} + t_{RF\text{setup}}$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	$t_{RF\text{read}}$	150
Register file setup	$t_{RF\text{setup}}$	20

$$T_c =$$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	$t_{RF\text{read}}$	150
Register file setup	$t_{RF\text{setup}}$	20

$$\begin{aligned}T_c &= t_{pcq_PC} + 2t_{\text{mem}} + t_{RF\text{read}} + t_{\text{mux}} + t_{\text{ALU}} + t_{RF\text{setup}} \\&= [30 + 2(250) + 150 + 25 + 200 + 20] \text{ ps} \\&= 925 \text{ ps}\end{aligned}$$

Single-Cycle Performance Example

- For a program with 100 billion instructions executing on a single-cycle MIPS processor,

Execution Time =

Single-Cycle Performance Example

- For a program with 100 billion instructions executing on a single-cycle MIPS processor,


$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(925 \times 10^{-12} \text{ s}) \\ &= 92.5 \text{ seconds}\end{aligned}$$

Pipelined MIPS Processor


- Temporal parallelism
- Divide single-cycle processor into 5 stages:
 - Fetch
 - Decode
 - Execute
 - Memory
 - Writeback
- Add pipeline registers between stages

Single-Cycle vs. Pipelined Performance


Single-Cycle

 

Pipelined

 


Single-Cycle and Pipelined Datapath

 


Corrected Pipelined Datapath

 - WriteReg must arrive at the same time as Result



Pipelined Control

 

Same control unit as single-cycle processor

Pipeline Hazards

- Occurs when an instruction depends on results from previous instruction that hasn't completed.
- Types of hazards:
 - **Data hazard:** register value not written back to register file yet
 - **Control hazard:** next instruction not decided yet (caused by branches)

Pipelining Abstraction

