


**EECS150 - Digital Design**  
**Lecture 17 - Finite State Machines**  
**Revisited**

March 13, 2012


John Wawrzynek
 
# Finite State Machines (FSMs)



- FSM circuits are a type of *sequential circuit*:
  - output depends on present *and* past inputs
    - effect of past inputs is represented by the current *state*



 - Behavior is represented by *State Transition Diagram*:
  - traverse one edge per clock cycle.



# FSM Implementation

 
 


- Flip-flops form *state register*
- number of states  $\leq 2^{\text{number of flip-flops}}$
- CL (combinational logic) calculates next state and output
- **Remember: The FSM follows exactly one edge per cycle.**

So far we have learned how to implement in Verilog. Now we learn how to design "by hand" to the gate level.




# Formal Design Process

  
 
## “State Transition Diagram”


- circuit is in one of two “states”.
- transition on each cycle with each new input, over exactly one arc (edge).
- Output depends on which state the circuit is in.



# Formal Design Process

State Transition Table:

present state	OUT	IN	next state
EVEN	0	0	EVEN
EVEN	0	1	ODD
ODD	1	0	ODD
ODD	1	1	EVEN

 

Invent a code to represent states:

Let 0 = EVEN state, 1 = ODD state

present state (ps)	OUT	IN	next state (ns)
0	0	0	0
0	0	1	1
1	1	0	1
1	1	1	0

Derive logic equations from table (how?):

$$OUT = PS$$

$$NS = PS \text{ xor } IN$$

# Formal Design Process


Logic equations from table:

$$\text{OUT} = \text{PS}$$

$$\text{NS} = \text{PS} \text{ xor } \text{IN}$$

- Circuit Diagram:

 - XOR gate for NS calculation
- DFF to hold present state
- no logic needed for output in this example.



# Formal Design Process

Review of Design Steps:


1. Specify **circuit function** (English)
2. Draw **state transition diagram**
3. Write down **symbolic state transition table**
4. Write down **encoded state transition table**
5. Derive **logic equations**
6. Derive **circuit diagram**

Register to hold state

Combinational Logic for Next State and Outputs




# Combination Lock Example

 

- Used to allow entry to a locked room:  
2-bit serial combination. Example 01,11:
  1. Set switches to 01, press ENTER
  2. Set switches to 11, press ENTER
  3. OPEN is asserted (OPEN=1).If wrong code, ERROR is asserted (after second combo word entry).  
Press Reset at anytime to try again.


# Combinational Lock STD

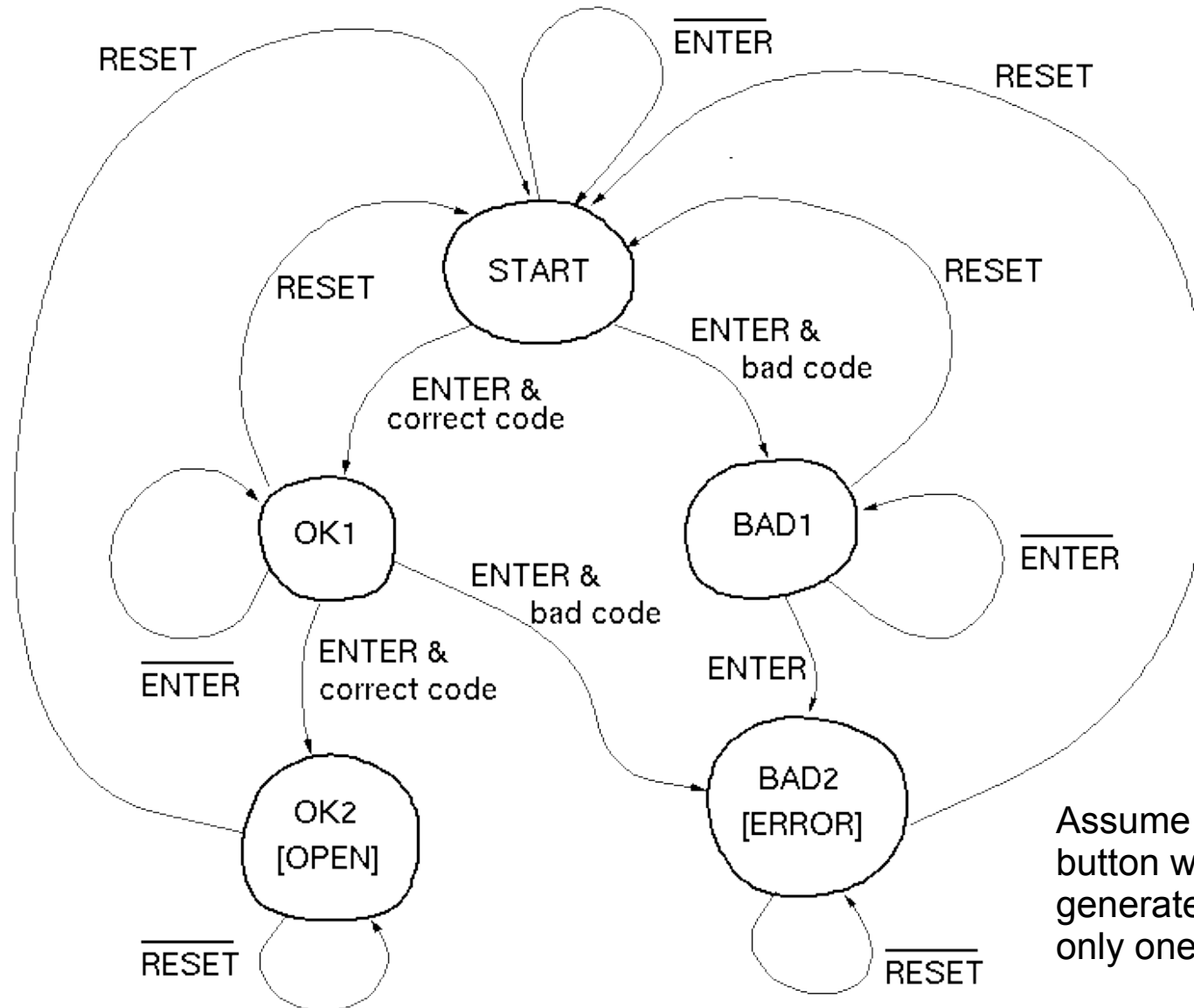

# Symbolic State Transition Table

RESET	ENTER	COM1	COM2	Preset State	Next State	OPEN	ERROR
0	0	*	*	START	START	0	0
0	1	0	*	START	BAD1	0	0
0	1	1	*	START	OK1	0	0
0	0	*	*	OK1	OK1	0	0
0	1	*	0	OK1	BAD2	0	0
0	1	*	1	OK1	OK2	0	0
0	*	*	*	OK2	OK2	1	0
0	0	*	*	BAD1	BAD1	0	0
0	1	*	*	BAD1	BAD2	0	0
0	*	*	*	BAD2	BAD2	0	1
1	*	*	*	*	START	0	0

 
Decoder logic for checking combination (01,11):



ENTER	COM1	COM2	PS2	PS1	PS0	NS2	NS1	NS0
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0
1	0	0	0	0	0	1	0	0
1	0	1	0	0	0	1	0	0
1	1	0	0	0	0	0	0	1
1	1	1	0	0	0	0	0	1
0	0	0	0	0	1	0	0	1
0	0	1	0	0	1	0	0	1
0	1	0	0	0	1	0	0	1
0	1	1	0	0	1	0	0	1
1	0	0	0	0	1	1	0	1
1	1	0	0	0	1	1	0	1
1	0	1	0	0	1	0	1	1
1	1	1	0	0	1	0	1	1
0	0	0	0	1	1	0	1	1
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	0	1	1	0	1	1
1	0	0	0	1	1	0	1	1
1	0	1	0	1	1	0	1	1
1	1	0	0	1	1	0	1	1
1	1	1	0	1	1	0	1	1
0	0	0	1	0	0	1	0	0
0	0	1	1	0	0	1	0	0
0	1	0	1	0	0	1	0	0
0	1	1	1	0	0	1	0	0
1	0	0	1	0	0	1	0	1
1	0	1	1	0	0	1	0	1
1	1	0	1	0	0	1	0	1
1	1	1	1	0	0	1	0	1
0	0	0	1	0	1	1	0	1
0	0	1	1	0	1	1	0	1
0	1	0	1	0	1	1	0	1
0	1	1	1	0	1	1	0	1
1	0	0	1	0	1	1	0	1
1	0	1	1	0	1	1	0	1
1	1	0	1	0	1	1	0	1
1	1	1	1	0	1	1	0	1

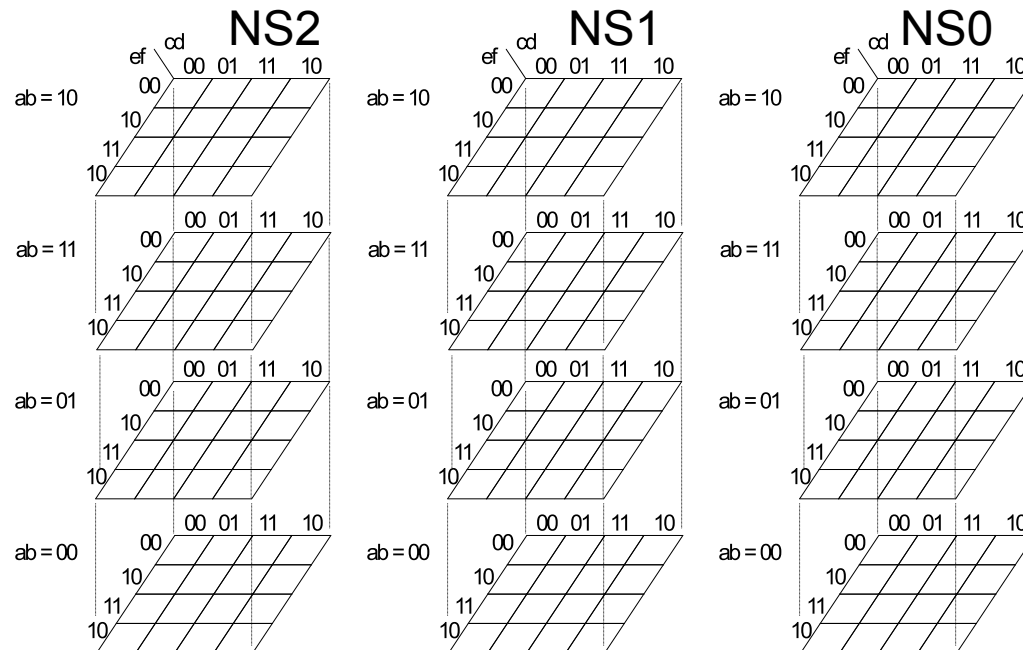
# Encoded ST Table

- Assign states:  
START=000, OK1=001, OK2=011  
BAD1=100, BAD2=101
- Omit reset. Assume that primitive flip-flops has reset input.
- Rows not shown have *don't cares* in output. Correspond to invalid PS values.



- What are the output functions for OPEN and ERROR?

# State Encoding

 

- In general:

# of possible FSM state =  $2^{\# \text{ of Flip-flops}}$

Example:


state1 = 01, state2 = 11, state3 = 10, state4 = 00

- However, often more than  $\log_2(\# \text{ of states})$  FFs are used, to simplify logic at the cost of more FFs.
- Extreme example is one-hot state encoding.

# State Encoding

- **One-hot encoding of states.**
- One FF per state.



Ex: 3 States

 

- Why one-hot encoding?
  - Simple design procedure.
    - Circuit matches state transition diagram (example next page).
  - Often can lead to simpler and faster “next state” and output logic.
- Why not do this?
  - Can be costly in terms of Flip-flops for FSMs with large number of states.
- FPGAs are “Flip-flop rich”, therefore one-hot state machine encoding is often a good approach.


# One-hot encoded FSM

- Even Parity Checker Circuit:

  



Circuit generated through direct inspection of the STD.

- In General:

 

- FFs must be initialized for correct operation (only one 1)


# One-hot encoded combination lock

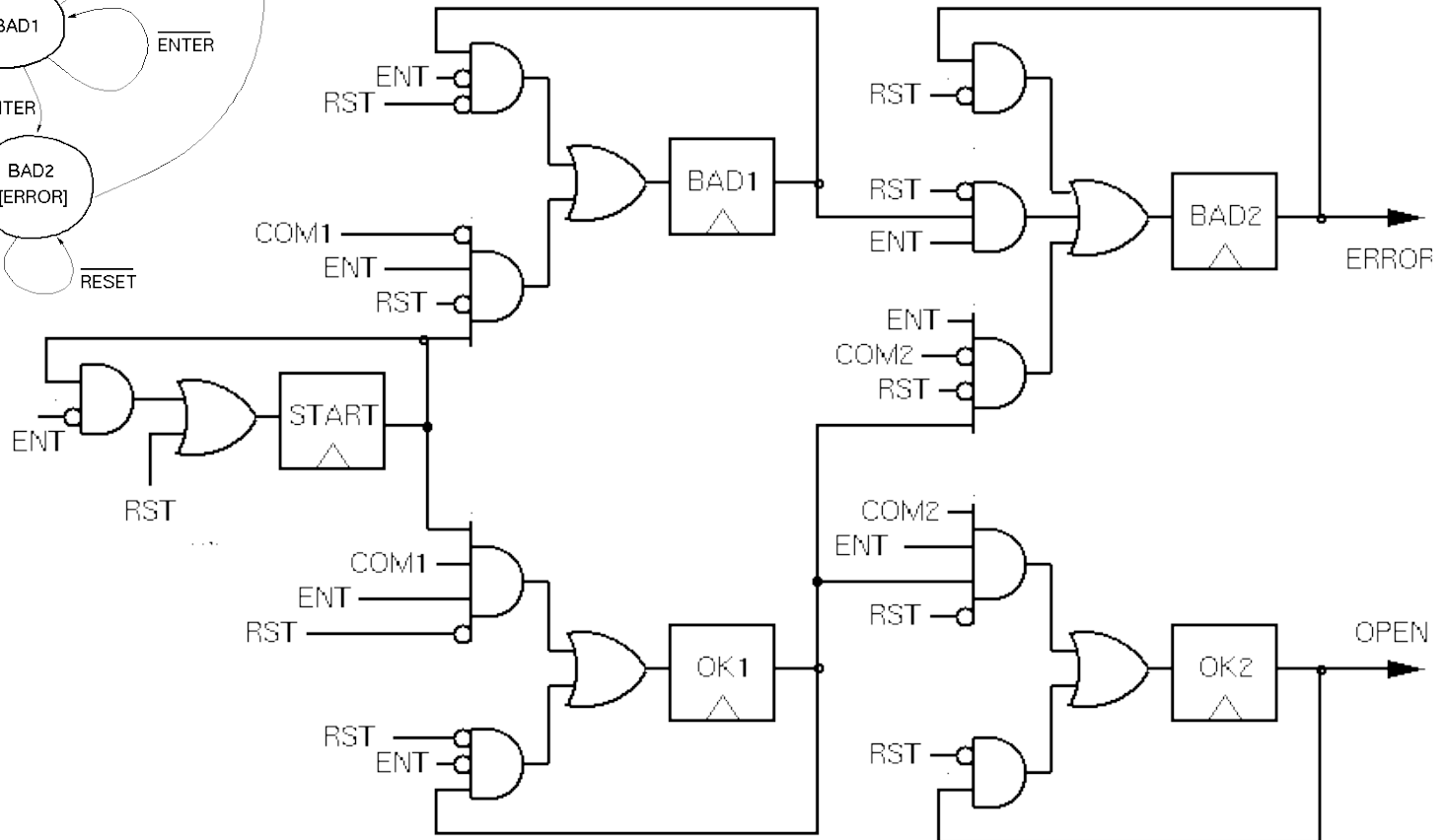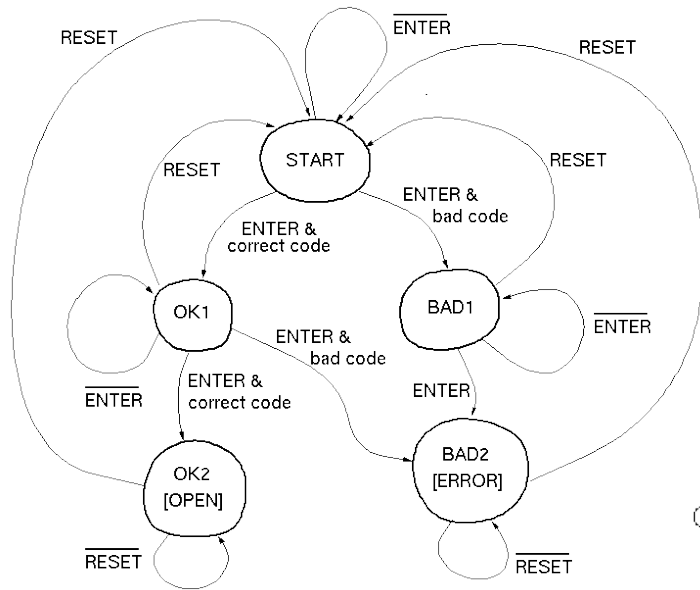




# FSM Implementation Notes

- General FSM form:

 

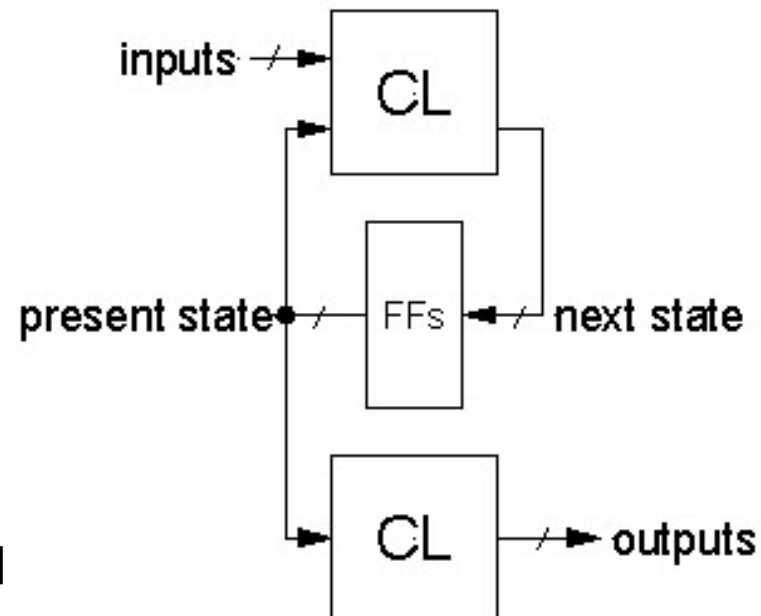- All examples so far generate output based only on the present state:




- Commonly name **Moore Machine**  
(If output functions include both present state and input then called a **Mealy Machine**)

# Finite State Machines

 - **Example: Edge Detector**


Bits are received one at a time (one per cycle),  
such as: 000111010  $\longrightarrow$  *time*

Design a circuit that asserts  
its output for one cycle when  
the input bit stream changes  
from 0 to 1.



Try two different solutions.

# State Transition Diagram Solution A

 


	IN	PS	NS	OUT
ZERO	0	00	00	0
	1	00	01	0
CHANGE	0	01	00	1
	1	01	11	1
ONE	0	11	00	0
	1	11	11	0

# Solution A, circuit derivation

	IN	PS	NS	OUT
ZERO	0	00	00	0
	1	00	01	0
CHANGE	0	01	00	1
	1	01	11	1
ONE	0	11	00	0
	1	11	11	0

		PS				
		00	01	11	10	
IN	0	0	0	0	-	$NS_1 = IN PS_0$
	1	0	1	1	-	


		PS				
		00	01	11	10	
IN	0	0	0	0	-	$NS_0 = IN$
	1	1	1	1	-	

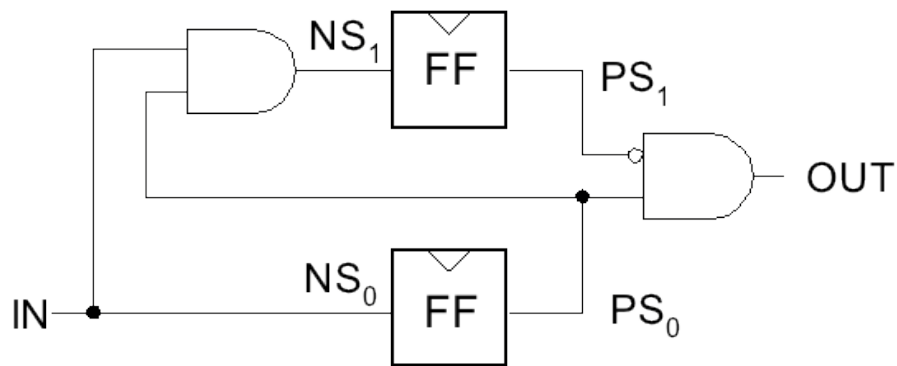

		PS				
		00	01	11	10	
IN	0	0	1	0	-	$OUT = \overline{PS_1} PS_0$
	1	0	1	0	-	
 
# Solution B


*Output depends not only on PS but also on input, IN*



Let ZERO=0,  
ONE=1


IN	PS	NS	OUT
0	0	0	0
0	1	0	0
1	0	1	1
1	1	1	0

NS = IN, OUT = IN PS'

 

What's the *intuition* about this solution?

# Edge detector timing diagrams

 

- Solution A: output follows the clock
- Solution B: output changes with input rising edge and is asynchronous wrt the clock.

# FSM Comparison

## *Solution A*


### **Moore Machine**

- output function only of PS
- maybe more states (why?)
- synchronous outputs
  - no glitches
  - one cycle “delay”
  - full cycle of stable output

## *Solution B*
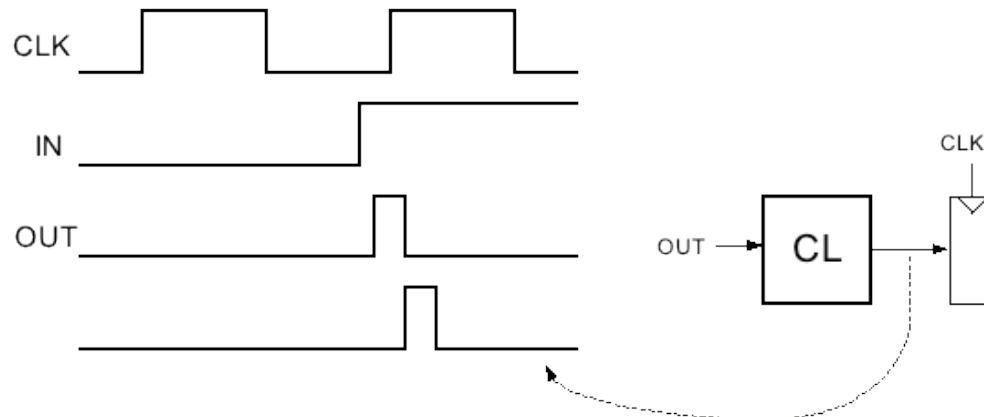
### **Mealy Machine**


- output function of both PS & input
- maybe fewer states
- asynchronous outputs
  - if input glitches, so does output
  - output immediately available
  - output may not be stable long enough to be useful (below):




If output of Mealy FSM goes through combinational logic before being registered, the CL might delay the signal and it could be missed by the clock edge.

# FSM Recap

## Moore Machine

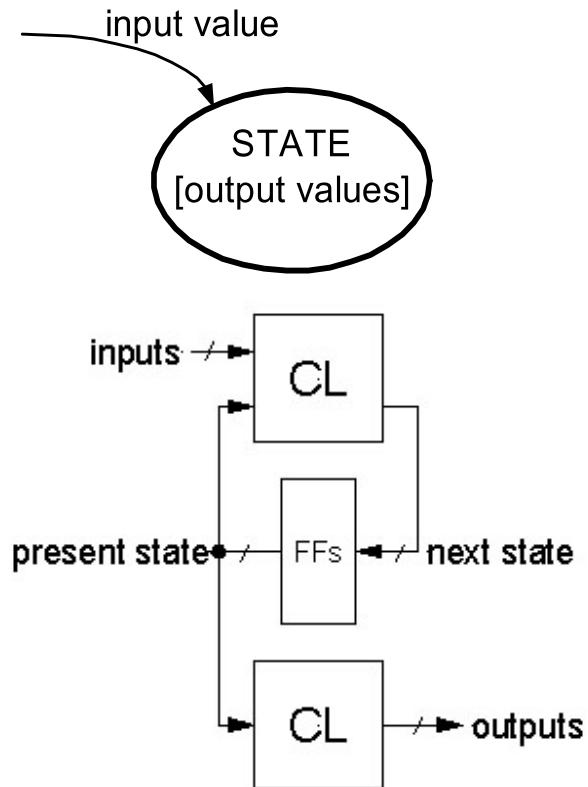

## Mealy Machine

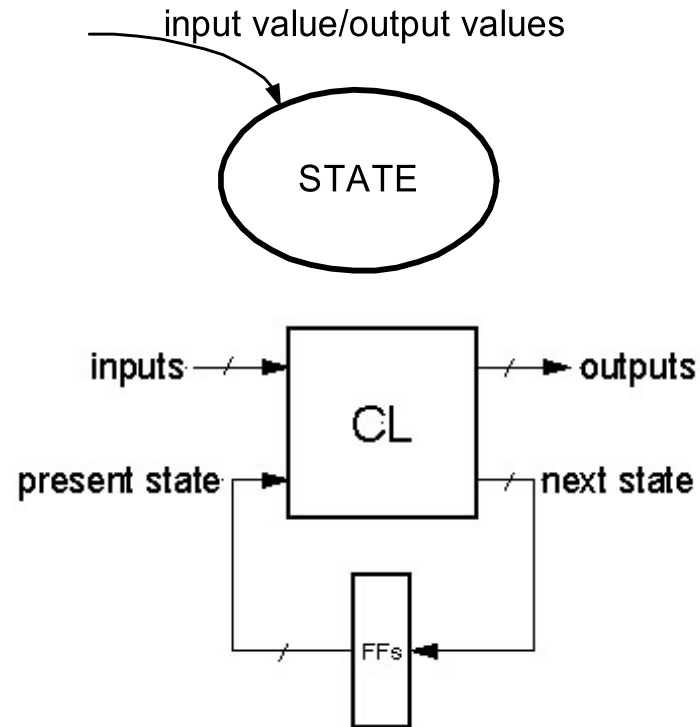


*Both machine types allow one-hot implementations.*



# Final Notes on Moore versus Mealy

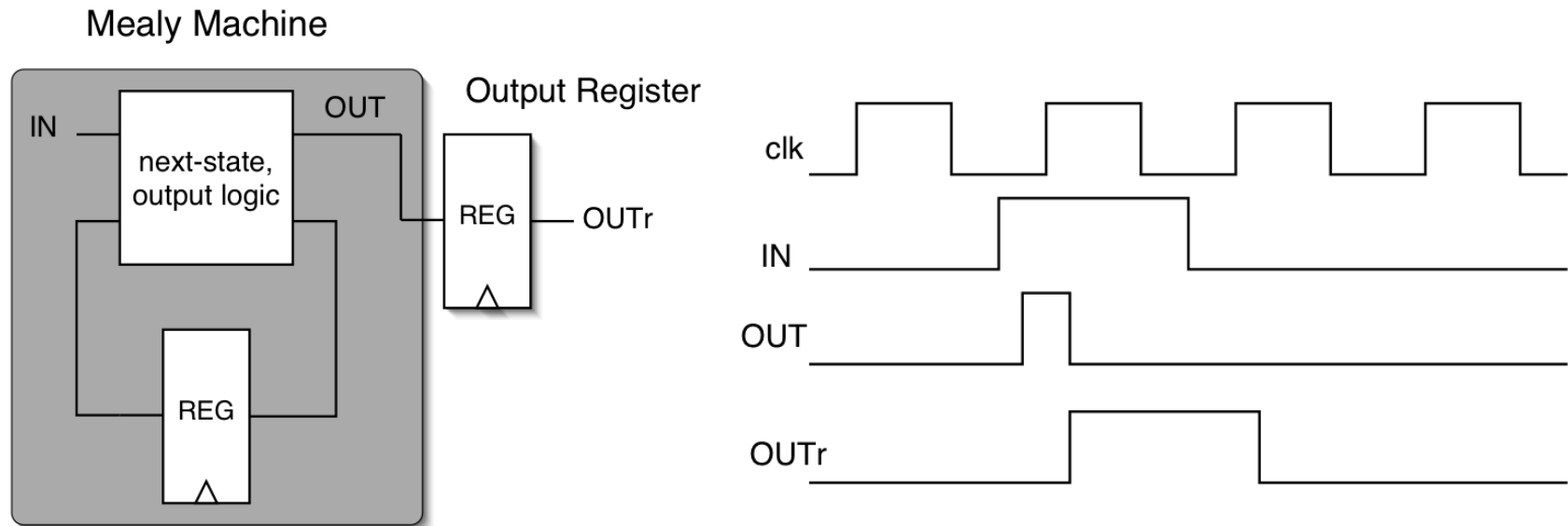1. A given state machine *could* have *both* Moore and Mealy style outputs. Nothing wrong with this, but you need to be aware of the timing differences between the two types.
2. The output timing behavior of the Moore machine can be achieved in a Mealy machine by “registering” the Mealy output values:




# General FSM Design Process with Verilog

## Design Steps: Implementation

1. Specify **circuit function** (English)
2. Draw **state transition diagram**
3. Write down **symbolic state transition table**
4. Assign encodings (bit patterns) to symbolic states
5. Code as Verilog behavioral description
  - ✓ Use parameters to represent encoded states.
  - ✓ Use separate always blocks for register assignment and CL logic block.
  - ✓ Use case for CL block. Within each case section assign all outputs and next state value based on inputs. *Note: For Moore style machine make outputs dependent only on state not dependent on inputs.*

# FSMs in Verilog


## Mealy Machine

 

```

always @(posedge clk)
    if (rst) ps <= ZERO;
    else ps <= ns;
always @(ps in)
    case (ps)
    ZERO: if (in) begin
            out = 1'b1;
            ns = ONE;
        end
        else begin
            out = 1'b0;
            ns = ZERO;
        end
    ONE: if (in) begin
            out = 1'b0;
            ns = ONE;
        end
        else begin
            out = 1'b0;
            ns = ZERO;
        end
    default: begin
            out = 1'bx;
            ns = default;
        end
    end
  
```

## Moore Machine

 

```

always @(posedge clk)
    if (rst) ps <= ZERO;
    else ps <= ns;
always @(ps in)
    case (ps)
    ZERO: begin
            out = 1'b0;
            if (in) ns = CHANGE;
            else ns = ZERO;
        end
    CHANGE: begin
            out = 1'b1;
            if (in) ns = ONE;
            else ns = ZERO;
        end
    ONE: begin
            out = 1'b0;
            if (in) ns = ONE;
            else ns = ZERO;
        end
    default: begin
            out = 1'bx;
            ns = default;
        end
    end
  
```