
CS 150

Digital Design

Lecture 12 – DRAM

2012-2-23

Professor John Wawrzynek

today's lecture by John Lazzaro


TAs: Shaoyi Cheng, Daiwei Li, James Parker

www-inst.eecs.berkeley.edu/~cs150/



Today's Lecture: DRAM

* DRAM, Xilinx, and You

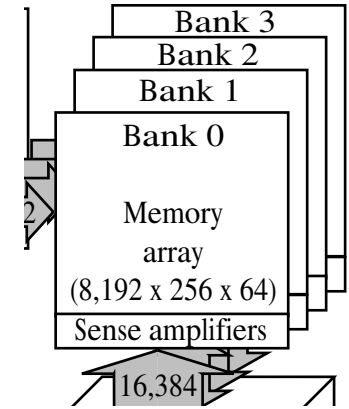

* DRAM: Bottom-up





* DRAM: Top-down




DDR2 SO-DIMM on ML505 Board

DDR2: Double-Data Rate, 2nd generation





 
 


SO-DIMM: Small-Outline,
Dual Inline Memory Module

DDR2 SO-DIMM Module

 

CS 150 L12: DRAM

     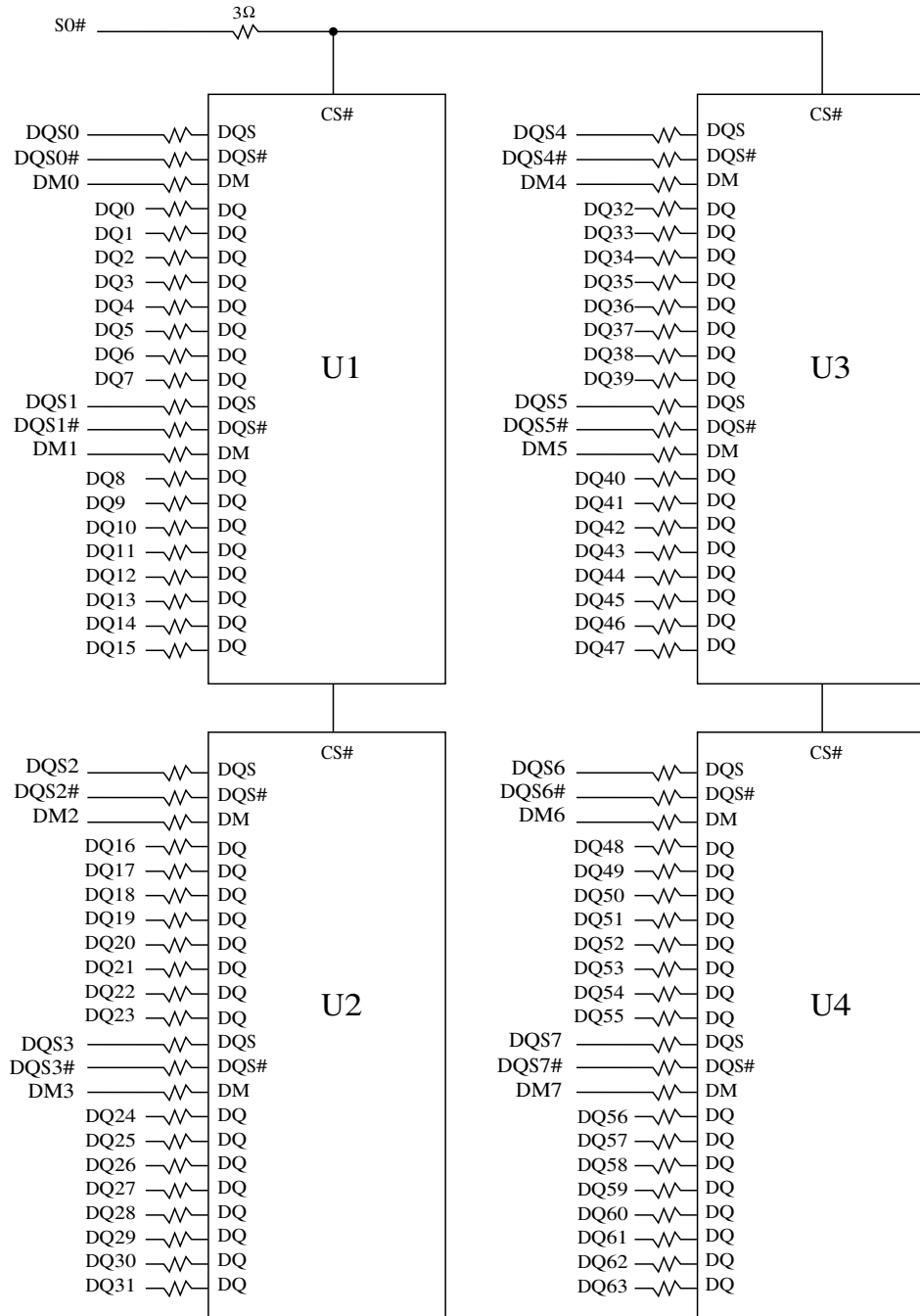


DRAM chips are wired in parallel and run in lockstep.

Project controller: Xilinx-supplied IP

Your project's Verilog code sees a FIFO R/W interface.

Xilinx IP translates FIFO requests to DRAM commands.

DDR2 SO-DIMM

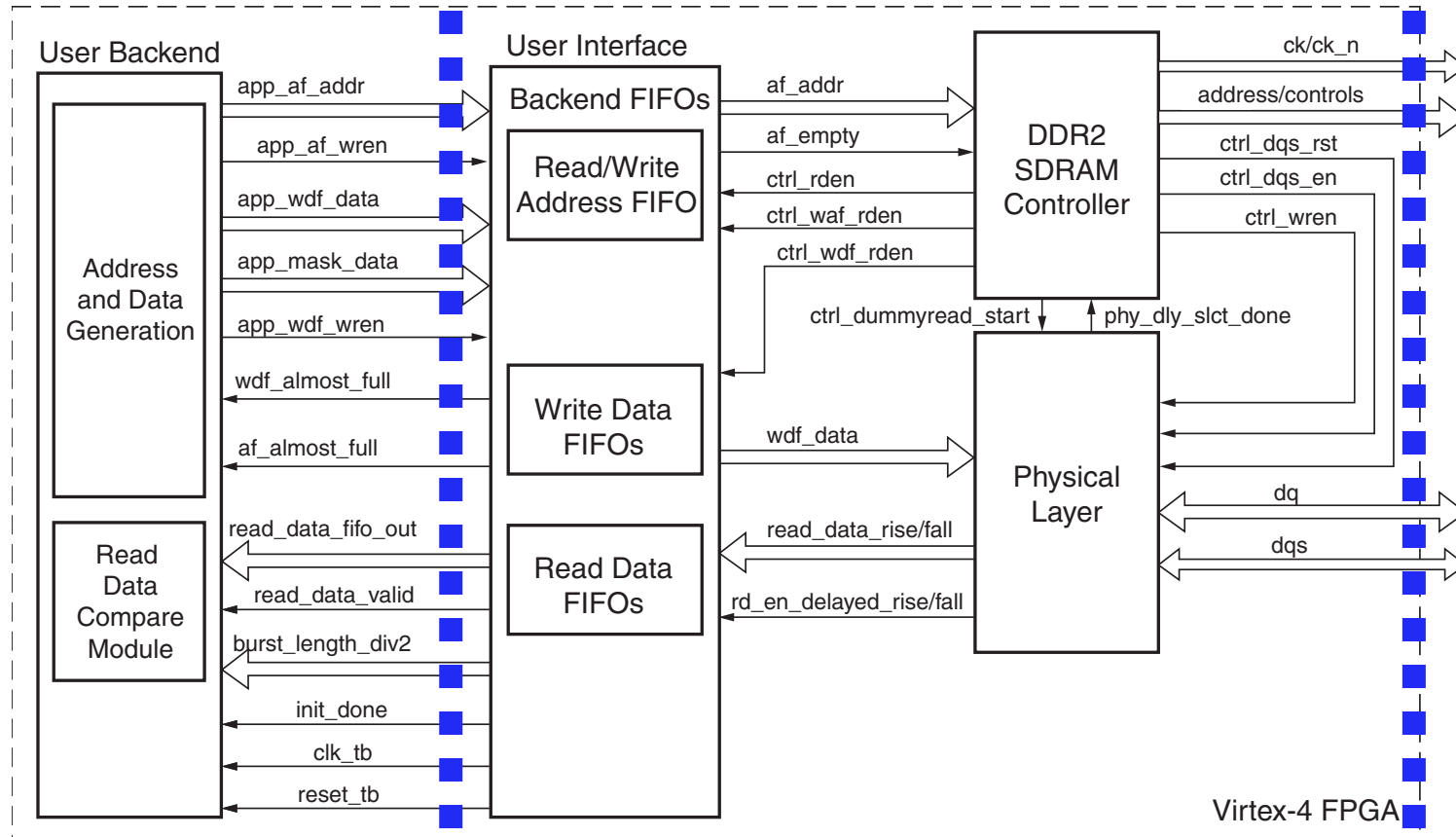

UG086_c3_07_091508

Today's Lecture: DRAM

* DRAM, Xilinx, and You

* **DRAM: Bottom-up**

* DRAM: Top-down


To understand the DRAM controller, you need to understand how a DRAM chip works. Otherwise, it just seems like **magic.**



Capacitance




Recall: Building a capacitor

 

Recall: Capacitors in action

 Because the dielectric is an insulator, and does not conduct.



After circuit "settles" ...

$$Q = C V = C * 1.5 \text{ Volts (D cell)}$$


Q: Charge stored on capacitor

C: The capacitance of the device: function of device shape and type of dielectric.

After battery is removed:



$$\text{Still, } Q = C * 1.5 \text{ Volts}$$

Capacitor "remembers" charge

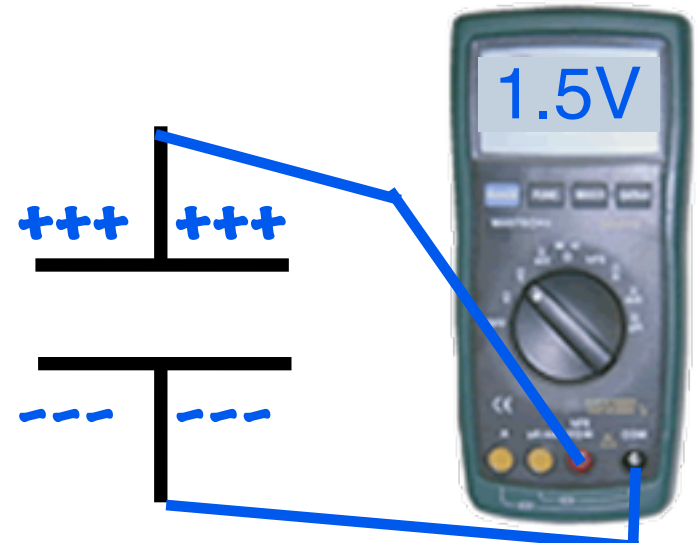

Storing computational state as charge

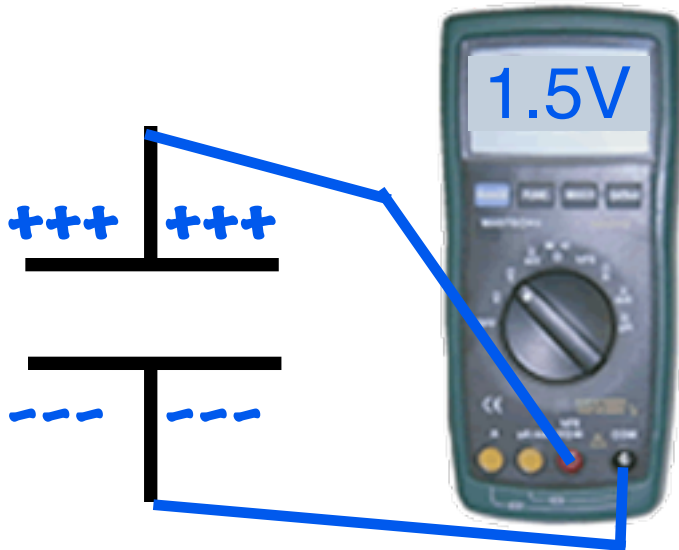 State is coded as the amount of **energy** stored by a device.



State is read by **sensing** the amount of energy

Problems: **noise** changes Q (up or down), **parasitics** leak or source Q . Fortunately, Q cannot change **instantaneously**, but that only gets us in the ballpark.

MOS Transistors

Two diodes and a capacitor in an interesting arrangement. So, we begin with a diode review ...





Diodes in action ...

Resistor



Light emitting diode (LED)

Light on?

  



Yes!

Light on?

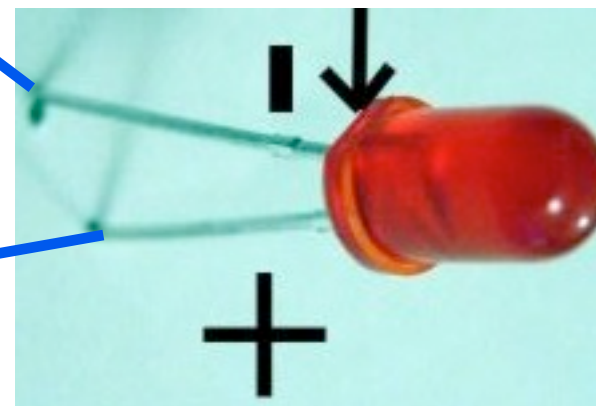 

No!

Diodes: Current vs Voltage

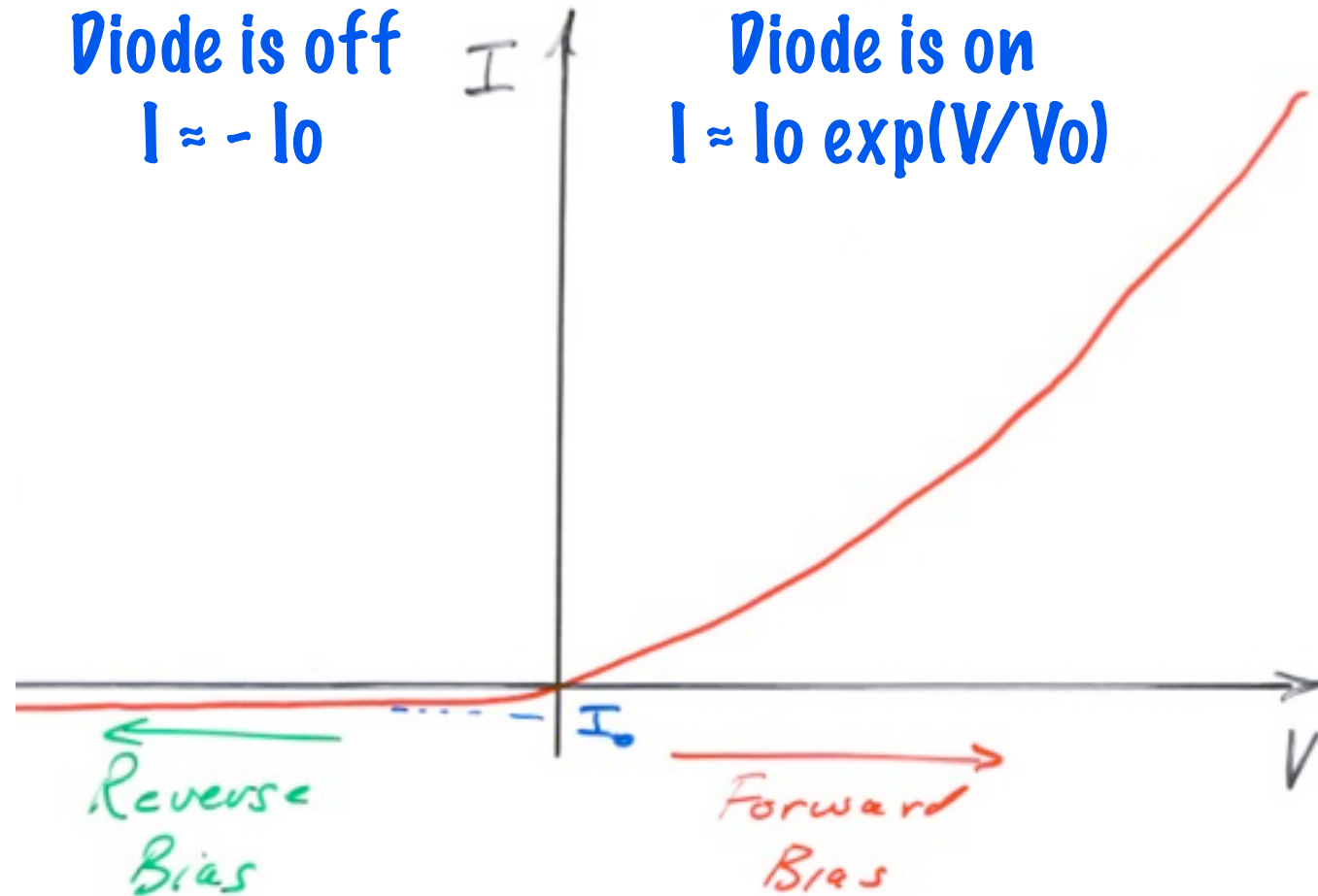
 


$$I = I_0 [\exp(V/V_0) - 1]$$


I_0 range: 1fA to 1nA

V_0 range: 25mV to 60 mV

How to make a silicon diode ...

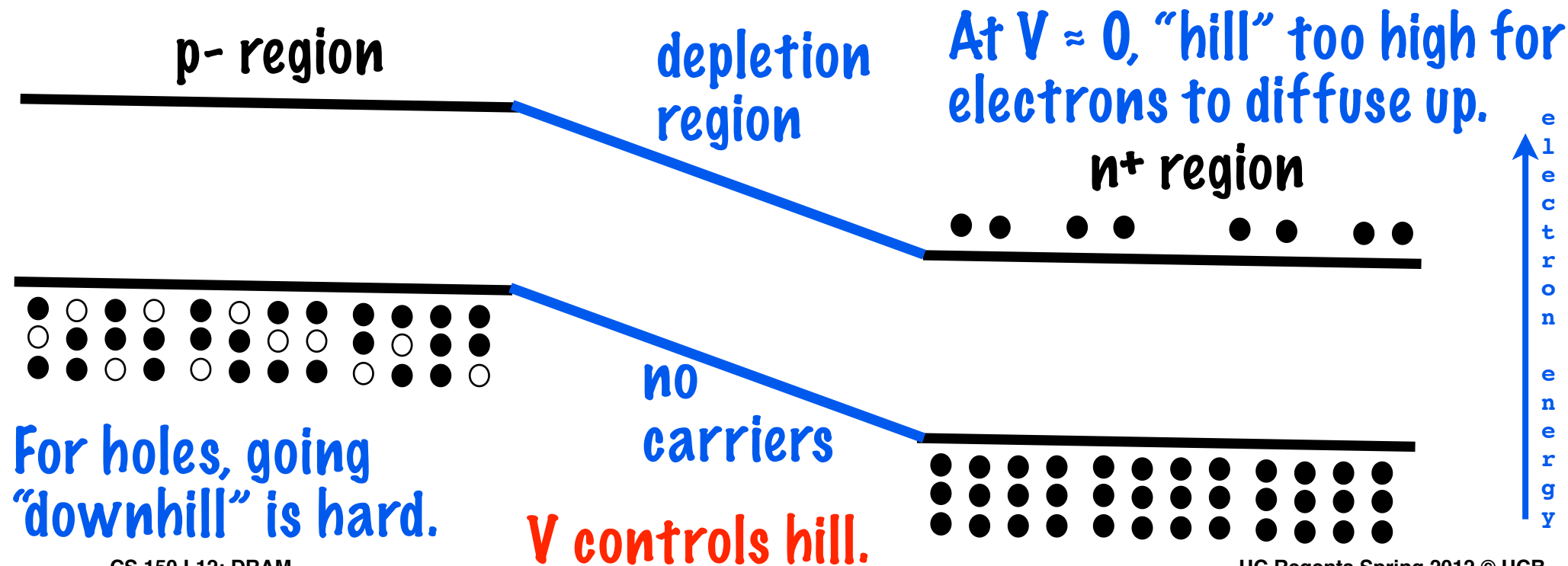 

Note: IC Diodes are biased “off”!

 

$V1, V2 > 0V$. Diodes “off”, only current is I_0 “leakage”.

$$I = I_0 [\exp(V/V_0) - 1]$$


Anodes of all diodes on wafer connected to ground.

MOS Transistors

Two diodes and a capacitor in an interesting arrangement ...





What we want: the perfect switch.

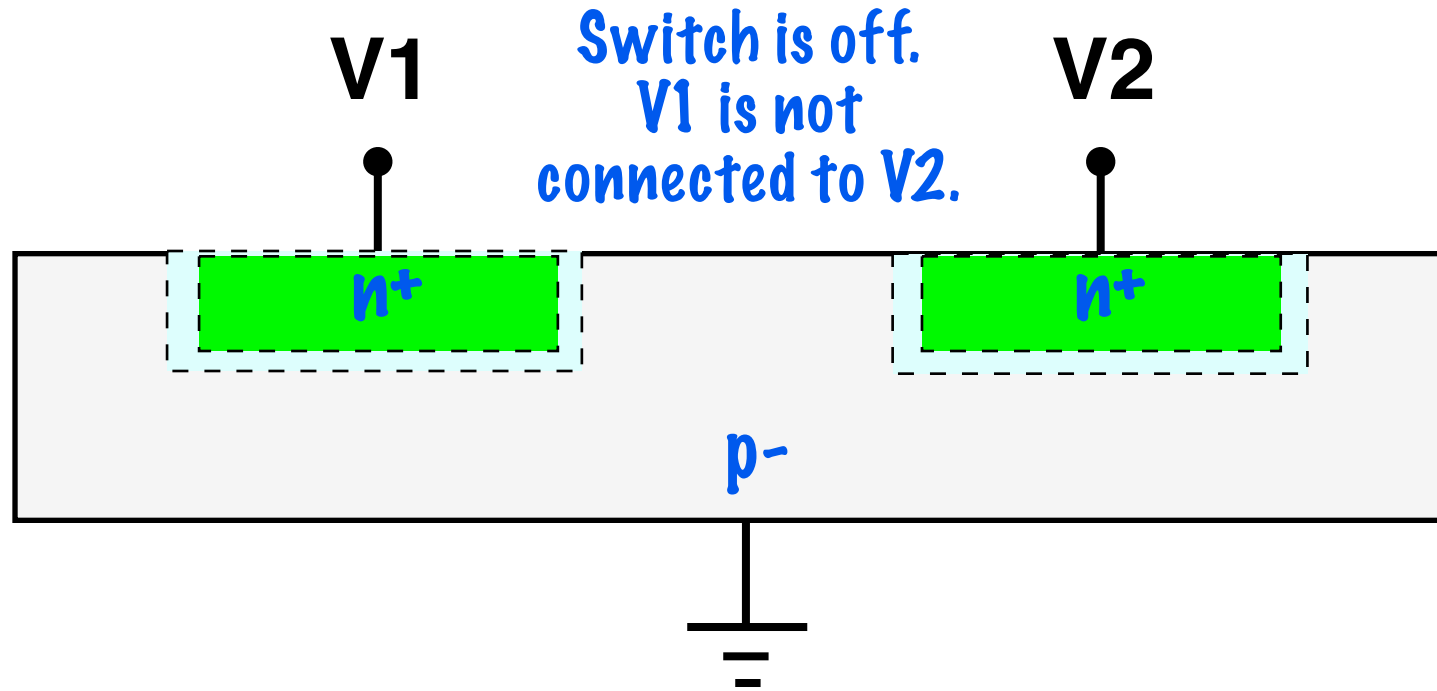


We want to turn a p-type region into an n-type region under voltage control.

 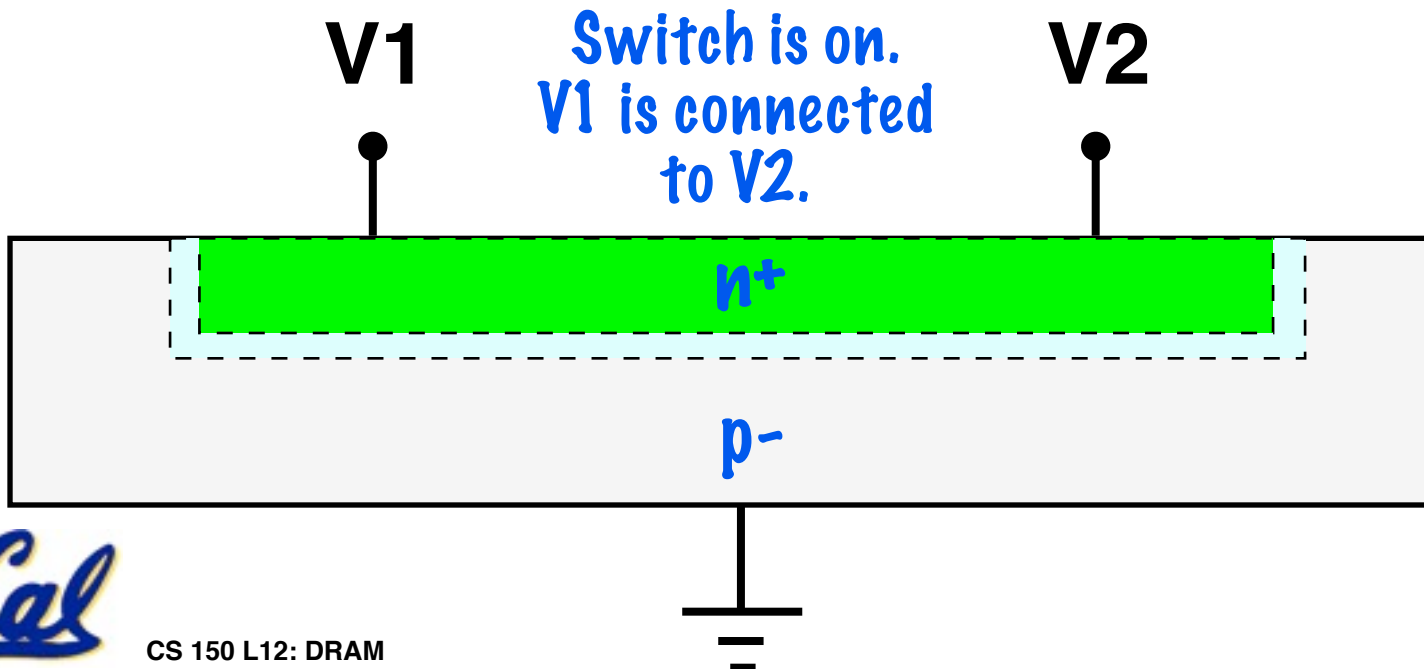We need electrons to fill valence holes and add conduction band electrons




An n-channel MOS transistor (nFET)

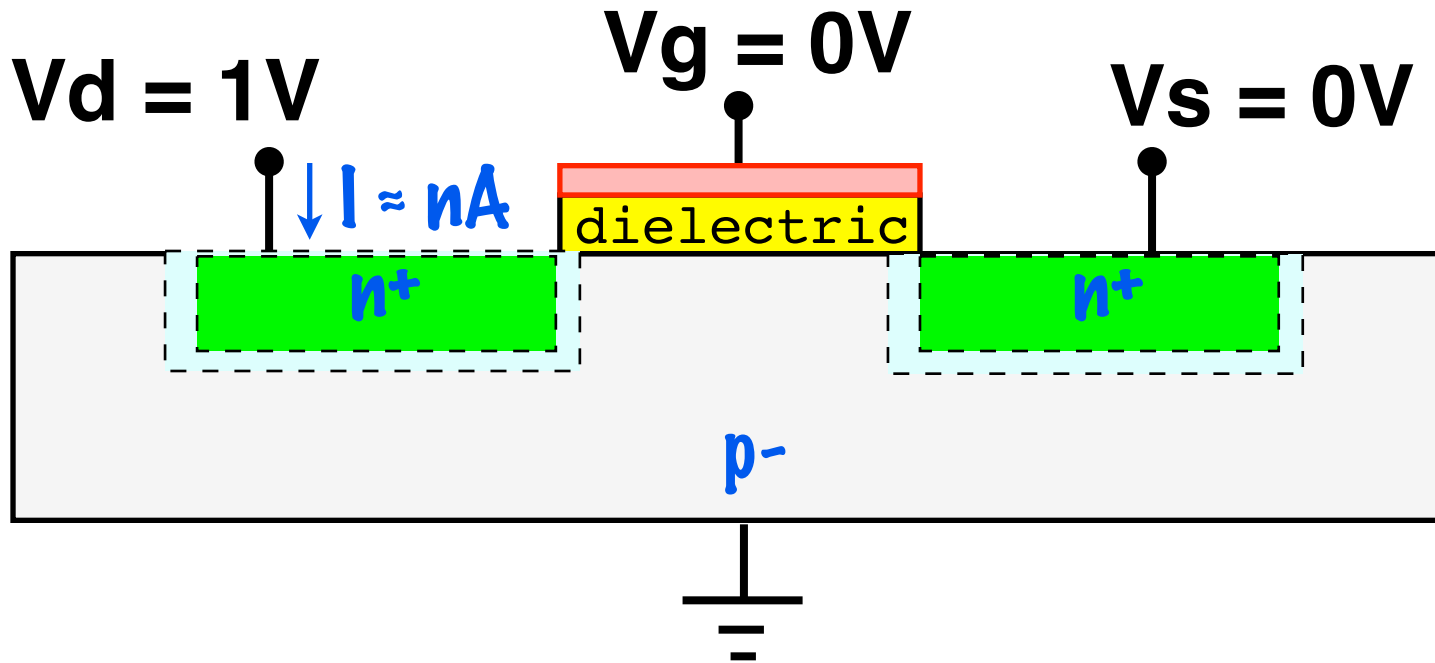

Polysilicon gate, dielectric, and substrate form a capacitor.


nFet is **off**
(I is "leakage")

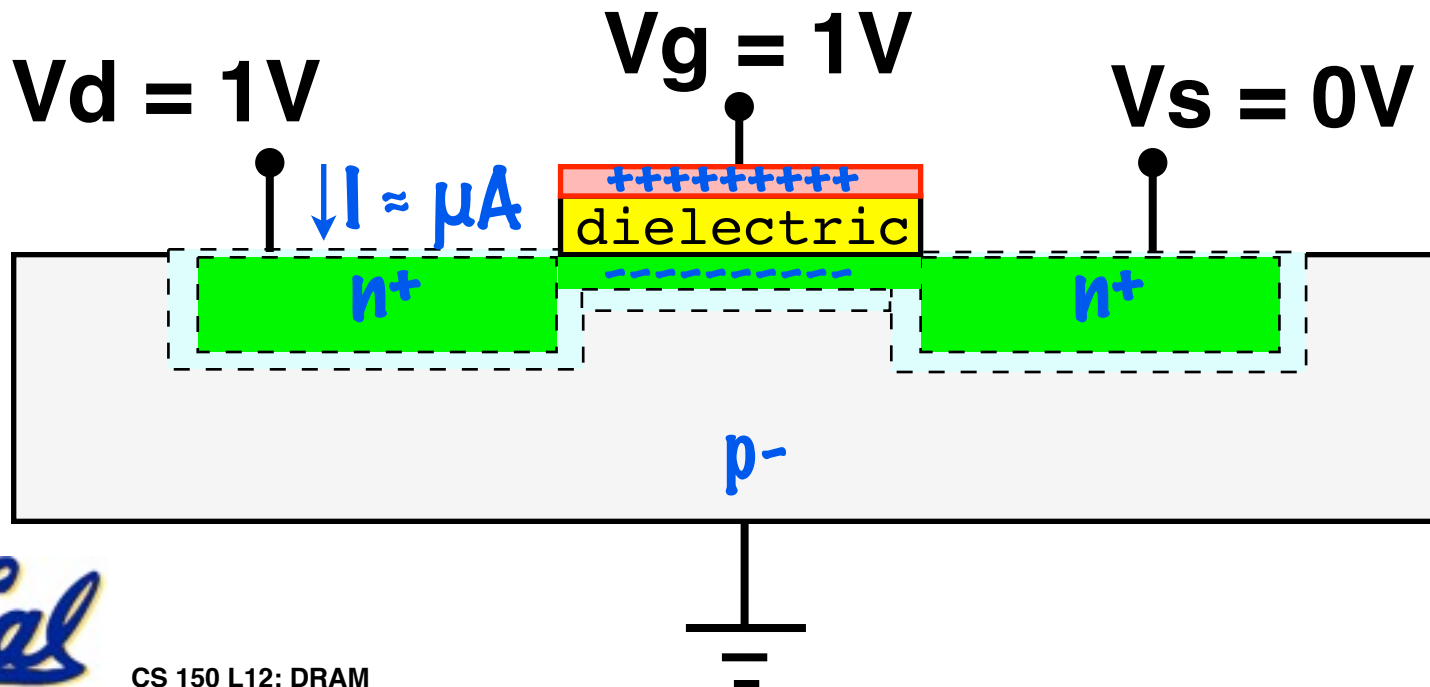


$V_g = 1V$, small region near the surface turns from p-type to n-type.

nFet is **on**

Mask set for an n-Fet (circa 1986)

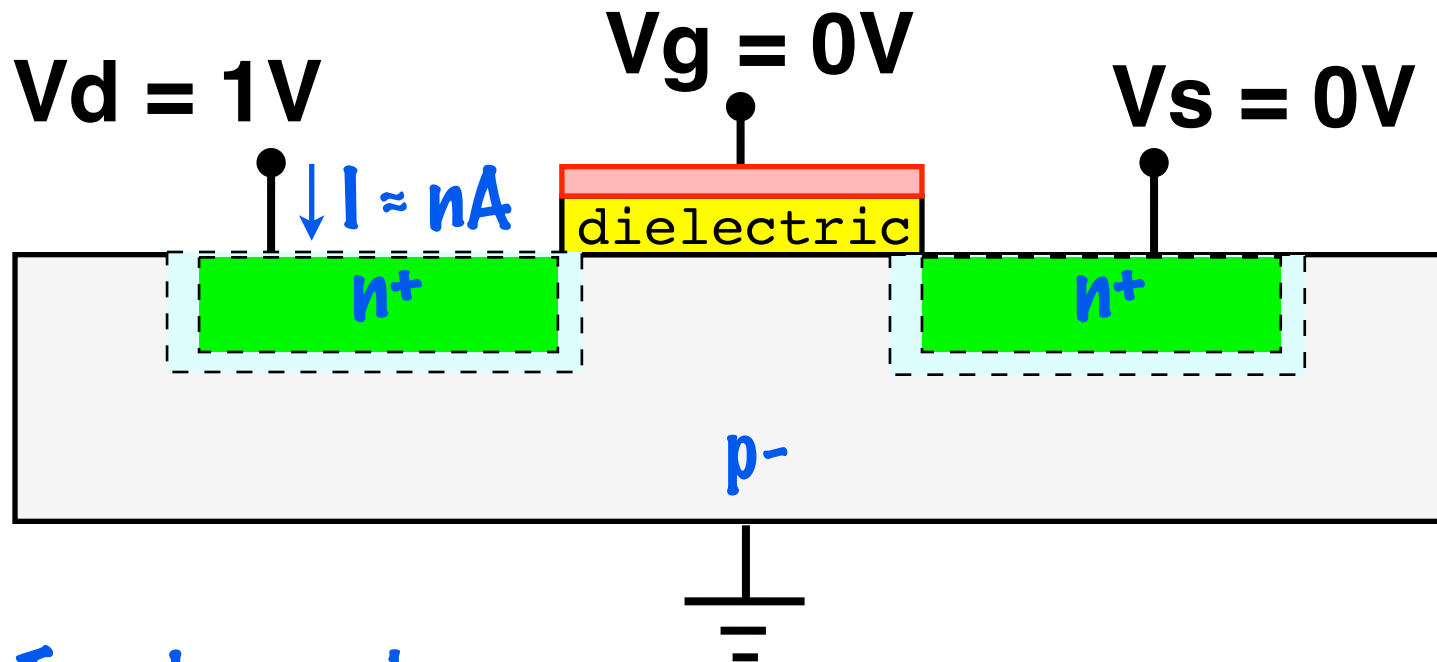

Top-down view:

 

Masks

- #1: n^+ diffusion
- #2: poly (gate)
- #3: diff contact
- #4: metal


Layers to do
p-Fet not shown.
Modern
processes have 6
to 10 metal
layers (or more)
(in 1986: 2).

Dynamic Memory Cells



Recall: Capacitors in action

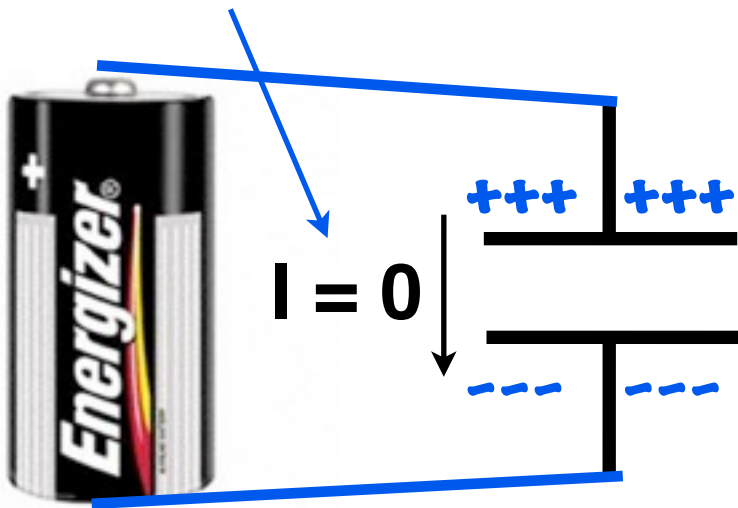Because the dielectric is an insulator, and does not conduct.



After circuit "settles" ...

$$Q = C V = C * 1.5 \text{ Volts (D cell)}$$


Q: Charge stored on capacitor

C: The capacitance of the device: function of device shape and type of dielectric.




After battery is removed:

$$\text{Still, } Q = C * 1.5 \text{ Volts}$$


Capacitor "remembers" charge

 

DRAM cell: 1 transistor, 1 capacitor

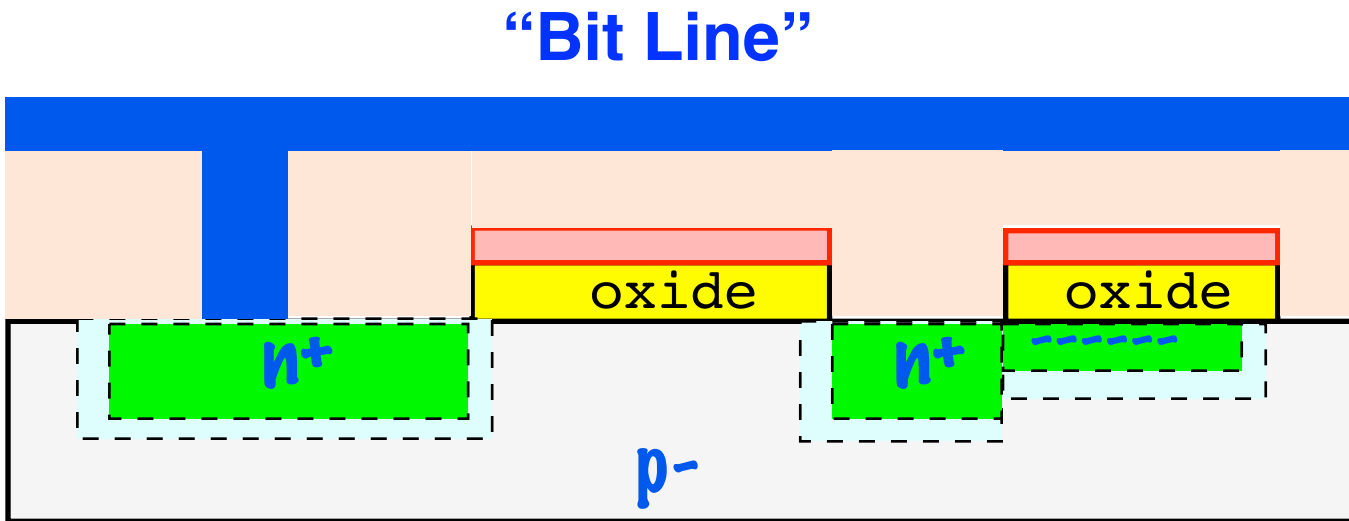 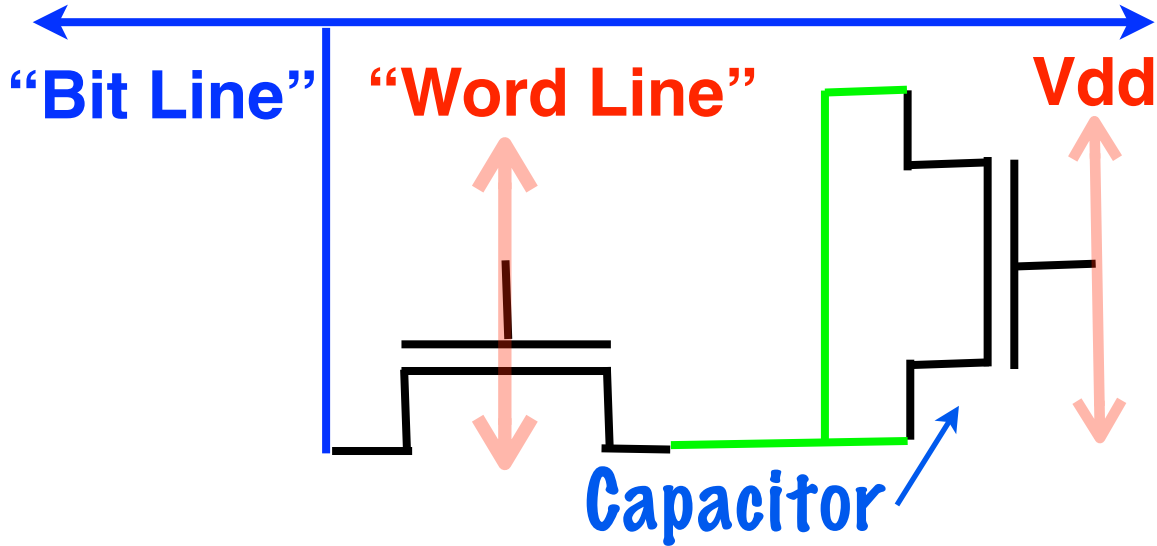


Why Vcap values start out at ground.

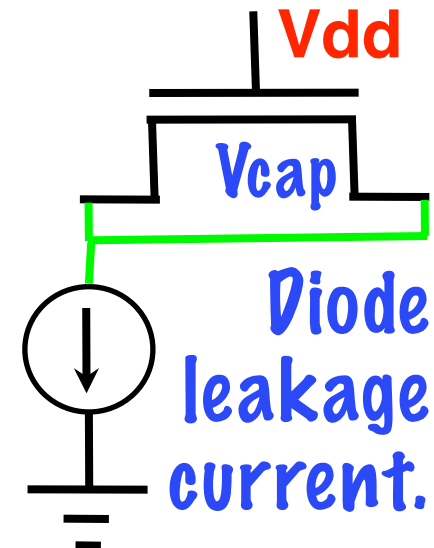

Word Line and Vdd run on “z-axis”



A 4 x 4 DRAM array (16 bits)

 

Invented after SRAM, by Robert Dennard

United States Patent Office

3,387,286

Patented June 4, 1968



1

3,387,286

FIELD-EFFECT TRANSISTOR MEMORY

Robert H. Dennard, Croton-on-Hudson, N.Y., assignor to International Business Machines Corporation, Armonk, N.Y., a corporation of New York

Filed July 14, 1967, Ser. No. 653,415

21 Claims. (Cl. 340-173)

2

5
 tinent in disclosing various concepts and structures which have been developed in the application of field-effect transistors to different types of memory applications, the primary thrust up to this time in conventional read-write random access memories has been to connect a plurality of field-effect transistors in each cell in a latch configuration. Memories of this type require a large number of active devices in each cell and therefore each cell re-

FIG. 1


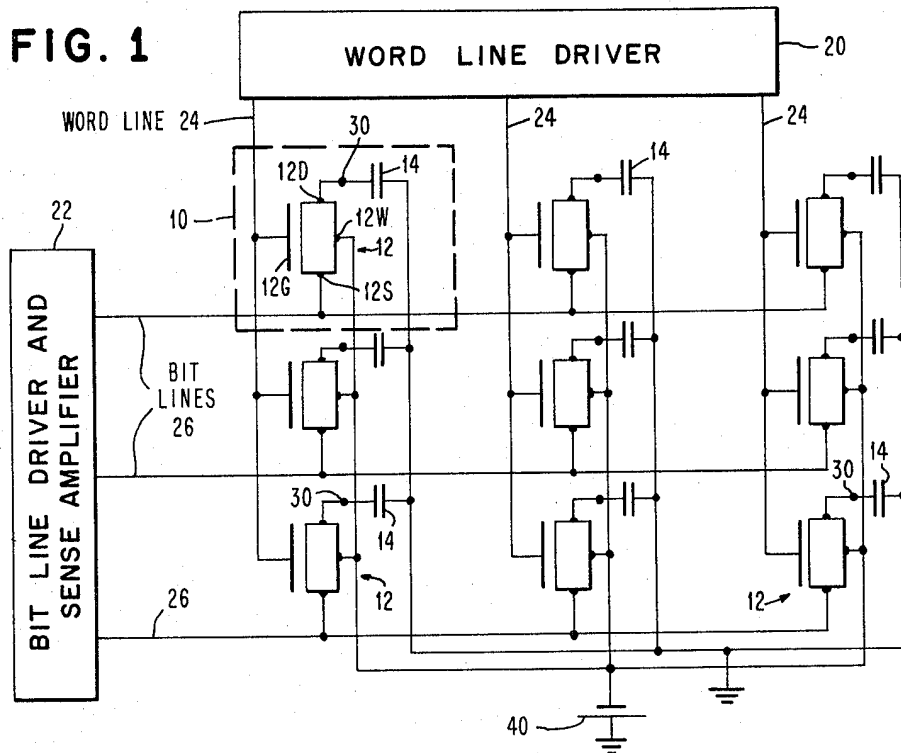



FIG. 2

 

INVENTOR
 ROBERT H. DENNARD

BY *John E. Long*
 ATTORNEY

DRAM Circuit Challenge #1: Writing


 


$V_{dd} - V_{th}$. Bad, we store less charge. Why do we not get V_{dd} ?

$I_{ds} = k [V_{gs} - V_{th}]^2$,
but "turns off" when $V_{gs} \leq V_{th}$!

$V_{gs} = V_{dd} - V_c$. When $V_{dd} - V_c = V_{th}$, charging effectively stops!


DRAM Challenge #2: Destructive Reads

 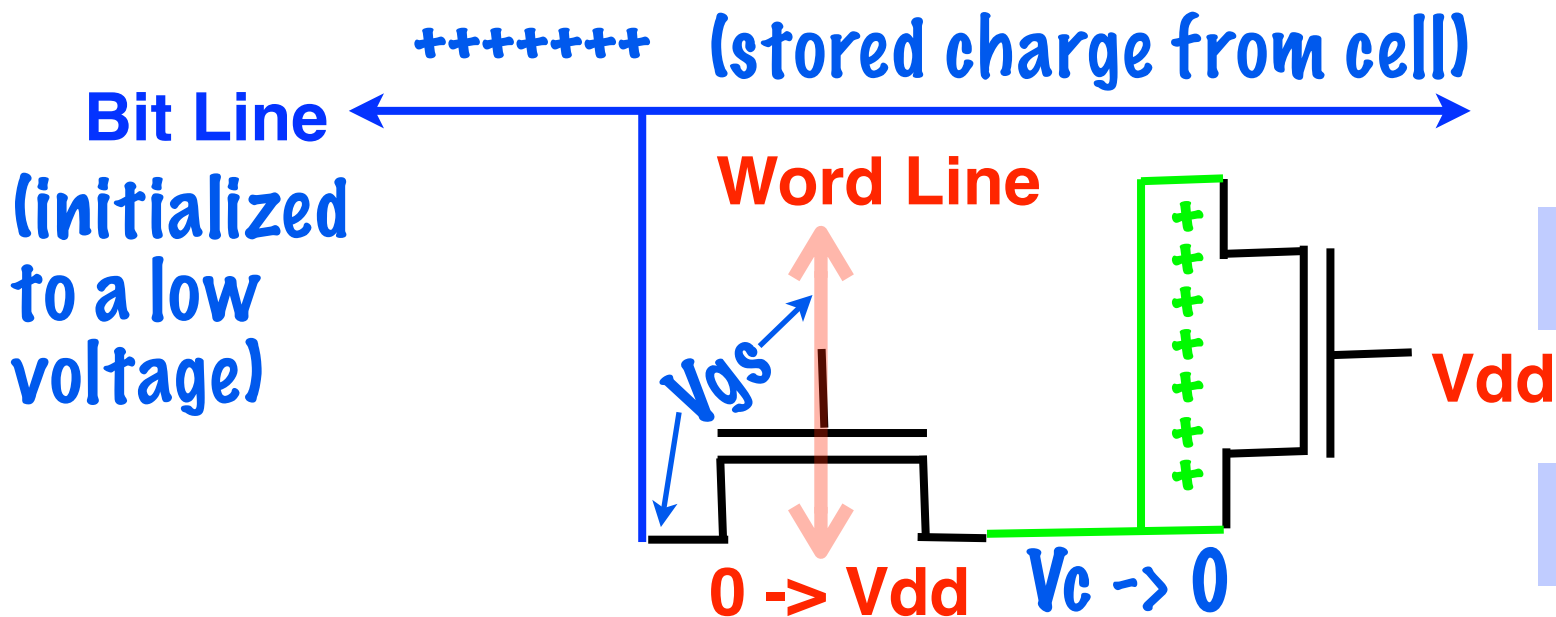

Raising the word line removes the charge from every cell it connects to!

DRAMs **write back** after each read.


DRAM Circuit Challenge #3a: Sensing

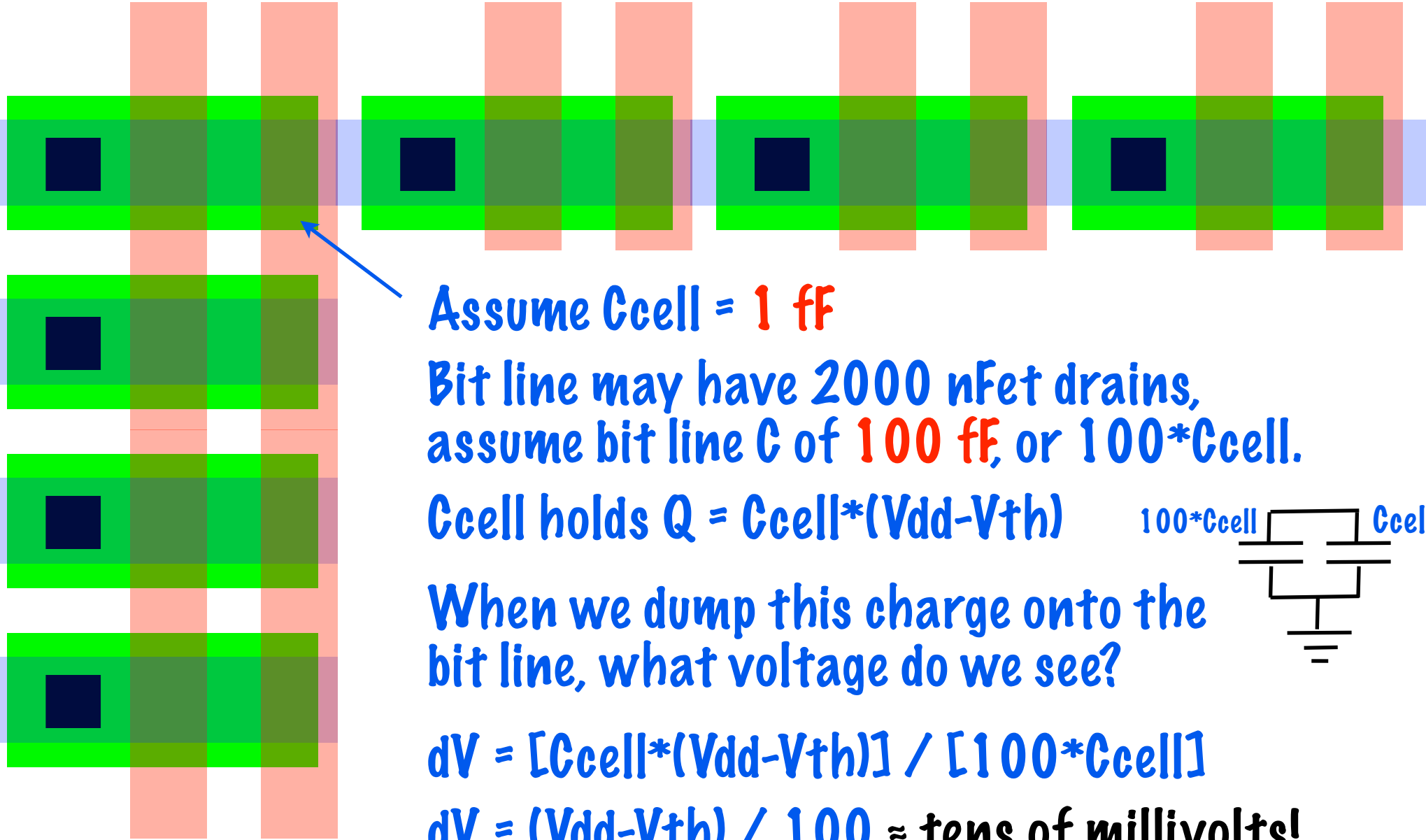

Assume $C_{cell} = 1 \text{ fF}$

Bit line may have 2000 nFet drains,
assume bit line C of 100 fF , or $100 * C_{cell}$.

 C_{cell} holds $Q = C_{cell} * (V_{dd} - V_{th})$



When we dump this charge onto the
bit line, what voltage do we see?


$$dV = [C_{cell} * (V_{dd} - V_{th})] / [100 * C_{cell}]$$

$$dV = (V_{dd} - V_{th}) / 100 \approx \text{tens of millivolts!}$$

In practice, scale array to get a 60mV signal.




DRAM Circuit Challenge #3b: Sensing

 


How do we reliably sense a 60mV signal?
Compare the bit line against the voltage on a "dummy" bit line.

Bit line to sense


Dummy bit line

 



"Dummy" bit line.
Cells hold no charge.

 

DRAM Challenge #4: Leakage ...

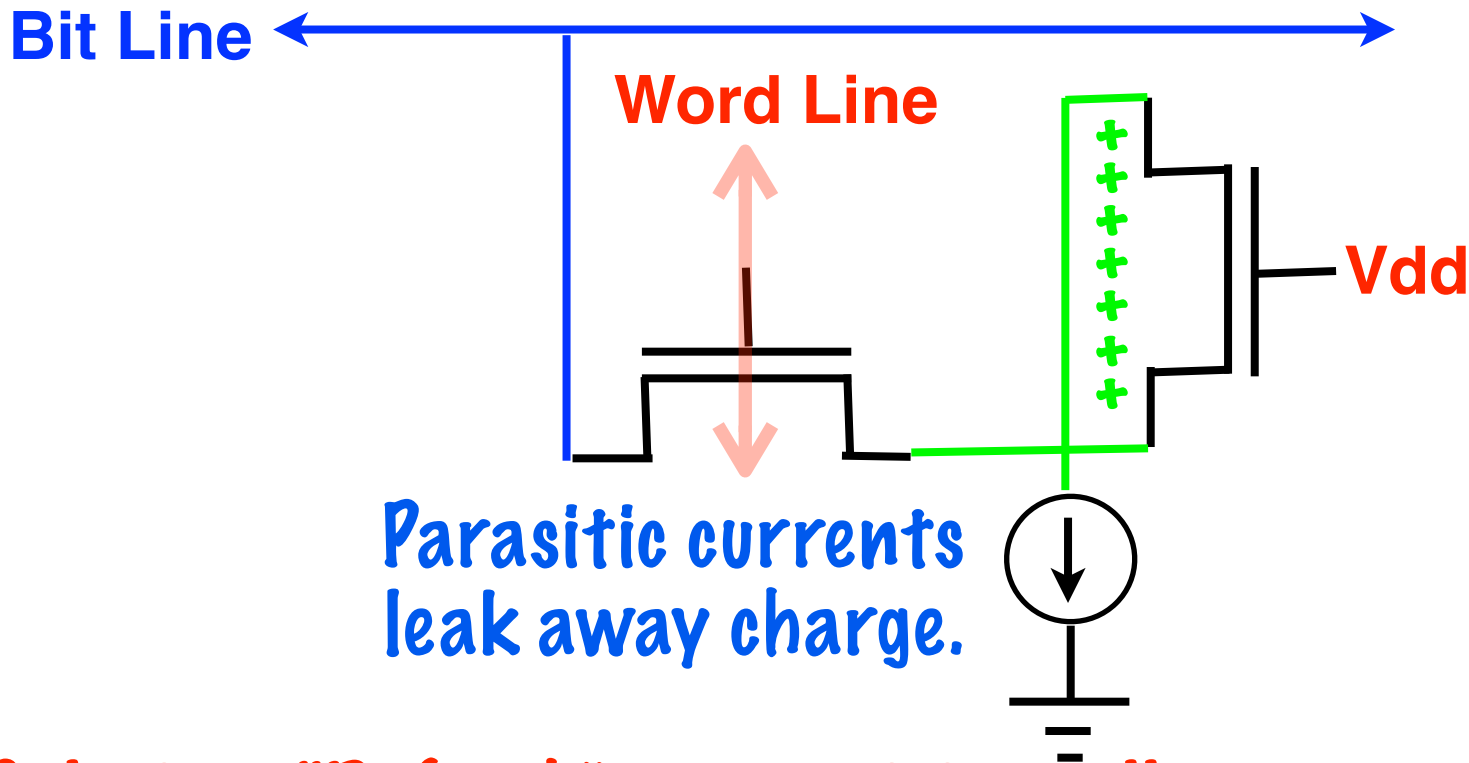


  Solution: "Refresh", by rewriting cells at regular intervals (tens of milliseconds)





Diode leakage ...

DRAM Challenge #5: Cosmic Rays ...

 

Cell capacitor holds 25,000 electrons (or less). Cosmic rays that constantly bombard us can release the charge!

  Solution: Store extra bits to detect and correct random bit flips (ECC).



Cosmic ray hit.


DRAM Challenge 6: Yield




If one bit is bad, do we throw chip away?

Solution: add **extra bit lines** (i.e. 80 when you only need 64). During testing, find the bad bit lines, and use high current to burn away **"fuses"** put on chip to remove them.

Extra bit lines.
Used for "sparing".

 


Moore's Law for CPUs and DRAMs

 

From: "Facing the Hot Chips Challenge Again", Bill Holt, Intel, presented at Hot Chips 17, 2005.

Main driver: device scaling ...

 

Twice the
circuitry in the
same space
(architectural
innovation)

OR


The same
circuitry in half
the space
(cost reduction)

=


Half the die size
for the same
capability than
in the prior
process

From: "Facing the Hot Chips Challenge Again", Bill Holt, Intel, presented at Hot Chips 17, 2005.

Process Scaling: Why chips don't fry

 

IC process scaling
("Moore's Law")

 


Due to reducing V and C (length and width of C s decrease, but plate distance gets smaller).

Recent slope more shallow because V is being scaled less aggressively.



From: "Facing the Hot Chips Challenge Again", Bill Holt, Intel, presented at Hot Chips 17, 2005.

DRAM Challenge 7: Scaling

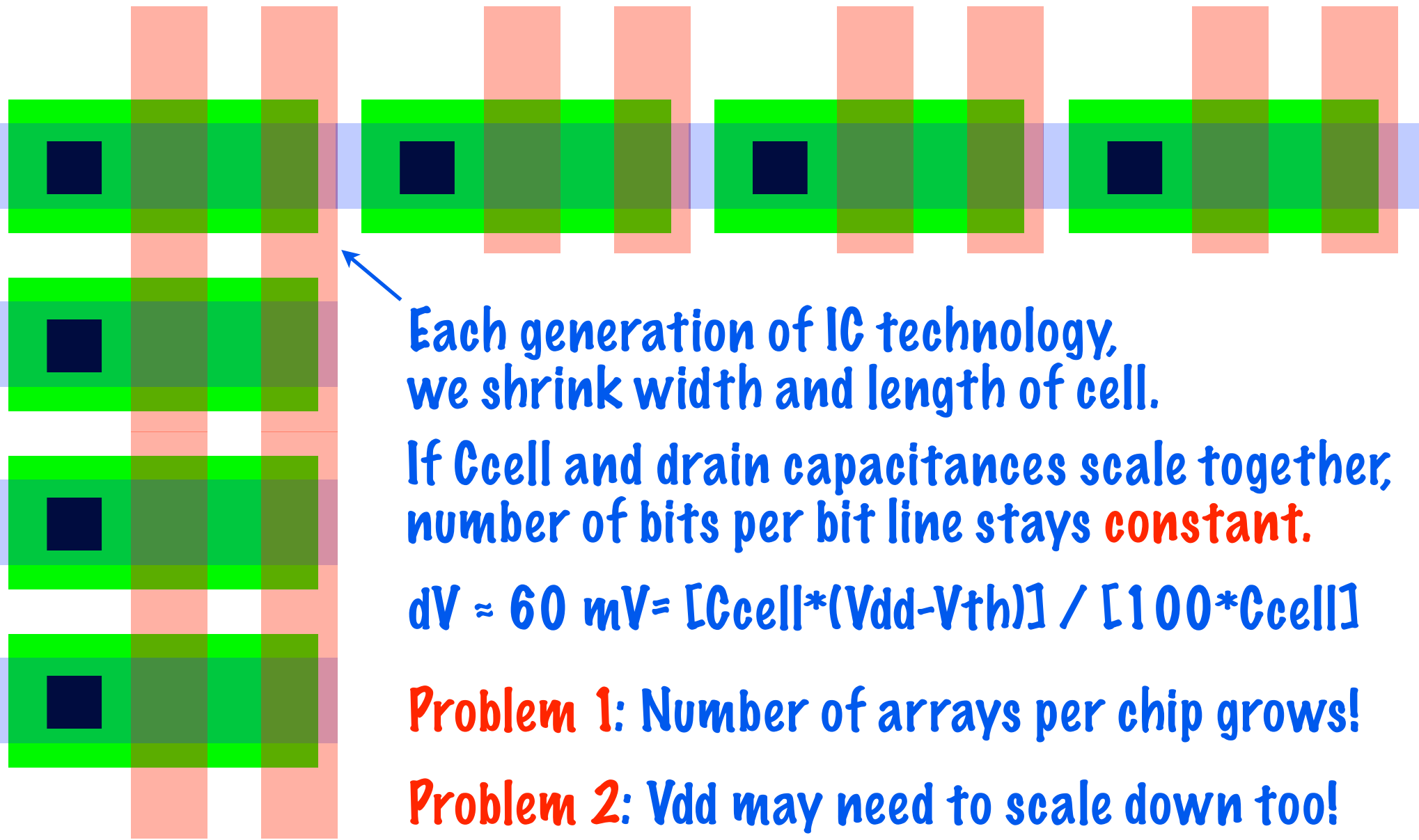


Solution: Constant Innovation of Cell Capacitors!

Poly-diffusion Ccell is ancient history

 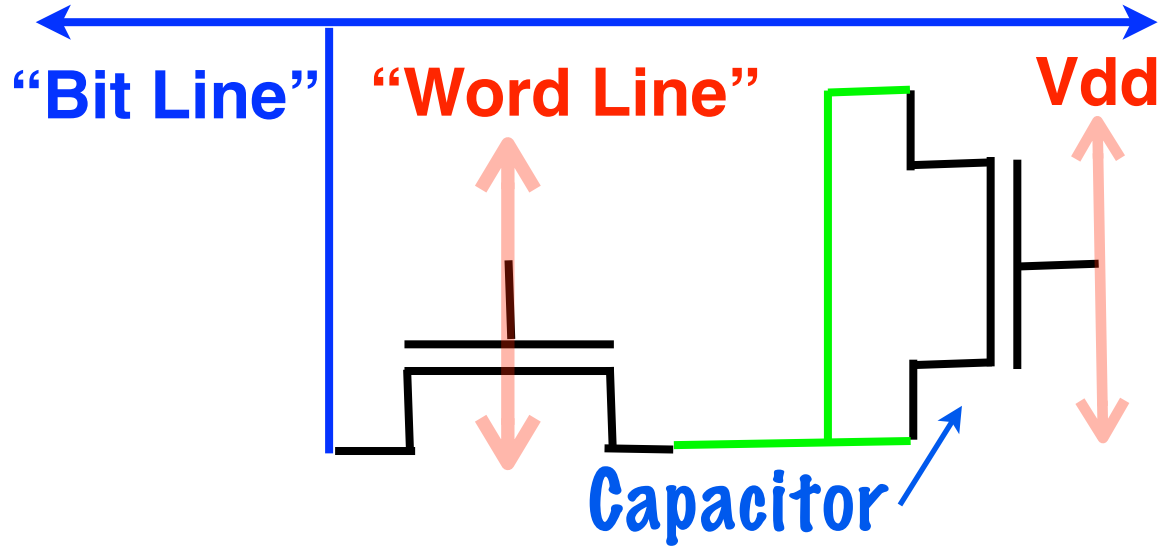

"Bit Line"

 

Word Line and Vdd run on "z-axis"



Early replacement: “Trench” capacitors


 


Figure 4


SEM photomicrograph of 0.25- μm trench DRAM cell suitable for scaling to 0.15 μm and below. Reprinted with permission from [17]; © 1995 IEEE.

Final generation of trench capacitors

 



The companies that kept scaling trench capacitors for commodity DRAM chips went out of business.

Modern cells: “stacked” capacitors

 

Micron 1-Gbit DDR2 50-nm SDRAM

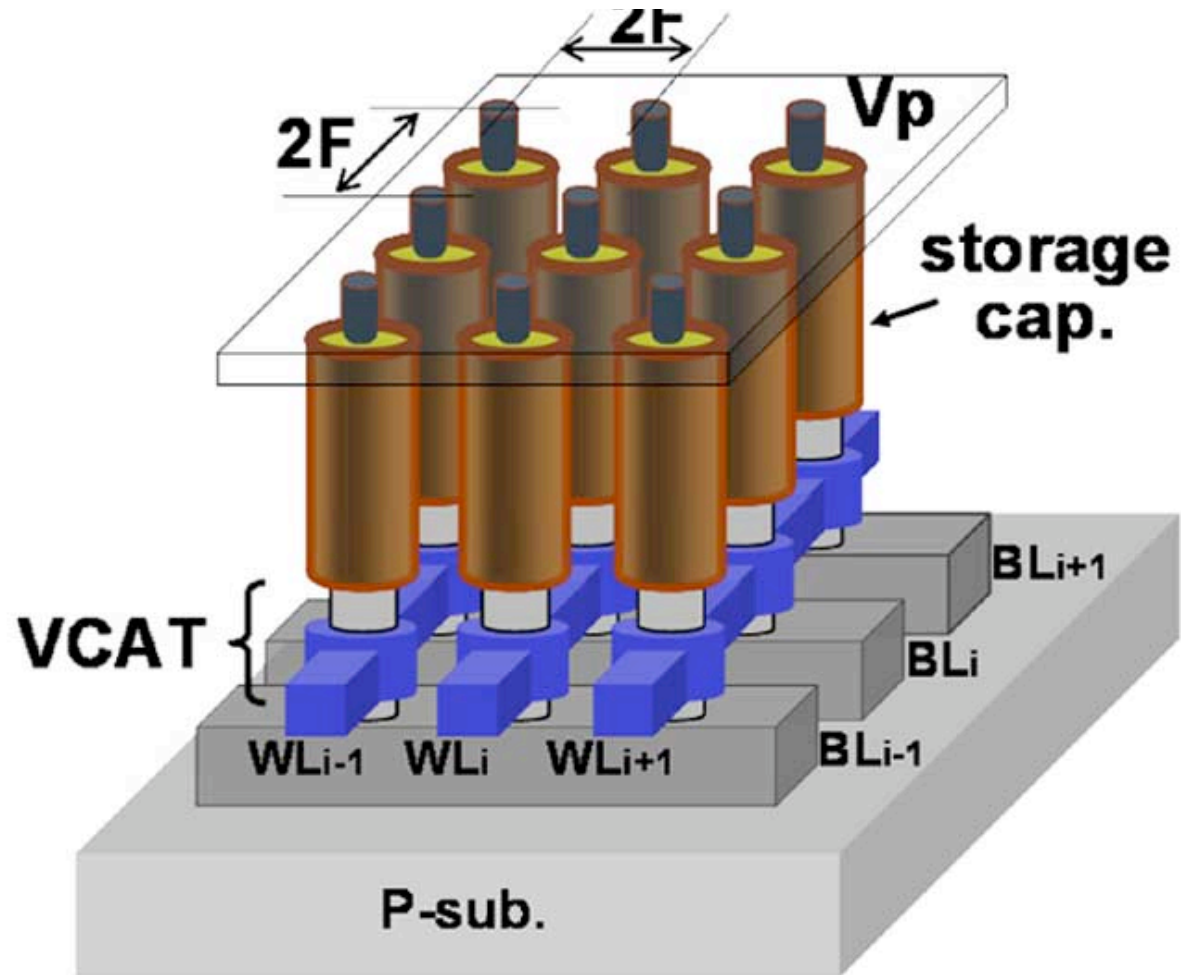 In the labs: Vertical cell transistors ...




880

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 45, NO. 4, APRIL 2010

A 31 ns Random Cycle VCAT-Based $4F^2$ DRAM With Manufacturability and Enhanced Cell Efficiency

Ki-Whan Song, Jin-Young Kim, Jae-Man Yoon, Sua Kim, Huijung Kim, Hyun-Woo Chung, Hyungi Kim, Kanguk Kim, Hwan-Wook Park, Hyun Chul Kang, Nam-Kyun Tak, Dukha Park, Woo-Seop Kim, *Member, IEEE*, Yeong-Taek Lee, Yong Chul Oh, Gyo-Young Jin, Jeihwan Yoo, Donggun Park, *Senior Member, IEEE*, Kyungseok Oh, Changhyun Kim, *Senior Member, IEEE*, and Young-Hyun Jun

Micron 50nm 1-Gbit DDR2 die photo

 


Today's Lecture: DRAM

* DRAM, Xilinx, and You

* DRAM: Bottom-up

* DRAM: Top-down

 

Memory Arrays



512Mb: x4, x8, x16 DDR2 SDRAM
Features




**“Word Line”
“Row”**

**Bit Line
“Column”**


**People
buy
DRAM for
the bits.
“Edge”
circuits
are
overhead.**

 **So, we
amortize
the edge
circuits
over big
arrays.**




A “bank” of 128 Mb (512Mb chip -> 4 banks)

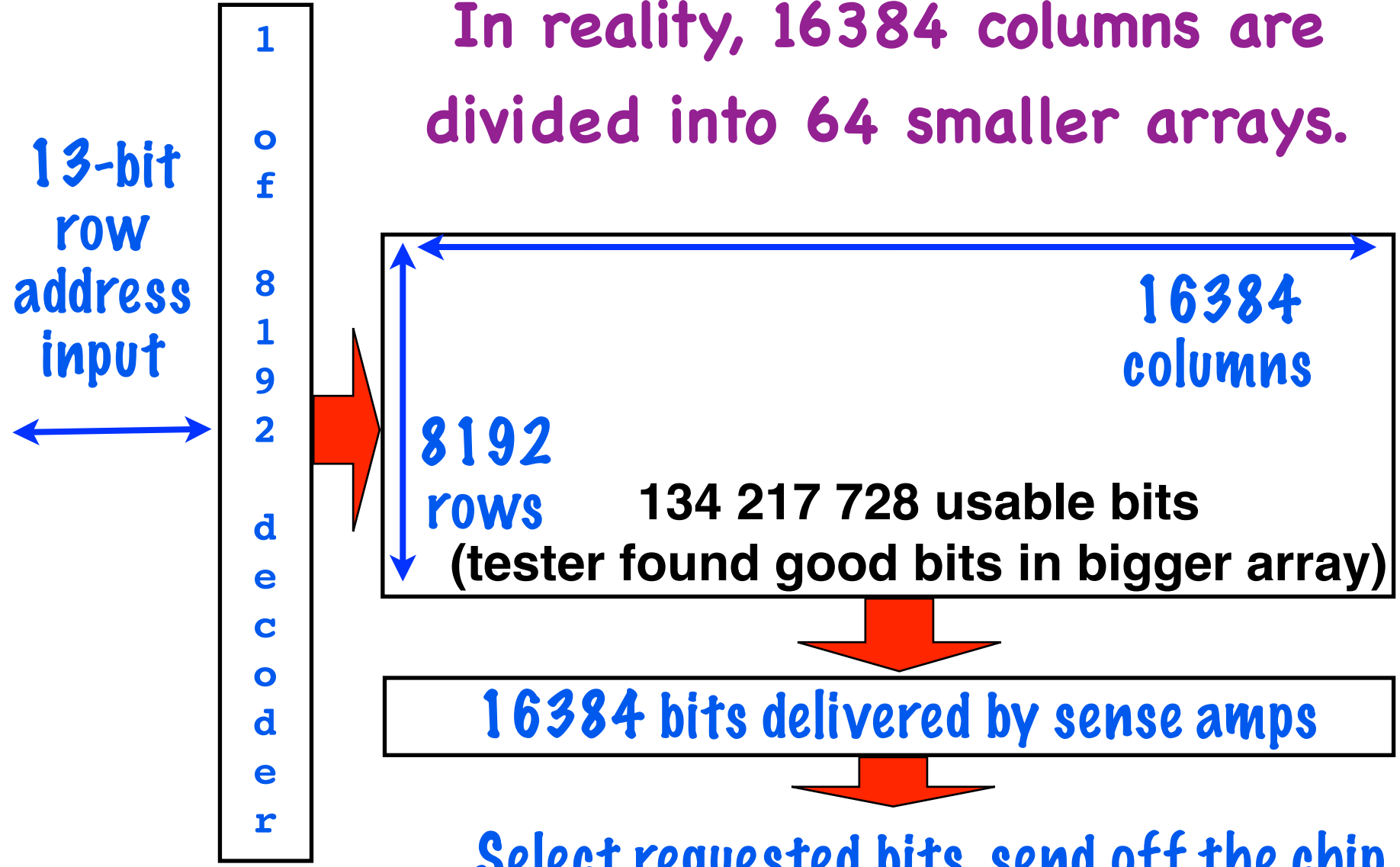In reality, 16384 columns are divided into 64 smaller arrays.



Recall DRAM Challenge #3b: Sensing

 


[...]

How do we reliably sense a 60mV signal?


Compare the bit line against the voltage on a "dummy" bit line.

Bit line to sense

Dummy bit line

 


"Dummy" bit line.
Cells hold no charge.

 


“Sensing” is row read into sense amps

Slow! This **2.5ns** period DRAM (**400 MT/s**) can do row reads at only **55 ns** (**18 MHz**).


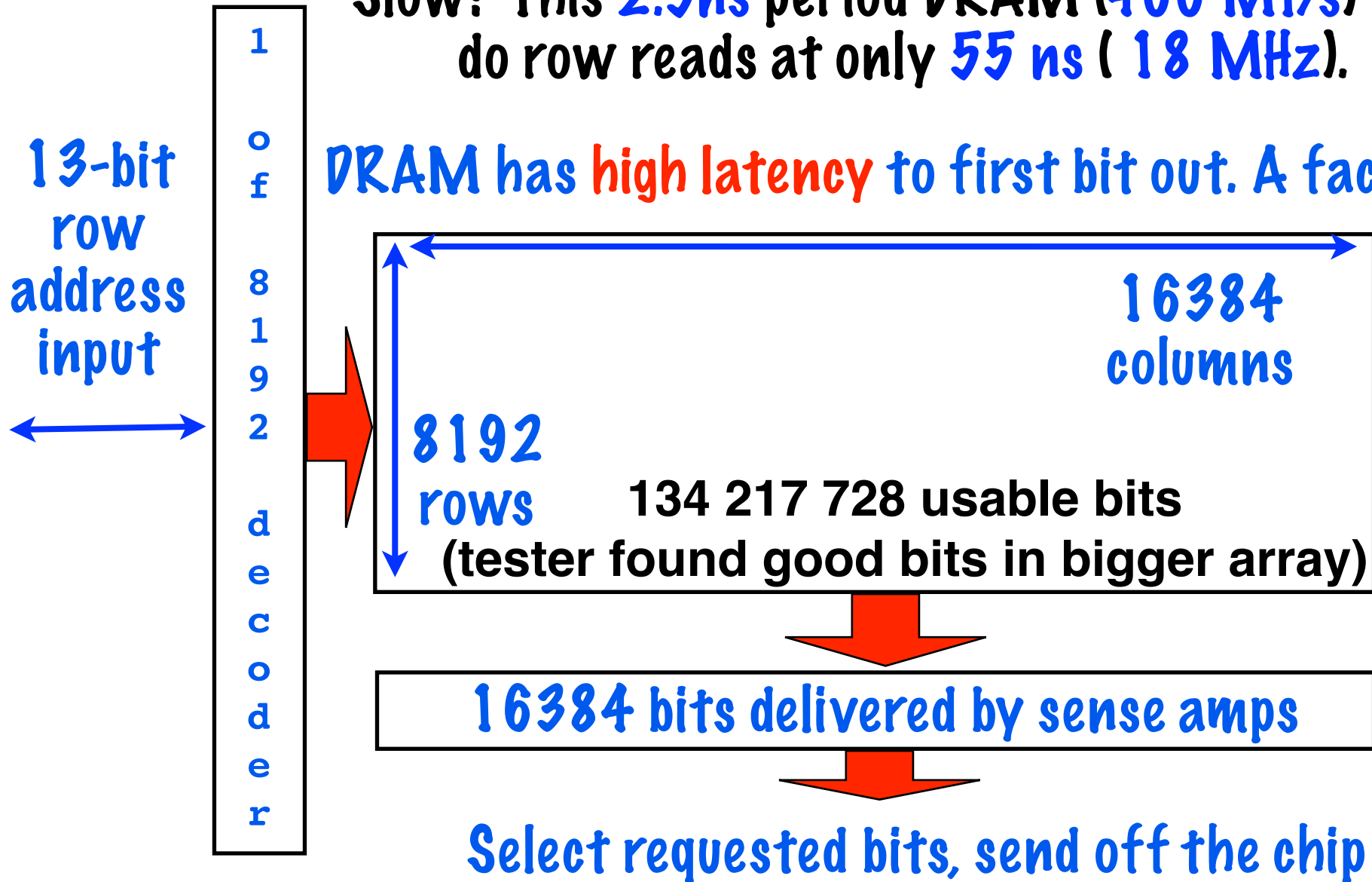
DRAM has **high latency** to first bit out. A fact of life.



An ill-timed refresh may add to latency

 

  
Solution: "Refresh", by rewriting cells at regular intervals (tens of milliseconds)




Latency is not the same as bandwidth!

Thus, push to faster DRAM interfaces

13-bit row address input

 

 What if we want all of the 16384 bits?
In row access time (55 ns) we can do
22 transfers at 400 MT/s.
16-bit chip bus $\rightarrow 22 \times 16 = 352 \text{ bits} \ll 16384$
Now the row access time looks fast!



16384 bits delivered by sense amps

Select requested bits, send off the chip




Sadly, it's rarely this good ...


What if we want all of the 16384 bits?

The "we" for a CPU would be the program running on the CPU.

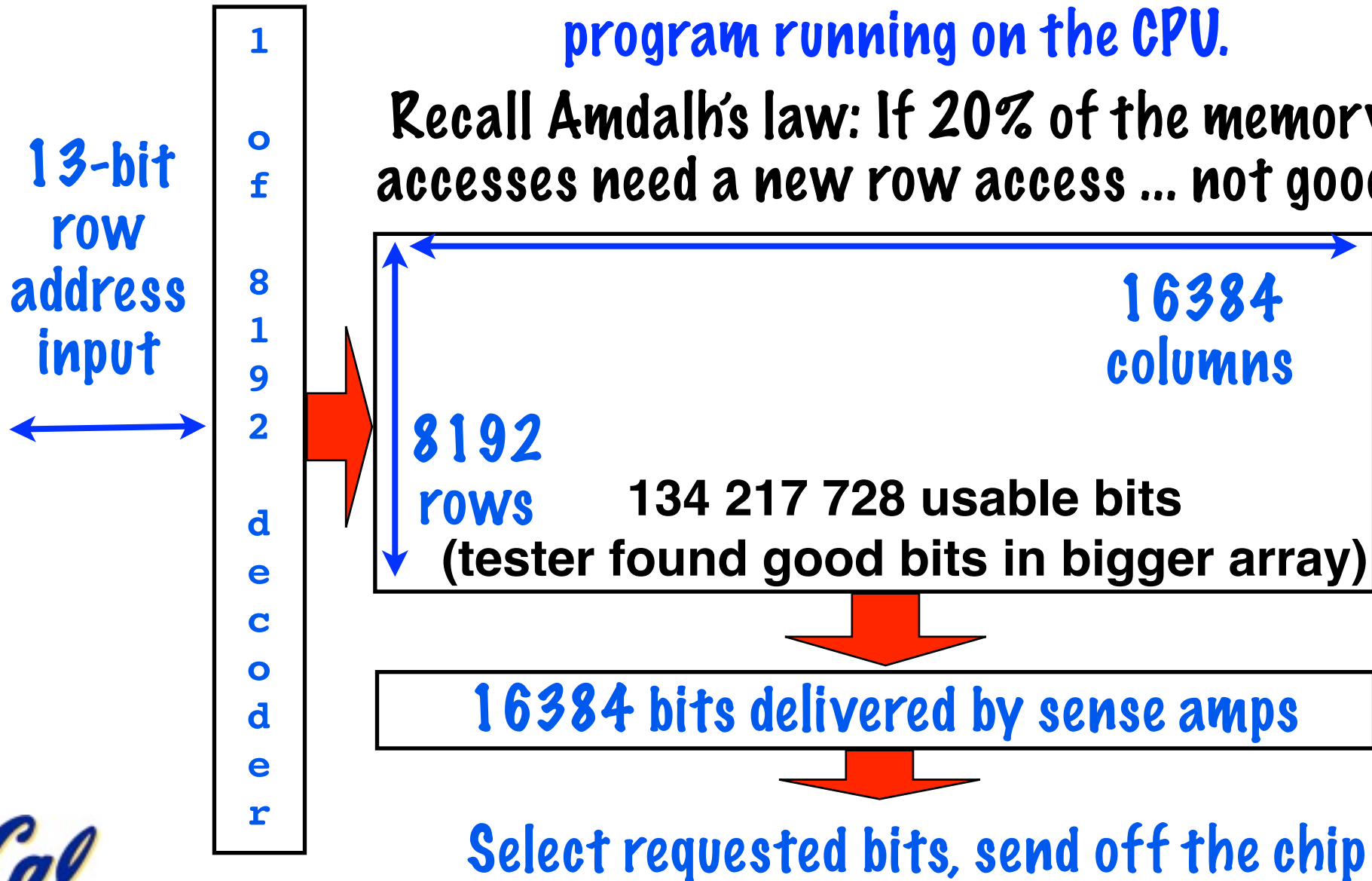Recall Amdahl's law: If 20% of the memory accesses need a new row access ... not good.



DRAM latency/bandwidth chip features

 

Columns: Design the right interface for CPUs to request the subset of a column of data it wishes:

16384 bits delivered by sense amps



Select requested bits, send off the chip



Interleaving: Design the right interface to the 4 memory banks on the chip, so several row requests run in parallel.

Bank 1

Bank 2

Bank 3


Bank 4



Off-chip interface for the Micron part ...

A clocked bus:
200 MHz clock,
data transfers on
both edges (**DDR**).

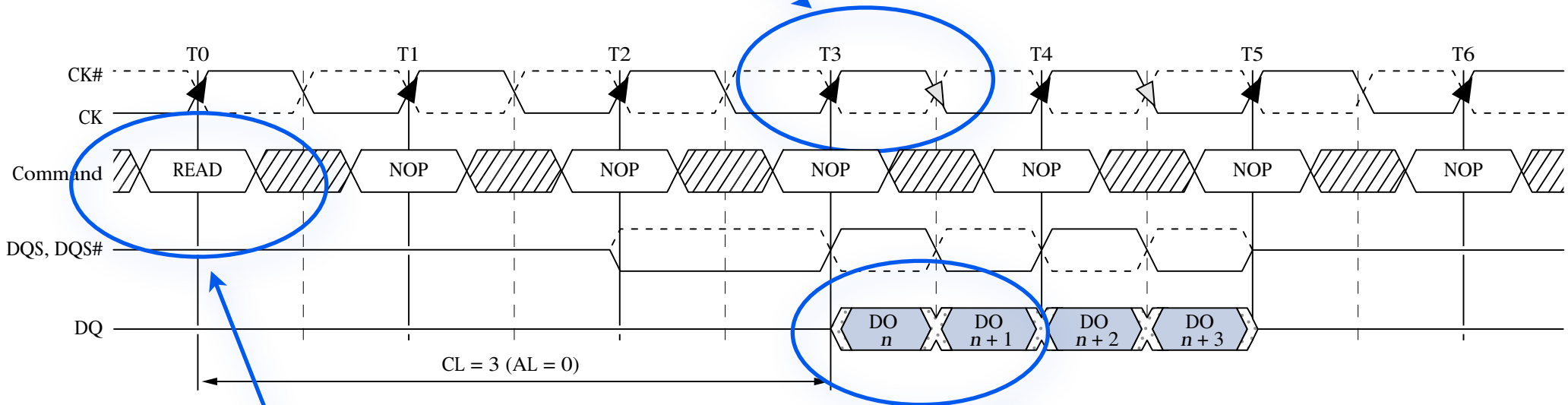Note! This example is **best-case!**
To access a new row, a slow **ACTIVE**
command must run before the **READ**.




DRAM is controlled via
commands
(READ, WRITE,
REFRESH, ...)

Synchronous data
output.



Opening a row before reading ...


Auto-Precharge
READ

 

55 ns between row opens.




However, we can read columns quickly

 


**Note: This is a “normal read” (not Auto-Precharge).
Both READs are to the same bank, but different columns.**



Why can we read columns quickly?

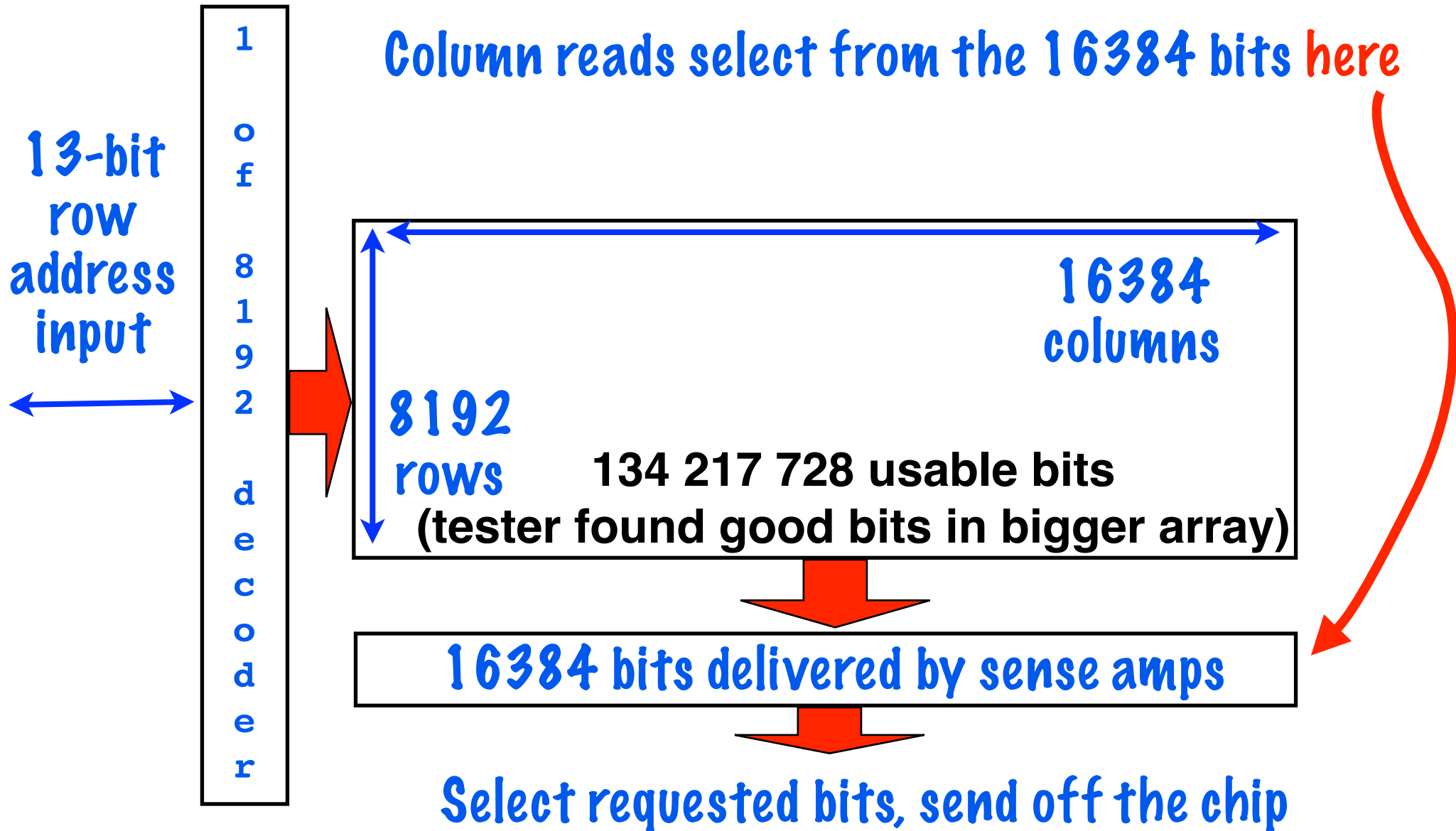

 Interleave: Access all 4 banks in parallel



Interleaving: Design the right interface to the 4 memory banks on the chip, so several row requests run in parallel.

Bank a

Bank b


Bank c

Bank d



Can also do other commands on banks concurrently.



Only part of a bigger story ...

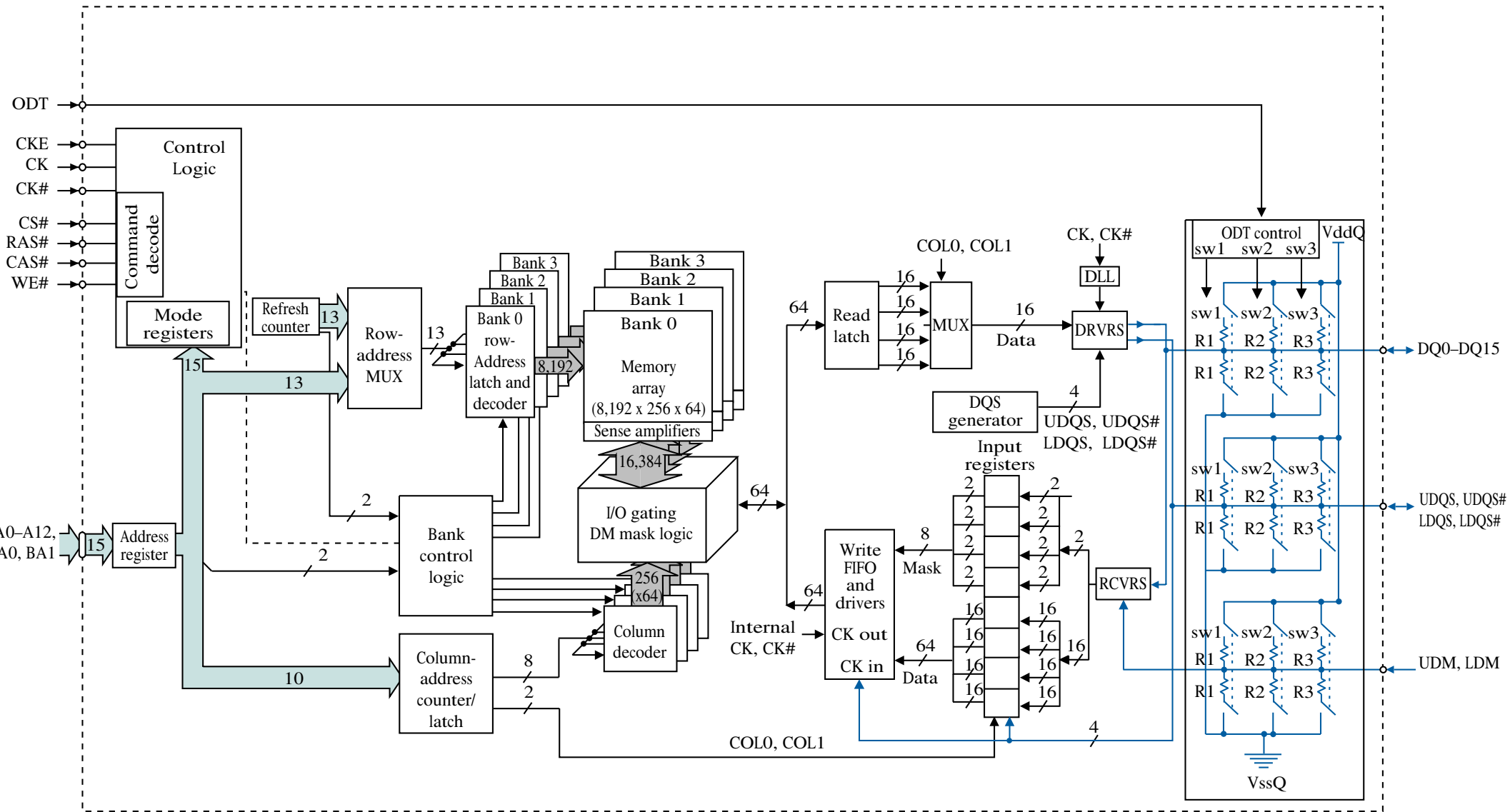

Only part of a bigger story ...

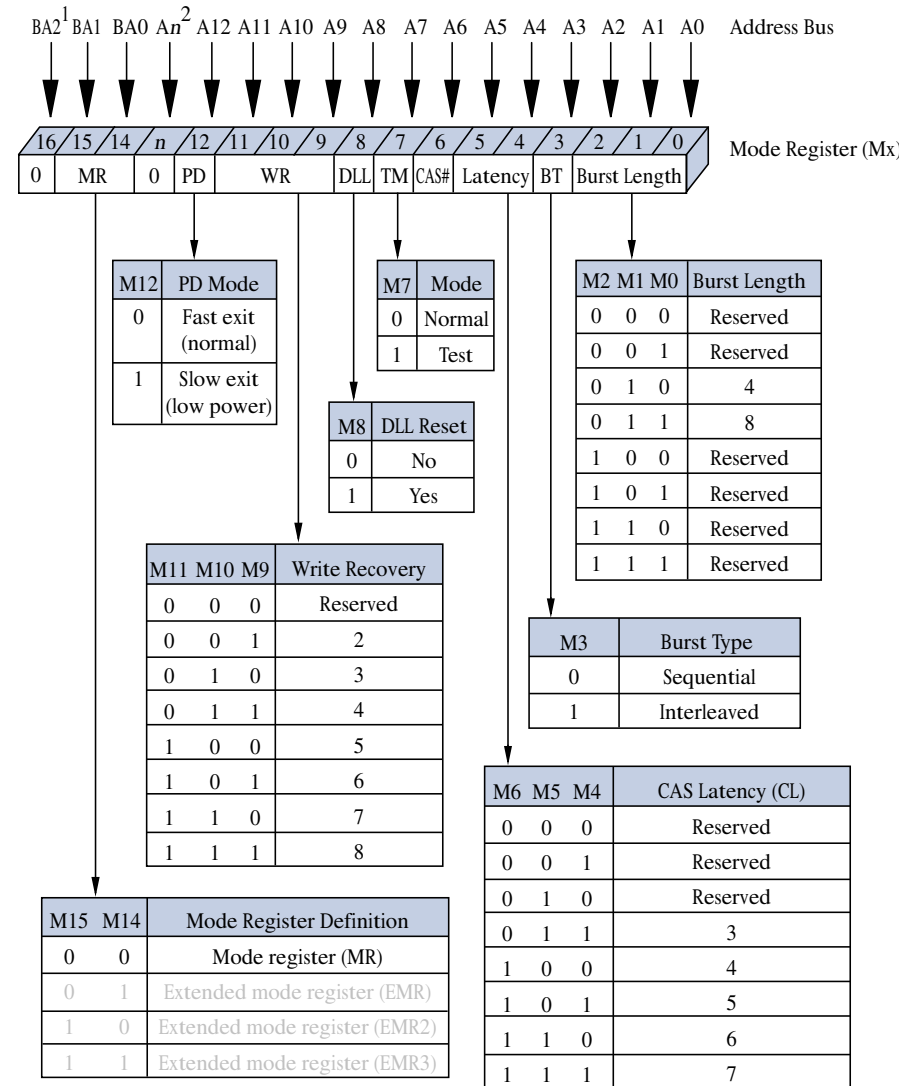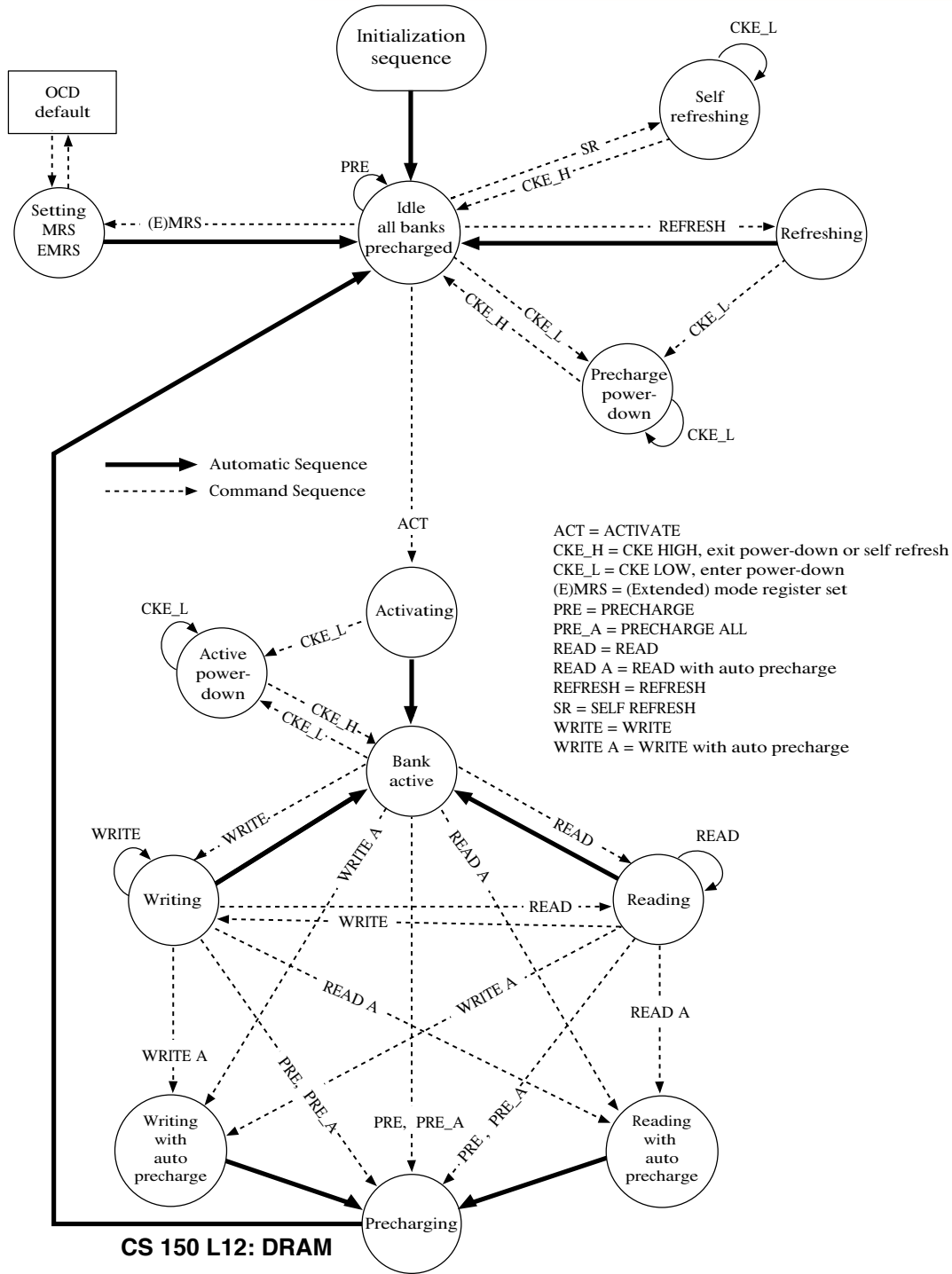


Present and Future ...



MacBook Air ... too thin to use DIMMs



Mainboard: fills about 25% of the laptop

 


35 W-h battery: 63% of 2006 MacBook's 55 W-h

Main board




Core i5: CPU + DRAM controller

Top

 

4GB DRAM soldered to the main board




Bottom

 

3-D memory stack

1 Gbit stacked DRAM with TSV (512 Mbit × 2 strata)

DRAM die size	10.7 mm × 13.3 mm
DRAM die thickness	50 μm
TSV count in DRAM	1,560
DRAM capacity	512 Mbit/die × 2 strata
CMOS logic die size	17.5 mm × 17.5 mm
CMOS logic die thickness	200 μm
CMOS logic bump count	3,497
CMOS logic process	0.18 μm CMOS
DRAM-logic FTI via pitch	50 μm
Package size	33 mm × 33 mm
BGA terminal	520 pin / 1mm pitch

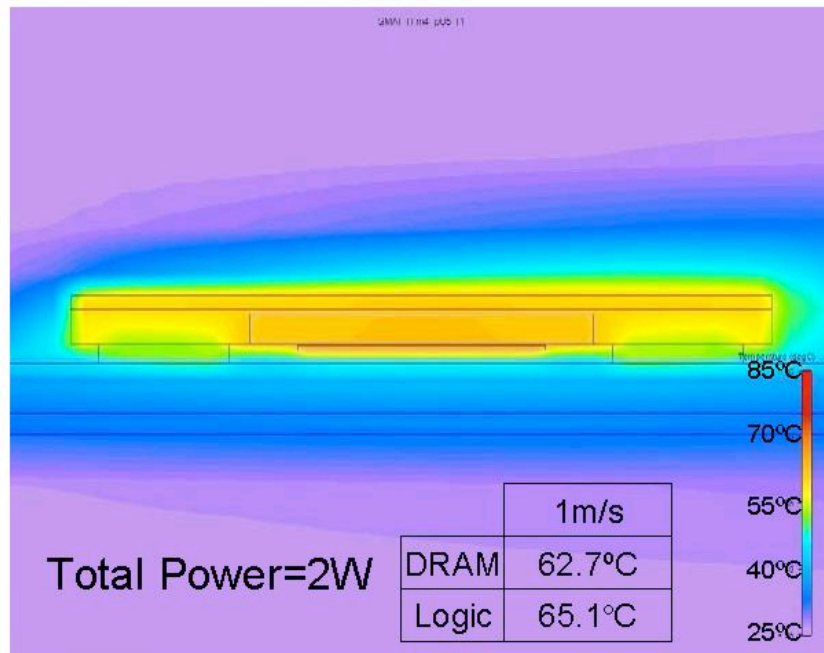  


A 3D Stacked Memory Integrated on a Logic Device Using SMAFTI Technology

Yoichiro Kurita¹, Satoshi Matsui¹, Nobuaki Takahashi¹, Koji Soejima¹, Masahiro Komuro¹, Makoto Itou¹, Chika Kakegawa¹, Masaya Kawano¹, Yoshimi Egawa², Yoshihiro Saeki², Hidekazu Kikuchi², Osamu Kato², Azusa Yanagisawa², Toshiro Mitsuhashi², Masakazu Ishino³, Kayoko Shibata³, Shiro Uchiyama³, Junji Yamada³, and Hiroaki Ikeda³

¹NEC Electronics, ²Oki Electric Industry, and ³Elpida Memory
1120 Shimokuzawa, Sagami-hara, Kanagawa 229-1198, Japan

y.kurita@necel.com

Next week's lectures: Timing ...

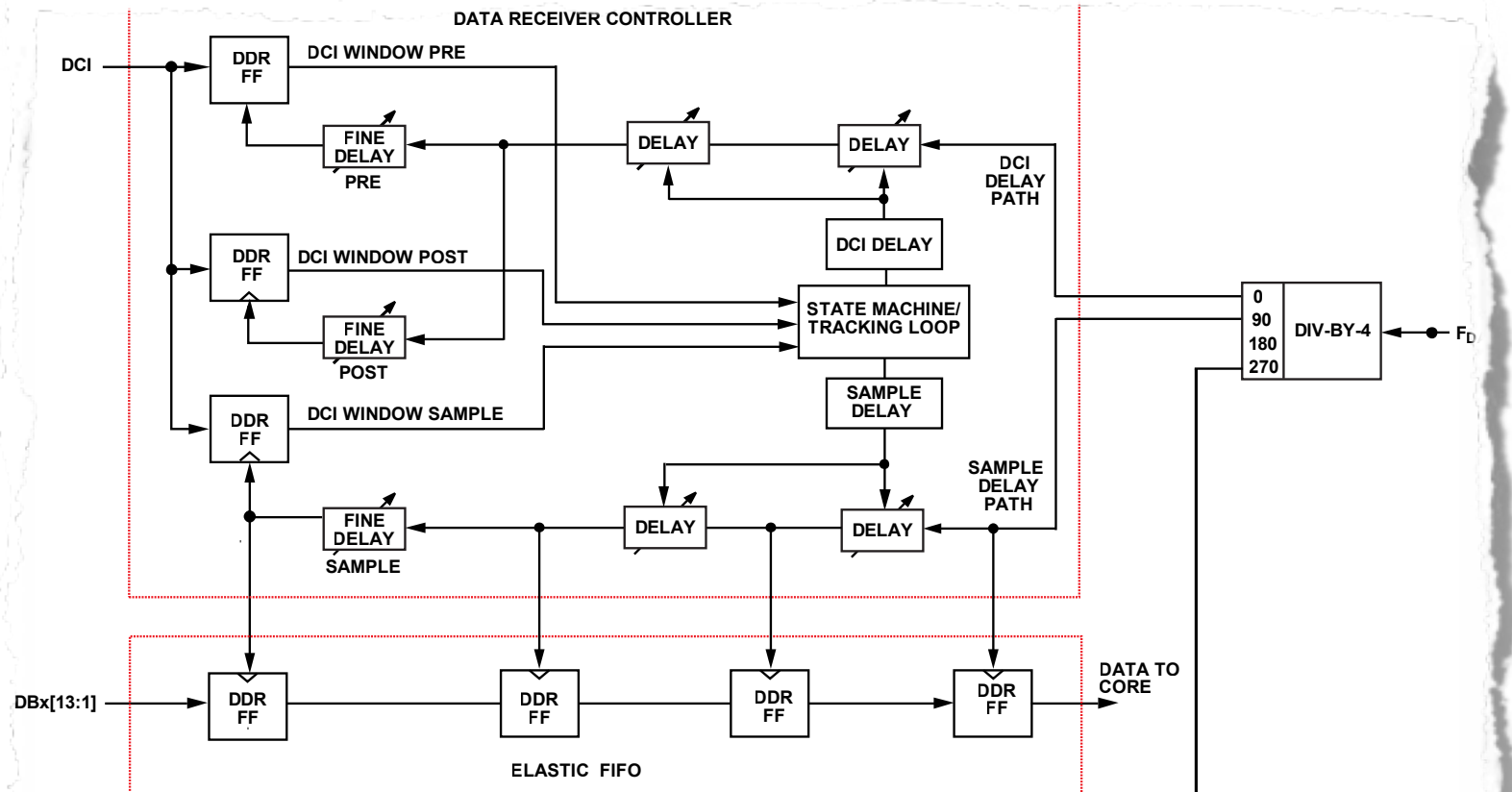

7	Tue 2/28	Lec #13: Timing (1) (Slides) Reading: 3.5-3.6
	Thu 3/1	Lec #14: Timing (2) (Slides)