

**EECS150 - Digital Design**  
**Lecture 20 - Arithmetic Blocks,**  
**Part 2 + Shifters**

March 22, 2012

John Wawrzynek


# Multiplication

$$\begin{array}{rcccc}
 a_3 & a_2 & a_1 & a_0 & \leftarrow \textit{Multiplicand} \\
 b_3 & b_2 & b_1 & b_0 & \leftarrow \textit{Multiplier} \\
 \hline
 & & X & & \\
 & & a_3b_0 & a_2b_0 & a_1b_0 & a_0b_0 \\
 & & a_3b_1 & a_2b_1 & a_1b_1 & a_0b_1 \\
 & a_3b_2 & a_2b_2 & a_1b_2 & a_0b_2 & \\
 a_3b_3 & a_2b_3 & a_1b_3 & a_0b_3 & & \\
 \hline
 & & \dots & a_1b_0+a_0b_1 & a_0b_0 & \leftarrow \textit{Product}
 \end{array}$$

} *Partial products*

*Many different circuits exist for multiplication. Each one has a different balance between speed (performance) and amount of logic (cost).*

# “Shift and Add” Multiplier

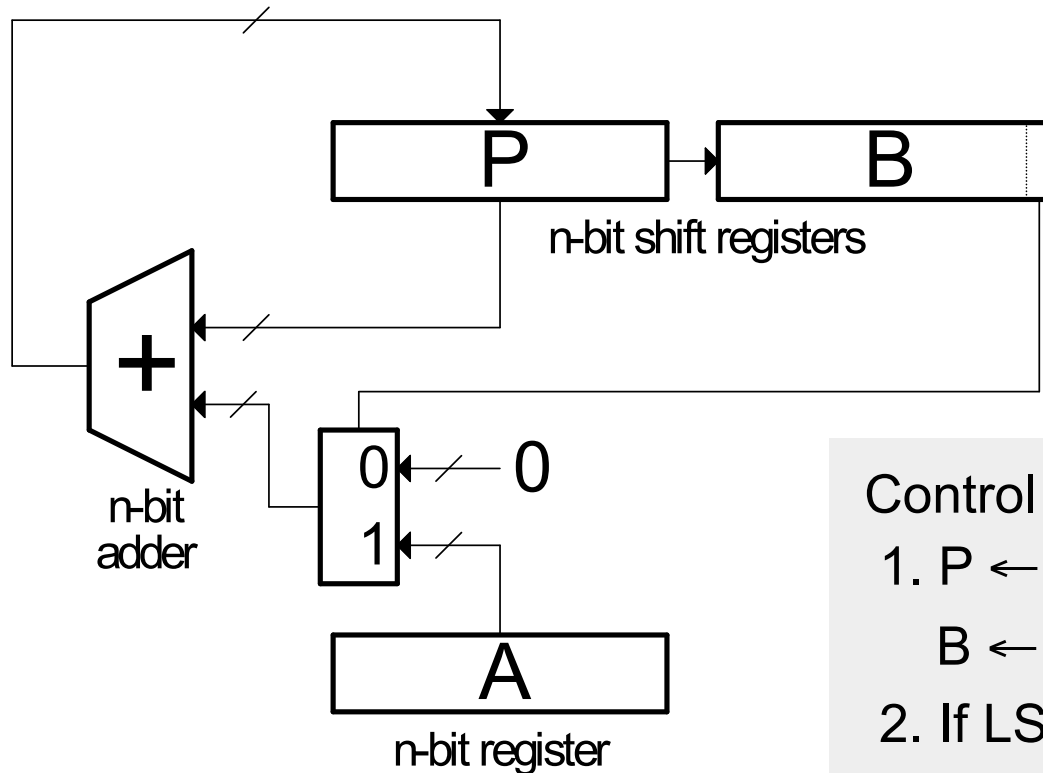

- Sums each partial product, one at a time.
- In binary, each partial product is shifted versions of A or 0.

## Control Algorithm:

1.  $P \leftarrow 0$ ,  $A \leftarrow$  multiplicand,  
 $B \leftarrow$  multiplier
2. If LSB of  $B == 1$  then add  $A$  to  $P$   
else add 0
3. Shift  $[P][B]$  right 1
4. Repeat steps 2 and 3  $n-1$  times.
5.  $[P][B]$  has product.

- Cost  $\propto n$ ,  $T = n$  clock cycles.
- What is the critical path for determining the min clock period?

# “Shift and Add” Multiplier

## Signed Multiplication:

*Remember* for 2's complement numbers MSB has negative weight:


$$X = \sum_{i=0}^{N-2} x_i 2^i - x_{n-1} 2^{n-1}$$

$$\begin{aligned} \text{ex: } -6 &= 11010_2 = 0 \cdot 2^0 + 1 \cdot 2^1 + 0 \cdot 2^2 + 1 \cdot 2^3 - 1 \cdot 2^4 \\ &= 0 + 2 + 0 + 8 - 16 = -6 \end{aligned}$$

- Therefore for multiplication:
  - a) subtract final partial product
  - b) sign-extend partial products
- Modifications to shift & add circuit:
  - a) adder/subtractor
  - b) sign-extender on P shifter register
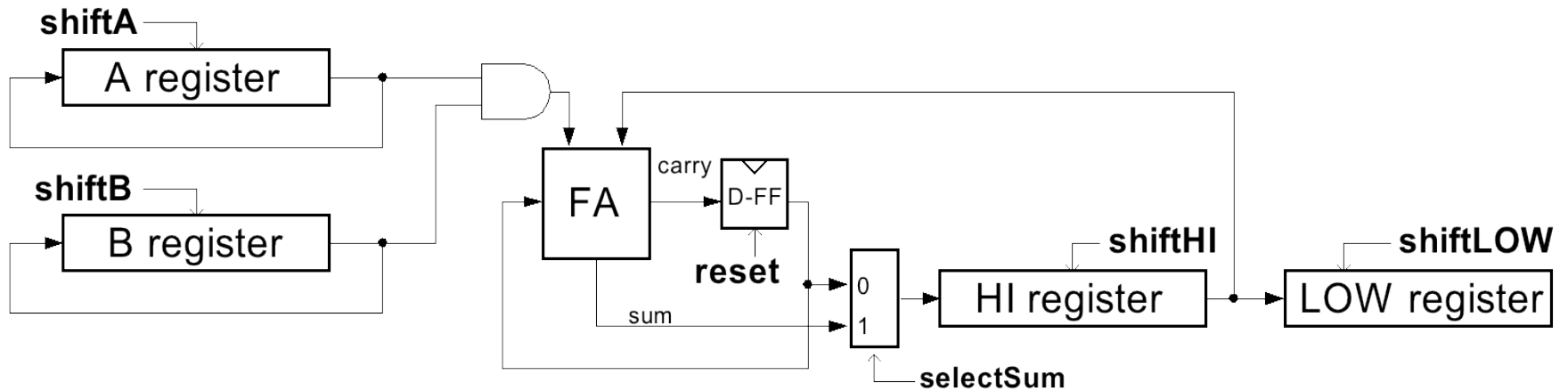
# Bit-serial Multiplier

- Bit-serial multiplier ( $n^2$  cycles, one bit of result per  $n$  cycles):



- Control Algorithm:

```


repeat n cycles { // outer (i) loop
  repeat n cycles{ // inner (j) loop
    shiftA, selectSum, shiftHI
  }
  shiftB, shiftHI, shiftLOW, reset
}

```

**Note:** The occurrence of a control signal  $x$  means  $x=1$ . The absence of  $x$  means  $x=0$ .
 
# Array Multiplier

Single cycle multiply: Generates all  $n$  partial products simultaneously.



# Carry-Save Addition

- Speeding up multiplication is a matter of speeding up the summing of the partial products.
- “Carry-save” addition can help.
- Carry-save addition passes (saves) the carries to the output, rather than propagating them.


- Example: sum three numbers,  $3_{10} = 0011$ ,  $2_{10} = 0010$ ,  $3_{10} = 0011$

$$\begin{array}{r}
 3_{10} \quad 0011 \\
 + 2_{10} \quad 0010 \\
 \hline
 c \quad 0100 = 4_{10} \\
 s \quad 0001 = 1_{10} \\
 \hline
 3_{10} \quad 0011 \\
 + \quad \quad 0010 \\
 \hline
 c \quad 0010 = 2_{10} \\
 s \quad 0110 = 6_{10} \\
 \hline
 1000 = 8_{10}
 \end{array}$$


The first two additions (3<sub>10</sub> + 2<sub>10</sub> and 3<sub>10</sub> + 3<sub>10</sub>) are grouped by a bracket on the right labeled "carry-save add".  
 The second two additions (3<sub>10</sub> + 2<sub>10</sub> and 3<sub>10</sub> + 3<sub>10</sub>) are grouped by a bracket on the left labeled "carry-propagate add".

- In general, *carry-save* addition takes in 3 numbers and produces 2.
- Whereas, *carry-propagate* takes 2 and produces 1.
- With this technique, we can avoid carry propagation until final addition

# Carry-save Circuits

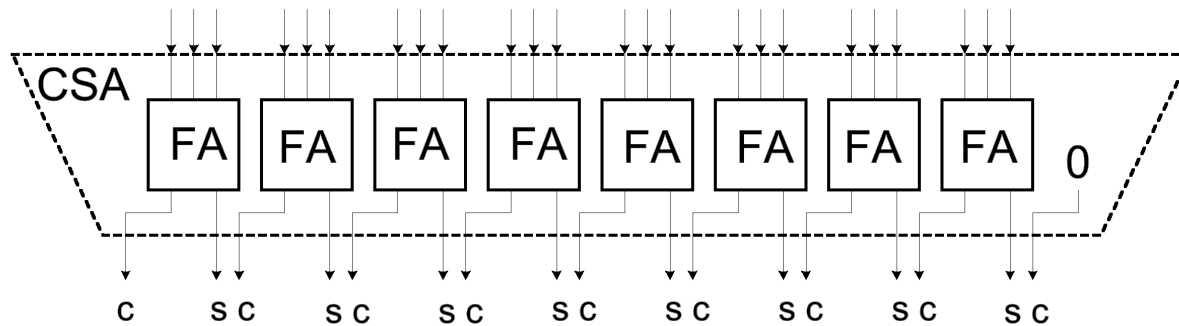


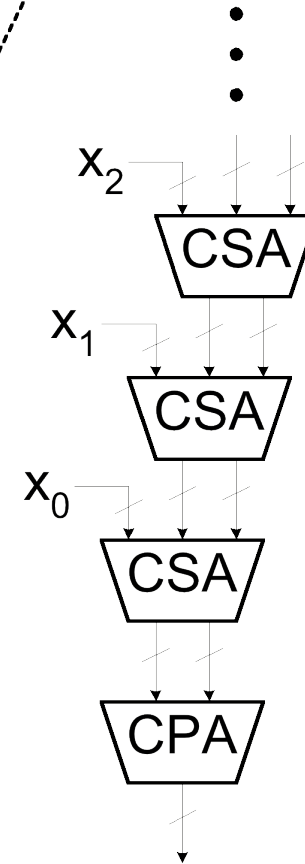- When adding sets of numbers, carry-save can be used on all but the final sum.
- Standard adder (carry propagate) is used for final sum.
- Carry-save is fast (no carry propagation) and cheap (same cost as ripple adder)





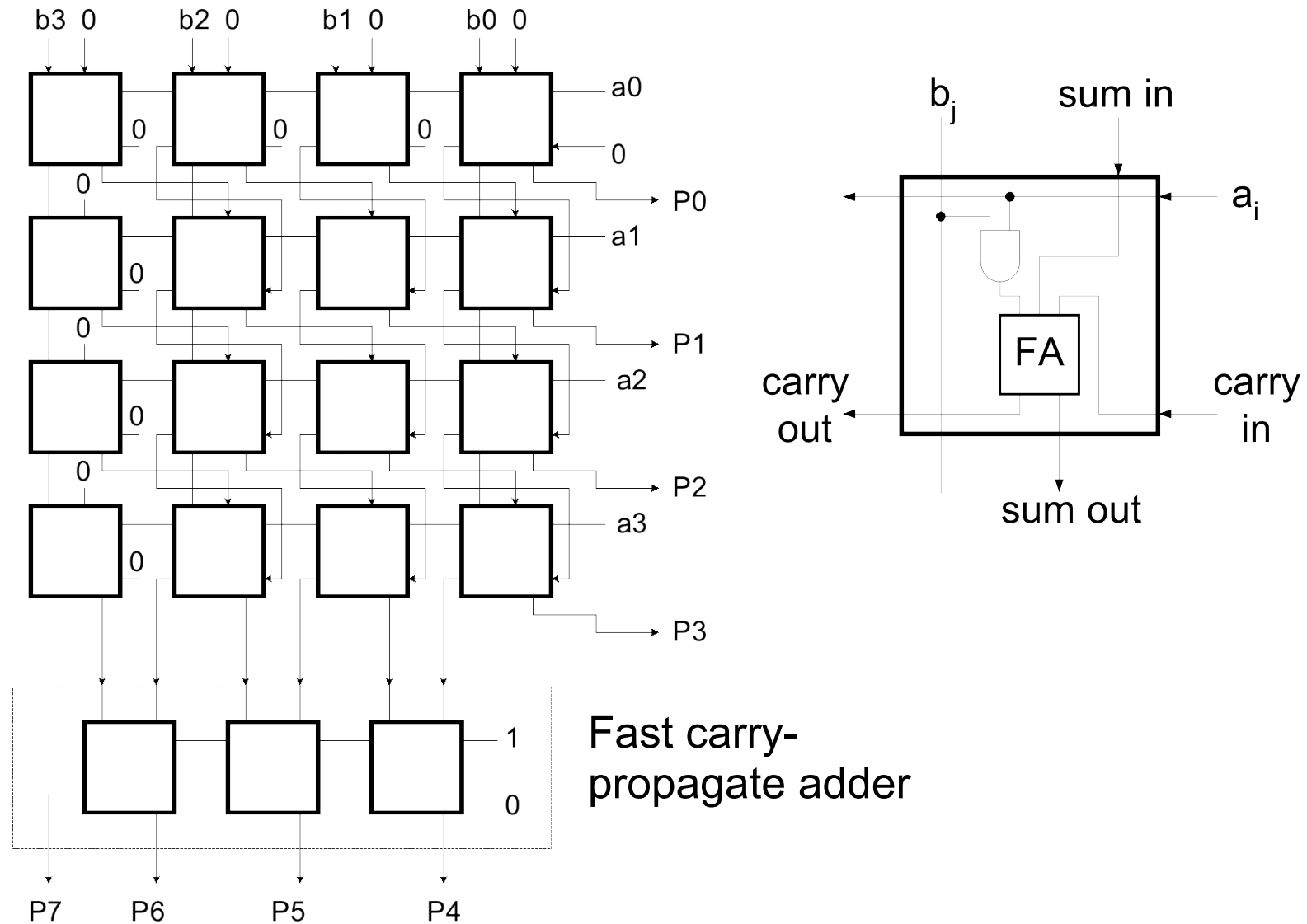
# Array Multiplier using Carry-save Addition


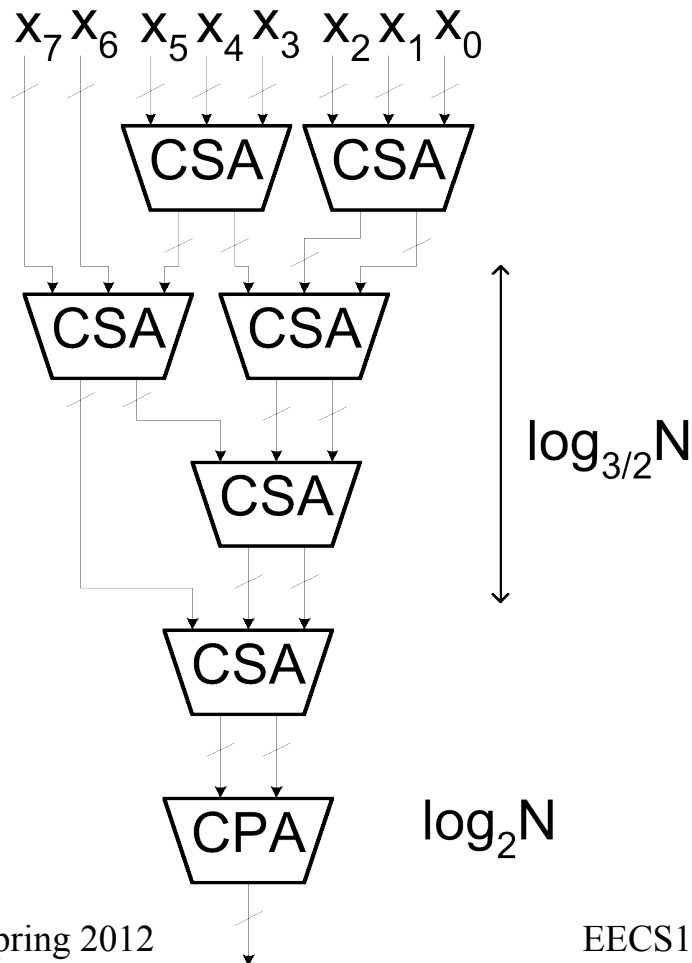
# Carry-save Addition

CSA is associative and commutitive. For example:

$$(((X_0 + X_1) + X_2) + X_3) = ((X_0 + X_1) + (X_2 + X_3))$$



- A balanced tree can be used to reduce the logic delay.
- This structure is the basis of the **Wallace Tree Multiplier**.
- Partial products are summed with the CSA tree. Fast CPA (ex: CLA) is used for final sum.
- Multiplier delay  $\propto \log_{3/2} N + \log_2 N$


# Constant Multiplication

- *Our discussion so far has assumed both the multiplicand (A) and the multiplier (B) can vary at runtime.*
- What if one of the two is a constant?

$$Y = C * X$$

- “Constant Coefficient” multiplication comes up often in signal processing and other hardware. Ex:

$$y_i = \alpha y_{i-1} + x_i$$

 


where  $\alpha$  is an application dependent constant that is hard-wired into the circuit.

- How do we build an array style (combinational) multiplier that takes advantage of the constancy of one of the operands?
 
# Multiplication by a Constant


- If the constant  $C$  in  $C \cdot X$  is a power of 2, then the multiplication is simply a shift of  $X$ .
- Ex:  $4 \cdot X$




- What about division?
- What about multiplication by non-powers of 2?
 
# Multiplication by a Constant

- In general, a combination of fixed shifts and addition:
  - Ex:  $6 * X = 0110 * X = (2^2 + 2^1) * X$




- Details:

 
 
# Multiplication by a Constant


- Another example:  $C = 23_{10} = 010111$



- *In general, the number of additions equals the number of 1's in the constant minus one.*
- Using carry-save adders (for all but one of these) helps reduce the delay and cost, but the number of adders is still the number of 1's in  $C$  minus 2.
- Is there a way to further reduce the number of adders (and thus the cost and delay)?
 
# Multiplication using Subtraction

- *Subtraction is ~ the same cost and delay as addition.*
- Consider  $C \cdot X$  where  $C$  is the constant value  $15_{10} = 01111_2$ .  
 $C \cdot X$  requires 3 additions.
- We can “recode” 15  
from  $01111 = (2^3 + 2^2 + 2^1 + 2^0)$   
to  $1000\bar{1} = (2^4 - 2^0)$   
where  $\bar{1}$  means negative weight.
- Therefore,  $15 \cdot X$  can be implemented with only one subtractor.



# Canonic Signed Digit Representation

- CSD represents numbers using 1,  $\bar{1}$ , & 0 with the least possible number of non-zero digits.
  - Strings of 2 or more non-zero digits are replaced.
  - Leads to a unique representation.

- To form CSD representation might take 2 passes:

- First pass: replace all occurrences of 2 or more 1's:

$$01..10 \text{ by } 10..\bar{1}0$$

- Second pass: same as a above, plus replace  $0\bar{1}10$  by  $00\bar{1}0$

- Examples:

$$011101 = 29$$

$$100\bar{1}01 = 32 - 4 + 1$$

$$0010111 = 23$$

$$001100\bar{1}$$

$$010\bar{1}00\bar{1} = 32 - 8 - 1$$

$$0110110 = 54$$

$$10\bar{1}10\bar{1}0$$


$$100\bar{1}0\bar{1}0 = 64 - 8 - 2$$

- Can we further simplify the multiplier circuits?



 
# “Constant Coefficient Multiplication” (KCM)


Binary multiplier:  $Y = 231 * X = (2^7 + 2^6 + 2^5 + 2^2 + 2^1 + 2^0) * X$



 - CSD helps, but the multipliers are limited to shifts followed by adds.
  - CSD multiplier:  $Y = 231 * X = (2^8 - 2^5 + 2^3 - 2^0) * X$





 
- How about shift/add/shift/add ...?
  - KCM multiplier:  $Y = 231 * X = 7 * 33 * X = (2^3 - 2^0) * (2^5 + 2^0) * X$



- No simple algorithm exists to determine the optimal KCM representation.
- Most use exhaustive search method.

   
# Fixed Shifters / Rotators

- “fixed” shifters  
“hardwire” the shift amount into the circuit.
- Ex: verilog:  $X \gg 2$ 
  - (right shift  $X$  by 2 places)
- Fixed shift/rotator is nothing but wires!  
So what?



# Variable Shifters / Rotators

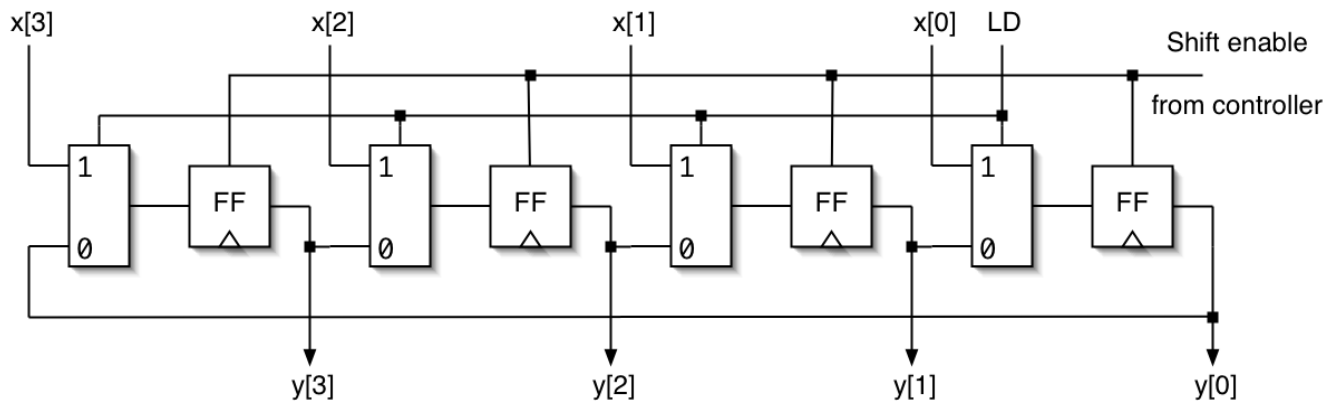
- Example:  $X \gg S$ , where  $S$  is unknown when we synthesize the circuit.
- Uses: shift instruction in processors (ARM includes a shift on every instruction), floating-point arithmetic, division/multiplication by powers of 2, etc.
- One way to build this is a simple shift-register:
  - a) Load word,
  - b) shift enable for  $S$  cycles,
  - c) read word.




- Worst case delay  $O(N)$ , not good for processor design.
- Can we do it in  $O(\log N)$  time and fit it in one cycle?
 
# Log Shifter / Rotator

- $\log(N)$  stages, each shifts (or not) by a power of 2 places,




# LUT Mapping of Log shifter

 


Efficient with 2to1 multiplexors, for instance, 3LUTs.

 Virtex6 has 6LUTs. Naturally makes 4to1 muxes:




Reorganize shifter to use 4to1 muxes.

 

Final stage uses F7 mux

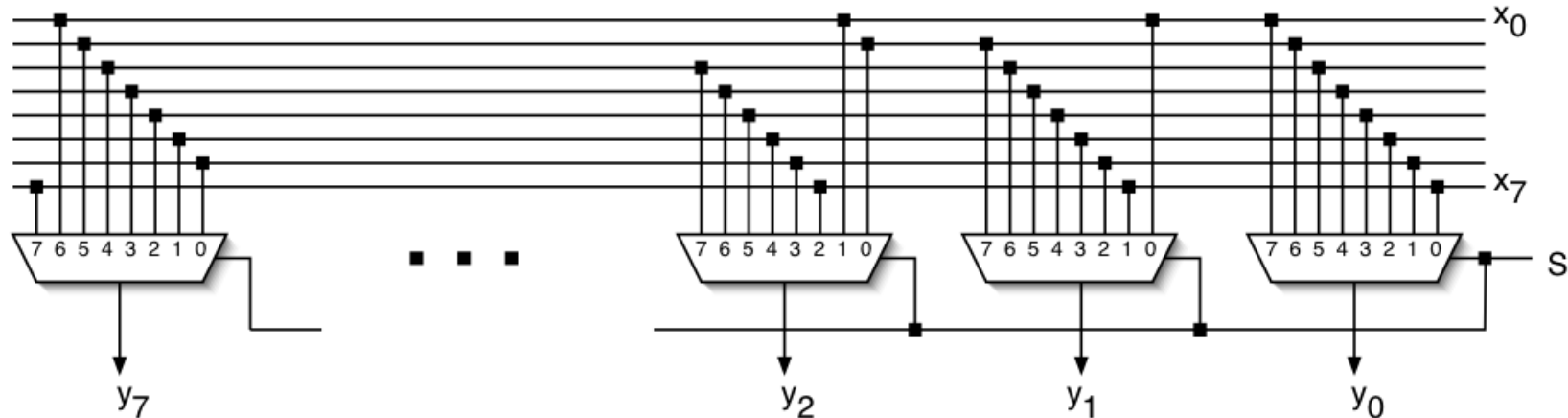
# “Improved” Shifter / Rotator

- How about this approach? Could it lead to even less delay?



- What is the delay of these big muxes?
- Look a transistor-level implementation?


# Barrel Shifter

 

Cost/delay?

- (don't forget the decoder)

# Connection Matrix

 


Generally useful structure:

- $N^2$  control points.
- What other interesting functions can it do?



# Cross-bar Switch

 

- $N \log(N)$  control signals.
- Supports all interesting permutations
  - All one-to-one and one-to-many connections.
- Commonly used in communication hardware (switches, routers).