

CS 61C: Great Ideas in Computer Architecture (Machine Structures)

Single-Cycle Processor Design

Instructors:
Randy H. Katz
David A. Patterson

<http://inst.eecs.Berkeley.edu/~cs61c/fa10>

10/30/10 Fall 2010 -- Lecture #26 1

Agenda

- MIPS-lite Datapath
- Administrivia
- Technology Break
- CPU Timing

10/30/10 Fall 2010 -- Lecture #26 2

Agenda

- MIPS-lite Datapath
- Administrivia
- Technology Break
- CPU Timing

10/30/10 Fall 2010 -- Lecture #26 3

The MIPS-lite Subset

- ADDU and SUBU

31	26	21	16	11	6	0
op	rs	rt	rd	shamt	funct	
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	
- OR Immediate:

31	26	21	16	0
op	rs	rt	immediate	
6 bits	5 bits	5 bits	16 bits	
- LOAD and STORE Word

31	26	21	16	0
op	rs	rt	immediate	
6 bits	5 bits	5 bits	16 bits	
- BRANCH:

31	26	21	16	0
op	rs	rt	immediate	
6 bits	5 bits	5 bits	16 bits	

10/30/10 Fall 2010 -- Lecture #26 4

Register Transfer Language (RTL)

- RTL gives the meaning of the instructions


```
{op, rs, rt, rd, shamt, funct} ← MEM[ PC ]
{op, rs, rt, Imm16} ← MEM[ PC ]
```
- All start by fetching the instruction

Inst Register Transfers

```
ADDU R[rd] ← R[rs] + R[rt]; PC ← PC + 4
SUBU R[rd] ← R[rs] - R[rt]; PC ← PC + 4
ORI  R[rt] ← R[rs] | zero_ext(Imm16); PC ← PC + 4
LOAD R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
STORE MEM[ R[rs] + sign_ext(Imm16) ] ← R[rt]; PC ← PC + 4
BEQ  if ( R[rs] == R[rt] )
      then PC ← PC + 4 + (sign_ext(Imm16) || 00)
      else PC ← PC + 4
```

10/30/10 Fall 2010 -- Lecture #26 5

Processor Design Process

- Five steps to design a processor:
 - Step 1: Analyze instruction set to determine datapath requirements
 - Step 2: Select set of datapath components & establish clock methodology
 - Step 3: Assemble datapath components that meet the requirements
 - Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer
 - Step 5: Assemble the control logic

10/30/10 Fall 2010 -- Lecture #26 6

Step 1: Requirements of the Instruction Set


- Memory (MEM)
 - Instructions & data (will use one for each)
- Registers (R: 32 x 32)
 - Read RS
 - Read RT
 - Write RT or RD
- PC
- Extender (sign/zero extend)
- Add/Sub/OR unit for operation on register(s) or extended immediate
- Add 4 (+ maybe extended immediate) to PC
- Compare registers?

10/30/10

Fall 2010 – Lecture #26

7

Generic Steps of Datapath

 


10/30/10

Fall 2010 – Lecture #26

8

Step 2: Components of the Datapath

 - Combinational Elements
- Storage Elements + Clocking Methodology
- Building Blocks



10/30/10

Fall 2010 – Lecture #26

9

ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:


```
ADDU R[rd] = R[rs] + R[rt]; ...
SUBU R[rd] = R[rs] - R[rt]; ...
ORI  R[rt] = R[rs] | zero_ext(Imm16)...
BEQ  if ( R[rs] == R[rt] )...
```
- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND, Set Less Than (1 if A < B, 0 otherwise)
- ALU follows Chapter 5


10/30/10

Fall 2010 – Lecture #26

10

Storage Element: Idealized Memory

- Memory (idealized)
 - One input bus: Data In
 - One output bus: Data Out
- Memory word is found by:
 - Address selects the word to put on Data Out
 - Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
 - CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block: Address valid ⇒ Data Out valid after “access time”

 


10/30/10

Fall 2010 – Lecture #26

11

Storage Element: Register (Building Block)

 - Similar to D Flip Flop except
 - N-bit input and output
 - Write Enable input
- Write Enable:
 - Negated (or deasserted) (0): Data Out will not change
 - Asserted (1): Data Out will become Data In on positive edge of clock



10/30/10

Fall 2010 – Lecture #26

12

Storage Element: Register File

- Register File consists of 32 registers:
 - Two 32-bit output buses: busA and busB
 - One 32-bit input bus: busW
- Register is selected by:
 - RA (number) selects the register to put on busA (data)
 - RB (number) selects the register to put on busB (data)
 - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- Clock input (clk)
 - Clk input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - RA or RB valid \Rightarrow busA or busB valid after "access time."

10/30/10 Fall 2010 - Lecture #26 13

Step 3: Assemble DataPath Meeting Requirements

- Register Transfer Requirements \Rightarrow Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation
- Common RTL operations
 - Fetch the Instruction: $mem[PC]$
 - Update the program counter:
 - Sequential Code: $PC \leftarrow PC + 4$
 - Branch and Jump: $PC \leftarrow$ "something else"

10/30/10 Fall 2010 - Lecture #26 14

Step 3: Add & Subtract

- $R[rd] = R[rs] \text{ op } R[rt]$ (addu rd,rs,rt)
 - Ra, Rb, and Rr come from instruction's Rs, Rt, and Rd fields
- ALUctr and RegWr: control logic after decoding the instruction

31	26	21	16	11	6	0
op	rs	rt	rd	shamt	funct	
6 bits		5 bits	5 bits	5 bits	5 bits	6 bits

- ... Already defined the register file & ALU

10/30/10 Fall 2010 - Lecture #26 15

Agenda

- MIPS-lite
- Administrivia
- Technology Break
- CPU Design

10/30/10 Fall 2010 - Lecture #26 16

Agenda

- MIPS-lite
- Administrivia
- Technology Break
- CPU Design

10/30/10 Fall 2010 - Lecture #26 17

Agenda

- MIPS-lite
- Administrivia
- Technology Break
- CPU Timing

10/30/10 Fall 2010 - Lecture #26 18

Clocking Methodology

- Storage elements clocked by same edge
- Flip-flops (FFs) and combinational logic have some delays
 - Gates: delay from input change to output change
 - Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF (set-up time), and we have the usual clock-to-Q delay
- “Critical path” (longest path through logic) determines length of clock period

10/30/10 Fall 2010 – Lecture #26 19

Register-Register Timing: One Complete Cycle

10/30/10 Fall 2010 – Lecture #26 20

Logical Operations with Immediate

- $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$

31	26	21	16	15	0
op rs rt immediate					
31 6 bits 5 bits 5 bits 16 15 16 bits 0					
0000000000000000 immediate					
16 bits 16 bits					

But we're writing to Rt register??

10/30/10 Fall 2010 – Lecture #26 21

Logical Operations with Immediate

- $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$

31	26	21	16	15	0
op rs rt immediate					
31 6 bits 5 bits 5 bits 16 15 16 bits 0					
0000000000000000 immediate					
16 bits 16 bits					

What about Rt register read??

10/30/10 Fall 2010 – Lecture #26 22

Load Operations

- $R[rt] = Mem[R[rs] + SignExt[imm16]]$
- Example: lw rt, rs, imm16

31	26	21	16	15	0
op rs rt immediate					
6 bits 5 bits 5 bits 16 bits					

10/30/10 Fall 2010 – Lecture #26 23

Load Operations

- $R[rt] = Mem[R[rs] + SignExt[imm16]]$
- Example: lw rt, rs, imm16

31	26	21	16	15	0
op rs rt immediate					
6 bits 5 bits 5 bits 16 bits					

10/30/10 Fall 2010 – Lecture #26 24

RTL: The Add Instruction

31	26	21	16	11	6	0					
op		rs		rt		rd		shamt		funct	
6 bits		5 bits		5 bits		5 bits		5 bits		6 bits	

add rd, rs, rt

- MEM[PC] Fetch the instruction from memory
- R[rd] = R[rs] + R[rt] The actual operation
- PC = PC + 4 Calculate the next instruction's address

10/30/10 Fall 2010 - Lecture #26 25

Instruction Fetch Unit at the Beginning of Add

- Fetch the instruction from Instruction memory:
Instruction = MEM[PC]
- same for all instructions

10/30/10 Fall 2010 - Lecture #26 26

Single Cycle Datapath during Add

31	26	21	16	11	6	0					
op		rs		rt		rd		shamt		funct	

R[rd] = R[rs] + R[rt]

10/30/10 Fall 2010 - Lecture #26 27

Instruction Fetch Unit at End of Add

- PC = PC + 4
- Same for all instructions except: Branch and Jump

10/30/10 Fall 2010 - Lecture #26 28

Single Cycle Datapath during Or Immediate

31	26	21	16	immediate							
op		rs		rt							

- R[rt] = R[rs] OR ZeroExt[Imm16]**

10/30/10 Fall 2010 - Lecture #26 29

Single Cycle Datapath during Or Immediate

31	26	21	16	immediate							
op		rs		rt							

- R[rt] = R[rs] OR ZeroExt[Imm16]**

10/30/10 Fall 2010 - Lecture #26 30

