

inst.eecs.berkeley.edu/~cs61c
UC Berkeley CS61C : Machine Structures

**Lecture 25 –
 Representations of Combinational Logic Circuits**



Senior Lecturer SOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia

Conway's Life Logic Gates \Rightarrow

Berlekamp, Conway and

Guy in their "Winning Ways" series
 showed how a glider was a 1, no
 glider a 0, & how to build logic gates!




en.wikipedia.org/wiki/Conway%27s_Game_of_Life

CS61C L25 Representations of Combinational Logic Circuits (1)

Garcia, Fall 2014 © UCB

Truth Tables

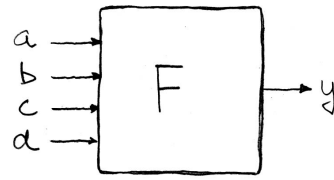

How many Fs
 (4-input devices)
 @ Radio Shack?



CS61C L25 Representations of Combinational Logic Circuits (2)

a	b	c	d	y
0	0	0	0	F(0,0,0,0)
0	0	0	1	F(0,0,0,1)
0	0	1	0	F(0,0,1,0)
0	0	1	1	F(0,0,1,1)
0	1	0	0	F(0,1,0,0)
0	1	0	1	F(0,1,0,1)
0	1	1	0	F(0,1,1,0)
0	1	1	1	F(0,1,1,1)
1	0	0	0	F(1,0,0,0)
1	0	0	1	F(1,0,0,1)
1	0	1	0	F(1,0,1,0)
1	0	1	1	F(1,0,1,1)
1	1	0	0	F(1,1,0,0)
1	1	0	1	F(1,1,0,1)
1	1	1	0	F(1,1,1,0)
1	1	1	1	F(1,1,1,1)

Garcia, Fall 2014 © UCB

TT Example #1: 1 iff one (not both) a,b=1


a	b	y
0	0	0
0	1	1
1	0	1
1	1	0



CS61C L25 Representations of Combinational Logic Circuits (4)

Garcia, Fall 2014 © UCB

TT Example #2: 2-bit adder

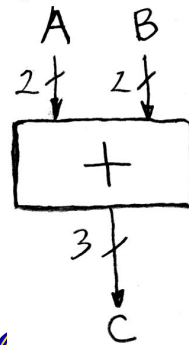

CS61C L25 Representations of Combinational Logic Circuits (5)

A	B	C
$a_1 a_0$	$b_1 b_0$	$c_2 c_1 c_0$
00	00	000
00	01	001
00	10	010
00	11	011
01	00	001
01	01	010
01	10	011
01	11	100
10	00	010
10	01	011
10	10	100
10	11	101
11	00	011
11	01	100
11	10	101
11	11	110

How
 Many
 Rows?

Garcia, Fall 2014 © UCB

TT Example #3: 32-bit unsigned adder

A	B	C
000 ... 0	000 ... 0	000 ... 00
000 ... 0	000 ... 1	000 ... 01
.	.	.
.	.	.
.	.	.
111 ... 1	111 ... 1	111 ... 10

How
 Many
 Rows?



CS61C L25 Representations of Combinational Logic Circuits (6)

Garcia, Fall 2014 © UCB

TT Example #4: 3-input majority circuit


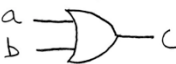

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



CS61C L25 Representations of Combinational Logic Circuits (7)

Garcia, Fall 2014 © UCB

Logic Gates (1/2)

AND		ab	c
		00	0
		01	0
		10	0
OR		ab	c
		00	0
		01	1
		10	1
NOT		a	b
		0	1
		1	0



CS61C L25 Representations of Combinational Logic Circuits (8)

Garcia, Fall 2014 © UCB

And vs. Or review – Dan's mnemonic

AND Gate

Symbol



Definition


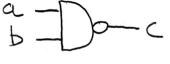
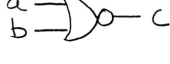
A	B	C
0	0	0
0	1	0
1	0	0
1	1	1



CS61C L25 Representations of Combinational Logic Circuits (9)

Garcia, Fall 2014 © UCB

Logic Gates (2/2)

XOR		ab	c
		00	0
		01	1
		10	1
NAND		ab	c
		00	1
		01	1
		10	1
NOR		ab	c
		00	1
		01	0
		10	0
		11	0



CS61C L25 Representations of Combinational Logic Circuits (10)

Garcia, Fall 2014 © UCB

2-input gates extend to n-inputs

• N-input XOR is the only one which isn't so obvious

• It's simple: XOR is a 1 iff the # of 1s at its input is odd ⇒

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1




CS61C L25 Representations of Combinational Logic Circuits (11)

Garcia, Fall 2014 © UCB

Truth Table ⇒ Gates (e.g., majority circ.)

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

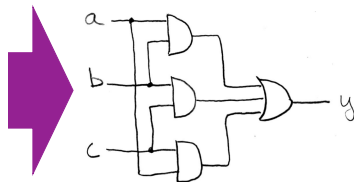


CS61C L25 Representations of Combinational Logic Circuits (12)

Garcia, Fall 2014 © UCB

Truth Table ⇒ Gates (e.g., FSM circ.)

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

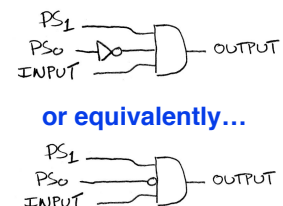

or equivalently...



CS61C L25 Representations of Combinational Logic Circuits (13)

Garcia, Fall 2014 © UCB

Administrivia

- How many hours on project 2 so far?
 - 0-10
 - 10-20
 - 30-40
 - 50-60
 - 60-70




CS61C L25 Representations of Combinational Logic Circuits (14)

Garcia, Fall 2014 © UCB

Boolean Algebra

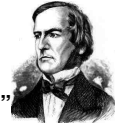- George Boole, 19th Century mathematician
- Developed a mathematical system (algebra) involving logic
 - later known as “Boolean Algebra”
- Primitive functions: AND, OR and NOT
- The power of BA is there's a one-to-one correspondence between circuits made up of AND, OR and NOT gates and equations in BA




CS61C L25 Representations of Combinational Logic Circuits (15)

Garcia, Fall 2014 © UCB

+ means OR, • means AND, \bar{x} means NOT

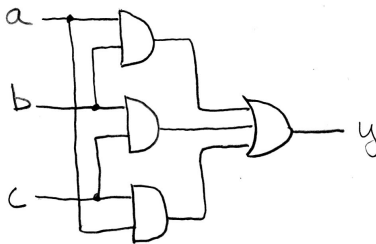Boolean Algebra (e.g., for majority fun.)



$$y = a \cdot b + a \cdot c + b \cdot c$$

$$y = ab + ac + bc$$




CS61C L25 Representations of Combinational Logic Circuits (16)


Garcia, Fall 2014 © UCB

Boolean Algebra (e.g., for FSM)

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

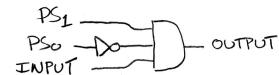

or equivalently...

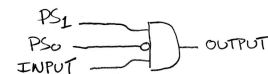


$$y = PS_1 \cdot \overline{PS_0} \cdot INPUT$$



CS61C L25 Representations of Combinational Logic Circuits (17)

Garcia, Fall 2014 © UCB

BA: Circuit & Algebraic Simplification

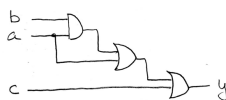


original circuit

$$y = ((ab) + a) + c$$

equation derived from original circuit

$$\begin{aligned} &= ab + a + c \\ &= a(b + 1) + c \\ &= a(1) + c \\ &= a + c \end{aligned}$$

algebraic simplification

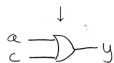

simplified circuit

BA also great for circuit verification
Circ X = Circ Y?
use BA to prove!



CS61C L25 Representations of Combinational Logic Circuits (18)

Garcia, Fall 2014 © UCB

Laws of Boolean Algebra

$x \cdot \bar{x} = 0$	$x + \bar{x} = 1$	complementarity
$x \cdot 0 = 0$	$x + 1 = 1$	laws of 0's and 1's
$x \cdot 1 = x$	$x + 0 = x$	identities
$x \cdot x = x$	$x + x = x$	idempotent law
$x \cdot y = y \cdot x$	$x + y = y + x$	commutativity
$(xy)z = x(yz)$	$(x + y) + z = x + (y + z)$	associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	distribution
$xy + x = x$	$(x + y)x = x$	uniting theorem
$\bar{x}y + x = x + y$	$(\bar{x} + y)x = xy$	uniting theorem v.2
$\bar{x} \cdot \bar{y} = \overline{x + y}$	$\bar{x} + \bar{y} = \overline{x \cdot y}$	DeMorgan's Law



CS61C L25 Representations of Combinational Logic Circuits (19)

Garcia, Fall 2014 © UCB

Boolean Algebraic Simplification Example

$$\begin{aligned}
 y &= ab + a + c \\
 &= a(b + 1) + c && \text{distribution, identity} \\
 &= a(1) + c && \text{law of 1's} \\
 &= a + c && \text{identity}
 \end{aligned}$$




Canonical forms (1/2)

abc	y	Sum-of-products (ORs of ANDs)
$\bar{a} \cdot \bar{b} \cdot \bar{c}$	000	
$\bar{a} \cdot \bar{b} \cdot c$	001	
	010	
	011	
$a \cdot \bar{b} \cdot \bar{c}$	100	
	101	
$a \cdot b \cdot \bar{c}$	110	
	111	



Canonical forms (2/2)
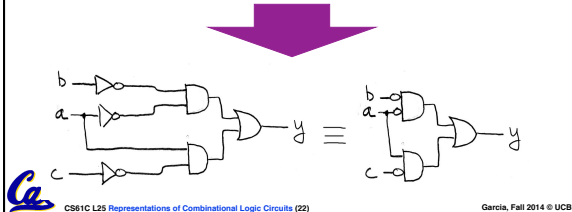
$$\begin{aligned}
 y &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c} \\
 &= \bar{a}\bar{b}(\bar{c} + c) + a\bar{b}(\bar{c} + c) && \text{distribution} \\
 &= \bar{a}\bar{b}(1) + a\bar{b}(1) && \text{complementarity} \\
 &= \bar{a}\bar{b} + a\bar{b} && \text{identity}
 \end{aligned}$$



Peer Instruction

- 1) $(a+b) \cdot (\bar{a}+b) = b$
- 2) N-input gates can be thought of cascaded 2-input gates. I.e., $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$ where Δ is one of AND, OR, XOR, NAND
- 3) You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	123
a:	FFF
a:	FFT
b:	FTF
b:	FTT
c:	TFF
d:	TFT
e:	TTT



"And In conclusion..."

- Pipeline big-delay CL for faster clock
- Finite State Machines extremely useful
 - You'll see them again in 150, 152 & 164
- Use this table and techniques we learned to transform from 1 to another

