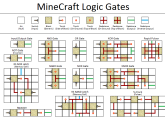


Lecture 26 – Combinational Logic Blocks




Senior Lecturer SOE Dan Garcia
www.cs.berkeley.edu/~ddgarcia

MineCraft Logic Gates ⇒
 Using redstone circuits, which are “structures that can be built to active or control mechanisms”, you can create all the logic gates using MineCraft.



Review

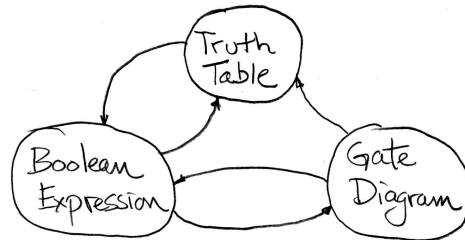
- Use this table and techniques we learned to transform from 1 to another



Today


- Data Multiplexors
- Arithmetic and Logic Unit
- Adder/Subtractor

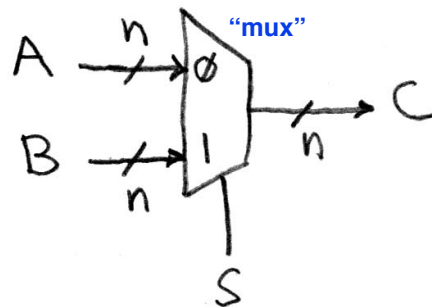Data Multiplexor (here 2-to-1, n-bit-wide)



N instances of 1-bit-wide mux


How many rows in TT?

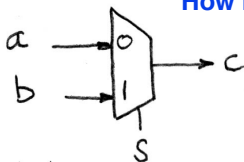

$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1)) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$


How do we build a 1-bit-wide mux?

$$\bar{s}a + sb$$

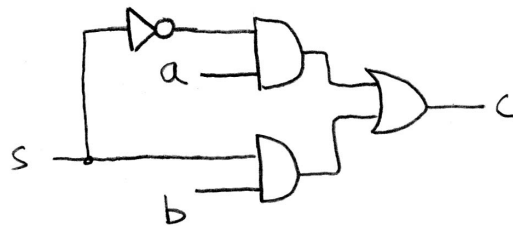

4-to-1 Multiplexor?

How many rows in TT?

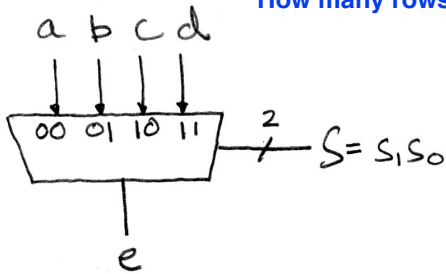


$$e = \overline{s_1}\overline{s_0}a + \overline{s_1}s_0b + s_1\overline{s_0}c + s_1s_0d$$



Is there any other way to do it?

Hint: NCAA tourney!

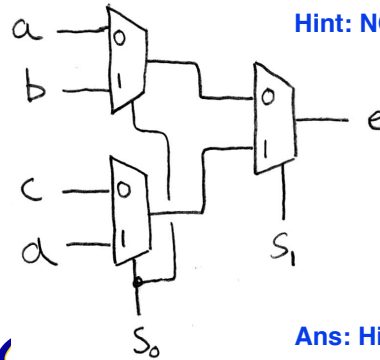


Ans: Hierarchically!



Arithmetic and Logic Unit

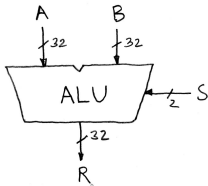
- Most processors contain a special logic block called "Arithmetic and Logic Unit" (ALU)
- We'll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR



when S=00, R=A+B
 when S=01, R=A-B
 when S=10, R=A AND B
 when S=11, R=A OR B



Our simple ALU

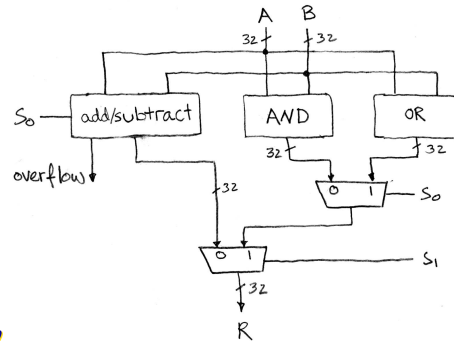

Administrivia

- How did you find project 2?
 - a) Hated it
 - b) Disliked it
 - c) Neutral
 - d) Liked it
 - e) Loved it



Adder/Subtractor Design -- how?

- Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer



Adder/Subtractor – One-bit adder LSB...

	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0

a_0	b_0	s_0	c_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$



Adder/Subtractor – One-bit adder (1/2)...

	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0


a_i	b_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i =$$

$$c_{i+1} =$$



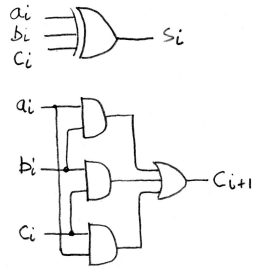Adder/Subtractor – One-bit adder (2/2)...




$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$



N 1-bit adders \Rightarrow 1 N-bit adder

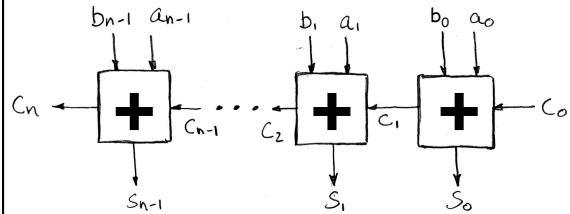


What about overflow?
Overflow = c_n ?



What about overflow?

• Consider a 2-bit signed # & overflow:

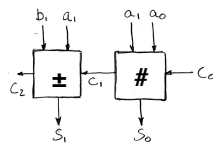- 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



• Highest adder

- $C_1 = \text{Carry-in} = C_{in}$, $C_2 = \text{Carry-out} = C_{out}$
- No C_{out} or $C_{in} \Rightarrow$ NO overflow!

What op? • C_{in} , and $C_{out} \Rightarrow$ NO overflow!


- C_{in} , but no $C_{out} \Rightarrow$ A, B both > 0, overflow!
- C_{out} , but no $C_{in} \Rightarrow$ A, B both < 0, overflow!



What about overflow?

• Consider a 2-bit signed # & overflow:

- 10 = -2
- 11 = -1
- 00 = 0
- 01 = 1

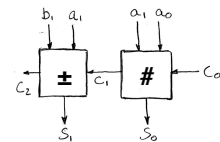


• Overflows when...

- C_{in} , but no $C_{out} \Rightarrow$ A, B both > 0, overflow!
- C_{out} , but no $C_{in} \Rightarrow$ A, B both < 0, overflow!

$$\text{overflow} = c_n \text{ XOR } c_{n-1}$$



Extremely Clever Subtractor

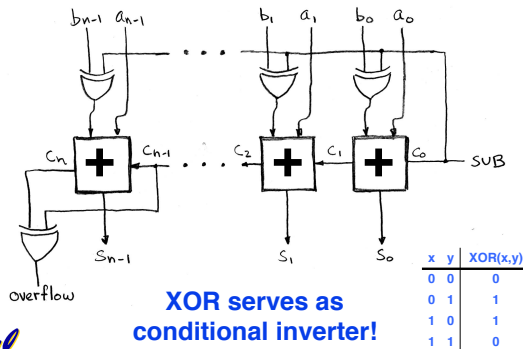

Cal

CS61C L26 Combinational Logic Blocks (19)

Garcia, Fall 2014 © UCB

Peer Instruction

- 1) Truth table for mux with 4-bits of signals has 2^4 rows
- 2) We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl

	12
a)	FF
b)	FT
c)	TF
d)	TT

Cal

CS61C L26 Combinational Logic Blocks (20)

Garcia, Fall 2014 © UCB

“And In conclusion...”

- Use muxes to select among input
 - S input bits selects 2^S inputs
 - Each input can be n-bits wide, indep of S
- Can implement muxes hierarchically
- ALU can be implemented using a mux
 - Coupled with basic block elements
- N-bit adder-subtractor done using N 1-bit adders with XOR gates on input
 - XOR serves as conditional inverter

Cal

CS61C L26 Combinational Logic Blocks (22)

Garcia, Fall 2014 © UCB