

CS 61C  
Great Ideas in Computer Architecture  
(Machine Structures)

Lecture: Single-Cycle CPU  
Datapath Design

Guest Lecturer TA: Shreyas Chand  
<http://inst.eecs.berkeley.edu/~cs61c>


## Review

- Use muxes to select among inputs
  - S control bits selects from  $2^S$  inputs
  - Each input can be n-bits wide, indep of S
- Can implement muxes hierarchically
- ALU can be implemented using a mux
  - Coupled with basic block elements
- N-bit adder-subtractor done using N 1-bit adders with XOR gates on input
  - XOR serves as conditional inverter

## Agenda

- Stages of the Datapath
- Datapath Instruction Walkthroughs
- Datapath Design

## Five Components of a Computer

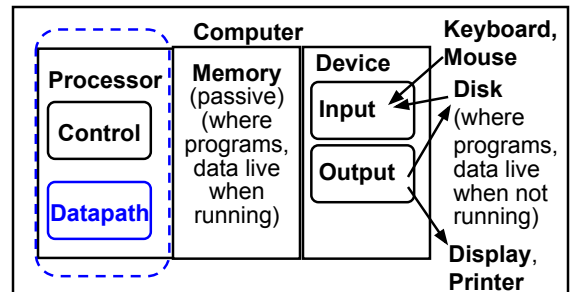

## The CPU

- **Processor (CPU)**: the active part of the computer that does all the work (data manipulation and decision-making)
- **Datapath**: portion of the processor that contains hardware necessary to perform operations required by the processor (**the brawn**)
- **Control**: portion of the processor (also in hardware) that tells the datapath what needs to be done (**the brain**)

## Stages of the Datapath : Overview

- Problem: a single, atomic block that “executes an instruction” (performs all necessary operations beginning with fetching the instruction) would be too bulky and inefficient
- Solution: break up the process of “executing an instruction” into **stages**, and then connect the stages to create the whole datapath
  - smaller stages are easier to design
  - easy to optimize (change) one stage without touching the others

## Five Stages of the Datapath

- Stage 1: *Instruction Fetch*
- Stage 2: *Instruction Decode*
- Stage 3: *ALU (Arithmetic-Logic Unit)*
- Stage 4: *Memory Access*
- Stage 5: *Register Write*

## Stages of the Datapath (1/5)

- There is a wide variety of MIPS instructions: so what general steps do they have in common?
- Stage 1: **Instruction Fetch**
  - no matter what the instruction, the 32-bit instruction word must first be fetched from memory (the cache-memory hierarchy)
  - also, this is where we **Increment PC** (that is,  $PC = PC + 4$ , to point to the next instruction: byte addressing so + 4)

## Stages of the Datapath (2/5)

- Stage 2: **Instruction Decode**
  - upon fetching the instruction, we next gather data from the fields (decode all necessary instruction data)
  - first, read the `opcode` to determine instruction type and field lengths
  - second, read in data from all necessary registers
    - for `add`, read two registers
    - for `addi`, read one register
    - for `jal`, no reads necessary

## Stages of the Datapath (3/5)

- Stage 3: **ALU (Arithmetic-Logic Unit)**
  - the real work of most instructions is done here: arithmetic (+, -, \*, /), shifting, logic (&, |), comparisons (`slt`)
  - what about loads and stores?
    - `lw $t0, 40($t1)`
    - the address we are accessing in memory = the value in `$t1` PLUS the value 40
    - so we do this addition in this stage


## Stages of the Datapath (4/5)

- Stage 4: **Memory Access**
  - actually only the load and store instructions do anything during this stage; the others remain idle during this stage or skip it all together
  - since these instructions have a unique step, we need this extra stage to account for them
  - as a result of the cache system, this stage is expected to be fast

## Stages of the Datapath (5/5)

- Stage 5: **Register Write**
  - most instructions write the result of some computation into a register
  - examples: arithmetic, logical, shifts, loads, `slt`
  - what about stores, branches, jumps?
    - don't write anything into a register at the end
    - these remain idle during this fifth stage or skip it all together


## Generic Steps of Datapath

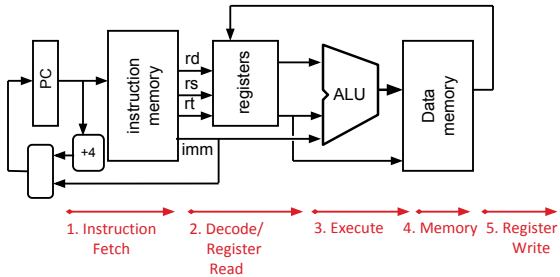

## Datapath Walkthroughs (1/3)

- `add $r3,$r1,$r2 # r3 = r1+r2`
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is an `add`, then read registers `$r1` and `$r2`
  - Stage 3: add the two values retrieved in Stage 2
  - Stage 4: idle (nothing to write to memory)
  - Stage 5: write result of Stage 3 into register `$r3`


## Example: `add` Instruction

 

## Datapath Walkthroughs (2/3)

- `slti $r3,$r1,17 # if (r1 < 17) r3 = 1 else r3 = 0`
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is an `slti`, then read register `$r1`
  - Stage 3: compare value retrieved in Stage 2 with the integer 17
  - Stage 4: idle
  - Stage 5: write the result of Stage 3 (1 if reg source was less than signed immediate, 0 otherwise) into register `$r3`


## Example: `slti` Instruction

 

## Datapath Walkthroughs (3/3)

- `sw $r3,17($r1) # Mem[r1+17]=r3`
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is a `sw`, then read registers `$r1` and `$r3`
  - Stage 3: add 17 to value in register `$r1` (retrieved in Stage 2) to compute address
  - Stage 4: write value in register `$r3` (retrieved in Stage 2) into memory address computed in Stage 3
  - Stage 5: idle (nothing to write into a register)

## Example: `sw` Instruction

 


## Why Five Stages? (1/2)

- Could we have a different number of stages?
  - Yes, and other architectures do
- So why does MIPS have five if instructions tend to idle for at least one stage?
  - Five stages are the union of all the operations needed by all the instructions.
  - One instruction uses all five stages: the `load`


## Why Five Stages? (2/2)

- `lw $r3, 17($r1) # r3=Mem[r1+17]`
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is a `lw`, then read register `$r1`
  - Stage 3: add 17 to value in register `$r1` (retrieved in Stage 2)
  - Stage 4: read value from memory address computed in Stage 3
  - Stage 5: write value read in Stage 4 into register `$r3`

## Example: `lw` Instruction

 


## Peer Instruction

 

How many places in this diagram will need a multiplexer to select one from multiple inputs?  
 a) 0    b) 1    c) 2    d) 3    e) 4 or more


## Peer Instruction

 

How many places in this diagram will need a multiplexer to select one from multiple inputs?  
 a) 0    b) 1    c) 2    **d) 3**    e) 4 or more
 
## Datapath and Control

- Datapath based on data transfers required to perform instructions
- Controller causes the right transfers to happen



## What Hardware Is Needed? (1/2)


- PC: a register that keeps track of address of the *next* instruction to be fetched
- General Purpose Registers
  - Used in Stages 2 (Read) and 5 (Write)
  - MIPS has 32 of these
- Memory
  - Used in Stages 1 (Fetch) and 4 (R/W)
  - Caches makes these stages as fast as the others (on average, otherwise multicycle stall)

## What Hardware Is Needed? (2/2)

- ALU
  - Used in Stage 3
  - Performs all necessary functions: arithmetic, logicals, etc.
- Miscellaneous Registers
  - One stage per clock cycle: Registers inserted between stages to hold intermediate data and control signals as they travel from stage to stage
  - Note: Register is a general purpose term meaning something that stores bits. Realize that not all registers are in the “register file”

 
## CPU Clocking (1/2)

- For each instruction, how do we control the flow of information through the datapath?
- Single Cycle CPU: All stages of an instruction completed within one long clock cycle
  - Clock cycle sufficiently long to allow each instruction to complete all stages without interruption within one cycle


 
## CPU Clocking (2/2)

- Alternative multiple-cycle CPU: only one stage of instruction per clock cycle
  - Clock is made as long as the slowest stage



- Several significant advantages over single cycle execution: Unused stages in a particular instruction can be skipped OR instructions can be pipelined (overlapped)

## Processor Design

- Analyze instruction set architecture (ISA) to determine datapath requirements
  - Meaning of each instruction is given by register transfers
  - Datapath must include storage element for ISA registers
  - Datapath must support each register transfer
- Select set of datapath components and establish clocking methodology
- Assemble datapath components to meet requirements
- Analyze each instruction to determine sequence of control point settings to implement the register transfer
- Assemble the control logic to perform this sequencing

## Summary

- CPU design involves Datapath, Control
  - 5 Stages for MIPS Instructions
    1. Instruction Fetch
    2. Instruction Decode & Register Read
    3. ALU (Execute)
    4. Memory
    5. Register Write
- Datapath timing: single long clock cycle or one short clock cycle per stage

## Instruction Level Parallelism

