


**CS 61C: Great Ideas in Computer Architecture (Machine Structures)**  
**Lecture 28: Single-Cycle CPU**  
*Datapath Control Part 1*

Guest Lecturer: Sagar Karandikar  
<http://inst.eecs.berkeley.edu/~cs61c/>

<http://research.microsoft.com/apps/pubs/default.aspx?id=212001>  
**Technology In the News**  
**Microsoft “Catapult”, ISCA 2014**

FPGAs are “programmable” hardware used by computer architects and digital circuit designers, lie somewhere between CPUs and custom chips (ASICs).




“Microsoft published a paper at ISCA about using FPGAs in datacenters for page ranking processing for Bing. In a test deployment, MS reported up to 95% more throughput for only 10% more power. The added TCO was less than 30%. Microsoft used Altera Stratix V FPGAs in a PCIe form-factor with 8GB of DDR3 RAM on each board. The FPGAs were connected using a 10Gb SAS network.” - AnandTech

### Review

- CPU design involves Datapath, Control
  - 5 Stages for MIPS Instructions
    1. Instruction Fetch
    2. Instruction Decode & Register Read
    3. ALU (Execute)
    4. Memory
    5. Register Write
- Datapath timing: single long clock cycle or one short clock cycle per stage

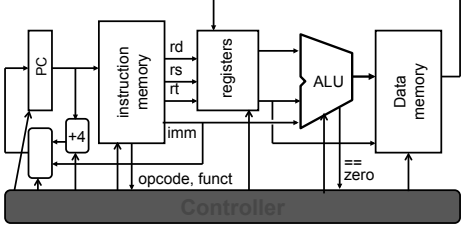
### Datapath and Control

- Datapath based on data transfers required to perform instructions
- Controller causes the right transfers to happen



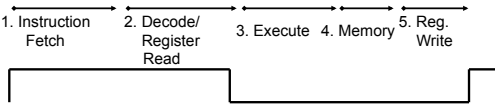
### CPU Clocking (1/2)

- For each instruction, how do we control the flow of information through the datapath?
- Single Cycle CPU: All stages of an instruction completed within one long clock cycle
  - Clock cycle sufficiently long to allow each instruction to complete all stages without interruption within one cycle


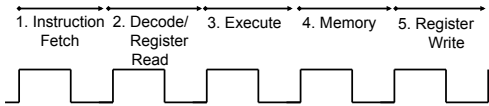
### CPU Clocking (2/2)

- Alternative multiple-cycle CPU: only one stage of instruction per clock cycle
  - Clock is made as long as the slowest stage




- Several significant advantages over single cycle execution:
  - Unused stages in a particular instruction can be skipped
  - OR instructions can be pipelined (overlapped)

### Agenda

- Stages of the Datapath
- Datapath Instruction Walkthroughs
- Datapath Design

### Five Components of a Computer

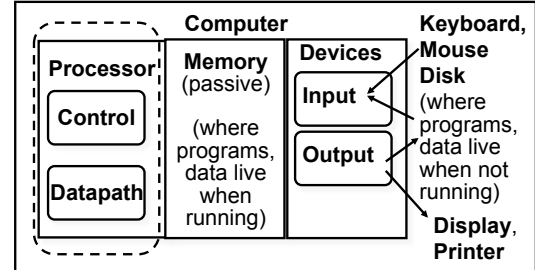


### Processor Design: 5 steps

- Step 1: Analyze instruction set to determine datapath requirements
  - Meaning of each instruction is given by register transfers
  - Datapath must include storage element for ISA registers
  - Datapath must support each register transfer
- Step 2: Select set of datapath components & establish clock methodology
- Step 3: Assemble datapath components that meet the requirements
- Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer
- Step 5: Assemble the control logic
 
### The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:



- The different fields are:
  - op: operation ("opcode") of the instruction
  - rs, rt, rd: the source and destination register specifiers
  - shamt: shift amount
  - funct: selects the variant of the operation in the "op" field
  - address / immediate: address offset or immediate value
  - target address: target address of jump instruction

### The MIPS-lite Subset

- **ADDU and SUBU**
  - addu rd,rs,rt
  - subu rd,rs,rt
- **OR Immediate:**
  - ori rt,rs,imm16
- **LOAD and STORE Word**
  - lw rt,rs,imm16
  - sw rt,rs,imm16
- **BRANCH:**
  - beq rs,rt,imm16

### Register Transfer Level (RTL)

- Colloquially called "Register Transfer Language"
- RTL gives the meaning of the instructions
- All start by fetching the instruction itself

```


{op, rs, rt, rd, shamt, funct} ← MEM[ PC ]
{op, rs, rt, Imm16} ← MEM[ PC ]
Inst Register Transfers
ADDU R[rd] ← R[rs] + R[rt]; PC ← PC + 4
SUBU R[rd] ← R[rs] - R[rt]; PC ← PC + 4
ORI R[rt] ← R[rs] | zero_ext(Imm16); PC ← PC + 4
LOAD R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
STORE MEM[ R[rs] + sign_ext(Imm16) ] ← R[rt]; PC ← PC + 4
BEQ if ( R[rs] == R[rt] )
    PC ← PC + 4 + {sign_ext(Imm16), 2'b00}
    else PC ← PC + 4
    
```

### Step 1: Requirements of the Instruction Set

- Memory (MEM)
  - Instructions & data (will use one for each)
- Registers (R: 32, 32-bit wide registers)
  - Read RS
  - Read RT
  - Write RT or RD
- Program Counter (PC)
- Extender (sign/zero extend)
- Add/Sub/OR/etc unit for operation on register(s) or extended immediate (ALU)
- Add 4 (+ maybe extended immediate) to PC
- Compare registers?
 
### Step 2: Components of the Datapath

- Combinational Elements
- Storage Elements + Clocking Methodology
- Building Blocks




### ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:
 

```
ADDU R[rd] = R[rs] + R[rt]; ...
SUBU R[rd] = R[rs] - R[rt]; ...
ORI  R[rt] = R[rs] | zero_ext(Imm16)...
```
- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND, Set Less Than (1 if A < B, 0 otherwise)
- ALU follows Chapter 5

 
### Storage Element: Idealized Memory

- “Magic” Memory
  - One input bus: Data In
  - One output bus: Data Out
- Memory word is found by:
  - For Read: Address selects the word to put on Data Out
  - For Write: Set Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
  - CLK input is a factor ONLY during write operation
  - During read operation, behaves as a combinational logic block: Address valid ⇒ Data Out valid after “access time”



 
### Storage Element: Register (Building Block)

- Similar to D Flip Flop except
  - N-bit input and output
  - Write Enable input
- Write Enable:
  - Negated (or deasserted) (0): Data Out will not change
  - Asserted (1): Data Out will become Data In on positive edge of clock



 
### Storage Element: Register File

- Register File consists of 32 registers:
  - Two 32-bit output busses: busA and busB
  - One 32-bit input bus: busW
- Register is selected by:
  - RA (number) selects the register to put on busA (data)
  - RB (number) selects the register to put on busB (data)
  - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- Clock input (clk)
  - Clk input is a factor ONLY during write operation
  - During read operation, behaves as a combinational logic block:
    - RA or RB valid ⇒ busA or busB valid after “access time.”



 
### Step 3a: Instruction Fetch Unit

- Register Transfer Requirements  $\Rightarrow$  Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation
- Common RTL operations
  - Fetch the Instruction:  $mem[PC]$
  - Update the program counter:
    - Sequential Code:  $PC \leftarrow PC + 4$
    - Branch and Jump:  $PC \leftarrow$  "something else"



 
### Step 3b: Add & Subtract

- $R[rd] = R[rs] \text{ op } R[rt]$  ( $addu \ rd, \ rs, \ rt$ )
  - $Ra, Rb,$  and  $Rw$  come from instruction's  $Rs, Rt,$  and  $Rd$  fields




 - ALUctr and RegWr: control logic after decoding the instruction





- ... Already defined the register file & ALU

### Clocking Methodology

 


- Storage elements clocked by same edge
- Flip-flops (FFs) and combinational logic have some delays
  - Gates: delay from input change to output change
  - Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF (set-up time), and we have the usual clock-to-Q delay
- "Critical path" (longest path through logic) determines length of clock period
  
### Register-Register Timing: One Complete Cycle


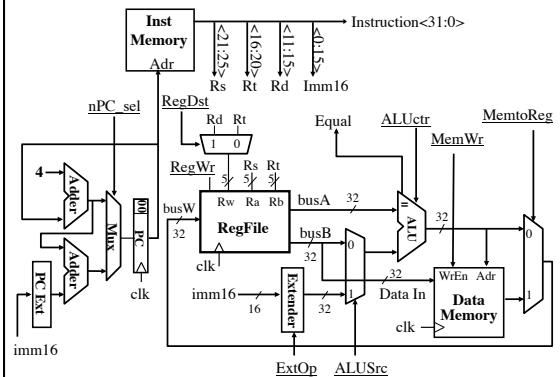
### Putting it All Together: A Single Cycle Datapath



### Processor Design: 3 of 5 steps

- Step 1: Analyze instruction set to determine datapath requirements
  - Meaning of each instruction is given by register transfers
  - Datapath must include storage element for ISA registers
  - Datapath must support each register transfer
- Step 2: Select set of datapath components & establish clock methodology
- Step 3: Assemble datapath components that meet the requirements
- Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer
- Step 5: Assemble the control logic