

# CS 61C Fall 2015

## Guerrilla Section 3: Synchronous Digital Systems

### Problem 1:


- a) Convert the following truth table to a Boolean expression and simplify it. An X means we don't care about the value of that output (it can be either 0 or 1).

A	B	C	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	X
1	1	1	X

- b) Draw the transition state diagram from a FSM that reads a binary string bit-by-bit and outputs whether the total number of 1s seen since the beginning is divisible by 3.



 - c) For the circuit below, assume that the setup time is 15ns, hold time is 30ns, and the AND gate delay is 10ns. If the clock rate is 10 MHz and x updates 25ns after the rising edge of the clock, what are the minimum and maximum values for the clk-to-Q delay to ensure proper functionality?



Min: \_\_\_\_\_ ns

Max: \_\_\_\_\_ ns

- d) Fill in the truth table for a 3-bit majority circuit and build it using logic gates. A 3-bit majority circuit outputs 1 if 2 or more bits are 1, otherwise it outputs 0.


A	B	C	Out
0	0	0	0
1	1	1	1

- e) Reduce the Boolean expression  $AB + ABC + ABCD + ABCDE + ABCDEF$  and draw the logic gate.

- f) Reduce the Boolean expression  $!(A + !B) * !(C + D + E) + (A + B)*(!C)$ . How many and/or/not gates needed?

 
**Problem 2:**

Assume all inputs (A, B) are clocked registers (note: A and B are separate from the registers shown below directly after them). For all registers assume clk-to-q is 1 ns, setup time is 1 ns, hold time is 1 ns and that they are initialized to 0. Assume the delay for each logic gate is 1 ns.



i. Find the max delay and the fastest possible clock rate such that the behavior of the ?

ii. Assume each clock cycle lasts 10 ns. Draw the signals below (assume registers are initially 0).

 

**Problem 3:**

Using only NAND gates build:

i) NOT GATE

ii) AND GATE

ii) OR GATE

ii) XOR GATE