

UC Berkeley  
Teaching Professor  
Dan Garcia

# CS61C


Great Ideas  
in  
**Computer Architecture**  
(a.k.a. Machine Structures)



UC Berkeley  
Professor  
Bora Nikolić

## Introduction to Synchronous Digital Systems (SDS) State

**Accumulator**

 


# Uses for State Elements

---

- **As a place to store values for some indeterminate amount of time:**
  - Register files (like x0-x31 on the RISC-V)
  - Memory (caches, and main memory)
- **Help control the flow of information between combinational logic blocks.**
  - State elements are used to hold up the movement of information at the inputs to combinational logic blocks and allow for orderly passage.
 
# Accumulator Example

- Why do we need to control the flow of information?



- Want:

$S = 0 ;$


`for (i=0 ; i<n ; i++)`

$S = S + X_i$

- Assume

- Each  $X$  value is applied in succession, one per cycle.
- After  $n$  cycles the sum is present on  $S$ .


# First try...Does this work?

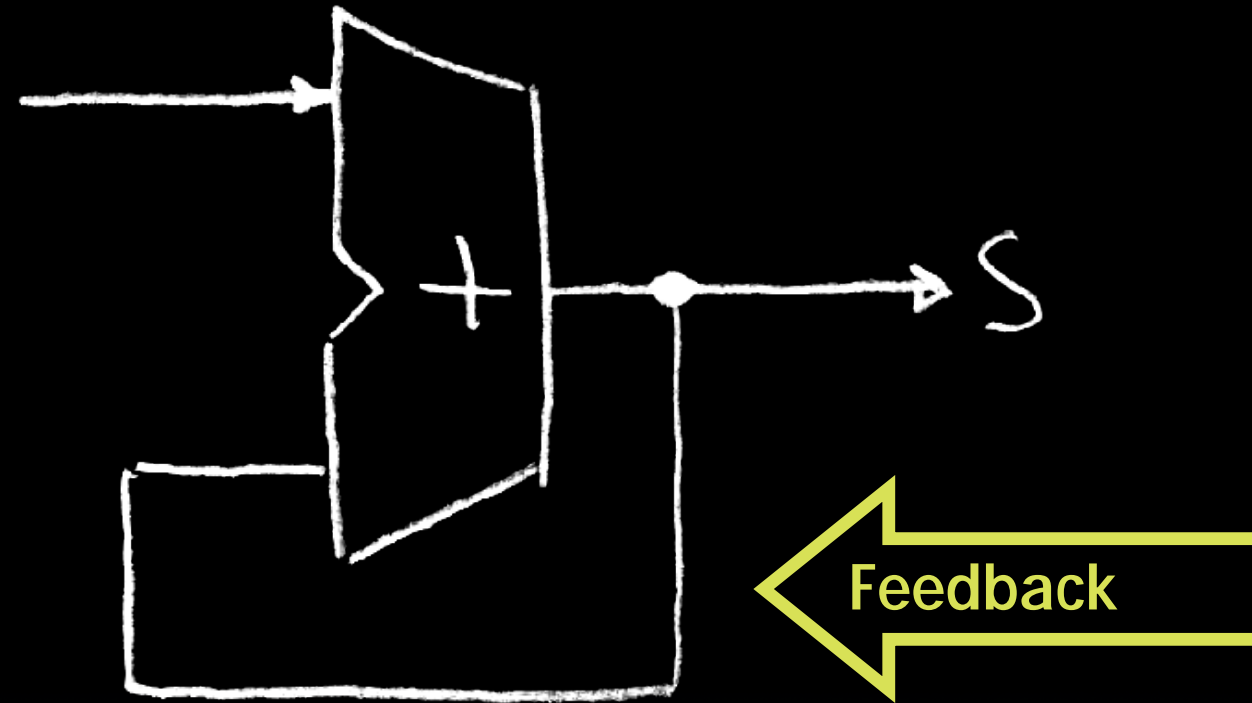


- **Nope!**
  - Reason #1... What is there to control the next iteration of the '**for**' loop?
  - Reason #2... How do we say: '**s=0**'?
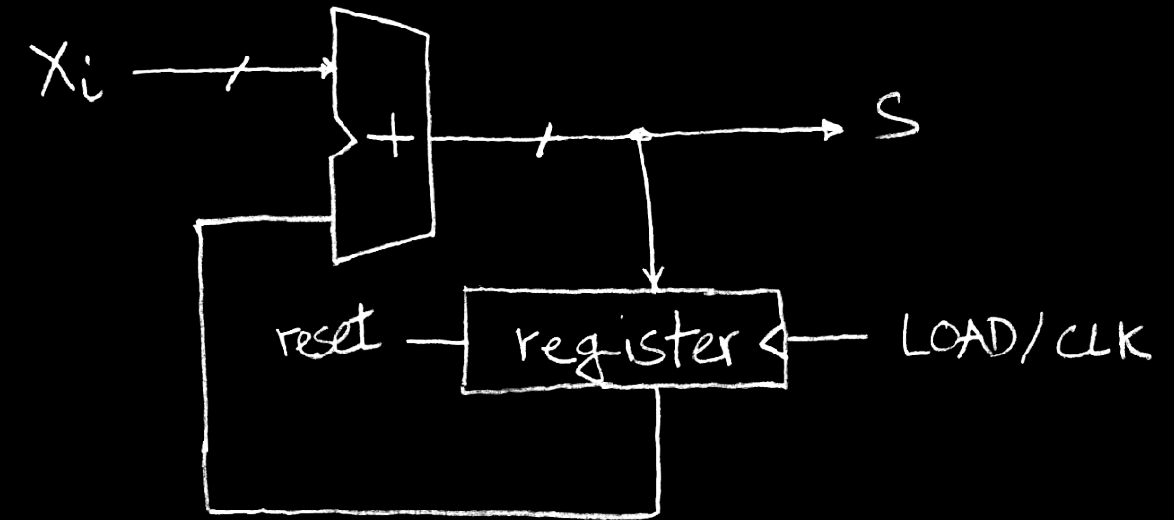
# Second try...How about this?

- Register is used to hold up the transfer of data to adder.




Rough timing...

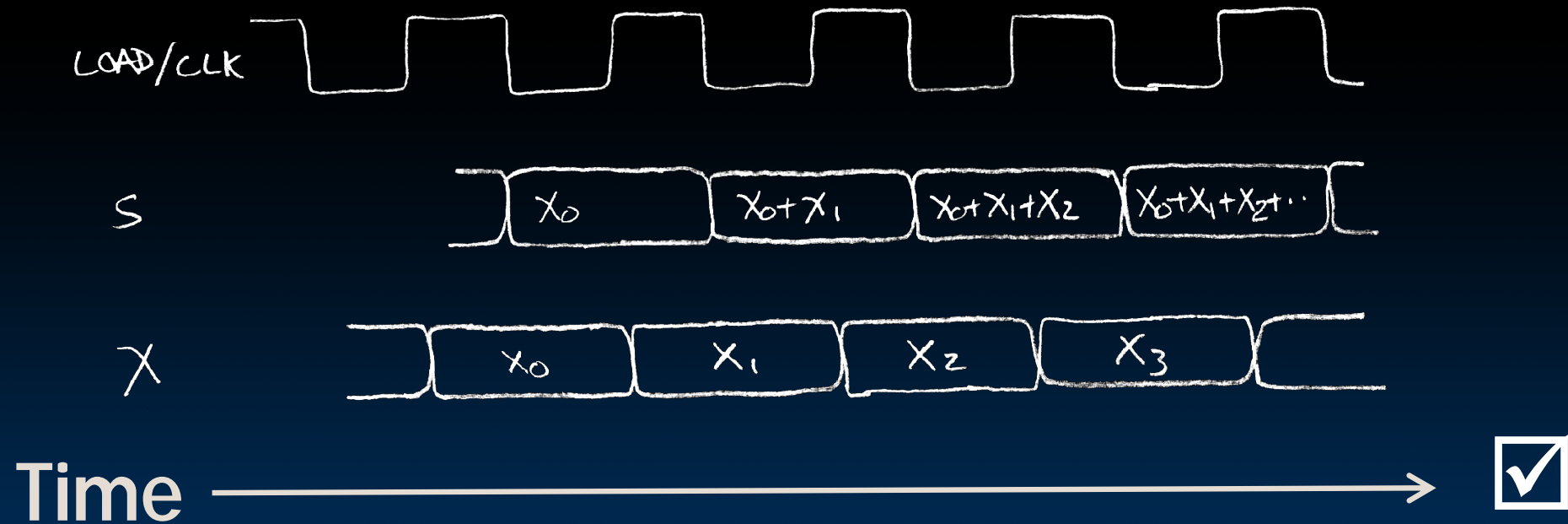

# Register Details

## Flip-flops

# Register Details...What's inside?

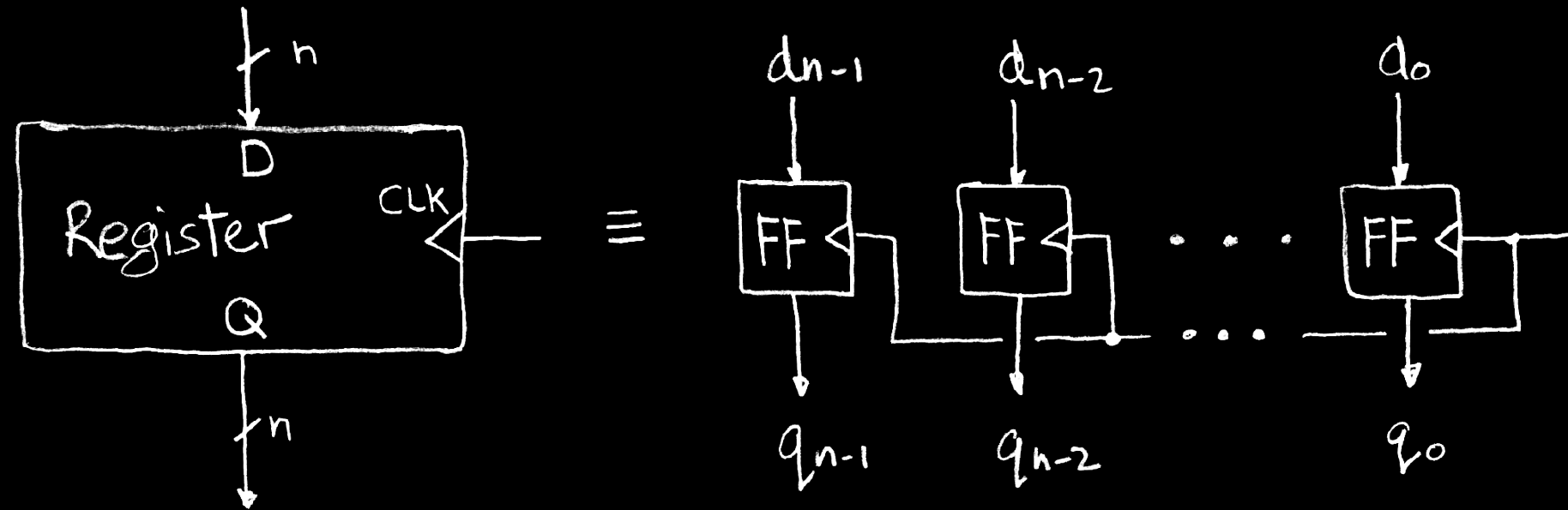


- n instances of a “**Flip-Flop**”
- **Flip-flop** name because the output flips and flops between and 0,1
- D is “data”, Q is “output”
- Also called “D-type Flip-Flop”
  - There used to be other types of flip-flops


 
# What's the timing of a Flip-flop? (1/2)



- Edge-triggered d-type flip-flop
  - This one is "rising edge-triggered"
  - Also called "positive edge"




There also exist "falling edge" FFs



- "On the rising edge of the clock, the input **d** is sampled and transferred to the output. At all other times, the input **d** is ignored."

- Example waveforms:

  



# What's the timing of a Flip-flop? (2/2)

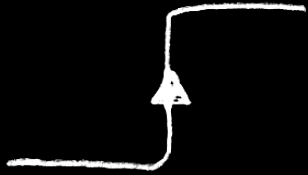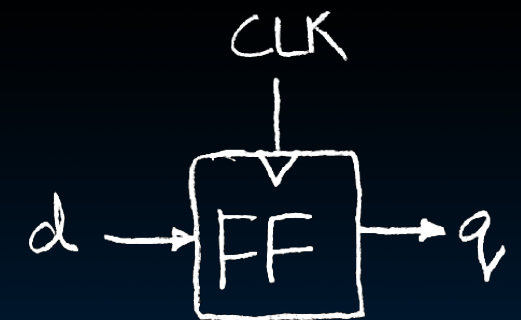 - Edge-triggered d-type flip-flop
  - This one is "rising edge-triggered" 
- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."
- Example waveforms (more detail):





# Accumulator Revisited
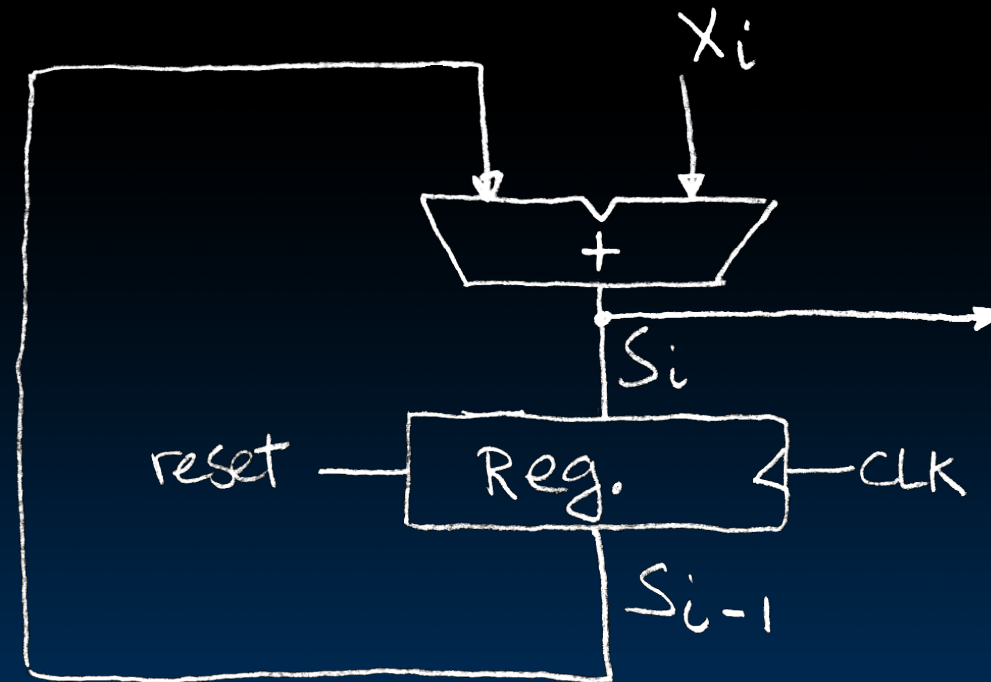 
# Accumulator Revisited (proper timing 1/2)



- Reset input to register is used to force it to all zeros (takes priority over D input).
- $S_{i-1}$  holds the result of the  $i^{\text{th}}-1$  iteration.
- Analyze circuit timing starting at the output of the register.
 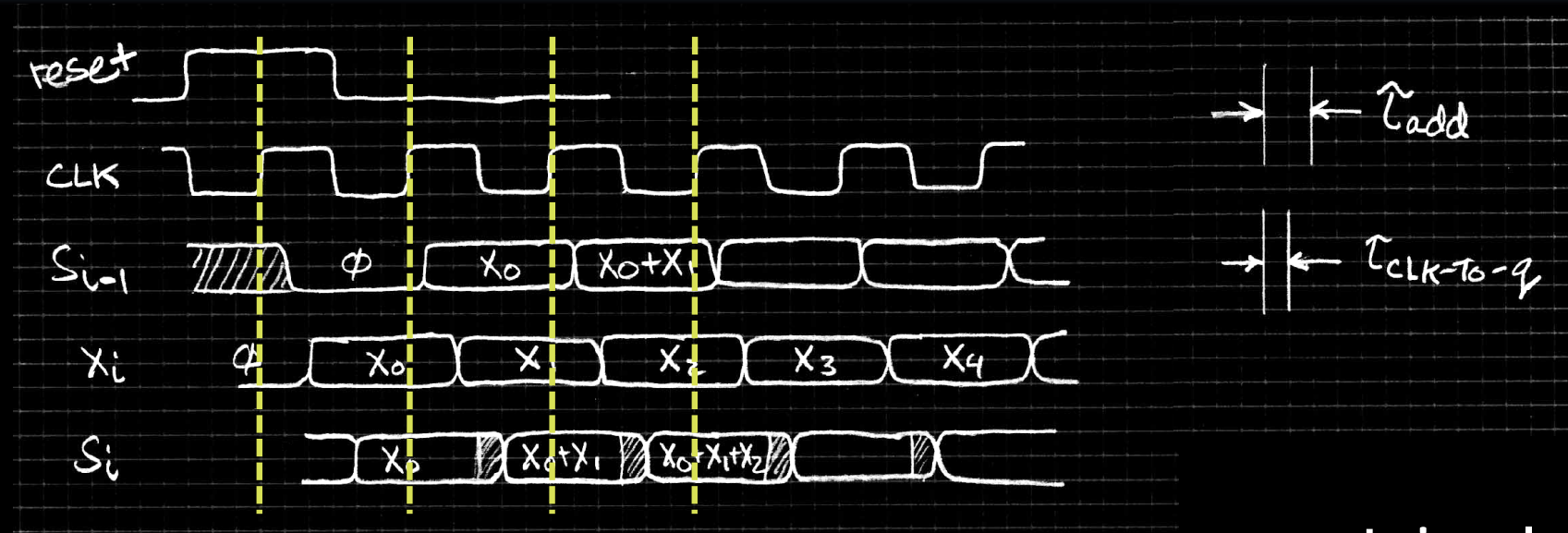
# Accumulator Revisited (proper timing 2/2)




- reset signal shown.
- Also, in practice  $X$  might not arrive to the adder at the same time as  $S_{i-1}$
- $S_i$  temporarily is wrong, but register always captures correct value.
- In good circuits, instability never happens around rising edge of  $clk$ .



# Pipelining for Performance
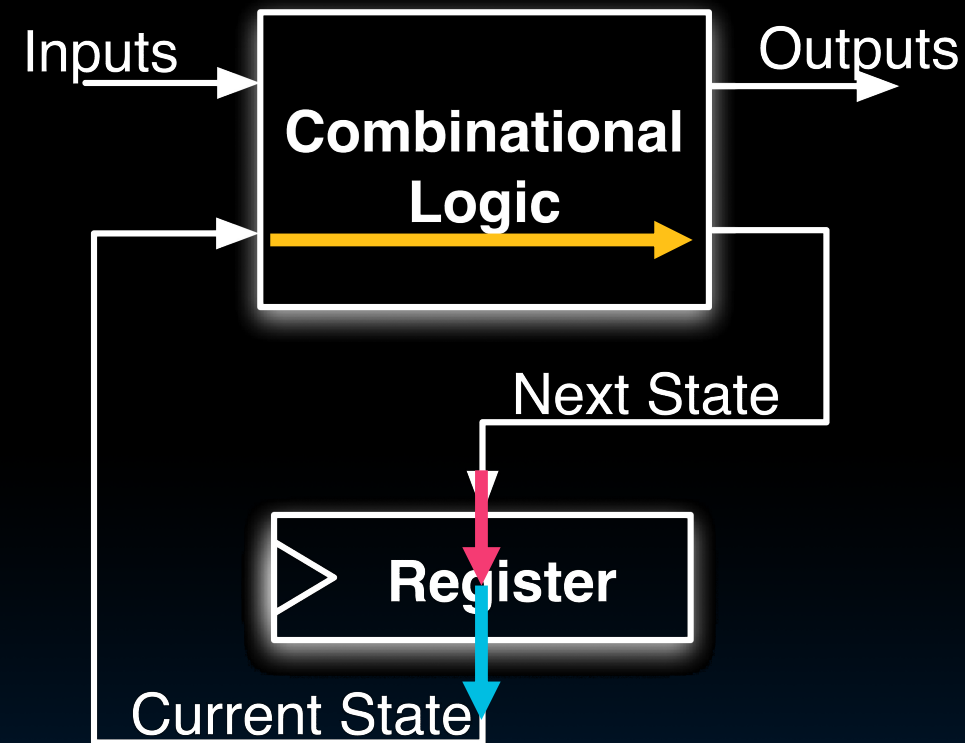
# Maximum Clock Frequency

- What is the maximum clock frequency of this circuit? (Hint: Frequency = 1 / Period)





$$\text{Max Delay} = \text{CLK-to-Q Delay} + \text{CL Delay} + \text{Setup Time}$$

# Pipelining to improve performance (1/2)

- **Extra Registers** are often added to help speed up the clock rate.

Timing...

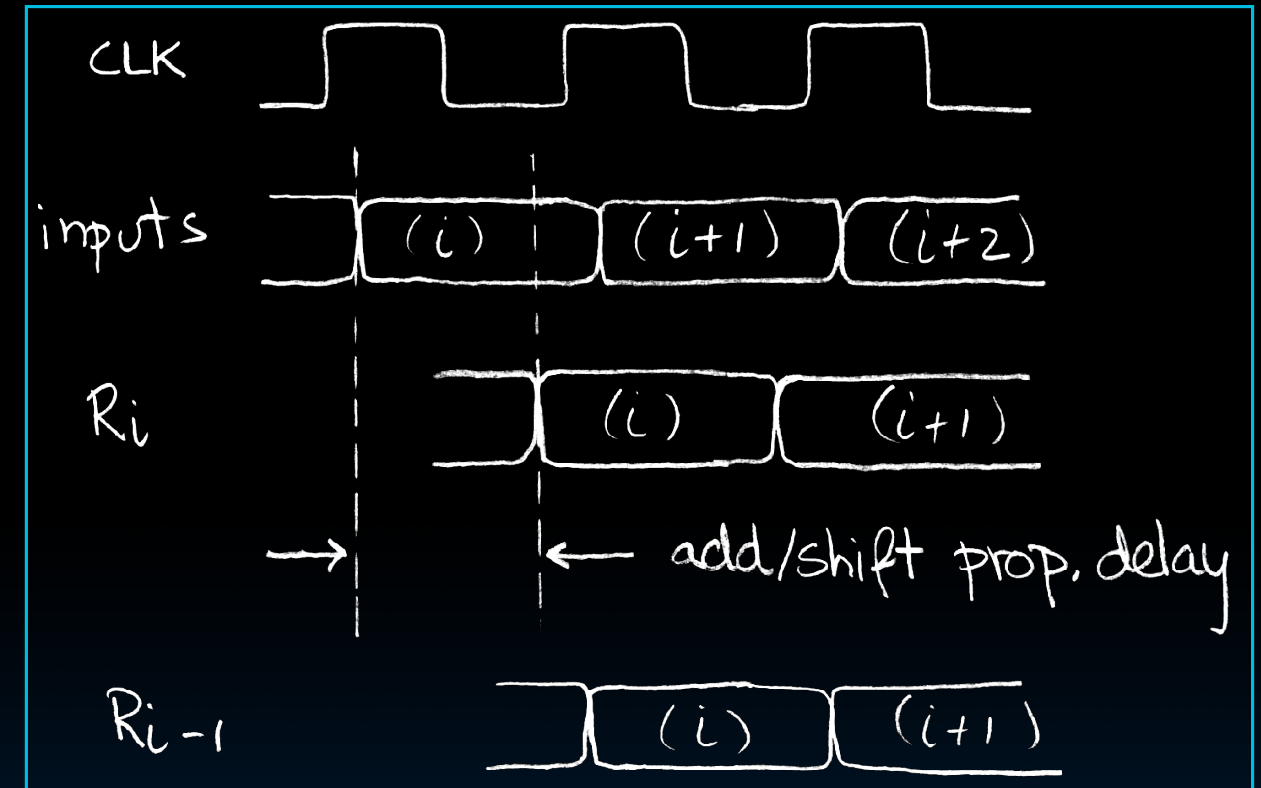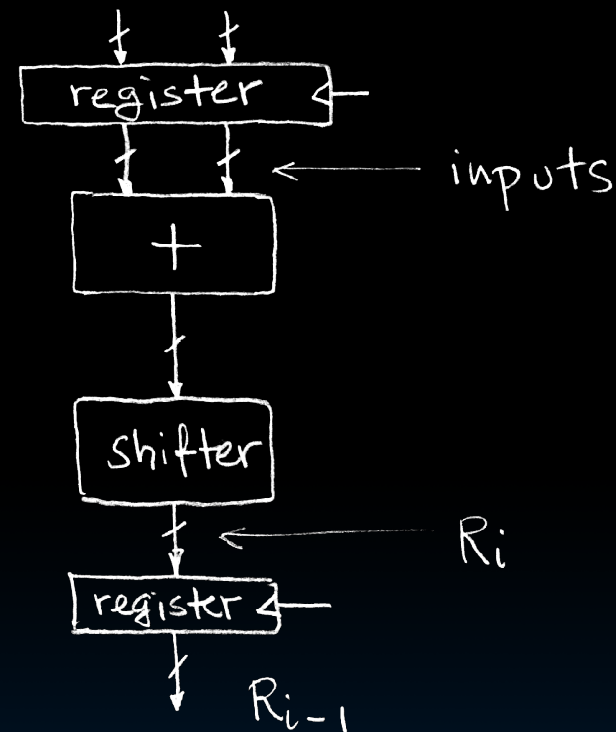



- **Note: Delay of 1 clock cycle from input to output.**
- **Clock period limited by propagation delay of adder/shifter.**




# Pipelining to improve performance (2/2)

- Insertion of register allows higher clock frequency.
- More outputs per second.

## Timing...

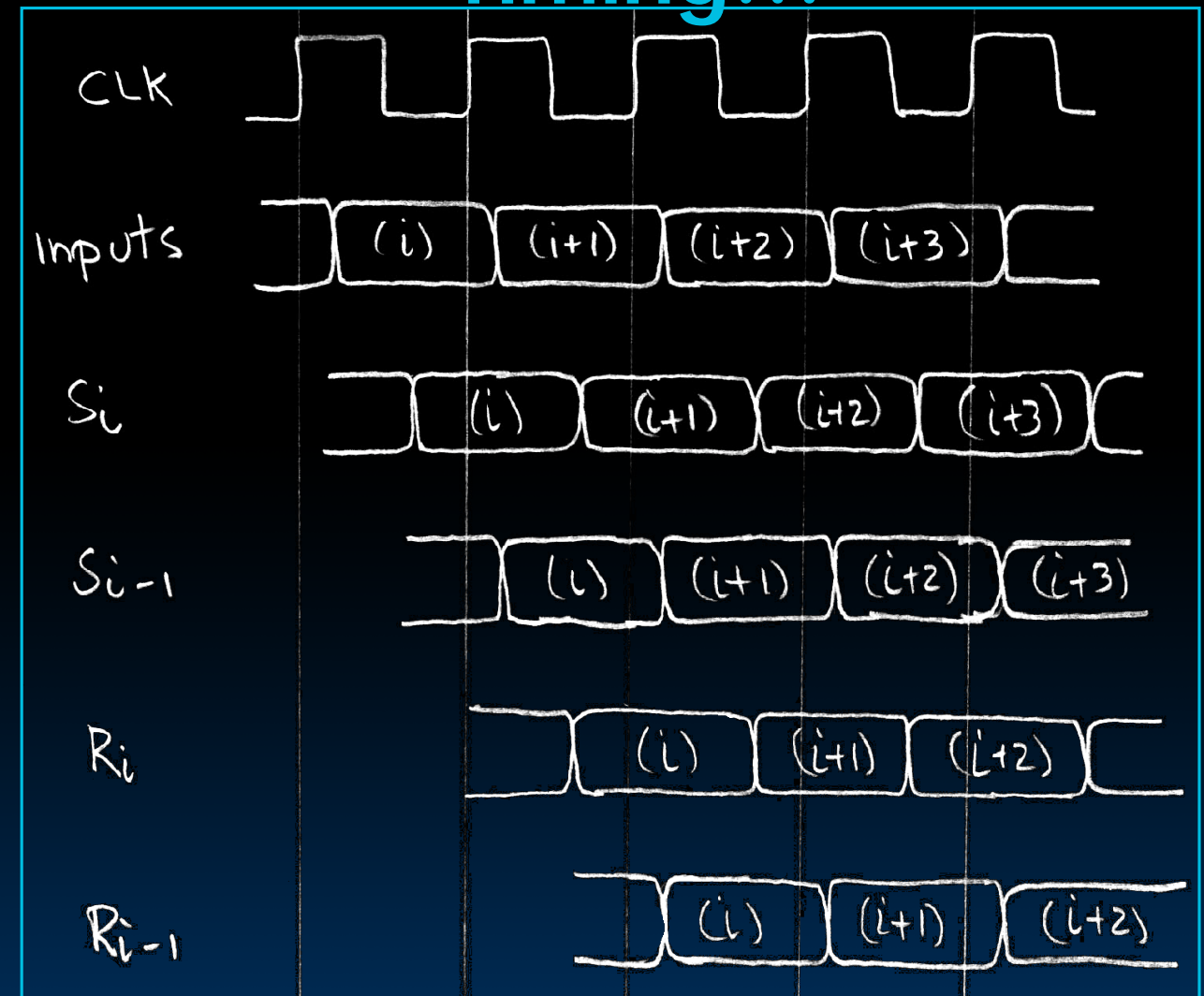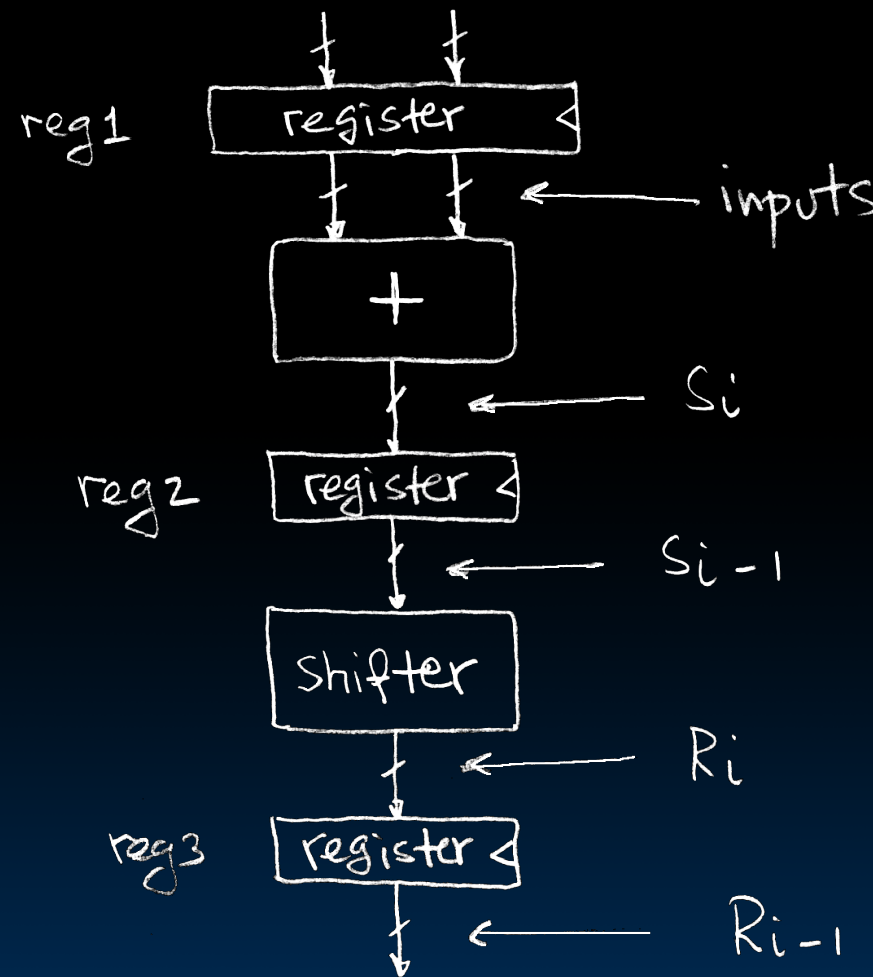

 

# Recap of Timing Terms

---


- **Clock (CLK)** - steady square wave that synchronizes system
- **Setup Time** - when the input must be stable before the rising edge of the CLK
- **Hold Time** - when the input must be stable after the rising edge of the CLK
- **"CLK-to-Q"** Delay - how long it takes the output to change, measured from the rising edge of the CLK
- **Flip-flop** - one bit of state that samples every rising edge of the CLK (positive edge-triggered)
- **Register** - several bits of state that samples on rising edge of CLK or on LOAD (positive edge-triggered)



# Finite State Machines

 
# Finite State Machines (FSM) Introduction

- You have seen FSMs in other classes
  - Same basic idea
- The function can be represented with a **"state transition diagram"**
- With combinational logic and registers, any FSM can be implemented in hardware.



 
# Finite State Machine Example: 3 ones...

- FSM to detect the occurrence of 3 consecutive 1's in the input.




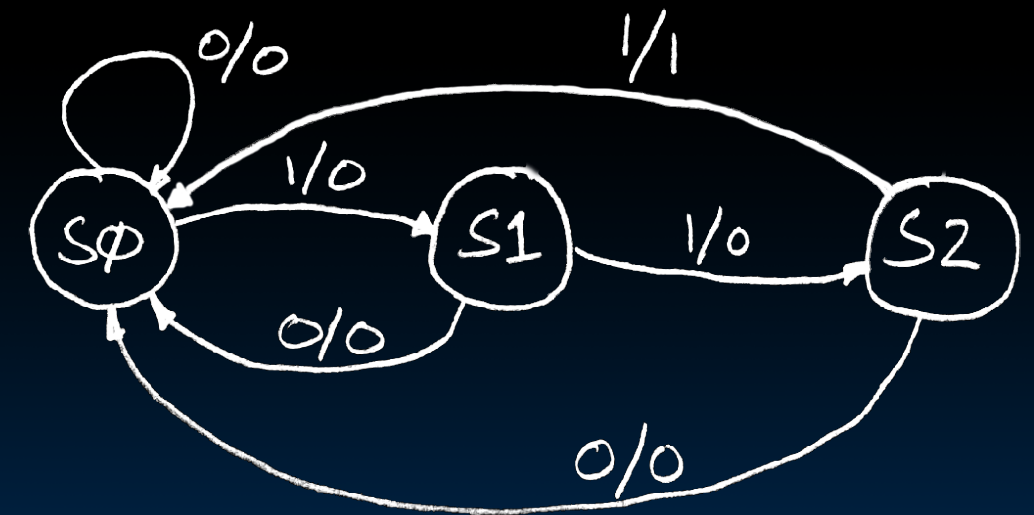- Draw the FSM...
  - Assume state transitions are controlled by the clock: on each clock cycle the machine checks the inputs and moves to a new state and produces a new output...



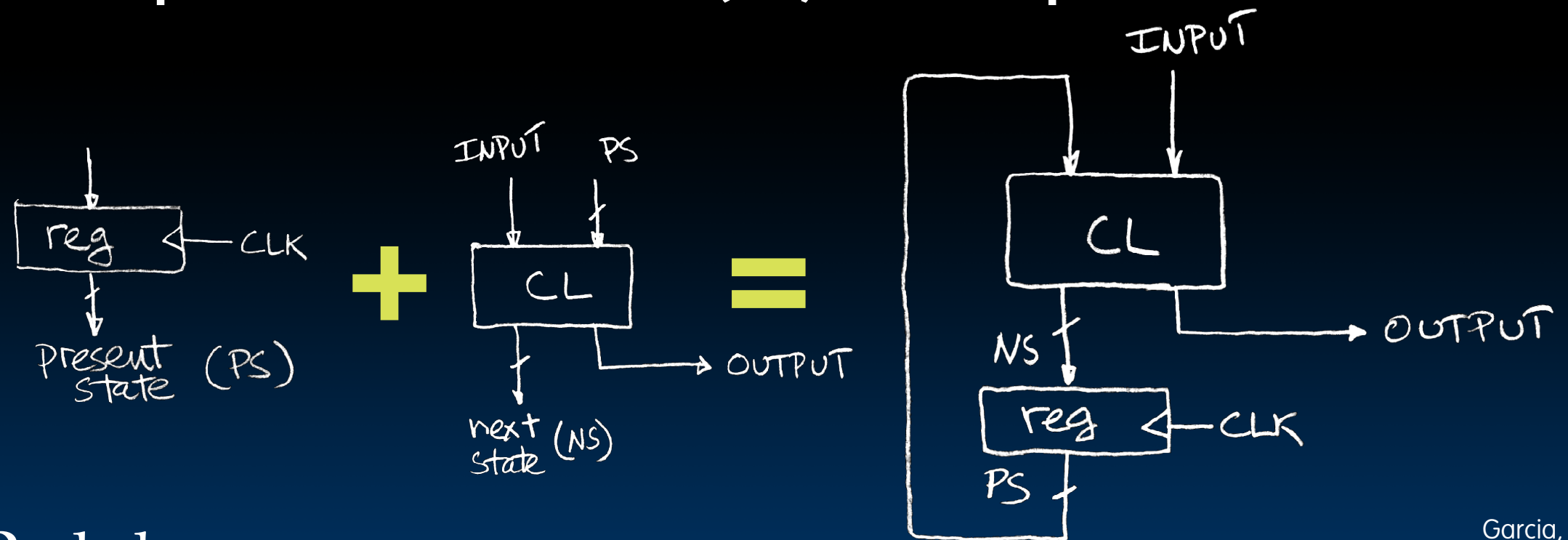
# Hardware Implementation of FSM

- ... Therefore a register is needed to hold the representation of which state the machine is in.
  - Use a unique bit pattern for each state.
- Combinational logic circuit is used to implement a function mapping the input and present state (PS) input to the next state (NS) and output.



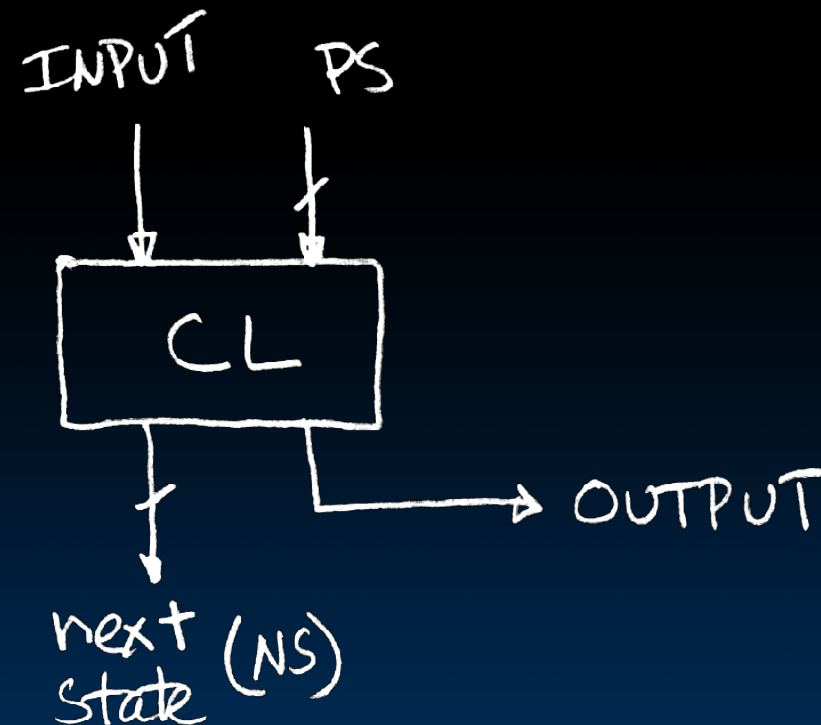
# Hardware for FSM: Combinational Logic

- Next lecture we will discuss the detailed implementation, but for now can look at its functional specification, truth table form.




PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

# General Model for Synchronous Systems

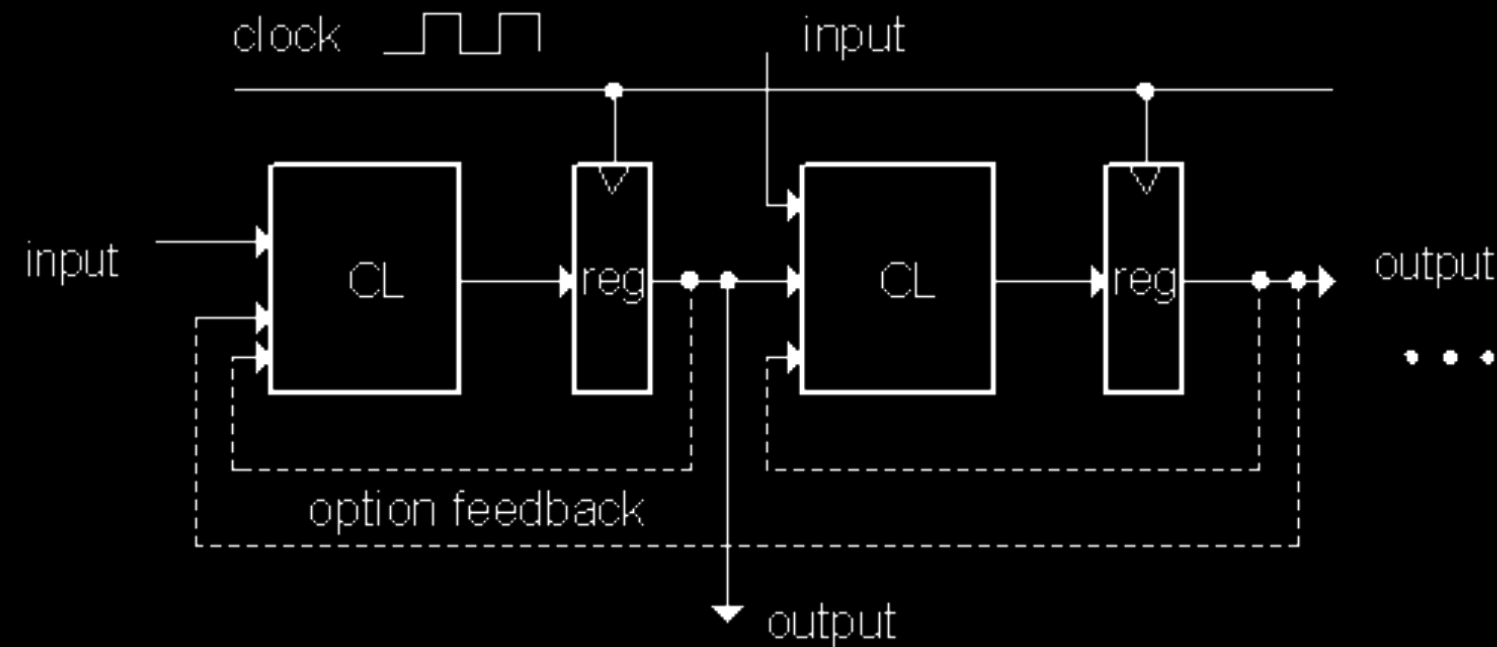


 
- Collection of CL blocks separated by registers.
- Registers may be back-to-back and CL blocks may be back-to-back.
- Feedback is optional.
- Clock signal(s) connects only to clock input of registers.





# Design Hierarchy

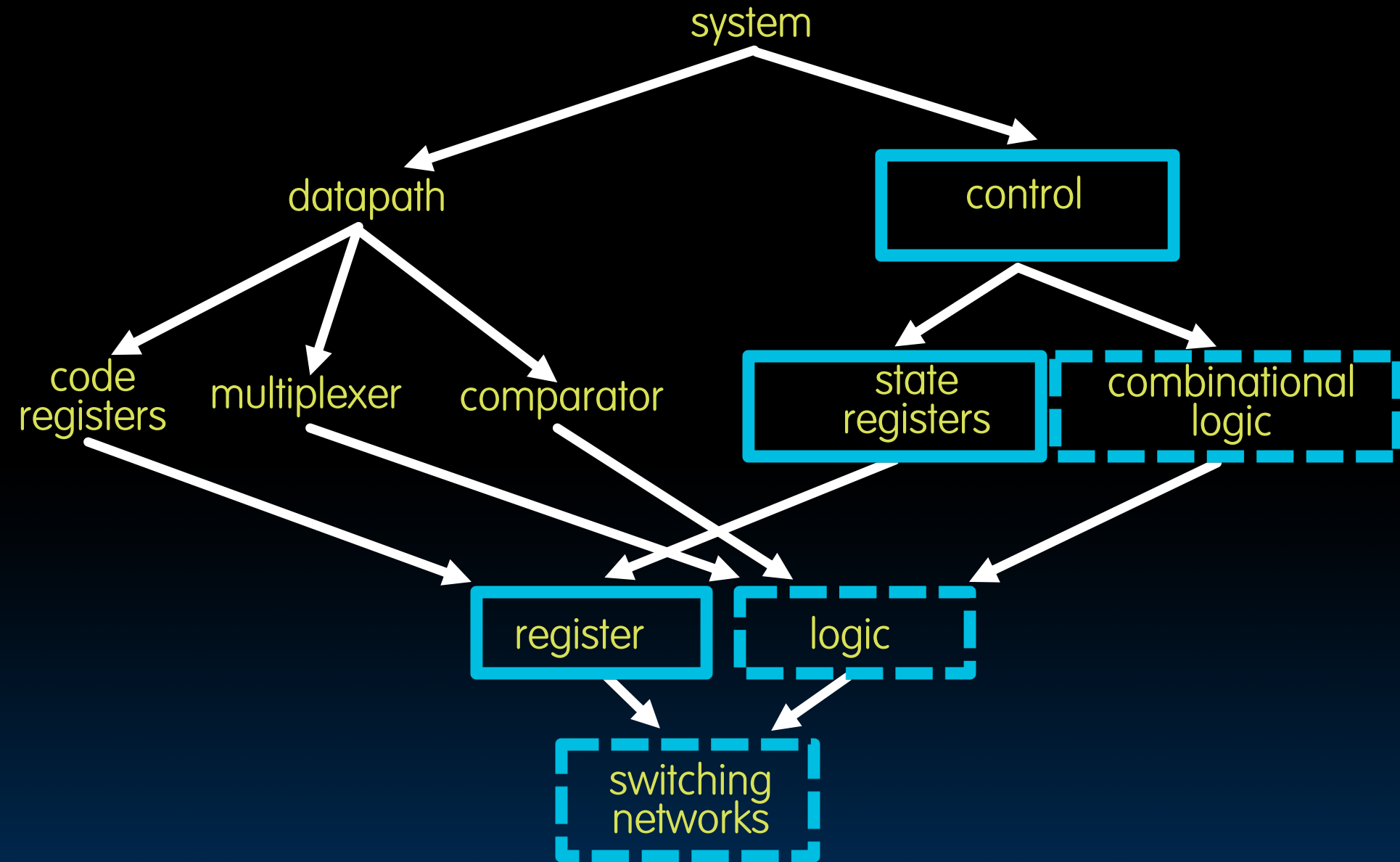

 

# “And In conclusion...”

---

- **State elements are used to:**
  - Build memories
  - Control the flow of information between other state elements and combinational logic
- **D-flip-flops used to build registers**
- **Clocks tell us when D-flip-flops change**
  - setup and hold times are important
- **We pipeline long-delay CL for faster clock**
- **Finite state machines extremely useful**
  - You’ll see them again 151A, 152, 164, 172, ...

