

UC Berkeley
Teaching Professor
Dan Garcia

CS61C

Great Ideas
in
Computer Architecture
(a.k.a. Machine Structures)




UC Berkeley
Professor
Bora Nikolić


Combinational Logic Blocks

Data Multiplexors

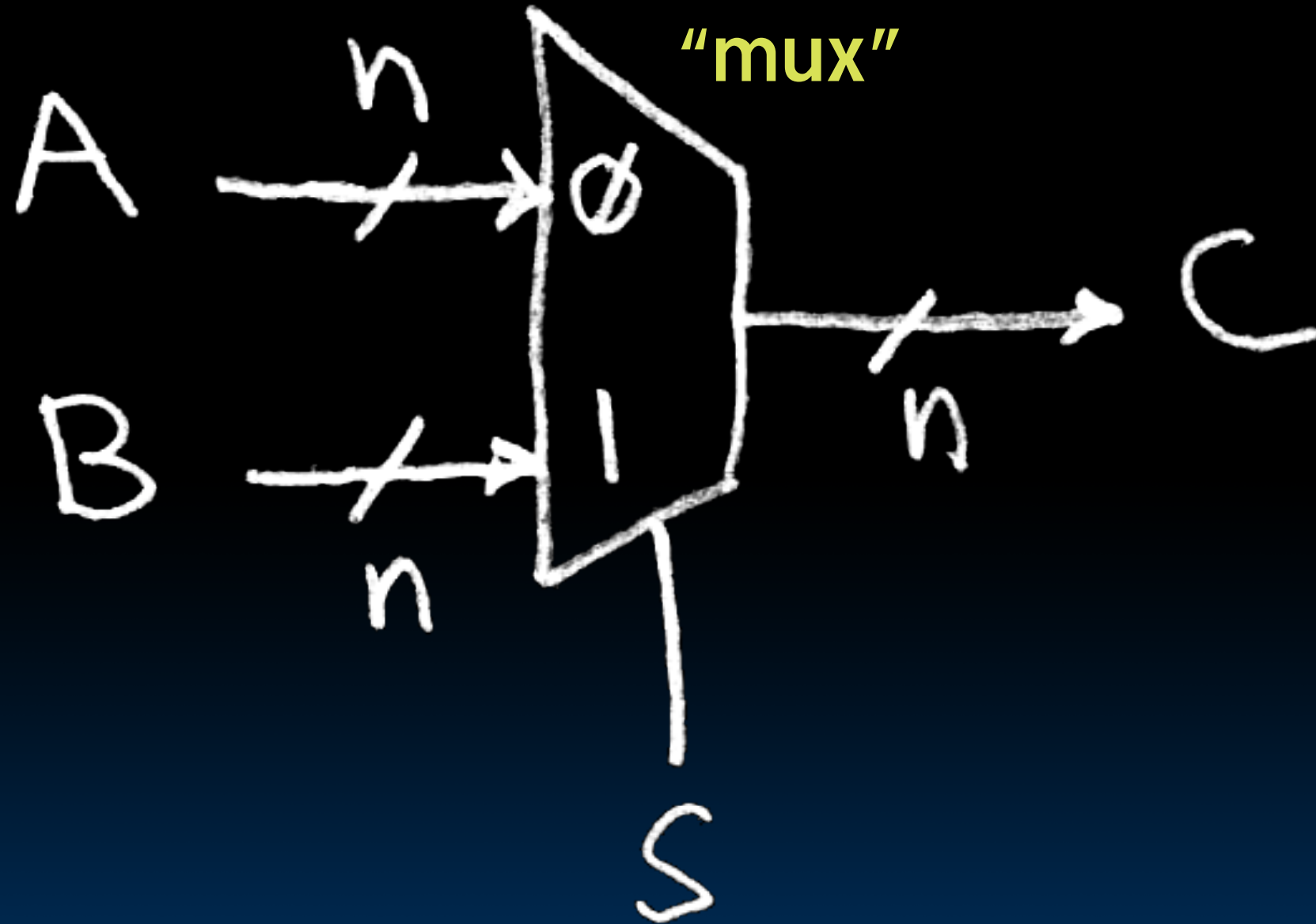Data Multiplexor (here 2-to-1, n-bit-wide)



N instances of 1-bit-wide mux

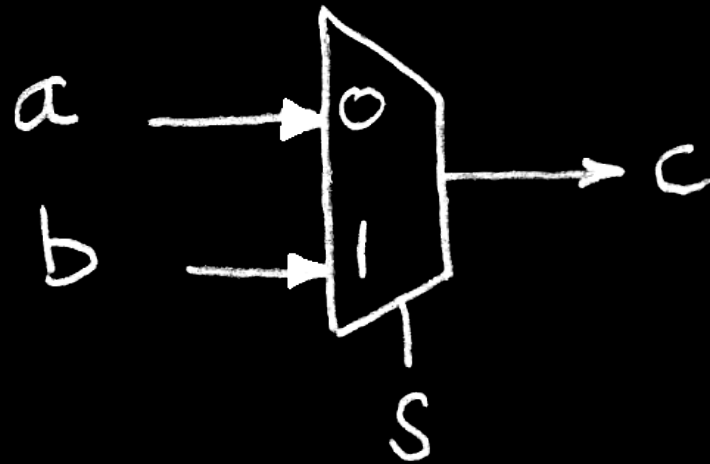

How many rows in TT?


$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$

| s | ab | c |
|---|----|---|
| 0 | 00 | 0 |
| 0 | 01 | 0 |
| 0 | 10 | 1 |
| 0 | 11 | 1 |
| 1 | 00 | 0 |
| 1 | 01 | 1 |
| 1 | 10 | 0 |
| 1 | 11 | 1 |

| s | c |
|---|---|
| 0 | a |
| 1 | b |

How do we build a 1-bit-wide mux?

$$\bar{s}a + sb$$

 

4-to-1 Multiplexor?


- How many rows in the Truth Table?

when $S=00$, $e=a$

when $S=01$, $e=b$

when $S=10$, $e=c$

when $S=11$, $e=d$

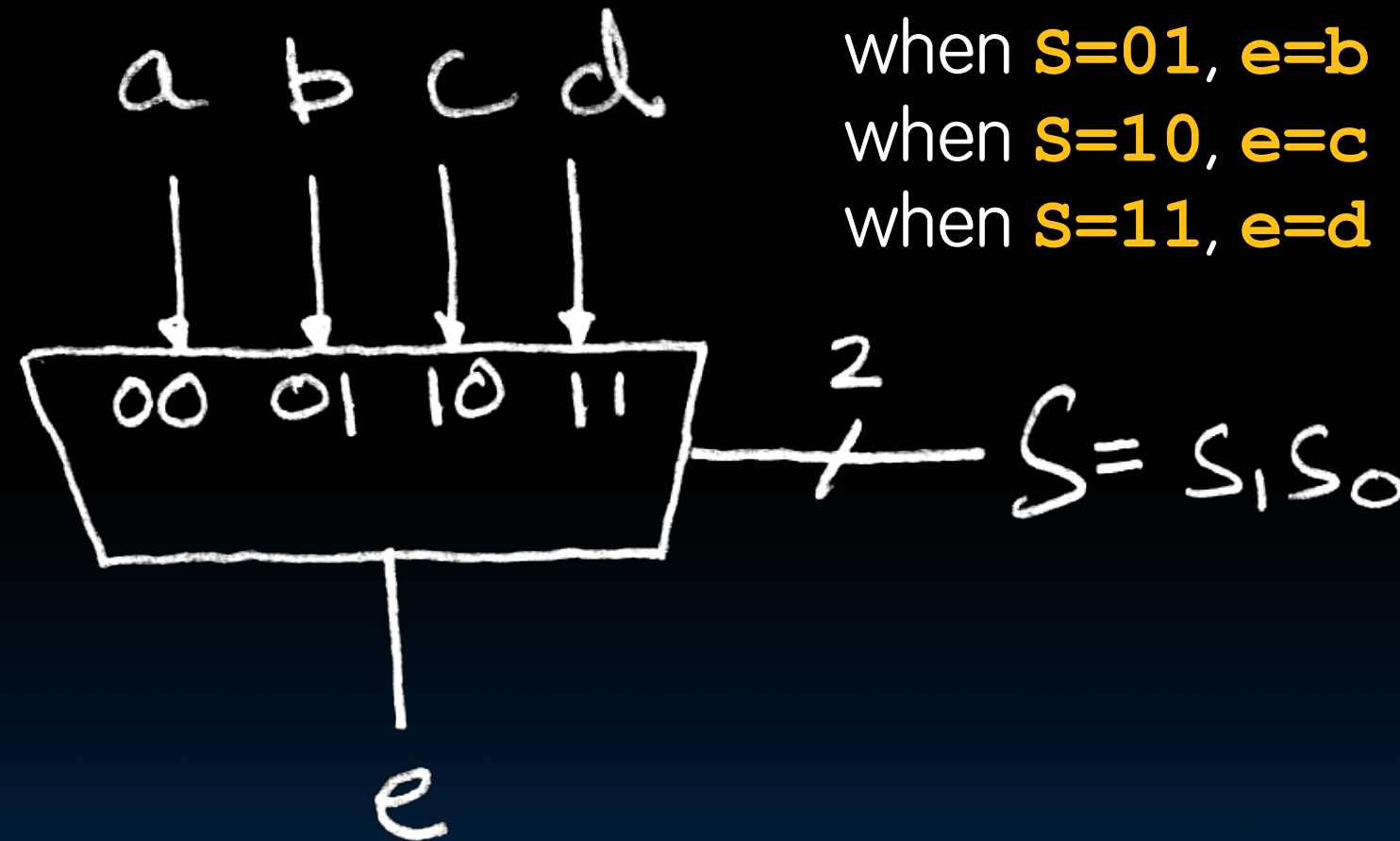


| $s_1 s_0$ | c |
|-----------|-----|
| 0 0 | a |
| 0 1 | b |
| 1 0 | c |
| 1 1 | d |

$$e = \overline{s_1} \cdot \overline{s_0} a + \overline{s_1} s_0 b + s_1 \overline{s_0} c + s_1 s_0 d$$

Mux: is there any other way to do it?

Hint: NCAA tourney!

 


Ans: Hierarchically!



Arithmetic Logic Unit (ALU)


Arithmetic and Logic Unit

- Most processors contain a special logic block called "Arithmetic and Logic Unit" (ALU)
- We'll show you an easy one that does ADD, SUB, bitwise AND (&), bitwise OR (|)

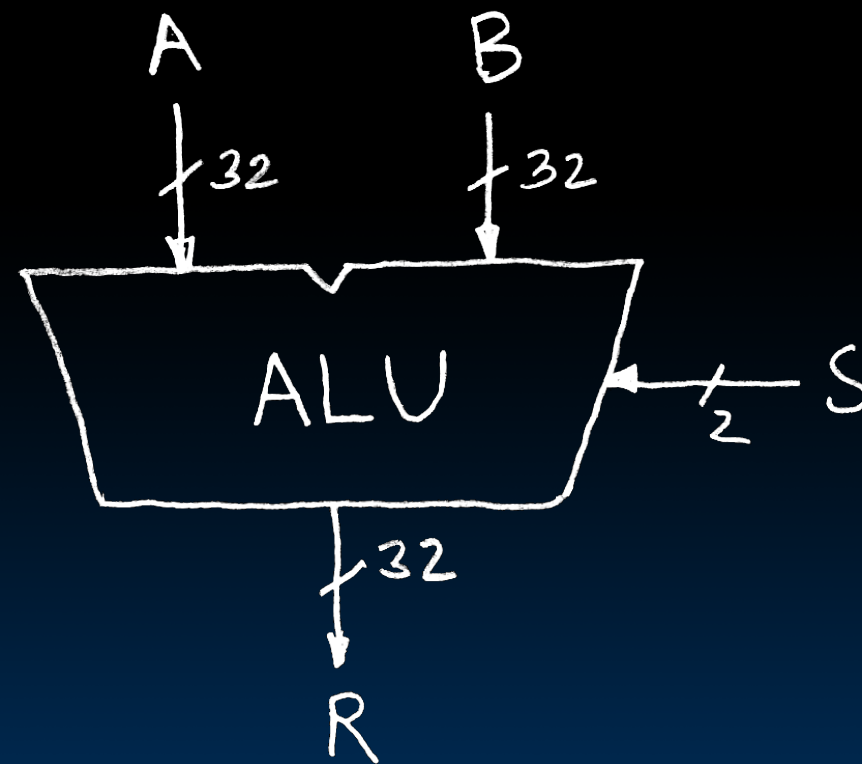


when $S=00$, $R=A+B$
 when $S=01$, $R=A-B$
 when $S=10$, $R=A \& B$
 when $S=11$, $R=A | B$

Our simple ALU

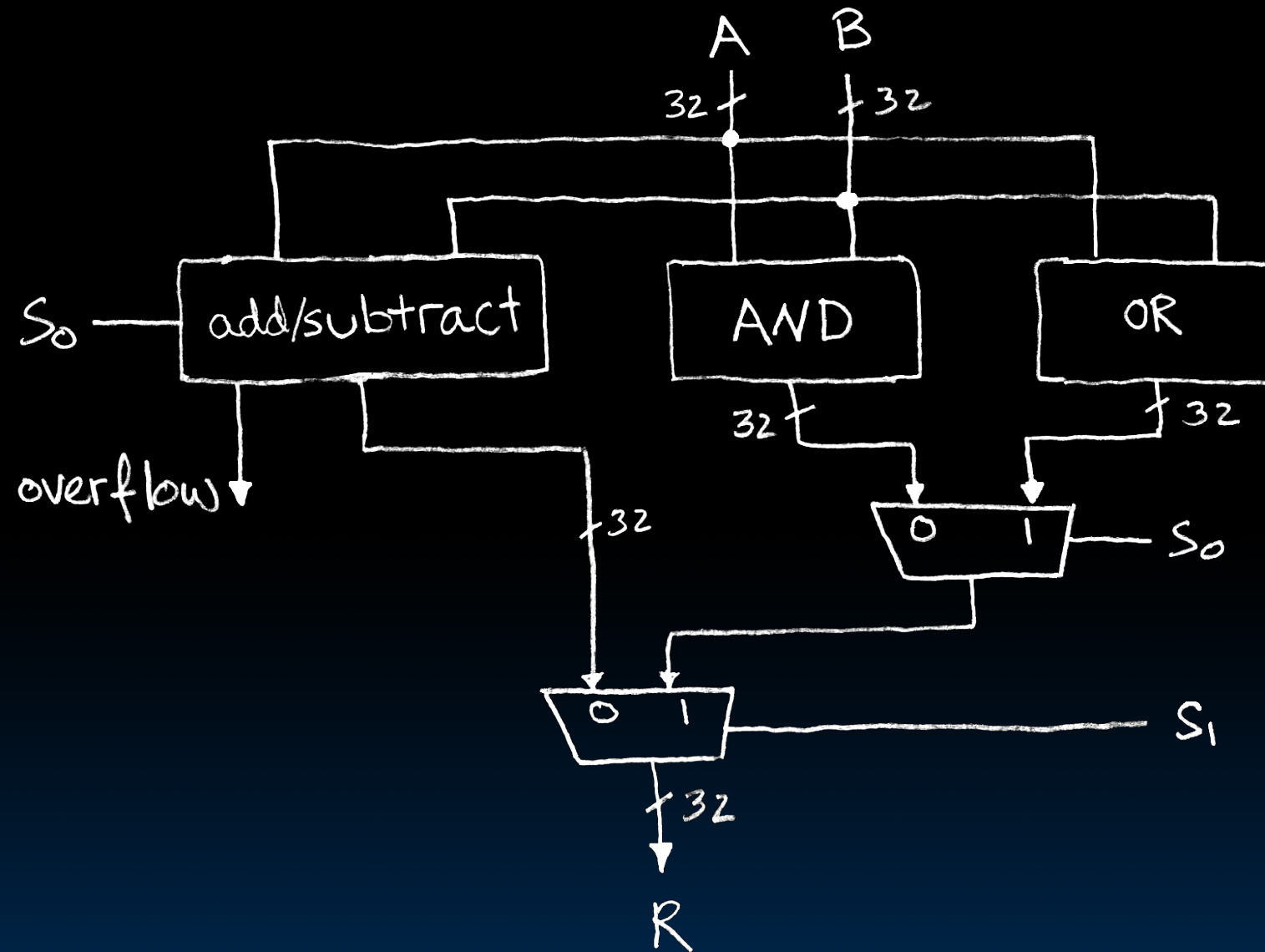


**Adder /
Subtractor**

 

Adder / Subtractor Design – how?

 - Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer




Adder / Subtractor – One-bit adder LSB...

| | | | | |
|-------|-------|-------|-------|-------|
| | a_3 | a_2 | a_1 | a_0 |
| + | b_3 | b_2 | b_1 | b_0 |
| <hr/> | | | | |
| | s_3 | s_2 | s_1 | s_0 |

| a_0 | b_0 | s_0 | c_1 |
|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

$$s_0 = a_0 \text{ XOR } b_0$$

$$c_1 = a_0 \text{ AND } b_0$$

 




Adder / Subtractor – One-bit adder (1/2)...

$$\begin{array}{rcccc}
 & a_3 & a_2 & a_1 & a_0 \\
 + & b_3 & b_2 & b_1 & b_0 \\
 \hline
 s_3 & s_2 & s_1 & s_0 &
 \end{array}$$

| a_i | b_i | c_i | s_i | c_{i+1} |
|-------|-------|-------|-------|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

$$\begin{aligned}
 s_i &= \text{XOR}(a_i, b_i, c_i) \\
 c_{i+1} &= \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i
 \end{aligned}$$

  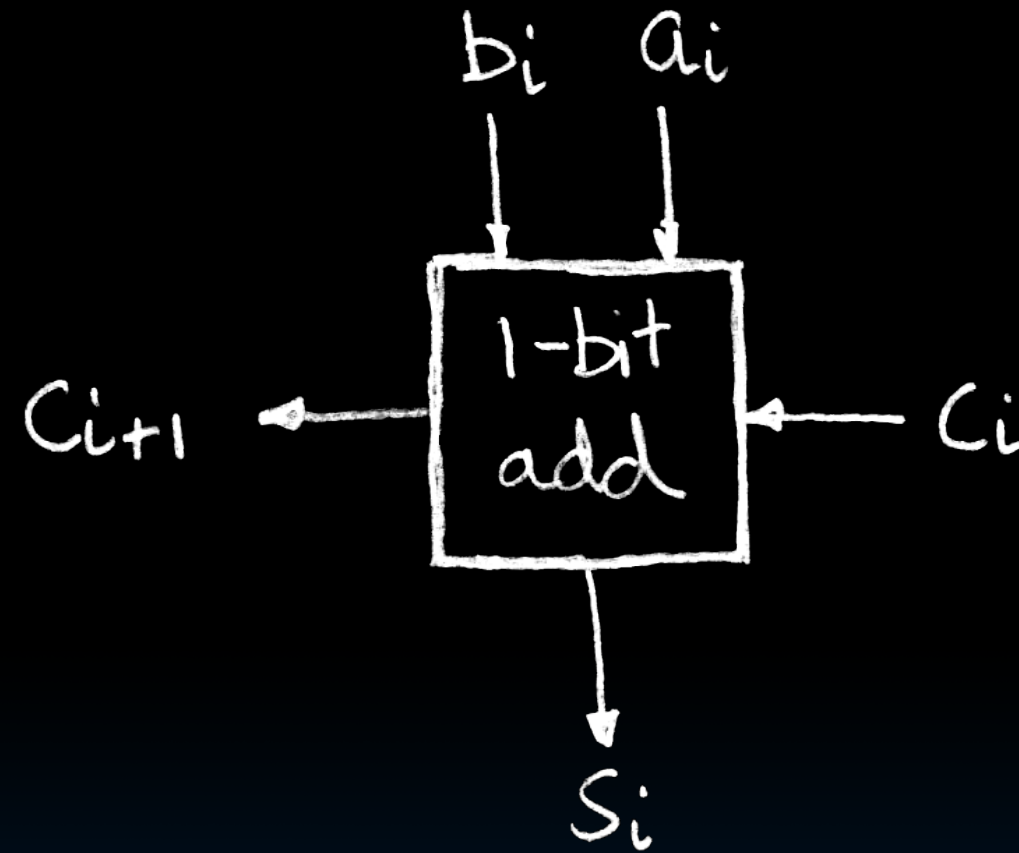
Adder / Subtractor – One-bit adder (2/2)...



$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

N 1-bit adders \rightarrow 1 N-bit adder

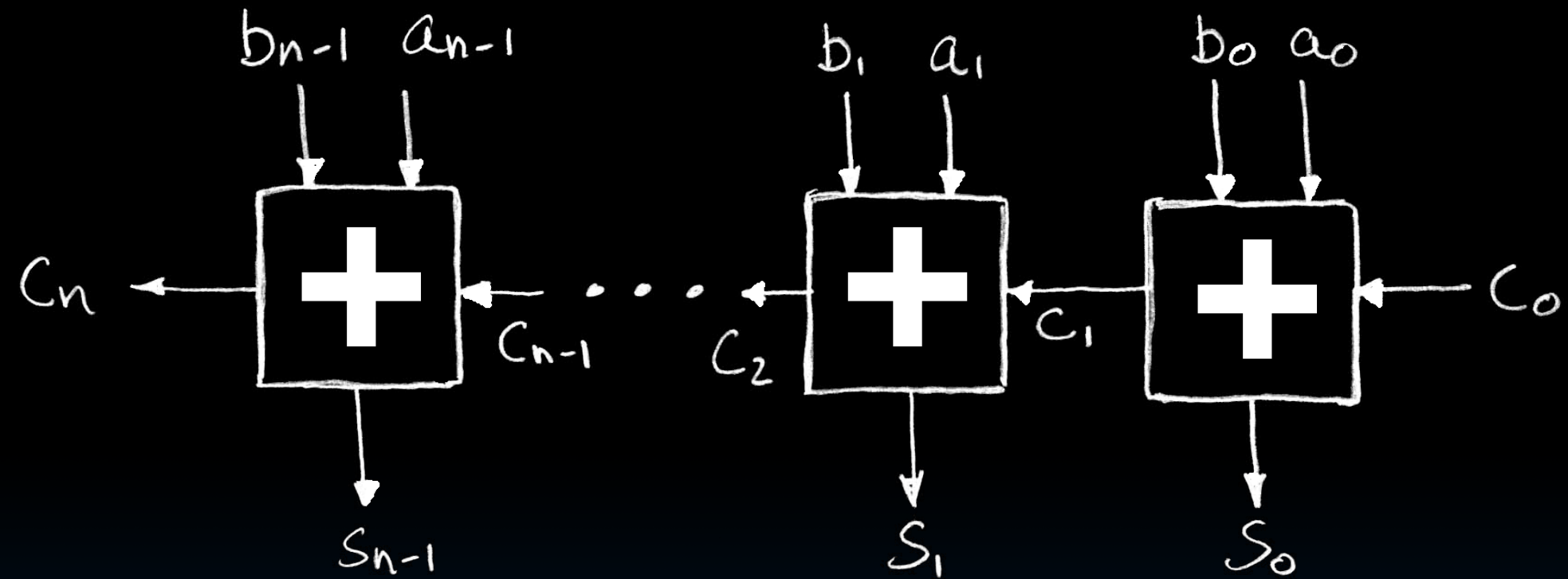

What about overflow?

Overflow = c_n ?

Sum of two 2-bit numbers...

11
"-1"

10
"-2"

01
"1"

00
"0"

+

c_1

$a_1 \ a_0$

+ $b_1 \ b_0$

$c_2 \ s_1 \ s_0$

$b_1 \ a_1$

$b_0 \ a_0$

c_2 c_1 c_0

s_1 s_0

11
+11

110

10
+10

100

10
+11

101

1
01
+01

10

1
01
+10

11

1
01
+11

100

00
+00

00

00
+01

01

00
+10

10

00
+11

11

00
"0"

01
"1"

10
"-2"

11
"-1"

- Let's add
 - First unsigned
 - Then signed (Two's Complement)
 - When do the lowest 2 bits of sum not represent correct sum?
 - Is there a pattern of when this happens?
Hint: Check out the carry-bit and the sum-4s-column-bit
- Highest adder
 - C_{in} = Carry-in = c_1 , C_{out} = Carry-out = c_2
 - No C_{out} or C_{in} → NO overflow!
 - C_{in} and C_{out} → NO overflow!
 - C_{in} , but no C_{out} → A,B both > 0, **overflow!**
 - C_{out} , but no C_{in} → A or B are -2, **overflow!**


What operation is this?


overflow = $c_n \text{ XOR } c_{n-1}$



Subtractor Design

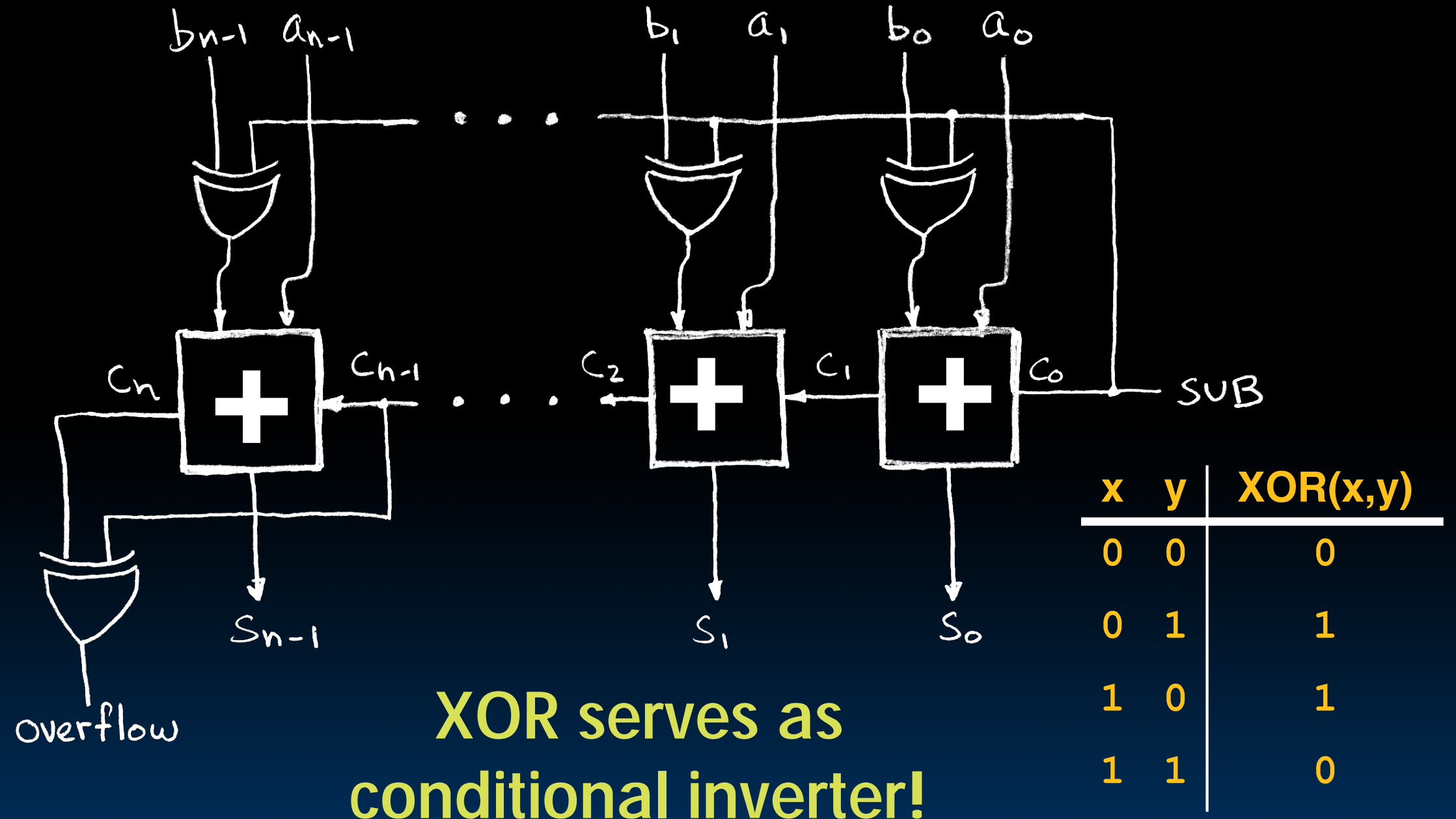Extremely Clever Subtractor: $A - B = A + (-B)$



 

“And In conclusion...”

- **Use muxes to select among input**
 - S input bits selects 2^S inputs
 - Each input can be n -bits wide, indep of S
- **Can implement muxes hierarchically**
- **ALU can be implemented using a mux**
 - Coupled with basic block elements
- **N -bit adder-subtractor done using N 1-bit adders with XOR gates on input**
 - XOR serves as conditional inverter

