

inst.eecs.berkeley.edu/~cs61c

CS61C : Machine Structures

Lecture #20

Introduction to Synchronous Digital Systems




2008-3-12

Scott Beamer, Guest Lecturer


Wifi in Air Coast to Coast



Review

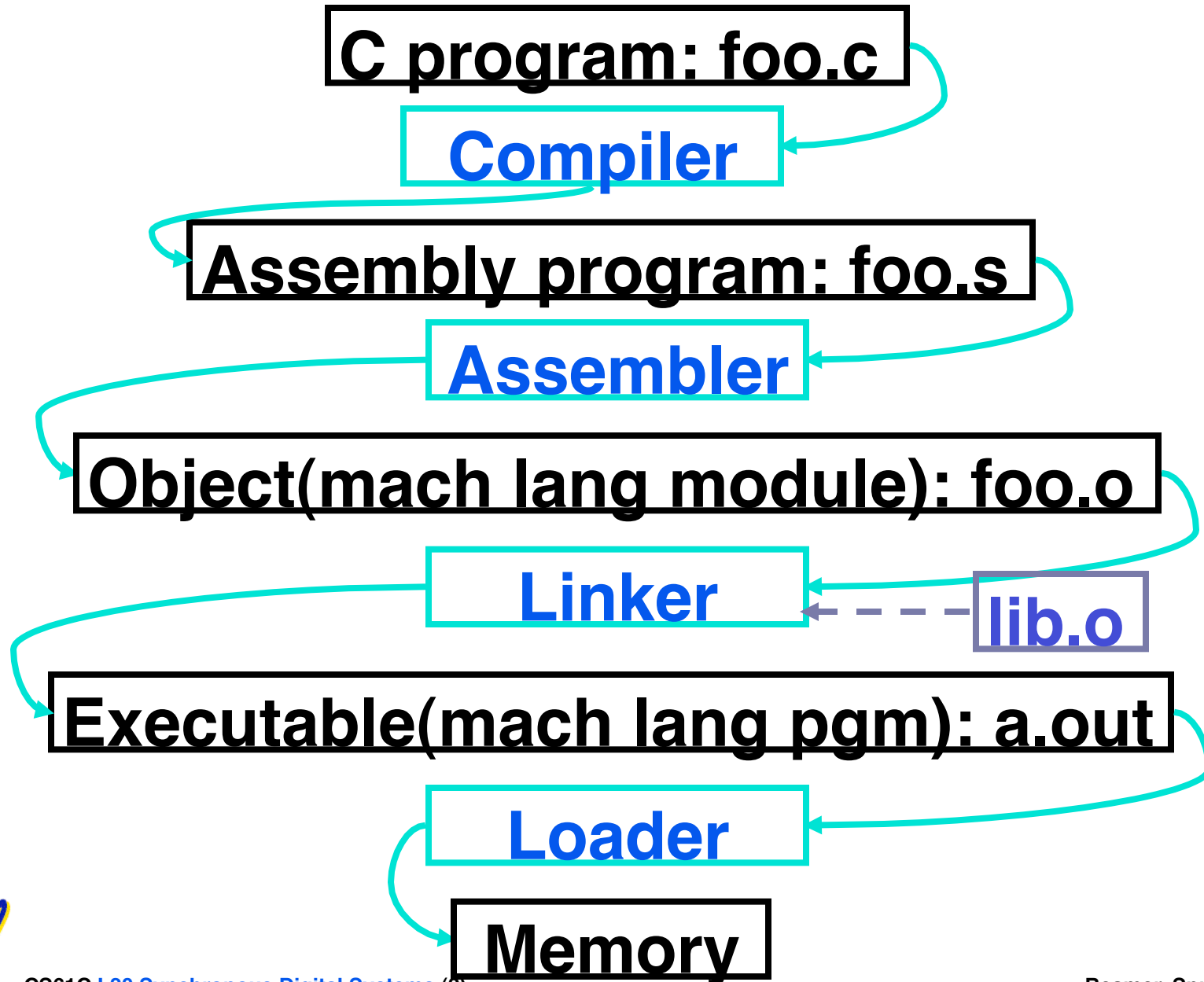

What are “Machine Structures”?

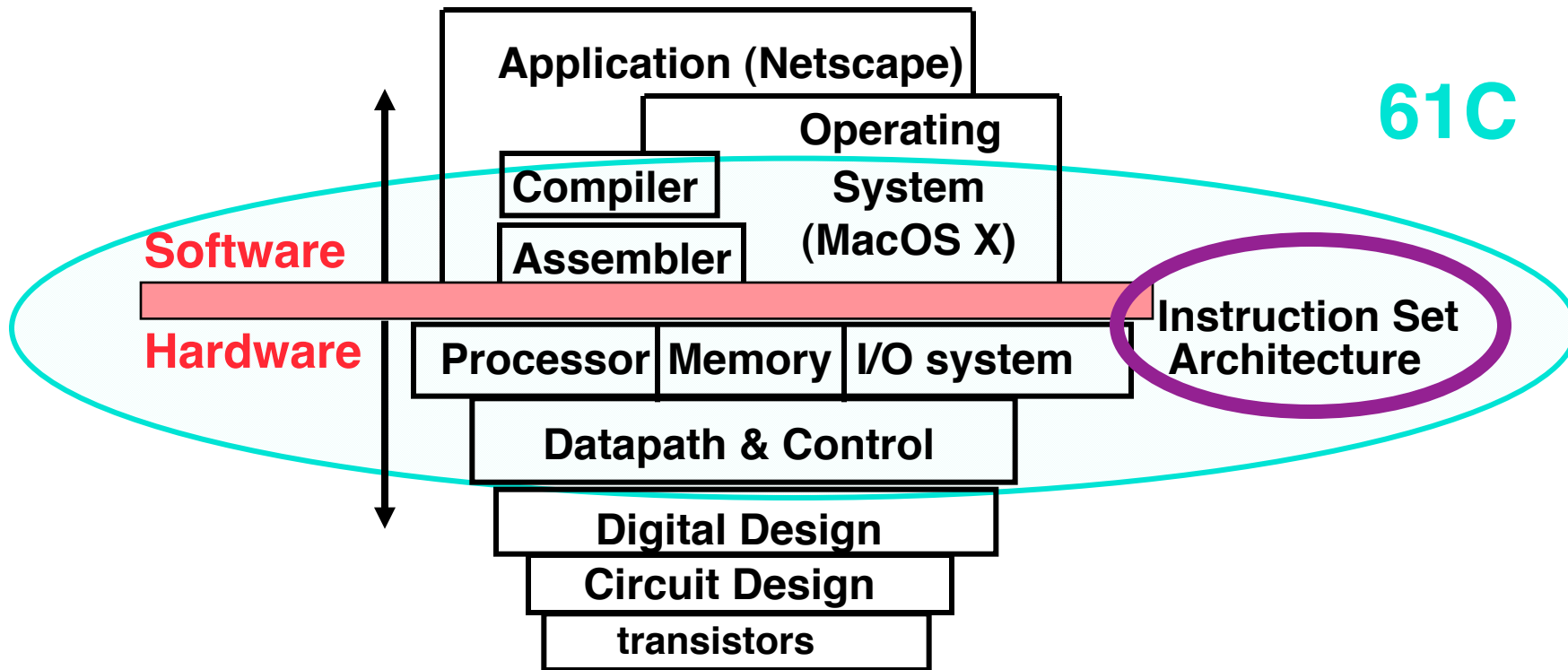

Coordination of many *levels of abstraction*


ISA is an important abstraction level:
contract between HW & SW



Below the Program


- High-level language program (in C)
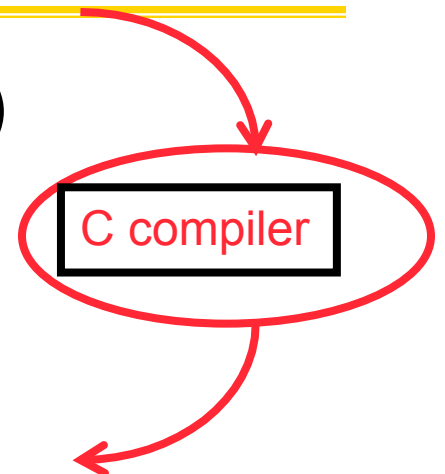
```
swap  int v[], int k){
      int temp;
      temp = v[k];
      v[k] = v[k+1];
      v[k+1] = temp;
}
```



- Assembly language program (for MIPS)
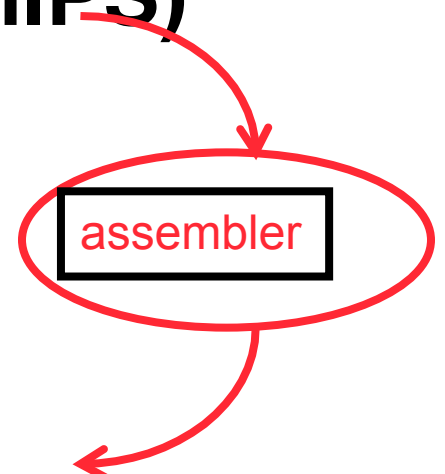
```
swap: sll    $2, $5, 2
      add    $2, $4, $2
      lw     $15, 0($2)
      lw     $16, 4($2)
      sw     $16, 0($2)
      sw     $15, 4($2)
      jr     $31
```



- Machine (object) code (for MIPS)



```
000000 00000 00101 0001000010000000
000000 00100 00010 0001000000100000 . . .
```

Synchronous Digital Systems

The hardware of a processor, such as the MIPS, is an example of a Synchronous Digital System

Synchronous:

- Means all operations are coordinated by a central **clock**.
 - It keeps the “heartbeat” of the system!

Digital:

- Mean all values are represented by discrete values
- Electrical signals are treated as 1's and 0's and grouped together to form words.



Logic Design


- **Next 4 weeks: we'll study how a modern processor is built; starting with basic elements as building blocks.**
- **Why study hardware design?**
 - **Understand capabilities and limitations of hardware in general and processors in particular.**
 - **What processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)**
 - **Background for more detailed hardware courses (CS 150, CS 152)**
 - **There is just so much you can do with processors. At some point you may need to design your own custom hardware.**



PowerPC Die Photograph



Let's look closer...

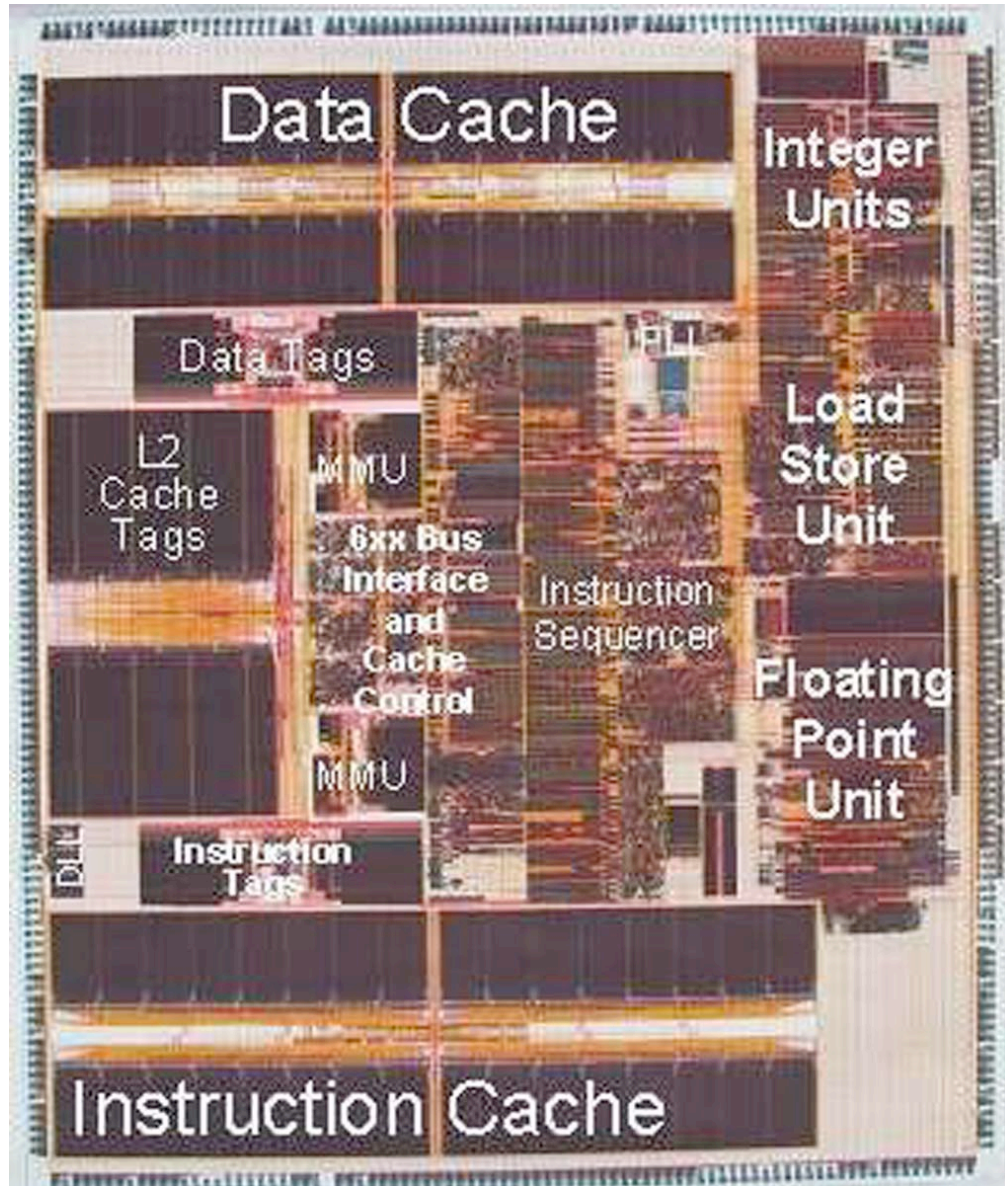


Transistors 101

- **MOSFET**

- Metal-Oxide-Semiconductor Field-Effect Transistor


- Come in two types:

- n-type NMOSFET
 - p-type PMOSFET

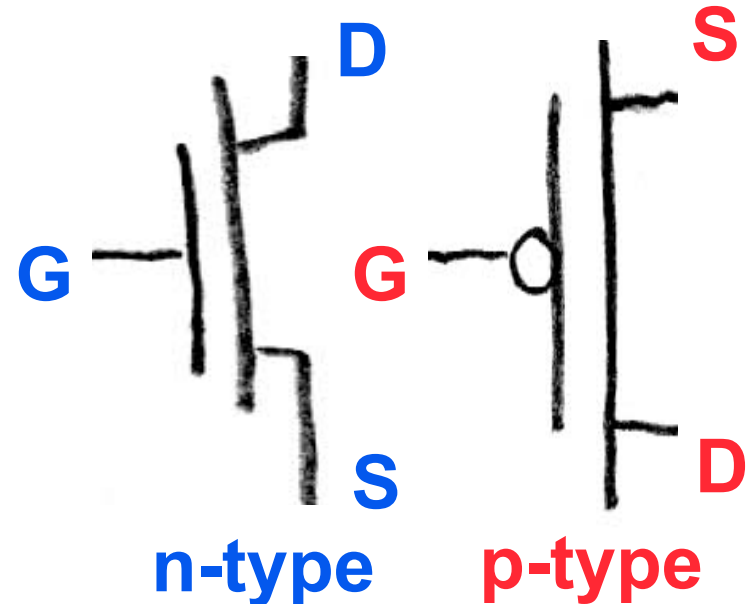

- For **n-type** (**p-type** opposite)

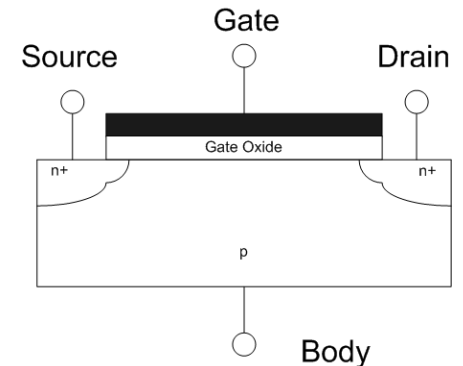- If voltage not enough between G & S, transistor turns “off” (cut-off) and Drain-Source NOT connected
 - If the G & S voltage is high enough, transistor turns “on” (saturation) and Drain-Source ARE connected




Side view



www.wikipedia.org/wiki/Mosfet


Transistor Circuit Rep. vs. Block diagram

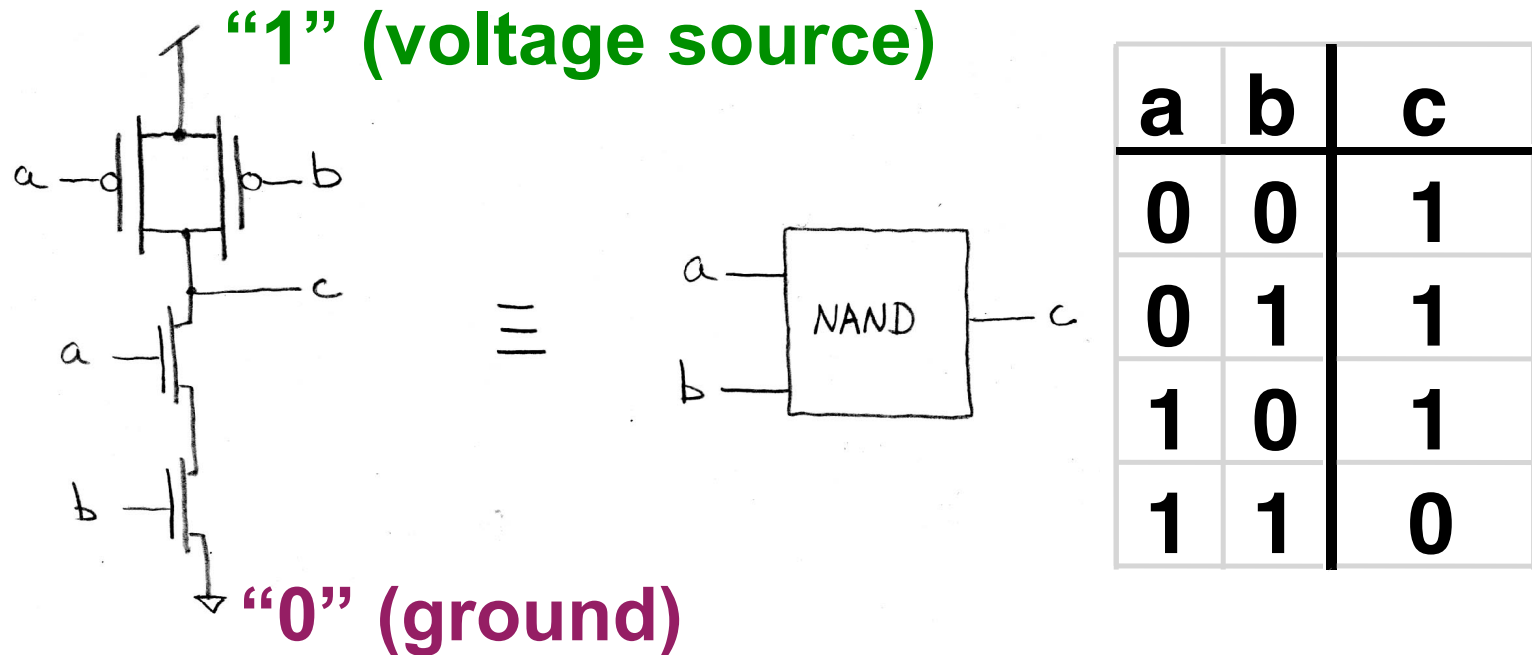- Chips is composed of nothing but transistors and wires.
- Small groups of transistors form useful building blocks.



- Block are organized in a hierarchy to build higher-level blocks: ex: adders.



Signals and Waveforms: Clocks

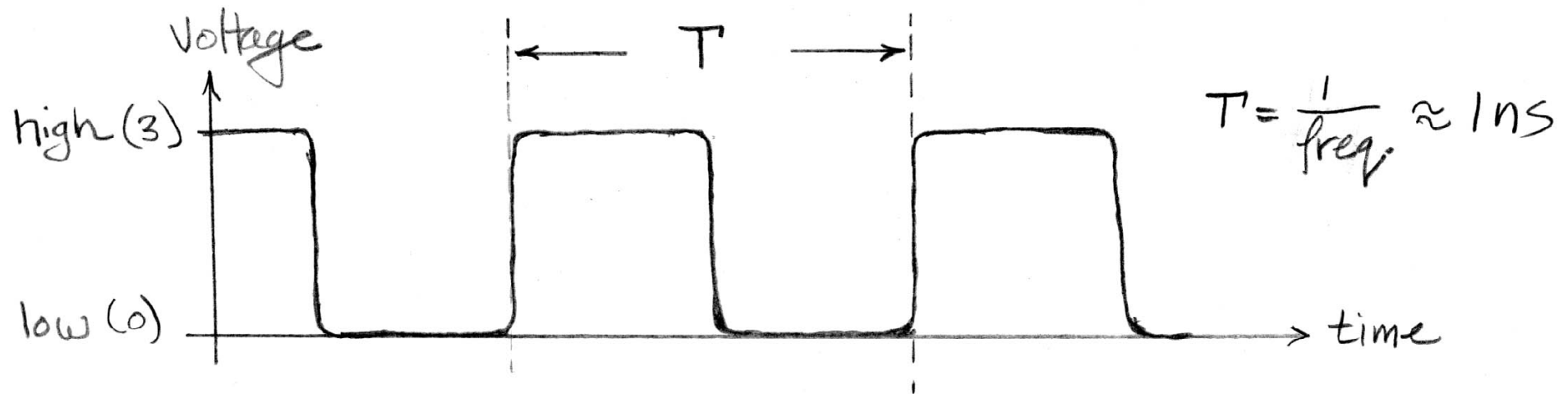

• Signals


- When **digital** is only treated as 1 or 0
- Is transmitted over wires continuously
- Transmission is effectively instant
 - Implies that any wire only contains 1 value at a time

Signals and Waveforms

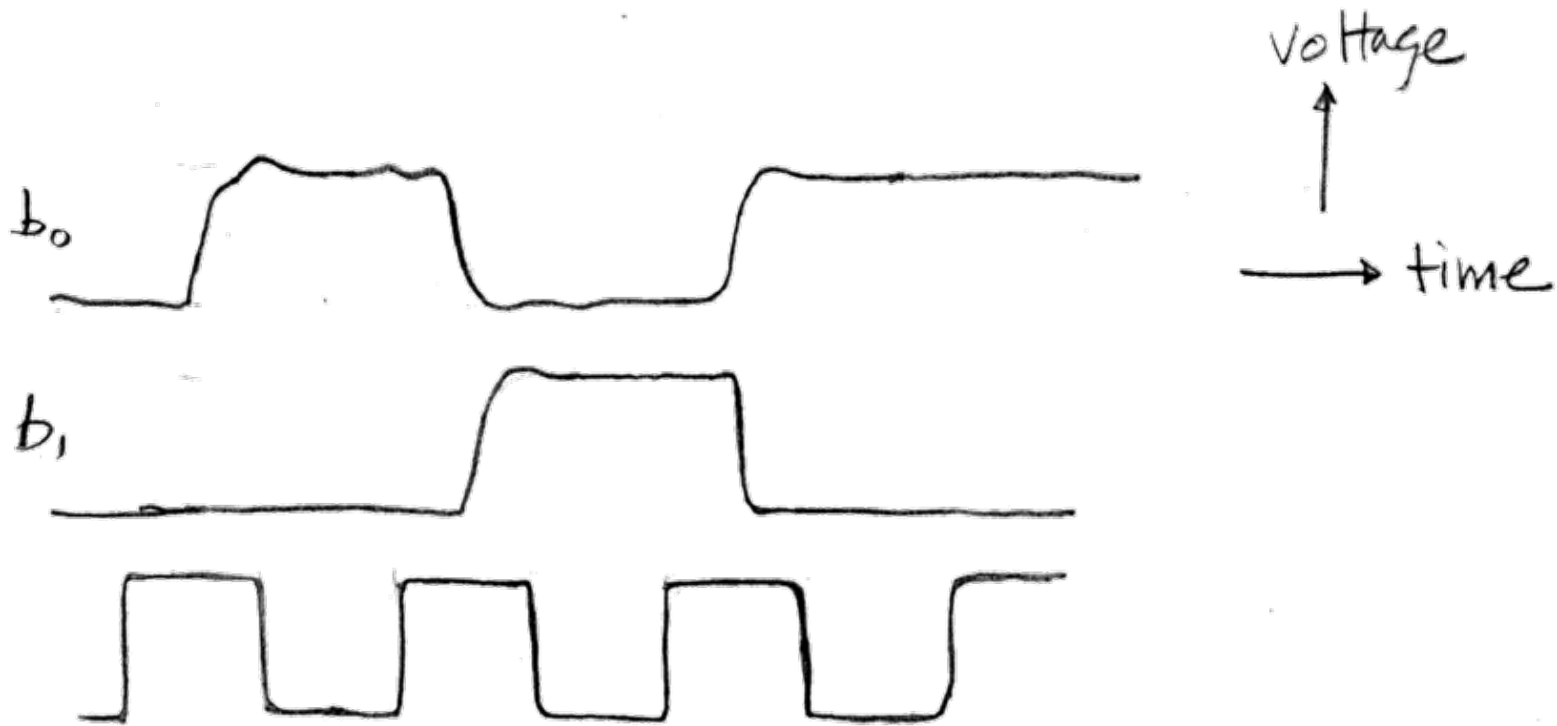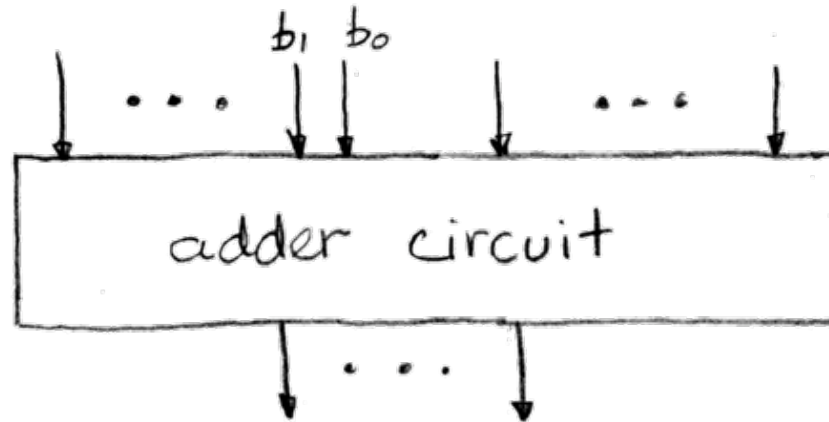

Signals and Waveforms: Grouping

x_3 x_2 x_1 x_0
↓ ↓ ↓ ↓


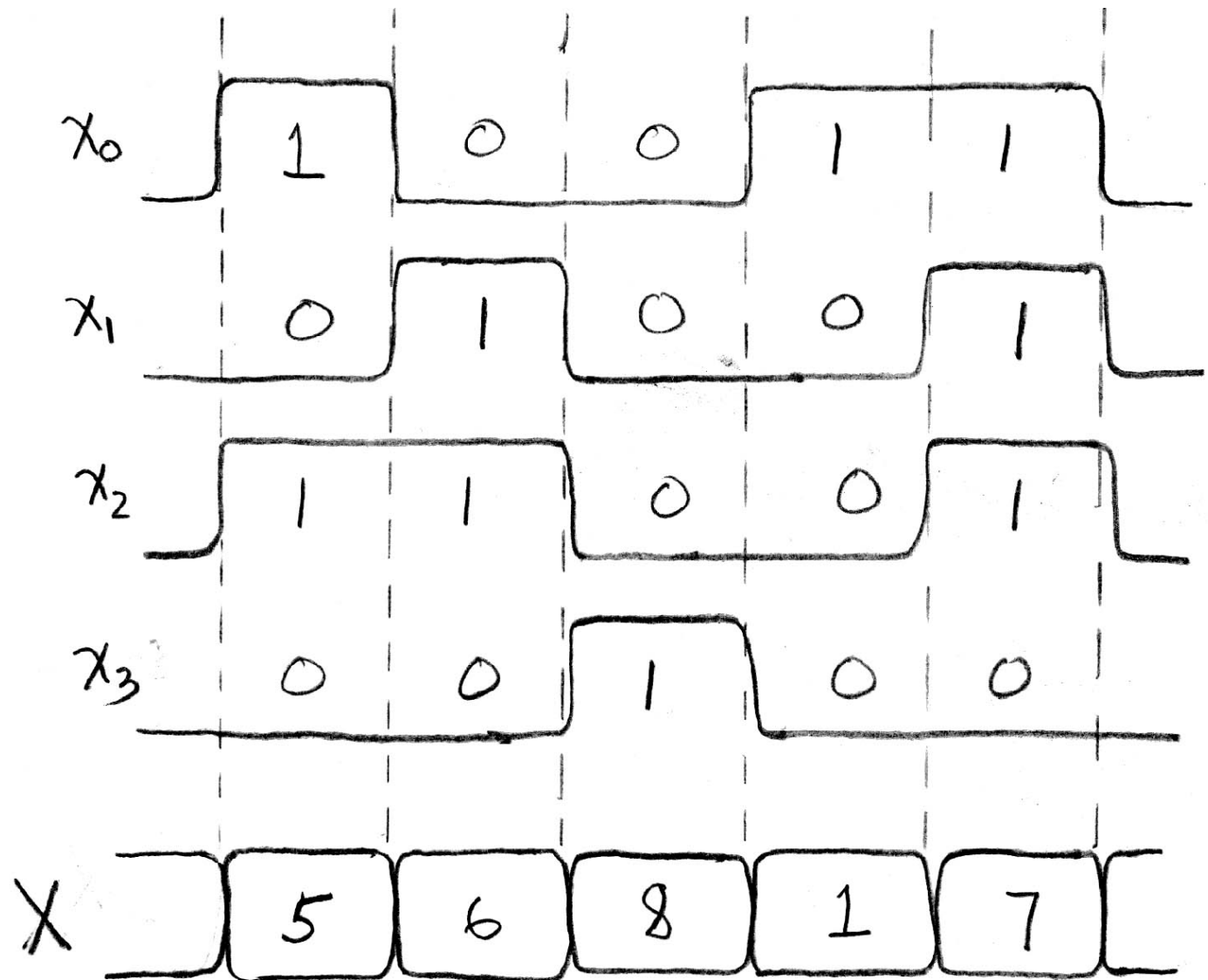


Signals and Waveforms: Circuit Delay



$$A = [a_3, a_2, a_1, a_0]$$

$$B = [b_3, b_2, b_1, b_0]$$

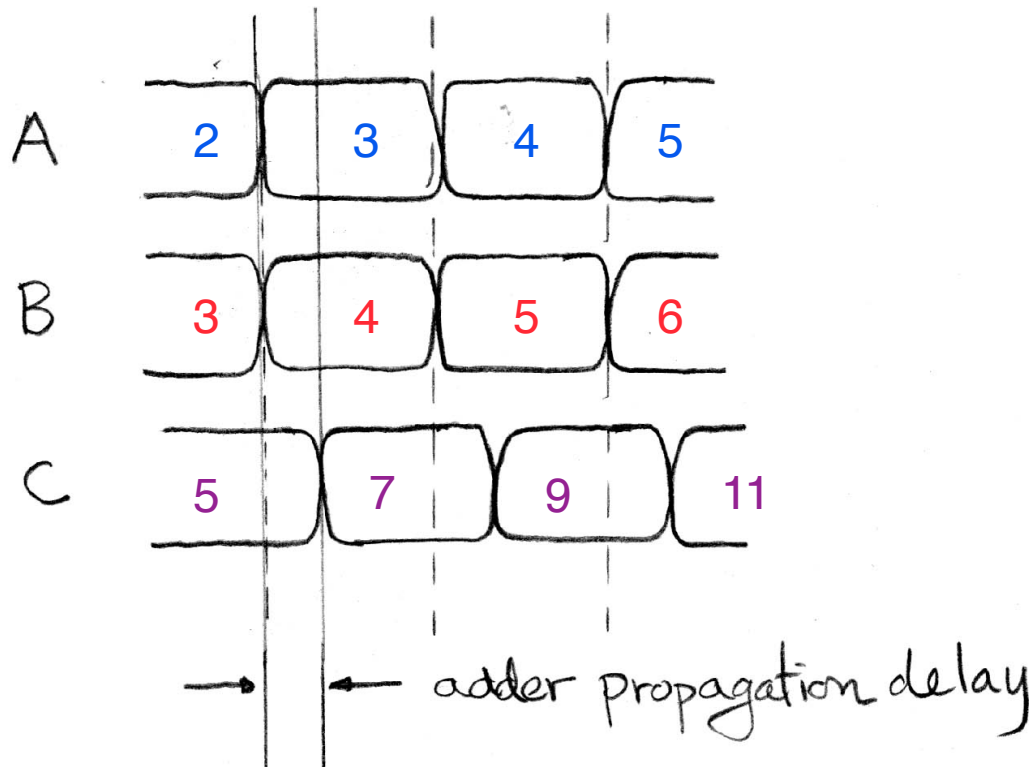
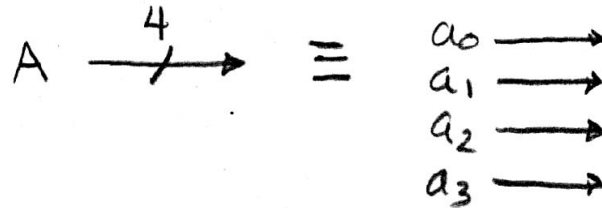


Type of Circuits

- **Synchronous Digital Systems are made up of two basic types of circuits:**
- **Combinational Logic (CL) circuits**
 - Our previous adder circuit is an example.
 - **Output is a function of the inputs only.**
 - Similar to a pure function in mathematics, $y = f(x)$. (No way to store information from one invocation to the next. No side effects)
- **State Elements: circuits that store information.**



Circuits with STATE (e.g., register)

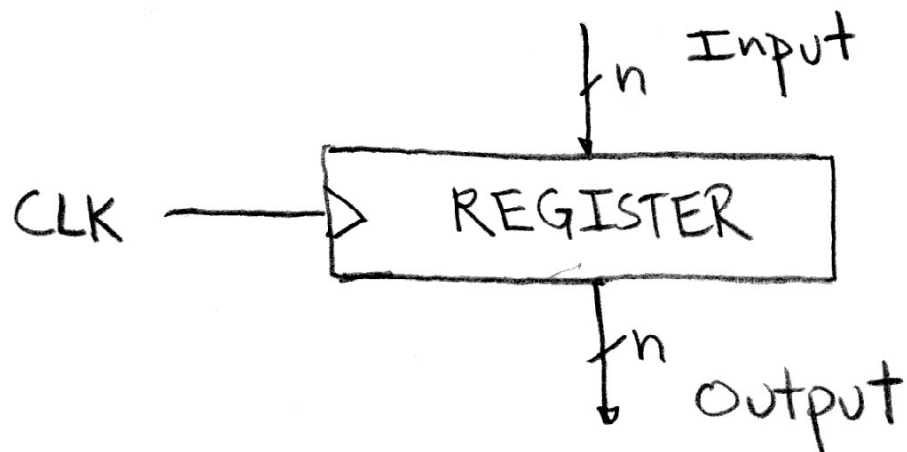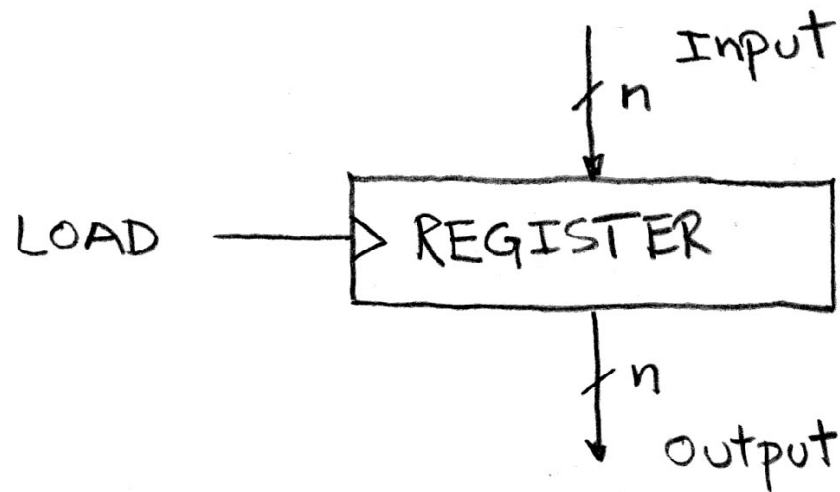


Peer Instruction

- A. SW **can peek** at HW (past ISA abstraction boundary) for optimizations
- B. SW **can depend** on particular HW implementation of ISA
- C. Timing diagrams serve as a **critical debugging tool** in the EE toolkit

	ABC
0:	FFF
1:	FFT
2:	FTF
3:	FTT
4:	TFF
5:	TFT
6:	TF
7:	TTT



Sample Debugging Waveform

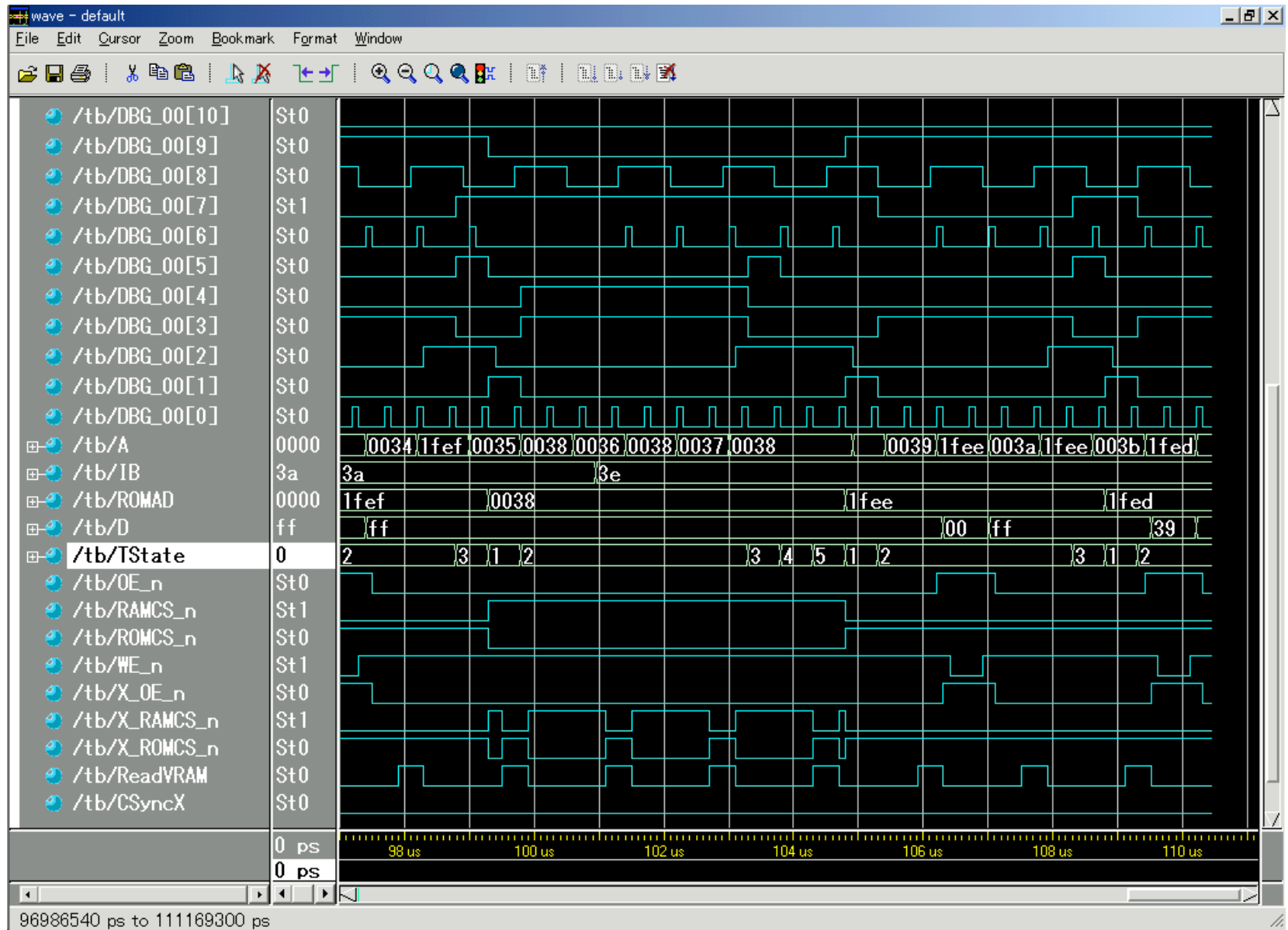

And in conclusion...

- **ISA is very important abstraction layer**
 - **Contract between HW and SW**
- **Clocks control pulse of our circuits**
- **Voltages are analog, quantized to 0/1**
- **Circuit delays are fact of life**
- **Two types of circuits:**
 - **Stateless Combinational Logic (&,!,~)**
 - **State circuits (e.g., registers)**

