



inst.eecs.berkeley.edu/~cs61c
UCB CS61C : Machine Structures

**Lecture 25
 CPU design (of a single-cycle CPU)**

Lecturer SOE
 Dan Garcia

Hi to Travis Grogan
 from NE Texas!

2008-03-31



GOOGLE GAMES (CAL VS STANFORD)!

Sat 2008-04-26 @ Google in Mountain View (Google will provide shuttles to MV) *"Think you got game? Compete for victory in challenges that test your creative, mental and "athletic" mettle at the Google Games! Teams of 5 will go head to head in rigorous events: Geek Trivia, Lego Building, Puzzles and "Athletic" contests. Find four friends (it helps to have a CS background) and register here..."*

<http://spreadsheets.google.com/viewform?key=pqUAXemApTXWzlmif4z1jTQ>



Review

- CPU design involves Datapath, Control
 - Datapath in MIPS involves 5 CPU stages
 1. Instruction Fetch
 2. Instruction Decode & Register Read
 3. ALU (Execute)
 4. Memory
 5. Register Write




CS61C L8 CPU Design : Designing a Single-Cycle CPU (8)

Garcia, Spring 2008 © UCB

Datapath Summary

 - The datapath based on data transfers required to perform instructions
- A controller causes the right transfers to happen



CS61C L8 CPU Design : Designing a Single-Cycle CPU (8)

Garcia, Spring 2008 © UCB

How to Design a Processor: step-by-step

1. Analyze instruction set architecture (ISA)
 - ⇒ datapath requirements
 1. meaning of each instruction is given by the register transfers
 2. datapath must include storage element for ISA registers
 3. datapath must support each register transfer
2. Select set of datapath components and establish clocking methodology
3. Assemble datapath meeting requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic




CS61C L8 CPU Design : Designing a Single-Cycle CPU (8)

Garcia, Spring 2008 © UCB

Review: The MIPS Instruction Formats

 - All MIPS instructions are 32 bits long. 3 formats:




- The different fields are:
 - op: operation ("opcode") of the instruction
 - rs, rt, rd: the source and destination register specifiers
 - shamt: shift amount
 - funct: selects the variant of the operation in the "op" field
 - address / immediate: address offset or immediate value
 - target address: target address of jump instruction



CS61C L8 CPU Design : Designing a Single-Cycle CPU (8)

Garcia, Spring 2008 © UCB

Step 1a: The MIPS-lite Subset for today

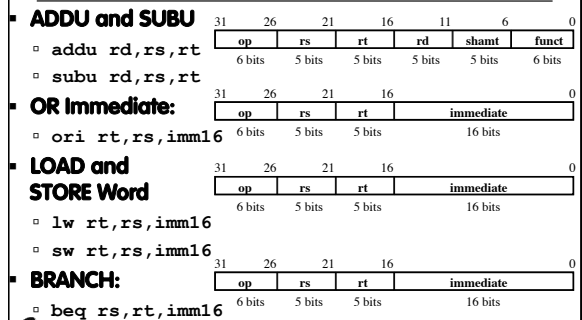

CS61C L8 CPU Design : Designing a Single-Cycle CPU (8)

Garcia, Spring 2008 © UCB

Register Transfer Language (RTL)

- RTL gives the meaning of the instructions (ASOLSB)

$(op, rs, rt, rd, shamt, funct) \leftarrow MEM[PC]$

$(op, rs, rt, Imm16) \leftarrow MEM[PC]$

- All start by fetching the instruction

inst ← Register Transfers

ADDU $R[rd] \leftarrow R[rs] + R[rt]; \quad PC \leftarrow PC + 4$

SUBU $R[rd] \leftarrow R[rs] - R[rt]; \quad PC \leftarrow PC + 4$

ORI $R[rt] \leftarrow R[rs] | zero_ext(Imm16); \quad PC \leftarrow PC + 4$

LOAD $R[rt] \leftarrow MEM[R[rs] + sign_ext(Imm16)]; \quad PC \leftarrow PC + 4$

STORE $MEM[R[rs] + sign_ext(Imm16)] \leftarrow R[rt]; \quad PC \leftarrow PC + 4$

BEQ if $(R[rs] == R[rt])$ then
 $PC \leftarrow PC + 4 + (sign_ext(Imm16) \ll 00)$
 else $PC \leftarrow PC + 4$

Cal

CMSC 158 CPU Design : Designing a Single-Cycle CPU (7)

©ards, Spring 2008 © UCS

Step 1: Requirements of the Instruction Set

- Memory (MEM)
 - instructions & data (will use one for each)
- Registers (R: 32 x 32)
 - read RS
 - read RT
 - Write RT or RD
- PC
- Extender (sign/zero extend)
- Add/Sub/OR unit for operation on register(s) or extended immediate
- Add 4 (+ maybe extended immediate) to PC
- Compare registers?

Cal

CMSC 158 CPU Design : Designing a Single-Cycle CPU (8)

©ards, Spring 2008 © UCS

Step 2: Components of the Datapath

- Combinational Elements
- Storage Elements
 - Clocking methodology


Cal

CMSC 158 CPU Design : Designing a Single-Cycle CPU (9)


©ards, Spring 2008 © UCS

Combinational Logic Elements (Building Blocks)


- Adder

 

- MUX

 

- ALU

 

Cal

CMSC 158 CPU Design : Designing a Single-Cycle CPU (10)

©ards, Spring 2008 © UCS

ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:


```
ADDU  R[rd] = R[rs] + R[rt]; ...
SUBU  R[rd] = R[rs] - R[rt]; ...
ORI   R[rt] = R[rs] | zero_ext(Imm16) ...
BEQ   if ( R[rs] == R[rt] ) ...
```
- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND, Set Less Than (1 if A < B, 0 otherwise)
- ALU follows chap 5

Cal

CMSC 158 CPU Design : Designing a Single-Cycle CPU (11)

©ards, Spring 2008 © UCS

Administrivia

- Read the book! Important to understand lecture and for project.
 - P&H 5.1-5.4
- TAs will cover lec; I'll be representing Cal at a workshop in DC this wed/thu/fri. Topic?
 - Make a priority list of the most critical issues facing computing education in the US now.
 - Identify potential solutions to the most critical needs
 - Set forward a plan of action to solve the problems identified.

Cal

CMSC 158 CPU Design : Designing a Single-Cycle CPU (12)

©ards, Spring 2008 © UCS

What Hardware Is Needed? (1/2)

- **PC: a register which keeps track of memory addr of the next instruction**
- **General Purpose Registers**
 - used in Stages 2 (Read) and 5 (Write)
 - MIPS has 32 of these
- **Memory**
 - used in Stages 1 (Fetch) and 4 (R/W)
 - cache system makes these two stages as fast as the others, on average




What Hardware Is Needed? (2/2)

- **ALU**
 - used in Stage 3
 - something that performs all necessary functions: arithmetic, logicals, etc.
 - we'll design details later
- **Miscellaneous Registers**
 - In implementations with only one stage per clock cycle, registers are inserted between stages to hold intermediate data and control signals as they travels from stage to stage.
 - Note: Register is a general purpose term meaning something that stores bits. Not all registers are in the "register file".




Storage Element: Idealized Memory

- **Memory (idealized)**
 - One input bus: Data In
 - One output bus: Data Out
- **Memory word is found by:**
 - Address selects the word to put on Data Out
 - Write Enable = 1: address selects the memory word to be written via the Data In bus
- **Clock input (CLK)**
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - Address valid ⇒ Data Out valid after "access time."

 


Storage Element: Register (Building Block)

 - **Similar to D Flip Flop except**
 - N-bit input and output
 - Write Enable input
- **Write Enable:**
 - negated (or deasserted) (0): Data Out will not change
 - asserted (1): Data Out will become Data In on positive edge of clock



Storage Element: Register File

- **Register File consists of 32 registers:**
 - Two 32-bit output busses: busA and busB
 - One 32-bit input bus: busW
- **Register is selected by:**
 - RA (number) selects the register to put on busA (data)
 - RB (number) selects the register to put on busB (data)
 - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- **Clock input (clk)**
 - The clk input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - RA or RB valid ⇒ busA or busB valid after "access time."

 


Step 3: Assemble DataPath meeting requirements

- **Register Transfer Requirements**
⇒ Datapath Assembly
- **Instruction Fetch**
- **Read Operands and Execute Operation**



3a: Overview of the Instruction Fetch Unit


 
- The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{"something else"}$



Cal

3b: Add & Subtract

  - $R[\text{rd}] = R[\text{rs}] \text{ op } R[\text{rt}]$ Ex.: `addU rd,rs,rt`
 - Ra, Rb, and Rr come from instruction's Rs, Rt, and Rd fields
 - ALUctr and RegWr: control logic after decoding the instruction



Cal

... Already defined the register file & ALU

Peer Instruction

- Our ALU is a synchronous device
- We should use the main ALU to compute $\text{PC}=\text{PC}+4$
- The ALU is inactive for memory reads or writes.

	ABC
0:	FFF
1:	FFT
2:	FTF
3:	FTT
4:	TFF
5:	TFT
6:	TF T
7:	TTT

Cal

How to Design a Processor: step-by-step

- Analyze instruction set architecture (ISA)
 - ⇒ datapath requirements
 - meaning of each instruction is given by the register transfers
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- Select set of datapath components and establish clocking methodology
- Assemble datapath meeting requirements
- Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- Assemble the control logic (hard part!)

Cal