

`inst.eecs.berkeley.edu/~cs61c/su06`  
**CS61C : Machine Structures**

## **Lecture #16 – Datapath**



**2006-07-25**


**Andy Carle**




CS 61C L16 Datapath (1)

A Carle, Summer 2006 © UCB

# Anatomy: 5 components of any Computer

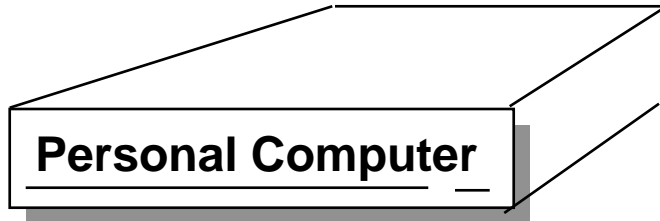

This week

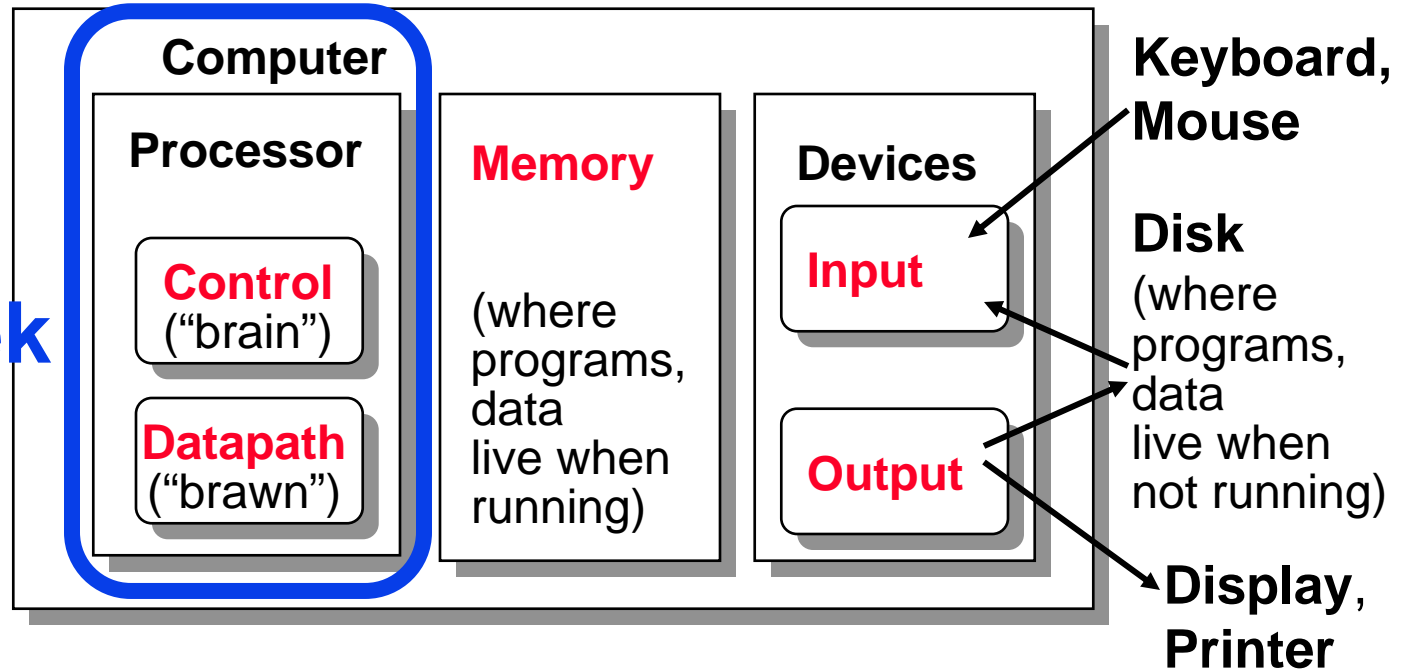

# Outline

---

- **Design a processor: step-by-step**
- **Requirements of the Instruction Set**
- **Hardware components that match the instruction set requirements**



# How to Design a Processor: step-by-step


- 1. Analyze instruction set architecture (ISA)  
=> datapath requirements
  - meaning of each instruction is given by the *register transfers*
  - datapath must include storage element for ISA registers
  - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology
- 3. Assemble datapath meeting requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic




# Step 1: The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:


- R-type

 

- I-type

 

- J-type

 


- The different fields are:

- op**: operation (“opcode”) of the instruction
- rs, rt, rd**: the source and destination register specifiers
- shamt**: shift amount
- funct**: selects the variant of the operation in the “op” field
- address / immediate**: address offset or immediate value
- target address**: target address of jump instruction




# Step 1: The MIPS-lite Subset for today


## • ADD and SUB

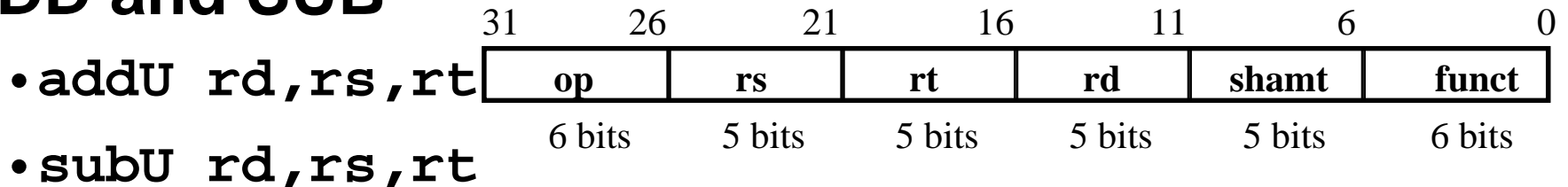


## • OR Immediate:

 

## • LOAD and STORE Word

 

## • BRANCH:

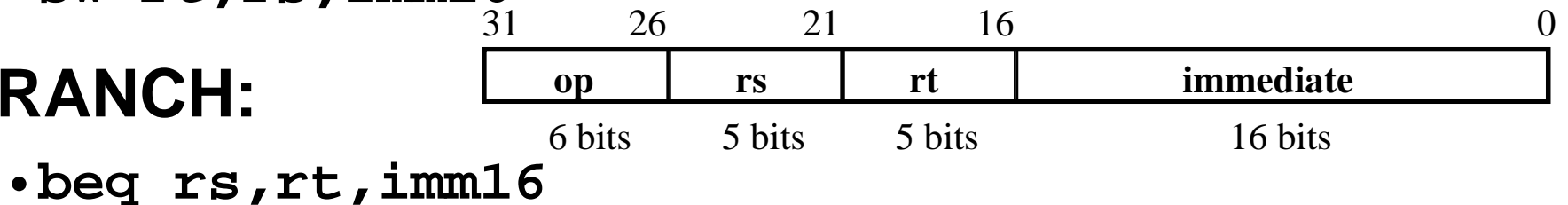

# Step 1: Register Transfer Language

- RTL gives the meaning of the instructions

$\{op, rs, rt, rd, shamt, funct\} = MEM[PC]$

$\{op, rs, rt, Imm16\} = MEM[PC]$

- All start by fetching the instruction

inst Register Transfers

ADDU  $R[rd] = R[rs] + R[rt];$   $PC = PC + 4$

SUBU  $R[rd] = R[rs] - R[rt];$   $PC = PC + 4$

ORI  $R[rt] = R[rs] | zero\_ext(Imm16);$   $PC = PC + 4$

LOAD  $R[rt] = MEM[R[rs] + sign\_ext(Imm16)]; PC = PC + 4$

STORE  $MEM[R[rs] + sign\_ext(Imm16)] = R[rt]; PC = PC + 4$

BEQ  $if ( R[rs] == R[rt] ) then PC = PC + 4 +$   
 $sign\_ext(Imm16) \ll 2$   
 $else PC = PC + 4$



# Step 1: Requirements of the Instruction Set


---

- **Memory (MEM)**
  - instructions & data
- **Registers (R: 32 x 32)**
  - read RS
  - read RT
  - Write RT or RD
- **PC**
- **Extender (sign extend)**
- **Add and Sub register or extended immediate**
- **Add 4 or extended immediate to PC**





# Step 1: Abstract Implementation

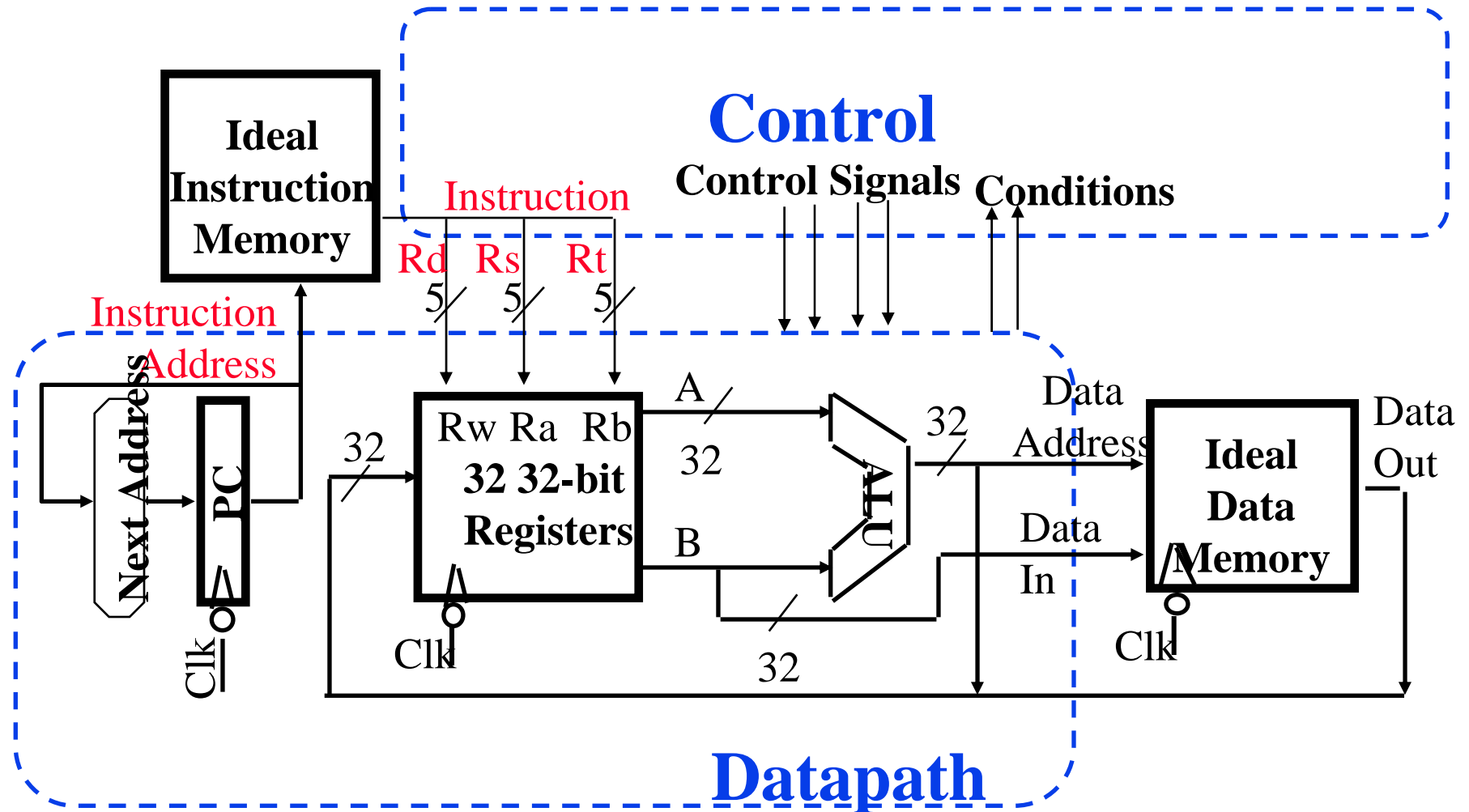

# How to Design a Processor: step-by-step

- **1. Analyze instruction set architecture (ISA) => datapath requirements**
  - meaning of each instruction is given by the *register transfers*
  - datapath must include storage element for ISA registers
  - datapath must support each register transfer
- **2. Select set of datapath components and establish clocking methodology**
- **3. Assemble datapath meeting requirements**
- **4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.**
- **5. Assemble the control logic (hard part!)**




## **Step 2a: Components of the Datapath**

- **Combinational Elements**
- **Storage Elements**
  - **Clocking methodology**





# Combinational Logic: More Elements

- **Adder**

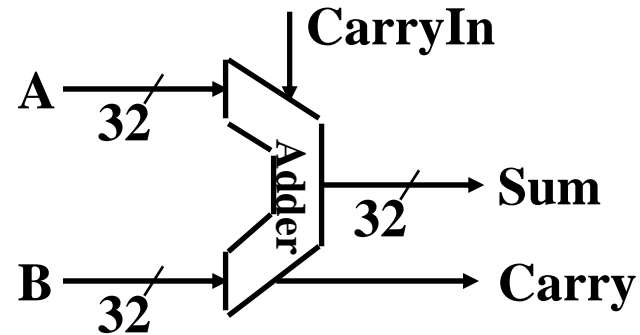

- **MUX**

 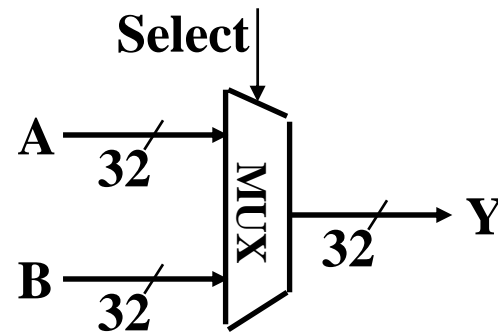

# ALU Needs for MIPS-lite + Rest of MIPS

---

- Addition, subtraction, logical OR, ==:

ADDU  $R[rd] = R[rs] + R[rt]; \dots$

SUBU  $R[rd] = R[rs] - R[rt]; \dots$

ORI  $R[rt] = R[rs] \mid \text{zero\_ext}(\text{Imm16}) \dots$

BEQ `if ( R[rs] == R[rt] )...`

- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND,  
Set Less Than (1 if  $A < B$ , 0 otherwise)
- ALU follows chap 5



# Storage Element: Idealized Memory

- **Memory (idealized)**


- One input bus: Data In
- One output bus: Data Out

- **Memory word is selected by:**

- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus


- **Clock input (CLK)**

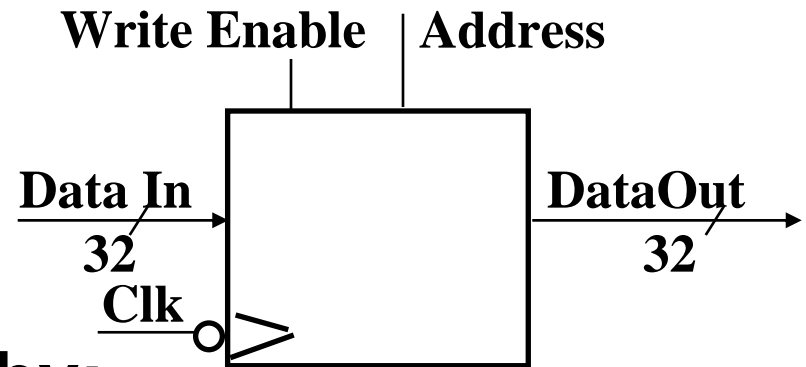- The CLK input is a factor **ONLY** during write operation
- During read operation, behaves as a combinational logic block:
  - Address valid => Data Out valid after “access time.”


 
# Storage Element: Register (Building Block)

- **Similar to D Flip Flop except**
  - N-bit input and output
  - Write Enable input
- **Write Enable:**
  - negated (or deasserted) (0):  
Data Out will not change
  - asserted (1):  
Data Out will become Data In



# Storage Element: Register File

- Register File consists of 32 registers:

- Two 32-bit output busses:

busA and busB

- One 32-bit input bus: busW


- Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- Clock input (CLK)

- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:

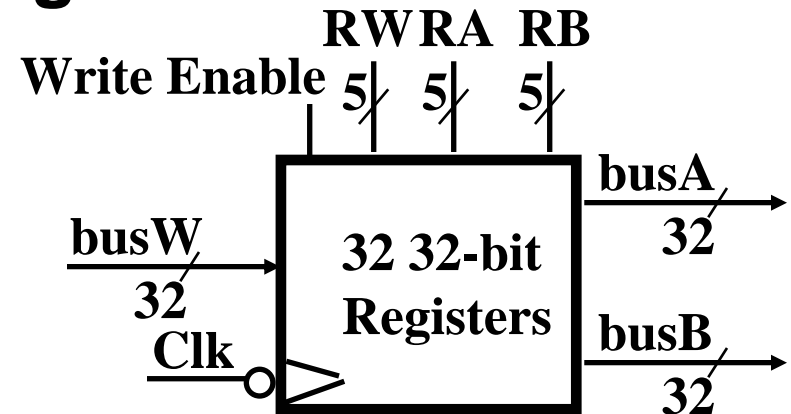- RA or RB valid => busA or busB valid after “access time.”





# Administrivia

---

- **Project 2 due Friday**
  - **Hope you've already started**
- **HW5 (maybe HW56?) out soon**



## Step 3: Assemble DataPath meeting requirements


---

- Register Transfer Requirements  
⇒ Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation


 
## 3a: Overview of the Instruction Fetch Unit


- The common RTL operations
  - Fetch the Instruction:  $\text{mem}[\text{PC}]$
  - Update the program counter:
    - Sequential Code:  $\text{PC} = \text{PC} + 4$
    - Branch and Jump:  $\text{PC} = \text{“something else”}$



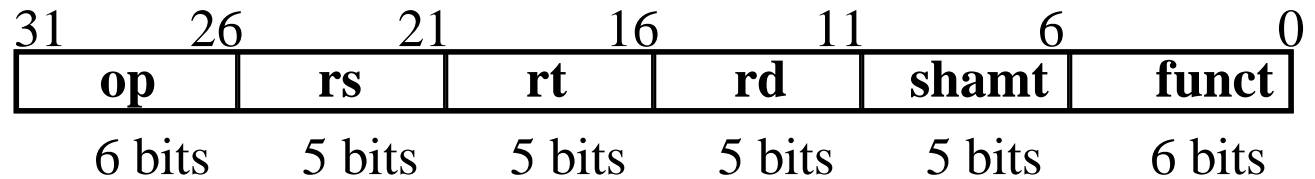
## 3b: Add & Subtract

•  $R[rd] = R[rs] \text{ op } R[rt]$  Ex.: `addU rd,rs,rt`

• Ra, Rb, and Rw come from instruction's **Rs**, **Rt**, and **Rd** fields




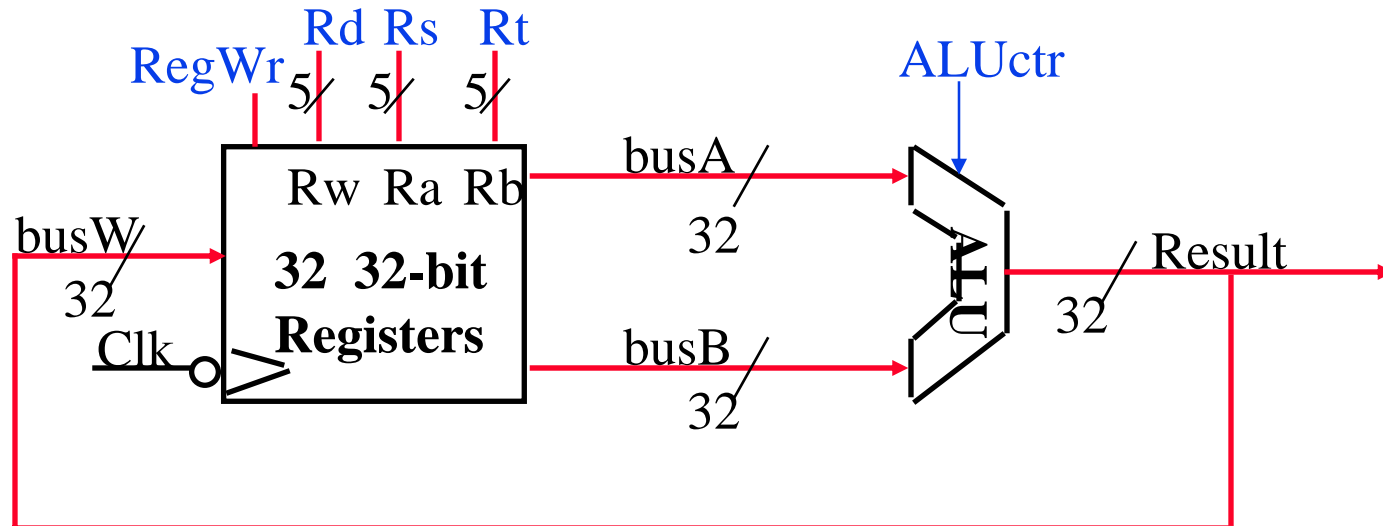• **ALUctr** and **RegWr**: control logic after decoding the instruction



• Already defined register file, ALU



# Clocking Methodology

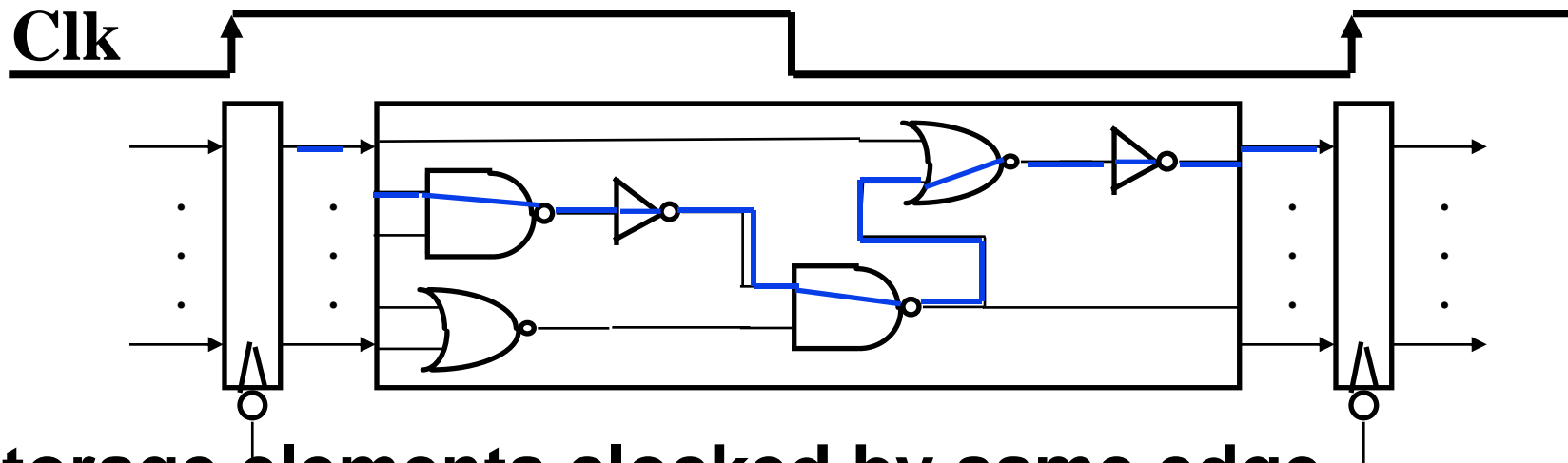

- **Storage elements clocked by same edge**
- **Being physical devices, flip-flops (FF) and combinational logic have some delays**
  - **Gates: delay from input change to output change**
  - **Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF, and we have the usual clock-to-Q delay**
- **“Critical path” (longest path through logic) determines length of clock period**



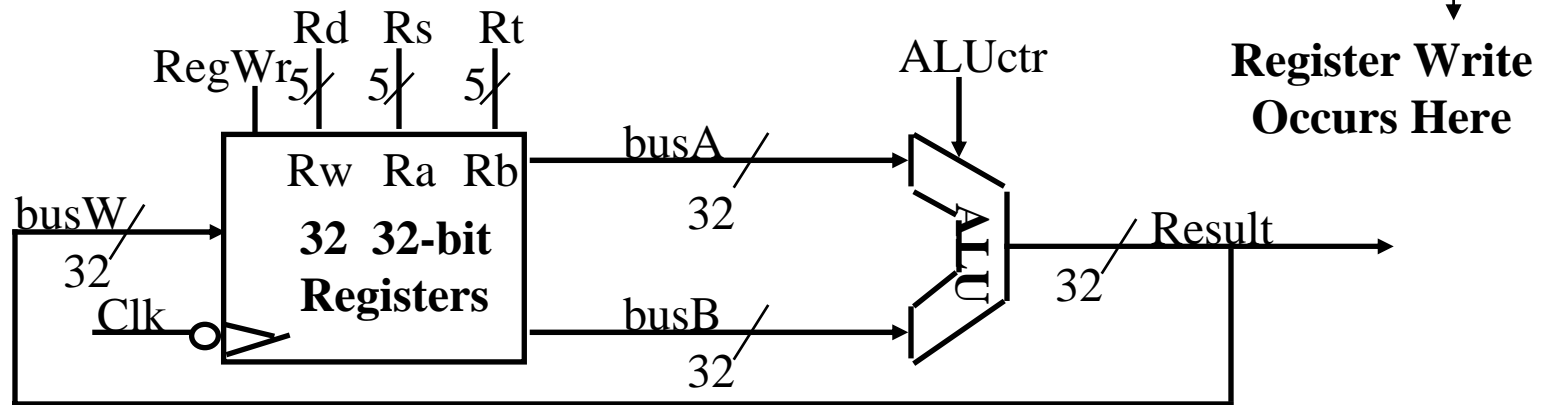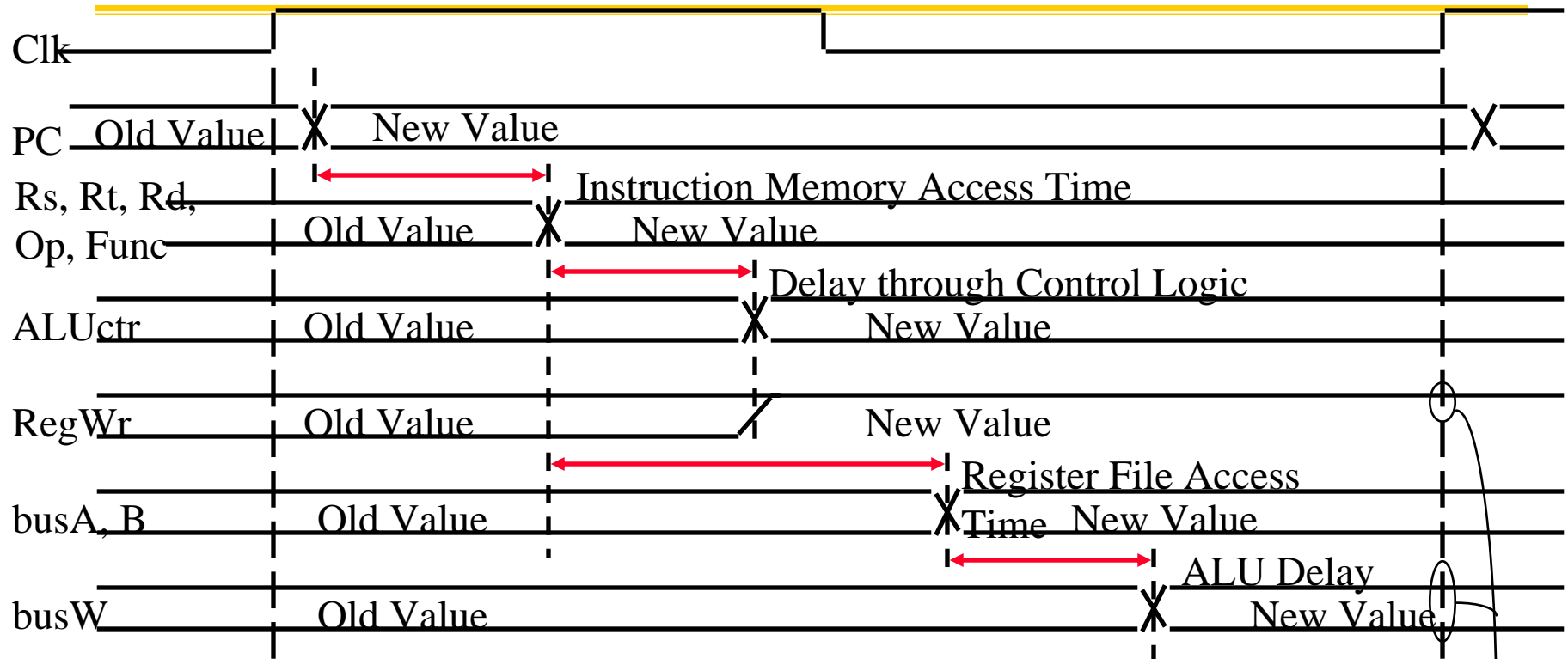
# Register-Register Timing: One complete cycle



 
# 3c: Logical Operations with Immediate

- $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$





*What about Rt register read??*

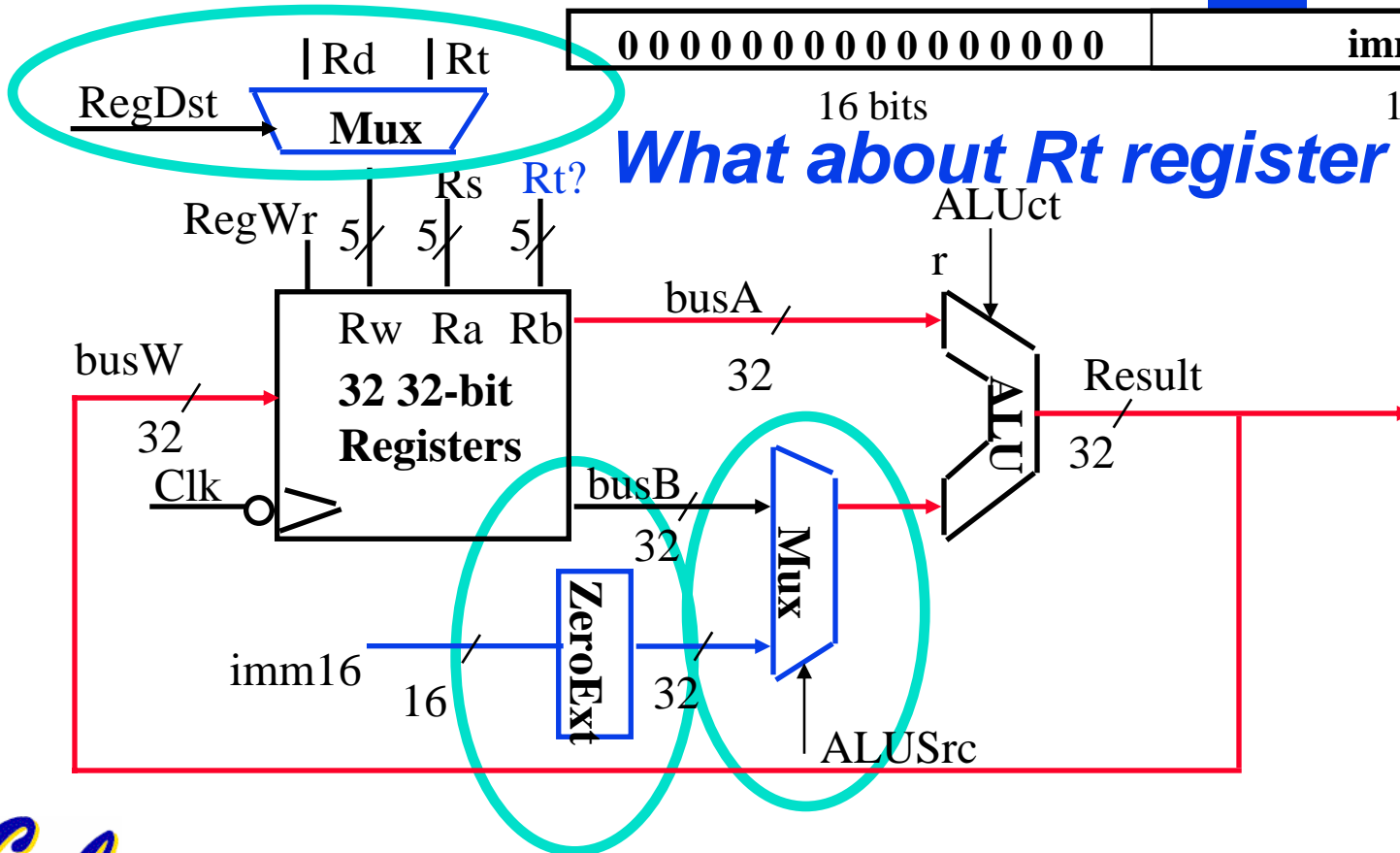

• Already defined 32-bit MUX; Zero Ext?
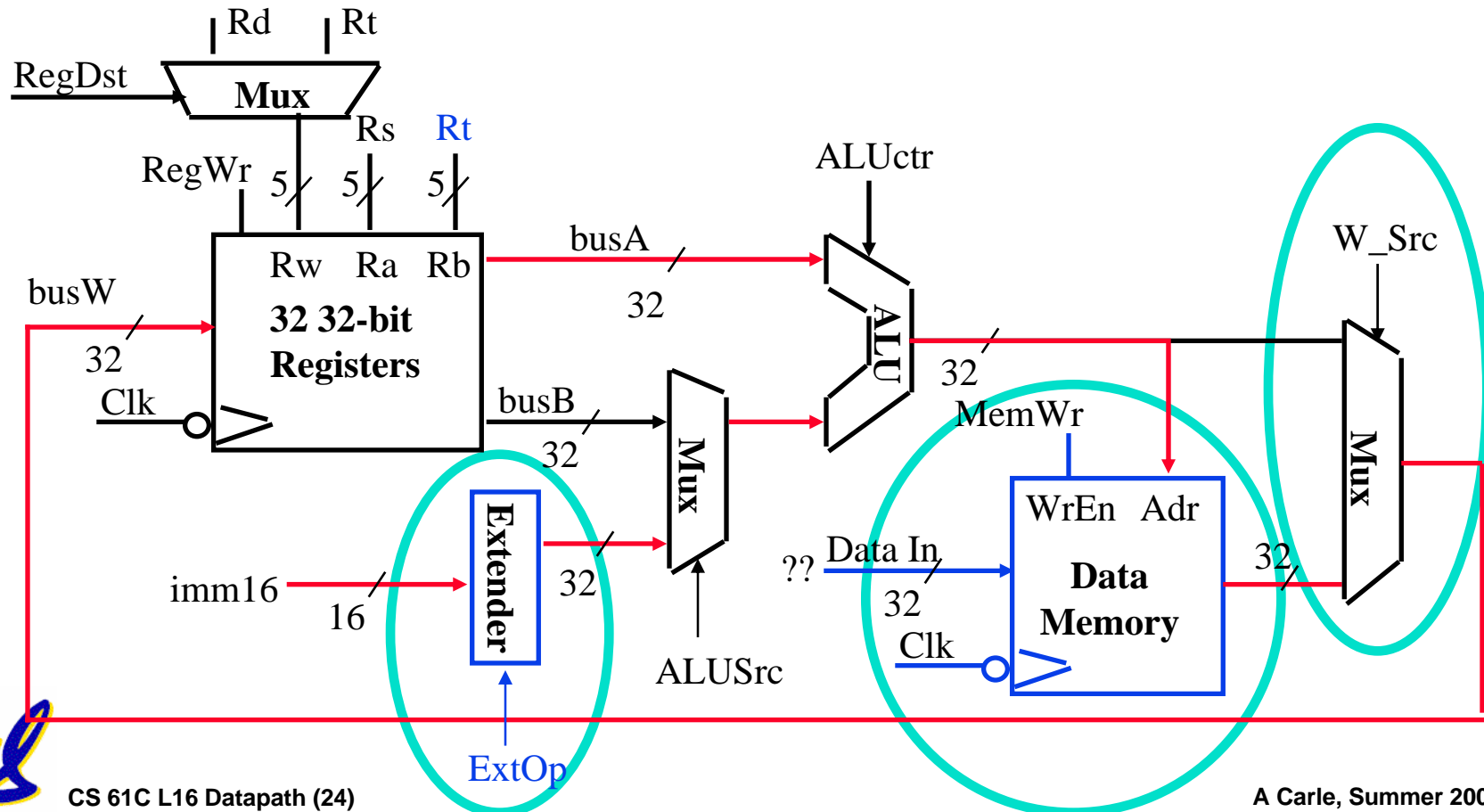 
## 3d: Load Operations


- $R[rt] = Mem[R[rs] + SignExt[imm16]]$   
Example: `lw rt, rs, imm16`





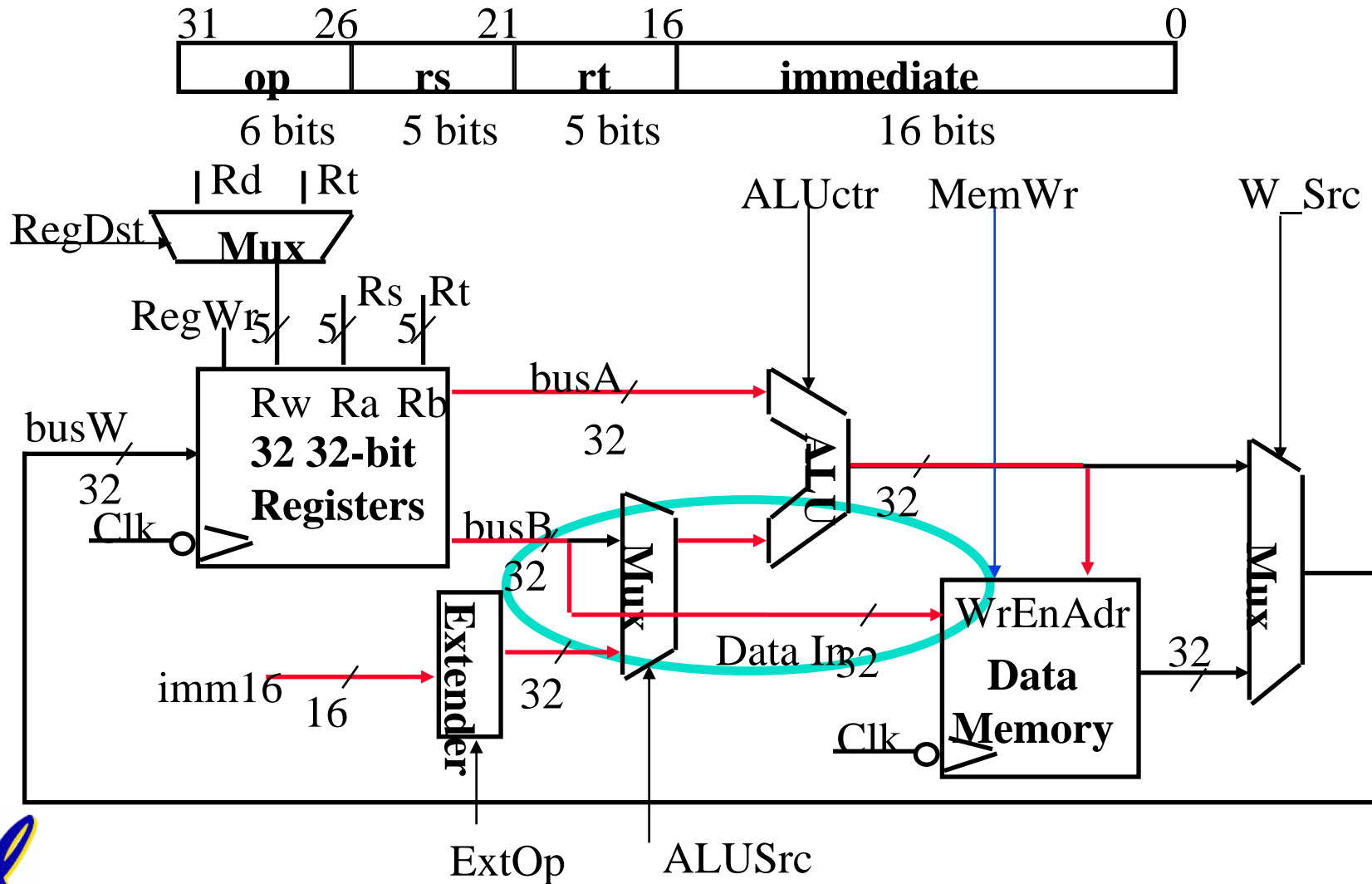
# 3e: Store Operations

- $\text{Mem}[ R[\text{rs}] + \text{SignExt}[\text{imm16}] ] = R[\text{rt}]$   
 Ex.: `sw rt, rs, imm16`



## 3f: The Branch Instruction

---

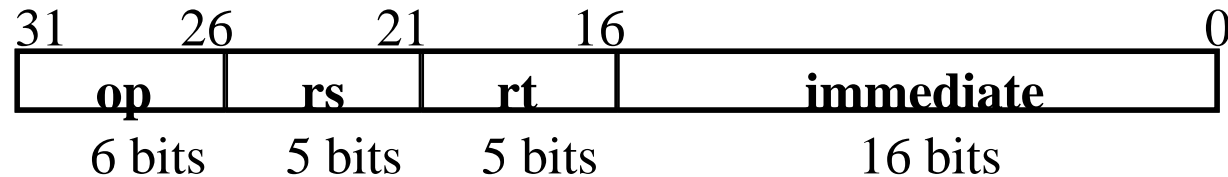



- **beq rs, rt, imm16**
  - **mem[PC] Fetch the instruction from memory**
  - **Equal = R[rs] == R[rt] Calculate branch condition**
  - **if (Equal) Calculate the next instruction's address**
    - **PC = PC + 4 + ( SignExt(imm16) x 4 )**
  - else**
    - **PC = PC + 4**



# Datapath for Branch Operations


- **beq** rs, rt, imm16

**Datapath generates condition (equal)**

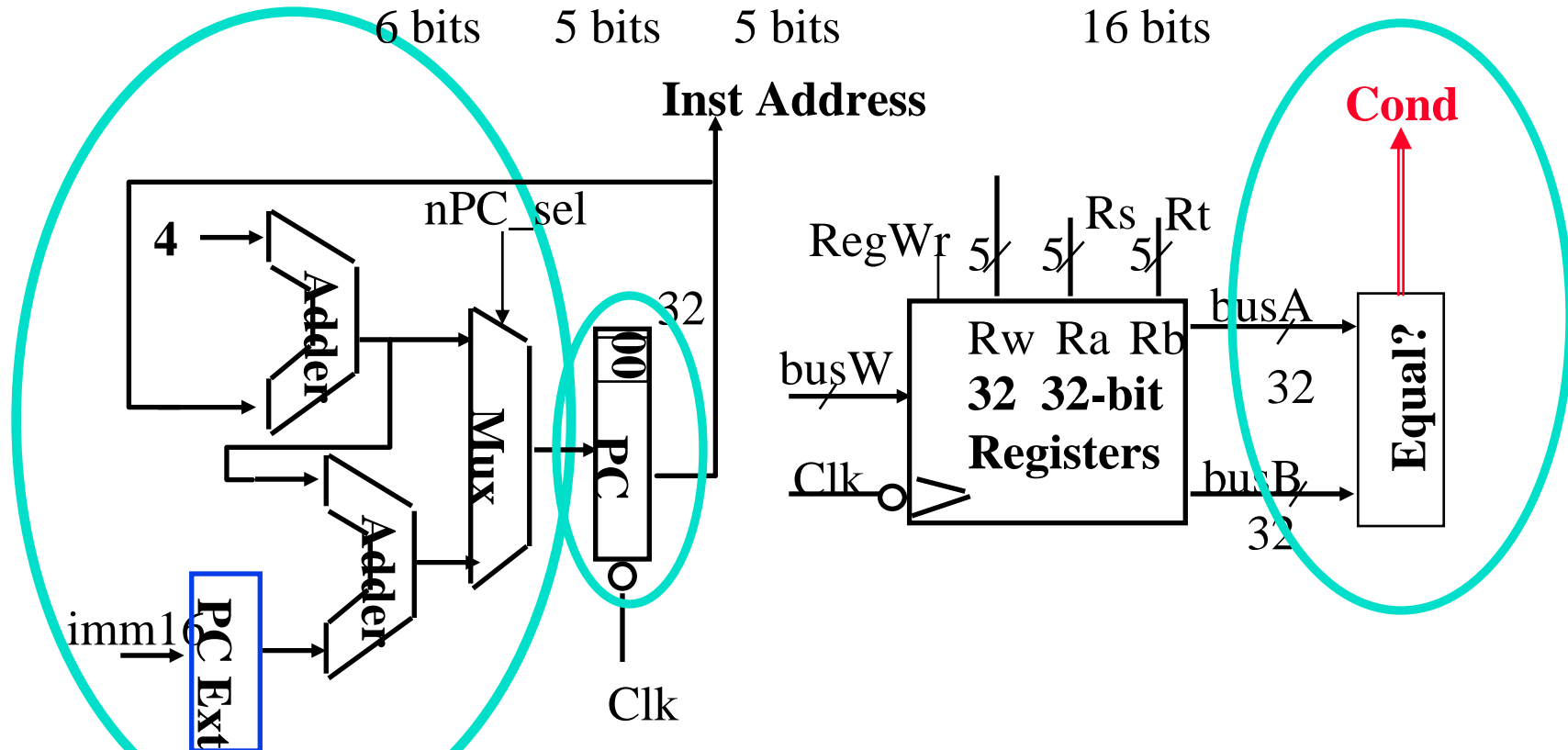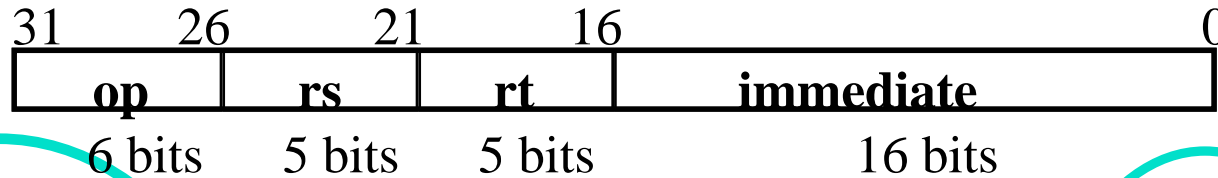

• **Already MUX, adder, sign extend, zero**
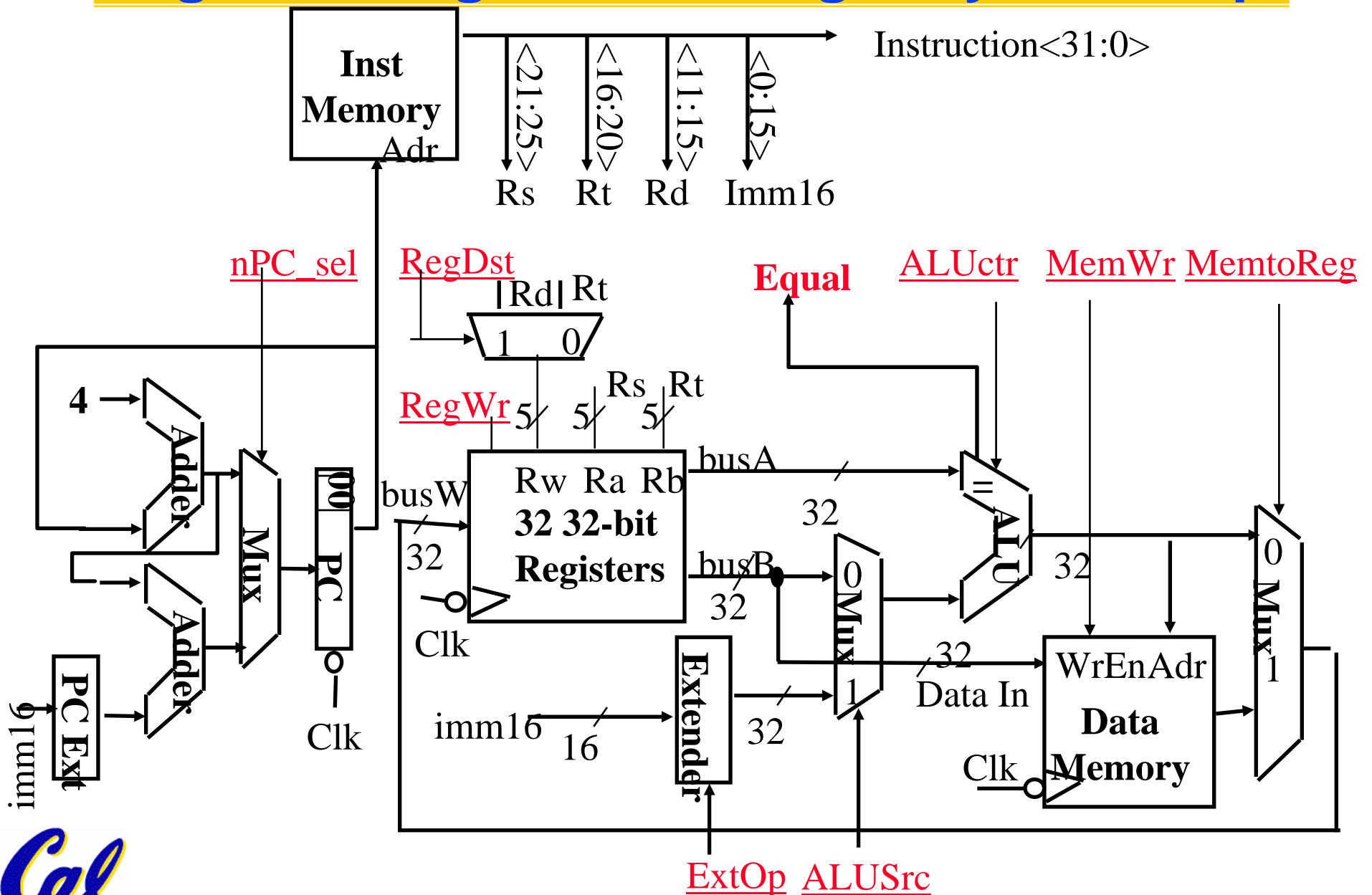
# Putting it All Together: A Single Cycle Datapath



# Peer Instruction

---

- A. Our **ALU** is a synchronous device
- B. We should use the **main ALU** to compute  $PC=PC+4$
- C. The **ALU is inactive** for memory reads or writes.



# Summary: Single cycle datapath

## ◦ 5 steps to design a processor

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

## ◦ Control is the hard part

## ◦ Next time!

