


inst.eecs.berkeley.edu/~cs61c
CS61C : Machine Structures

Lecture 17
Combinational Logic Blocks and Intro to CPU Design

2010-07-20



Instructor Paul Pearce

Passwords that are simple, AND safe→

Researchers at Harvard and Microsoft have developed a new scheme for password requirements that simply mandates that no single password may be "too popular." Their findings will be presented at Hot Topics in Security next month.

<http://www.technologyreview.com/computing/25826/>

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (1) Pearce, Summer 2010 © UCB

Review

• Use this table and techniques we learned to transform from 1 to another

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (2) Pearce, Summer 2010 © UCB

Today

- Data Multiplexors
- Arithmetic and Logic Unit
- Adder/Subtractor
- Datapath design

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (3) Pearce, Summer 2010 © UCB

Data Multiplexor (here 2-to-1, n-bit-wide)

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (4) Pearce, Summer 2010 © UCB

N instances of 1-bit-wide mux

How many rows in TT?

$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1)) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (5) Pearce, Summer 2010 © UCB


How do we build a 1-bit-wide mux?

$\bar{s}a + sb$

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (6) Pearce, Summer 2010 © UCB

4-to-1 Multiplexor?

How many rows in TT?

 

$$e = \overline{s_1}\overline{s_0}a + \overline{s_1}s_0b + s_1\overline{s_0}c + s_1s_0d$$


Cal

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (7)

Pearce, Summer 2010 © UCB

Is there any other way to do it?

Hint: NCAA tourney!

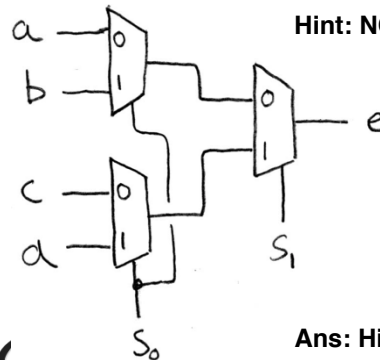

Ans: Hierarchically!


Cal

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (8)

Pearce, Summer 2010 © UCB

Arithmetic and Logic Unit

 - Most processors contain a special logic block called "Arithmetic and Logic Unit" (ALU)
- We'll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR




when *S*=00, *R*=*A*+*B*
 when *S*=01, *R*=*A*-*B*
 when *S*=10, *R*=*A* AND *B*
 when *S*=11, *R*=*A* OR *B*

Cal

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (9)

Pearce, Summer 2010 © UCB

Our simple ALU

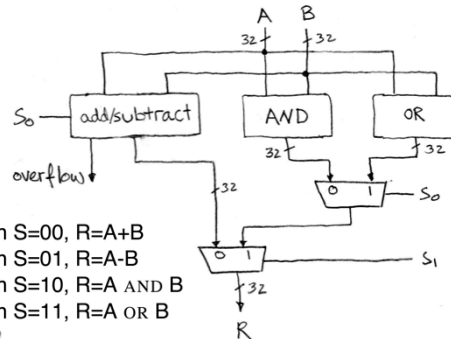

when *S*=00, *R*=*A*+*B*
 when *S*=01, *R*=*A*-*B*
 when *S*=10, *R*=*A* AND *B*
 when *S*=11, *R*=*A* OR *B*

Cal

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (10)

Pearce, Summer 2010 © UCB

Adder/Subtractor Design -- how?

- Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer

Cal

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (11)

Pearce, Summer 2010 © UCB

Administrivia

- If you want a regrade for your midterm, staple a paper with your explanation (clearly indicating on what question you want more points) to your exam and turn it in to your TA in section Monday
 - We'll regrade the exam and your score MIGHT go down...
 - We will regrade with respect to the established rubric, so that all tests are graded equally
- Project 2 will be done with 1 partner (groups of 2). Start thinking about who you want to work with.
 - Hint: Your best friend may not be the best choice for a partner. Projects ruin friendships.
- HW6 due tomorrow at midnight.

Cal

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (12)

Pearce, Summer 2010 © UCB

Adder/Subtractor – One-bit adder LSB...

+	a_3	a_2	a_1	a_0	a_0	b_0	s_0	c_1
	b_3	b_2	b_1	b_0		0	0	0
	s_3	s_2	s_1	s_0		0	1	0
						1	0	0
						1	0	1

$s_0 =$
 $c_1 =$




Adder/Subtractor – One-bit adder (1/2)...

+	a_3	a_2	a_1	a_0	a_i	b_i	c_i	s_i	c_{i+1}
	b_3	b_2	b_1	b_0		0	0	0	0
	s_3	s_2	s_1	s_0		0	1	1	0
						0	1	0	0
						1	0	1	0
						1	0	0	1
						1	1	1	1

$s_i =$
 $c_{i+1} =$



 
Adder/Subtractor – One-bit adder (2/2)...



$s_i = \text{XOR}(a_i, b_i, c_i)$
 $c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$



N 1-bit adders \Rightarrow 1 N-bit adder

 


What about overflow?
Overflow = c_n ?



What about overflow?

• Consider a 2-bit signed # & overflow:

 - 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



• Highest adder

- $C_1 = \text{Carry-in} = C_{in}$, $C_2 = \text{Carry-out} = C_{out}$
- No C_{out} or $C_{in} \Rightarrow$ NO overflow!

What op? • C_{in} , and $C_{out} \Rightarrow$ NO overflow!


- C_{in} , but no $C_{out} \Rightarrow$ A,B both > 0, overflow!
- C_{out} , but no $C_{in} \Rightarrow$ A,B both < 0, overflow!



What about overflow?

• Consider a 2-bit signed # & overflow:

- 10 = -2
- 11 = -1
- 00 = 0
- 01 = 1

 

• Overflows when...

- C_{in} , but no $C_{out} \Rightarrow$ A,B both > 0, overflow!
- C_{out} , but no $C_{in} \Rightarrow$ A,B both < 0, overflow!

overflow = $c_n \text{ XOR } c_{n-1}$



Extremely Clever Subtractor

$A - B = A + (-B)$; how do we make “-B”?

x	y	xor
0	0	0
0	1	1
1	0	1
1	1	0

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (19) Pearce, Summer 2010 © UCB

Five Components of a Computer

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (20) Pearce, Summer 2010 © UCB

The CPU

- **Processor (CPU):** the active part of the computer, which does all the work (data manipulation and decision-making)
- **Datapath:** portion of the processor which contains hardware necessary to perform operations required by the processor (the brawn)
- **Control:** portion of the processor (also in hardware) which tells the datapath what needs to be done (the brain)

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (21) Pearce, Summer 2010 © UCB

Stages of the Datapath : Overview

- **Problem:** a single, atomic block which “executes an instruction” (performs all necessary operations beginning with fetching the instruction) would be too bulky and inefficient
- **Solution:** break up the process of “executing an instruction” into stages, and then connect the stages to create the whole datapath
 - smaller stages are easier to design
 - easy to optimize (change) one stage without touching the others

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (22) Pearce, Summer 2010 © UCB

Stages of the Datapath (1/5)

- There is a wide variety of MIPS instructions: so what general steps do they have in common?
- **Stage 1: Instruction Fetch**
 - no matter what the instruction, the 32-bit instruction word must first be fetched from memory (the cache-memory hierarchy)
 - also, this is where we increment PC (that is, $PC = PC + 4$, to point to the next instruction: byte addressing so + 4)

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (23) Pearce, Summer 2010 © UCB

Stages of the Datapath (2/5)

- **Stage 2: Instruction Decode**
 - upon fetching the instruction, we next gather data from the fields (decode all necessary instruction data)
 - first, read the opcode to determine instruction type and field lengths
 - second, read in data from all necessary registers
 - for add, read two registers
 - for addi, read one register
 - for jal, no reads necessary

CS61C L17 Combinational Logic Blocks and Intro to CPU Design (24) Pearce, Summer 2010 © UCB

Stages of the Datapath (3/5)

• Stage 3: ALU (Arithmetic-Logic Unit)

- the real work of most instructions is done here: arithmetic (+, -, *, /), shifting, logic (&, !), comparisons (s₁t)
- what about loads and stores?
 - lw \$t0, 40(\$t1)
 - the address we are accessing in memory = the value in \$t1 PLUS the value 40
 - so we do this addition in this stage



Stages of the Datapath (4/5)

• Stage 4: Memory Access

- actually only the load and store instructions do anything during this stage; the others remain idle during this stage or skip it all together
- since these instructions have a unique step, we need this extra stage to account for them
- as a result of the cache system, this stage is expected to be fast




Stages of the Datapath (5/5)

• Stage 5: Register Write

- most instructions write the result of some computation into a register
- examples: arithmetic, logical, shifts, loads, stl
- what about stores, branches, jumps?
 - don't write anything into a register at the end
 - these remain idle during this fifth stage or skip it all together



Generic Steps of Datapath

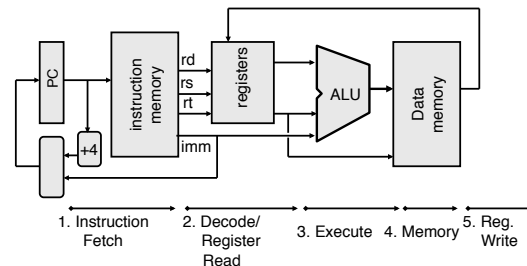

Peer Instruction

- 1) Truth table for mux with 4-bits of select is 2^4 rows long
- 2) We could cascade N 1-bit shifters to make 1 N-bit shifter for srl, srl

- | | |
|----|----|
| | 12 |
| a) | FF |
| b) | FT |
| c) | TF |
| d) | TT |



“And In conclusion...”

- Use muxes to select among input
 - S input bits selects 2^S inputs
 - Each input can be n-bits wide, independent of S
- Can implement muxes hierarchically
- ALU can be implemented using a mux
 - Coupled with basic block elements
- N-bit adder-subtractor done using N 1-bit adders with XOR gates on input
 - XOR serves as conditional inverter
- CPU design involves Datapath, Control
 - Datapath in MIPS involves 5 CPU stages
 1. Instruction Fetch
 2. Instruction Decode & Register Read
 3. ALU (Execute)
 4. Memory
 5. Register Write

