

Lecture 18
CPU Design: The Single-Cycle I

2010-07-21




Instructor Paul Pearce

**Nasty new windows
vulnerability ⇒**

Security researchers have discovered a new Windows vulnerability in the shortcut system of the Windows Shell (Explorer). An exploit already exists such that simply viewing an infected USB drive causes a rootkit to be installed on the victim's system. Here's the fun part: The rootkit is signed by RealTek!



In Review: Generic Steps of Datapath

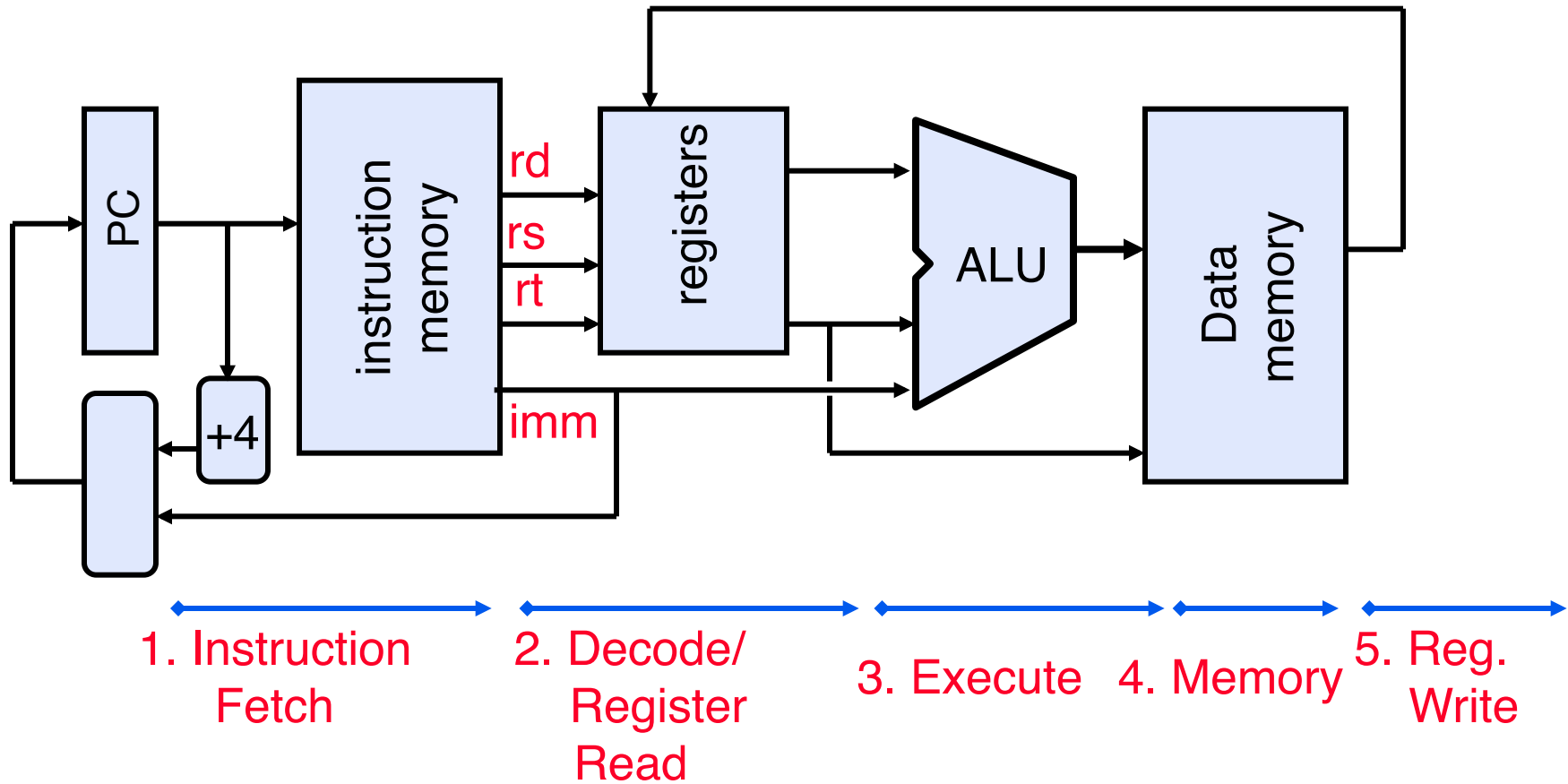


Datapath Walkthroughs (1/3)

- **add** \$3, \$1, \$2 # $R[3] = R[1] + R[2]$
 - **Stage 1: fetch this instruction, inc. PC**
 - **Stage 2: decode to find it's an add, then read registers \$1 and \$2**
 - **Stage 3: add the two values retrieved in Stage 2**
 - **Stage 4: idle (nothing to write to memory)**
 - **Stage 5: write result of Stage 3 into register \$3**



Example: add Instruction

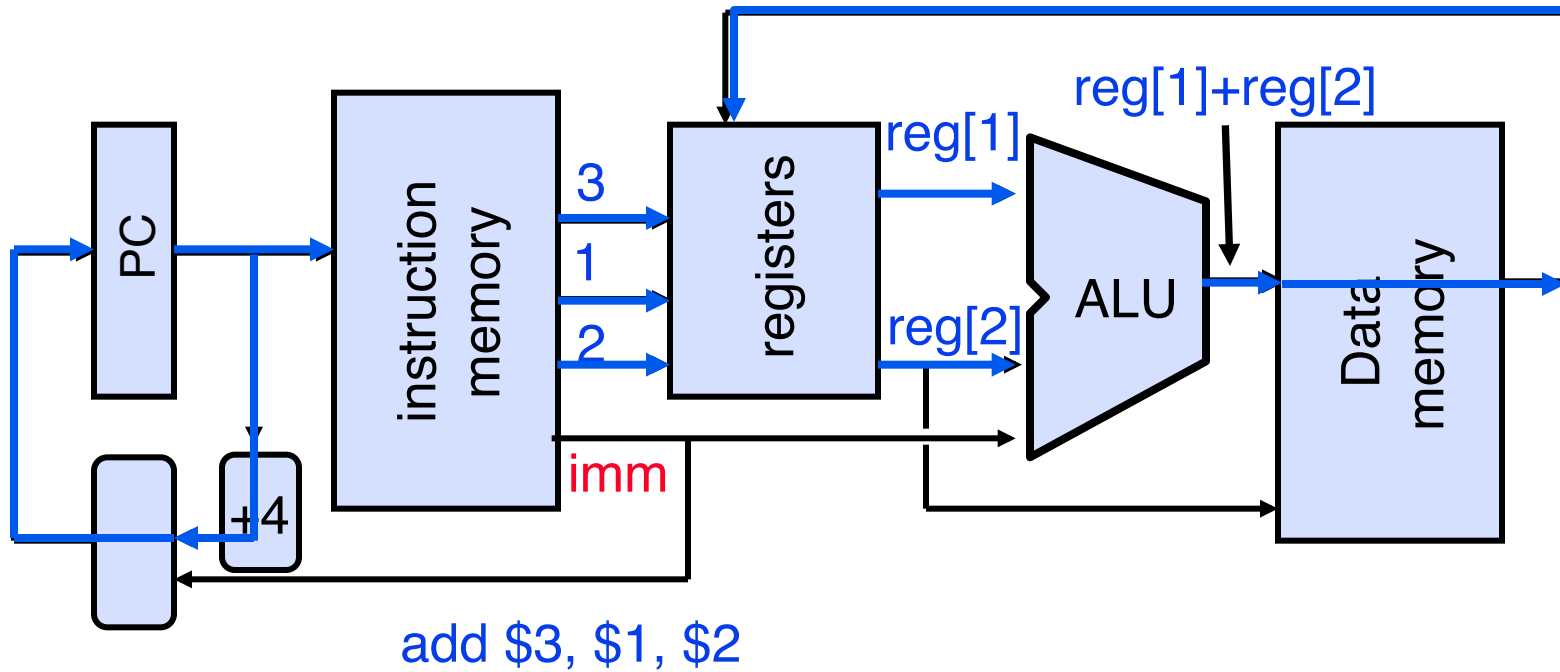


Datapath Walkthroughs (2/3)

- **s1ti \$3, \$1, 17**
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's an s1ti, then read register \$1
 - Stage 3: compare value retrieved in Stage 2 with the integer 17
 - Stage 4: idle
 - Stage 5: write the result of Stage 3 in register \$3



Example: `slti` Instruction

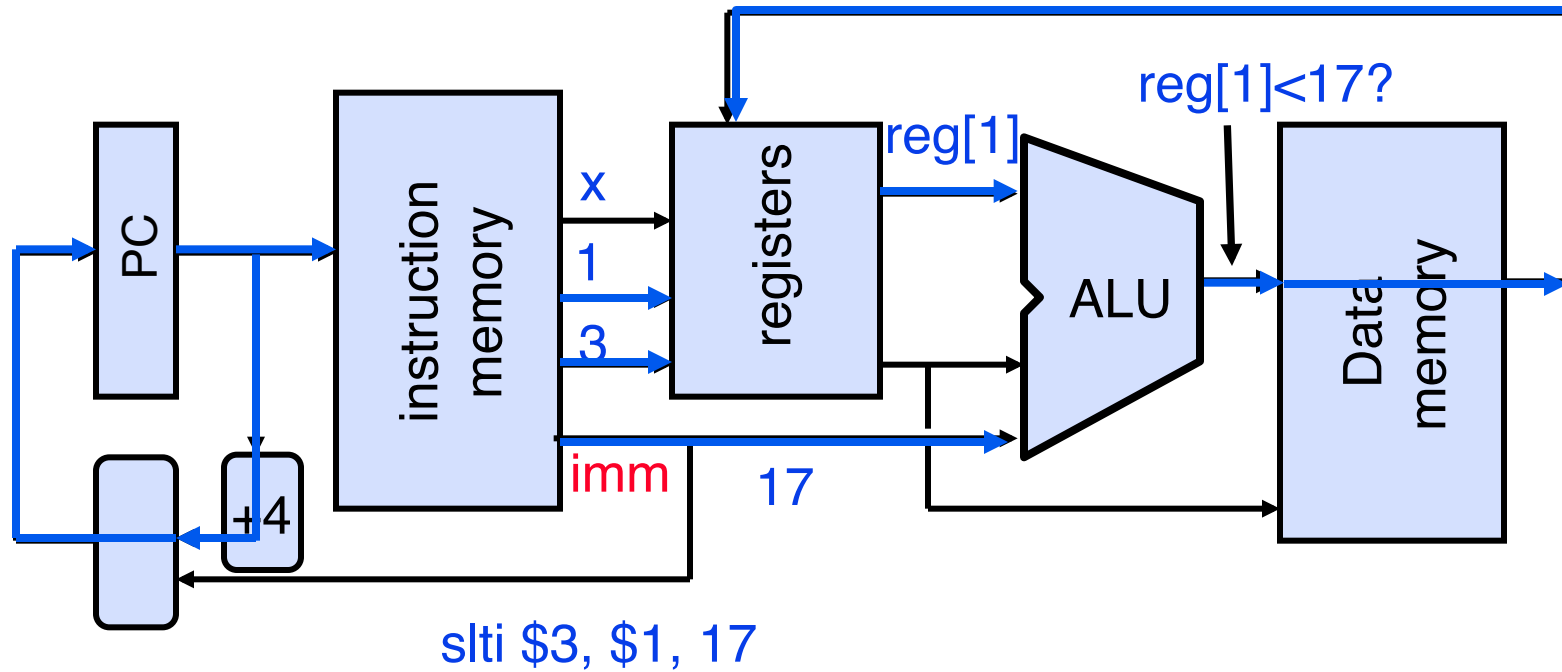


Datapath Walkthroughs (3/3)

- **sw \$3, 17(\$1)**
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's a sw, then read registers \$1 and \$3
 - Stage 3: add 17 to value in register \$1 (retrieved in Stage 2)
 - Stage 4: write value in register \$3 (retrieved in Stage 2) into memory address computed in Stage 3
 - Stage 5: idle (nothing to write into a register)



Example: sw Instruction

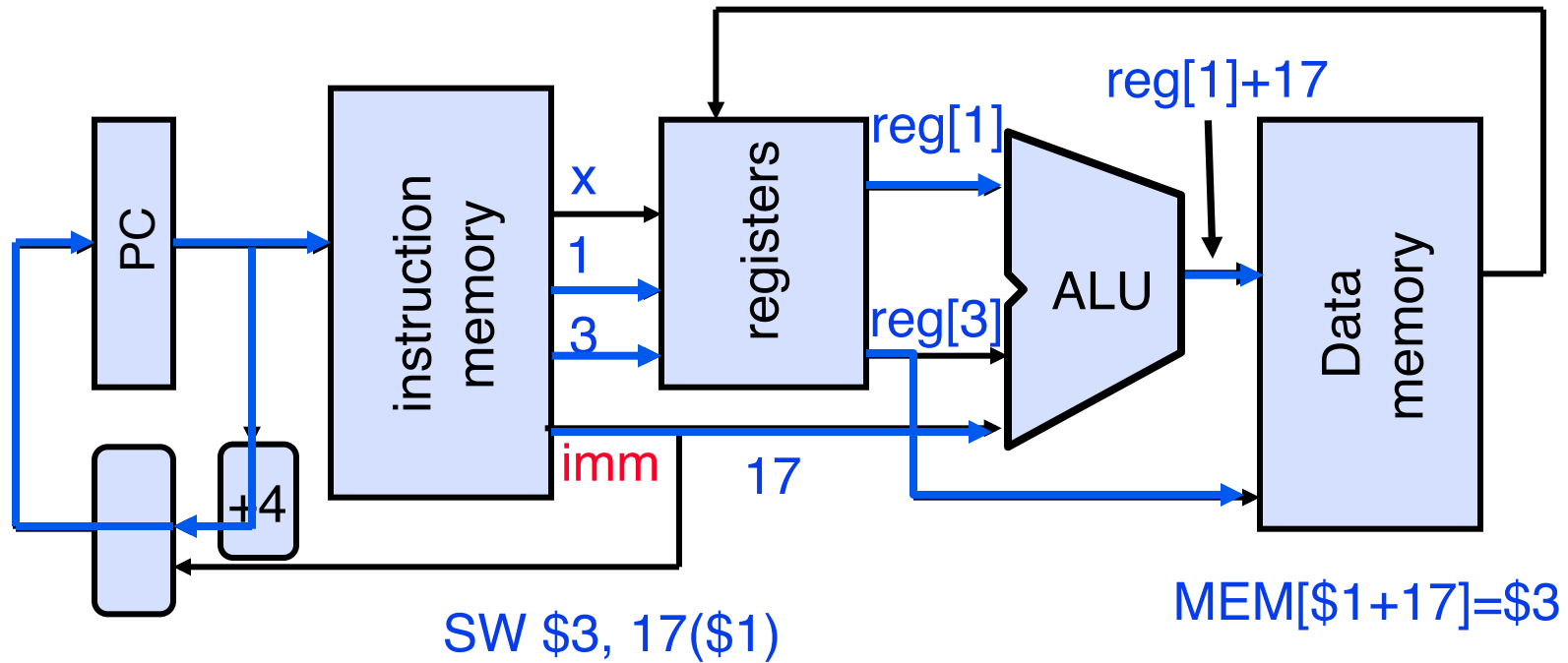

Why Five Stages? (1/2)

- **Could we have a different number of stages?**
 - **Yes, and other architectures do**
- **So why does MIPS have five if instructions tend to idle for at least one stage?**
 - **The five stages are the union of all the operations needed by all the instructions.**
 - **There is one instruction that uses all five stages: the **load****




Why Five Stages? (2/2)

- **lw \$3, 17(\$1)**
 - **Stage 1: fetch this instruction, inc. PC**
 - **Stage 2: decode to find it's a lw, then read register \$1**
 - **Stage 3: add 17 to value in register \$1 (retrieved in Stage 2)**
 - **Stage 4: read value from memory address compute in Stage 3**
 - **Stage 5: write value found in Stage 4 into register \$3**




Example: lw Instruction

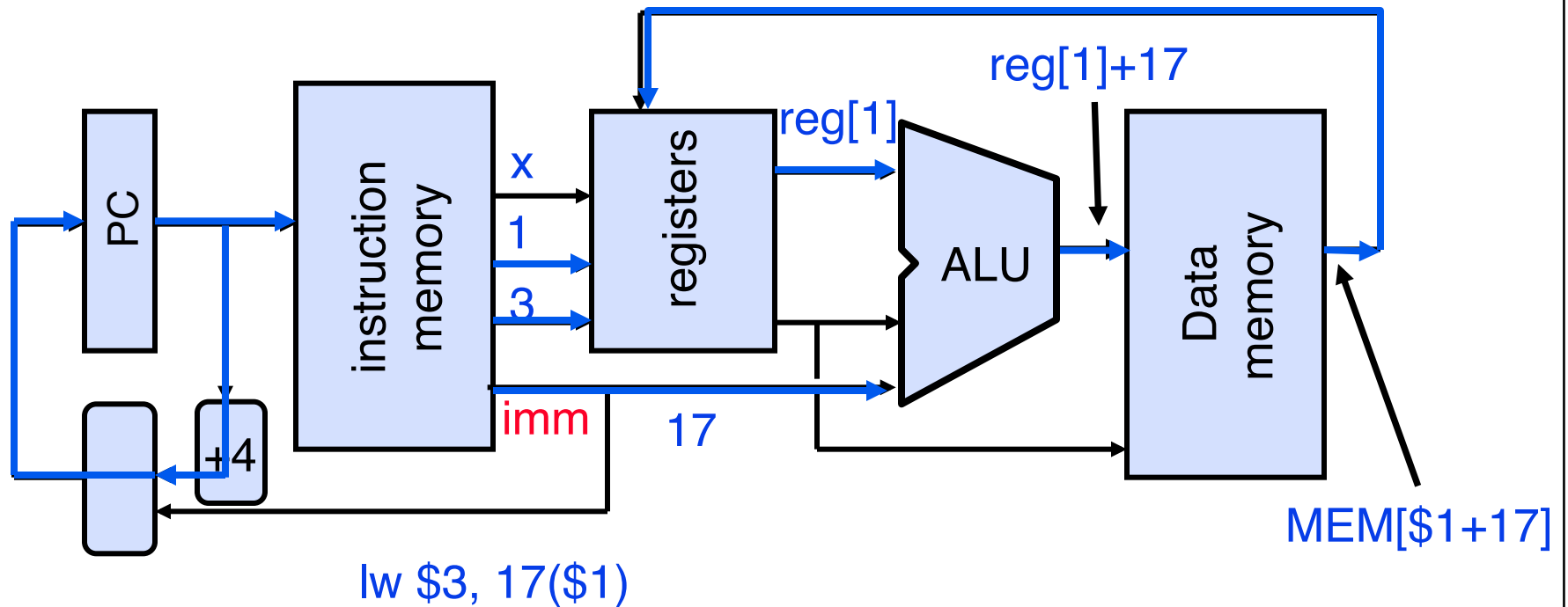

Datapath Summary

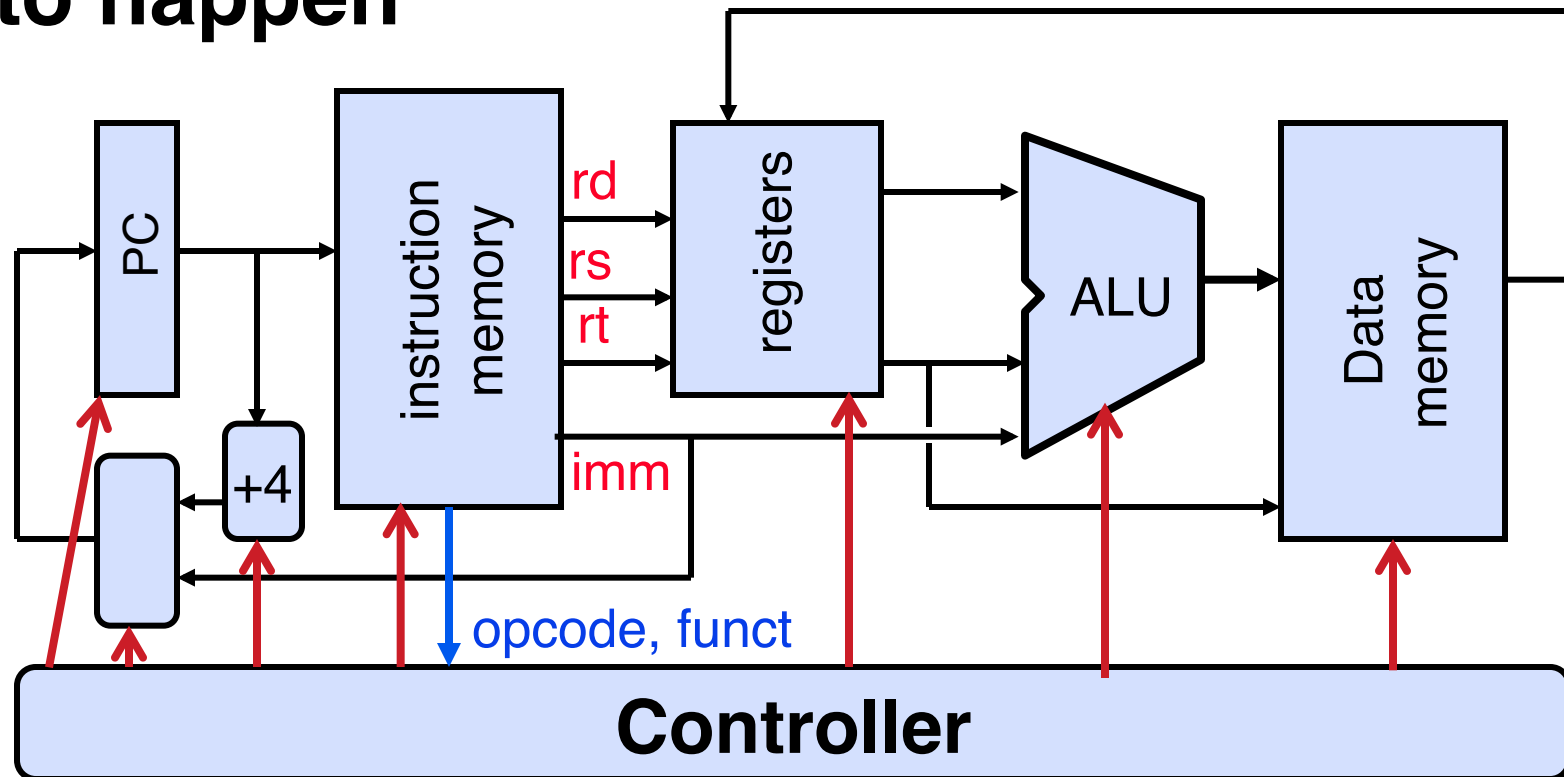- The datapath based on data transfers required to perform instructions
- A controller causes the right transfers to happen



Peer Instruction

- A. If the destination reg is the same as the source reg, we **could compute the incorrect value!**
- B. We're going to be able to read 2 registers and write a 3rd in **1 cycle**

	AB
A:	FF
B:	FT
C:	TF
D:	TT



Administrivia


- **Homework 6 due tonight**
- **Homework 7 due Saturday**
- **Midterm grades are in glookup**
- **Anything else?**



CPU clocking (1/2)

For each instruction, how do we control the flow of information through the datapath?

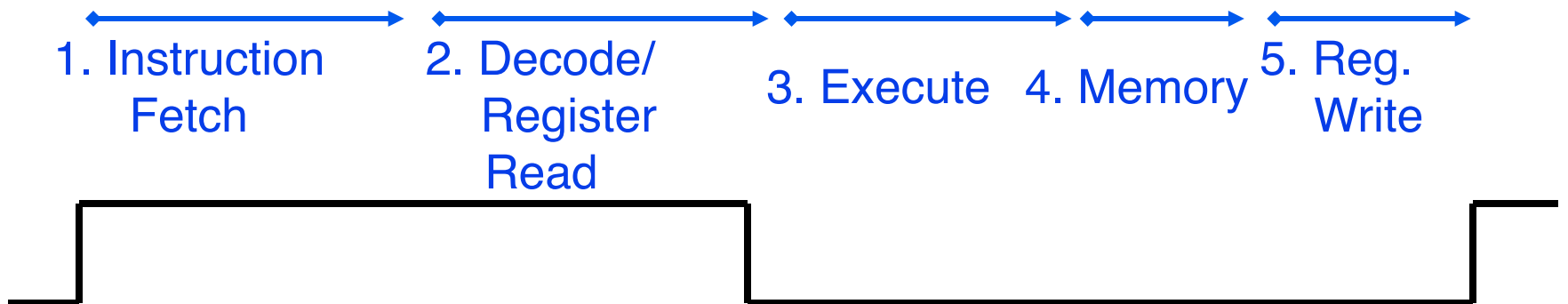
- **Single Cycle CPU: All stages of an instruction are completed within one long clock cycle.**
 - **The clock cycle is made sufficient long to allow each instruction to complete all stages without interruption and within one cycle.**



CPU clocking (2/2)

For each instruction, how do we control the flow of information through the datapath?

 - **Multiple-cycle CPU: Only one stage of instruction per clock cycle.**
 - **The clock is made as long as the **slowest** stage.**



- **Several significant advantages over single cycle execution: Unused stages in a particular instruction can be skipped OR instructions can be pipelined (overlapped).**




How to Design a Processor: step-by-step

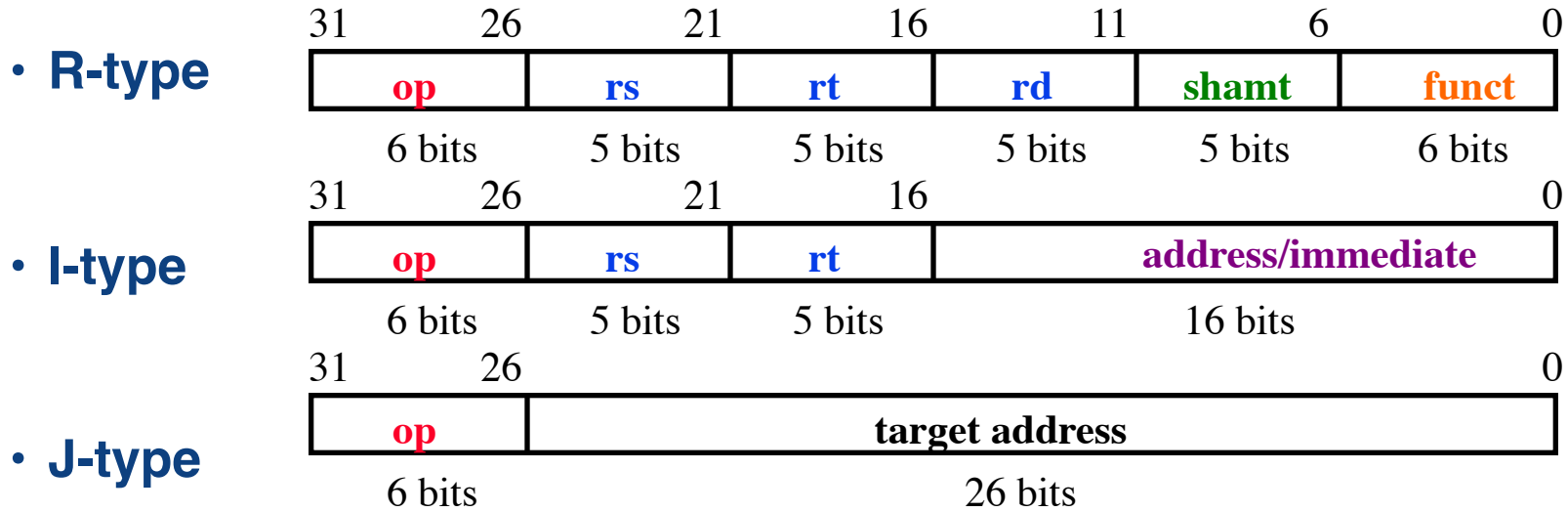- 1. Analyze instruction set architecture (ISA)**
⇒ datapath requirements
 1. meaning of each instruction is given by the **register transfers**
 2. datapath must include storage element for ISA registers
 3. datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology**
- 3. Assemble datapath meeting requirements**
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic



Review: The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:



- The different fields are:
 - **op**: operation (“opcode”) of the instruction
 - **rs, rt, rd**: the source and destination register specifiers
 - **shamt**: shift amount
 - **funct**: selects the variant of the operation in the “op” field
 - **address / immediate**: address offset or immediate value
 - **target address**: target address of jump instruction




Step 1a: The MIPS-lite Subset for today

• ADDU and SUBU


• `addu rd,rs,rt`

• `subu rd,rs,rt`

 

• OR Immediate:


• `ori rt,rs,imm16`

 

• LOAD and STORE Word


• `lw rt,rs,imm16`

• `sw rt,rs,imm16`

 

• BRANCH:

• `beq rs,rt,imm16`

 

Register Transfer Language (RTL)

- RTL gives the meaning of the instructions

$\{op, rs, rt, rd, shamt, funct\} \leftarrow MEM[PC]$

$\{op, rs, rt, Imm16\} \leftarrow MEM[PC]$

- All start by fetching the instruction

inst Register Transfers

ADDU $R[rd] \leftarrow R[rs] + R[rt];$ $PC \leftarrow PC + 4$

SUBU $R[rd] \leftarrow R[rs] - R[rt];$ $PC \leftarrow PC + 4$

ORI $R[rt] \leftarrow R[rs] \mid \text{zero_ext}(Imm16);$ $PC \leftarrow PC + 4$

LOAD $R[rt] \leftarrow MEM[R[rs] + \text{sign_ext}(Imm16)];$ $PC \leftarrow PC + 4$

STORE $MEM[R[rs] + \text{sign_ext}(Imm16)] \leftarrow R[rt];$ $PC \leftarrow PC + 4$

BEQ if ($R[rs] == R[rt]$) then
 $PC \leftarrow PC + 4 + (\text{sign_ext}(Imm16) \parallel 00)$
 else $PC \leftarrow PC + 4$



Step 1: Requirements of the Instruction Set

- **Memory (MEM)**
 - instructions & data (will use one for each)
- **Registers (R: 32 x 32)**
 - read RS
 - read RT
 - Write RT or RD
- **PC**
- **Extender (sign/zero extend)**
- **Add/Sub/OR unit for operation on register(s) or extended immediate**
- **Add 4 (+ maybe extended immediate) to PC**
- **Compare registers?**




Step 2: Components of the Datapath

- **Combinational Elements**
- **Storage Elements**
 - **Clocking methodology**




Combinational Logic Elements (Building Blocks)


- Adder

 

- MUX

 

- ALU

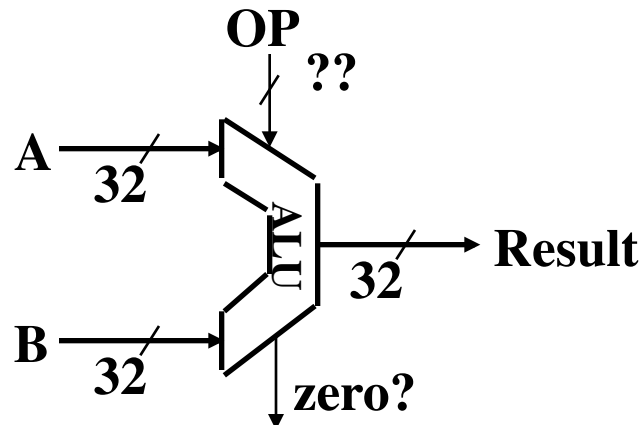

ALU Needs for MIPS-lite + Rest of MIPS

- **Addition, subtraction, logical OR, ==:**

ADDU $R[rd] = R[rs] + R[rt]; \dots$

SUBU $R[rd] = R[rs] - R[rt]; \dots$

ORI $R[rt] = R[rs] | \text{zero_ext}$
(Imm16) \dots

BEQ $\text{if} (R[rs] == R[rt]) \dots$

- **Test to see if output == 0 for any ALU operation gives == test. How?**
- **P&H also adds AND, Set Less Than (1 if $A < B$, 0 otherwise)**
- **ALU taken from chapter 4 (4th edition), chapter 5 (3rd edition)**



What Hardware Is Needed? (1/2)

- **PC: a register which keeps track of memory addr of the next instruction**
- **General Purpose Registers**
 - used in Stages 2 (Read) and 5 (Write)
 - MIPS has 31 of these (plus \$0)
- **Memory**
 - used in Stages 1 (Fetch) and 4 (R/W)
 - cache system makes these two stages as fast as the others, on average



What Hardware Is Needed? (2/2)

- **ALU**

- used in Stage 3
- something that performs all necessary functions: arithmetic, logicals, etc.
- we'll design details later

- **Miscellaneous Registers**

- In implementations with only one stage per clock cycle, registers are inserted between stages to hold intermediate data and control signals as they travel from stage to stage.
- Note: Register is a general purpose term meaning something that stores bits. Not all registers are in the “register file”.




Storage Element: Idealized Memory

- **Memory (idealized)**

- One input bus: **Data In**
- One output bus: **Data Out**

- **Memory word is found by:**

 - **Address selects the word to put on Data Out**
- **Write Enable = 1: address selects the memory word to be written via the Data In bus**



- **Clock input (CLK)**

- **The CLK input is a factor ONLY during write operation**
- **During read operation, behaves as a combinational logic block:**

- **Address valid \Rightarrow Data Out valid after “access time.”**




Storage Element: Register (Building Block)

- **Similar to D Flip Flop except**

- **N-bit input and output**
- **Write Enable input**

- **Write Enable:**

 
- **negated (or deasserted) (0):
Data Out will not change**
- **asserted (1):
Data Out will become Data In on positive
edge of clock**



Storage Element: Register File

- Register File consists of 32 registers:

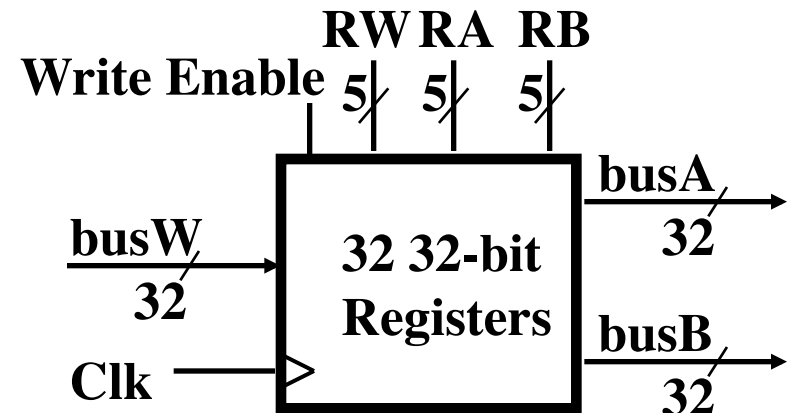- Two 32-bit output busses:
busA and busB
- One 32-bit input bus: busW



- Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- Clock input (clk)

- The clk input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:

- RA or RB valid \Rightarrow busA or busB valid after “access time.”




Step 3: Assemble DataPath meeting requirements

- Register Transfer **Requirements**
⇒ Datapath **Assembly**
- Lets start by analyzing the following Register Transfer Requirements, and build our datapath piece by piece based on those requirements
 - Instruction Fetch
 - add / subtract
 - We'll do the rest next time.




3a: Overview of the Instruction Fetch Unit

 - The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{“something else”}$




3b: Add & Subtract

 - $R[rd] = R[rs] \text{ op } R[rt]$ (`addu rd,rs,rt`)
- **Ra, Rb, and Rw** come from instruction's **Rs, Rt,** and **Rd** fields



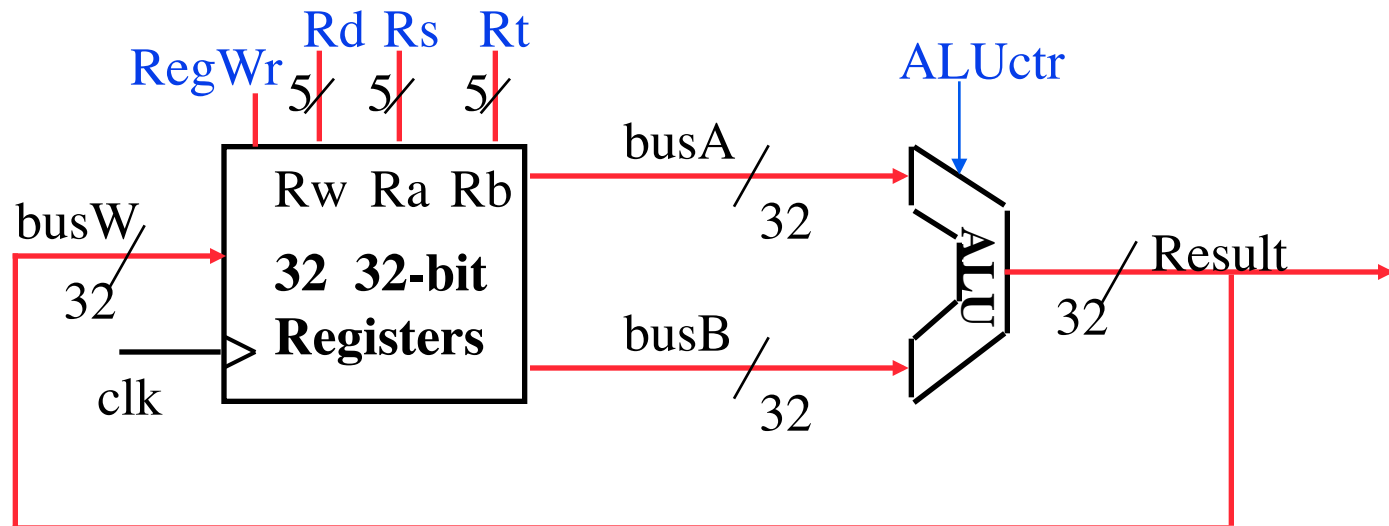- **ALUctr and RegWr: control logic after decoding the instruction**



... Already defined the register file & ALU

Peer Instruction

- 1) We should use the main ALU to compute $PC=PC+4$
- 2) The ALU is inactive for memory reads or writes.
- 3) The ALU is a synchronous device

	123
a)	FFF
b)	FFT
c)	FTF
d)	FTT
e)	TTT



How to Design a Processor: step-by-step

- 1. Analyze instruction set architecture (ISA)**
⇒ datapath requirements
 1. meaning of each instruction is given by the **register transfers**
 2. datapath must include storage element for ISA registers
 3. datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology**
- 3. Assemble datapath meeting requirements**
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic

