

CS61C : Machine Structures

Lecture 20 CPU Design: Control II & Pipelining I

2010-07-26



TA Noah Johnson


AN x64 PROCESSOR IS SCREAMING ALONG AT BILLIONS OF CYCLES PER SECOND TO RUN THE XNU KERNEL, WHICH IS FRANTICALLY WORKING THROUGH ALL THE POSIX-SPECIFIED ABSTRACTION TO CREATE THE DARWIN SYSTEM UNDERLYING OS X, WHICH IN TURN IS STRAINING ITSELF TO RUN FIREFOX AND ITS GECKO RENDERER, WHICH CREATES A FLASH OBJECT WHICH RENDERS DOZENS OF VIDEO FRAMES EVERY SECOND

BECAUSE I WANTED TO SEE A CAT JUMP INTO A BOX AND FALL OVER.




In Review: A Single Cycle Datapath

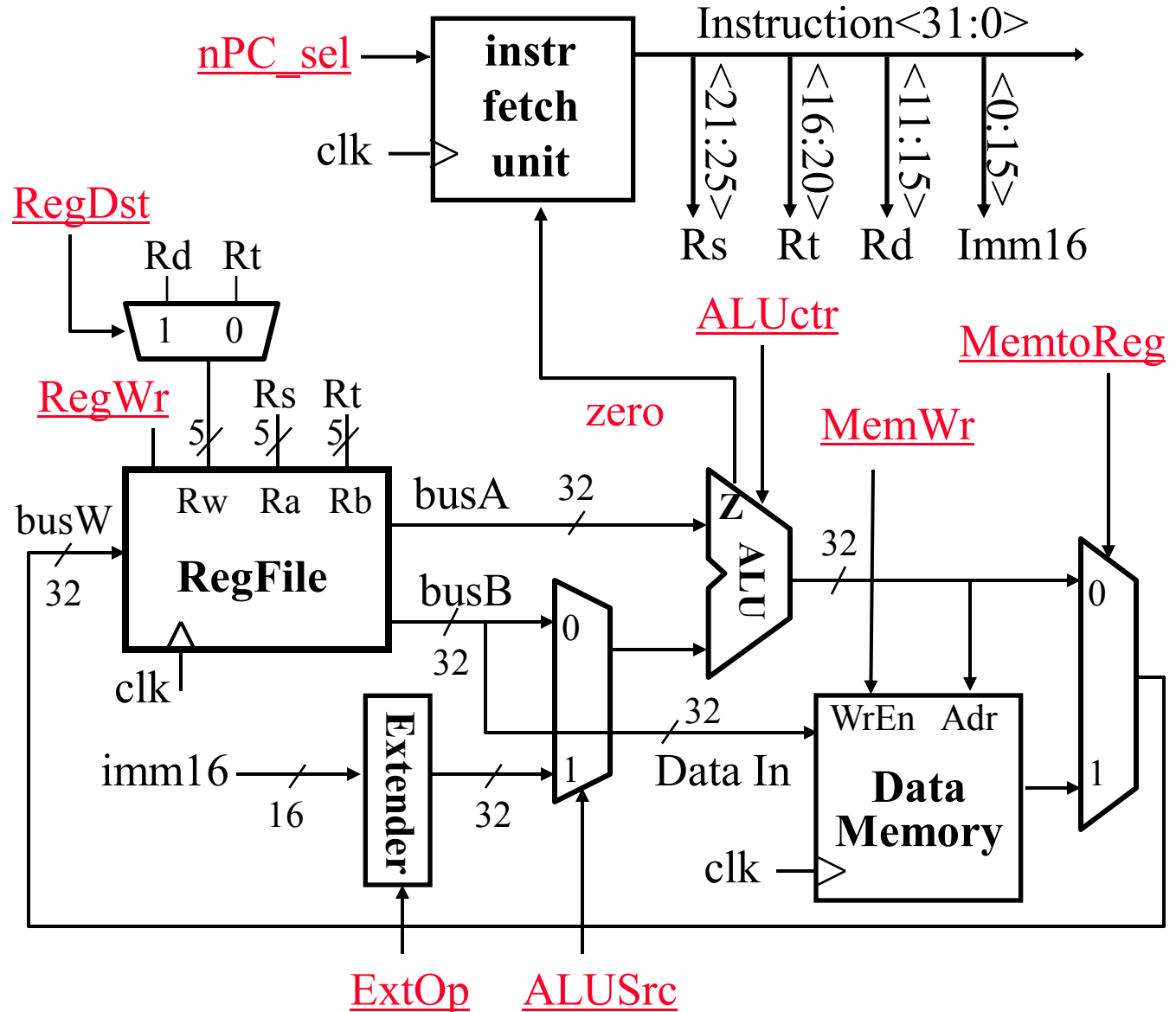- We have everything!
Now we just need to know how to **BUILD CONTROL**




Summary: Single-cycle Processor

- **5 steps to design a processor**
 - 1. Analyze instruction set → datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Assemble datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - **5. Assemble the control logic**
 - **Formulate Logic Equations**
 - **Design Circuits**

 

Step 4: Given Datapath: RTL → Control

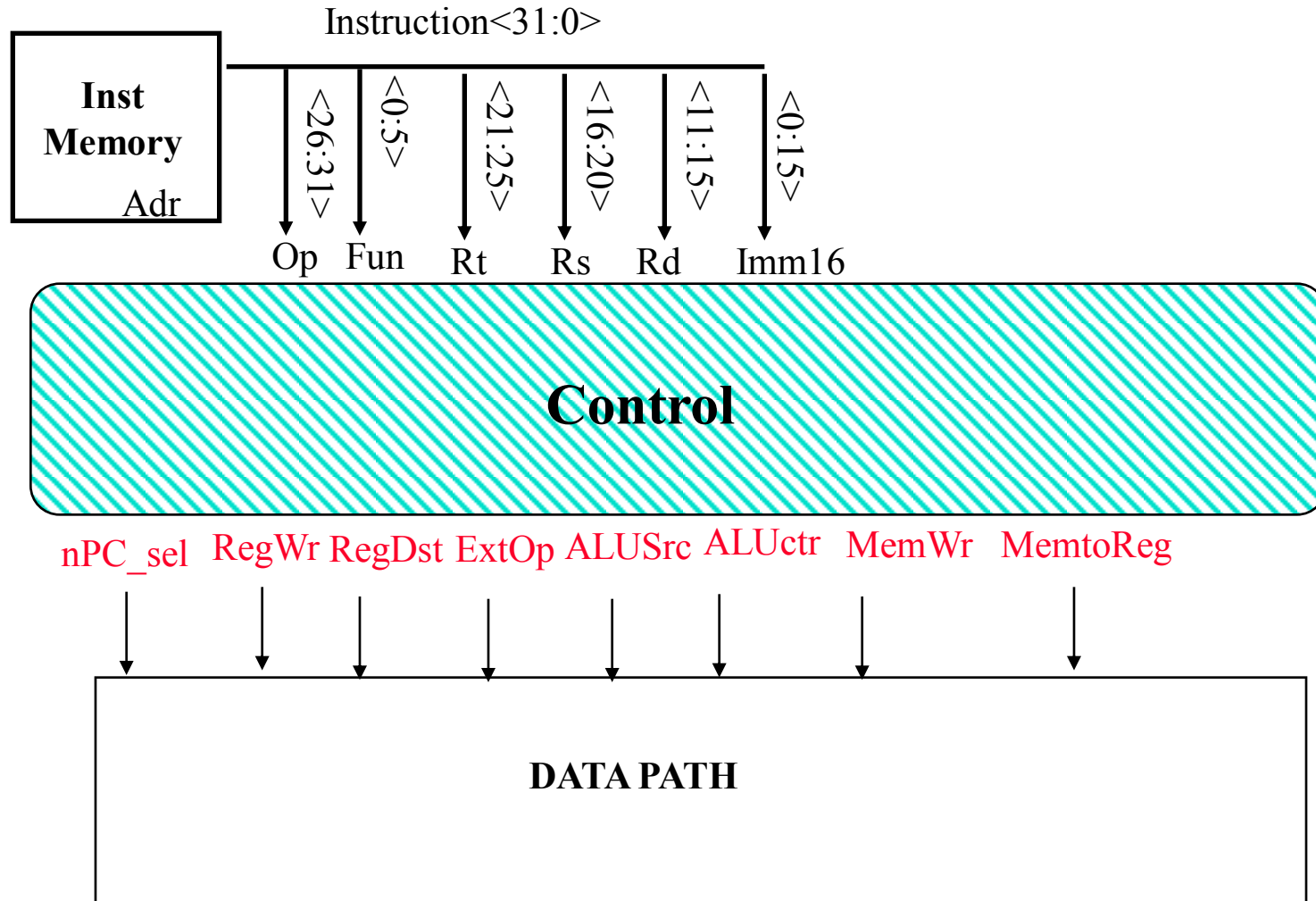

A Summary of the Control Signals (1/2)

inst Register Transfer

add $R[rd] \leftarrow R[rs] + R[rt];$ $PC \leftarrow PC + 4$

ALUSrc = RegB, ALUctr = "ADD", RegDst = rd, RegWr, nPC_sel = "+4"

sub $R[rd] \leftarrow R[rs] - R[rt];$ $PC \leftarrow PC + 4$

ALUSrc = RegB, ALUctr = "SUB", RegDst = rd, RegWr, nPC_sel = "+4"

ori $R[rt] \leftarrow R[rs] + \text{zero_ext}(\text{Imm16});$ $PC \leftarrow PC + 4$

ALUSrc = Im, Extop = "Z", ALUctr = "OR", RegDst = rt, RegWr, nPC_sel = "+4"

lw $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})];$ $PC \leftarrow PC + 4$

ALUSrc = Im, Extop = "sn", ALUctr = "ADD", MemtoReg,

RegDst = rt, RegWr, nPC_sel = "+4"

sw $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rs];$ $PC \leftarrow PC + 4$

ALUSrc = Im, Extop = "sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"

beq $\text{if} (R[rs] == R[rt]) \text{ then } PC \leftarrow PC + \text{sign_ext}(\text{Imm16}) \parallel 00 \text{ else } PC \leftarrow PC + 4$

nPC_sel = "br", ALUctr = "SUB"



A Summary of the Control Signals (2/2)

See Appendix A → **func**
 → **op**

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	?
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	x

	31	26	21	16	11	6	0	
R-type	op		rs	rt	rd	shamt	funct	add, sub
I-type	op		rs	rt	immediate			ori, lw, sw, beq
J-type	op		target address					jump



Boolean Expressions for Controller

RegDst = add + sub

ALUSrc = ori + lw + sw

MemtoReg = lw

RegWrite = add + sub + ori + lw

MemWrite = sw

nPCsel = beq

Jump = jump

ExtOp = lw + sw

ALUctr[0] = sub + beq (assume ALUctr is 00 ADD, 01: SUB, 10: OR)

ALUctr[1] = or

where,

rtype = $\sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet \sim op_1 \bullet \sim op_0$,

ori = $\sim op_5 \bullet \sim op_4 \bullet op_3 \bullet op_2 \bullet \sim op_1 \bullet op_0$

lw = $op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet op_1 \bullet op_0$

sw = $op_5 \bullet \sim op_4 \bullet op_3 \bullet \sim op_2 \bullet op_1 \bullet op_0$

beq = $\sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet op_2 \bullet \sim op_1 \bullet \sim op_0$


jump = $\sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet op_1 \bullet \sim op_0$

add = $rtype \bullet func_5 \bullet \sim func_4 \bullet \sim func_3 \bullet \sim func_2 \bullet \sim func_1 \bullet \sim func_0$


sub = $rtype \bullet func_5 \bullet \sim func_4 \bullet \sim func_3 \bullet \sim func_2 \bullet func_1 \bullet \sim func_0$

How do we
implement this in
gates?

Controller Implementation

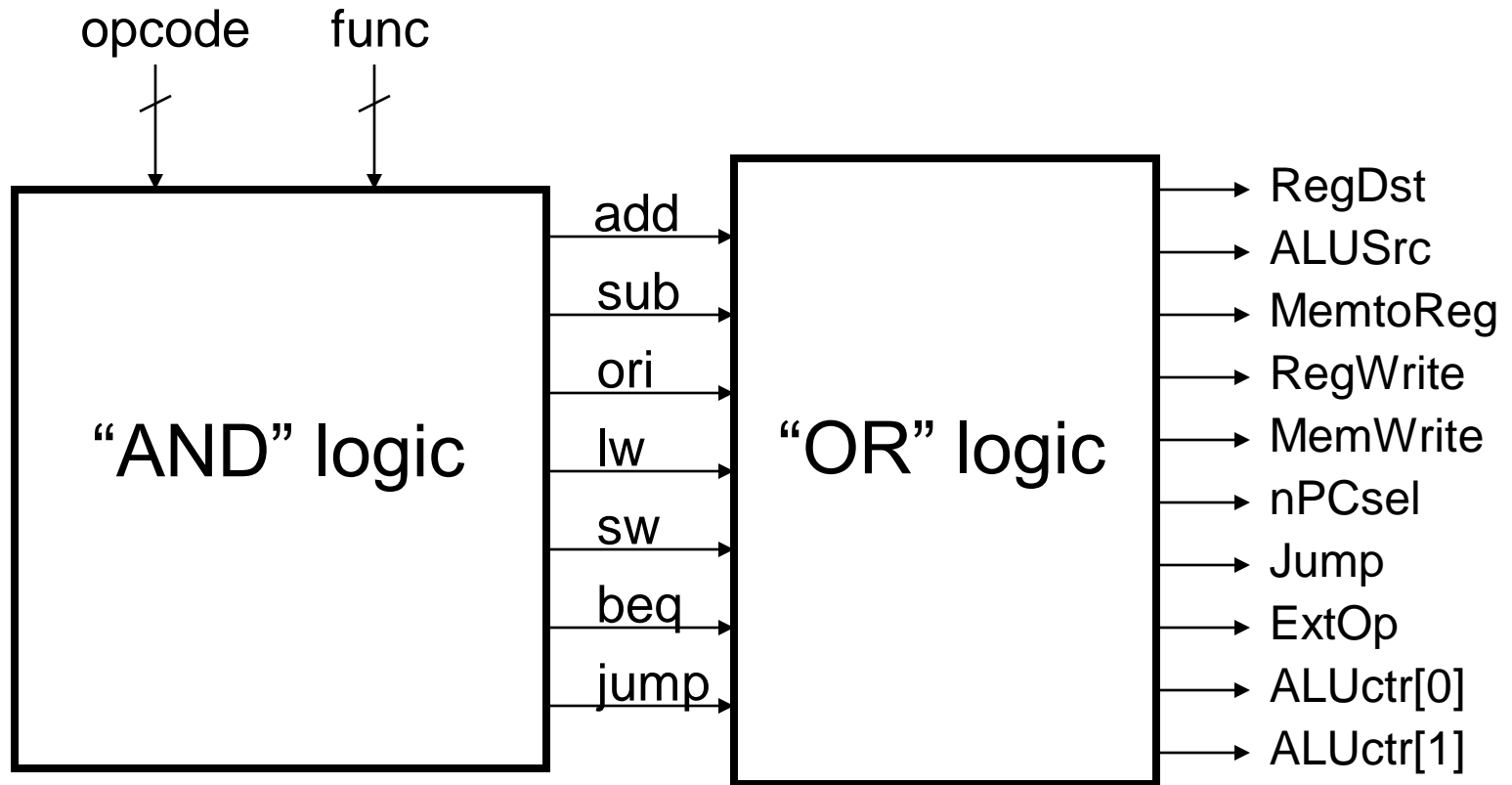

Peer Instruction

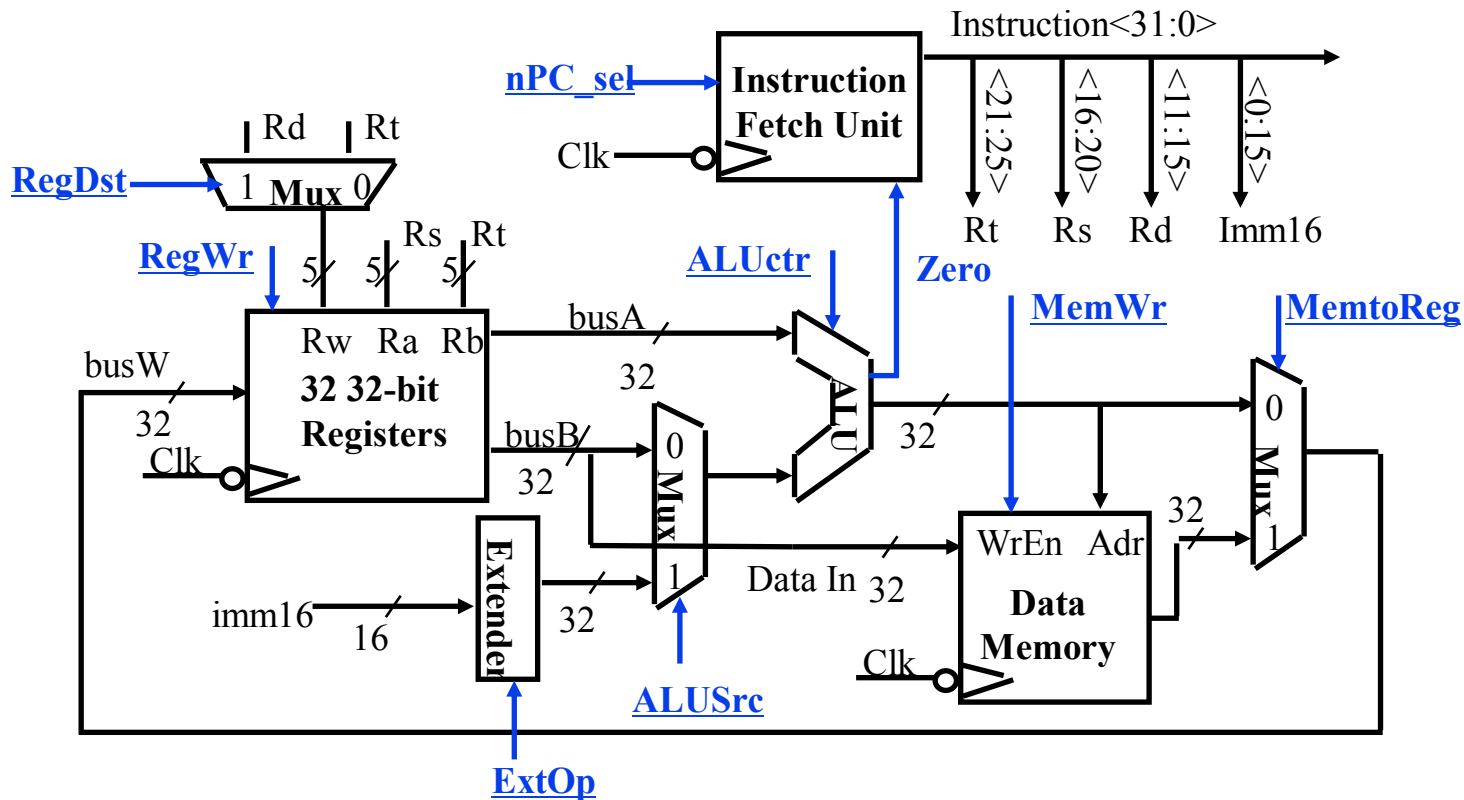


1) MemToReg='x' & ALUctr='sub'.
SUB or BEQ?

2) ALUctr='add'. Which 1 signal is different for all 3 of: ADD, LW, & SW?
RegDst or ExtOp?

- | | |
|----|----|
| | 12 |
| a) | SR |
| b) | SE |
| c) | BR |
| d) | BE |

Summary: Single-cycle Processor

- **5 steps to design a processor**
 - 1. Analyze instruction set → datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Assemble datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - 5. Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits

 

Review: Single cycle datapath


- 5 steps to design a processor

1. Analyze instruction set datapath **requirements**
2. **Select** set of datapath components & establish clock methodology
3. **Assemble** datapath meeting the requirements
4. **Analyze** implementation of each instruction to determine setting of control points that effects the register transfer.
5. **Assemble** the control logic

- **Control** is the hard part


- **MIPS** makes that easier

 - Instructions same size
- Source registers always in same place
- Immediates same size, location
- Operations always on registers/immediates



How We Build The Controller

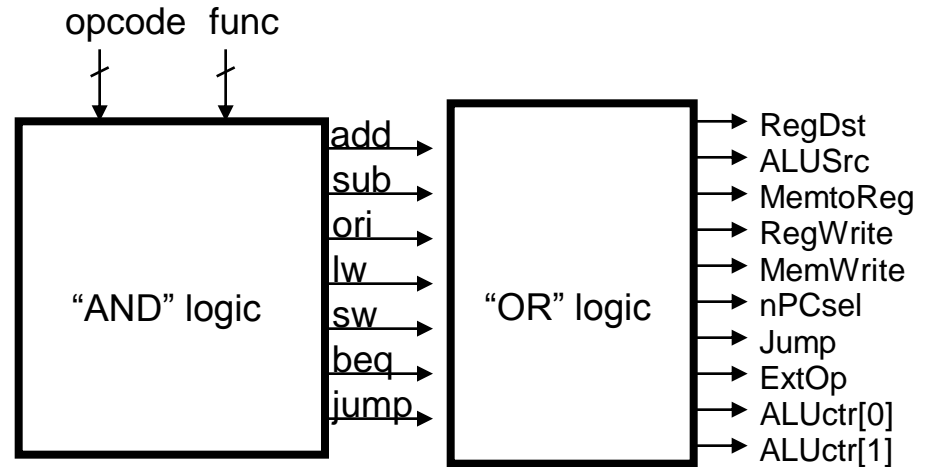RegDst = add + sub
ALUSrc = ori + lw + sw
MemtoReg = lw
RegWrite = add + sub + ori + lw
MemWrite = sw
nPCsel = beq
Jump = jump
ExtOp = lw + sw
ALUctr[0] = sub + beq (assume ALUctr is 0 ADD, 01: SUB, 10: OR)
ALUctr[1] = or



where,

$rtype = \sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet \sim op_1 \bullet \sim op_0$
 $ori = \sim op_5 \bullet \sim op_4 \bullet op_3 \bullet op_2 \bullet \sim op_1 \bullet op_0$
 $lw = op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet op_1 \bullet op_0$
 $sw = op_5 \bullet \sim op_4 \bullet op_3 \bullet \sim op_2 \bullet op_1 \bullet op_0$
 $beq = \sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet op_2 \bullet \sim op_1 \bullet \sim op_0$
 $jump = \sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet op_1 \bullet \sim op_0$

$add = rtype \bullet func_5 \bullet \sim func_4 \bullet \sim func_3 \bullet \sim func_2 \bullet \sim func_1 \bullet \sim func_0$
 $sub = rtype \bullet func_5 \bullet \sim func_4 \bullet \sim func_3 \bullet \sim func_2 \bullet func_1 \bullet \sim func_0$

Omigosh
 omigosh,
 do you know what
 this means?






Processor Performance

- Can we estimate the clock rate (frequency) of our single-cycle processor? We know:
 - 1 cycle per instruction
 - **lw** is the most demanding instruction.
 - Assume these delays for major pieces of the datapath:
 - Instr. Mem, ALU, Data Mem : 2ns each, regfile 1ns
 - Instruction execution requires: $2 + 1 + 2 + 2 + 1 = 8\text{ns}$
 - $\Rightarrow 125\text{ MHz}$
- What can we do to improve clock rate?
- Will this improve performance as well?
 - We want increases in clock rate to result in programs executing quicker.




Gotta Do Laundry

   - Ann, Brian, Cathy, Dave each have one load of clothes to wash, dry, fold, and put away
 - Washer takes 30 minutes
 - Dryer takes 30 minutes
 - “Folder” takes 30 minutes
 - “Stasher” takes 30 minutes to put clothes into drawers




Sequential Laundry

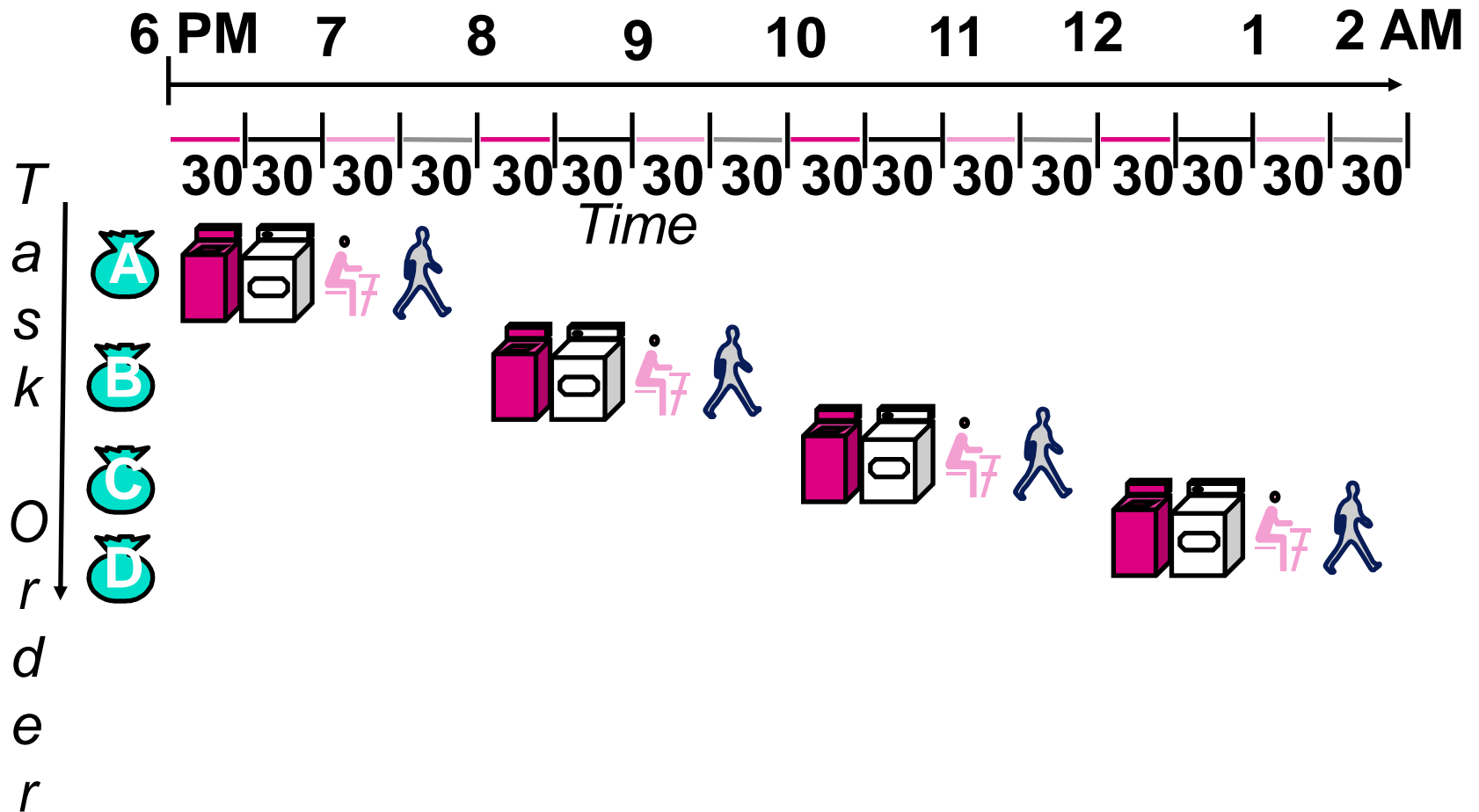

- Sequential laundry takes 8 hours for 4 loads



Pipelined Laundry

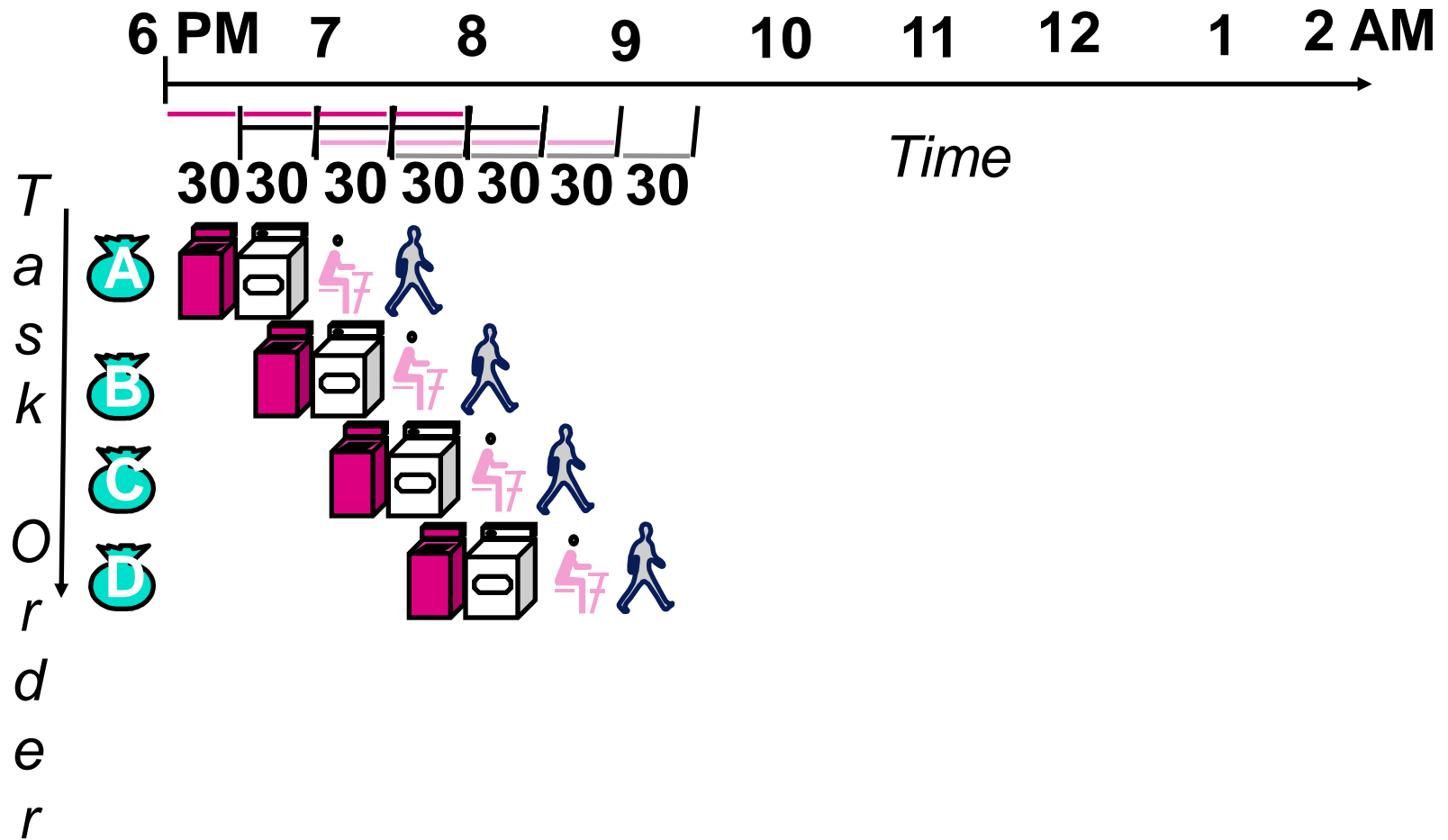

- Pipelined laundry takes 3.5 hours for 4 loads!




General Definitions

- **Latency**: time to completely execute a certain task
 - for example, time to read a sector from disk is disk access time or disk latency
- **Throughput**: amount of work that can be done over a period of time




Pipelining Lessons (1/2)

 

- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- **Multiple** tasks operating simultaneously using different resources
- Potential speedup = **Number pipe stages**
- Time to “**fill**” pipeline and time to “**drain**” it reduces speedup: 2.3X v. 4X in this example

Pipelining Lessons (2/2)

 


- Suppose new Washer takes 20 minutes, new Stasher takes 20 minutes. How much faster is pipeline?
- Pipeline rate limited by **slowest** pipeline stage
- Unbalanced lengths of pipe stages reduces speedup

Steps in Executing MIPS

 - 1) **IFtch**: Instruction Fetch, Increment PC
- 2) **Dcd**: Instruction Decode, Read Registers
- 3) **Exec**:
Mem-ref: Calculate Address
Arith-log: Perform Operation
- 4) **Mem**:
Load: Read Data from Memory
Store: Write Data to Memory
- 5) **WB**: Write Data Back to Register



Pipeline Hazard: Matching socks in later load



- A depends on D; **stall** since folder tied up

Administrivia

- **HW8 due tomorrow**
- **Project 2 due next Monday**
- **Newsgroup problems**
- **Reminder: Midterm regrades due today**




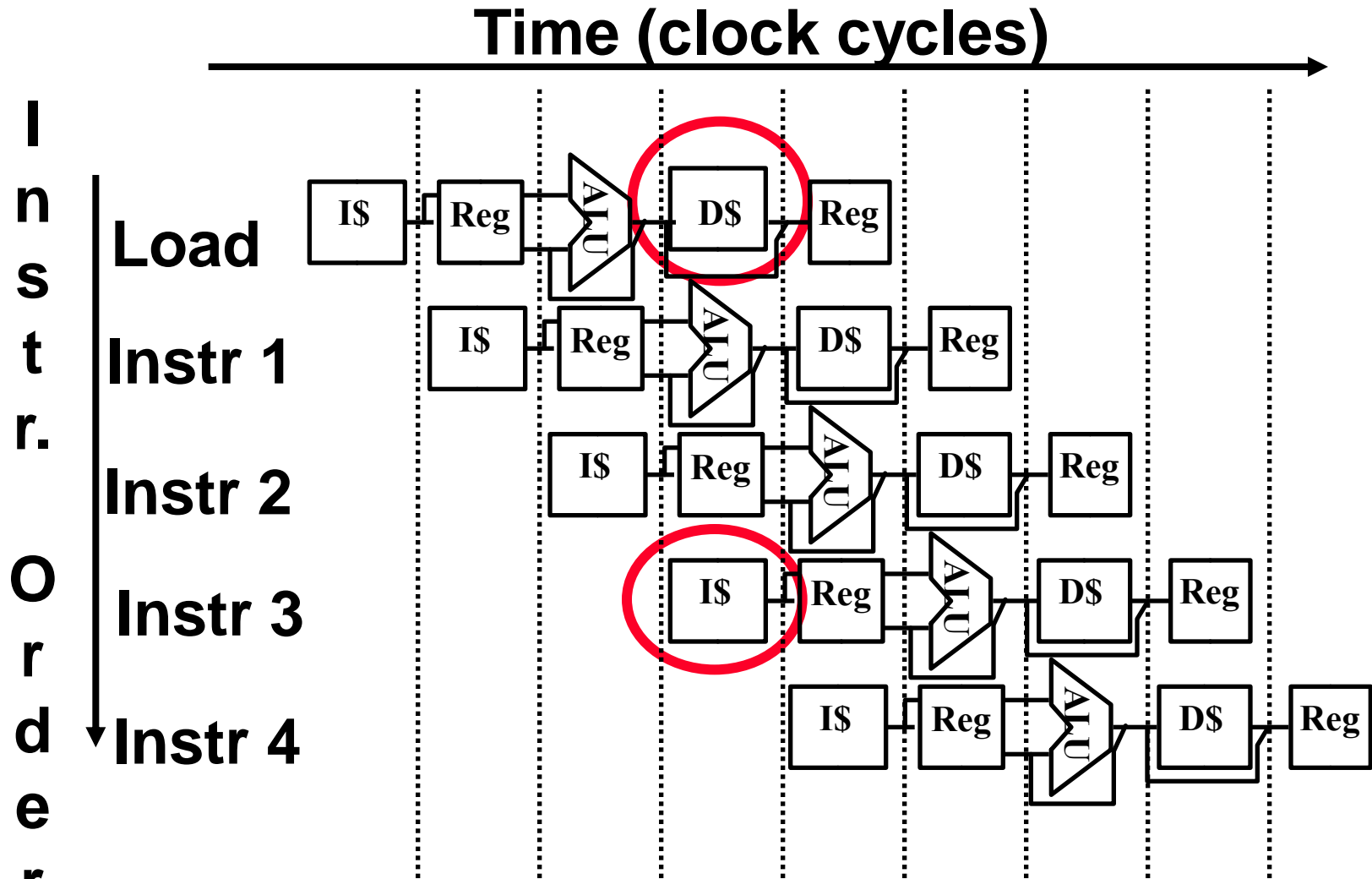Problems for Pipelining CPUs

- Limits to pipelining: **Hazards** prevent next instruction from executing during its designated clock cycle
 - **Structural hazards**: HW cannot support some combination of instructions (single person to fold and put clothes away)
 - **Control hazards**: Pipelining of branches causes later instruction fetches to wait for the result of the branch
 - **Data hazards**: Instruction depends on result of prior instruction still in the pipeline (missing sock)
- These might result in pipeline **stalls** or “**bubbles**” in the pipeline.



Structural Hazard #1: Single Memory (1/2)



Read same memory twice in same clock cycle




Structural Hazard #1: Single Memory (2/2)

- **Solution:**

- **infeasible and inefficient to create second memory**
- (We'll learn about this more next week)
- **so simulate this by having two Level 1 Caches** (a temporary smaller [of usually most recently used] copy of memory)
- **have both an L1 Instruction Cache and an L1 Data Cache**
- **need more complex hardware to control when both caches miss**



Structural Hazard #2: Registers (1/2)

 

Can we read and write to registers simultaneously?

Structural Hazard #2: Registers (2/2)

- **Two different solutions have been used:**
 - 1) **RegFile access is *VERY* fast: takes less than half the time of ALU stage**
 - **Write to Registers during first half of each clock cycle**
 - **Read from Registers during second half of each clock cycle**
 - 2) **Build RegFile with independent read and write ports**
- **Result: can perform Read and Write during same clock cycle**



Peer Instruction

- 1) Thanks to pipelining, I have reduced the time it took me to wash my one shirt.
- 2) Longer pipelines are always a win (since less work per stage & a faster clock).

	12
a)	FF
b)	FT
c)	TF
d)	TT



Things to Remember

- **Optimal Pipeline**

- **Each stage is executing part of an instruction each clock cycle.**
- **One instruction finishes during each clock cycle.**
- **On average, execute far more quickly.**

- **What makes this work?**

- **Similarities between instructions allow us to use same stages for all instructions (generally).**
- **Each stage takes about the same amount of time as all others: little wasted time.**



Bonus slides

- These are extra slides that used to be included in lecture notes, but have been moved to this, the “bonus” area to serve as a supplement.
- The slides will appear in the order they would have in the normal presentation


Bonus



The Single Cycle Datapath during Jump



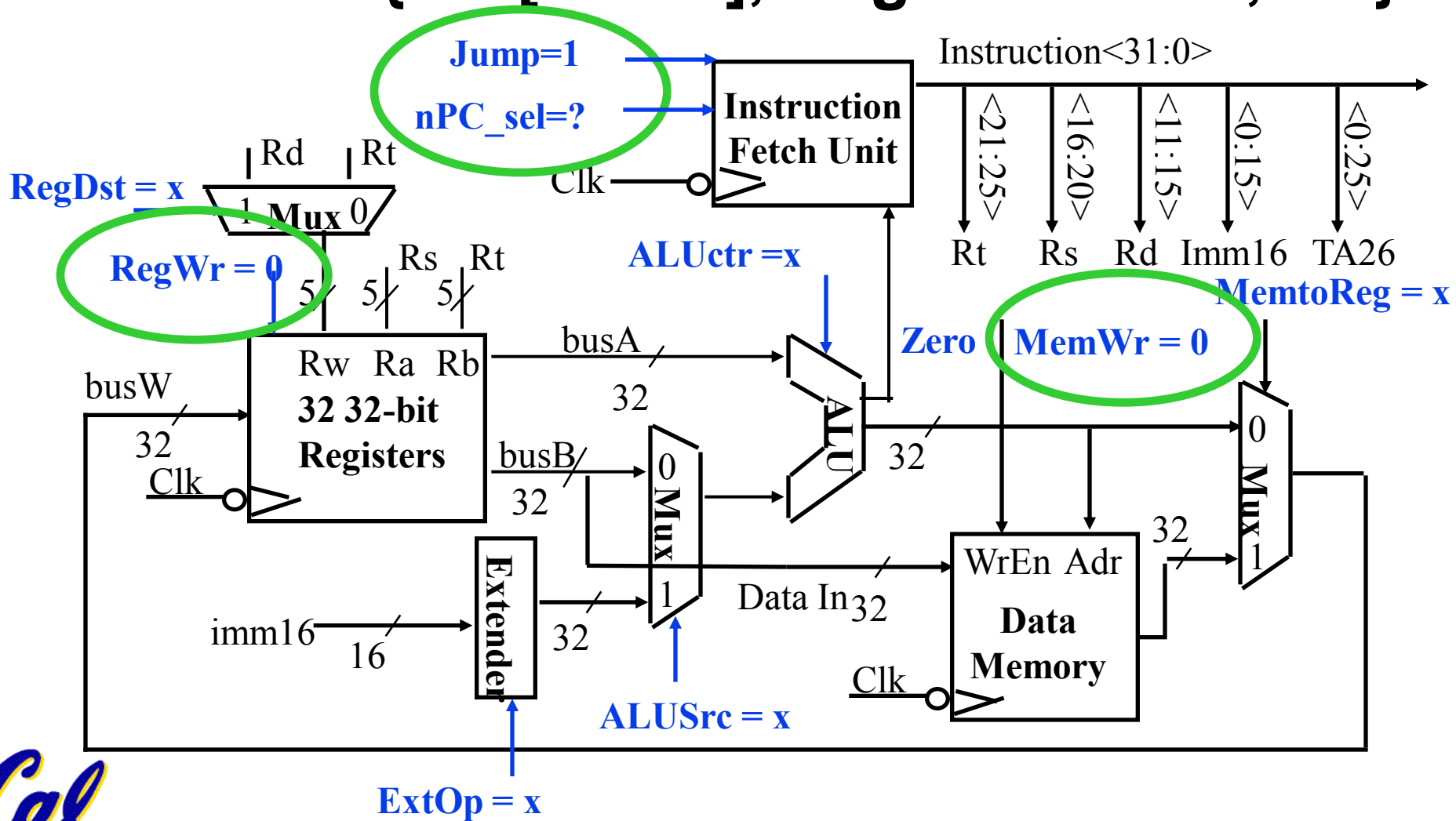
• **New PC = { PC[31..28], target address, 00 }**



Instruction Fetch Unit at the End of Jump



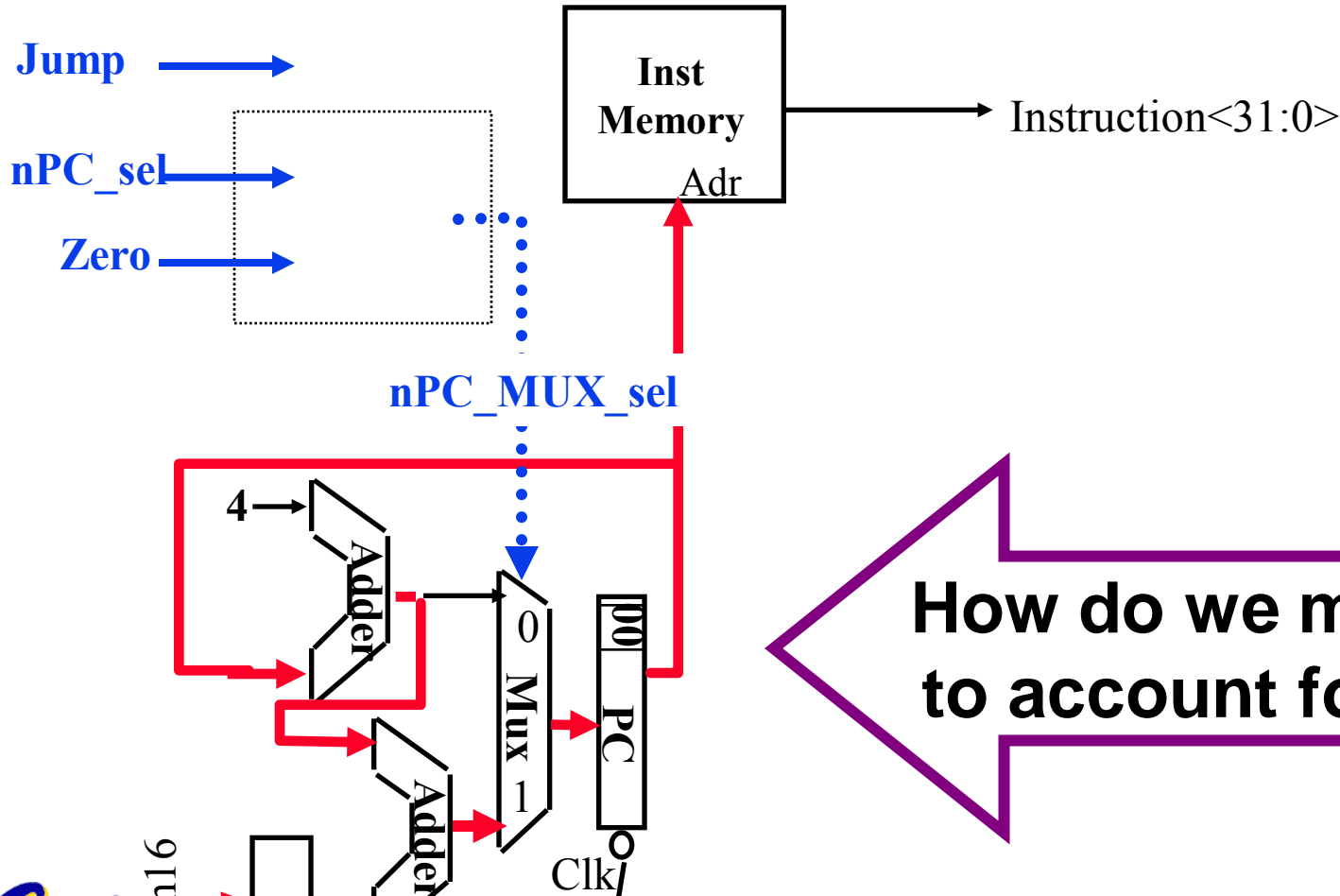• **New PC = { PC[31..28], target address, 00 }**




How do we modify this to account for jumps?

Instruction Fetch Unit at the End of Jump



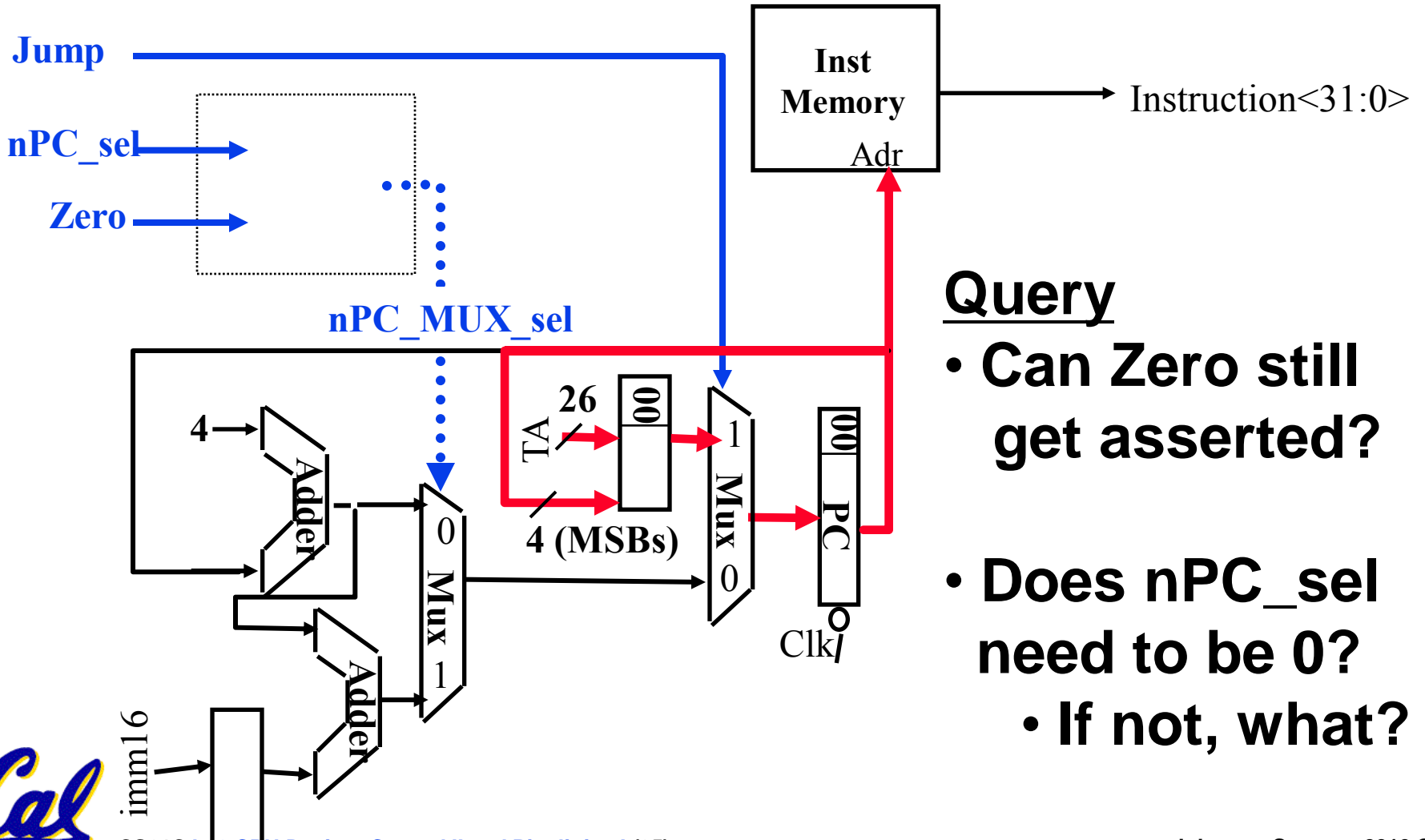• **New PC = { PC[31..28], target address, 00 }**



Query

- Can Zero still get asserted?
- Does nPC_sel need to be 0?
 - If not, what?

