

# CS 61C: Great Ideas in Computer Architecture

## Lecture 11: *Single-Cycle CPU, Datapath & Control Part 1*

Instructor: Sagar Karandikar  
sagark@eecs.berkeley.edu

<http://inst.eecs.berkeley.edu/~cs61c>

# Review

- Timing constraints in SDS
  - Setup time, Hold Time, Clock to Q time
- Use muxes to select among inputs
  - $S$  control bits select from  $2^S$  inputs
  - Each input can be  $n$ -bits wide, independent of  $S$
  - Can implement muxes hierarchically
- ALU can be implemented using a mux
  - Coupled with basic block elements

# How to design Adder/Subtractor?

- Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer

# Adder/Subtractor – One-bit adder LSB...

$$\begin{array}{rcccc} & \mathbf{a_3} & \mathbf{a_2} & \mathbf{a_1} & \mathbf{a_0} \\ + & \mathbf{b_3} & \mathbf{b_2} & \mathbf{b_1} & \mathbf{b_0} \\ \hline \mathbf{s_3} & \mathbf{s_2} & \mathbf{s_1} & \mathbf{s_0} & \end{array}$$

$\mathbf{a_0}$	$\mathbf{b_0}$	$\mathbf{s_0}$	$\mathbf{c_1}$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


$$s_0 =$$

$$c_1 =$$

# Adder/Subtractor – One-bit adder


(1/2) ...  $a_i$   $b_i$   $c_i$  |  $S_i$   $C_{i+1}$


# Adder/Subtractor – One-bit adder (2/2)

 

$$s_i = \text{XOR}(a_i, b_i, c_i)$$
$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$
 
# N 1-bit adders $\Rightarrow$ 1 N-bit adder




**What about overflow?**

**Overflow =  $c_n$ ?**





# Components of a Computer

 

# The CPU

- Processor (CPU): the active part of the computer that does all the work (data manipulation and decision-making)
- Datapath: portion of the processor that contains hardware necessary to perform operations required by the processor (the brawn)
- Control: portion of the processor (also in hardware) that tells the datapath what needs to be done (the brain)

# So...

- Let's build it!
  - Part 1: We'll see what the CPU looks like overall and run some instructions on it
  - Part 2: We'll start from our understanding of MIPS and incrementally add features/blocks to build the whole thing (today/Monday)

# Five Stages of Instruction Execution

- Stage 1: Instruction Fetch
- Stage 2: Instruction Decode
- Stage 3: ALU (Arithmetic-Logic Unit)
- Stage 4: Memory Access
- Stage 5: Register Write

# Stages of Execution (1/5)

- There is a wide variety of MIPS instructions: so what general steps do they have in common?
- Stage 1: Instruction Fetch
  - no matter what the instruction, the 32-bit instruction word must first be fetched from memory (the cache-memory hierarchy)
  - also, this is where we Increment PC (that is,  $PC = PC + 4$ , to point to the next instruction: byte addressing so + 4)

# Stages of Execution (2/5)

- Stage 2: Instruction Decode
  - upon fetching the instruction, we next gather data from the fields (decode all necessary instruction data)
  - first, read the opcode to determine instruction type and field lengths
  - second, read in data from all necessary registers
    - for add, read two registers
    - for addi, read one register
    - for jal, no reads necessary

# Stages of Execution (3/5)

- Stage 3: ALU (Arithmetic-Logic Unit)
  - the real work of most instructions is done here: arithmetic (+, -, \*, /), shifting, logic (&, |), comparisons (slt)
  - what about loads and stores?
    - lw \$t0, 40(\$t1)
    - the address we are accessing in memory = the value in \$t1 PLUS the value 40
    - so we do this addition in this stage

# Stages of Execution (4/5)


- Stage 4: Memory Access
  - actually only the load and store instructions do anything during this stage; the others remain idle during this stage or skip it all together
  - since these instructions have a unique step, we need this extra stage to account for them
  - as a result of the cache system, this stage is expected to be fast



# Stages of Execution (5/5)

- Stage 5: Register Write
  - most instructions write the result of some computation into a register
  - examples: arithmetic, logical, shifts, loads, slt
  - what about stores, branches, jumps?
    - don't write anything into a register at the end
    - these remain idle during this fifth stage or skip it all together

# Stages of Execution on Datapath

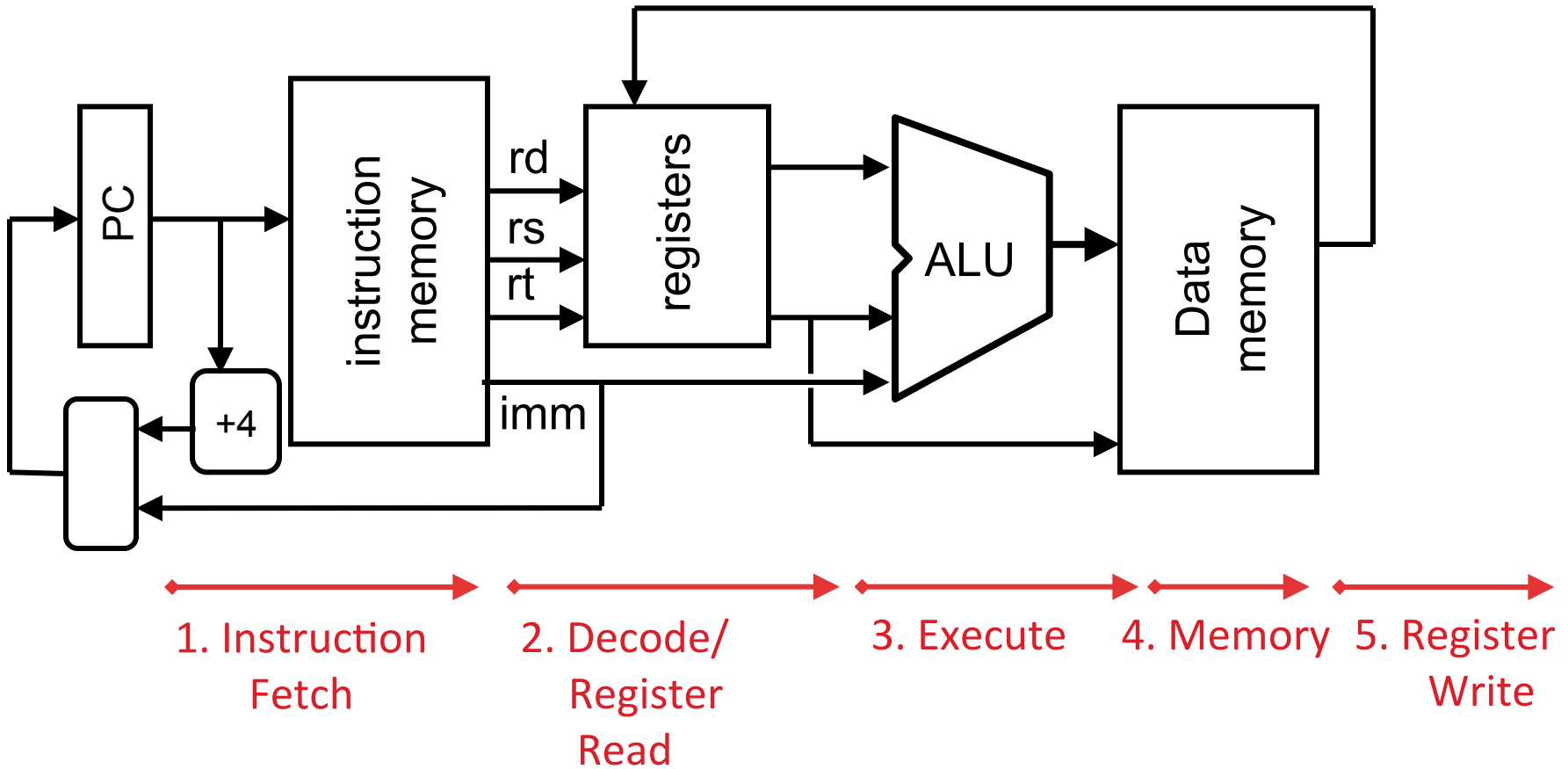

# In the News: BBC reveals design of the Micro Bit

- A “pocket-sized computer” set to be given to every 11- and 12-year old in Year 7 or equivalent in the UK
- Programmable array of LEDs, two buttons, built-in motion sensor
- Add-on power-pack that takes AA batteries for use as a “mobile” device
- USB, bluetooth connectivity



Scaling: Compared to the last BBC machine, the BBC micro (from 1981), the Micro Bit is:

- 18x faster
- 70 times smaller
- 617 times lighter


<http://www.bbc.com/news/technology-33409311>

Break

# Datapath Walkthroughs (1/3)

- `add $r3, $r1, $r2 # r3 = r1+r2`
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is an add, then read registers `$r1` and `$r2`
  - Stage 3: add the two values retrieved in Stage 2
  - Stage 4: idle (nothing to write to memory)
  - Stage 5: write result of Stage 3 into register `$r3`


# Example: add Instruction

 

# Datapath Walkthroughs (2/3)

- `slti $r3, $r1, 17`  
# if (r1 < 17) r3 = 1 else r3 = 0
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is an `slti`, then read register `$r1`
  - Stage 3: compare value retrieved in Stage 2 with the integer 17
  - Stage 4: idle
  - Stage 5: write the result of Stage 3 (1 if reg source was less than signed immediate, 0 otherwise) into register `$r3`

# Example: slti Instruction

 




# Datapath Walkthroughs (3/3)

- `sw $r3, 17($r1) # Mem[r1+17]=r3`
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is a sw, then read registers \$r1 and \$r3
  - Stage 3: add 17 to value in register \$r1 (retrieved in Stage 2) to compute address
  - Stage 4: write value in register \$r3 (retrieved in Stage 2) into memory address computed in Stage 3
  - Stage 5: idle (nothing to write into a register)

# Example: sw Instruction

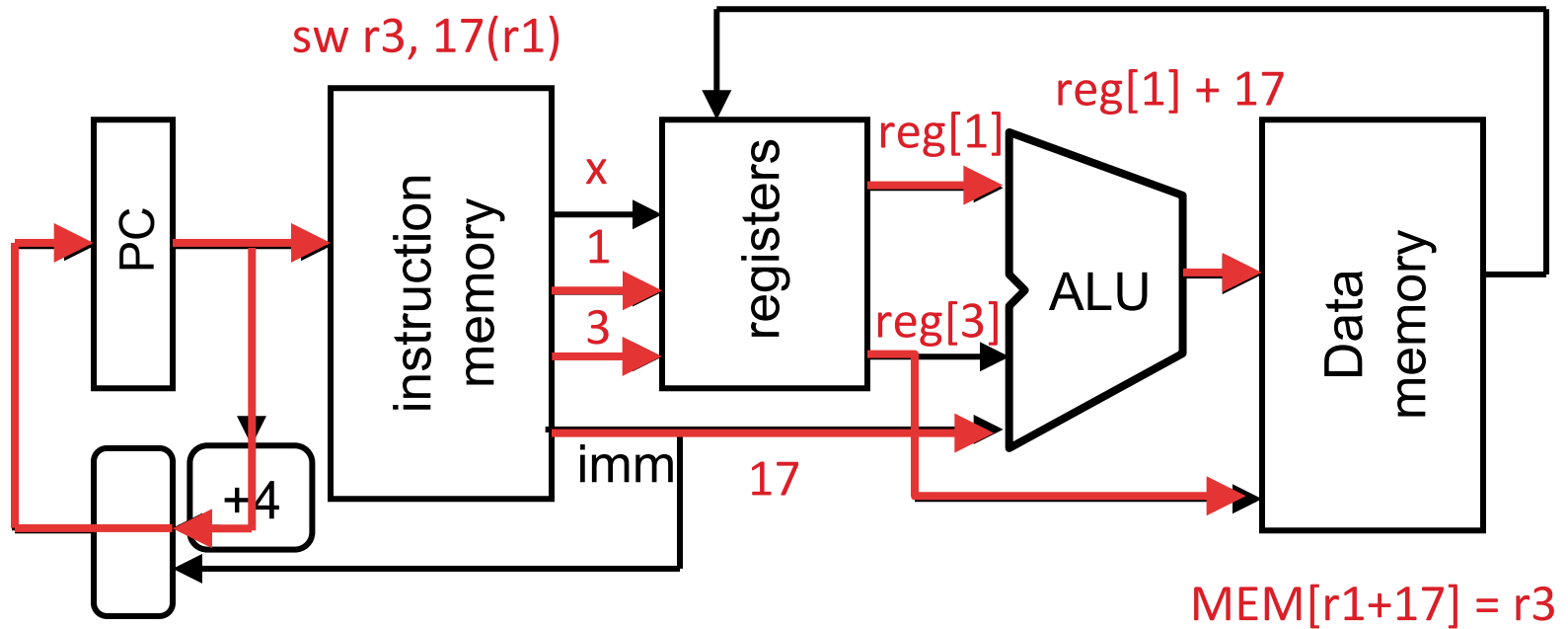


# Why Five Stages? (1/2)

- Could we have a different number of stages?
  - Yes, other ISAs have different natural number of stages
- Why does MIPS have five if instructions tend to idle for at least one stage?
  - Five stages are the union of all the operations needed by all the instructions.
  - One instruction uses all five stages: the load

# Why Five Stages? (2/2)

- `lw $r3, 17($r1) # r3=Mem[r1+17]`
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is a lw, then read register \$r1
  - Stage 3: add 17 to value in register \$r1 (retrieved in Stage 2)
  - Stage 4: read value from memory address computed in Stage 3
  - Stage 5: write value read in Stage 4 into register \$r3

# Example: lw Instruction

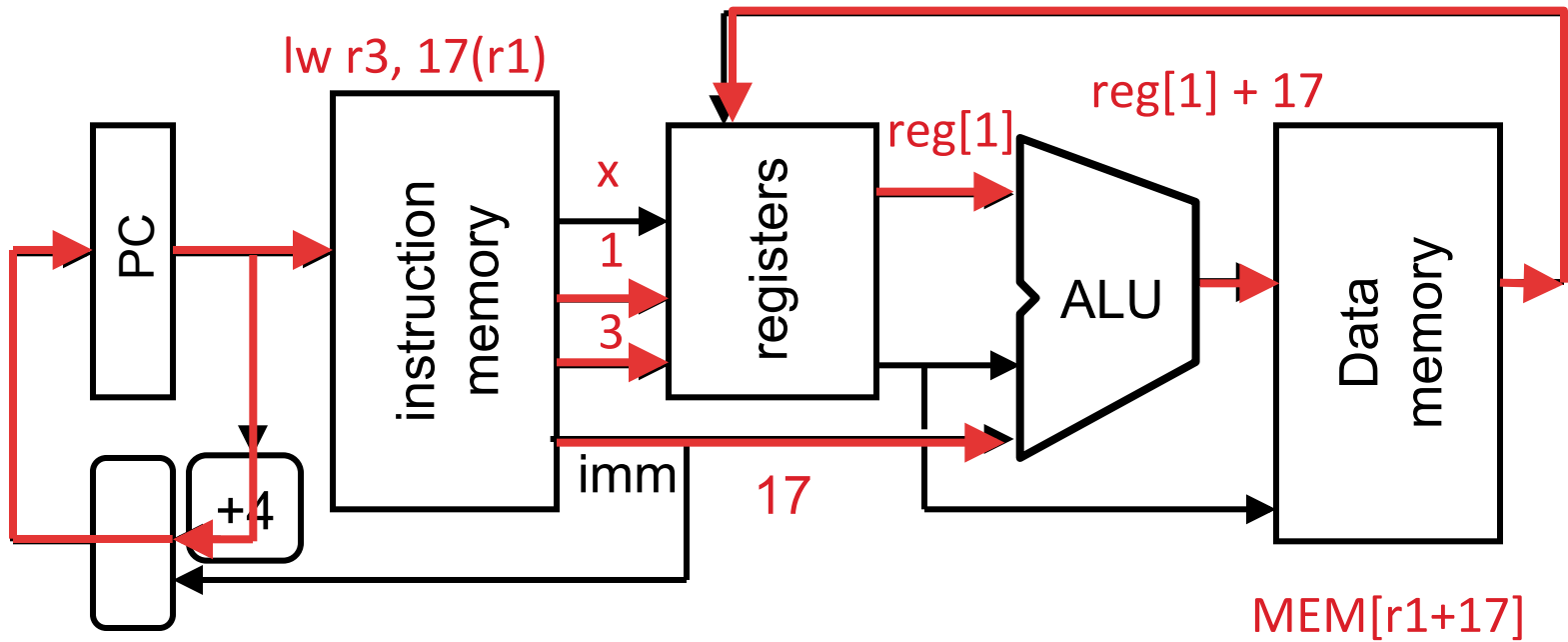

# Clickers/Peer Instruction

- Which type of MIPS instruction is active in the fewest stages?

A: LW

B: BEQ

C: J

D: JAL

E: ADDU

# Administrivia

- HW2 out
  - We recommend doing this before the midterm
- Proj 2-1 out
  - Make sure you test your code on hive machines, that's where we'll grade them
  - Team registration problems? Email Jay

# Administrivia


- Midterm is tomorrow
  - In this room, at this time
  - One double-sided 8.5"x11" handwritten cheatsheet
  - We'll provide a MIPS green sheet
  - No electronics
  - Covers up to and including last lecture (07/02)
  - **Review session slides posted on Piazza**
  - **Get some sleep!**



Break
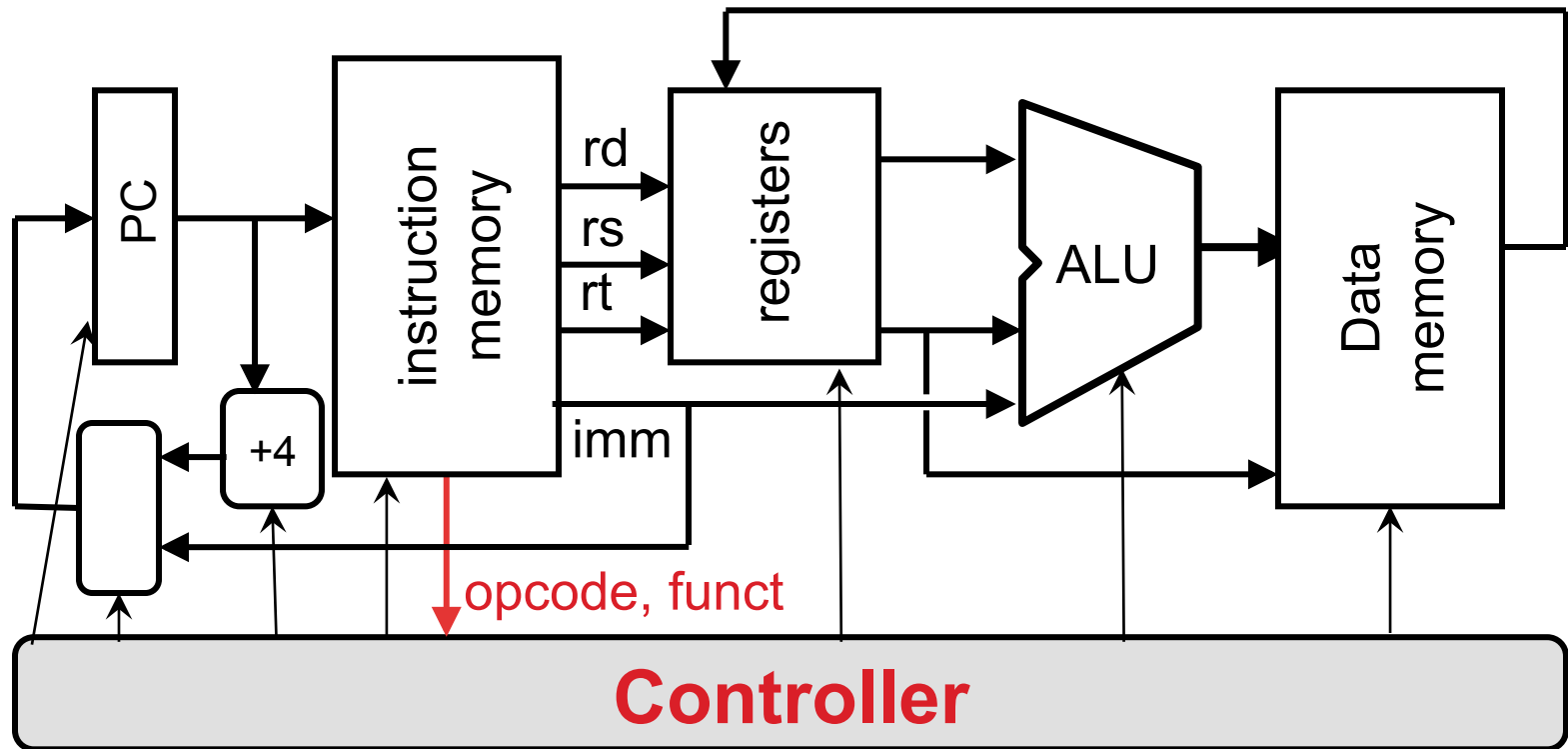
# Datapath and Control

- Datapath designed to support data transfers required by instructions
- Controller causes correct transfers to happen



# Processor Design: 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology


Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic
 
# The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:




- The different fields are:
  - **op**: operation (“opcode”) of the instruction
  - **rs, rt, rd**: the source and destination register specifiers
  - **shamt**: shift amount
  - **funct**: selects the variant of the operation in the “op” field
  - **address / immediate**: address offset or immediate value
  - **target address**: target address of jump instruction

# The MIPS-lite Subset


- ADDU and SUBU

- `addu rd,rs,rt`
- `subu rd,rs,rt`

 


- OR Immediate:

- `ori rt,rs,imm16`

 


- LOAD and STORE Word

- `lw rt,rs,imm16`
- `sw rt,rs,imm16`

 

- BRANCH:

- `beq rs,rt,imm16`

 

# Register Transfer Level (RTL)

- Colloquially called “Register Transfer Language”
- RTL gives the meaning of the instructions
- All start by fetching the instruction itself

```
{op , rs , rt , rd , shamt , funct} ← MEM[ PC ]
```

```
{op , rs , rt , Imm16} ← MEM[ PC ]
```

## Inst    Register Transfers

```
ADDU    R[rd] ← R[rs] + R[rt]; PC ← PC + 4
```

```
SUBU    R[rd] ← R[rs] - R[rt]; PC ← PC + 4
```

```
ORI     R[rt] ← R[rs] | zero_ext(Imm16); PC ← PC + 4
```

```
LOAD    R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
```

```
STORE   MEM[ R[rs] + sign_ext(Imm16) ] ← R[rt]; PC ← PC + 4
```

```
BEQ     if ( R[rs] == R[rt] )  
          PC ← PC + 4 + {sign_ext(Imm16), 2'b00}  
else PC ← PC + 4
```

# Real-World RTL

GitHub, Inc. [US] [https://github.com/ucb-bar/rocket/tree/master/...](https://github.com/ucb-bar/rocket/tree/master/)


ucb-bar / rocket Unwatch

branch: master rocket / src / main / scala / +

Merge pull request #10 from wsong83/fix

hcook authored 2 days ago

<a href="#">arbiter.scala</a>	Use HeaderlessTileLinkIO
<a href="#">btb.scala</a>	Rename some params, use refactored TileLink
<a href="#">consts.scala</a>	Renamed PCR to CSR
<a href="#">core.scala</a>	Clean up handling of icache's io.cpu.npc signal
<a href="#">csr.scala</a>	New machine-mode timer facility
<a href="#">ctrl.scala</a>	Update to privileged architecture 1.7
<a href="#">decode.scala</a>	fix decodelogic bug for bitwidths $\geq 64$ s/1L/BigInt(1)/
<a href="#">dpath.scala</a>	Fix an apparently benign PC sign-extension bug
<a href="#">dpath_alu.scala</a>	Rename some params, use refactored TileLink
<a href="#">fpu.scala</a>	Integrate divide/sqrt unit
<a href="#">icache.scala</a>	Clean up handling of icache's io.cpu.npc signal
<a href="#">instructions.scala</a>	New machine-mode timer facility
<a href="#">multiplier.scala</a>	Rename some params, use refactored TileLink
<a href="#">nbdcache.scala</a>	code clean in dcache, no need to check the condition twice.
<a href="#">package.scala</a>	Update to privileged architecture 1.7
<a href="#">ptw.scala</a>	Update to privileged architecture 1.7
<a href="#">rocc.scala</a>	HeaderlessTileLinkIO -> ClientTileLinkIO
<a href="#">tile.scala</a>	HeaderlessTileLinkIO -> ClientTileLinkIO
<a href="#">tlb.scala</a>	Update to privileged architecture 1.7
<a href="#">util.scala</a>	Update to privileged architecture 1.7

 




# Step 1: Requirements of the Instruction Set

- Memory (MEM)
  - Instructions & data (will use one for each)
- Registers (R: 32, 32-bit wide registers)
  - Read RS
  - Read RT
  - Write RT or RD
- Program Counter (PC)
- Extender (sign/zero extend)
- Add/Sub/OR/etc unit for operation on register(s) or extended immediate (ALU)
- Add 4 (+ maybe extended immediate) to PC
- Compare registers?


   
# Step 2: Components of the Datapath

- Combinational Elements
- Storage Elements + Clocking Methodology
- Building Blocks



# ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:

```
ADDU  R[rd] = R[rs] + R[rt]; ...
```

```
SUBU  R[rd] = R[rs] - R[rt]; ...
```


```
ORI   R[rt] = R[rs] | zero_ext(Imm16)...
```

```
BEQ   if ( R[rs] == R[rt] )...
```

- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND, Set Less Than (1 if  $A < B$ , 0 otherwise)
- ALU follows Chapter 5

 
# Storage Element: Idealized Memory

- “Magic” Memory
  - One input bus: Data In
  - One output bus: Data Out
- Memory word is found by:
  - For Read: Address selects the word to put on Data Out
  - For Write: Set Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
  - CLK input is a factor ONLY during write operation
  - During read operation, behaves as a combinational logic block: Address valid  $\Rightarrow$  Data Out valid after “access time”



 
# Storage Element: Register (Building Block)

- Similar to D Flip Flop except
  - N-bit input and output
  - Write Enable input
- Write Enable:
  - Negated (or deasserted) (0): Data Out will not change
  - Asserted (1): Data Out will become Data In on positive edge of clock



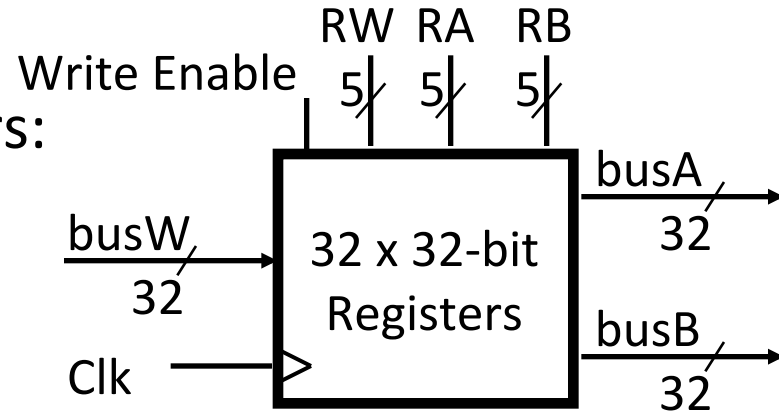
# Storage Element: Register File

- Register File consists of 32 registers:
  - Two 32-bit output busses: busA and busB
  - One 32-bit input bus: busW
- Register is selected by:
  - RA (number) selects the register to put on busA (data)
  - RB (number) selects the register to put on busB (data)
  - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- Clock input (clk)
  - Clk input is a factor ONLY during write operation
  - During read operation, behaves as a combinational logic block:
    - RA or RB valid  $\Rightarrow$  busA or busB valid after “access time.”



 
# Step 3a: Instruction Fetch Unit

- Register Transfer Requirements  $\Rightarrow$  Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation
- Common RTL operations
  - Fetch the Instruction:  
 $\text{mem}[\text{PC}]$
  - Update the program counter:
    - Sequential Code:  
 $\text{PC} \leftarrow \text{PC} + 4$
    - Branch and Jump:  
 $\text{PC} \leftarrow \text{“something else”}$



 
# Step 3b: Add & Subtract

- $R[rd] = R[rs] \text{ op } R[rt]$  (`addu rd,rs,rt`)
  - Ra, Rb, and Rw come from instruction's Rs, Rt, and Rd fields




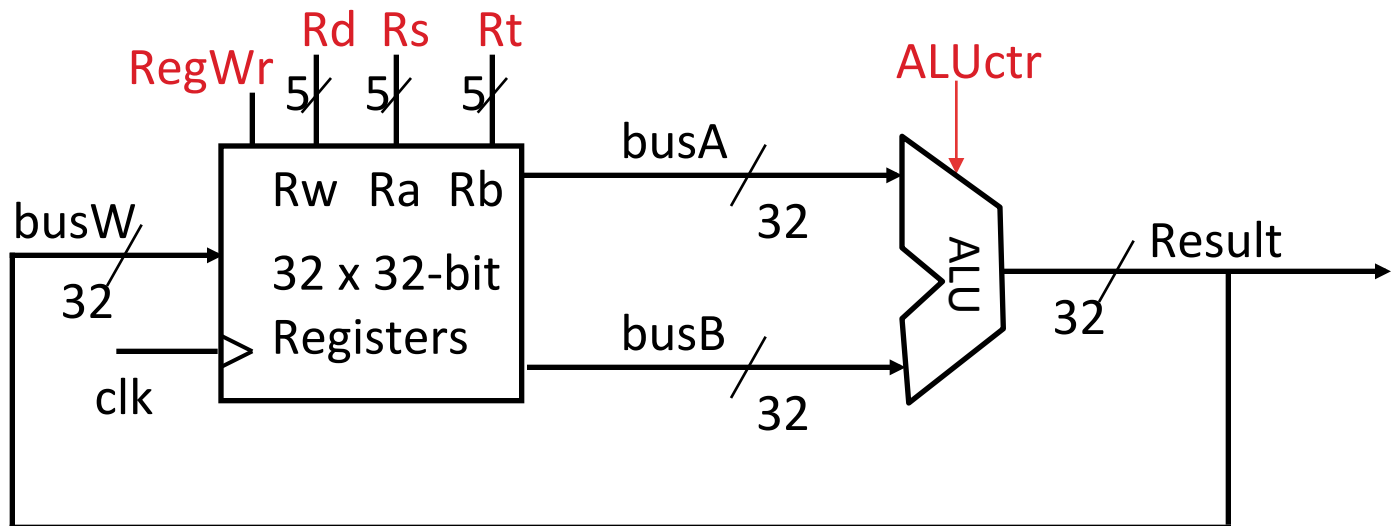- **ALUctr** and **RegWr**: control logic after decoding the instruction



- ... Already defined the register file & ALU



# Clocking Methodology

 

- Storage elements clocked by same edge
- Flip-flops (FFs) and combinational logic have some delays
  - Gates: delay from input change to output change
  - Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF (set-up time), and we have the usual clock-to-Q delay
- “Critical path” (longest path through logic) determines length of clock period



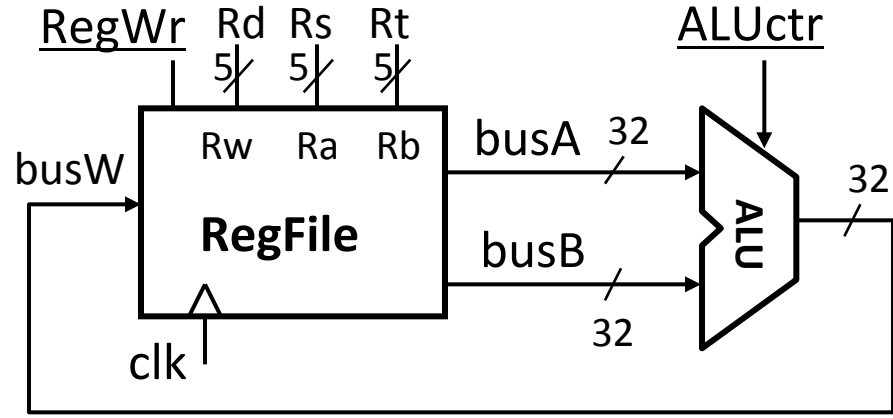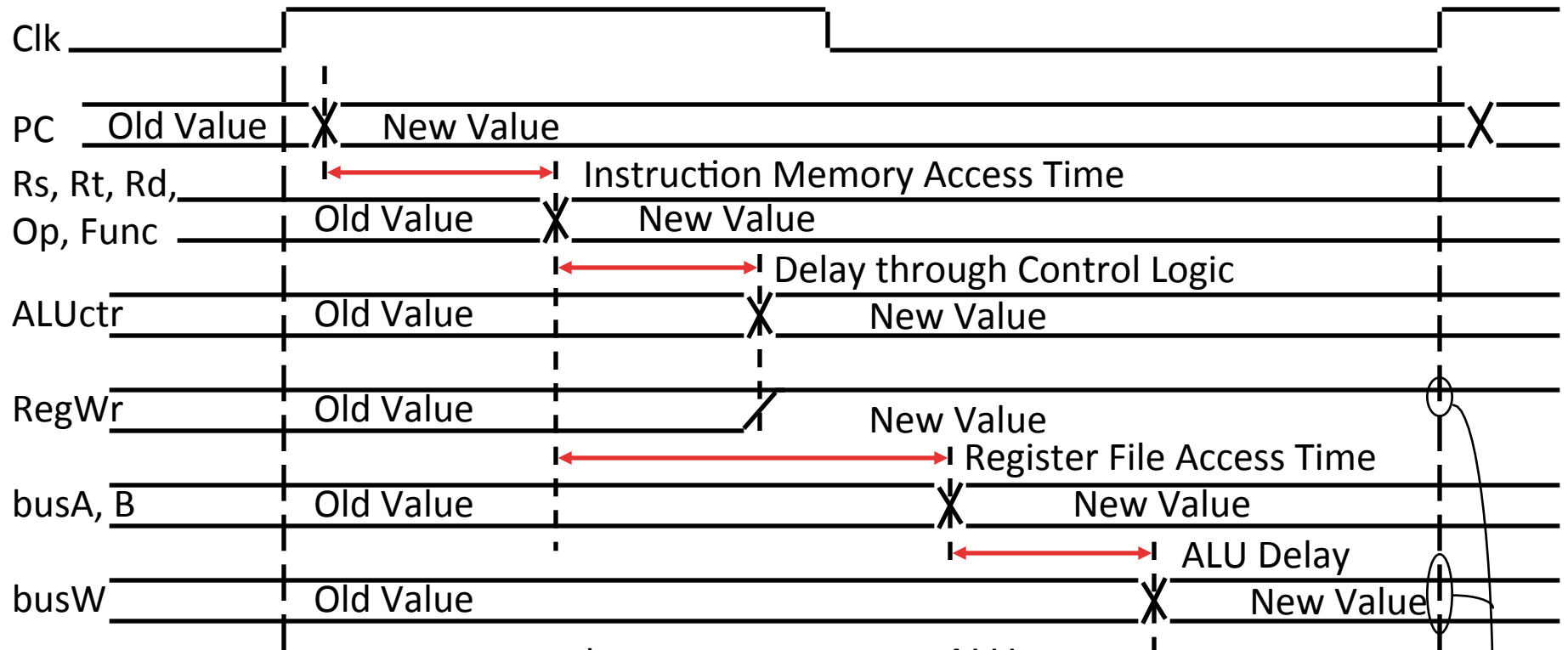
# Register-Register Timing: One Complete Cycle



Register Write Occurs Here
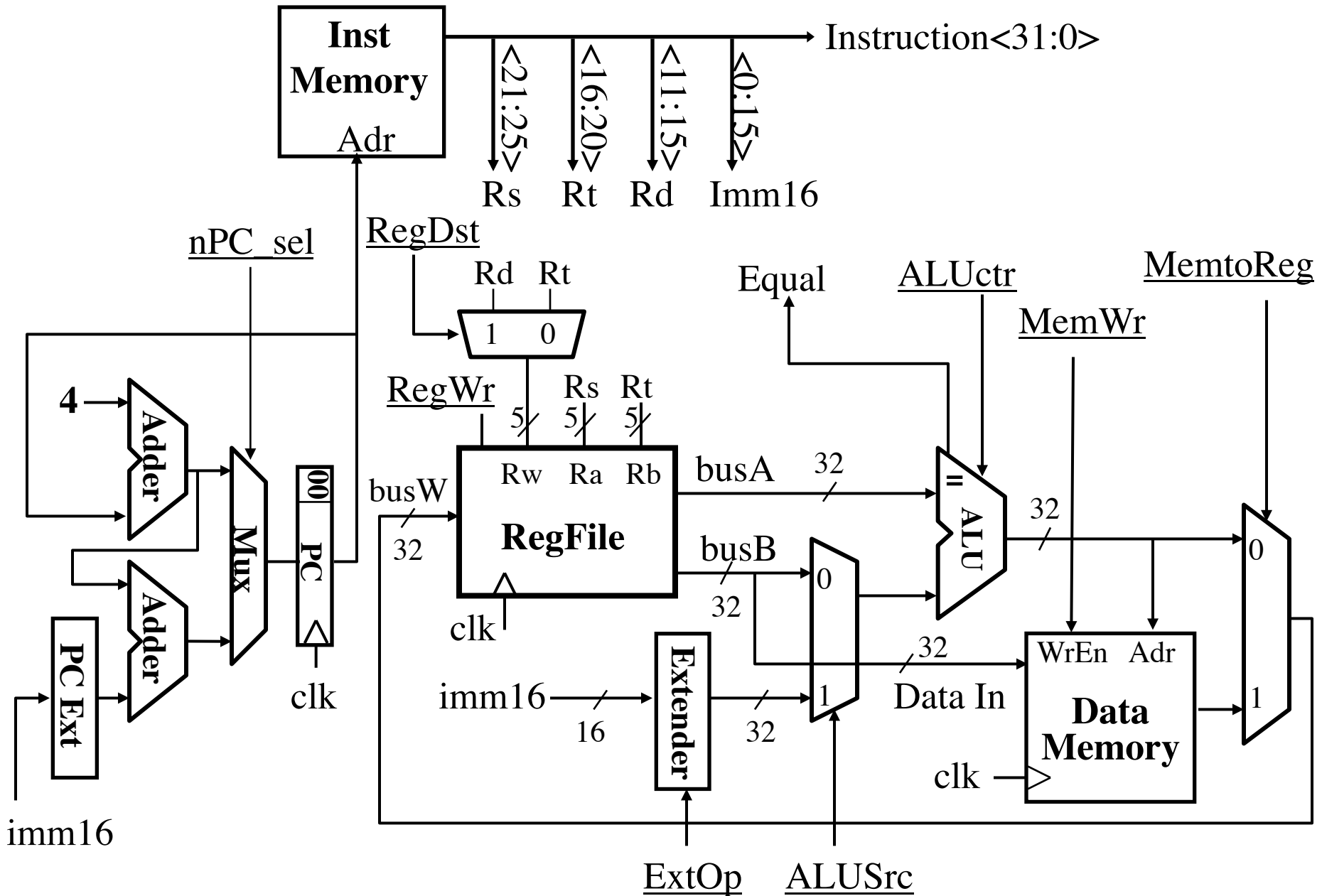
# Putting it All Together: A Single Cycle Datapath



# Processor Design: 3 of 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology

Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic

# In Conclusion

- “Divide and Conquer” to build complex logic blocks from smaller simpler pieces (adder)
- Five stages of MIPS instruction execution
- Mapping instructions to datapath components
- Single long clock cycle per instruction