

EE100

HOMEWORK SET 4

Fall 2004

Issued: September 20, 2004

Due: September 27, 2004

1. Do Problem 3.3.
2. Do Problem 3.4.
3. Do Problem 3.6.
4. Do Problem 3.8.
5. Do Problem 3.16.
6. Do Problem 3.20.

- 3.3** Using node voltage analysis in the circuit of Figure P3.3, find the currents i_1 and i_2 . $R_1 = 3 \Omega$; $R_2 = 1 \Omega$; $R_3 = 6 \Omega$.

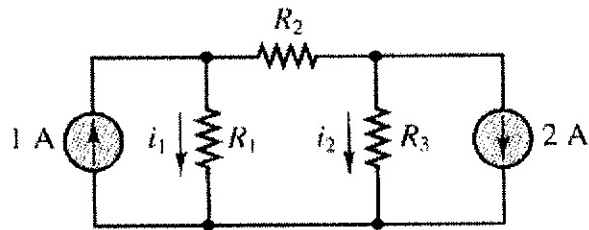


Figure P3.3

- 3.4** Use the mesh analysis to determine the currents i_1 and i_2 in the circuit of Figure P3.3.

- 3.6** Using node voltage analysis in the circuit of Figure P3.6, find the three indicated node voltages. Let $I = 0.2 \text{ A}$; $R_1 = 200 \Omega$; $R_2 = 75 \Omega$; $R_3 = 25 \Omega$; $R_4 = 50 \Omega$; $R_5 = 100 \Omega$; $V = 10 \text{ V}$.

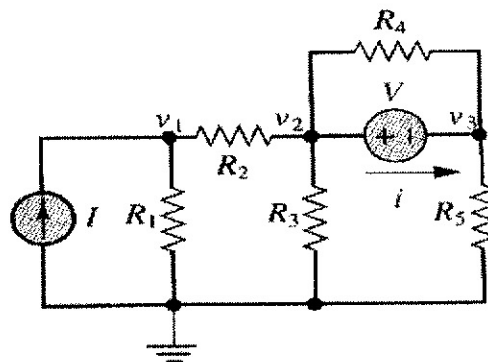


Figure P3.6

- 3.8** The circuit shown in Figure P3.8 is a Wheatstone bridge circuit. Use node voltage analysis to determine V_a and V_b , and thus determine $V_a - V_b$.

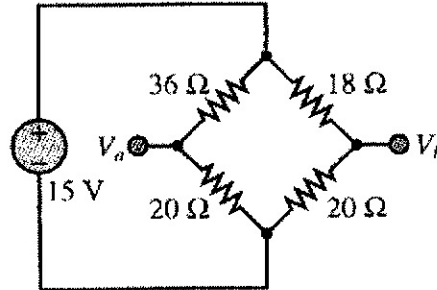


Figure P3.8

- 3.16** Use mesh current analysis to find the current i in the circuit of Figure P3.16. Let $V = 5.6$ V; $R_1 = 50$ Ω ; $R_2 = 1.2$ k Ω ; $R_3 = 330$ Ω ; $g_m = 0.2$ S; $R_4 = 440$ Ω .

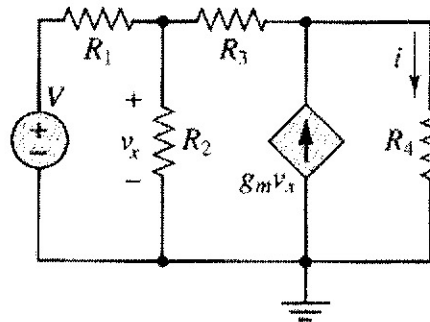


Figure P3.16

- 3.20** Using mesh current analysis, find the voltage gain $A_v = v_2/v_1$ in the circuit of Figure P3.20.

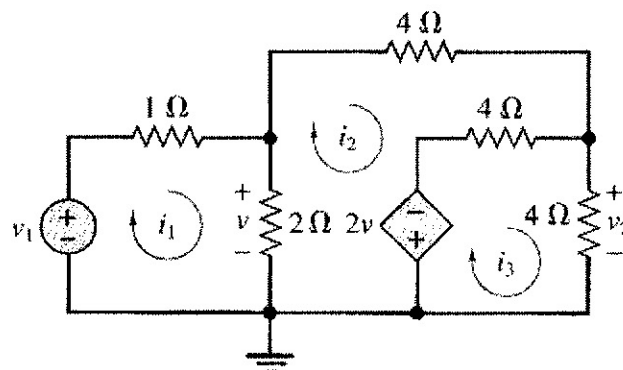


Figure P3.20