

Issued: November 1, 2004

Due: November 8, 2004

Problem 1.

For the circuit shown in Fig. 1 calculate $v_o(t)$ for $t \geq 0$, given $i_L(0) = 2 \text{ A}$.

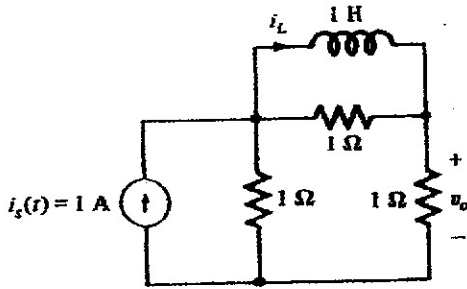


Figure 1

Problem 2.

For the circuit shown in Fig. 2 given $v_s = 10 \text{ V}$, $R_1 = 2 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $C = 1 \mu\text{F}$ and $i_c = 5 \text{ mA}$ at $t = 1 \text{ ms}$,

- (a) Calculate and sketch $v_R(t)$ for $t \geq 1 \text{ ms}$.
- (b) Repeat (a) with $R_2 = -1 \text{ k}\Omega$.
- (c) For part (a), what is the elapsed time for which v_R changes from 8 to 6 V?

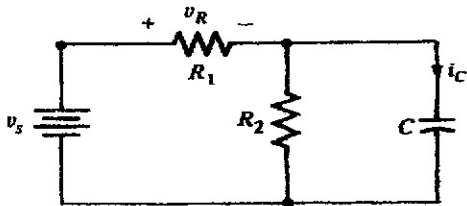


Figure 2

Problem 3.

The RC circuit in Fig. 3 (a) is driven by the stepwise signal shown in Fig. 3 (b). Assuming $v_c(0) = 2E_0$, calculate and sketch $i_2(t)$ for $t \geq 0$.

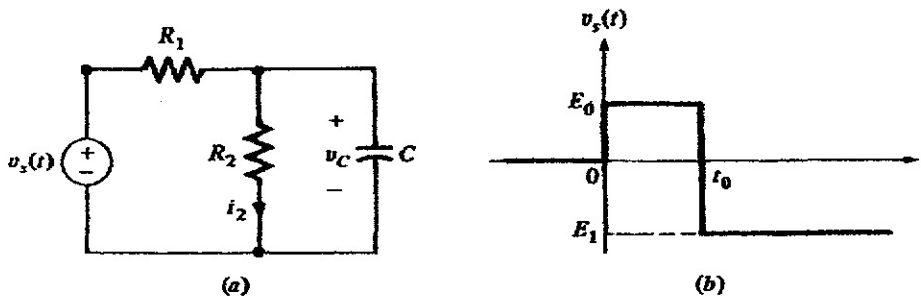


Figure 3

Problem 4.

Calculate and sketch $v(t)$, $t \geq 0$ for the circuit shown in Fig. 4 (a) with $i_s(t)$ as in Fig. 4 (b). Assume $v_c(0) = 0$.

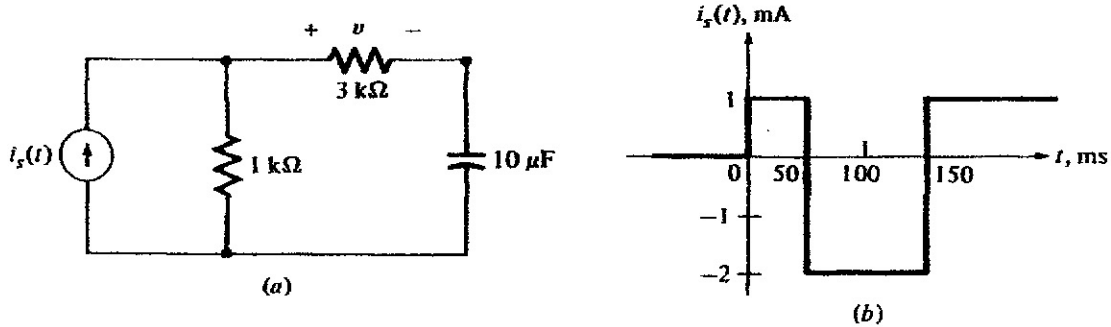


Figure 4

Problem 5.

The circuit in Fig. 5 (a) is to be used as a flip-flop. The v - i characteristic of the nonlinear resistor is given in Fig. 5 (b). In order to switch from Q_1 to Q_3 , a triggering signal, Fig. 5 (c) is applied. Determine the minimum duration of the pulse required for successful switching.

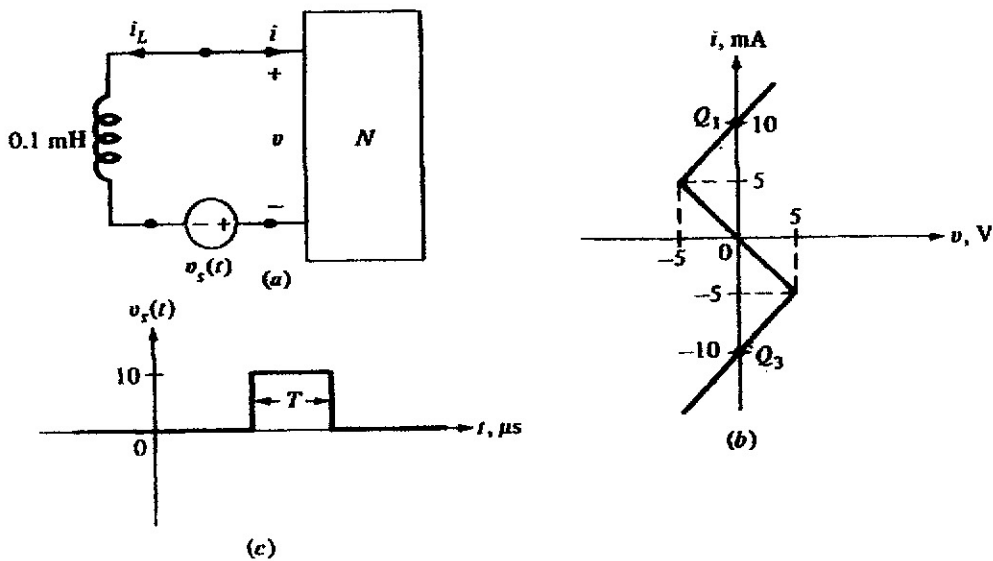


Figure 5