

REVISION TO HOMEWORK SET 12

Homework set 12 is due December 6, 2004.

The following two problems are added:

PROBLEM 6.

Do Problem 9.20 on 510 of textbook.

PROBLEM 7.

Do Problem 9.24 on page 510 of text.

where at $T = 300$ K

$$I_o = 2.030 \times 10^{-15} \text{ A} \quad V_T = \frac{kT}{q} \approx 26 \text{ mV}$$

$$v_S = 5.3 \text{ V} + 7 \cos(\omega t) \quad \text{mV}$$

$$\omega = 377 \text{ rad/s} \quad R = 4.6 \text{ k}\Omega$$

Determine, using superposition and the offset (or threshold) voltage model for the diode, the DC or Q point current through the diode.

9.20 If the diode in the circuit shown in Figure P9.18 is fabricated from silicon and

$$i_D = I_o(e^{v_D/V_T} - 1)$$

where at $T = 300$ K

$$I_o = 250 \times 10^{-12} \text{ A} \quad V_T = \frac{kT}{q} \approx 26 \text{ mV}$$

$$v_S = 4.2 \text{ V} + 110 \cos(\omega t) \quad \text{mV}$$

$$\omega = 377 \text{ rad/s} \quad R = 7 \text{ k}\Omega$$

and the DC operating point or quiescent point (Q point) is

$$I_{DQ} = 0.5458 \text{ mA} \quad V_{DQ} = 379.5 \text{ mV}$$

determine the equivalent small-signal AC resistance of the diode at room temperature at the Q point given.

9.21 If the diode in the circuit shown in Figure P9.18 is fabricated from silicon and

$$i_D = I_o(e^{v_D/V_T} - 1)$$

where at $T = 300$ K

$$I_o = 2.030 \times 10^{-15} \text{ A} \quad V_T = \frac{kT}{q} \approx 26 \text{ mV}$$

$$v_S = 5.3 \text{ V} + 70 \cos(\omega t) \quad \text{mV}$$

$$\omega = 377 \text{ rad/s} \quad R = 4.6 \text{ k}\Omega$$

and the DC operating point or quiescent point (Q point) is

$$I_{DQ} = 1.000 \text{ mA} \quad V_{DQ} = 0.700 \text{ V}$$

determine the equivalent small-signal AC resistance of the diode at room temperature at the Q point given.

9.22 A diode with the i - v characteristic shown in Figure 9.8 in the text is connected in series with a 5-V voltage source (in the forward bias direction) and a load resistance of 200Ω . Determine

- The load current and voltage.
- The power dissipated by the diode.
- The load current and voltage if the load is changed to 100Ω and 500Ω .

9.23 A diode with the i - v characteristic shown in Figure 9.32 in the text is connected in series with a 2-V voltage source (in the forward bias direction) and a

load resistance of 200Ω . Determine

- The load current and voltage.
- The power dissipated by the diode.
- The load current and voltage if the load is changed to 100Ω and 300Ω .

9.24 The diode in the circuit shown in Figure P9.18 is fabricated from silicon and

$$i_D = I_o(e^{v_D/V_T} - 1)$$

where at $T = 300$ K

$$I_o = 250 \times 10^{-12} \text{ A} \quad V_T = \frac{kT}{q} \approx 26 \text{ mV}$$

$$v_S = V_S + v_x = 4.2 \text{ V} + 110 \cos(\omega t) \quad \text{mV}$$

$$\omega = 377 \text{ rad/s} \quad R = 7 \text{ k}\Omega$$

The DC operating point or quiescent point (Q point) and the AC small-signal equivalent resistance at this Q point are

$$I_{DQ} = 0.548 \text{ mA} \quad V_{DQ} = 0.365 \text{ V} \quad r_d = 47.45 \Omega$$

Determine, using superposition, the AC voltage across the diode and the AC current through it.

9.25 The diode in the circuit shown in Figure P9.25 is fabricated from silicon and

$$R = 2.2 \text{ k}\Omega \quad V_{S2} = 3 \text{ V}$$

Determine the minimum value of V_{S1} at and above which the diode will conduct with a significant current.

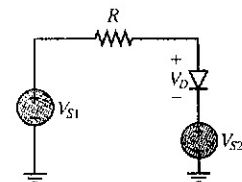


Figure P9.25

Section 9.4: Rectifier Circuits

9.26 Find the average value of the output voltage for the circuit of Figure P9.26 if the input voltage is sinusoidal with an amplitude of 5 V . Let $V_\gamma = 0.7 \text{ V}$.

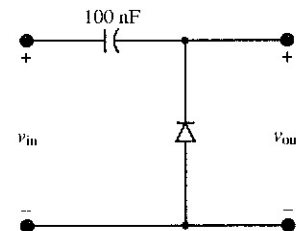


Figure P9.26