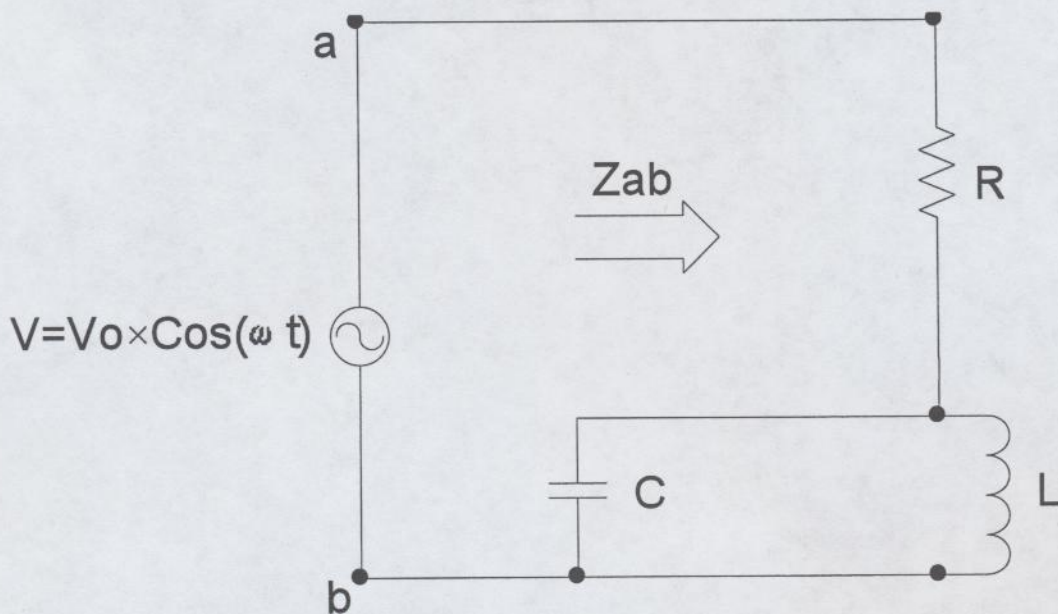


## PROBLEM 1 [5 points]



Find an expression for  $\omega$  (in terms of circuit variables  $L$ ,  $C$ , and/or  $R$ ) such that  $Z_{ab}$  (the impedance across nodes a and b) is purely resistive.

$$Z_{ab} = R + \left( \frac{1}{j\omega L} + j\omega C \right)^{-1} = R + \frac{j\omega L}{1 - \omega^2 LC}$$

purely resistive.  $\Rightarrow$  imaginary part = 0

$$\frac{j\omega L}{1 - \omega^2 LC} = 0 \quad \omega = 0$$

Expression for  $\omega$ :  $\neq 0$

#2 a) Inductor

$$\tau = \frac{L}{R} = 1 \text{ sec.}$$

$$t < 0 : \begin{aligned} i_L(t) &= 0 \\ v_L(t) &= 0 \end{aligned}$$

$$0 < t < \infty : i_L(0^+) = 0$$

$$i_L(\infty) = 10 \text{ A}$$

$$i_L(t) = 10 + (0-10)e^{-t/\tau} = 10 - 10e^{-t}$$

$$v_L(t) = L \frac{di}{dt} = 1 \times 10e^{-t} = 10e^{-t}$$

$$v_L(0^+) = 10 \text{ V}$$

$$v_L(\infty) = 0$$





Capacitor

$$\tau = RC = 1 \text{ sec}$$


$$t < 0 : \begin{aligned} i_C(t) &= 0 \\ v_C(t) &= 0 \end{aligned}$$

$$0 < t < \infty : \begin{aligned} i_C(0^+) &= 10 \text{ A} \\ i_C(\infty) &= 0 \end{aligned} \quad \left. \vphantom{\begin{aligned} i_C(0^+) &= 10 \text{ A} \\ i_C(\infty) &= 0 \end{aligned}} \right\} i_C(t) = 10e^{-t}$$
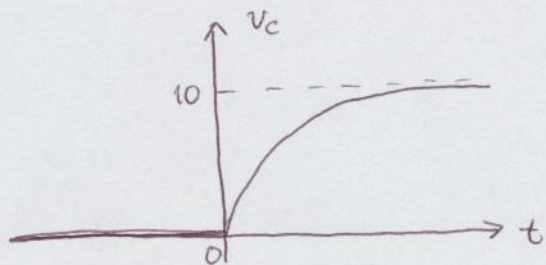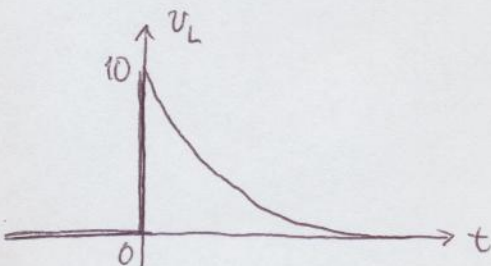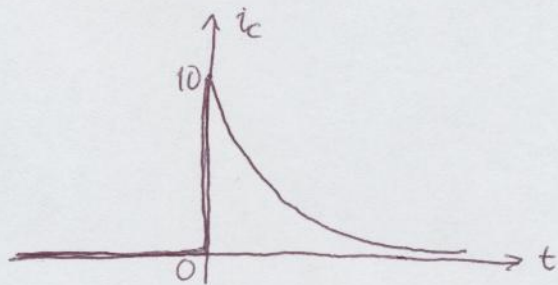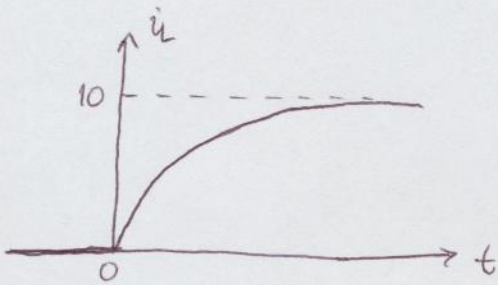
$$\begin{aligned} v_C(0^+) &= 0 \\ v_C(\infty) &= 10 \text{ V} \end{aligned} \quad \left. \vphantom{\begin{aligned} v_C(0^+) &= 0 \\ v_C(\infty) &= 10 \text{ V} \end{aligned}} \right\} v_C(t) = 10 - 10e^{-t}$$





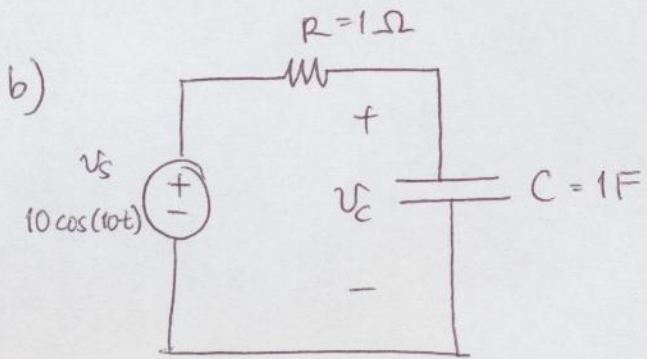

$t \rightarrow \infty$  : steady-state  
Use voltage divider


$$v_c = V_s \left| \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \right| = V_s \left| \frac{1}{1 + j\omega RC} \right| = \frac{V_s}{\sqrt{1^2 + \omega^2 RC}}$$

$$\begin{aligned} \omega &= 10 \text{ rad/s} \\ R &= 1 \Omega \\ C &= 1 \text{ F} \end{aligned}$$

$$v_c = 0.995 \text{ V}$$

PROBLEM 3 [8 points]

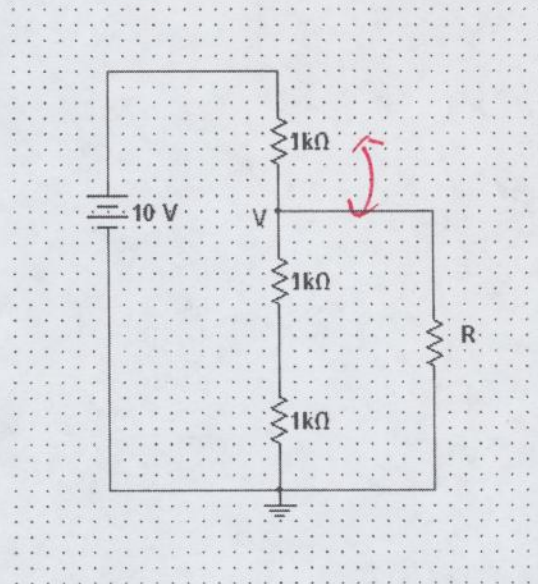(a) In the circuit below, find the value of R such that the node V has a voltage of 5 volts.



$$V = 5V$$


$$R_{eq} = \frac{2kR}{2k+R}$$

$$5V = 10 \frac{\frac{2kR}{2k+R}}{\frac{2kR}{2k+R} + 1k}$$

$$R = 2k\Omega$$

R: 2kΩ

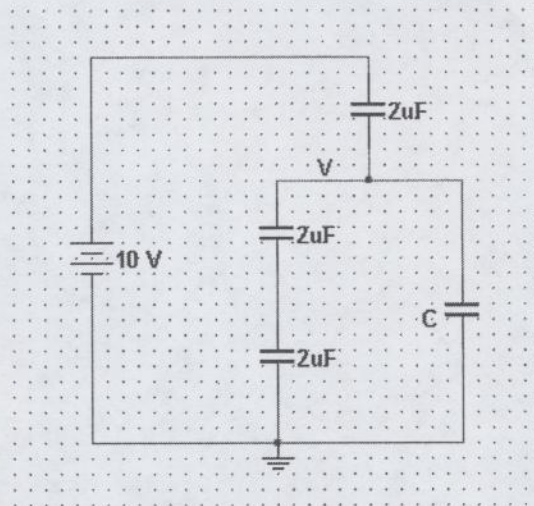(b) In the circuit below, find the value of C such that node V has a voltage of 5 volts.



$$C_{eq} = \left( \frac{1}{2\mu F} + \frac{1}{2\mu F} \right)^{-1} + C$$

$$V = 5V$$

$$2\mu F = C_{eq}$$

$$2\mu F = \frac{4(\mu F)^{-1}}{4\mu F} + C$$

$$C = 1\mu F$$


C: 1μF



**PROBLEM 4 [10 points]**

Consider the circuit shown below along with its the  $v$ - $i$  characteristic

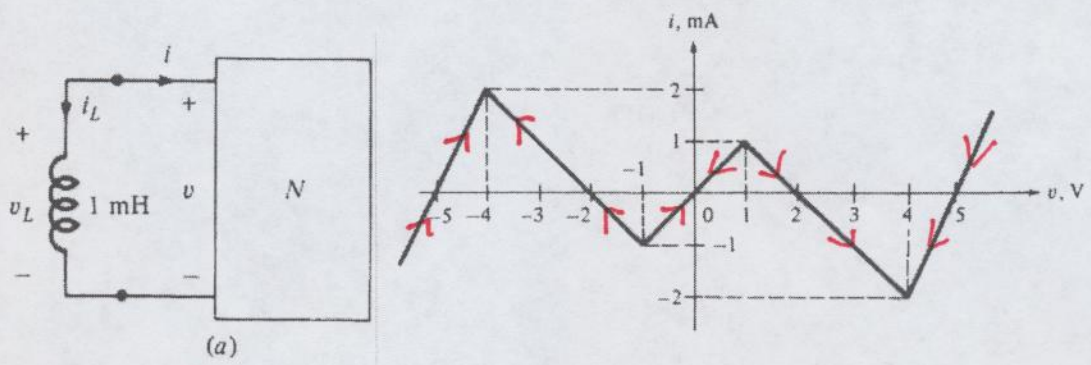(a) Sketch the dynamic route on the graph shown below.



$$V = L \frac{di}{dt}$$

$$V_L = -L \frac{di}{dt}$$

$$V > 0 \Rightarrow i \downarrow$$


$$V < 0 \Rightarrow i \uparrow$$

(b) For what range of initial condition  $i_L(0)$  does this circuit exhibit oscillation ?


Conditions on  $i_L(0)$ :  $V_L(0) < -1 \text{ V}$   
 $V_L(0) > 1 \text{ V}$

# Solution

#5

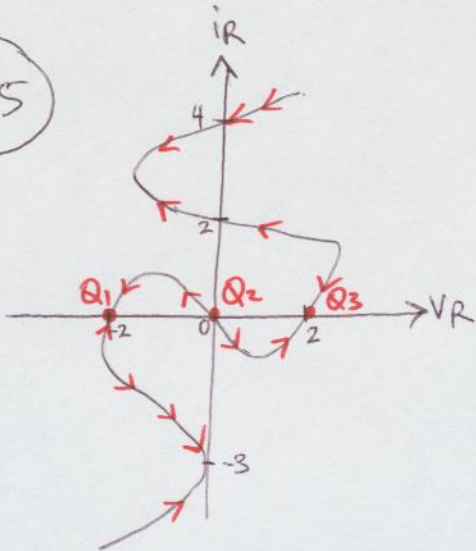

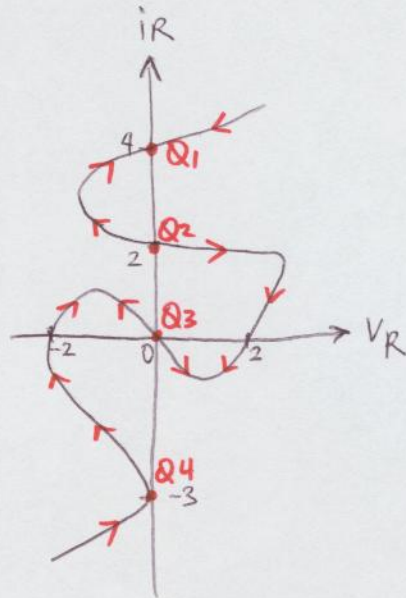- $Q_1$  stable
- $Q_2$  unstable
- $Q_3$  stable




- $Q_1$  stable
- $Q_2$  } unstable
- $Q_3$  }
- $Q_4$  }



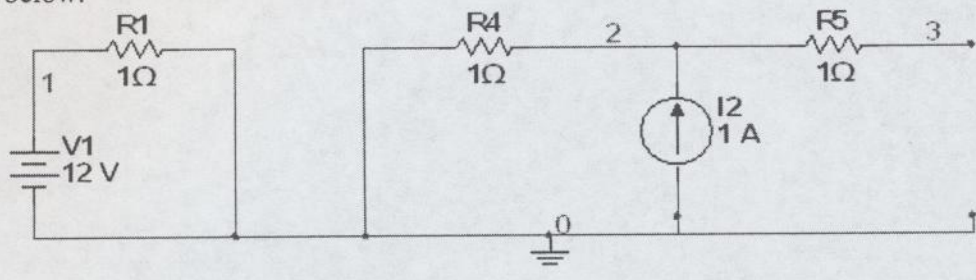**PROBLEM 6 [5 points]**

Find the Thévenin and Norton equivalent circuit across terminals 3 and 0 for the circuit below.




(a) Sketch the Thévenin equivalent circuit in the box:


Handwritten calculations and circuit sketches for the Thévenin equivalent:

- V<sub>OC</sub> calculation:** A circuit diagram shows a 1A current source in parallel with a 1Ω resistor. The voltage across the resistor is labeled  $V_{OC}$ . The calculation is:  $V_{OC} = (1A)(1\Omega) = 1V$ .
- i<sub>SC</sub> calculation:** A circuit diagram shows a 1A current source in parallel with two 1Ω resistors. The current through the rightmost resistor is labeled  $i_{SC}$ . The calculation is:  $i_{SC} = 0.5A$ .
- Thévenin Resistance:** The calculation is:  $R_{Th} = \frac{V_{OC}}{i_{SC}} = 2\Omega$ .
- Thévenin Equivalent Circuit:** A box contains a hand-drawn circuit consisting of a 1V DC voltage source in series with a 2Ω resistor, connected to terminals 3 and 0.

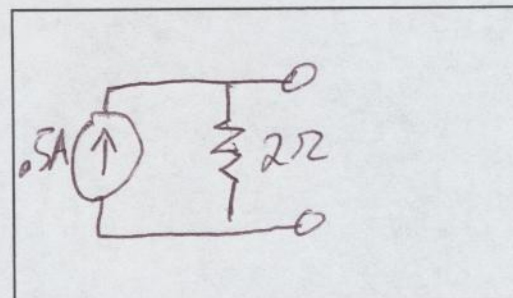
(b) Sketch the Norton equivalent circuit in the box:



PROBLEM 7 [10 points]

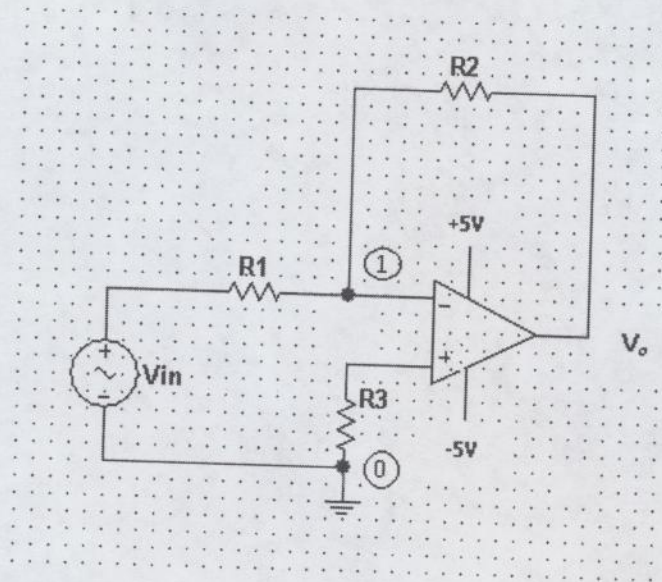

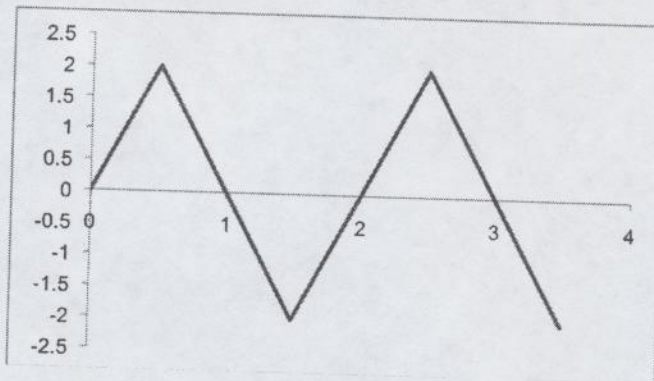
- (a) Assuming the op-amp in the circuit above is ideal, derive  $V_o$ , in the linear regime, in terms of  $V_{in}$ ,  $R_1$ ,  $R_2$ , and/or  $R_3$ . Show your work on the next page.
- (b) Find the gain ( $V_o / V_{in}$ ) in the *linear* regime for the circuit if  $R_1=1k\Omega$ ,  $R_2=5k\Omega$ , and  $R_3=1k\Omega$ .
- (c) Sketch the output voltage versus time if it is given the following input voltage:



$V_o: -V_{in} \frac{R_2}{R_1}$

Gain:  $-5$

Sketch the output voltage in the box:

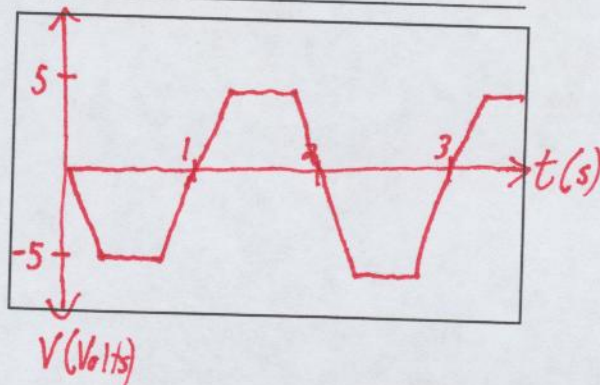



## EXTRA WORKSPACE FOR PROBLEM 7

a)

$$V^+ = V^- = 0$$

$$\frac{V_{in} - 0}{R_1} = \frac{0 - V_o}{R_2}$$

$$\frac{V_{in}}{R_1} = -\frac{V_o}{R_2}$$

$$V_o = -V_{in} \frac{R_2}{R_1}$$

$$b) \text{ Gain} = \frac{V_o}{V_{in}} = -\frac{R_2}{R_1} = -\frac{5000}{1000} = -5$$

PROBLEM 8 [15 points]

Non-linear Region

$V_o = +5$  or  $-5$


$\frac{V - V_o}{R_1} = i$

$i = \frac{V - 5}{R_1}$  ( $V_o = 5$ )

$i = \frac{V + 5}{R_1}$  ( $V_o = -5$ )

$i = \frac{V - 5}{R_1}$  valid for  $V \geq 2.5$

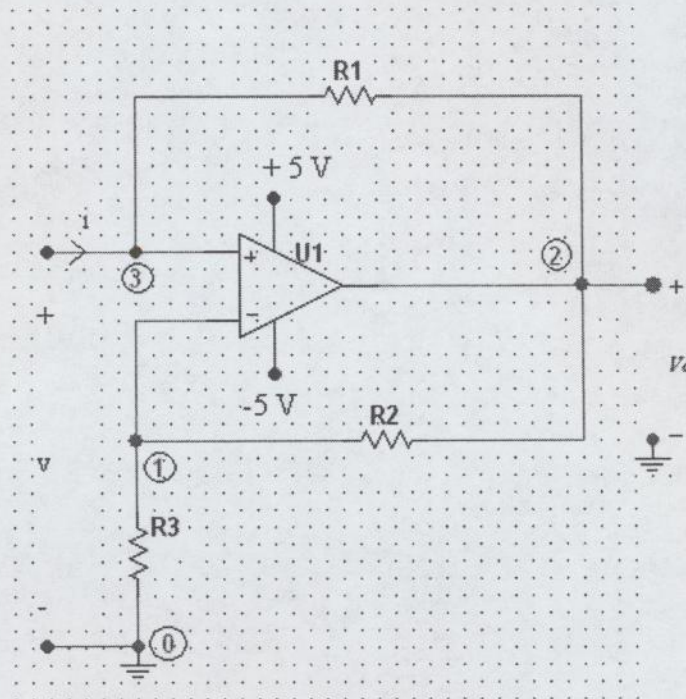$i = \frac{V + 5}{R_1}$  valid for  $V \leq -2.5$



a) Node 3  
(1)  $\frac{V_3 - V_o}{R_1} = i$  ( $V_3 = V$ )

Node 1  
(2)  $\frac{V_1 - V_o}{R_2} + \frac{V_1 - V_o}{R_3} = 0$  ( $V_1 = V_3 = V$ )

$V_1 \left( \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{V_o}{R_2}$

$V_o = V_1 R_2 \left( \frac{R_2 + R_3}{R_2 R_3} \right)$

$V_o = V_1 \frac{(R_2 + R_3)}{R_3}$

(1) + (2)  $\frac{V_3 - V_1 \frac{(R_2 + R_3)}{R_3}}{R_1} = i$

$\frac{V_3}{R_1} - \frac{V_1 (R_2 + R_3)}{R_1 R_3} = i$

$V_3 = V_1 = V$

$V \left( \frac{1}{R_1} - \frac{R_2 + R_3}{R_1 R_3} \right) = i$

$i = \frac{V}{R_1} \left( \frac{R_3 + R_2 - R_3}{R_3} \right)$

$i = -\frac{V R_2}{R_1 R_3}$

Linear Region

valid for  $-2.5 \leq V \leq 2.5$


(a) Derive an expression for  $i$  in terms of  $v$ ,  $R_1$ ,  $R_2$ , and  $R_3$  for all three regions of operation for the op-amp above. Show your work on the next page.

(b) If  $R_1=1k\Omega$ ,  $R_2=2k\Omega$ , and  $R_3=2k\Omega$  plot the IV characteristics below.

Expression for  $i =$

$i = -\frac{V R_2}{R_1 R_3}$	(linear)
$i = (V - 5)/R_1$	(+ve saturation)
$i = (V + 5)/R_1$	(-ve saturation)


Sketch  $i-v$  graph in the box:

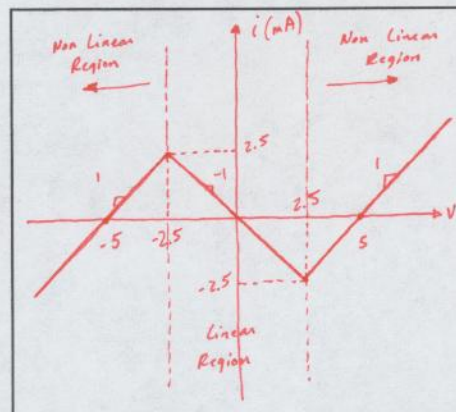



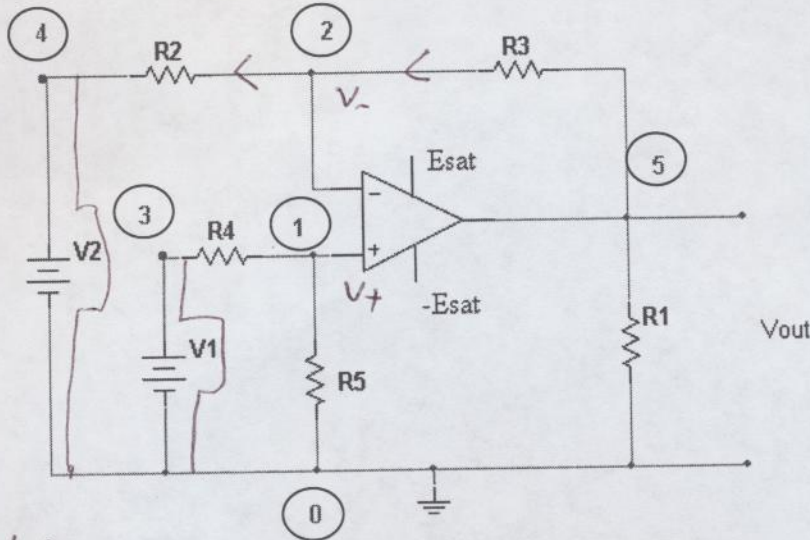**PROBLEM 9 [10 points]**

Find an algebraic expression for the voltage  $V_{out}$ , the voltage across resistor 1, in the linear region. Hint: use superposition.



Shorting  $V_1$ :

$V_+ = 0$ . By ideal opamp  $V_+ = V_- \rightarrow \frac{V_{out} - 0}{R_3} = \frac{0 - V_2}{R_2} \rightarrow V_{out} = -\frac{R_3}{R_2} V_2$

Shorting  $V_2$ :

$V_+ = \frac{R_5 V_1}{R_4 + R_5} \rightarrow V_+ = V_- \rightarrow \frac{V_- - 0}{R_2} = \frac{V_{out} - V_-}{R_3} \rightarrow V_{out} = \frac{R_3 + R_2}{R_2} V_- = \frac{(R_3 + R_2) R_5 V_1}{R_2 (R_4 + R_5)}$

→ voltage divider

By superposition  $V_{out} = \frac{(R_3 + R_2) R_5}{R_2 (R_4 + R_5)} V_1 - \frac{R_3}{R_2} V_2$

$V_{out}$  in the linear region (in terms of  $V_1, V_2, R_1, R_2, R_3, R_4$  and/or  $R_5$ ):




$$V_{out} = \frac{(R_3 + R_2) R_5}{R_2 (R_4 + R_5)} V_1 - \frac{R_3}{R_2} V_2$$

Find  $V_{out}$  if  $R_1 = R_2 = R_3 = R_4 = R_5 = 1\Omega, V_1 = V_2 = 1V, E_{sat} = 5V, -E_{sat} = -5V$ :

$$V_{out} = \frac{(2)(1)}{1(2)} - \frac{1}{1}(1) = 0$$

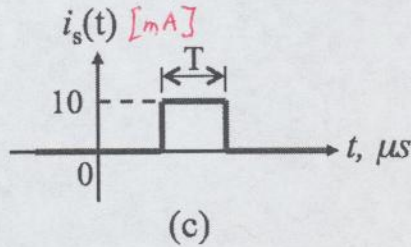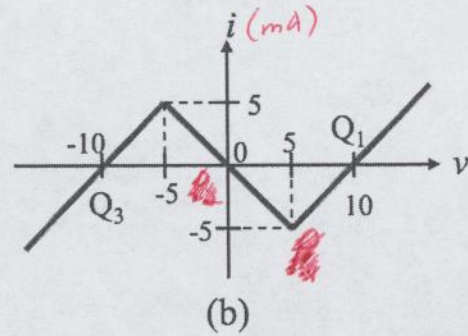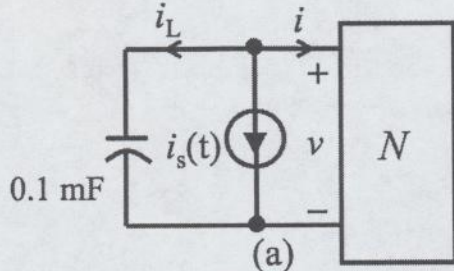**PROBLEM 10 [15 points]**

The circuit below is to be used as a flip-flop. In order to switch from  $Q_1$  to  $Q_3$  the triggering signal below is applied.



- (a) Determine the minimum duration  $T$  of the pulse required for successful switching. Show your work on the next page.
- (b) Sketch the relevant dynamic routes corresponding to a pulse width  $T = 0.15s$ .

(a) Minimum Duration of T: \_\_\_\_\_

(b) Sketch relevant dynamic routes in the box:

$$\textcircled{a} \quad Q_2 \rightarrow P_1: \tau = 0.1 \text{ mF} (1 \text{ k}\Omega) = 0.1 \text{ s}$$


$$t_1 = \tau \ln \left[ \frac{10-0}{5-0} \right] = 0.1 \ln[2]$$

$$= 0.0693 \text{ s}$$

$$P_1 \rightarrow P_2: \tau = -0.1 \text{ s}$$

$$t_2 = t_1 + \tau \ln \left[ \frac{5-10}{0-10} \right] = 2(0.1) \ln(2)$$
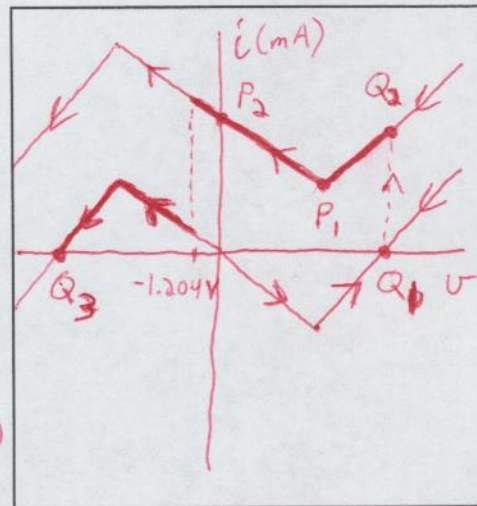
$$t_2 = \boxed{T_{\min} = 0.1386 \text{ s}}$$



$$\textcircled{b} \quad 0.15 - 0.1 \ln 2 = -0.1 \ln \left[ \frac{5-10}{v(t=0.15 \text{ s}) - 10} \right]$$

$$\hookrightarrow \boxed{v(t=0.15 \text{ s}) = -1.204 \text{ V}}$$