

Announcements / Conclude last lecture / Final Exam Review

Announcements → MAKE SURE ALL

UR ONLINE GRADES ARE CORRECT
BY 05/06/05 (THIS FRIDAY),
5:00pm

↳ H.W issues: post on forums

↳ Midterm issues: Bring it to my OH
on Thursday.

↳ FINISH PROJECT / TURN IN REPORT
BY 5:00 pm, 05/06/05 (THIS FRIDAY)
1 report/group, TURN IN A.W
BOX

↳ H.W scores in by tomorrow, lab
grades are coming in.

To conclude last lecture:

→ NO GRADE
CORRECTIONS AFTER
THIS

↳ What classes
can you take
after this?

EE

EE105: Transistors etc

EE401: Circuit design

One concept:

Semiconductor physics,

however just go

thru few lectures
in EE40

non EE:

IF U
WANNA GO
TO GRAD.
SCHOOL

Final Exam Review

Note:

(1) Final is on Friday the

13th (☹️): 12:30 - 3:30 pm
in 2050 VLSB

Note: **No MAKEUP FINAL!**

(2) Final will have 4 questions, 25 points each:

Month 1:
Circuit analysis
(i.e., node voltage
method)

Month 2:
RC, RL
Circuits

Month 3/4:
op-amps,
nonlinear diodes

Month 4:
Zener
diodes,
non linear,
graphical method

GRAD. SCHOOL

1) Math 104: Analysis

Math 110: Linear Algebra

2) Take grad. classes in
or major!

ex: EE221 → DEATH SENTENCE!

(3) GET A RESEARCH PAPER
PUBLISHED

Cheatsheet:

(3) (a) $\left. \begin{array}{l} \text{pages, } 8.5'' \times 11'', \text{ both sides, any font, any size.} \end{array} \right\}$



(b) Try to make it "nice numbers", but you may bring a calculator, you won't need

it!

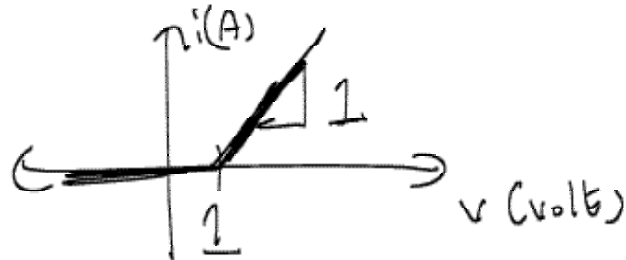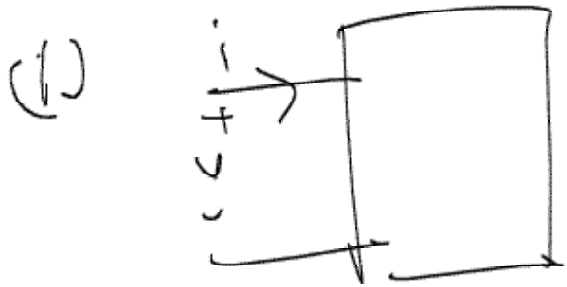(4) Review problems will be up by tomorrow

O, A session in before Monday
Justin's review session next
Tuesday.

Sample: I classify this as a ^{very} difficult problem:






a) Design a ^{realistic} circuit in the black box that has the $i-v$ characteristics shown. (no negative resistors, i.e., no -1Ω circuit is realistic)


b) (very, very, difficult): Is this the only circuit which has this $i-v$ characteristic? Justify your answer. No!

Notice circuit is nonlinear ($i-v$ graph is not one straight line)

\Rightarrow diode is present!



Solve using graphical method.

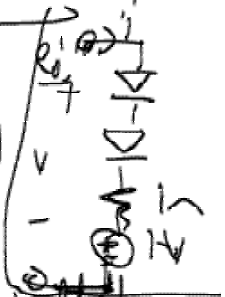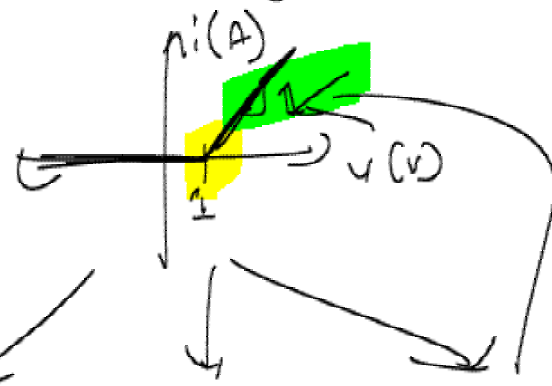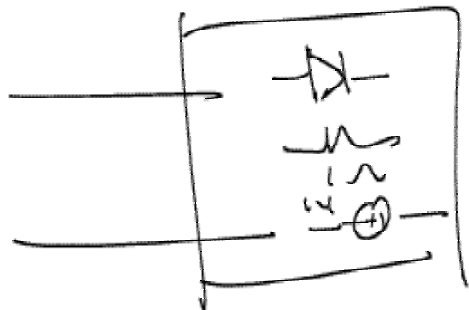

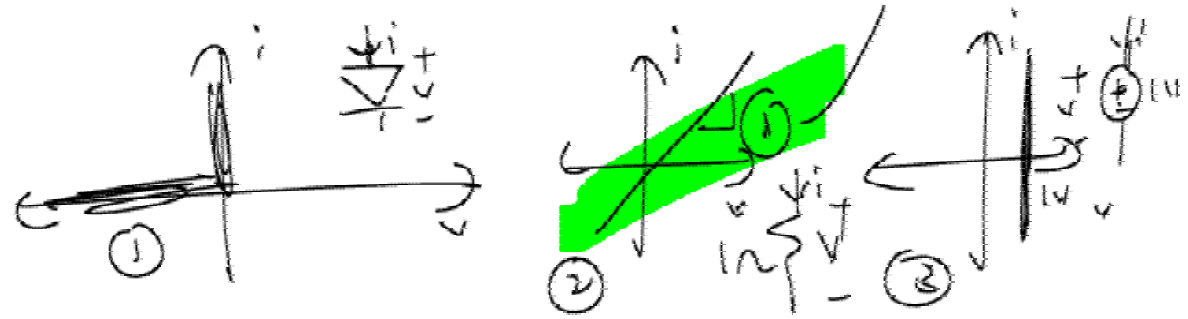


Notice you combine them in series

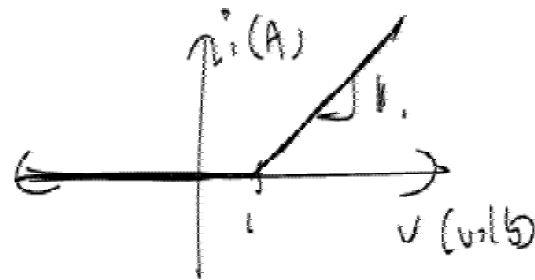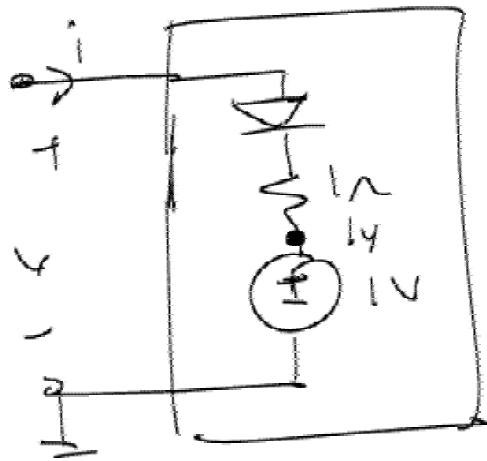
"because to get the given $i-v$, you graphically add (1), (2), (3) with constant current."



NOTE: DON'T MAKE THE PROBLEM MORE DIFFICULT THAN IT IS! I.E... DON'T THINK TOO MUCH... ex: How ||; lost H-w problem:

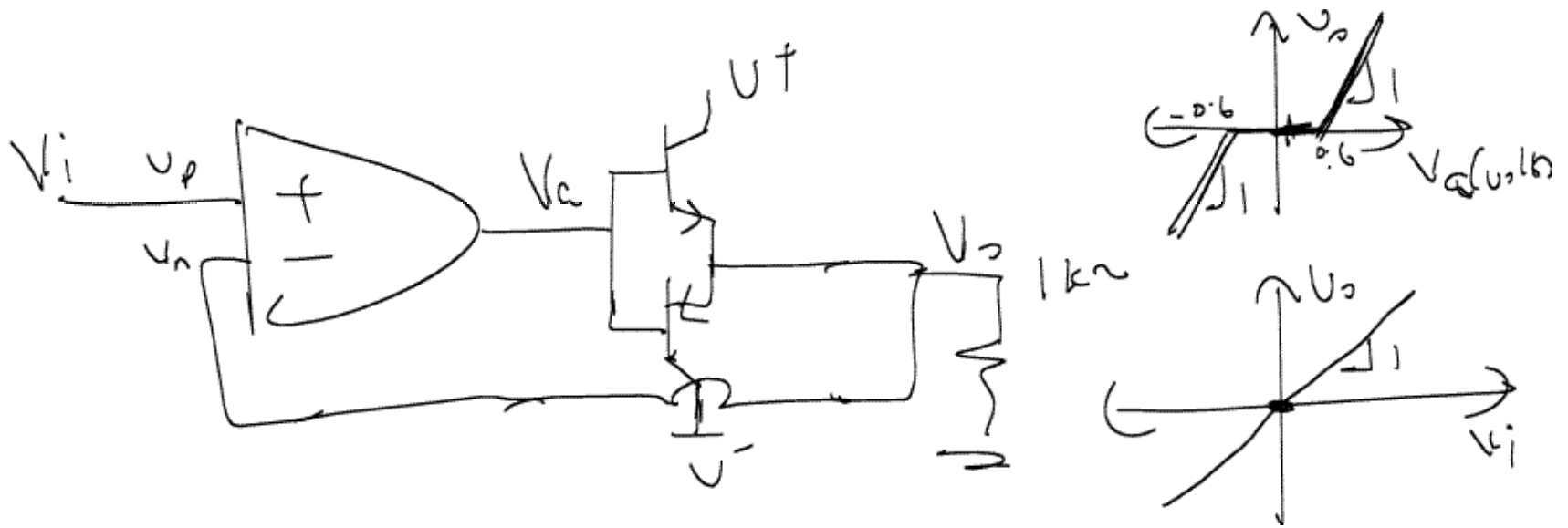

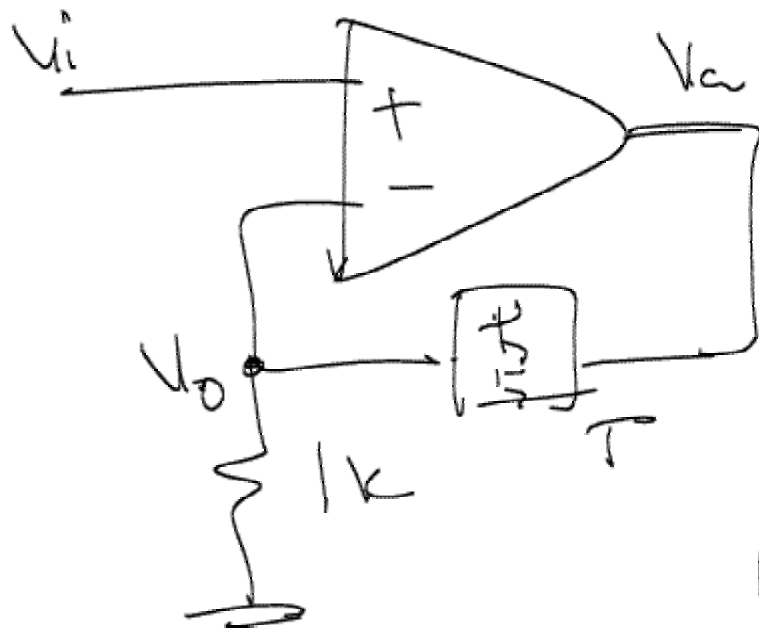
Why is $V_i = V_o$? , how do you know $V_p \approx V_n$??
 Turns out, problem is very difficult if op-amp is non-ideal:



(Q:) What happens if $V_o \in [-0.6, 0.6]$?

in other words, can you come up with a simple circuit model for T ?

A: open-circuit

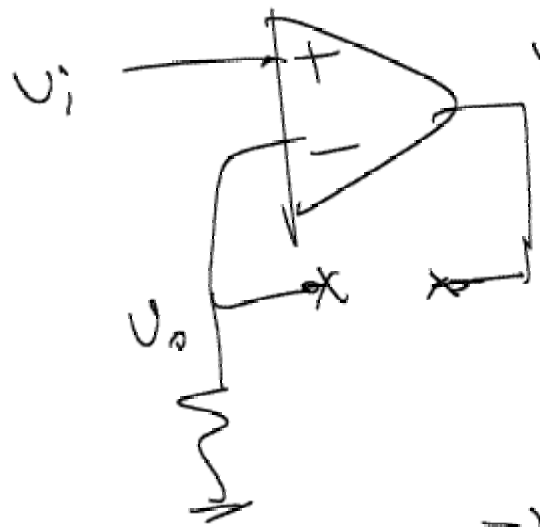

v_a ← in reality, this
 what happens if
 v_i is very small,
 transistors are open circuited

$$\Rightarrow v_a = A (v_i - v_o)$$

Huge! (10^6)


$$\text{Now, } v_o = 0 \text{ V}$$

$$\therefore v_a = 10^6 v_i \quad \text{if } v_i \approx 0.1 \mu\text{V,}$$

$$v_a = .1 \text{ V}$$

\Rightarrow SHOOT OUT OF NONLINEARITY.

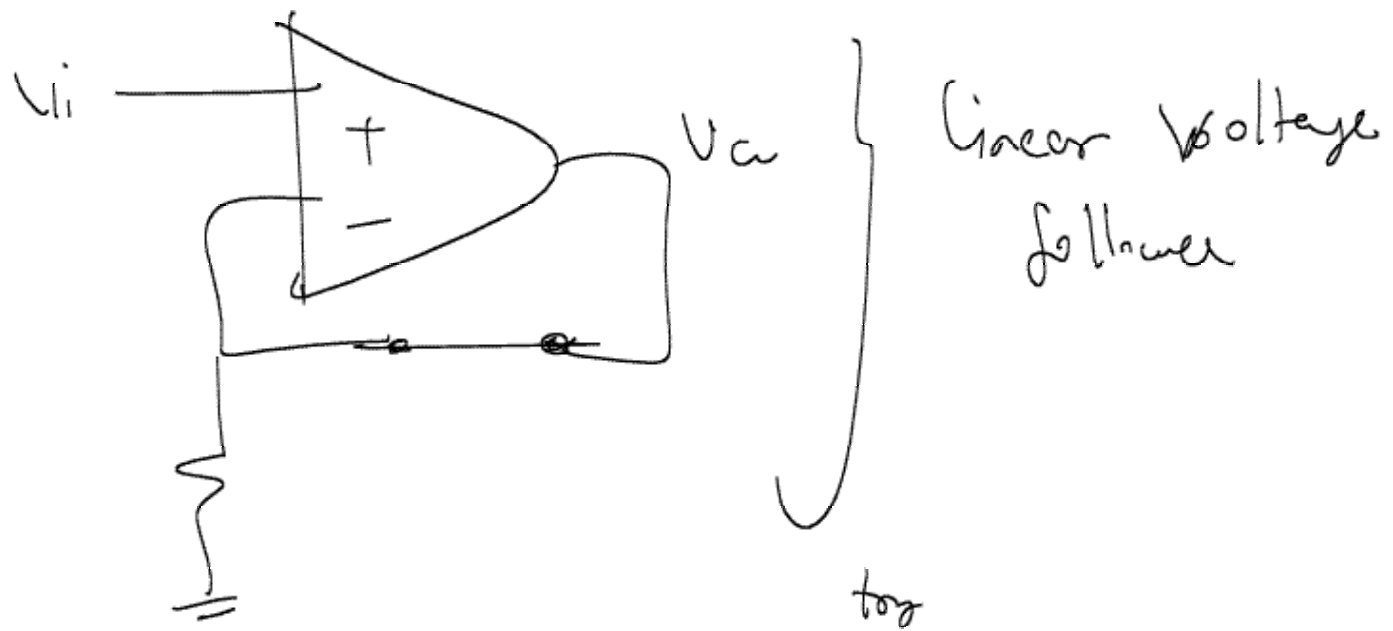If $V_a > 0.6$ 2 $V_a < -0.6 \Rightarrow V_a = V_i$



M. B. I. Don't think too hard \Rightarrow ^{too} simple circuits first!

K. I. S. S \Rightarrow keep it simple stupid.
