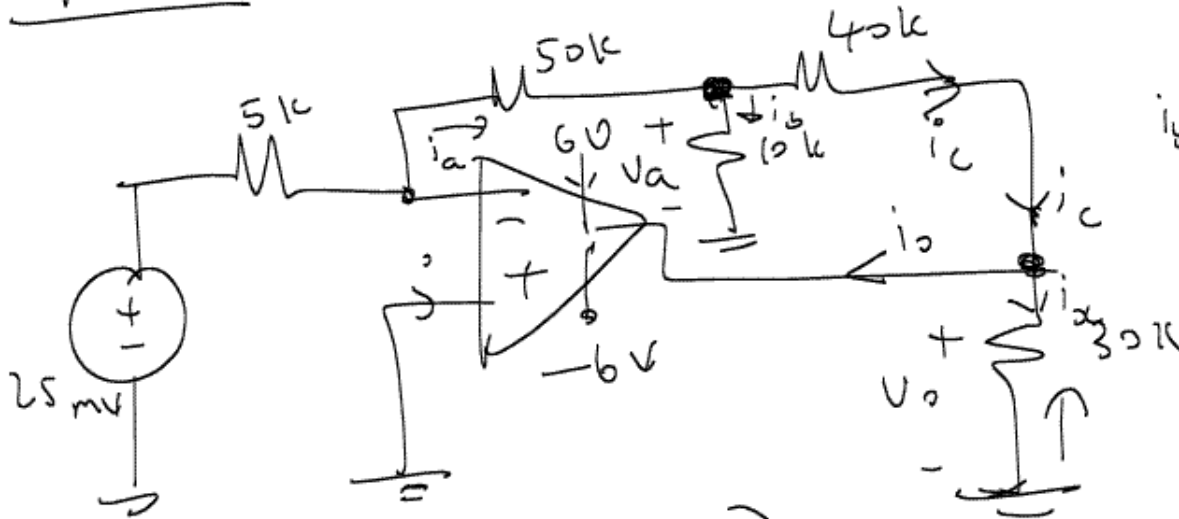


Chapter 5

(5.5)



Inverting amplifier

$$i_b = \frac{v_a}{10k} \checkmark$$

$$i_a = \checkmark$$


$$i_c + i_o = i_a$$


$$\Rightarrow i_c = \checkmark$$

$$V_o = \checkmark$$

$$i_a = \frac{V_o}{30k}$$
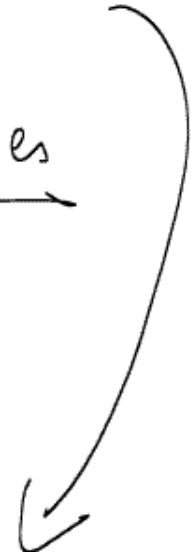
$$\textcircled{i_o + i_c = i_c} \checkmark \checkmark$$



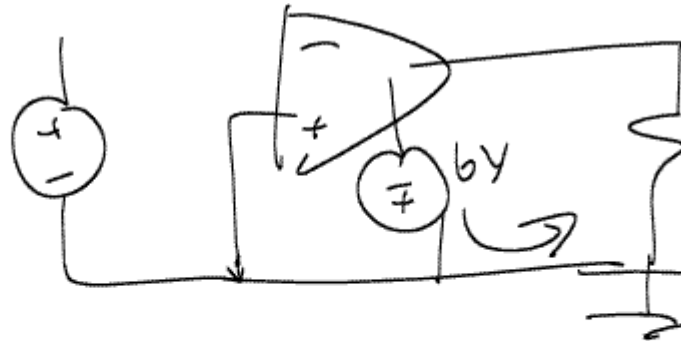


Q: Is output voltage unaffected by load (i.e. resistance) at the output?

A: Ideally: No, unaffected
 (world of the tablet PC, blackboard etc)

Non-ideality: IT MATTERS!!!!


Ex: Your audio project

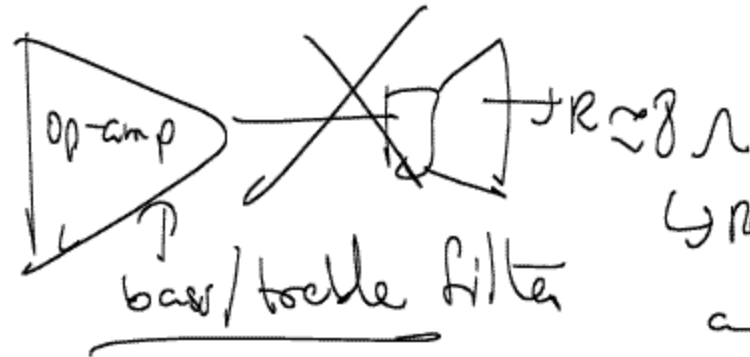


↳ Resistance of a speaker is too low

⇒ too much current from op-amp output.

Solution:

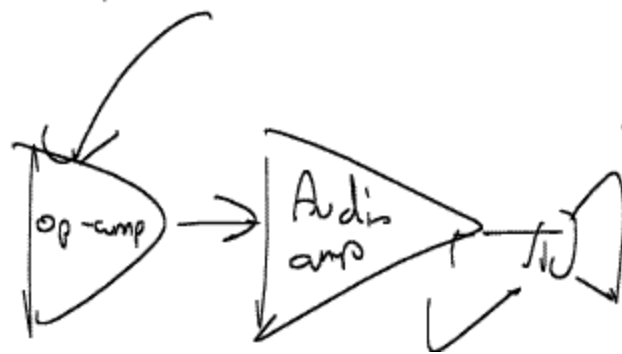

(5.11)

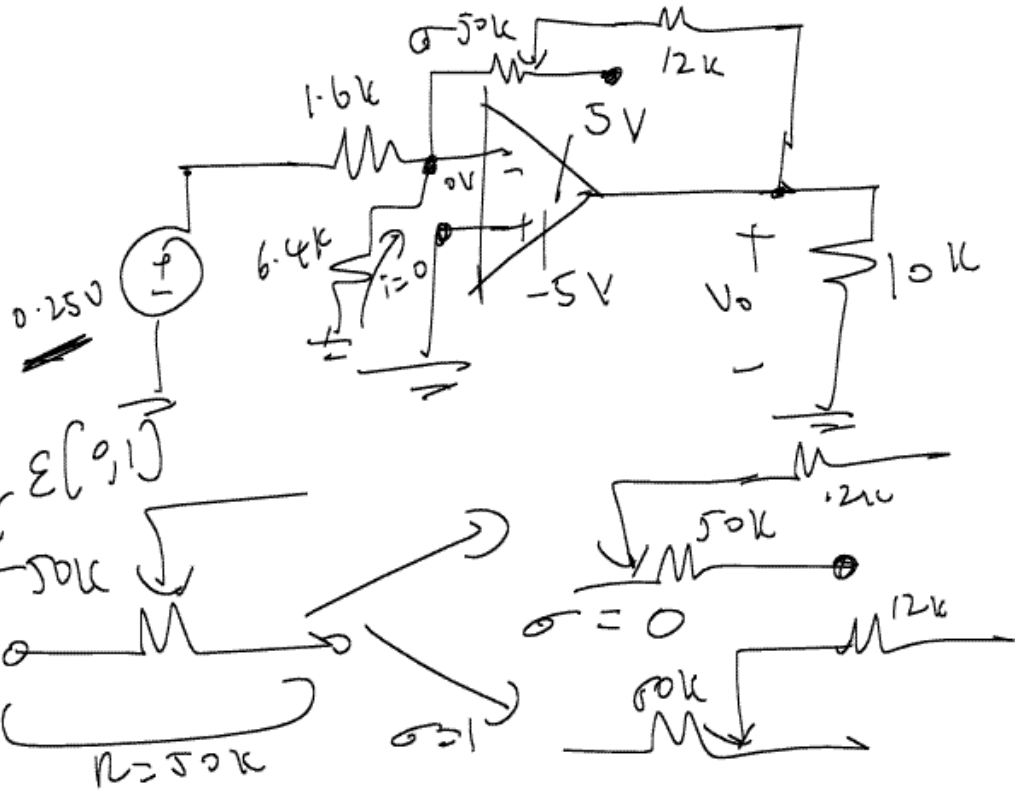


Note! Circuit symbol for potentiometer

(variable resistor) →


→ old school

(Q:) What resistors are important in amplifiers?

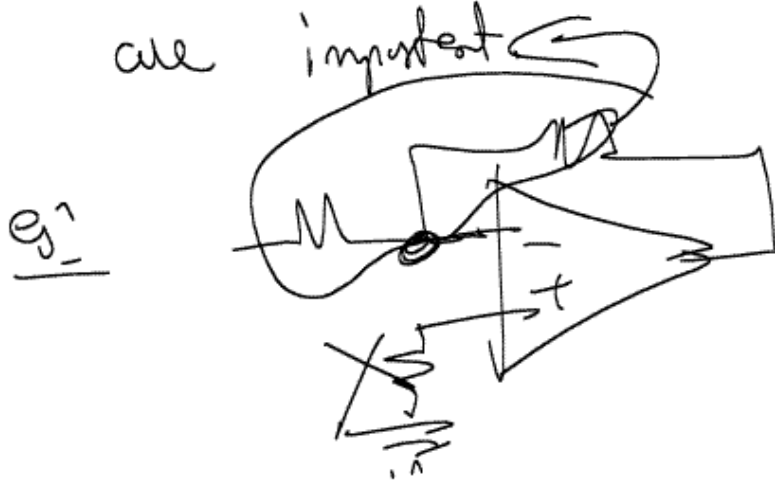A: Hard to say, usually ^{resistor connected} feedback paths are important



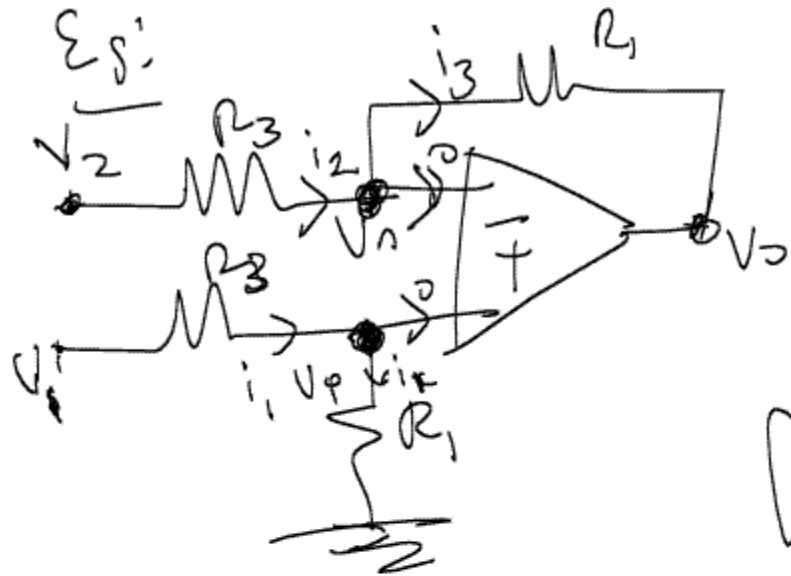Sometimes, you can't even tell if amplifier is inverting/noninverting.





Find $V_o = f(V_1, V_2)$.

Don't worry
about rails
(i.e., assume op-amp never
saturates)

Step (1)

Op-amp is linear: $V_n = V_p$

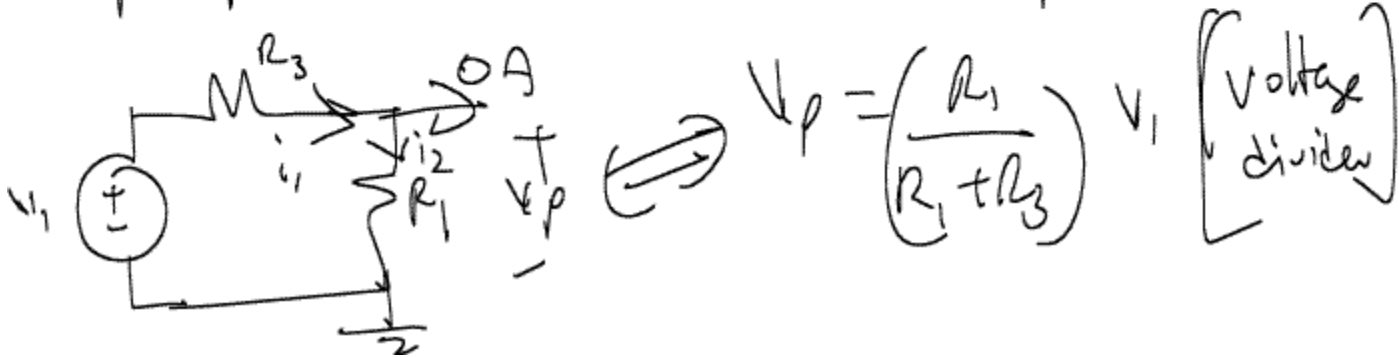

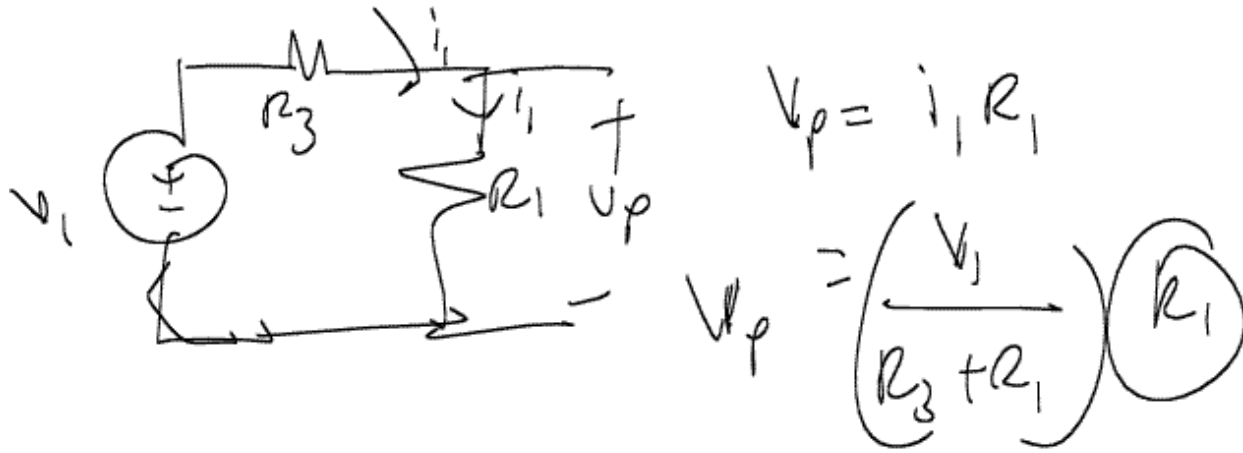

$$v_1 = \left(\frac{R_1}{R_1 + R_3} \right) v_1$$

Step 2: KCL @ v_n :

$$i_2 = i_3 \Rightarrow \frac{v_2 - v_n}{R_3} = \frac{v_n - v_o}{R_1}$$

$$\Rightarrow V_2 - V_0 = \frac{R_3}{R_1} (V_0 - V_0)$$

$$\Rightarrow V_2 - \left(\frac{R_1}{R_1 + R_3} \right) V_1 = \frac{R_3}{R_1} \left(\frac{R_1}{R_1 + R_3} V_1 - V_0 \right)$$

$$\Rightarrow V_2 - \frac{V_1 R_1}{R_1 + R_3} = \frac{R_3}{R_1 + R_3} V_1 - \frac{R_3}{R_1} V_0$$


$$\Rightarrow \frac{R_3}{R_1} V_0 = \frac{R_3 V_1}{R_1 + R_3} + \frac{R_1 V_1}{R_1 + R_3} - V_2$$

$$\frac{R_3 V_o}{R_2} = \frac{R_3 v_1 + R_1 v_1 - (R_1 + R_3) v_2}{R_1 + R_3}$$


Simplicity: $R_1 = R_3 = R$

$$\therefore V_o = \frac{R v_1 + R v_1 - 2R v_2}{2R}$$

$$V_o = v_1 - v_2$$

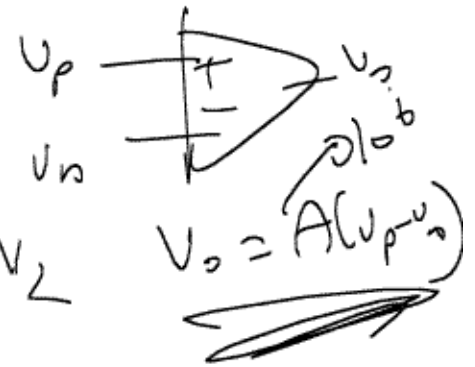

H.W #1 Addition

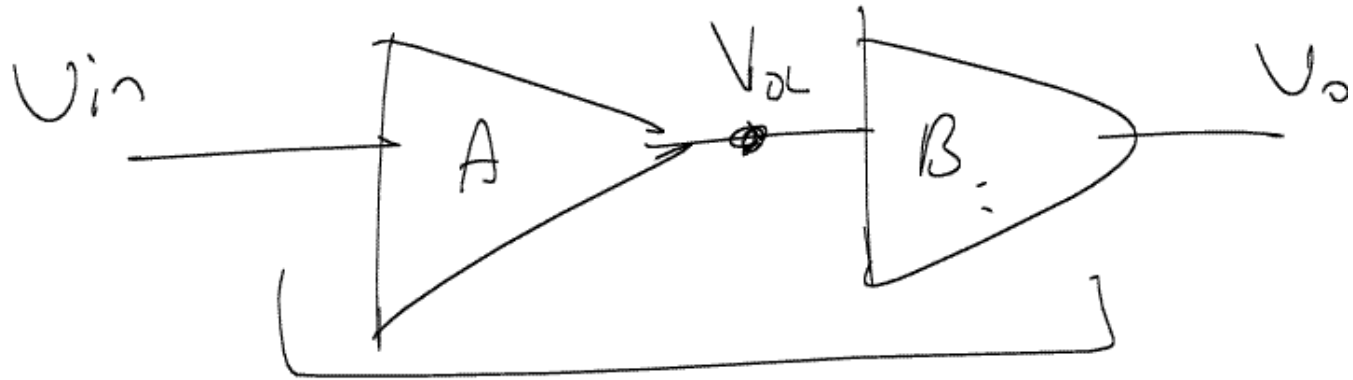


$$V_o = \underline{A \cdot B} V_{in}$$

$$V_x = \underline{A V_{in}}$$

$$V_o = B \cdot V_x$$

$$V_o = B [A V_{in}] \xrightarrow{\downarrow} \boxed{V_o / V_{in} = BA}$$

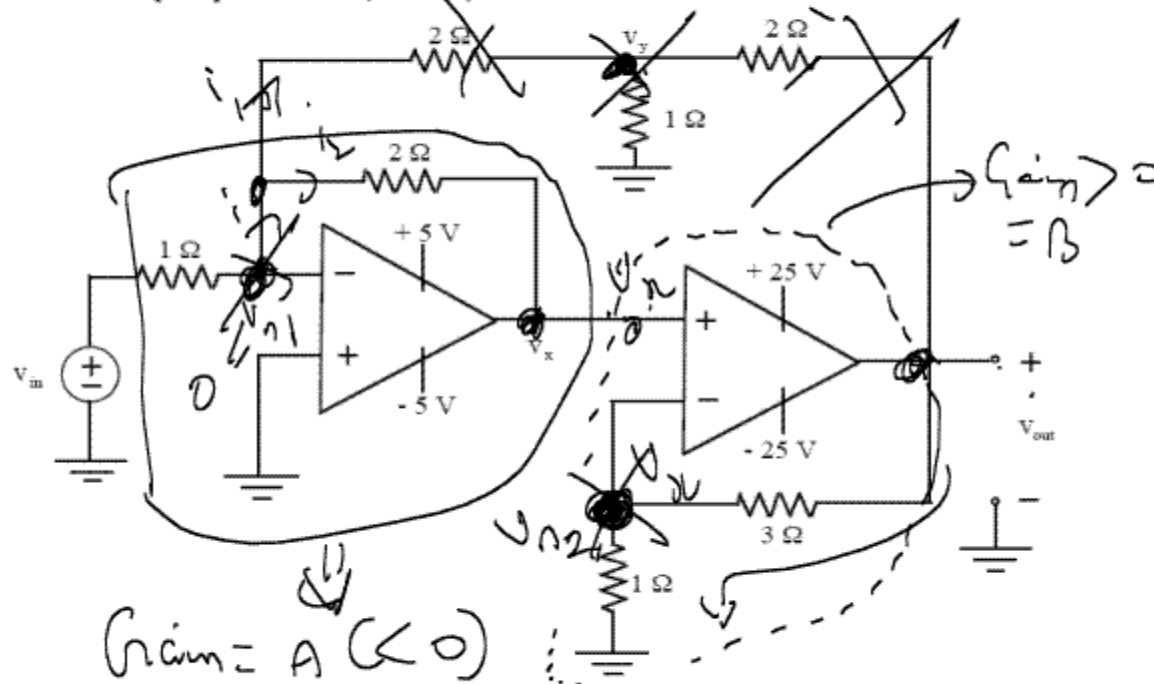loop gain for both op-amps is infinite ($A = \infty$).



a.) Is the above circuit inverting or non-inverting? Answer this by inspection only. Explain your logic.


(b) write KCL @ V_{n1} , V_y & V_{n2}

$$\begin{aligned} \text{KCL @ } V_{n1}: \quad \frac{V_{in} - 0}{L_2} &= i_1 + i_2 \\ &= \left(\frac{0 - V_y}{2} \right) + \left(\frac{0 - V_{n2}}{2} \right) \end{aligned}$$

KCL @ V_y : Relationship between V_y & V_{out}

KCL @ V_{n2} : Relationship between V_{out} & V_y
 $V_{out} = f(V_{in})$

(33)

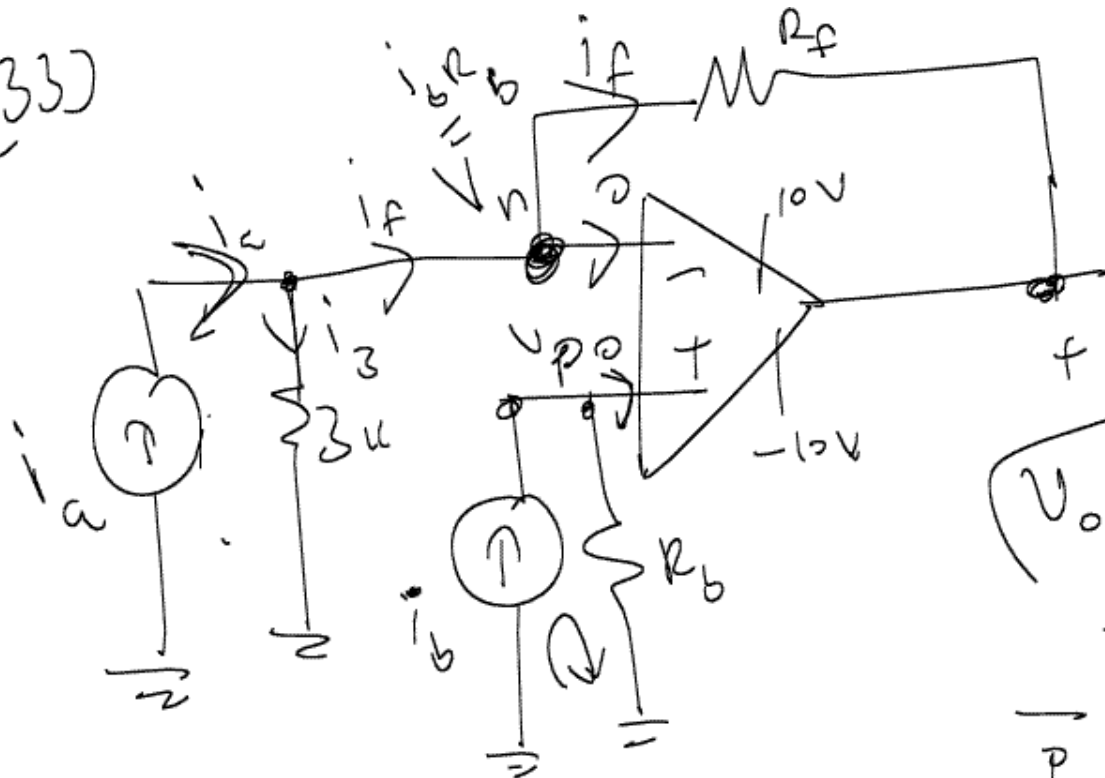

$$V_o = 2000 (i_b - i_a)$$

$$V_n = i_a (3\mu)$$

$$V_p = i_b (R_b)$$

Assume op-amp is ideal \Rightarrow $V_n = V_p = i_b (R_b)$


$$V_n = V_p = i_b (R_b)$$

$$i_3 = \frac{V_p}{3k} = \left(\frac{i_b R_b}{3k} \right) \quad ; \quad i_f + i_3 = i_a$$

$$i_f = i_a - \left(\frac{i_b R_b}{3k} \right) \quad \text{---} \quad i_f = \frac{V_p - V_o}{R_f}$$


$$= \frac{i_b R_b - V_o}{R_f}$$

(25)

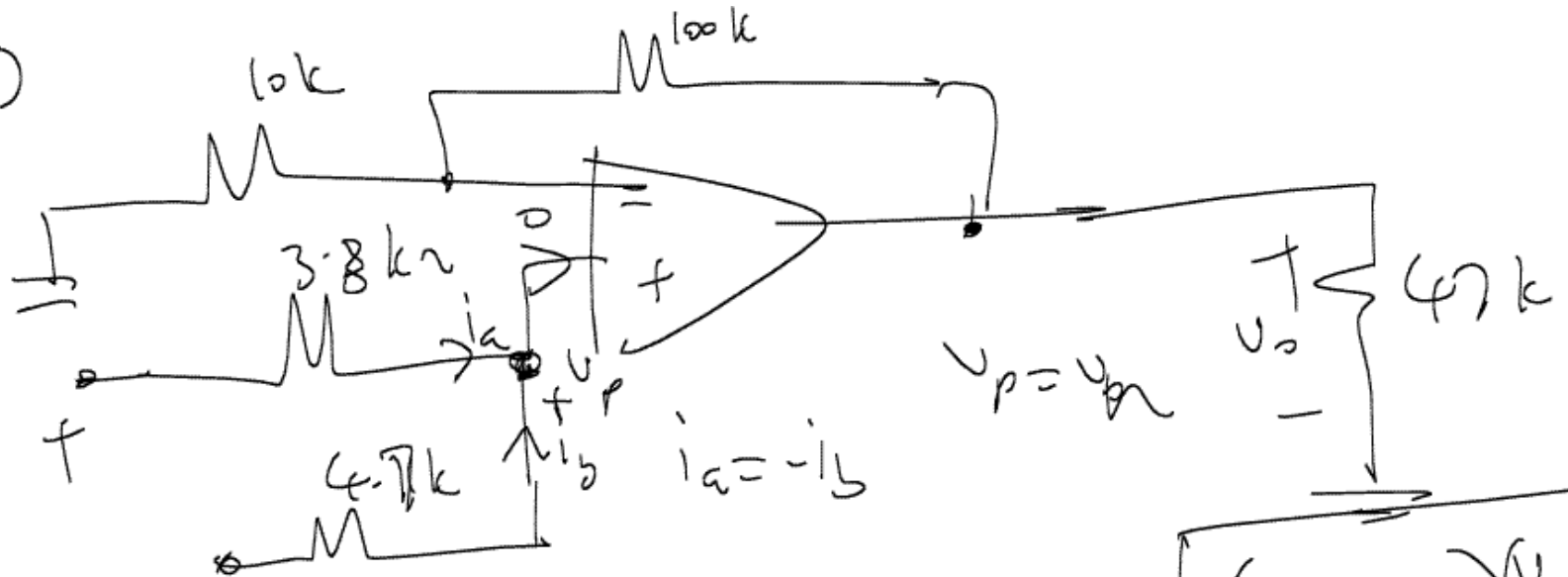

v_a
+
 v_b
-

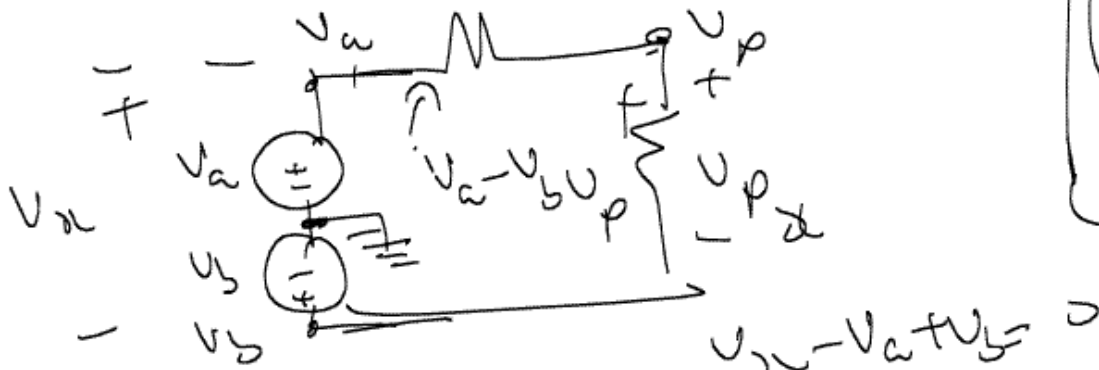But, $v_p = \left(\frac{4.7k}{4.7k + 3.8k} \right) (v_a - v_b) + v_b$



$$\therefore V_n = \left(\frac{4.7k}{8.0k} \right) (V_a - V_b) + V_b$$

$$\Rightarrow V_n = 0.5875 V_a + 0.4125 V_b$$

KCL @ V_n :

$$V_b = f(V_a + V_b)$$

$$\approx \alpha V_a + \beta V_b$$

$$\frac{0 - V_n}{10k} = \frac{V_n - V_b}{100k}$$

$$\Rightarrow V_n - V_o = 10 \cdot (-V_n)$$

$$\Rightarrow V_n = V_o$$

$$V_o = \frac{1}{1} \left(\frac{4 \cdot 1k}{8 \cdot 0k} \right) (V_a - V_b)$$

$V_a + V_b$