

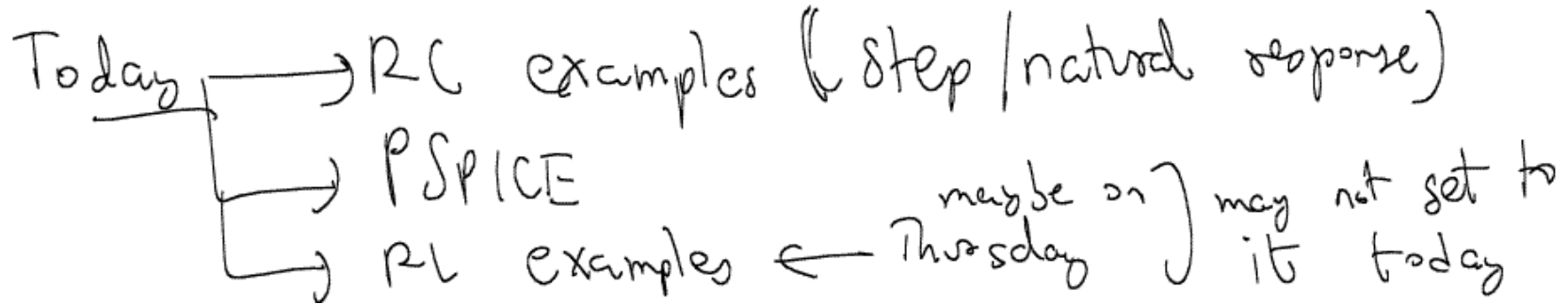


Lecture 11 - Chapter 7 Examples

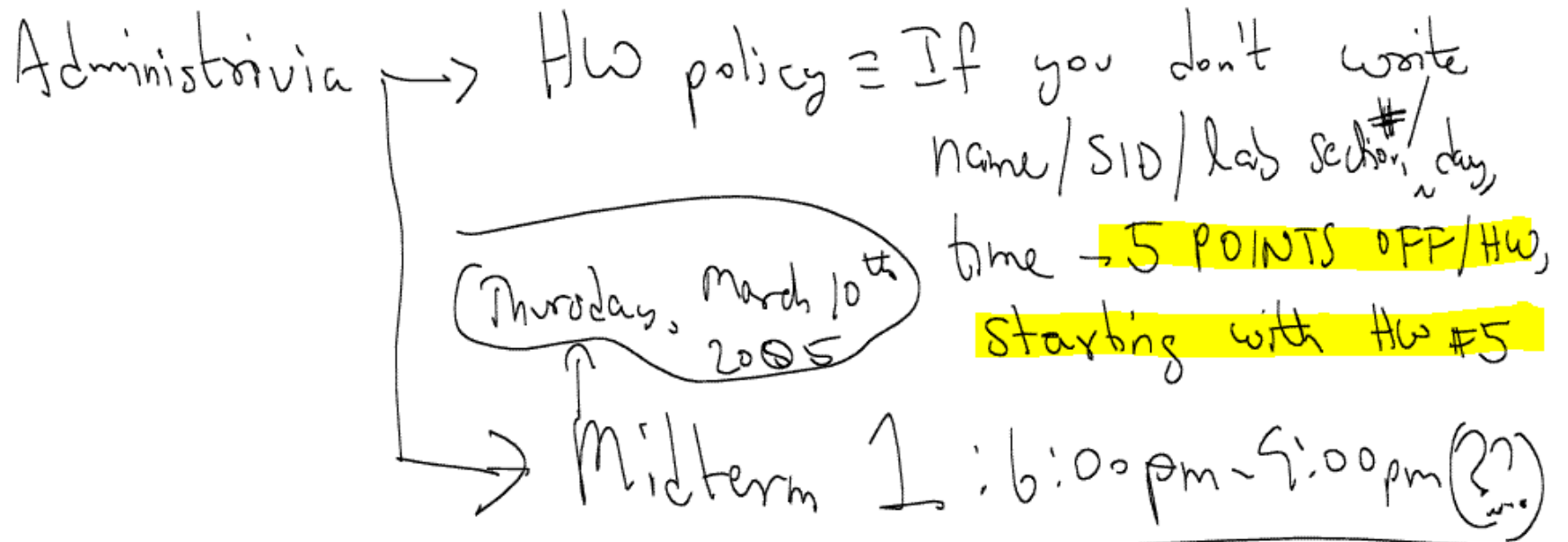


Recall:

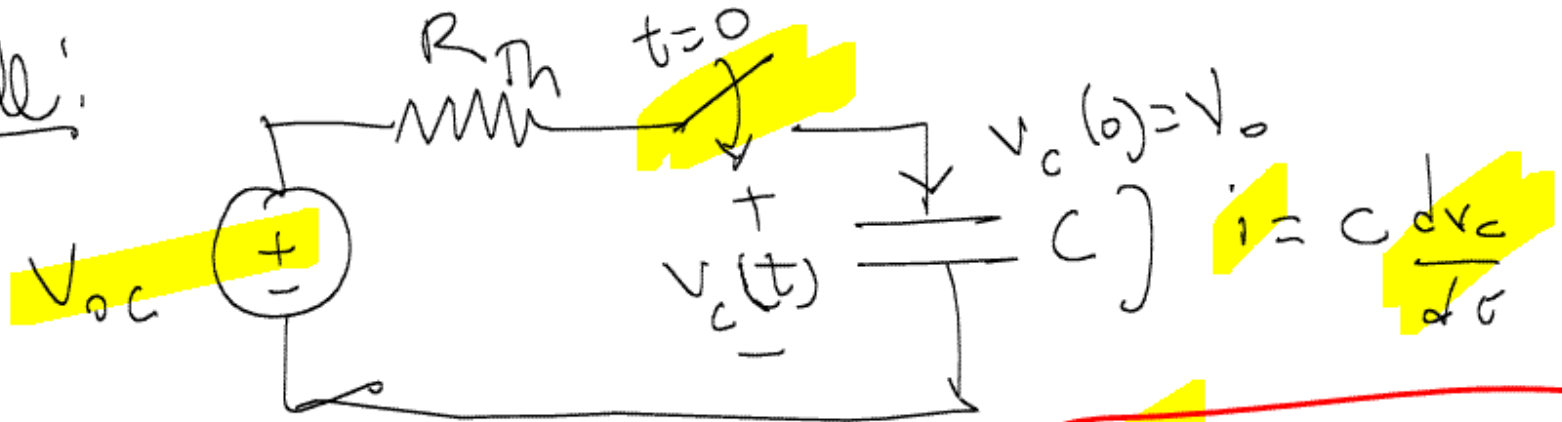


$$V_c(t) = V_{oc} + (V_0 - V_{oc}) e^{-\frac{t}{R_{Th}C}}$$

τ (time constant)

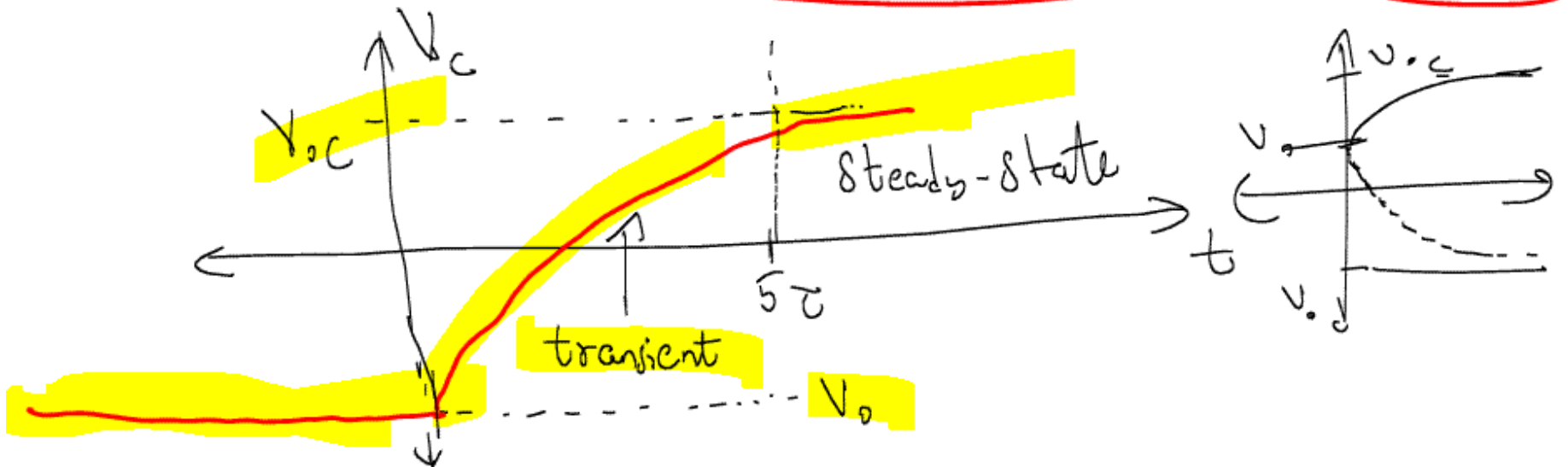

(p. 289)
 Example 7-8:


(a) Find $i(t)$, $v(t)$
 $(t > 0)$



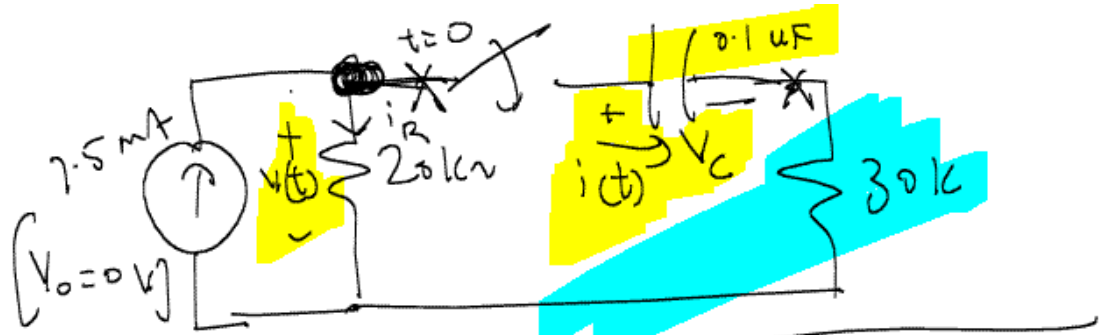


We will solve the circuit the difficult way first, find voltage across the capacitor & then use it to find $v(t)$, $i(t)$

$$V_c(t) = V_{oc} + (V_0 - V_{oc})e^{-\frac{t}{R_{th}C}}$$

$V_0 = 0$ V
 (initial voltage)

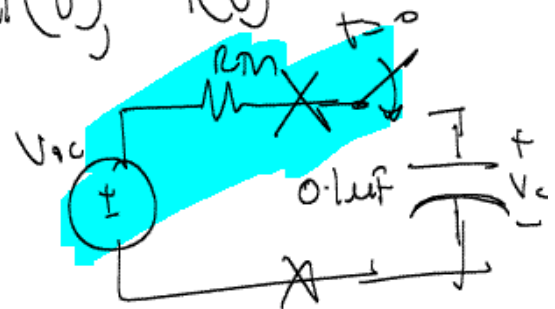

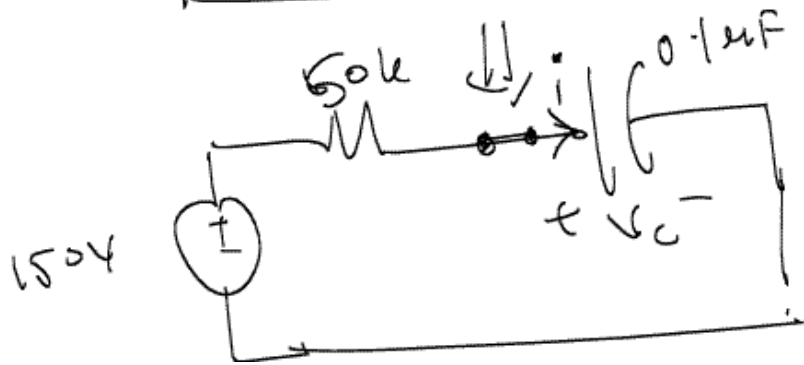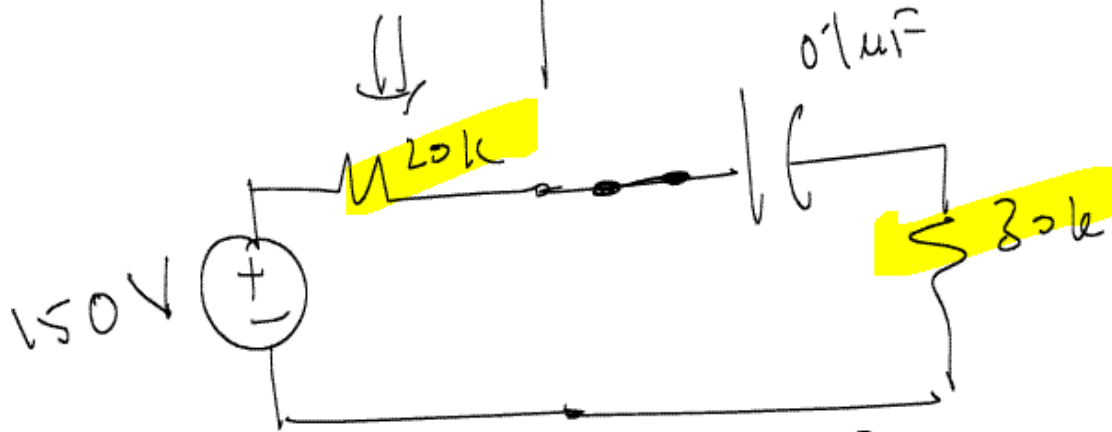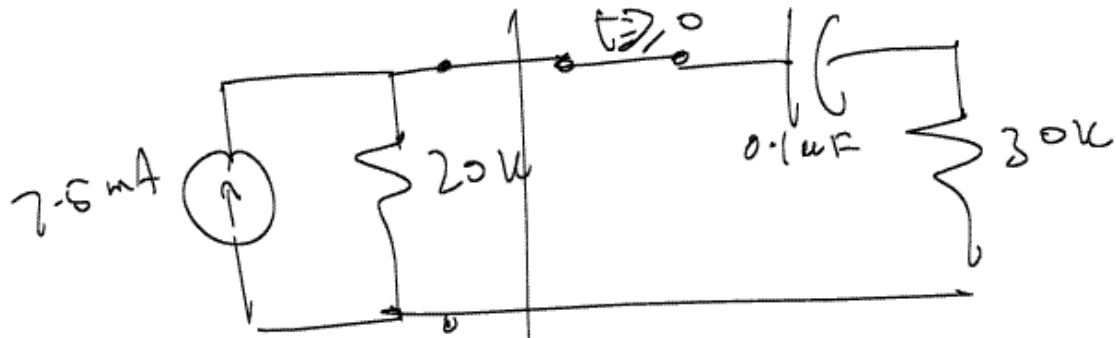

$$\begin{aligned}
 v_c(t) &= v_{oc} + (v_o - v_{oc}) e^{-\frac{t}{\tau}} \\
 &= v_{oc} (1 - e^{-\frac{t}{\tau}})
 \end{aligned}$$

$$V_{OC} = 150 \text{ V}$$

$$\tau = R_m C = (50 \text{ k}) (0.1 \mu)$$

$$\tau = 5 \text{ ms}$$


$$V_C(t) = 150 \left(1 - e^{-\frac{t}{5 \text{ ms}}}\right) \text{ volt}$$




Note: Why V_{OC} ?

Because as $t \rightarrow \infty$
 capacitor is fully charged

i.e., V_C is constant

$$\therefore i = C \frac{dV_C}{dt} = 0$$

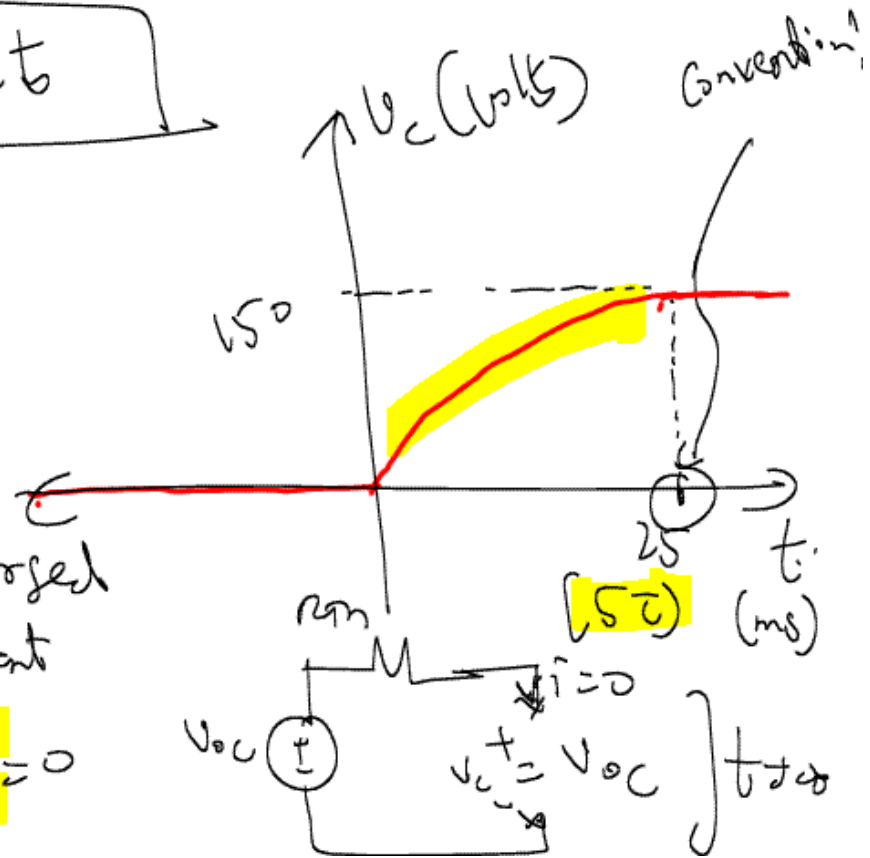

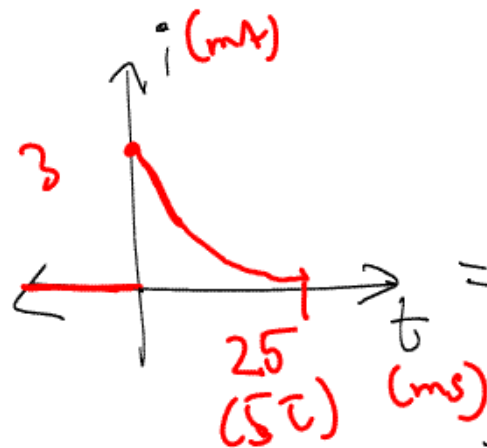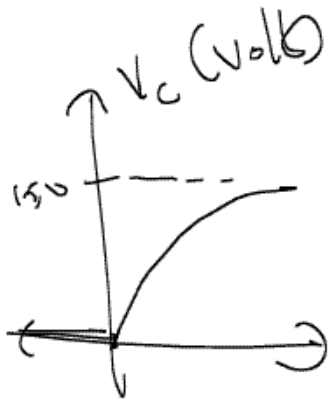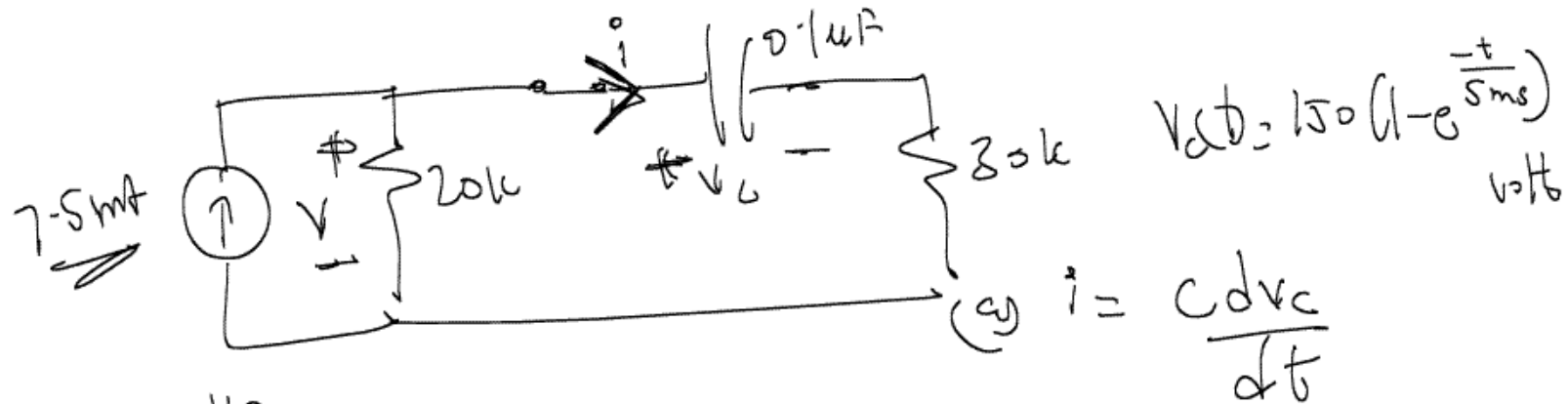

$$= (0.1 \mu) 150 \left[-e^{-\frac{t}{5ms}} \cdot -1 \right]$$

$$= 15 e^{-\frac{t}{5ms}} \text{ mA}$$


$$= 3 e^{-\frac{t}{5ms}} \text{ mA}$$

Notice:

(1) Voltage across a capacitor is continuous, ~~cannot~~ usually isn't. This is because $i = C \frac{dv}{dt} \rightarrow$ cannot change instantaneously

(2) Notice $i_C(t)$ is also an exponential with the same time constant!

We still have to find i_C

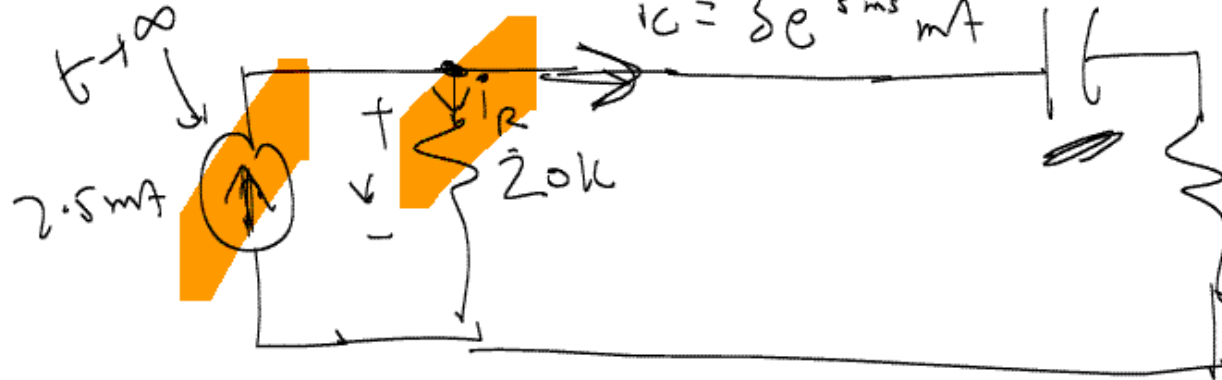

KCL: $7.5 \text{ mA} = i_R + i_C$
 $\Rightarrow i_R(t) = \left(7.5 - 3e^{-t/5 \text{ ms}} \right) \text{ mA}$

$$v(t) = (i_R)(20k) = (2.5 - 3e^{-\frac{t}{5ms}})(20k) \text{ mV}$$

$$v(t) = 150 - 60e^{-\frac{t}{5ms}} \text{ V}$$


"Easier" way to solve transient problems

$$f(t) = f_{\text{final}} + (f_{\text{initial}} - f_{\text{final}}) e^{-\frac{t}{\text{circuit time constant}}}$$

\swarrow $R_m C$ \searrow V/R_m

Example 7-8 is worked out using the method above; i.e., find final value(s), initial value(s) & time constant.

(p. 16), p. 308

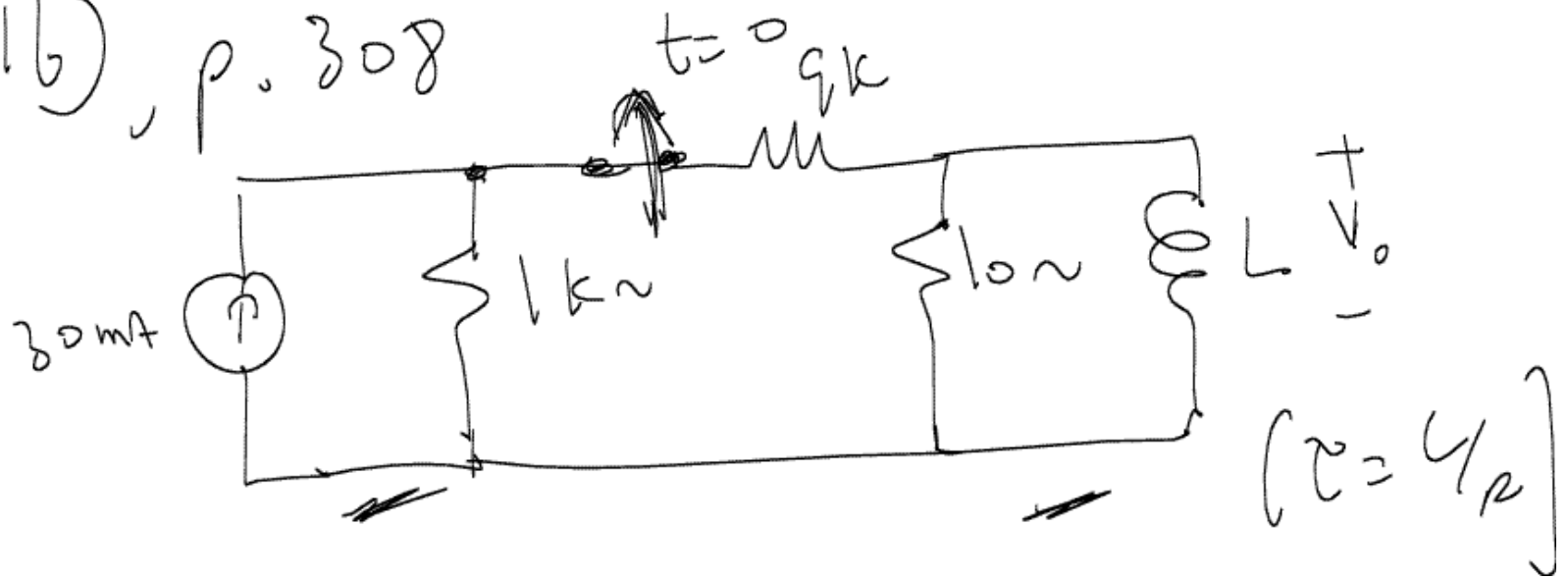

(Q:1) (a) Find value of L so that $V_o(t)$ equals $0.5 V_o(0^+)$ at $t = 1 \text{ ms}$

Note: (1) Inductors are "ducks" of capacitor

i.e.. Voltage is continuous in RC circuits,
Current is continuous in RL circuits
 $[V = L \frac{di}{dt}]$

(2) $t = 0^+$ means the "instant after" the switch is pushed.

i.e., RC: $V_{\text{capacitor}}(t=0^-) = V_{\text{capacitor}}(t=0^+)$

RL: $i_{\text{inductor}}(t=0^-) = i_{\text{inductor}}(t=0^+)$

Sol: $V_{\text{out}}(t) = V_{\text{out, final}} + (V_{\text{out, initial}} - V_{\text{out, final}}) e^{-t/\tau}$


$\tau = \frac{L}{R}$ ← unknown.

Given: $V_0(t=1\text{ms}) = \frac{1}{2} V_0(0^+)$

$$V_0(t=1\text{ms}) = \frac{1}{2} V_{0\text{initial}} \quad -t/\tau$$

$$\Rightarrow V_{0\text{final}} + \underline{\underline{(V_{0\text{initial}} - V_{0\text{final}}) e^{-t/\tau}}} = \frac{1}{2} V_{0\text{initial}}$$

$V_{o\text{ final}} = ?$

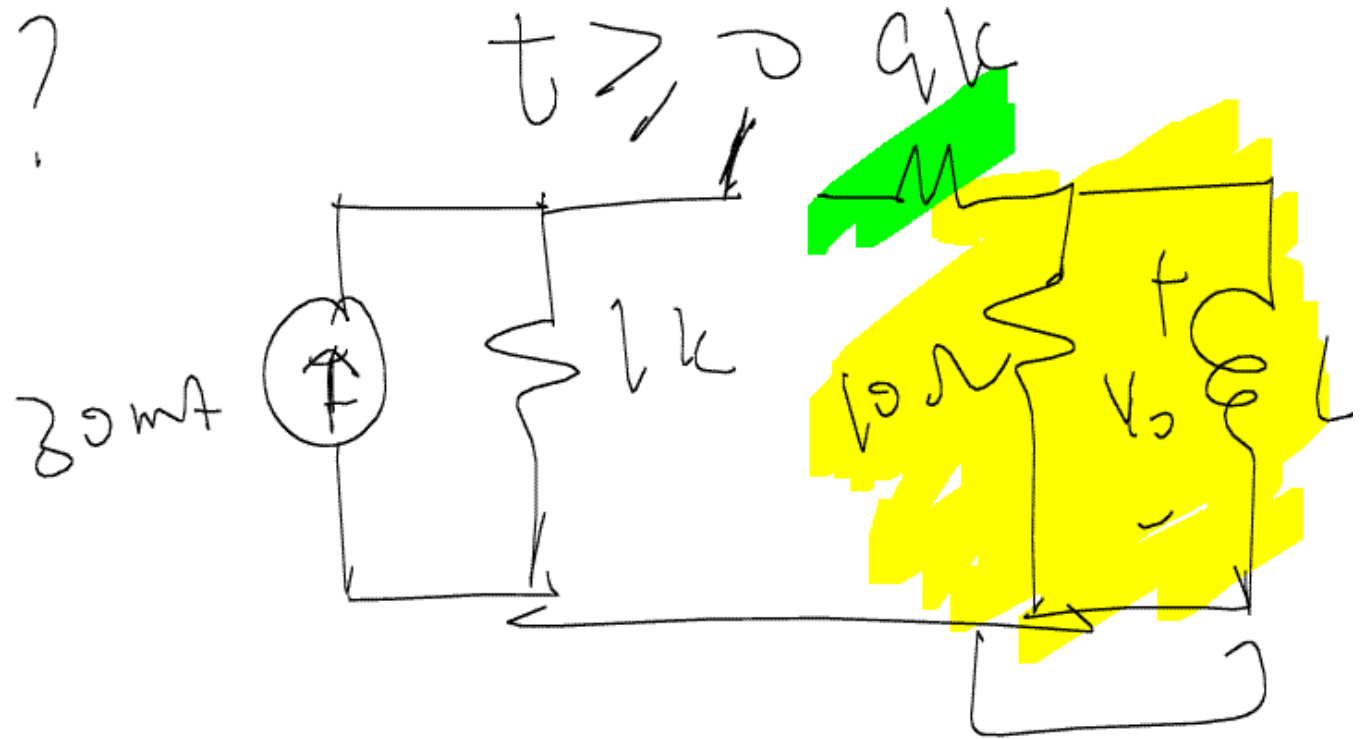

$\therefore V_{o\text{ final}} \rightarrow 0\text{ V}$

$\therefore V_o(t) = 0 + (V_{o\text{ initial}} - 0)e^{-t/\tau}$

inductor fully discharges

$$\begin{array}{c}
 \text{V}_{\text{initial}} \text{ @ } \frac{-t}{\tau} \Big|_{t=1\text{ms}} \\
 \hline
 \text{V}_{\text{initial}} \\
 \downarrow \\
 \text{V}_0 (e^t)
 \end{array}
 =
 \begin{array}{c}
 \text{V}_{\text{initial}} \\
 \downarrow \\
 \text{V}_0 (e^t)
 \end{array}$$

$$\Rightarrow \frac{-t}{\tau} = \ln\left(\frac{1}{2}\right)$$

$$\frac{-t \geq 1\text{ms}}{\tau_{R_{Th}}} \approx -0.693$$

$$\Rightarrow \frac{\frac{1 \text{ ms}}{L}}{10^2} = -0.693$$

$$\Rightarrow \frac{(-1 \text{ ms})(10^2)}{L} = -0.693$$


→

$$L = \frac{10 \text{ mH}}{0.693}$$

Midterm] spoiler (sorry TAs)



(Q1) Find v_x

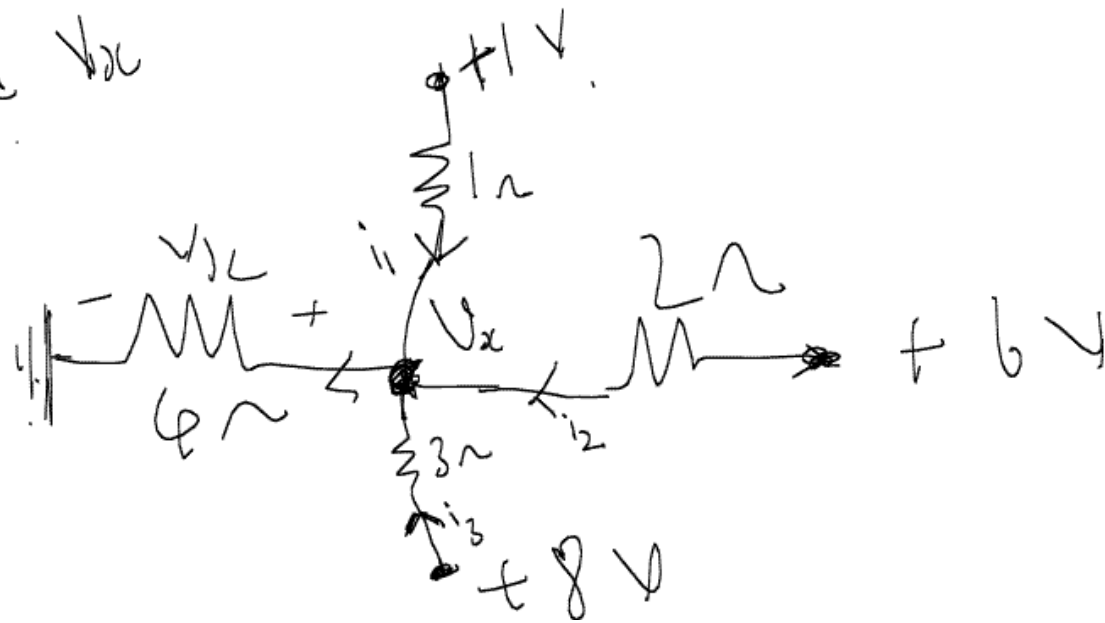

KCC, $i_1 + i_2 + i_3 = i_4$

$\Rightarrow \left(\frac{5 - V_{oc}}{1 \sim} + \frac{6 - V_{oc}}{2} + \frac{8 - V_{oc}}{3} = \frac{V_{oc}}{4} \right)$

Next time \rightarrow More RC/RL examples