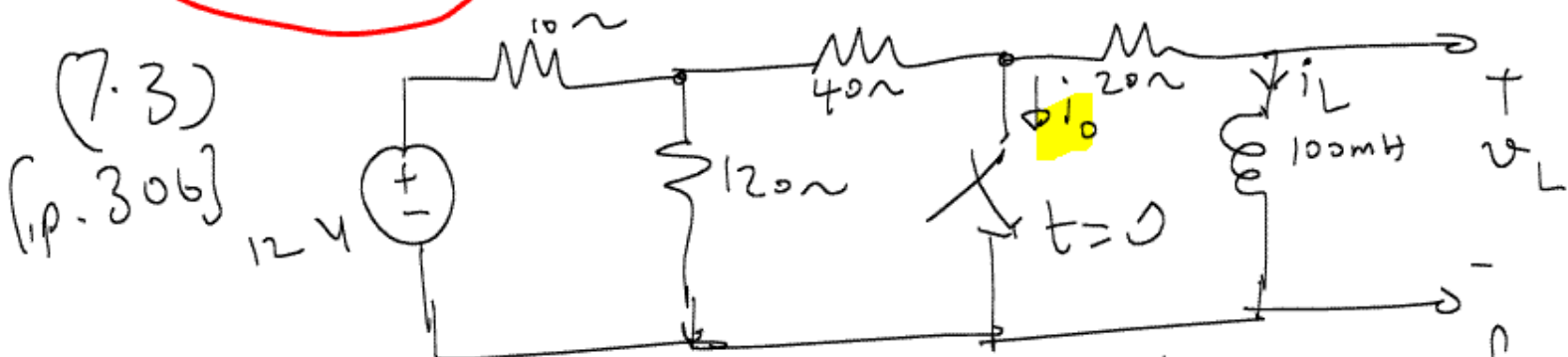


# lecture 12 - More chapters 7 examples

Administrivia: Lab next week: RC Circuits  
Midterm from 6:00-9:00 on Thursday??

**BY FRIDAY!**  
(tomorrow)

check Google groups (under MIDTERM 2)



Q: Switch is closed after being open for a long time


- (a) Find  $i_o(0^-)$  (instant before switch closes)
- (b) Find:  $i_L(0^-)$  (c)  $i_o(0^+)$  (d)  $i_L(0^+)$  (e) Find  $i_o(t \rightarrow \infty)$
- (f) Find  $i_L(t \rightarrow \infty)$  (g)  $i_L(t), t \geq 0$  (h)  $v_L(0^-), v_L(0^+)$
- (i)  $v_L(t \rightarrow \infty)$ , (k)  $v_L(t), t \geq 0$  (j)  $i_L(t), t \geq 0$
- Key:  $f(t) = f_{\text{final}} + (f_{\text{initial}} - f_{\text{final}}) e^{-t/\tau} \left[ \tau = \frac{L}{R} \right]$

Step (1): Draw three circuits, at  $t = 0^-$  (instant before switch closes)

$$L \frac{di}{dt} = V \Rightarrow i \text{ through an inductor cannot change instantly}$$



$t = 0^+$  (instant after switch closed)  
 $t \rightarrow \infty$

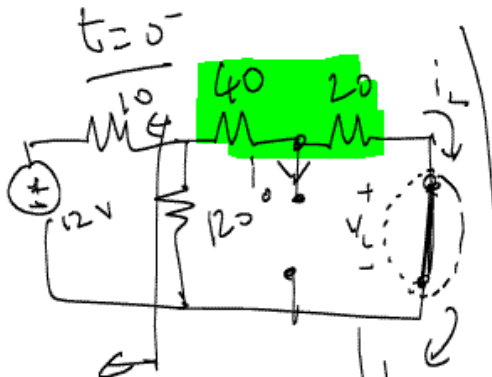as  $t \rightarrow \infty$ ,  $i = \text{constant} \Rightarrow V \rightarrow 0$




$i_o(0^-) = 0 \text{ A}$   
(open switch)

$V_L(0^-) = 0 \text{ V}$   
 $i_L(0^-)$

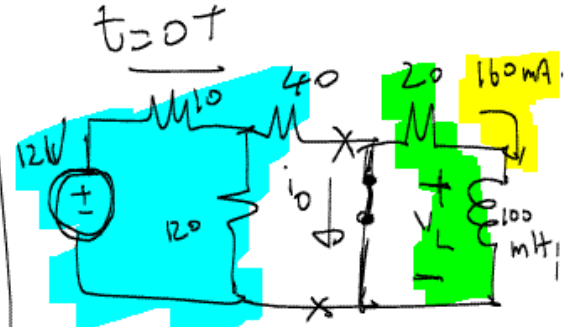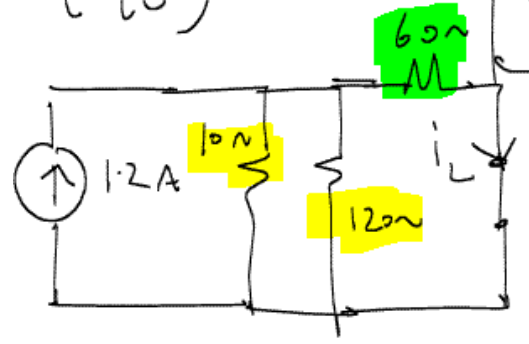


$i_L(0^-) = i_L(0^+)$

$i_L(0^+) = 160 \text{ mA}$

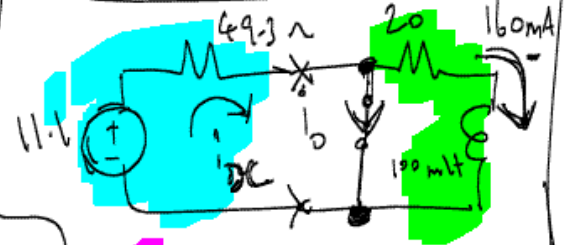


$i_{sc} = \frac{11.1}{49.3} \approx 225 \text{ mA}$

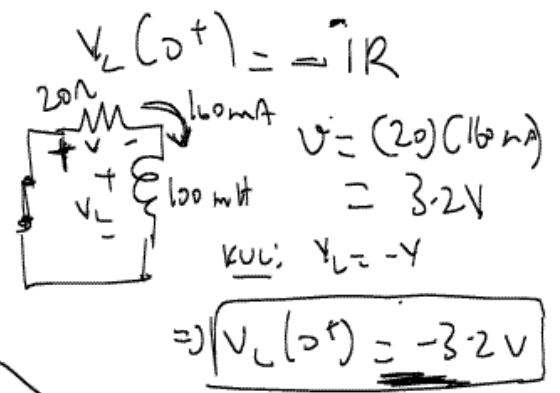$i_{sc} = i_o + 160 \text{ mA}$  (KCL)  
 $\Rightarrow i_o(0^+) = 65 \text{ mA}$



$t \rightarrow \infty$

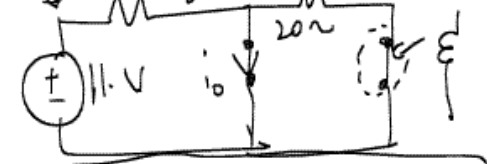
$V_L(t \rightarrow \infty) = 0 \text{ V}$   
 $i_L(t \rightarrow \infty) = 0 \text{ A}$



$i_o(t \rightarrow \infty) = i_{sc} = 225 \text{ mA}$

$$10 \parallel 120 = \frac{10 \cdot 120}{10 + 120}$$

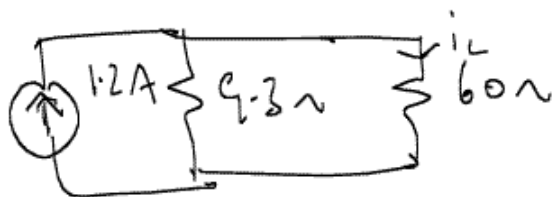
$$= \frac{1200}{130} \approx 9.3 \Omega$$



$$i_L(0^-) = \frac{9.3}{(9.3 + 60)} (1.2)$$

(current divider) = 0.16 A
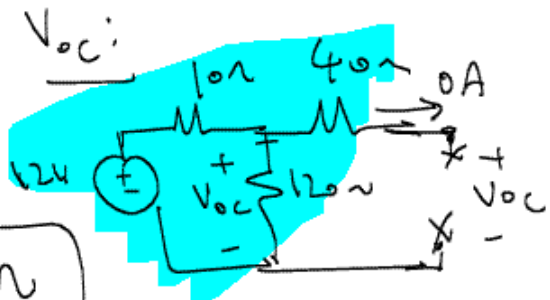
$$\Rightarrow i_L(0^-) = 160 \text{ mA}$$




$$V_{oc} = \left( \frac{120}{120 + 10} \right) 12$$

[voltage divider]



$$\Rightarrow V_{oc} = 11.1 \text{ V}$$

$$R_m = 49.3 \Omega$$

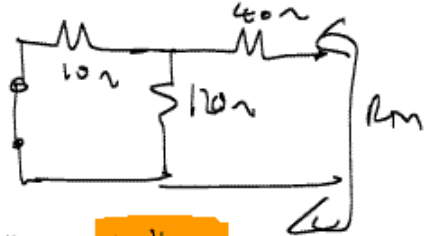


$$R_m = 10 \parallel 120 + 40 = 49.3 \Omega$$

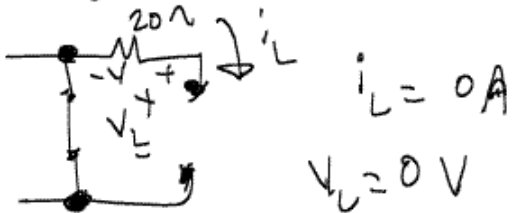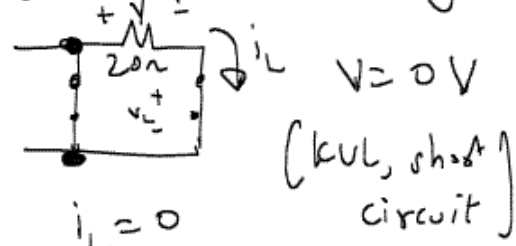Note: What kind of inductor model as  $t \rightarrow \infty$  [i.e., open or short]




KVL:  $V_L = V \Rightarrow i_L(20) = 0$

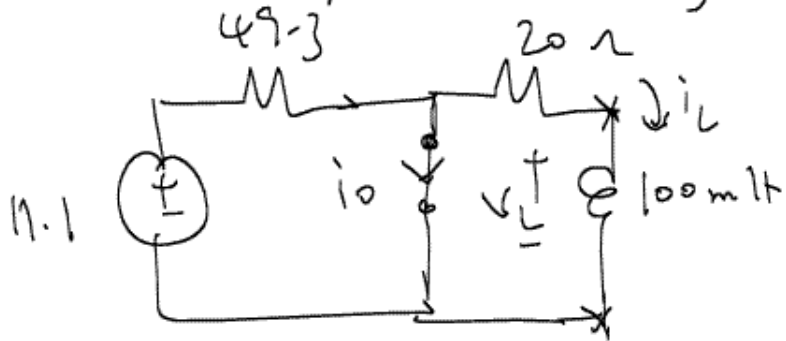What's left?  $\Rightarrow \tau, i_o(t), v_L(t), i_L(t)$


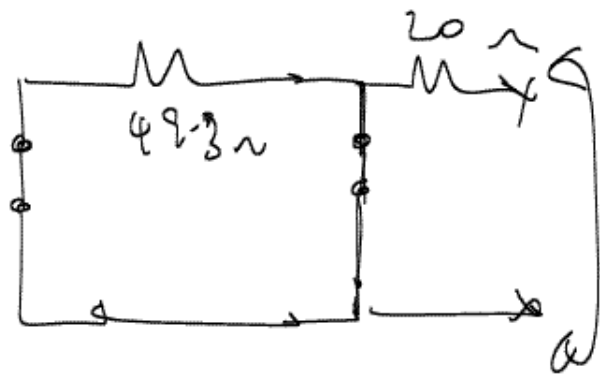
$$\tau = \frac{L}{R_{Th}} = \frac{100 \text{ mH}}{20 \Omega} = \underline{\underline{5 \text{ ms}}}$$



$$i_o = i_{of} + (i_{oi} - i_{of}) e^{-t/\tau}$$

$$R_{Th} = 20 \Omega \Rightarrow i_o = 225 + (65 - 225) e^{-t/5 \text{ ms}} \text{ mA}$$

$$\Rightarrow i_o = 225 - 160 e^{-t/5 \text{ ms}} \text{ mA}, t \geq 0^+$$

$$i_L(t) = i_{Lf} + (i_{Li} - i_{Lf}) e^{-t/\tau}$$

$$i_L(t) = 160 e^{-t/5 \text{ ms}} \text{ mA}, t \geq 0^+$$

$$v_L = v_{Lf} + (v_{Li} - v_{Lf}) e^{-t/\tau}$$

$$\Rightarrow v_L = -3.2 e^{-t/5 \text{ ms}} \text{ V}$$

Note:  $f(t) = f_{\text{final}} + (f_{\text{initial}} - f_{\text{final}}) e^{-t/\tau}$

$$f(t=0) = \cancel{f_{\text{final}}} + f_{\text{initial}} - \cancel{f_{\text{final}}} = f_{\text{initial}}$$

$$f(t \rightarrow \infty) = f_{\text{final}} //$$

---

Next time:  $\rightarrow$  Operational amplifiers 'intro.