

Lecture 17 - Op-amps intro.

Administrivia → (1) No HW this week 😊
(2) Midterms graded!

Today → op-amps intro.
→ pass midterms

Thursday: Justin lecture = op-amps!

Chapter 5 - Operational Amplifiers aka
Op amps.

Caution: Op-amps are difficult to
comprehend (initially). Many reasons, however


PRACTICE PROBLEMS!

Also, concept of
feedback \Rightarrow talk
about this after
SPRING BREAK


5-1 - Introduction

Op-amp

→
Circuit
Symbol

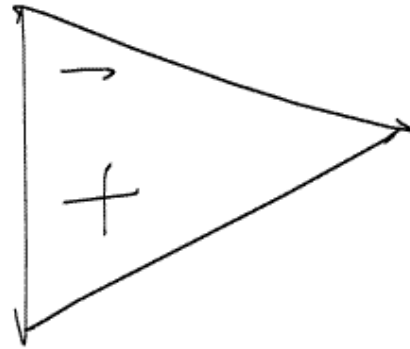

Actually:

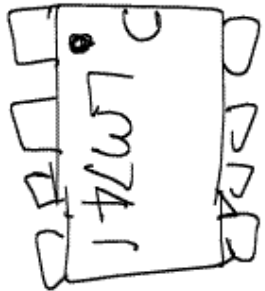


Why op-amps?

are very useful since

we can implement mathematical operations like adders, integrators etc &

amplifiers (voltage, current etc). To understand how op-amps work:

Step 1: Circuit terminology / model

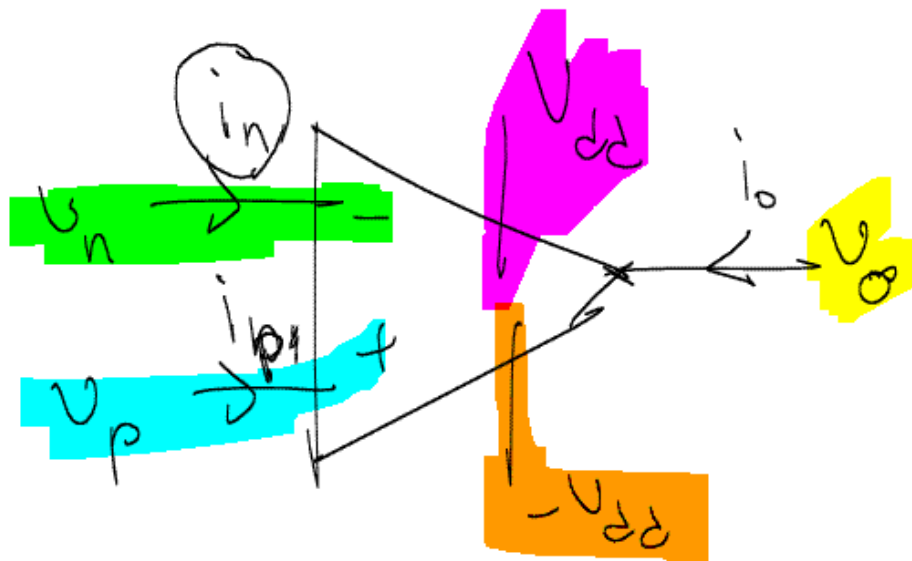

(1) Has three terminals:

(a) Output terminal

(b) inverting terminal


(c) non-inverting terminal

(d) positive rail


(e) negative rail

Note:



Can draw
an op-amp
any way you want

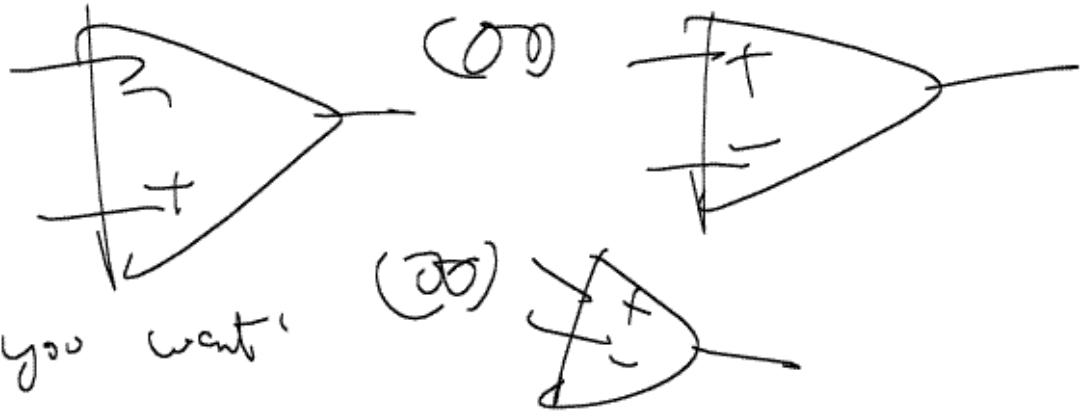

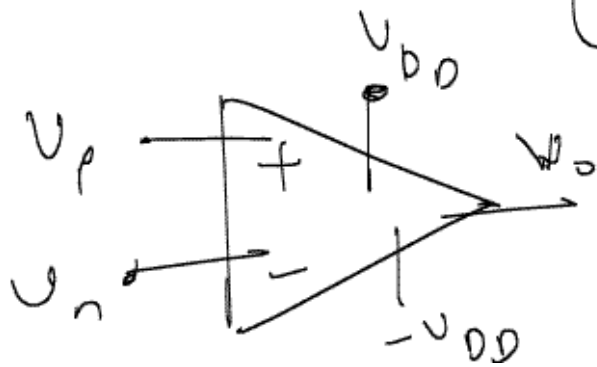① op-amp model: \rightarrow Ideal op-amp model \rightarrow 90% of our time
 \rightarrow non-ideal op-amp model



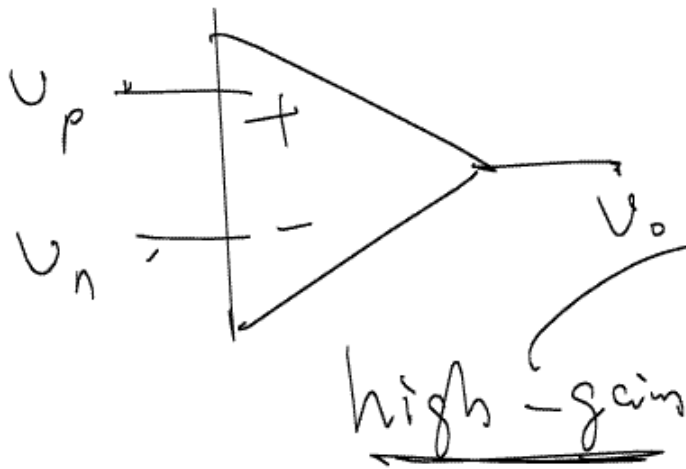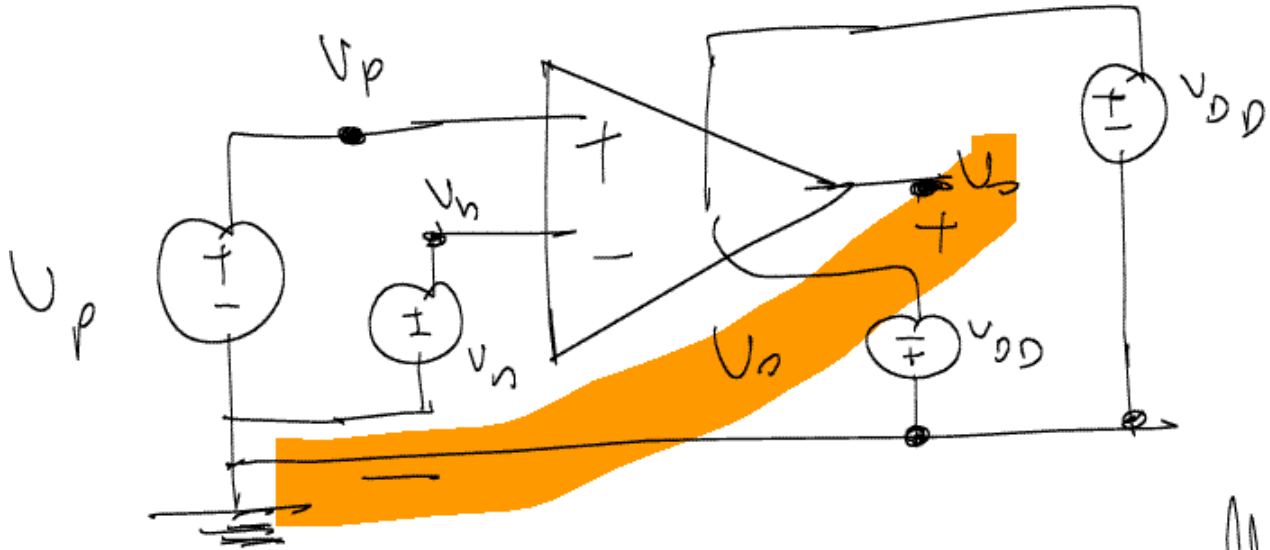Shorthand circuit notation \rightarrow get used to it




$$v_o = A (v_p - v_n) \quad (1)$$


usually 10^6


An op-amp is a high-gain differential amplifier

Why differential amplifiers?

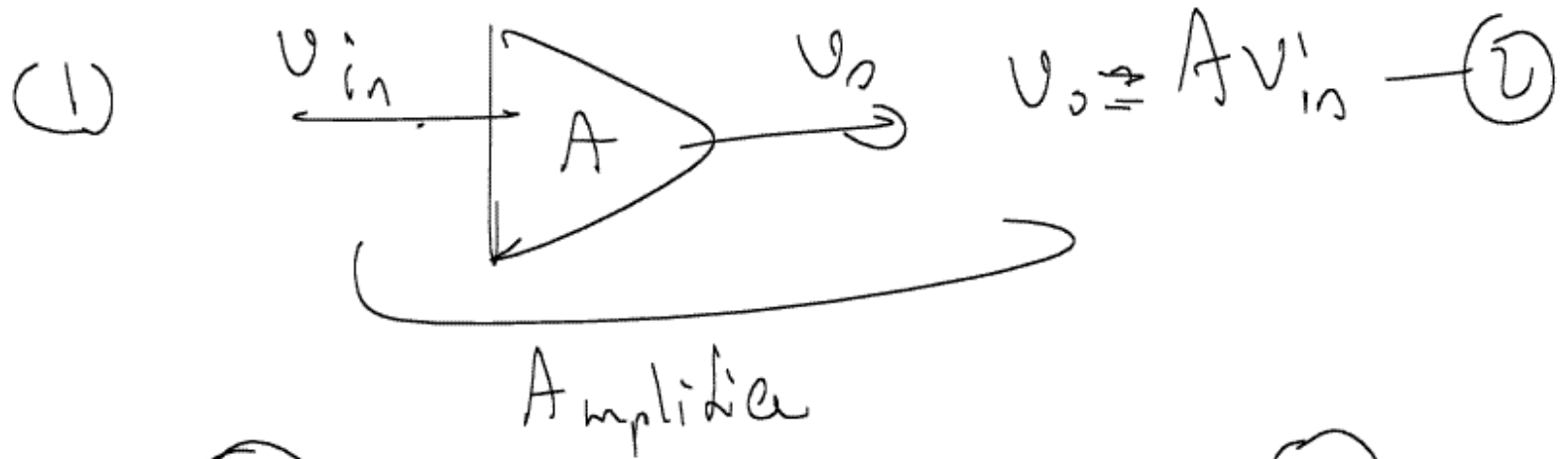

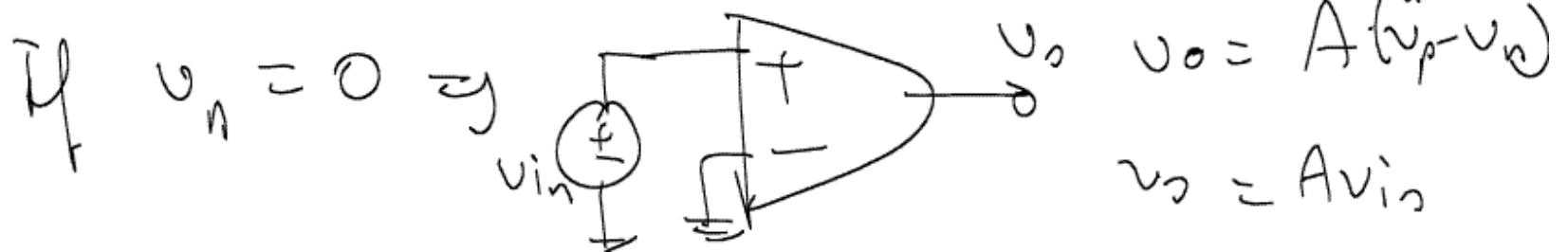Notice (2) is a subset of (1) $v_{in} = 0$



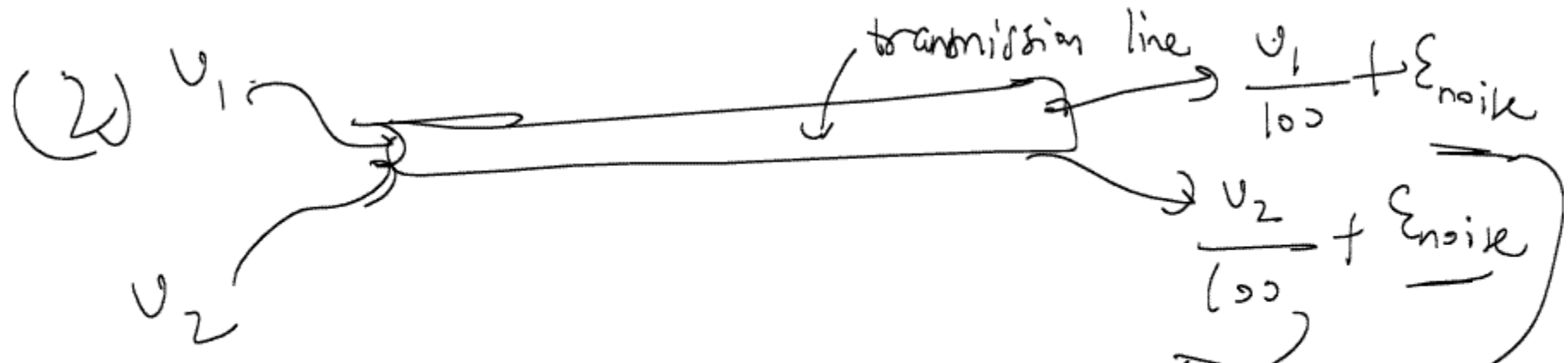

Conclusion: Very good

eliminating noise

at


~~$$U_3 = A \left(\frac{v_1}{100} + \epsilon_{\text{noise}} \right)$$~~

~~$$\left(\frac{v_2}{100} + \epsilon_{\text{noise}} \right)$$~~

Two problems:

(1) $A = 10^6$

eg:

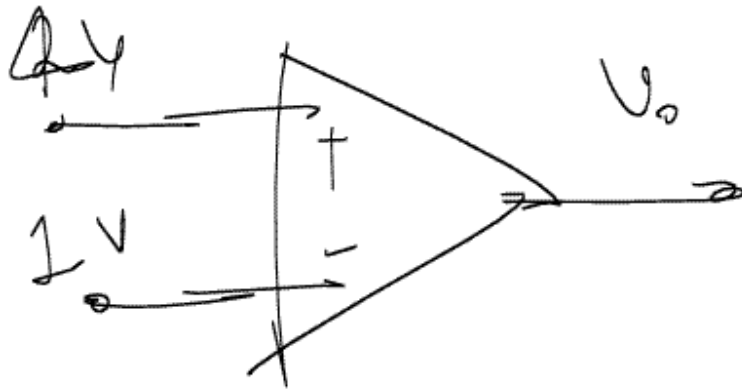



$$V_o = 10^6 (4 - 1)$$

$$= 3 \times 10^6$$

$$= 3 \text{ MV}$$

physically very difficult

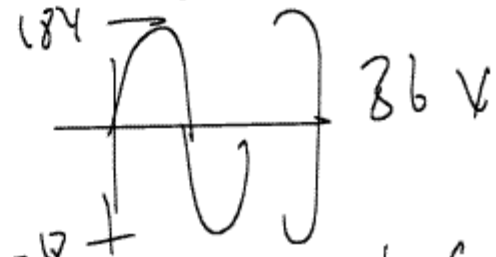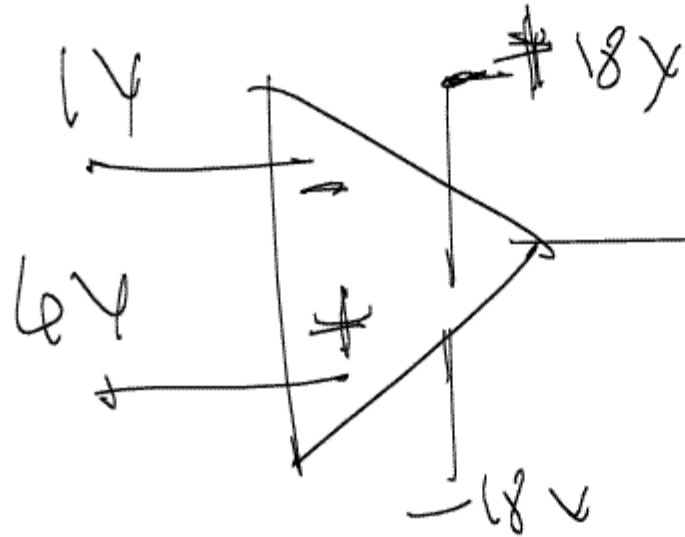In reality, the op-amp can amplify only upto the rail voltages



$$v_o = 10^6 (4 - 1)$$


$$= 3 \times 10^6 \text{ V}$$

$$\boxed{v_o = 18 \text{ V}}$$

θ_{JA} (junction-to-air) thermal resistance	100°C/W	100°C/W	25°C/W	100°C/W
θ_{JC} (junction-to-case)	N/A	N/A	25°C/W	N/A


- Note 4: For supply voltages less than $\pm 15V$, the absolute maximum input voltage is equal to the supply voltage.
- Note 5: Unless otherwise specified, these specifications apply for $V_S = \pm 15V$, $-55^\circ C \leq T_A \leq +125^\circ C$ (LM741/LM741A). For the LM741/LM741E, these specifications are limited to $0^\circ C \leq T_A \leq +70^\circ C$.
- Note 6: Calculated value from: $BW (MHz) = 0.35 / Rise\ Time(\mu s)$.
- Note 7: For military specifications see RET5741X BY LM741 and RET5741AX BY LM741A.
- Note 8: Human body model, 1.5 k Ω in series with 100 pF.

Schematic Diagram

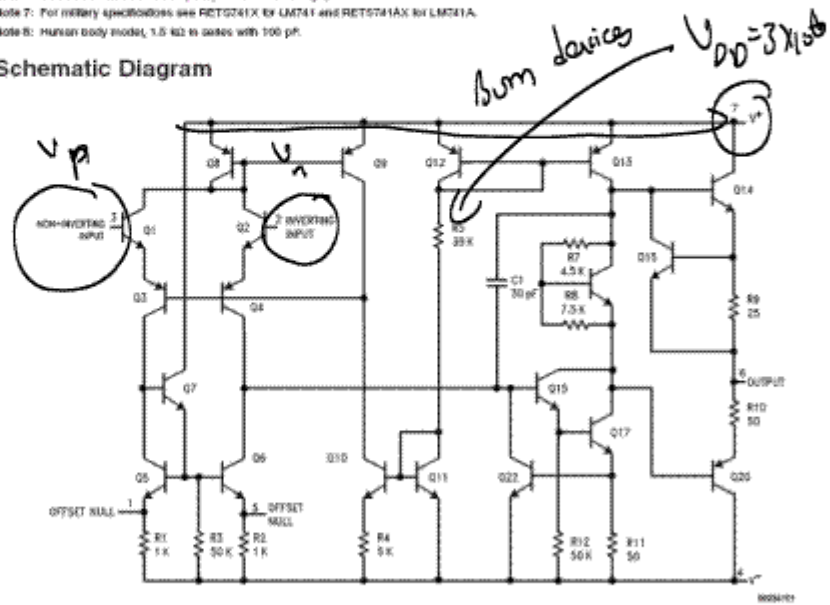

- Options
- LM741
 - General Description
 - Features
 - Connection Diagram
 - Typical Application
 - Absolute Maximum
 - Electrical Character
 - Schematic Diagram
 - Physical Dimension:

Ex 2:

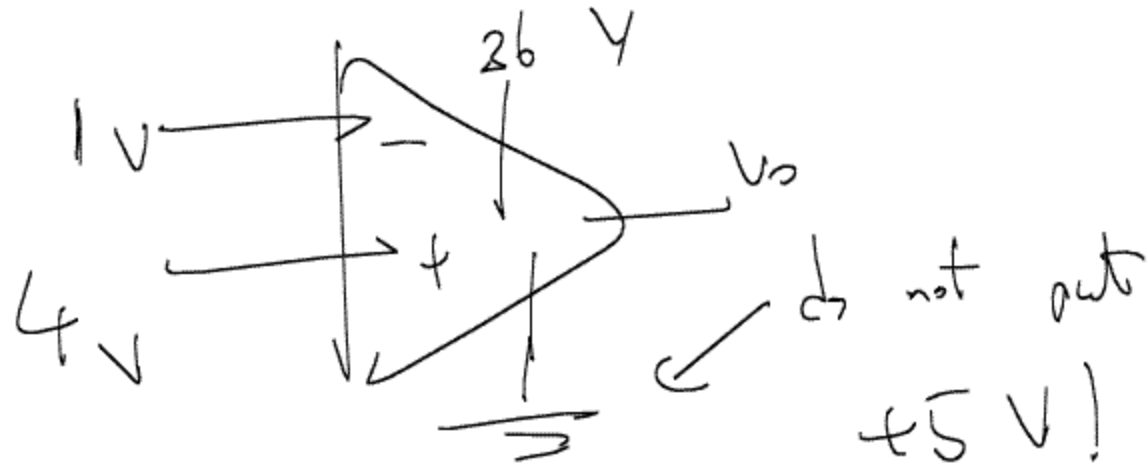


$$V_o = 10^6 (4 - 1)$$

$$= 10^6 (3) \leftarrow \text{Bigger than}$$

+86V (the positive supply)

$$\Rightarrow \boxed{V_o = 36V}$$

Ex 3:

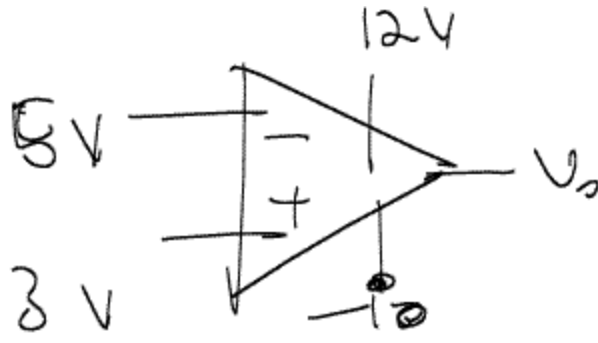


$$\begin{aligned} V_o &= A(V_p - V_n) \\ &= 10^6(3 - 5) \\ &= -2 \times 10^4 \text{ V} \end{aligned}$$

$V_o = -10 \text{ V}$

Notice: op-amp in this configuration is not very useful. It does not amplify, just reels

i.e.. $V_o = V_{DD} \text{ (or) } -V_{DD}$

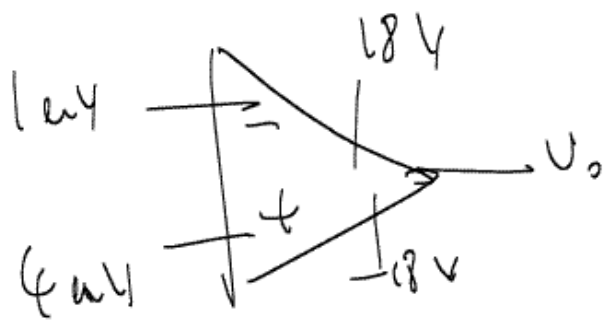So, to make use of the op-amp as an amplifier, we need to make sure that:



$$V_o \in [18, -18]$$

$$V_o = 10^6 (V_p - V_n)$$


(should be in μV)

$$V_o = 10^6 (4 \mu V - 1 \mu V)$$


$$= 3 V$$

ok, "real signals" are in the volts range (like you put 3 V into an amplifier, you get like 6 V output)

ANSWER: NEGATIVE FEEDBACK!

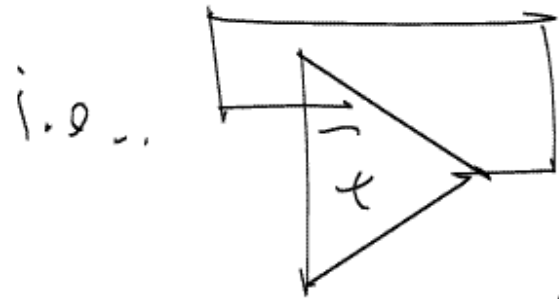

NOT THE SAME

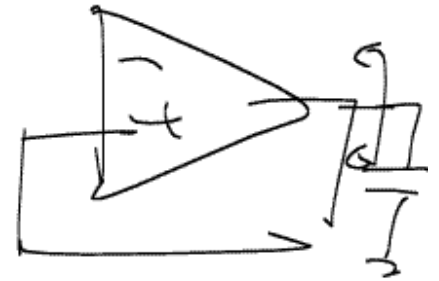

stable

unstable



Analogy:

For now, we will deal only with negative feedback

After spring break \Rightarrow positive feedback !!!!!!



: So why does negative feedback work in amplifiers \Rightarrow

GOLDEN RULE. FOR SOLVING
AN OP-AMP CIRCUIT IN
NEGATIVE FEEDBACK


Caution: Difficult to understand

THE RULE ↙

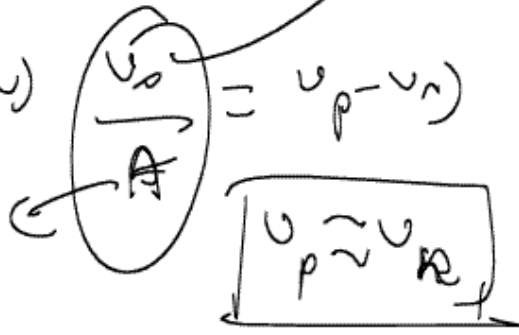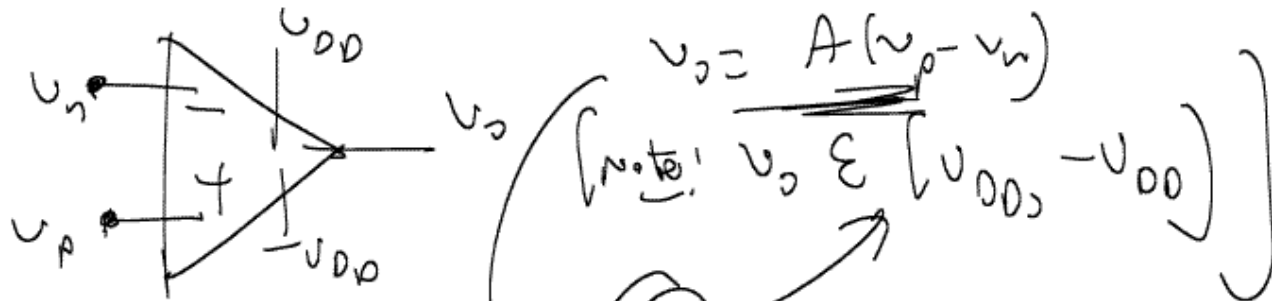
(1) $v_p \approx v_n$ if op-amp is not sailing!



Open-loop gain 156

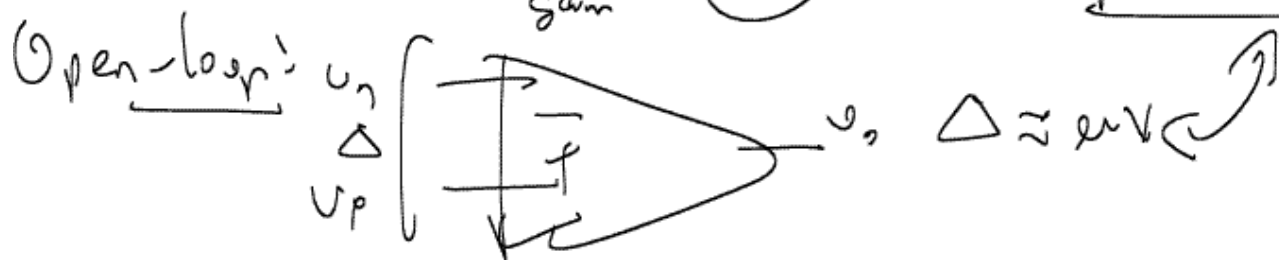


(2)

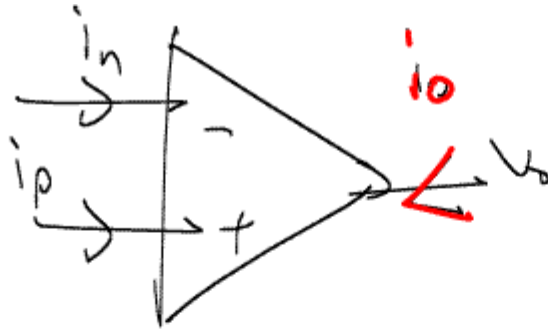

$$i_n \approx 0 \text{ \& } i_p \approx 0$$

BUT $i_o \neq 0$

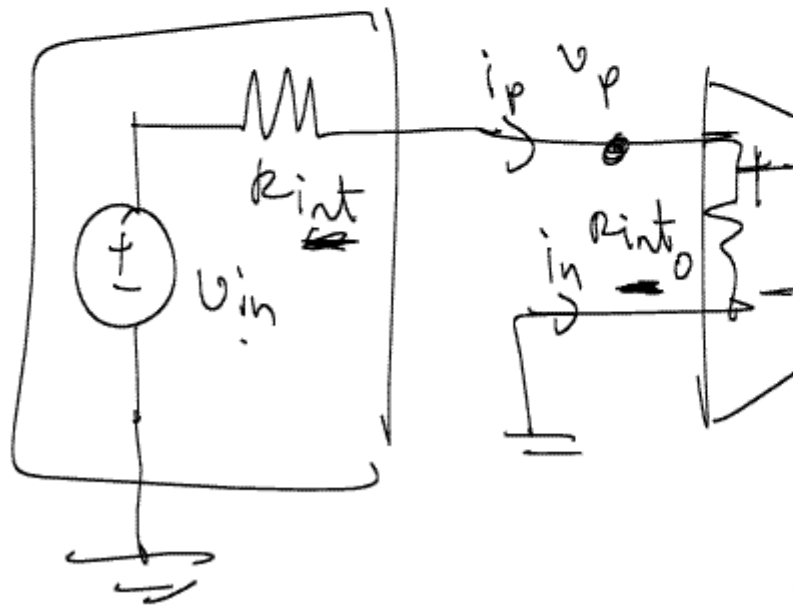This is because of the way an op-amp is built.



(want!) $v_o \approx A v_{in}$

i.e. $v_p = v_{in}$


$R_{int_0} \rightarrow \infty$ (usually $10^9 \Omega$)

$\Rightarrow i_p \approx i_n \approx 0$

Conclusion: (1) $i_p \approx i_n \approx 0$ (Note: $i_o \neq 0$)

(2) $v_p \approx v_n$ (if op-amp does not rail)

Es:

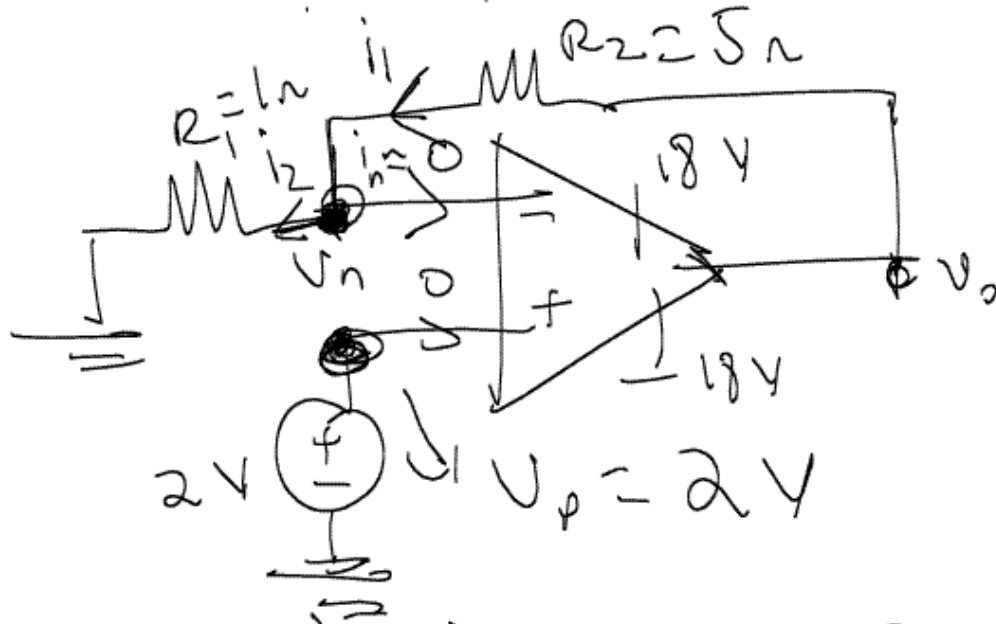

(Q1) Find $v_o = f(v_{in})$

Steps:

(1) $i_p \approx i_n \approx 0$ KCL @ v_n : $i_1 = i_2 + i_n$

$$\Rightarrow \frac{V_o - V_{in}}{R_2} = \frac{V_{in}}{R_1}$$

$$\Rightarrow \boxed{V_o = \left(1 + \frac{R_2}{R_1}\right) V_{in}}$$

In our case:

$$V_{in} = 2V, \quad R_2 = 5 \Omega$$

$$R_1 = 1 \Omega$$

$$\therefore V_o = (1 + 5) \cdot 2 = 12V$$

$(1 + R_2/R_1) \rightarrow$ closed loop gain