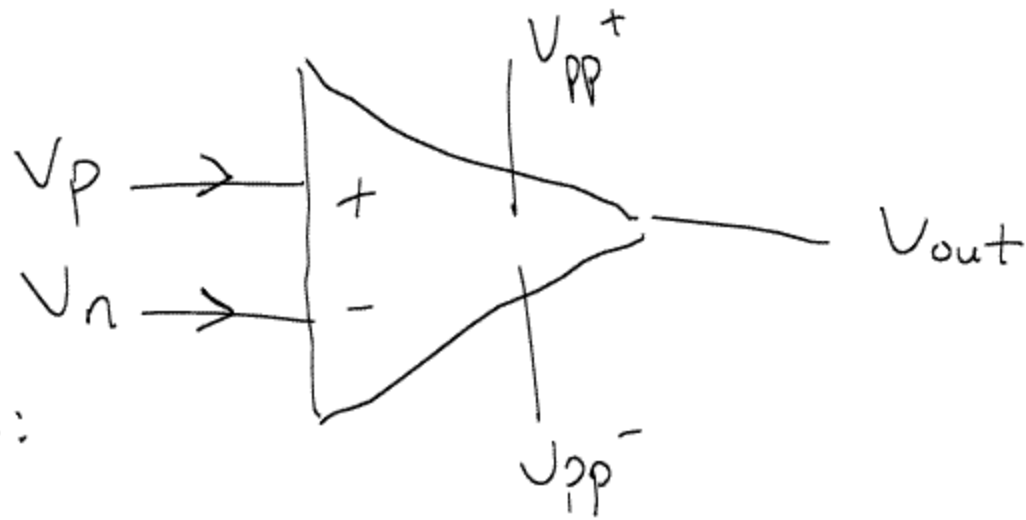


Lecture 18 03/17/05




IDEAL:

$$V_p = V_n$$

$$i_p = i_n = 0$$

Inverting

$$V_p = 0 = V_n$$

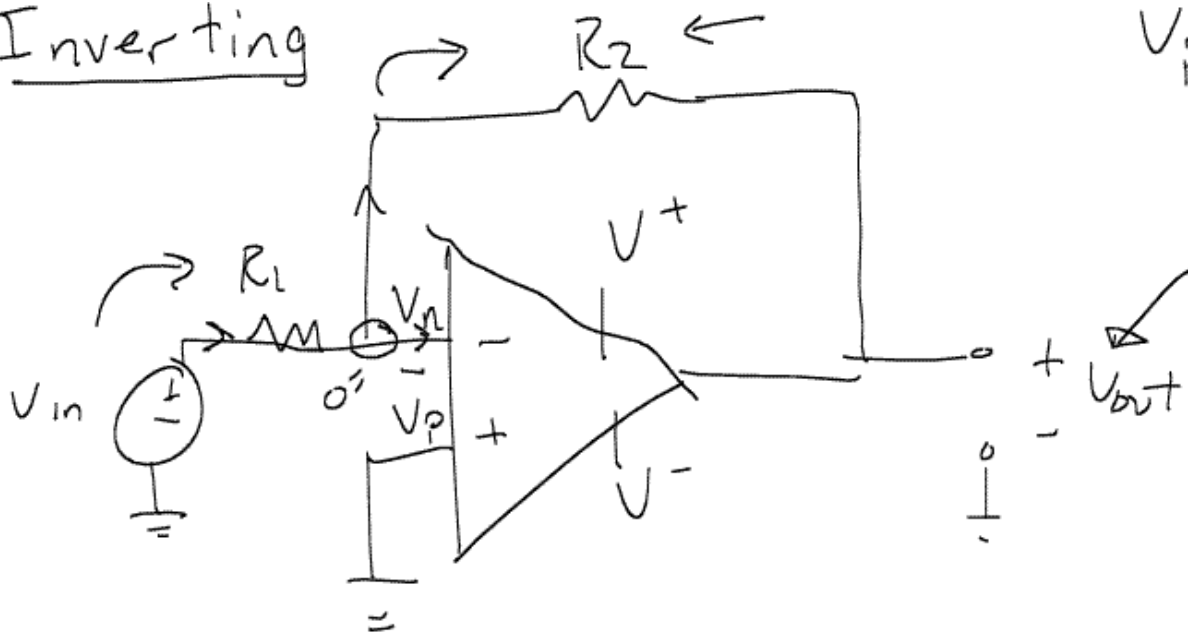


$$\frac{V_{in} - 0}{R_1} = \frac{0 - V_{out}}{R_2}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

V_{in} connected to V_n → Inverting
 V_{in} " " V_p → Non-inverting


Summing

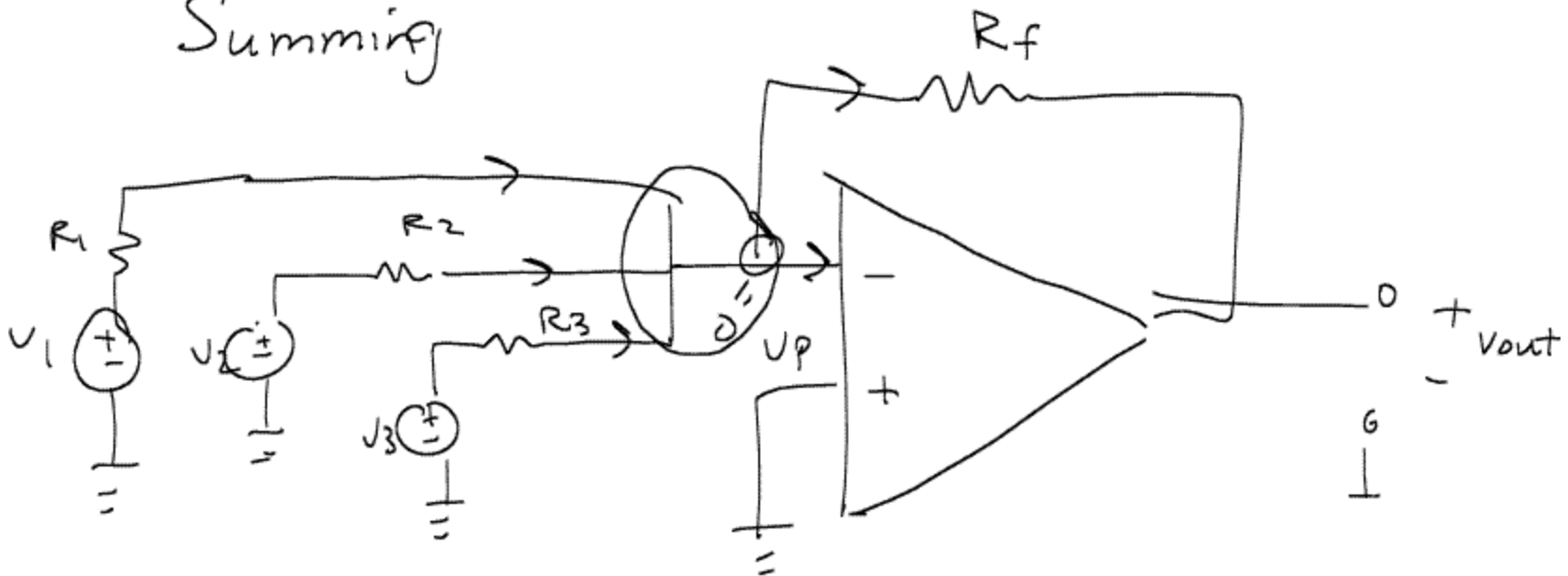

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{-V_{out}}{R_f}$$
$$V_{out} = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

Difference

$$V_p = V_n$$

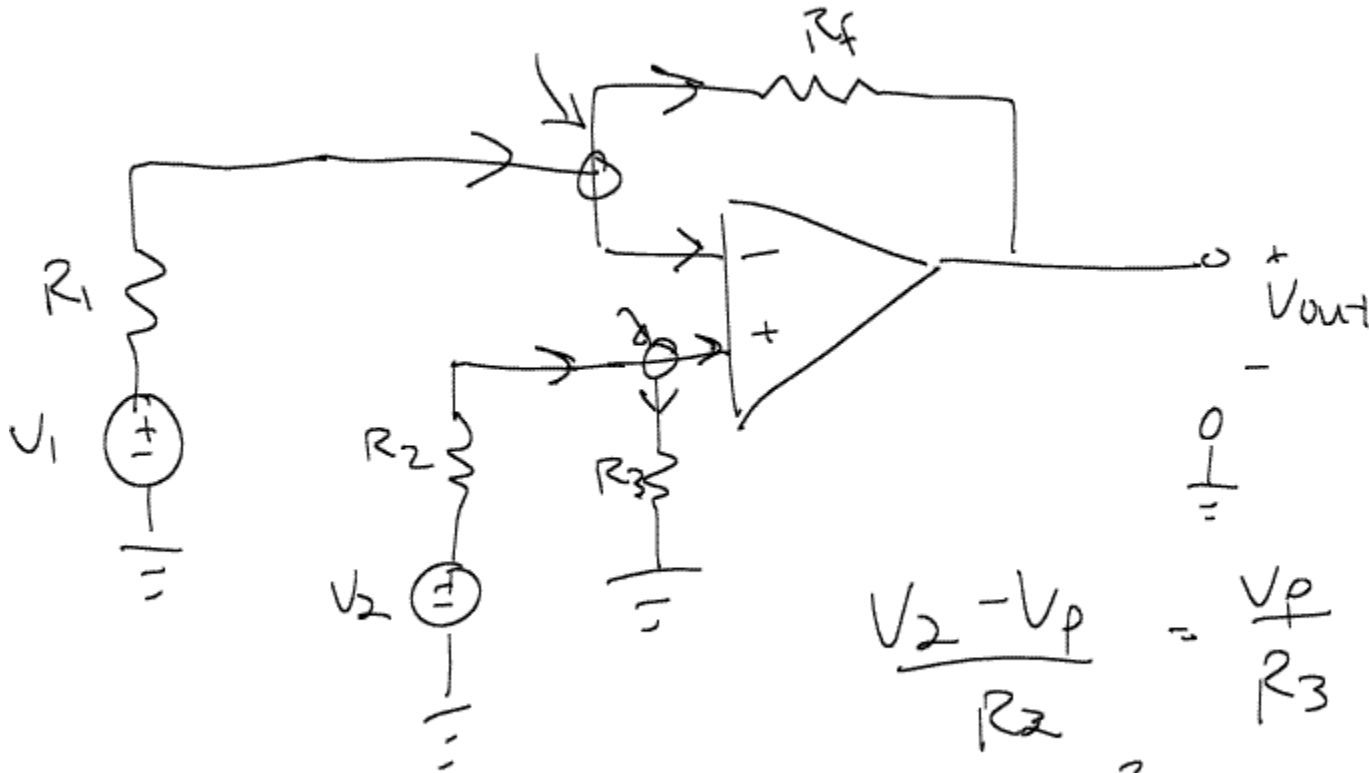


$$\frac{V_2 - V_p}{R_2} = \frac{V_p}{R_3}$$

$$V_p = \frac{R_3}{R_2 + R_3} V_2$$

$$\frac{V_1 - V_p}{R_1} = \frac{V_p - V_{out}}{R_f}$$

$$V_{out} = \frac{R_3 (R_1 + R_f)}{R_1 (R_2 + R_3)} V_2 - \frac{R_f}{R_1} V_1$$

Sample problem (not 5.3)

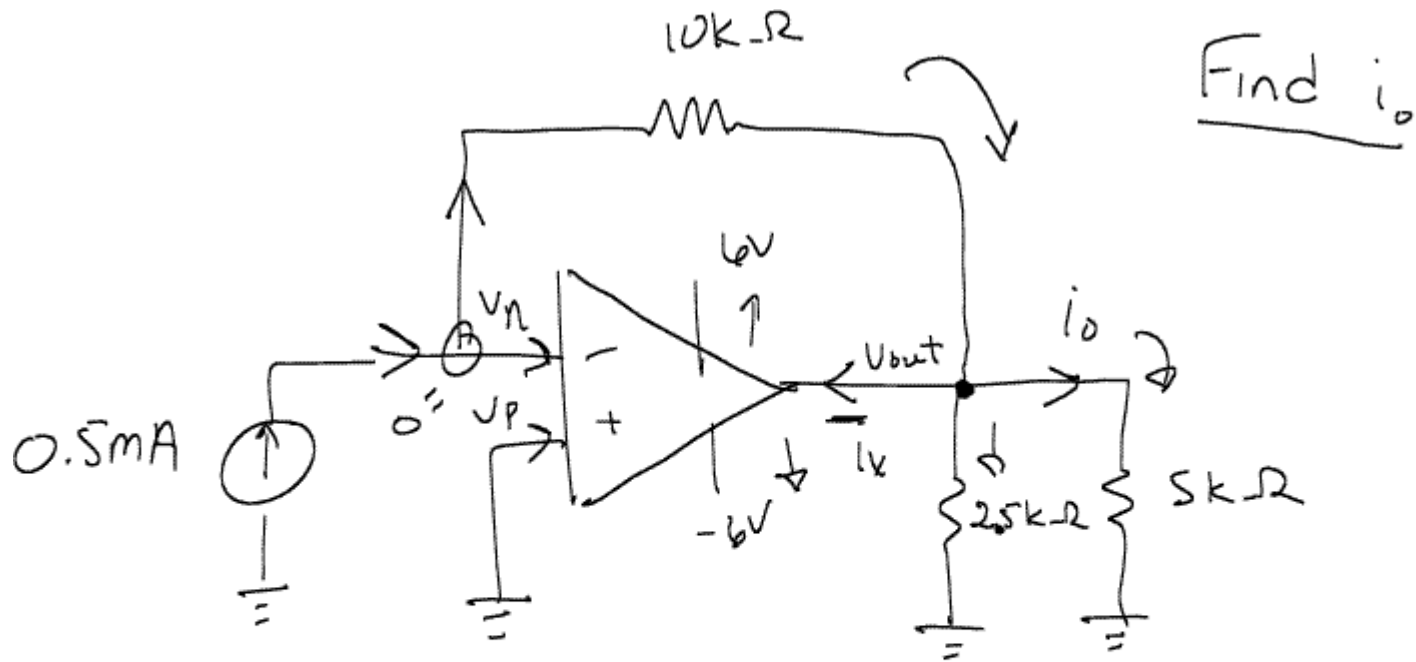



Nodal @ v_n : $0.5\text{mA} = \frac{0 - v_{out}}{10\text{k}}$ $v_{out} = -5\text{V}$

$$i_o = \frac{v_{out} - 0}{5\text{k}} = \underline{\underline{-0.001\text{A} = -1\text{mA}}}$$

Ex. 2

$$V_{out} = 2000(i_B - i_A)$$

$$\underline{V_p = V_n = R_1 i_B}$$

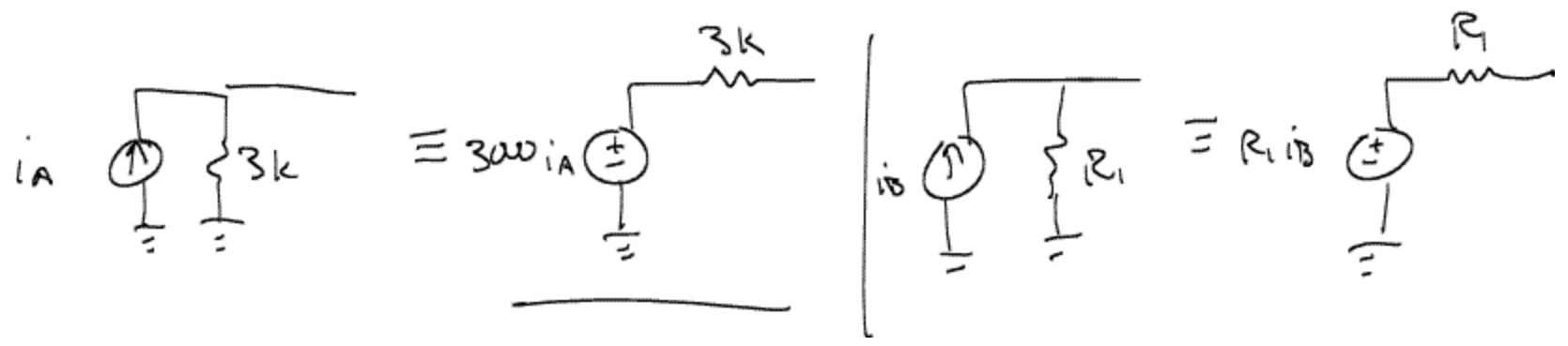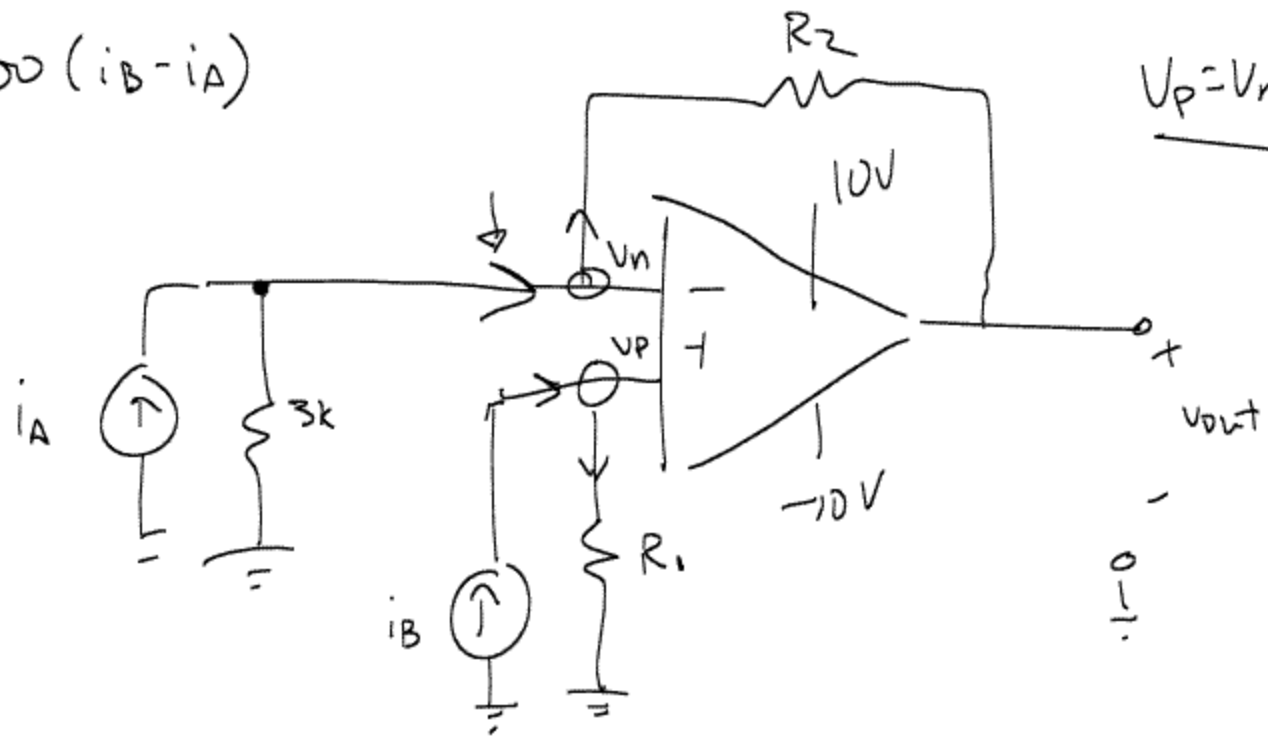

$$\frac{3000 i_A - R_1 i_B}{3000} = \frac{R_1 i_B - v_{out}}{R_2}$$

$$3000 i_A R_2 - R_1 R_2 i_B = 3000 R_1 i_B - 3000 v_{out}$$

$$v_{out} = \frac{3000 R_1 i_B - 3000 i_A R_2 + R_1 R_2 i_B}{3000}$$

$$v_{out} = \frac{(3000 R_1 + R_1 R_2) i_B - 3000 i_A R_2}{3000}$$

$$v_{out} = 2000 (i_B - i_A)$$

$$\rightarrow \frac{3000 R_1 + R_1 R_2}{3000} = 2000$$
$$\frac{3000 R_2}{3000} = 2000$$