

Lecture 19 - Intro. to nonlinear circuit analysis


Administrivia → Extra HW problem for homework due this week (HW #7 actually, incorrectly numbered)
→ HW #8

→ My Thursday evening office hours are in 277 Corro
(5:00-7:00)


rest of the semester
[6 weeks left!]

- This week: More opamps } nonlinear
- Next week: Diodes intro }
- midterm II (op-amps only)
- Project, Diode circuits, conclusion.

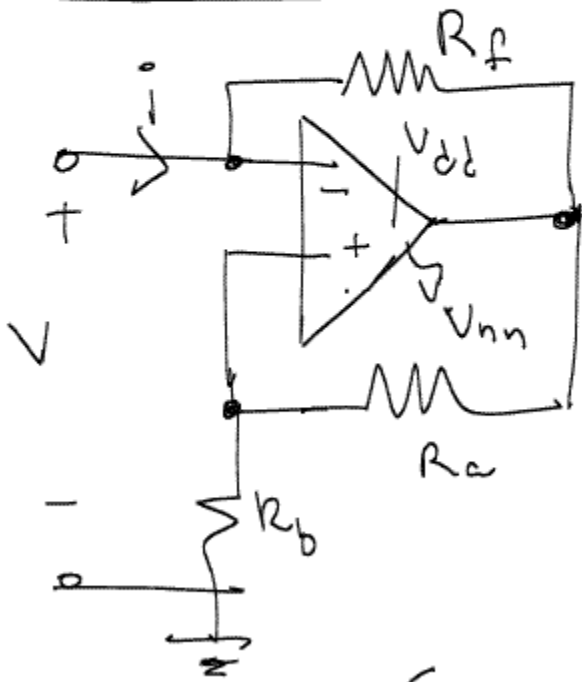Today: Negative resistance converter. \rightarrow Analysis
[i.e.. this week's lab]





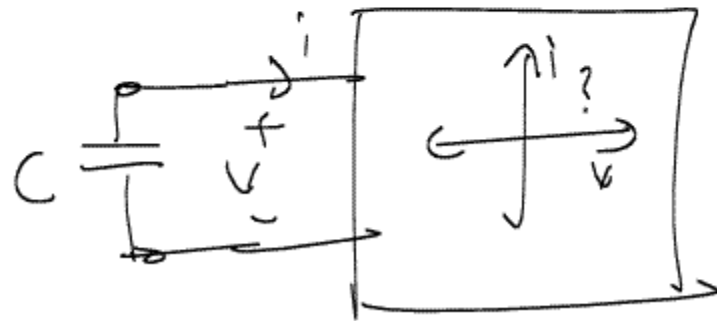Goal: Plot i vs. V . Once we get i vs. V we will use only this relationship



[Note: $C > 0$, $R_a, R_b, R_f > 0$, $V_{dd} > 0$, $V_{nn} < 0$]

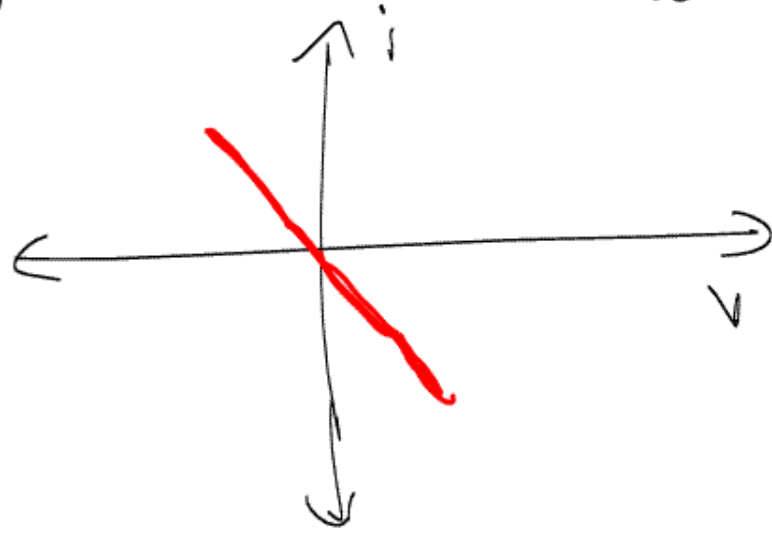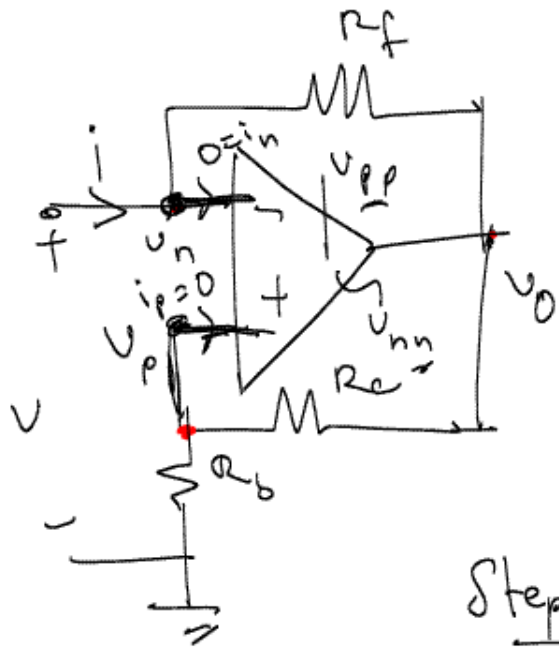Note: (1) Circuit has both positive & negative feedback
(explain difference on Thursday)




Step (1): Assume op-amp is in **linear**.

$$\Rightarrow V_o = A(v_p - v_n) \Rightarrow \boxed{v_p \approx v_n}$$

$\therefore \boxed{v_n = V \Rightarrow v_p = V}$. Now, we know $i_n = i_p = 0$

$$\therefore \hat{i} = \frac{V - V_o}{R_f} \quad \text{--- (1)}$$
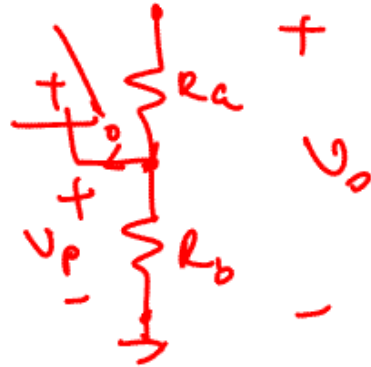
$$\therefore V_p = \frac{R_b}{R_a + R_b} V_o \quad \text{(voltage divider)}$$




$$\Rightarrow V = \frac{R_b}{R_a + R_b} V_o \Rightarrow \boxed{V_o = \frac{R_a + R_b}{R_b} V} \quad \text{--- (2)}$$

Substitute (2) in (1) $\Rightarrow \hat{i} = \frac{V}{R_f} - \frac{1}{R_f} \left[\frac{R_a + R_b}{R_b} V \right]$

$$\Rightarrow \boxed{\hat{i} = \frac{-R_a}{R_f R_b} V}$$

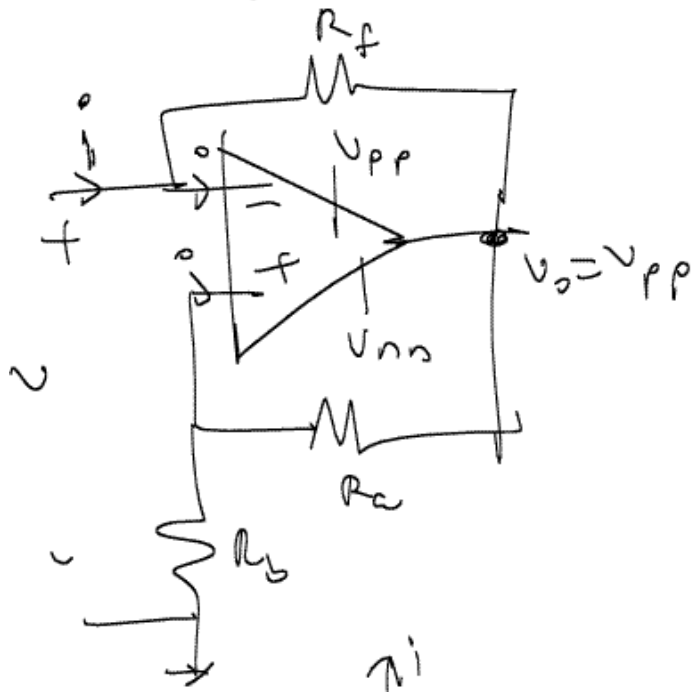Step (2): Assume op-amp is saturated (positive saturation)




Note: $V_n \neq V_p$ because $V_o = V_{pp}$

$$i = \frac{V - V_o}{R_f}$$

$$i = \frac{V - V_{pp}}{R_f}$$

To find x (V_x, i_x)

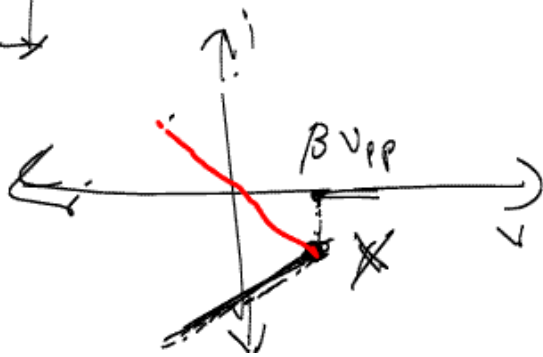
$$\Rightarrow \frac{-R_a V_x}{R_f R_b} = \frac{V - V_{pp}}{R_f}$$



$$\Rightarrow -R_c V_a = R_b V_a - R_b V_{pp}$$


$$\Rightarrow V_{ac} = \frac{R_b}{R_a + R_b} V_{pp}$$

β

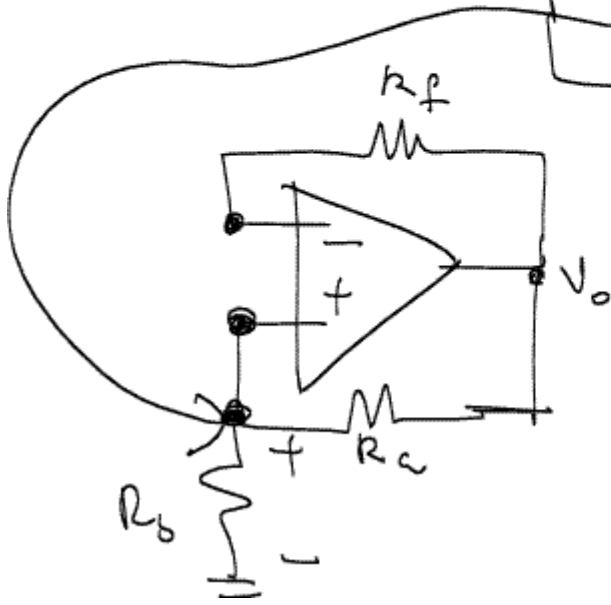


Similarly for negative saturation i.e.,

$$V_o = V_{nn} \quad (V_{nn} < 0)$$

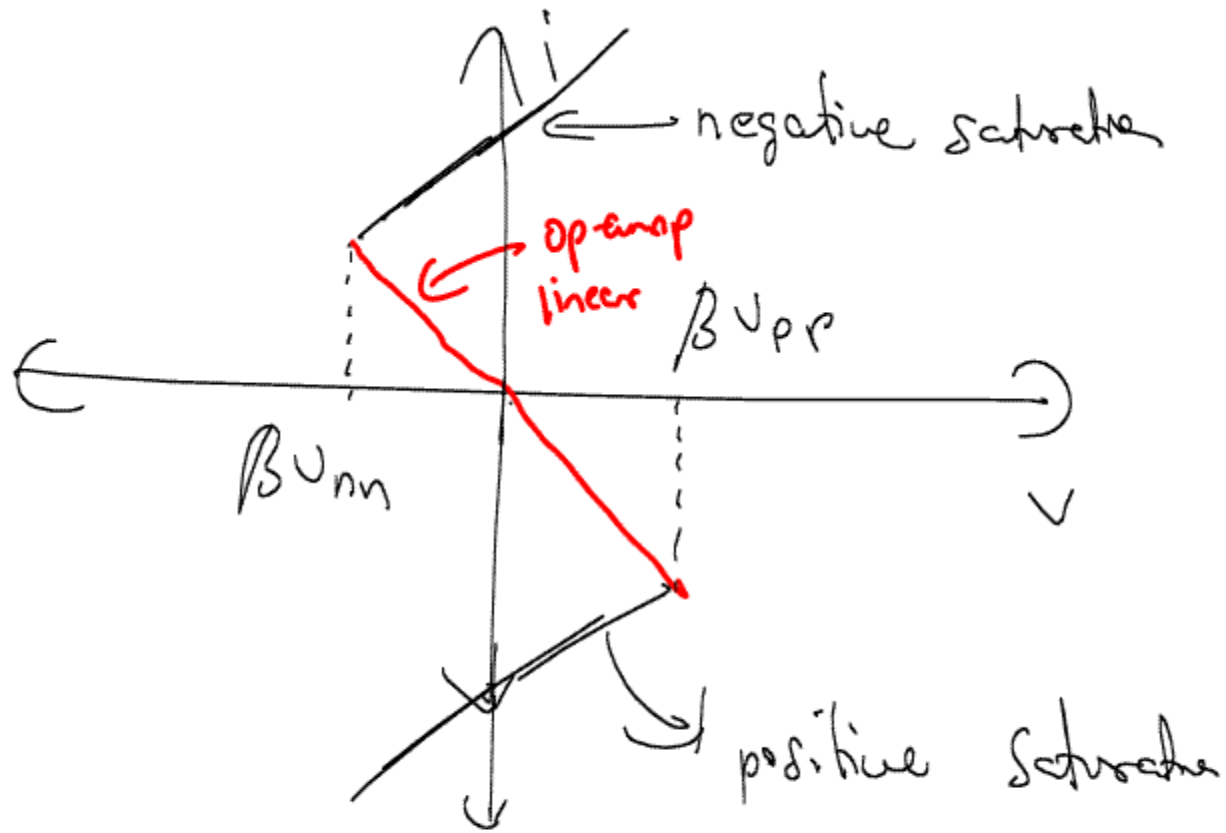




What do you mean by a "linear circuit"
 & what is a "non-linear circuit"?


Ex: $y = x$ ← Linear function Graphically:

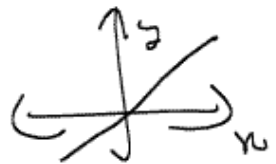$y = x^2$ ← Nonlinear function 


Circuits:

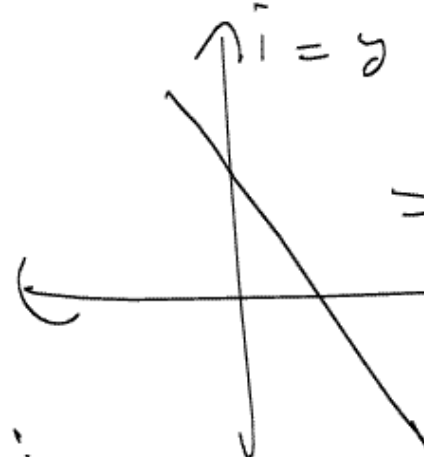(1)  ⇒ linear circuit

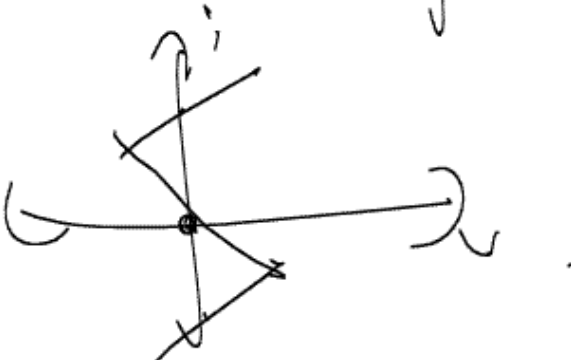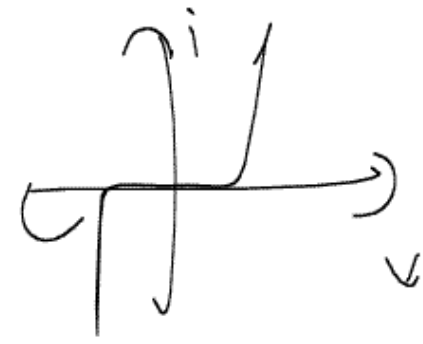(2)  ,  } Nonlinear

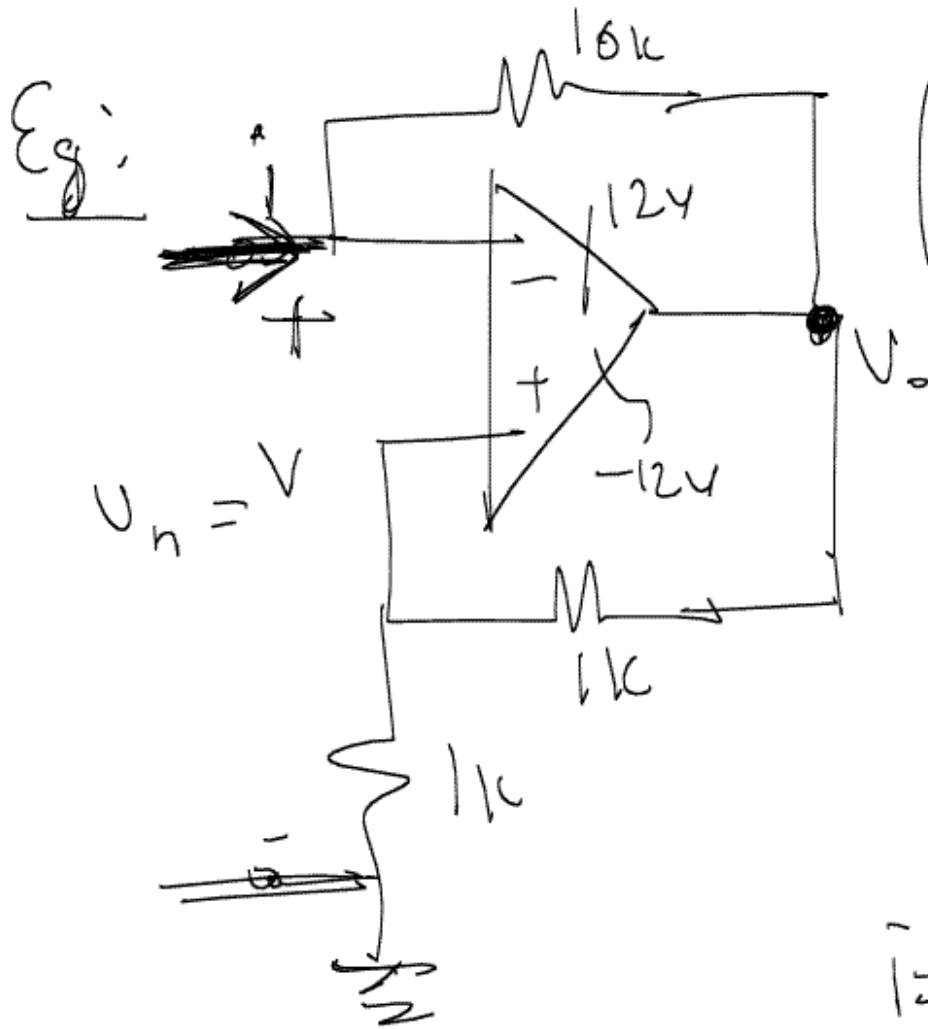



(lab circuit)

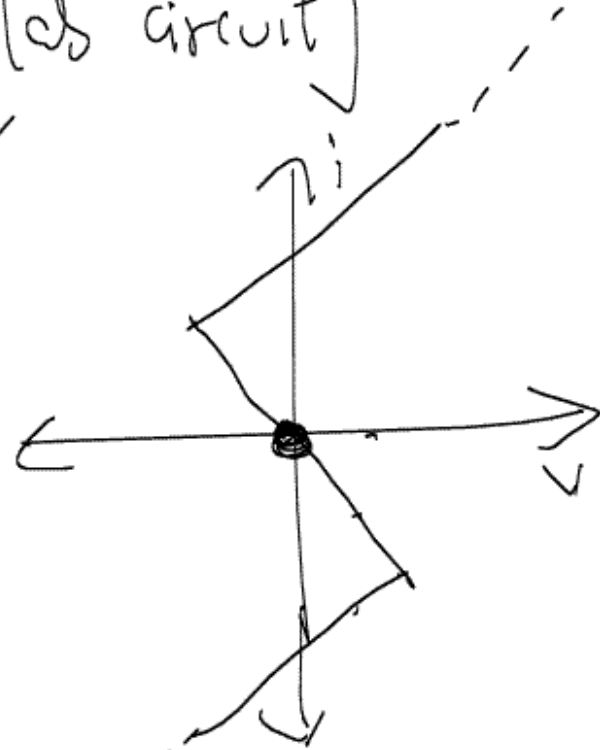

$i_i = 0$ (open-circuit) $\Rightarrow U = 0$
 (ideally)

In reality:

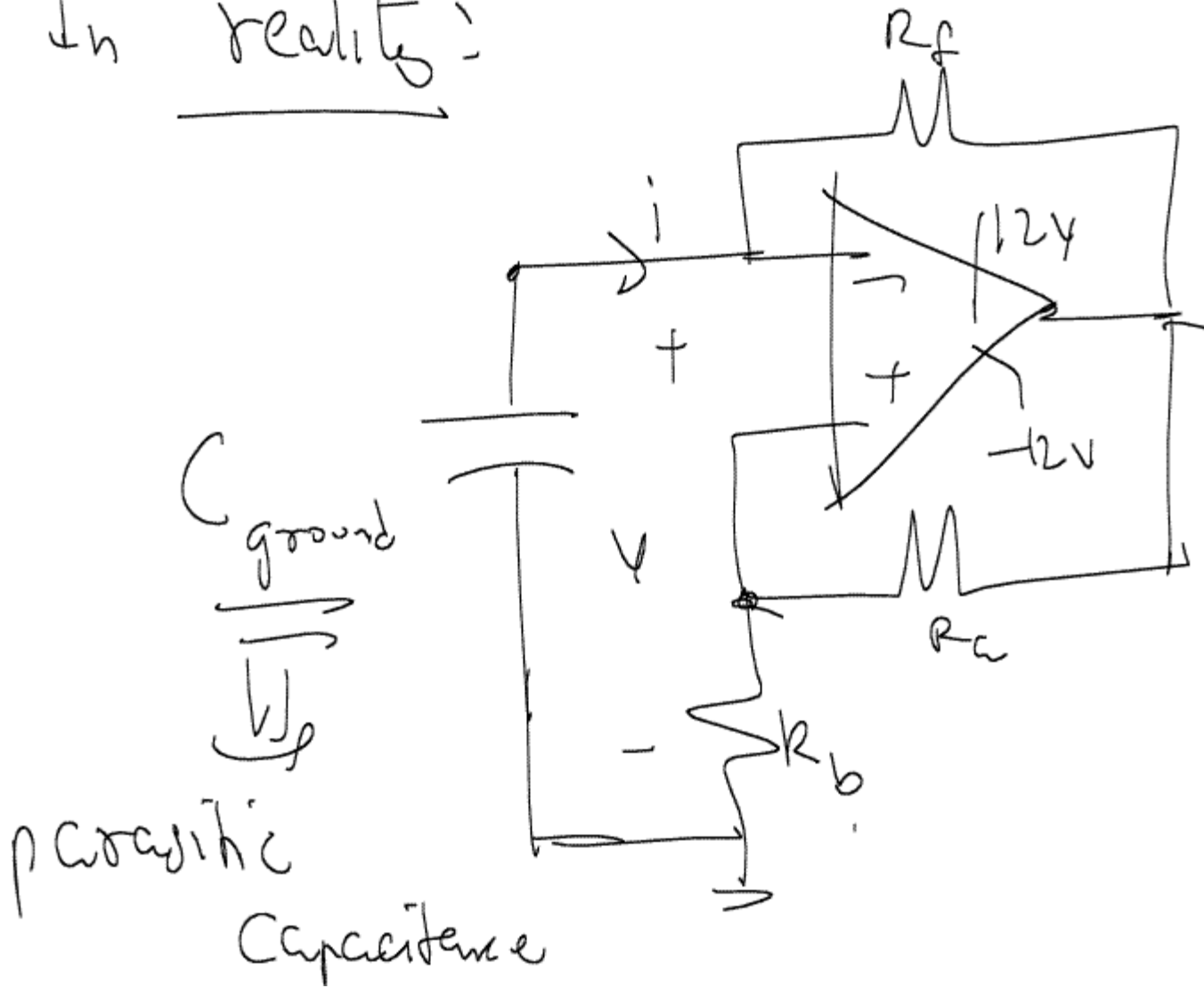

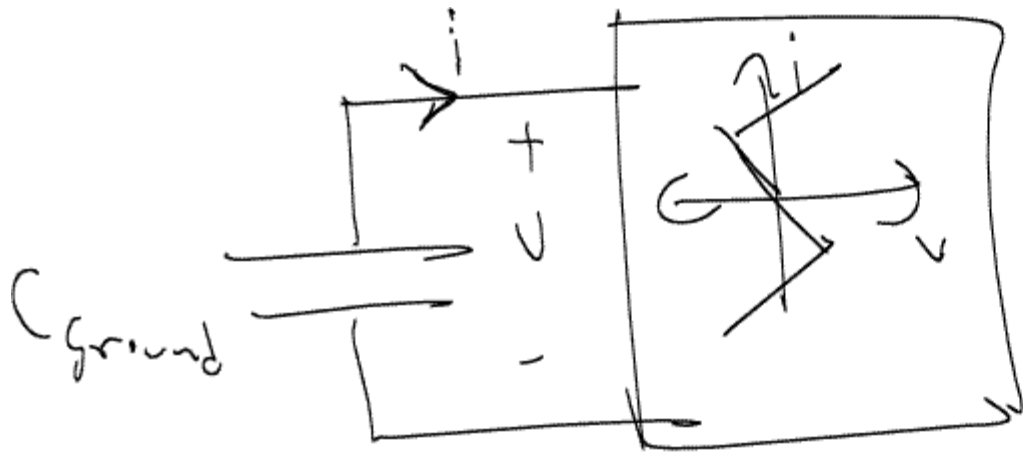


$$i_c = C \frac{dv_c}{dt}$$

$$i_i = -C_{\text{ground}} \frac{dv}{dt}$$

We now talk about

- (1) equilibrium points
- (2) stability

(1) Equilibrium points: $f'(t) = 0$

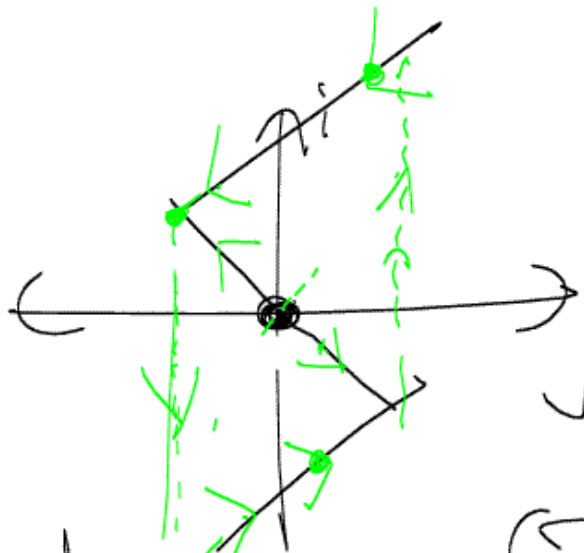

$$\Rightarrow \frac{dy}{dt} = 0$$

$$\Rightarrow \frac{i}{C_{ground}} = 0 \Rightarrow \boxed{\hat{i} = 0}$$

Analysis



stable

unstable



metastable




(2) Stability: $\hat{i} = -C_{ground} \frac{dy}{dt}$
 $[C_{ground} > 0]$

(3) $\hat{i} > 0, v'(t) < 0$


(4) $\hat{i} < 0, v'(t) > 0$

Using the KVL eqns. (3) & (4) \Rightarrow dynamic
route


Analysis:

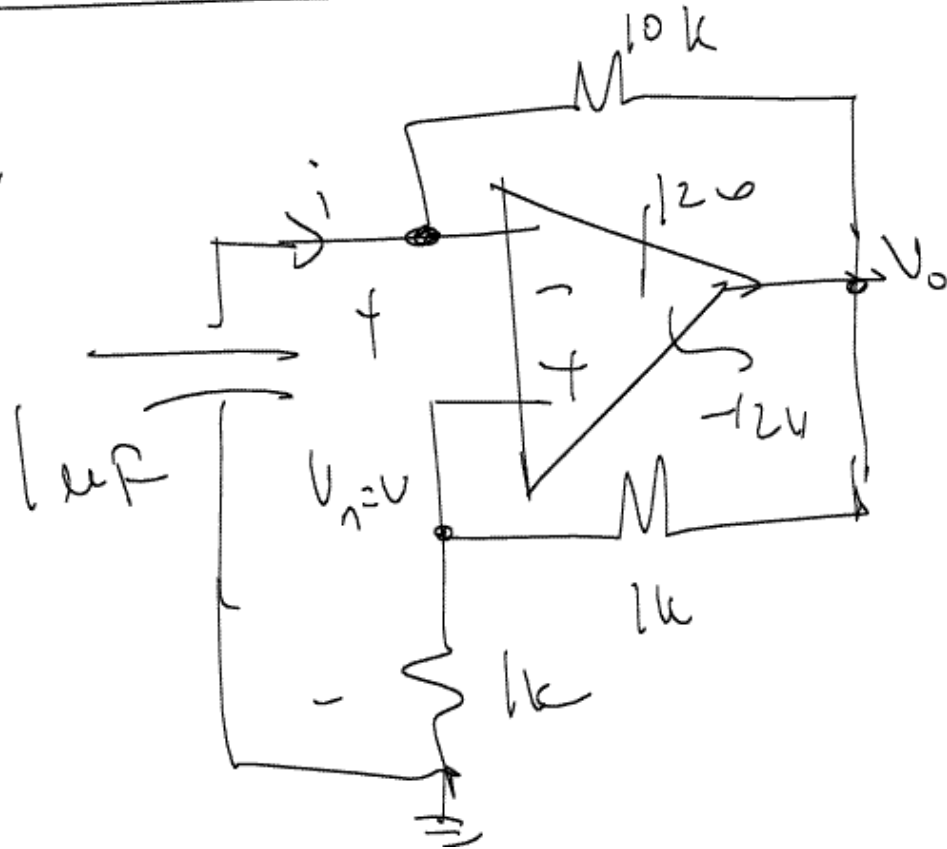


Goal: Find
 $V_n(t)$, $V_o(t)$

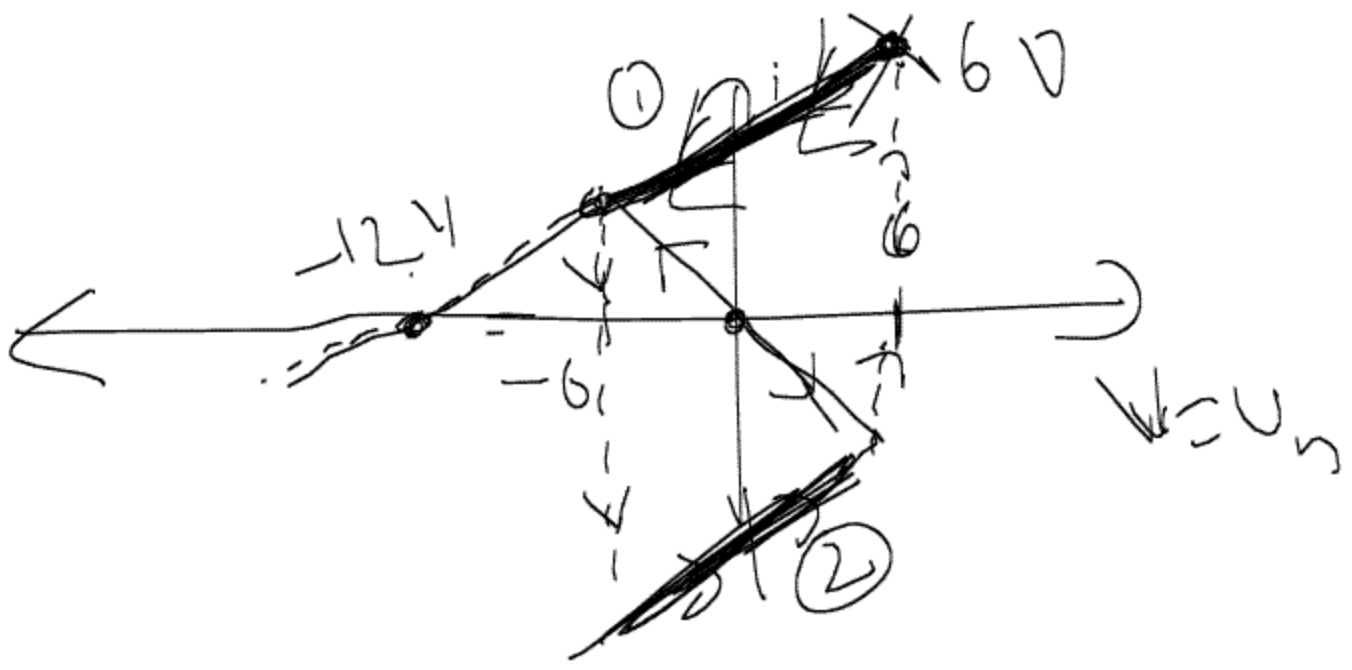

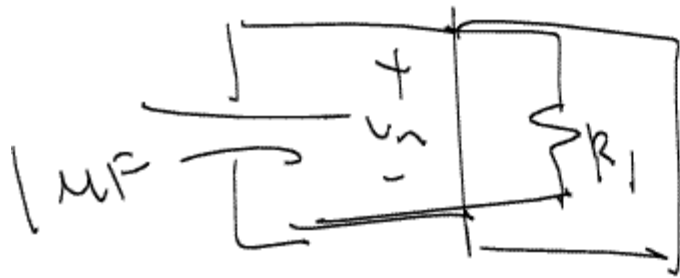Assume $V_n(0) = 0 \Rightarrow$ you quickly move
 out of the linear op-amp
 region


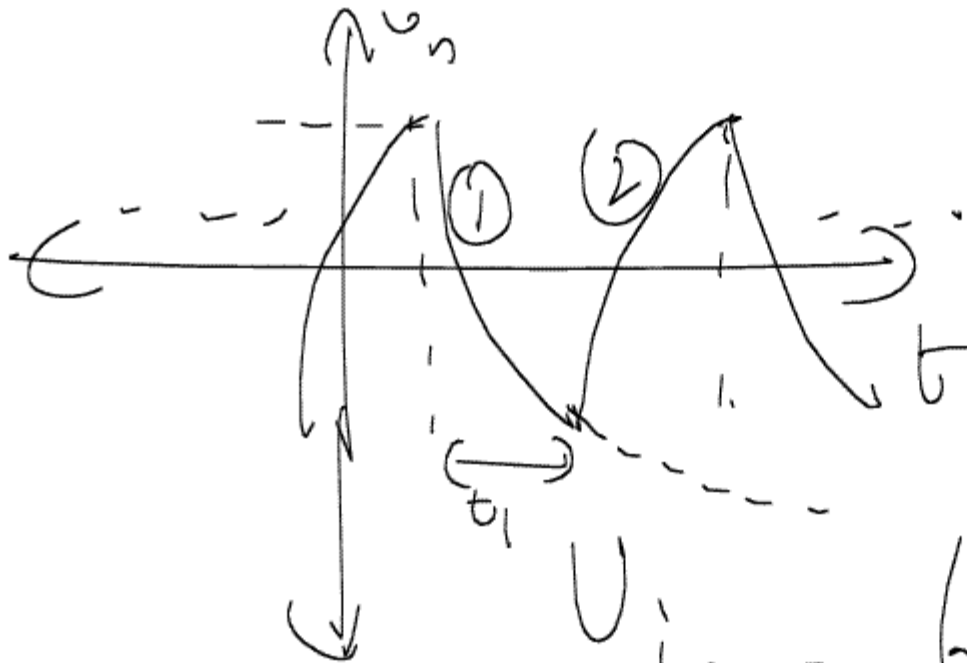
$$u_n(t) = u_{f0} + (u_{i0} - u_{f0}) e^{-t/R_1 C}$$




$$u_{i0} = 6V \quad u_{f0} = 12V$$

$R_i = \frac{1}{\Delta} \rightarrow$ will finish next lecture.

Now! AW questions


(5.25)

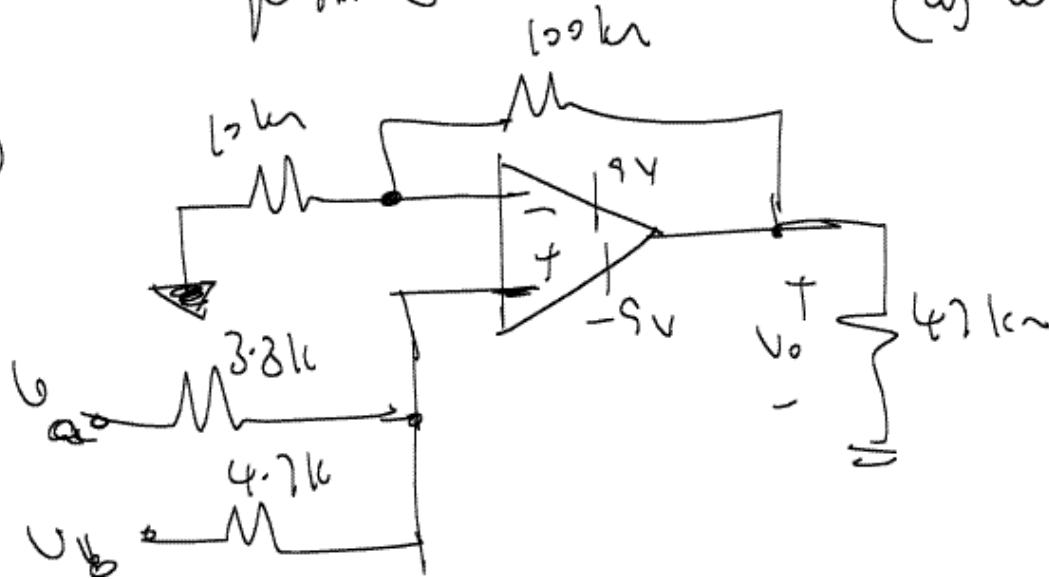


(a) What kind of amplifier?

Non-inverting ^{Summing} amplifier

i.e., $V_o \neq f(V_{in})$

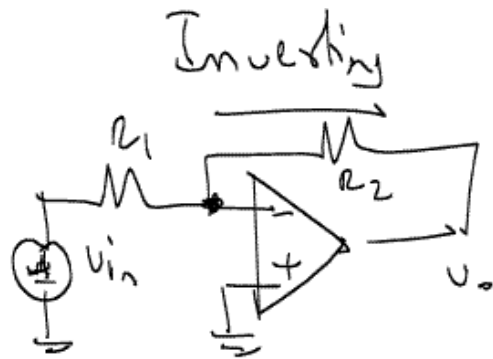

$$V_o = -\frac{R_2}{R_1} V_{in}$$

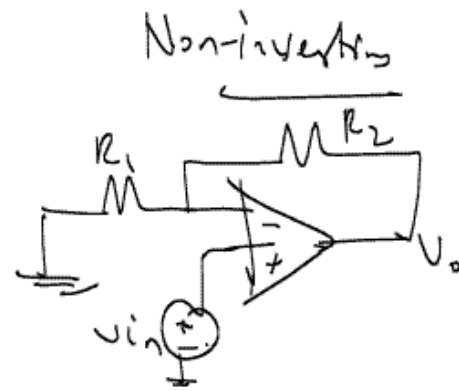

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

(Q.1) What are the weighting factors associated with V_a & V_b ?

$$V_o = \alpha V_a + \beta V_b$$

weighting factors

Why is a summing amplifier useful

