

LECTURE 2

Note Title

1/20/2005

- 1) Administrative — new lab sections
 - login/password for grades etc
 - ~~webct/blackboard~~
 - Office Hours start next week
-

TODAY

Note Title

1/20/2005

Chapter 1


- 1) Idea behind this class
- 2) Voltage & Current
- 3) Ideal basic circuit elements
- 4) Power & Energy

Chapter 2

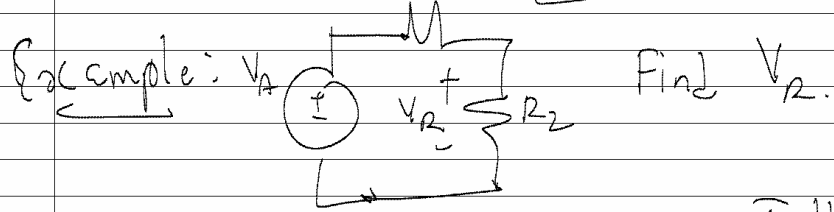- 1) Voltage, current source
- 2) Ohm's law
- 3) Building Circuit Models
- 4) Kirchoff's laws

Chapter 1 - Idea (goal) of this class (EE 100)

90% [GOAL: CIRCUIT ANALYSIS (NOT DESIGN/SYNTHESIS)]



PROBLEM: NONLINEAR → Talk about it later!

Chapter 1 - VOLTAGE & CURRENT

VOLTAGE
 Voltage is the separation of energy
 units $V = \frac{\Delta \omega}{\Delta q}$
 "Defined as" Volts

CURRENT
 is defined as the flow of positive charge
 $i = \frac{dq}{dt} \rightarrow C$
 units ampere

VOLTAGE

is like potential energy!
that is, voltage is "across" a battery


CURRENT

is like water flowing through a pipe
that is, current flowing through a battery.

Chapter 1 - IDEAL BASIC CIRCUIT ELEMENT

Note Title

1/20/2005

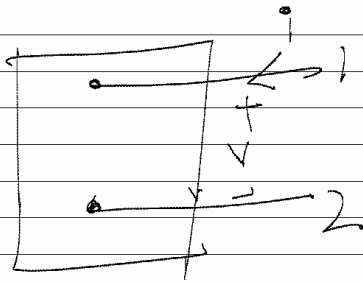


Three properties:

(1) Has only two terminals (for 99% of the class)

(2) has an $i-v$

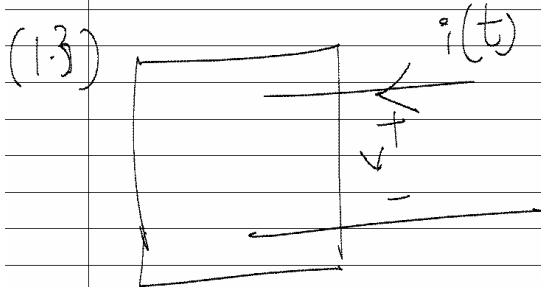(3) Cannot be subdivided further relationship (some exceptions exist)

page 16
 ASIDE - EXAMPLE: ASSESSING
OBJECTIVE 2



$$i(t) = 0 \quad t \leq 0$$


$$= 20e^{-5000t} \text{ A} \quad t \geq 0$$

Question: Calculate total charge (in μC)
 entering the element...

EXAMPLE 1 (cont'd)

Note Title

1/20/2005

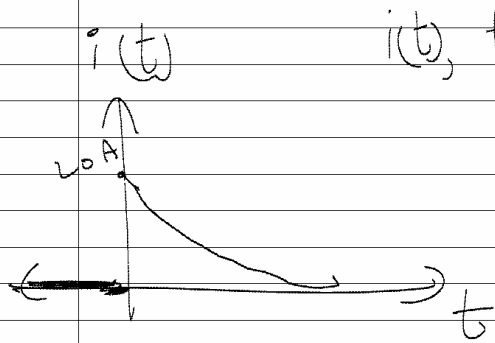

$i(t), t \geq 0$ is
 $20e^{-5000t} \text{ A}$

$$i \triangleq \frac{dq}{dt} \quad t \rightarrow \infty$$

$$\Rightarrow q = \int_{t=0}^{\infty} i \, dt$$

Note: charge $t \rightarrow \infty$ because you want total $t=0$

$$= \int_0^{\infty} 20e^{-5000t} dt$$

$$= \frac{20e^{-5000t}}{-5000} \Big|_{t=0}^{t=\infty}$$


$$= 20 \cdot \frac{1}{5000} = \frac{4}{1000} C = \frac{4000}{10^{-6}} C$$

$= 4000 \mu C$

Chapter 1 - Power & SIGN

Note Title

1/20/2005

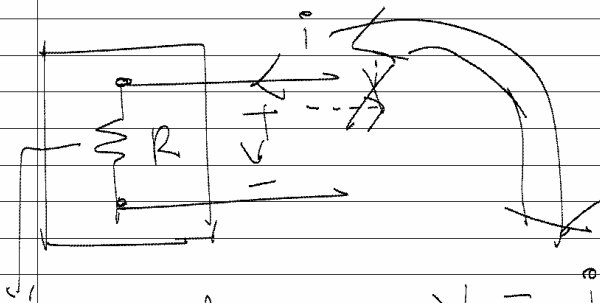


CONVENTION

SIGN CONVENTION

Symbol for a resistor!

$$v = iR \quad \text{Ohm's Law}$$

Resistance; Unit: ohm (Ω)

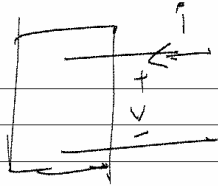Why  is positive convention?

Answer: Because of power

$$\text{power} = \frac{dW}{dt} = \frac{dW}{dq} \cdot \frac{dq}{dt} \quad \left[\begin{array}{l} \text{Chain} \\ \text{Rule} \end{array} \right]$$


$$p = v \cdot i \quad \text{Watts}$$

SIGN CONVENTION


Note Title

1/20/2005

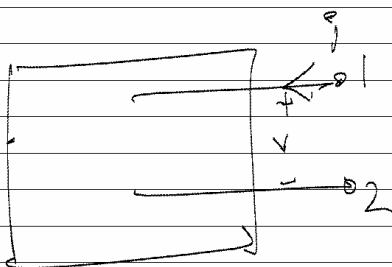We need to distinguish between power absorbed & power released!



1) Device is absorbing energy

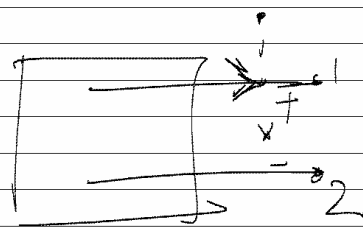

2) Device is releasing energy

because charges
are flowing from
+ to - \Rightarrow higher
potential to lower
potential, lost

energy is going into
device!
 $p = v_i$ Watts


$$p = -v_i$$

watts

Chapter 2 - Circuit Elements

Note Title


1/20/2005

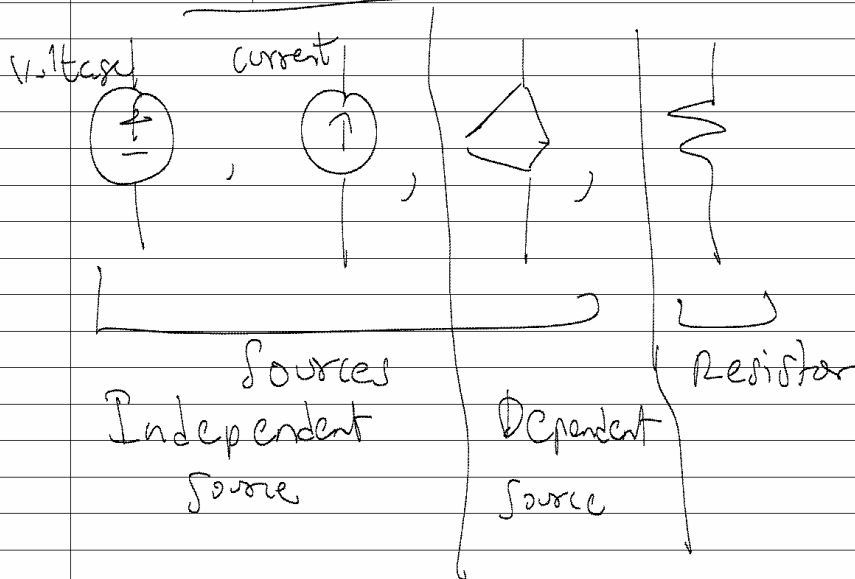

Dependent Voltage Sources

Note Title

1/20/2005

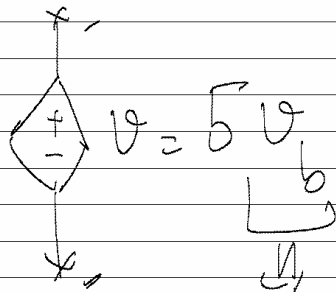


Example:

$$\text{If } V_b = 4V,$$


$$V = 20V$$

Voltage elsewhere
in the circuit

Similarly, we have current sources

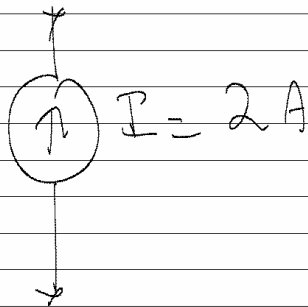

Independent
Current source

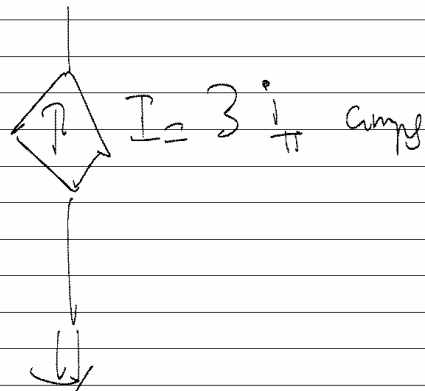

Dependent current
source


Circuit Terminology

Note Title

1/20/2005


Node: Point where two circuit elements meet

ex:

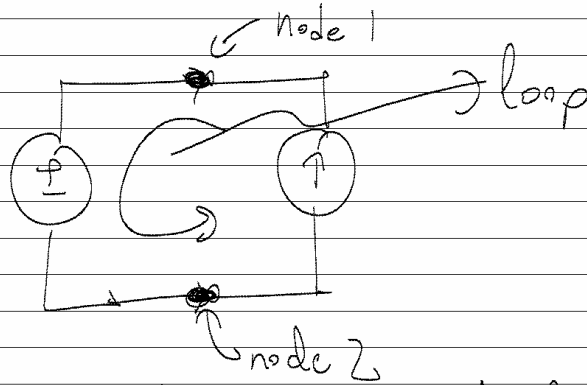


loop: If you start at one node & trace a path back to the same node

Examples of circuit

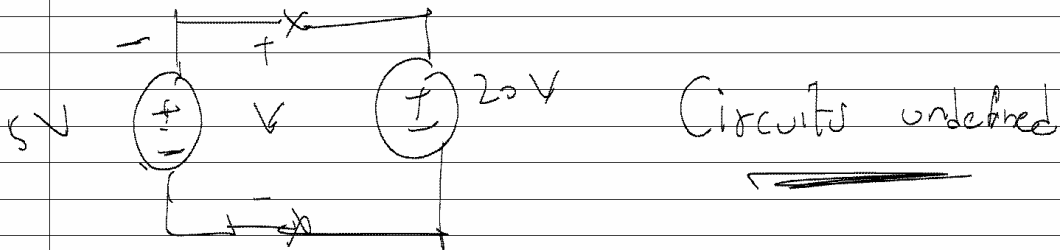

$$V = 5V \quad V = 20V$$

$$20 = 5$$

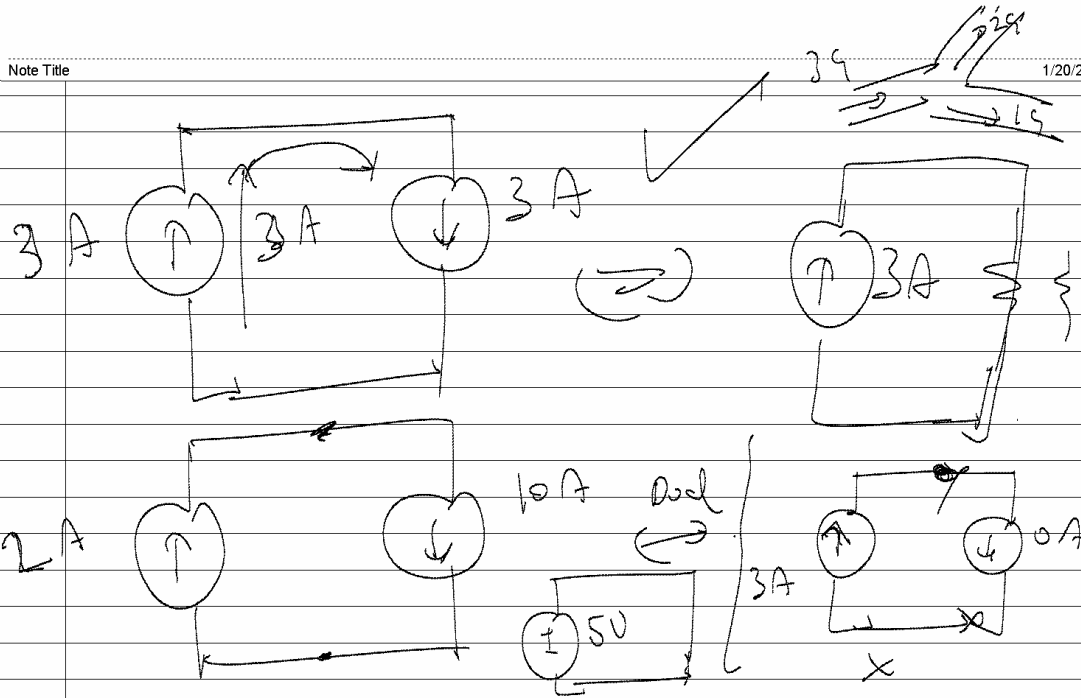

Ohm's LAW : describes a resistor.

