

Today - More op-amp circuits


Administrivia → My office hours today are
5:00 - 9:00 (not 5:00 - 7:00)
[in 277 (only)]

Today → (1) Finish deriving print characteristics of
nonlinear oscillator
[For details, look at EE100 webpage for Summer 06,
you can get to it from the EE100 homepage
↳ click on EE100 Fall Homepage & then again
click on EE100 Summer Homepage. Look under lecture notes]

(2) More op-amp circuit examples


(hold off on the mathematical explanation of)

Negative feedback

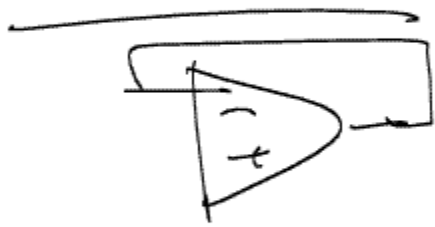

Amplifiers

positive feedback

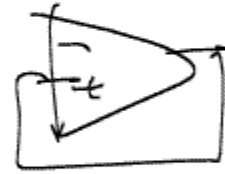




Oscillators

Explanation of feedback


Both



Recall:

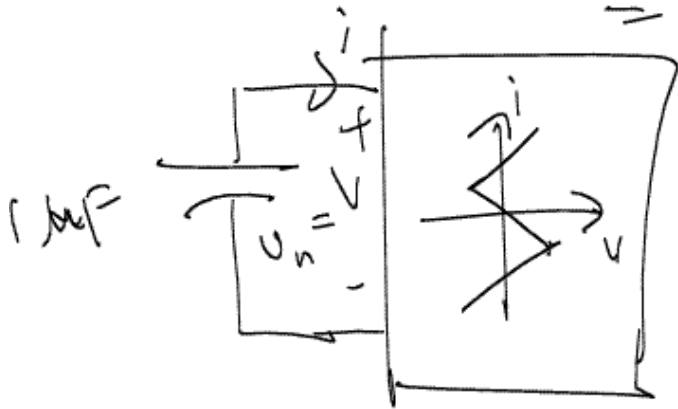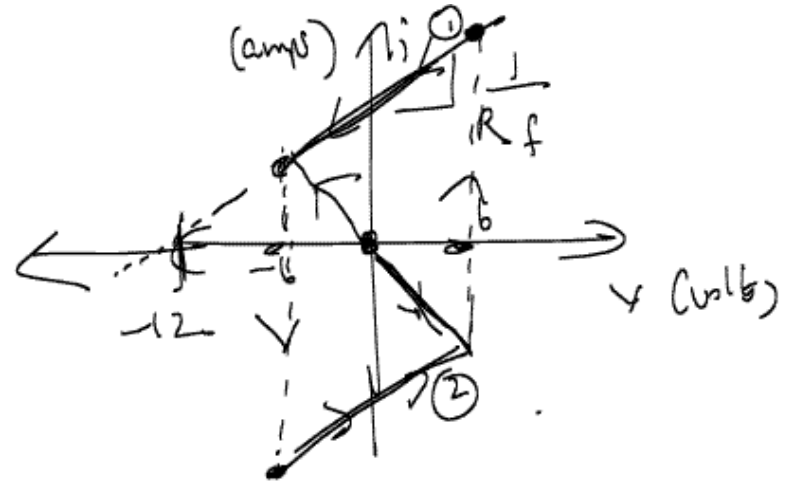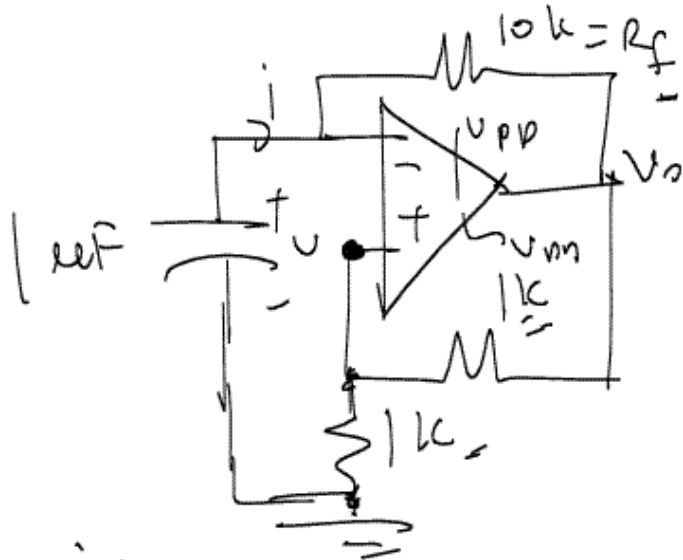


Region ①

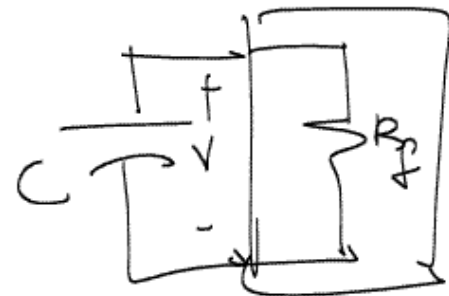

RC circuit

$$v(t) = v_f + (v_i - v_f) e^{-t/R_f C}$$

(Important)

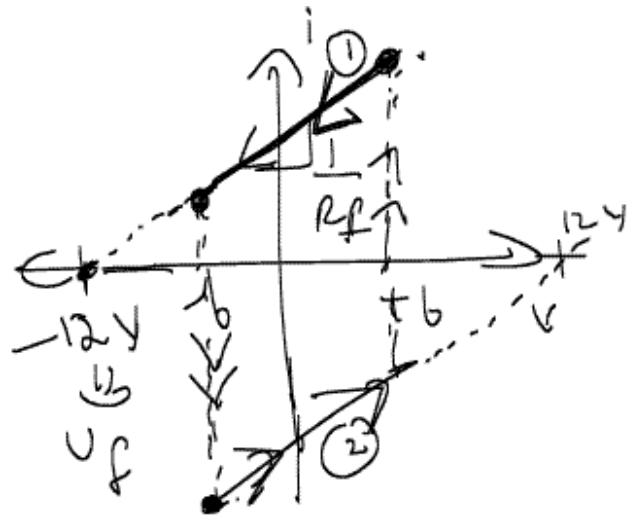

$$V_i = 6 \text{ V}$$

$V_f \equiv$ Capacitor is fully charged


$$\Rightarrow \bar{i} = 0 \Rightarrow -12 \text{ V}$$

$$R_f = 10 \text{ k}\Omega, \quad C = 1 \mu\text{F}$$

$$\therefore v(t) = -12 + (6 - (-12)) e^{-t/10\text{ms}}$$


Region ①

$$v(t) = -12 + 18 e^{-t/10\text{ms}}$$

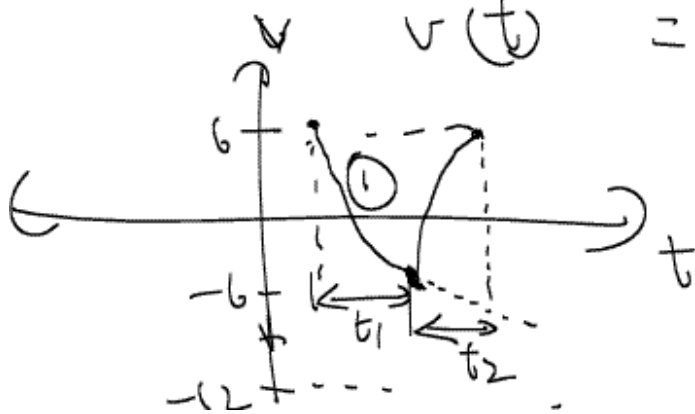

$$\therefore v(t_1) = -6 \text{ V}$$
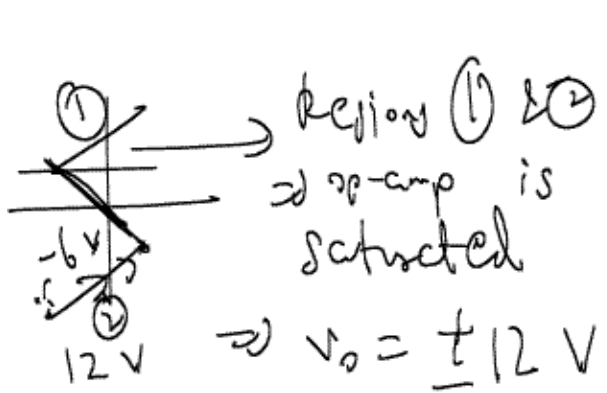
$$\Rightarrow -12 + 18 e^{-t_1/10\text{ms}} = -6$$





$$\Rightarrow 18 e^{-t/10ms} = 6$$

$$\Rightarrow t_1 = -10ms \cdot \ln \left[\frac{6}{18} \right]$$

$$\Rightarrow t_1 = \underline{\underline{11ms}}$$



By symmetry, $t_2 = t_1 = 11ms$
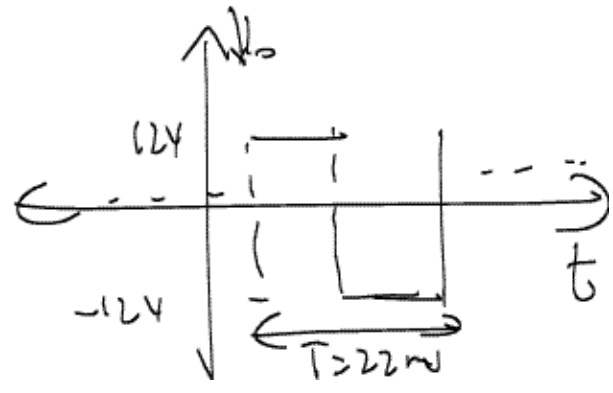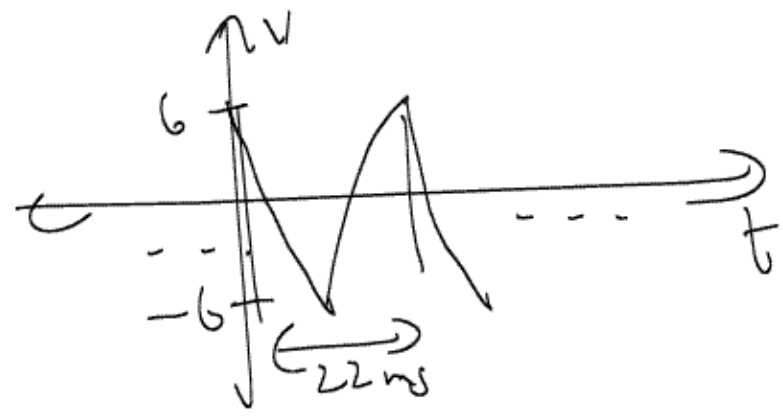
$$T = 22ms \Rightarrow \boxed{f = 45.45 \text{ Hz}}$$



\mathcal{E}_s :

$L = 10 \text{ mH}$

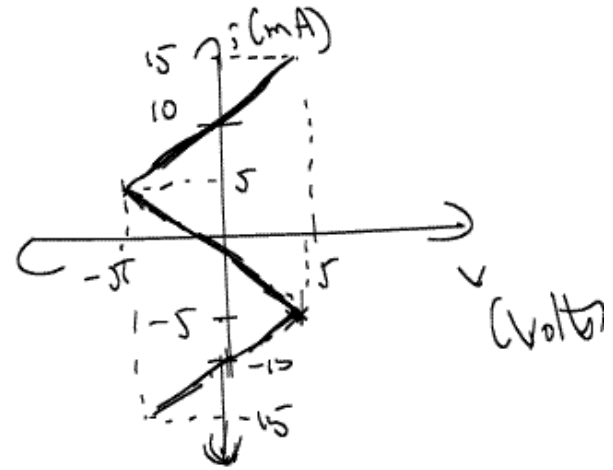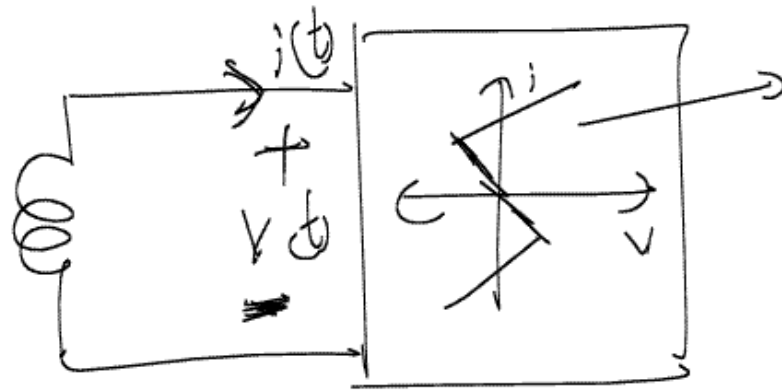

(Q:) What happens?


Start by writing i-v relationship.

eq. points

$$v(t) = -L \frac{di}{dt}$$

stability
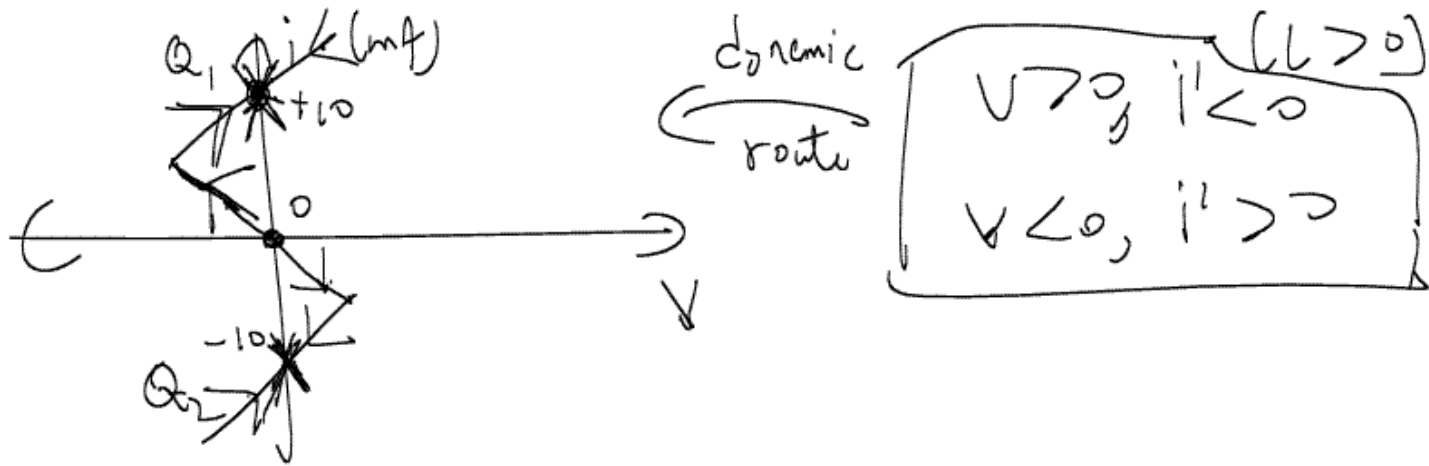
$$\frac{di}{dt} = 0 \Rightarrow -\frac{v}{L} = 0 \Rightarrow \boxed{v = 0}$$



$\therefore (0, 10 \text{ mA}), (0, -10 \text{ mA}) \Rightarrow$ stable equilibria

$(0, 0) \Rightarrow$ unstable equilibrium

This circuit is useful as "memory" \Rightarrow two stable




states $\rightarrow \left. \begin{aligned} (0, 10 \text{ mA}) &\Rightarrow \text{"1"} \\ (0, -10 \text{ mA}) &\Rightarrow \text{"0"} \end{aligned} \right\} \text{ Basis of a computer memory [like flip-flop]}$


(Network question) ^A How do I switch from

Q_1 to Q_2 ?


you give a push!

Answer:

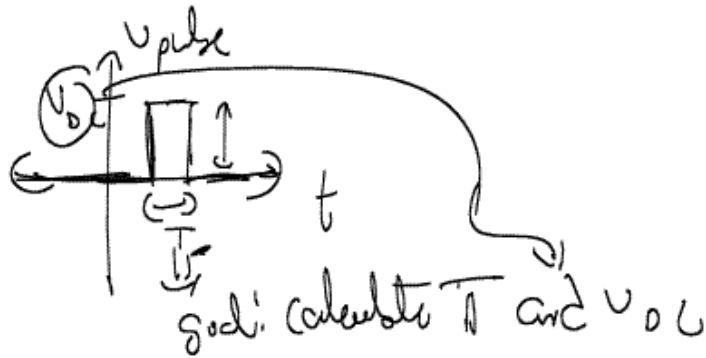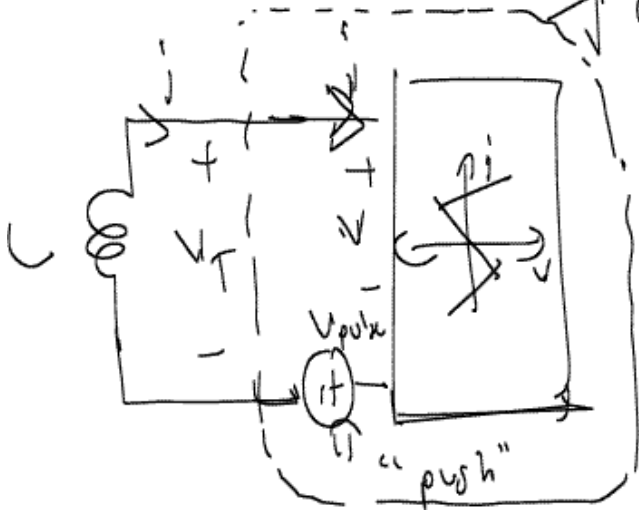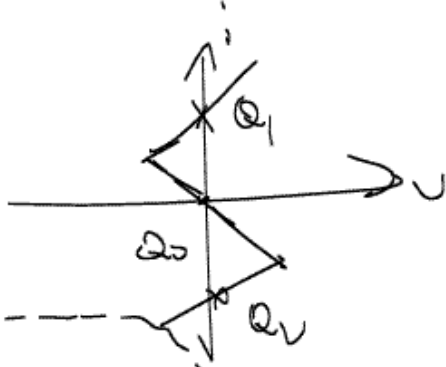


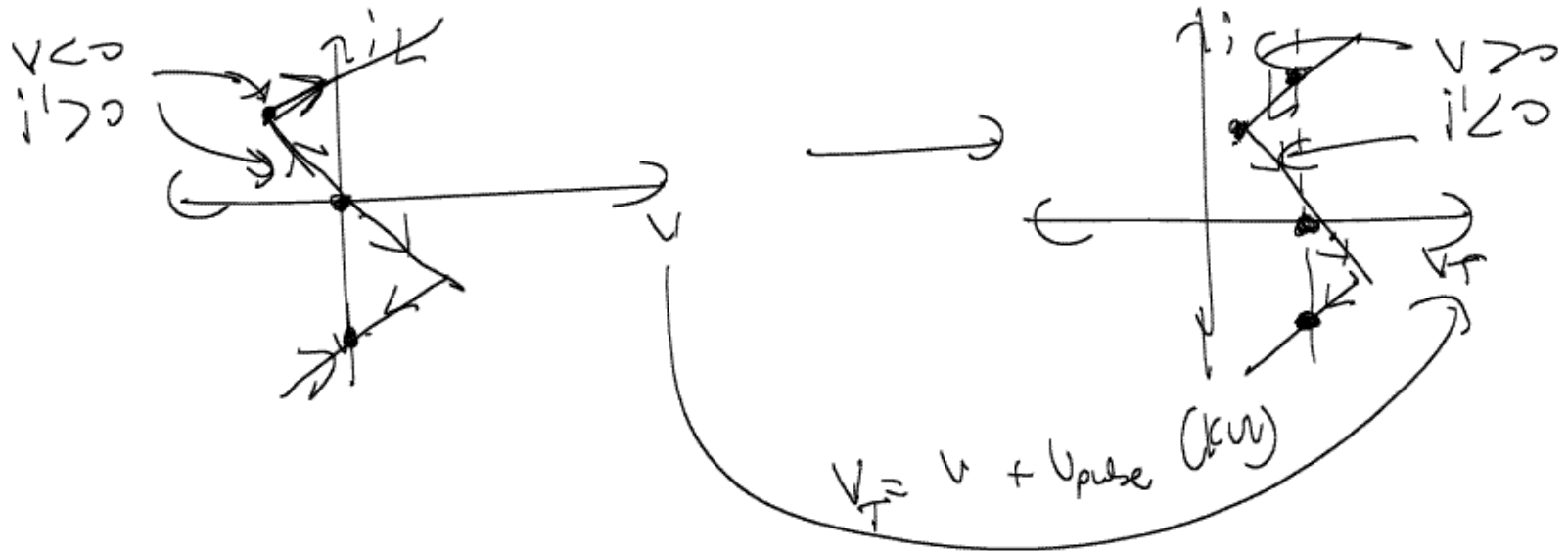


(Q:1) What happens if $V_{DC} = 10V$

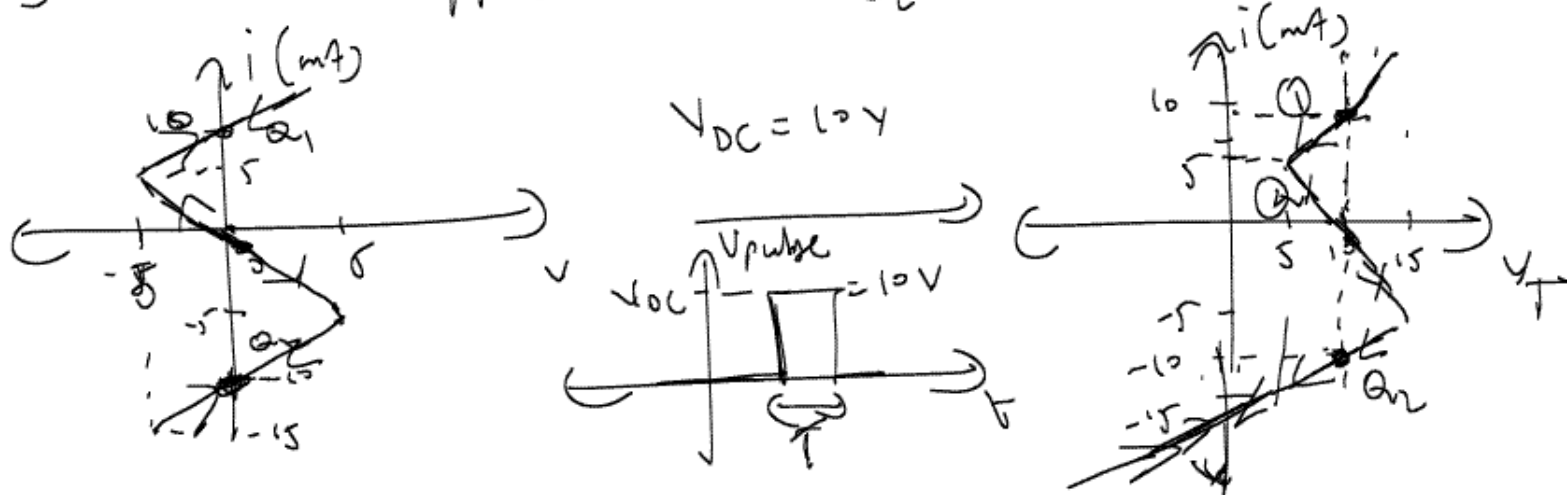

Q:2) What is minimum T ?

Region ①:

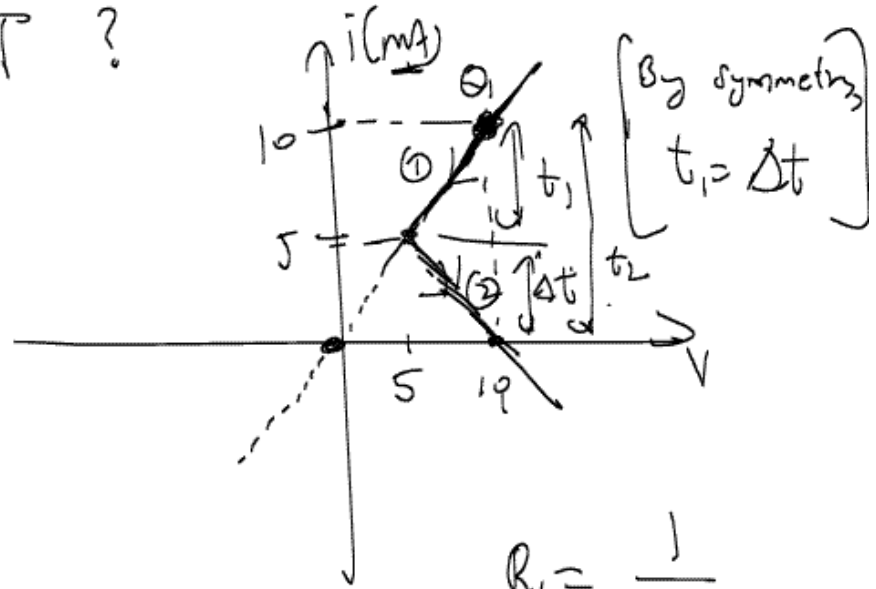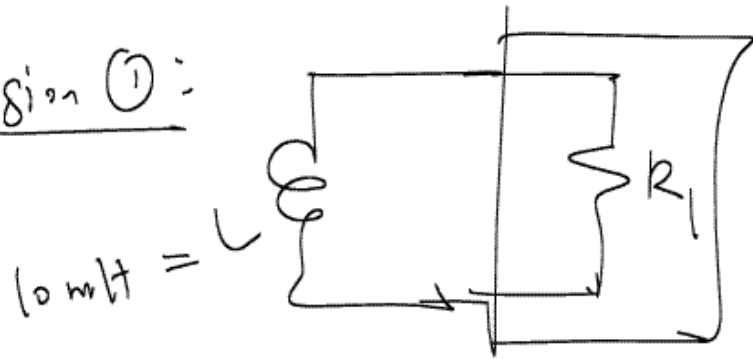

Inductor \Rightarrow v.k $i(t)$

Region ①: $i(t) = i_f + \underbrace{(i_i - i_f)}_{10 \text{ mA}} e^{-t/(L/R)}$

$$R_1 = \frac{1}{\Delta}$$

$$= \frac{1}{\frac{5 \text{ mA}}{5 \text{ V}}}$$

$$= \underline{\underline{1 \text{ k}}}$$

$V=0$ extrapolate to y-axis since if inductor is fully charged.

$$\therefore i_{\text{Region 1}}(t) = 10 e^{-t/10 \mu\text{s}} \text{ mA}$$


$$i_{\text{Region 1}}(t_1) = 5 \text{ mA}$$

$$\Rightarrow 10 e^{-t_1/10 \mu\text{s}} \cancel{\text{mA}} = 5 \cancel{\text{mA}}$$

$$\Rightarrow t_1 = \left[-\ln\left(\frac{5}{10}\right) \cdot 10 \mu\text{s} \right]$$

$$= -[-0.69] \cdot 10 \mu\text{s} = \underline{\underline{6.9 \mu\text{s}}}$$

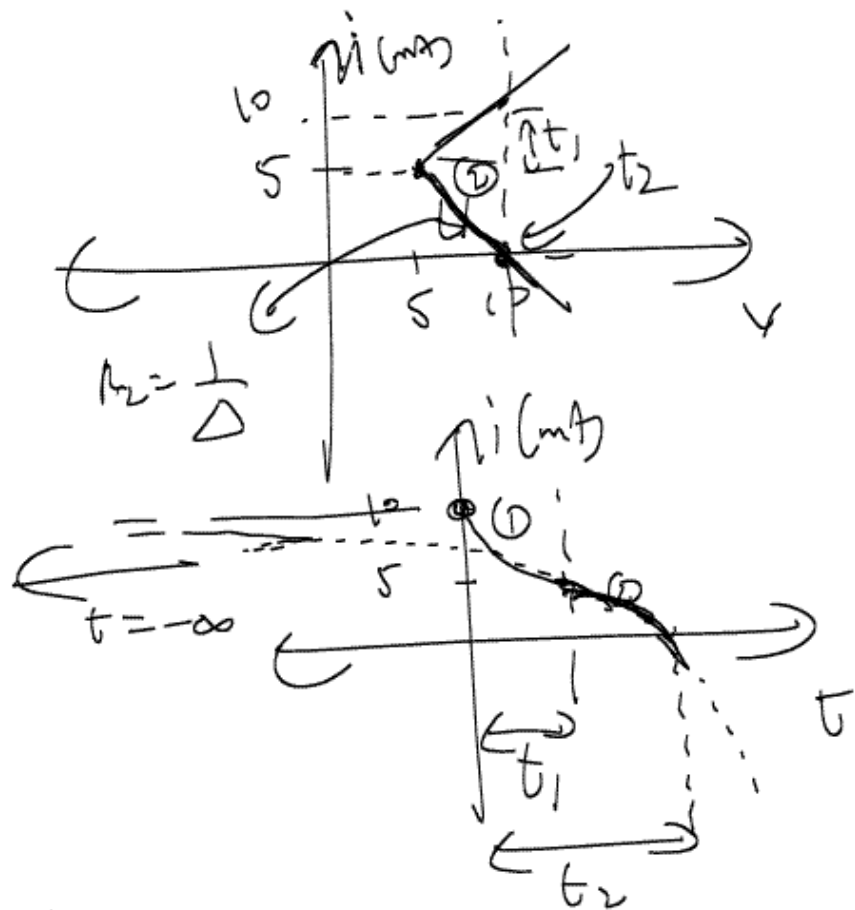Lets do region ②, little tricky because slope is negative!



$$i_{\text{Region 2}}(t) = i_f + (i_i - i_f) e^{-\frac{(t-t_1)}{\tau/R_2}}$$

$$i_f = 5 \text{ mA}$$

$$R_2 = -1 \text{ k}\Omega$$

$$i_{\text{Region 2}}(t) = i_f + (i_i - i_f) e^{-\frac{(t-t_1)}{10 \mu\text{s}}}$$


$$= i_f + (i_i - i_f) e^{\frac{(t-t_1)}{10 \mu\text{s}}}$$

Notice $i_f \neq \lim_{t \rightarrow \infty} i_{\text{Region 2}}(t)$

$$i_f = \lim_{t \rightarrow -\infty} i_{\text{Region 2}}(t)$$

"Trick" \rightarrow But mathematically,

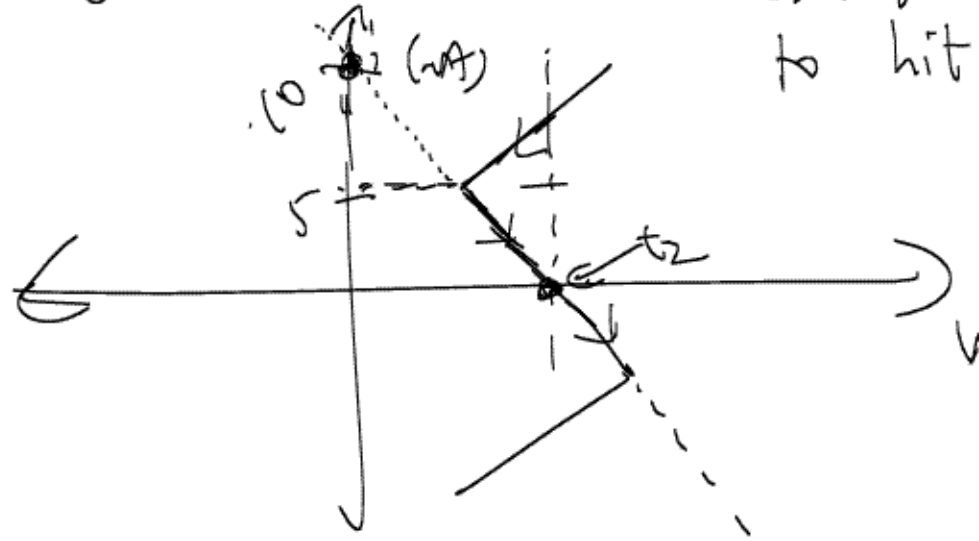Physically: $t \rightarrow -\infty$ "means" capacitor "backwards" to hit y-axis.



$$i_f = 10 \text{ mA}$$

$$\therefore i_{\text{region ②}}(t) = 10 + (5 - 10)e^{-\frac{(t - t_1)}{10 \mu\text{s}}}$$

$$i_{\text{region ①}}(t_2) = 0$$

$$\Rightarrow 10 - 5e^{\frac{(t_2 - t_1)}{10 \text{ us}}} = 0$$

$$\Rightarrow 10 = 5e^{(t_2 - t_1)/10 \text{ us}}$$

$$\Rightarrow (t_2 - t_1) = \underbrace{10 \text{ us} \ln(2)}$$

$$t_2 = 6.9 \text{ us} + 6.9 \text{ us}$$

$$\boxed{t_2 = 13.8 \text{ us}}$$

$$\boxed{T > 13.8 \text{ us}}$$

Next time → More nonlinear op-amp examples
↳ Intro to diodes