

Lecture 21 - Introduction to diodes.

Administrivia → Next week: midterm week

↳ look for info online by the end of this week.

↳ Topics: Op-amps: linear & nonlinear [HW #7]
[HW #8]

↳ Like midterm 1



↳ Thursday (02/07): Review session

↳ Tuesday (04/12): ^{In-lecture} QA session

(? ?) 5:00 pm - 7:00 pm: Justin review

↳ Thursday (04/14): MT II, makeup MT II

Today: (1) Questions from last time:

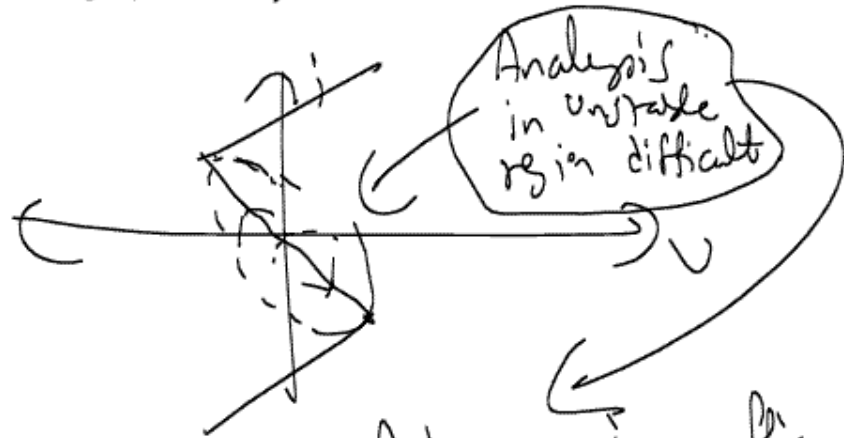
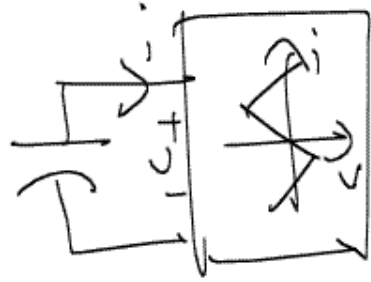


You are not responsible for such difficult regions. Ask me in office hours

For midterm \Rightarrow understand HW due this week, look at midterm II review problems

(2) Diodes: Intro, but first, I just feel like doing this problem:

(Ex.)

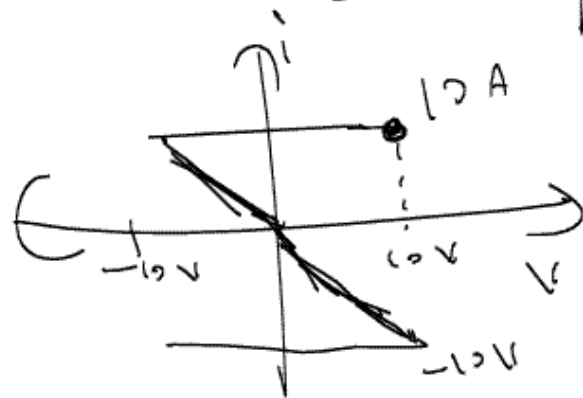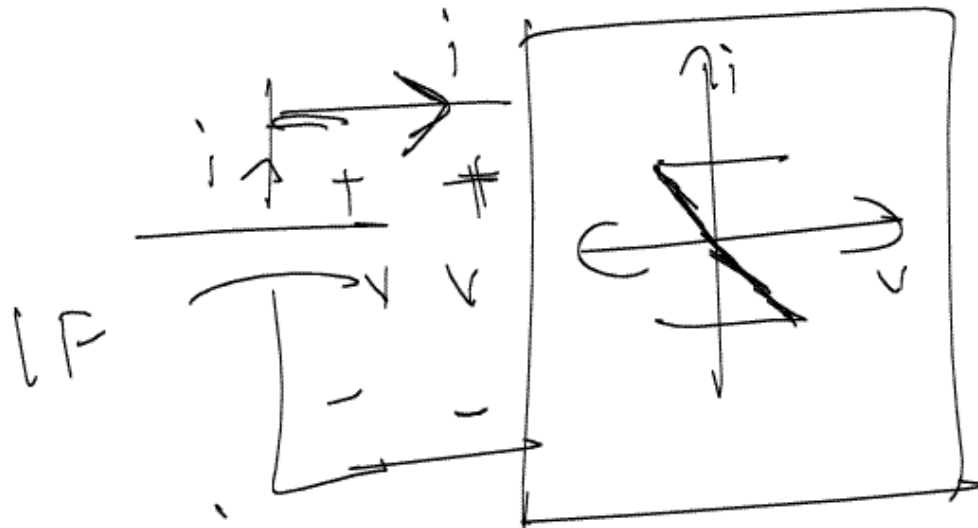

(Q.) ~~Find $i(t)$ & $v(t)$~~

(i) Plot $i(t)$ & $v(t)$

(ii) Find period of oscillator


[Note: I consider this a difficult problem on the midterm.]

Assume $v(0) = 10 \text{ V}$, $i(0) = 10 \text{ A}$

Step 1: Find equilibrium points & dynamic routes.

Eq. points: $f'(t) = 0 \Rightarrow \frac{dy}{dt} = 0 \Rightarrow \boxed{i = 0}$

Impasse point

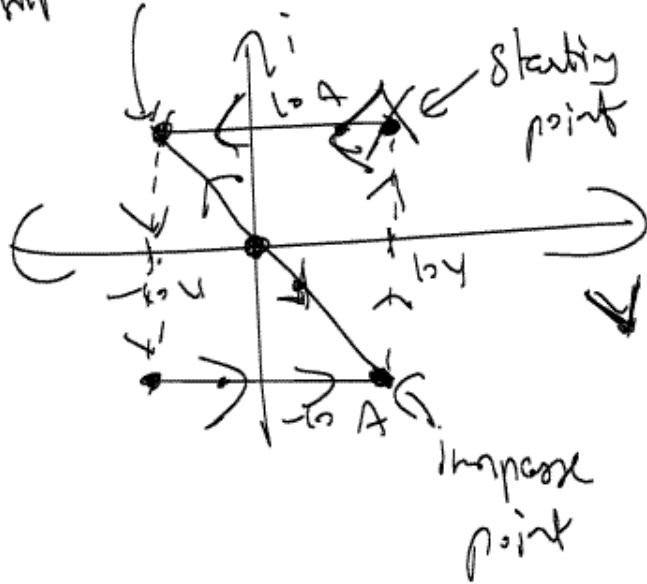



$$[i = -(\downarrow F) \frac{dy}{dt}]$$

Dynamic routes:


$$\begin{cases} i > 0, & v' < 0 \\ i < 0, & v' > 0 \end{cases}$$


be careful, don't
make stupid mistakes

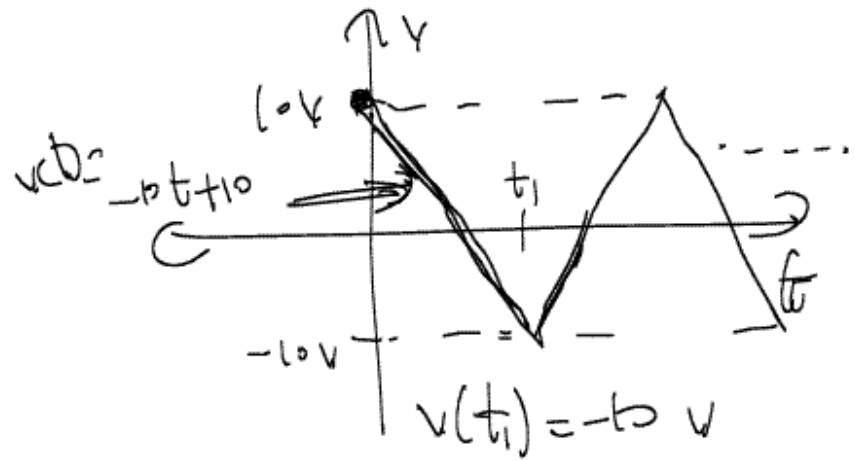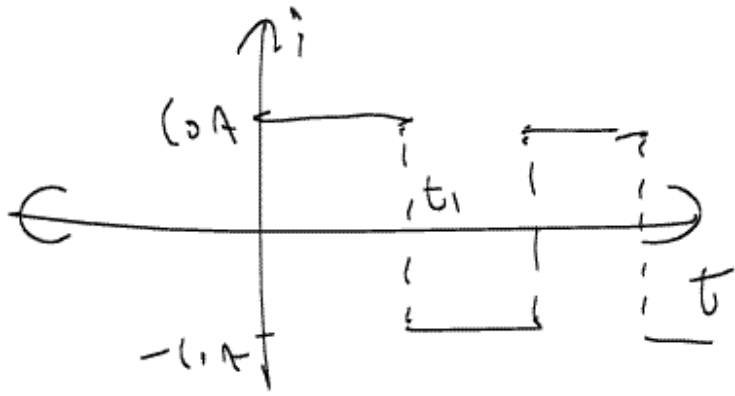Step 2: Good idea to ^{roughly} sketch $i(t)$ & $v(t)$





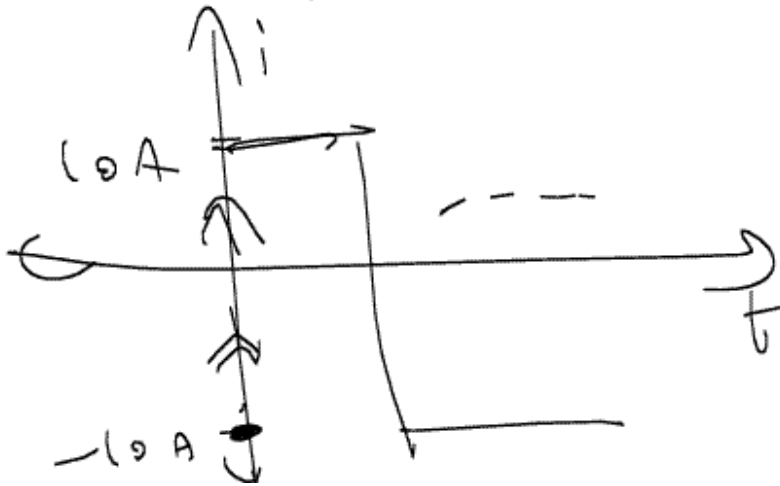Note: If we started at $v(0) = 10V, i(0) = -10A$



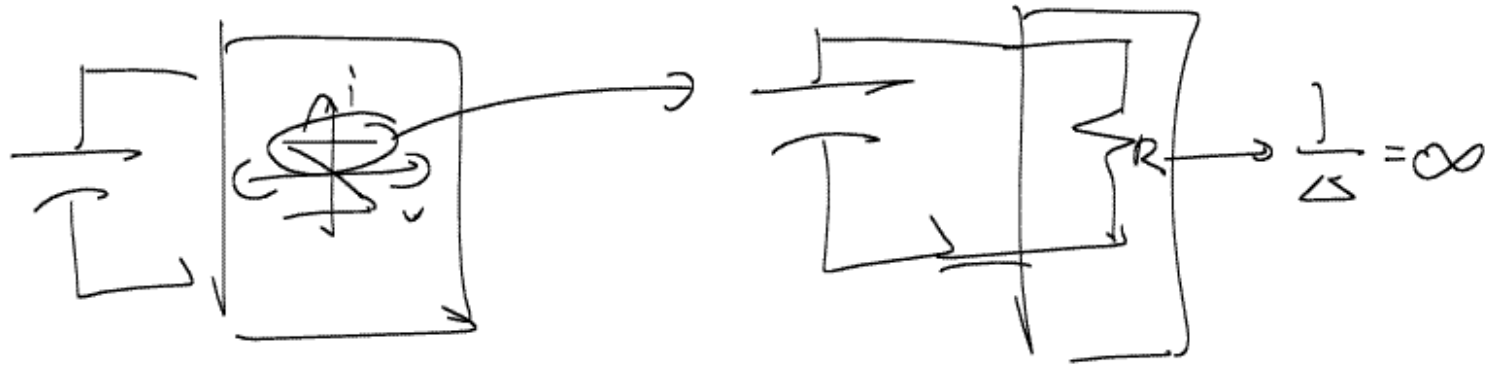

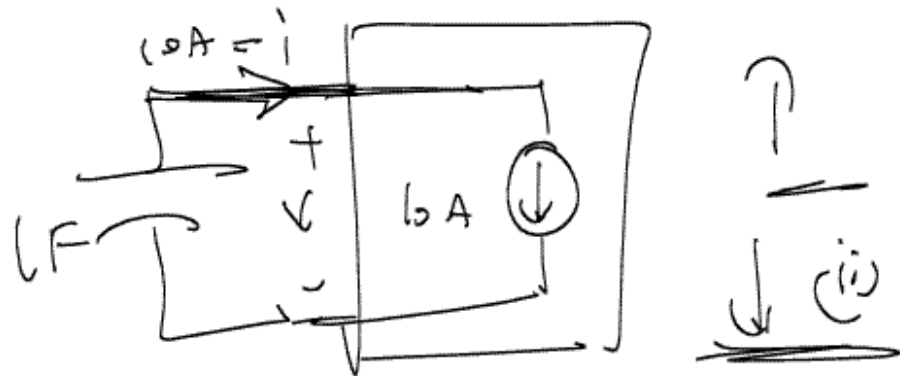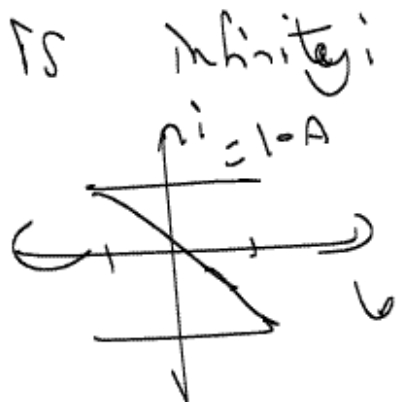This actually makes sense because in
 $V \in [10V, -10V]$, i is constant. In other words,
 the ^{Thévenin} resistance of an ideal current source
 is infinity.





Now, $i = -C \frac{dv}{dt} \Rightarrow 10 \text{ A} = -(1 \text{ F}) \frac{dv}{dt}$

$$\Rightarrow \frac{dv}{dt} = -10 \text{ A}$$

$$\Rightarrow v(t) = -10t + V_0$$

For t_0 , $v_0 = v(0) = 10 \text{ V} \therefore \boxed{v(t) = -10t + 10 \text{ V}}$

Step 3: Find period of oscillation:

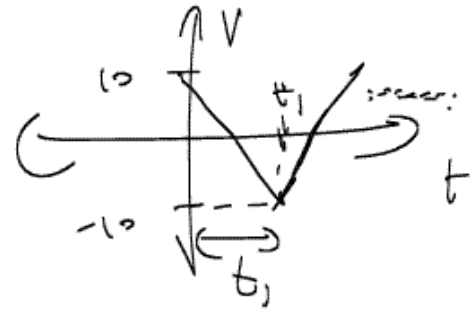
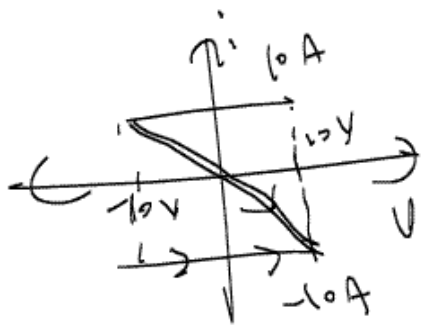


$$v(t_1) = -10$$

$$\Rightarrow -10t_1 + 10 = -10$$


$$\therefore \boxed{T = 2t_1 = 4 \text{ sec}} \Rightarrow t_1 = \frac{-20}{-10} \Rightarrow \boxed{t_1 = 2 \text{ sec}}$$

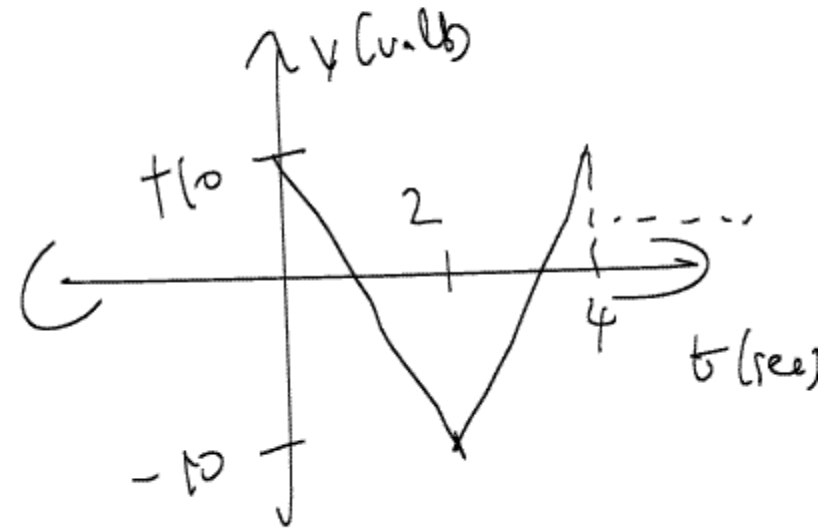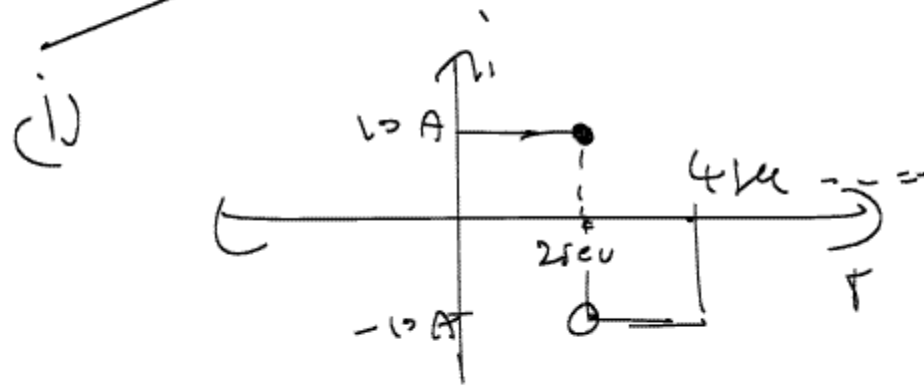~~(i) $i(t) = 10 A$ if $t \in [0, 2 \text{ sec})$~~



(ii) $T = 4 \text{ sec}$


Finally: Diodes

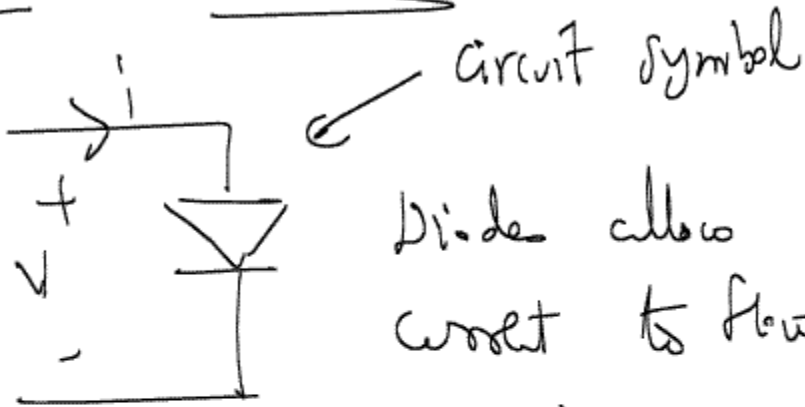

Diodes allow
current to flow

in only one

direction

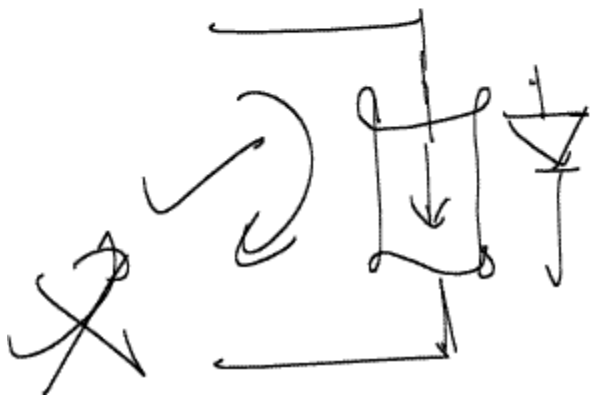


Mechanical Analogy

A diode is a
check-valve

↓
it allows water to
flow in only one
direction.


Ok, so what's hard about diodes \Rightarrow you need non-linearity to capture the behaviour


Reality:

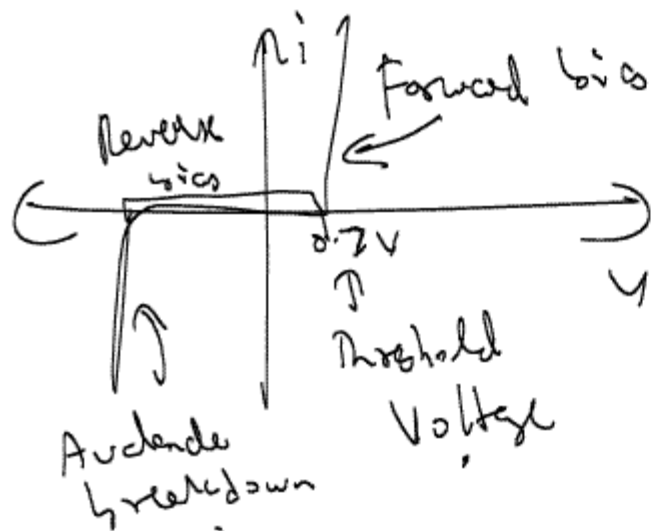



Threshold voltage: when the diode turns "on" \Rightarrow forward bias
mode off \Rightarrow reverse bias

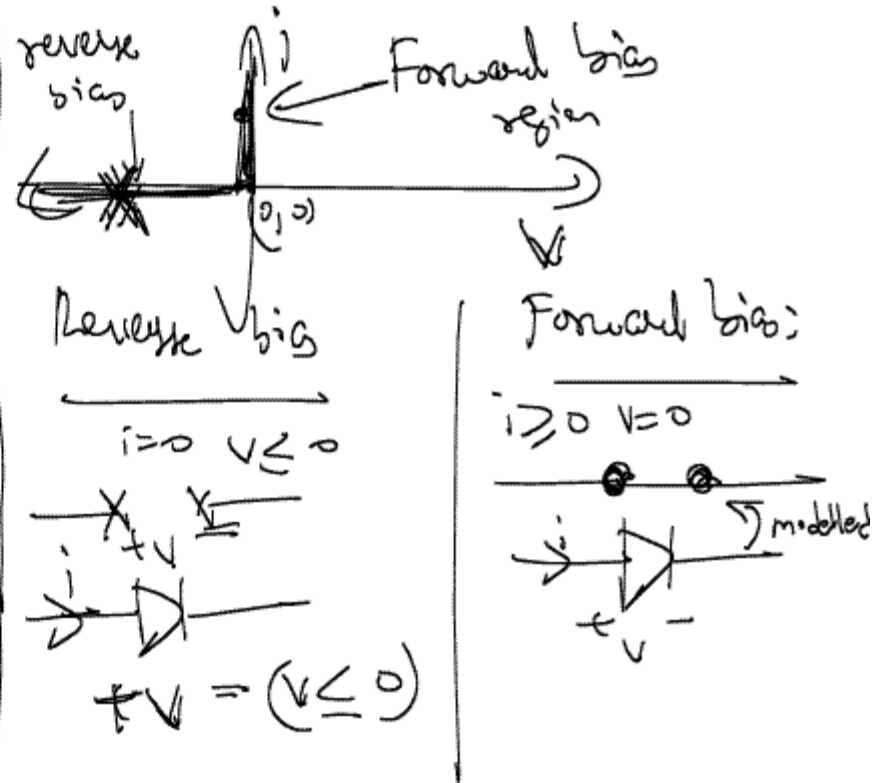
For us: (Ideal diode model)

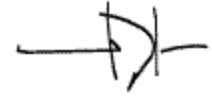

Note: many diodes exist:  : Regular switching diode

 : Zener diode

 : Tunnel diode

 Schottky diode

PS: You need to understand only switching diode


So, what's difficult about diodes is it is difficult to spot what region of operation (i.e., is diode on (or) off) the diode is in.

Moreover: if there is 1 diode in a circuit \rightarrow 2 states
on,
off

if there are 2 diodes \rightarrow 4 states
on, on
off, on
on, off
off, off


In other words, if you have n diodes in a circuit,
we have 2^n states, which is exponential ☹ .

Ex:

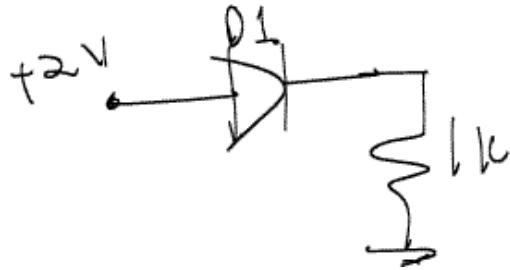

(Q:) Is diode on or off?
(Assume diode is ideal)

Note:

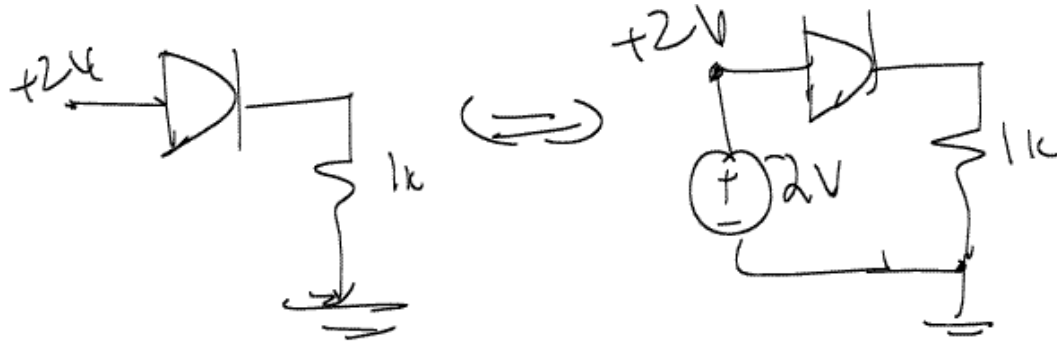

Steps in solving diode problems:

(1) Assume a state for each diode

**[MAKE AN EDUCATED GUESS, IF YOU
DON'T YOU WILL BE SORRY!]**



(2) Solve circuit - i.e., find I_s & V_s in circuit.

No contradictions: 😊. Solved circuit

(3) If you get a contradiction, change state for diodes repeat (2).



Hmm... assume diode off (step c)

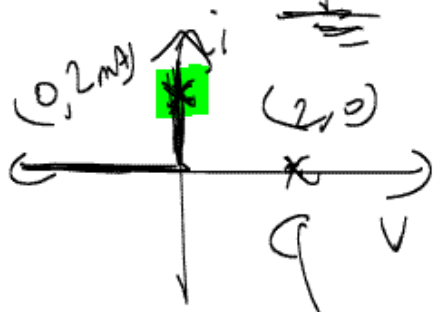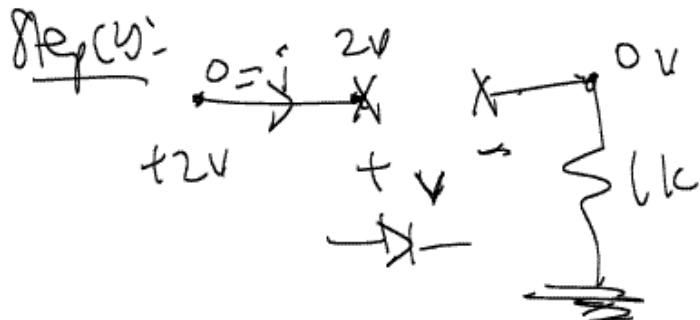


Now, diode is off, $v \leq 0$

INCOMPACT!

$$v = 2V, i = 0$$

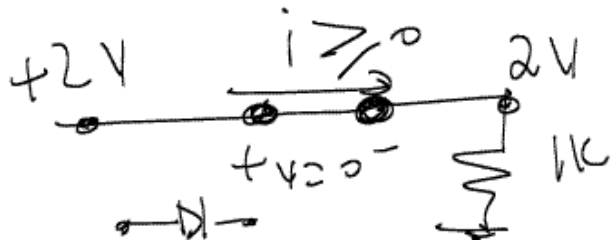\Rightarrow assumption is wrong \Rightarrow diode is on!




$$i = \frac{2V}{1k} = 2mA : (0V, 2mA)$$

Note: (1) $(0\text{ V}, 2\text{ mA})$ is called the operating point

(2) bias point (or) Q-point
(Quiescent) point.


Impart:

(2) What about $(0, 0)$?

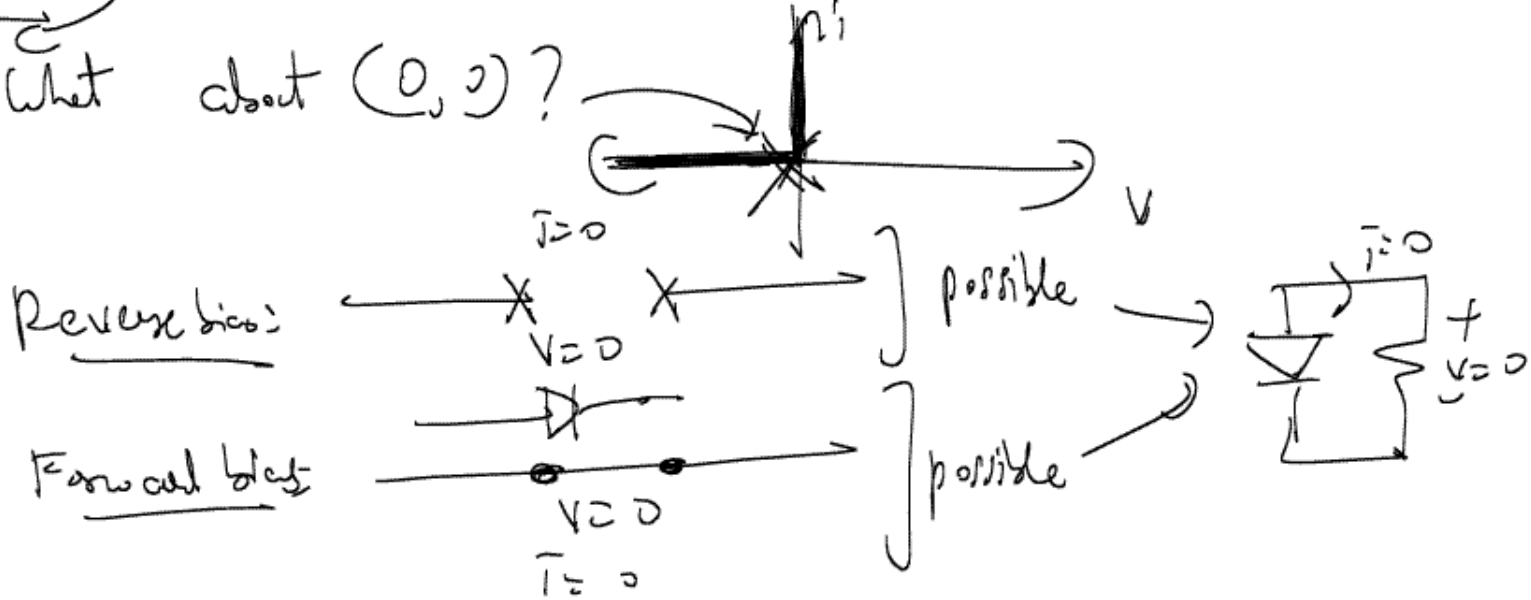

Conclusion: Diode model @ $(0, 0)$ depends on the circuit!

Ex 2:

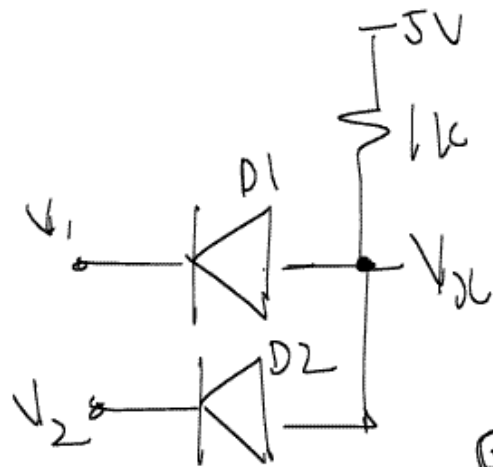


V_1	V_2	V_{out}
0	0	0
0	5	0
5	0	0
5	5	5

Fill in table


Ex (ii):

$V_1 = 0$
 $V_2 = 0$

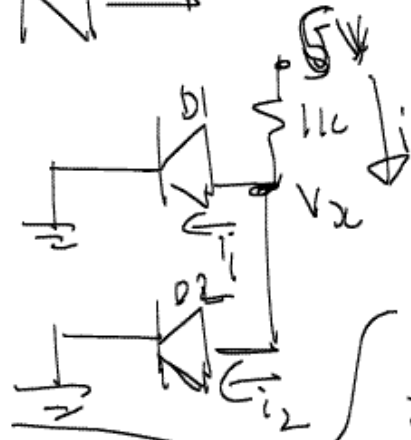

Hmm... looks like diodes are on

$\Rightarrow V_{out} = 0 \text{ V}$

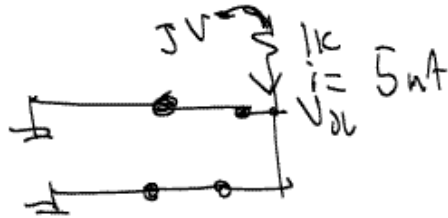

Finish after mt II

Next time: midterm II review
session.

→ look online for review problems
(posted by the end of the
week!)