

# Lecture 22 - MIDTERM II REVIEW SESSION

Administrivia

NO OFFICE HOURS  
TONIGHT  
[H.W IS EASY, 😊]

MIDTERM II REVIEW PROBLEMS  
ETC. WILL BE UP  
BY TOMORROW (04/08/05)

MIDTERM I → "ORGANIZATION" SAME AS MIDTERM I.

↳ Next Thursday (04/14)

↳ 2:00 pm - 5:00 pm, "MAKEUP" <sup>299 (000)</sup>  
(POST ON NEWSGROUP IF  
YOU WANT TAKE MAKEUP  
BY TOMORROW, (04/08),  
5:00 pm, P.S.T)

↳ 6:00 pm - 9:00 pm, 1 PLENARY


↳ 4 problems, all oramps.

- 4 problems
- (1) Op amp analysis <sup>(I)</sup> (like HW #7 i.e. chapter 5 problems)
  - (2) Flip-flop (like HW #9 problems from section, p-328)
  - (3) Op amp analysis <sup>(II)</sup> (little more difficult than (I))
  - (4) Oscillator (cc ←)

Note: "nice numbers" → e.g.  $24.99999999 = 25$   
 i.e. calculator not required.


Note:

(1)

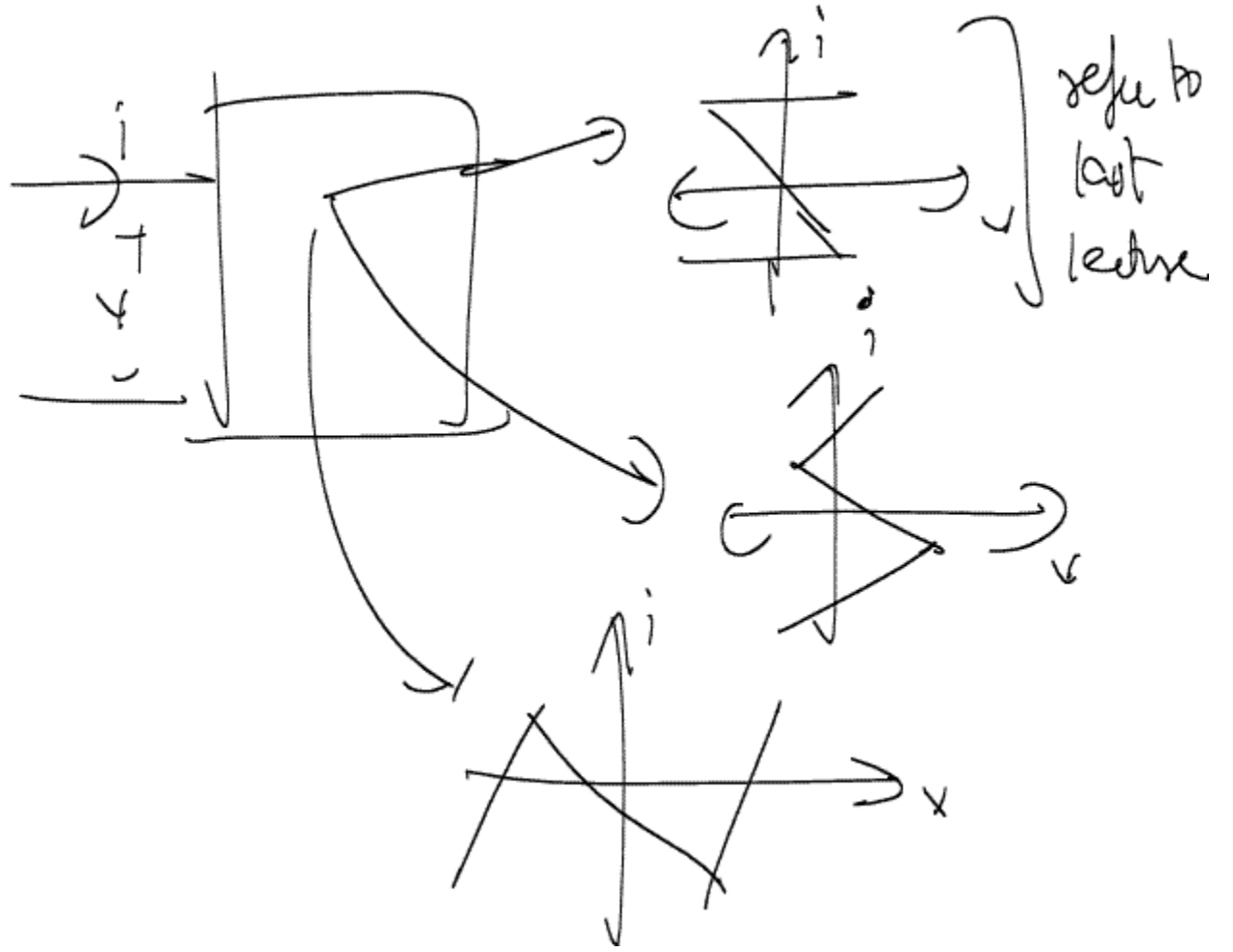


ps: Modelling dependent sources using op-amp:


VCVS

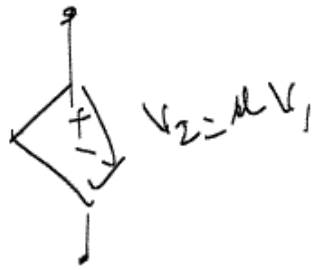



VCCS

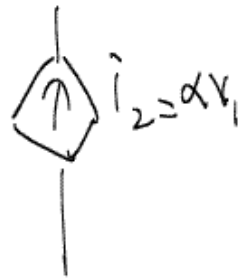

CCVS

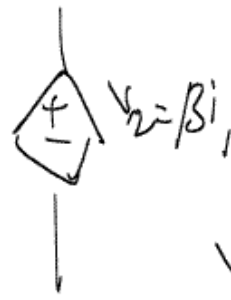


CCCS

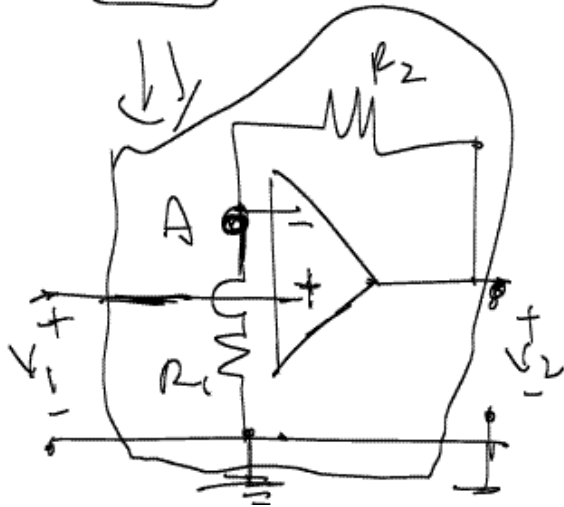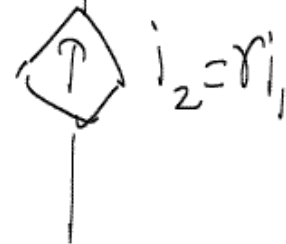

VCVS

Notice:

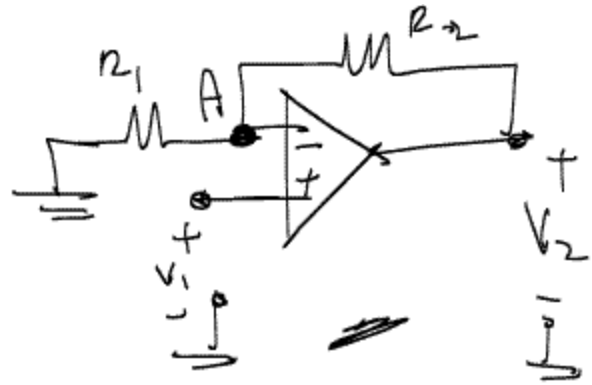


$$v_2 = \left(1 + \frac{R_2}{R_1}\right) v_1$$

$\underbrace{\hspace{10em}}_{\mu} \quad [\mu \geq 1]$


Non-inverting amplifier

If we want  $\mu < 1$

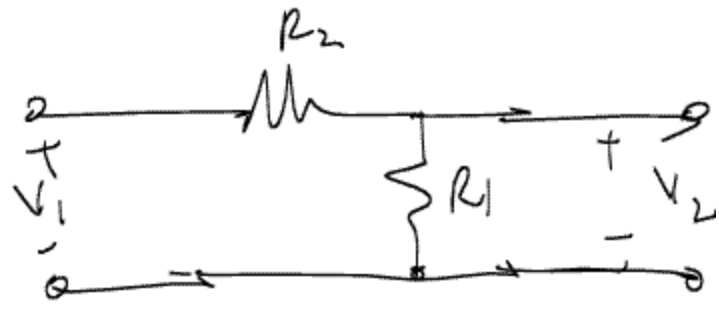

$$v_2 = \left(\frac{R_1}{R_1 + R_2}\right) v_1$$

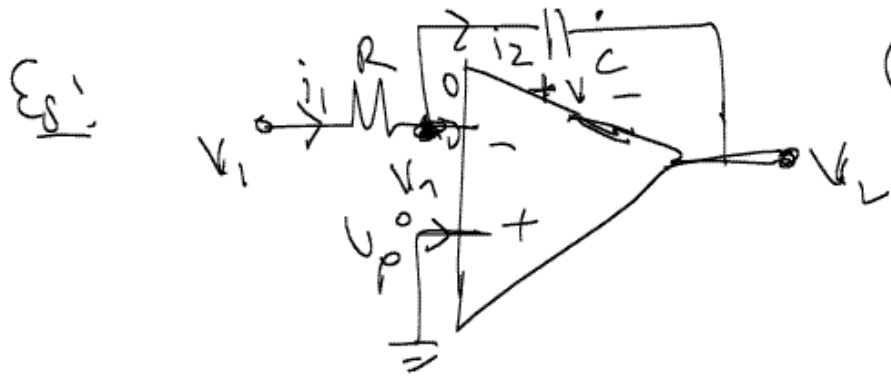$\underbrace{\hspace{10em}}_{\mu} \quad [\mu < 1]$



(Q.1) Find  $v_2 = f(v_1)$

ignore rails,  
assume op-amp  
is always ideal

Step 1):  $v_p \approx v_n, v_n = 0$


since  $v_p = 0$

Step 2): KCL @  $v_n$ :

$$i_1 = i_2 \Rightarrow$$


$$\frac{v_1 - 0}{R} = i_2 = C \frac{dv}{dt} = C \frac{d(0 - v_2)}{dt}$$

$$\boxed{i_2 = -C \frac{dv_2}{dt}}$$

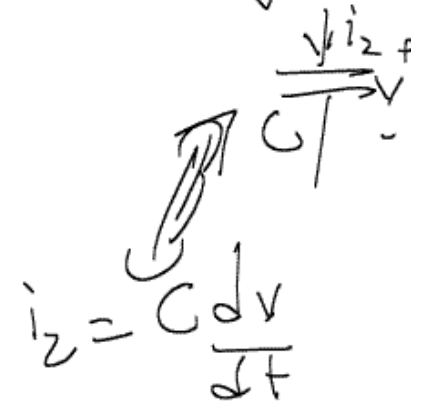


$$\frac{v_1}{R} = -C \frac{dv_2}{dt} \Rightarrow \boxed{v_2 = -\frac{1}{RC} \int v_1 dt}$$


Ex:

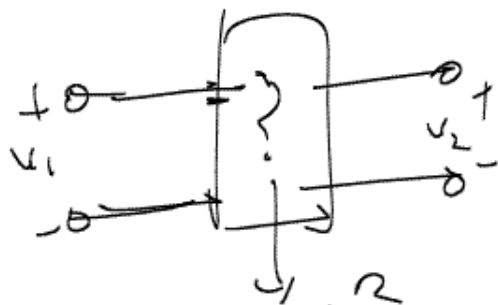

$$v_2 = \beta \frac{dv_1}{dt}$$

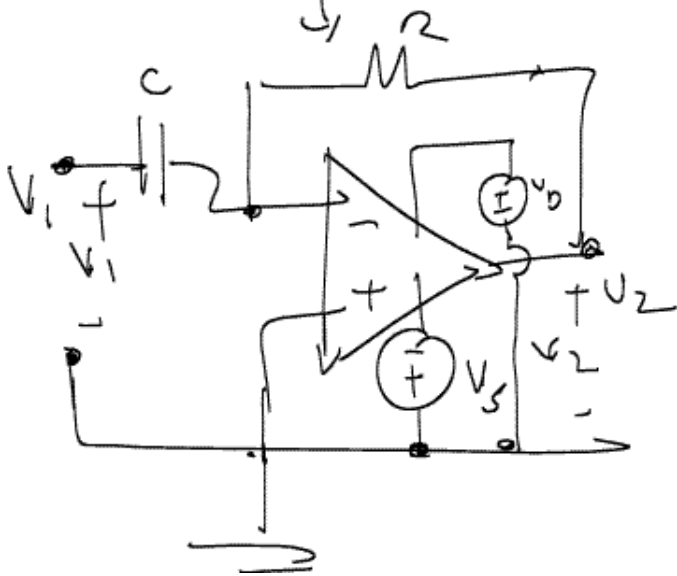



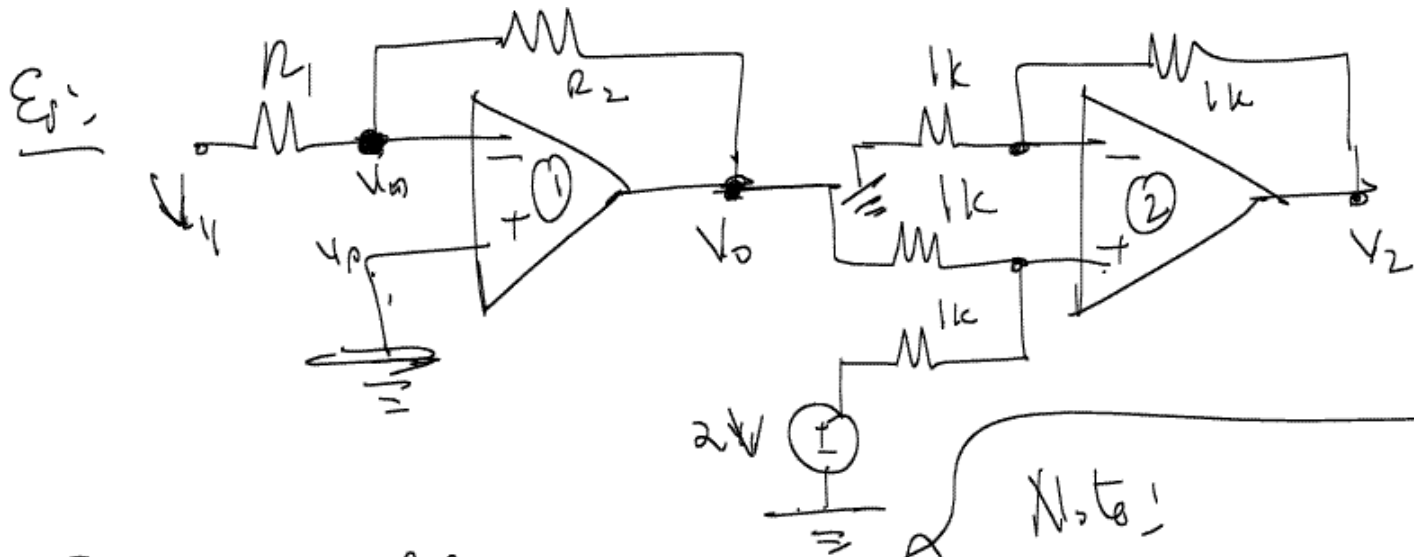

Find  $V_2 = f(V_1)$

P-1 (1)  $\Rightarrow$  inverting amplifier

$$V_0 = f(V_1) = \frac{-R_2}{R_1} V_1 \quad \text{--- (1)}$$

$\downarrow$  derivation in book, previous lecture notes

Note!

on your cheat sheet


$\hookrightarrow$  voltage follower

$\hookrightarrow$  inverting amplifier

$\hookrightarrow$  non-inverting amplifier

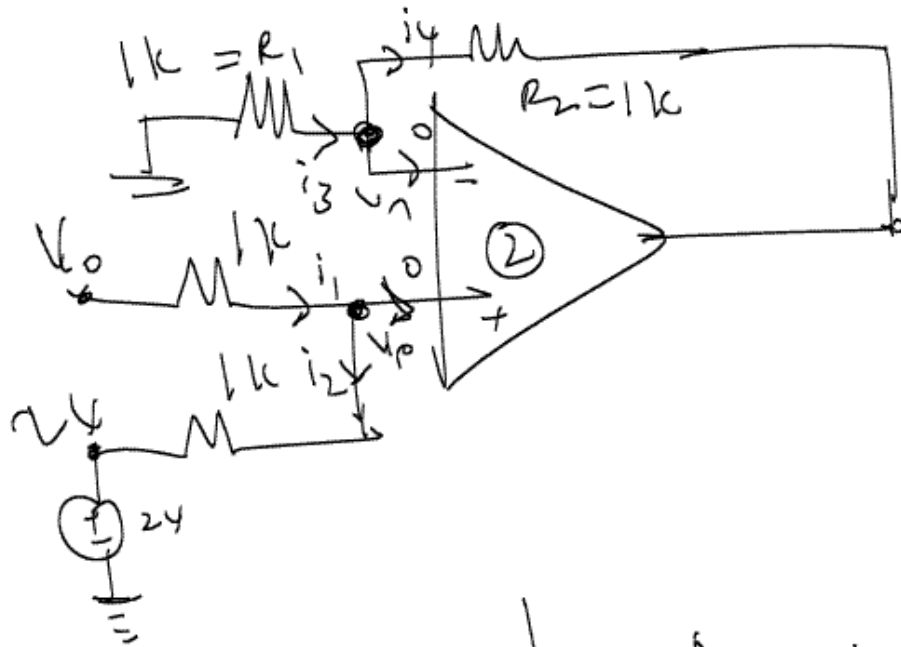$\hookrightarrow$  inverting summing amplifier, etc...





$$V_2 = f(V_1)$$

$V_2$

Step ①:  $V_p \approx V_n$ ,

here you have to find  $V_p$ .

KCL @  $V_n$ :  $i_3 = i_4$

$$\Rightarrow \frac{0 - V_n}{1k} = \frac{V_n - V_2}{1k}$$

↓

Now KCL @  $V_p$ :  $i_1 = i_2$

$$\Rightarrow \frac{V_0 - V_p}{1k} = \frac{V_p - 2}{1k}$$

$$\Rightarrow V_0 + 2 = 2V_p \Rightarrow \boxed{V_p = \frac{V_0 + 2}{2}}$$


$$\downarrow$$

$$\Rightarrow -V_o = V_n - V_2$$

$$\Rightarrow V_2 = 2V_n = 2V_p = 2 \left[ \frac{V_o + 2}{2} \right] \Rightarrow \boxed{V_2 = V_o + 2}$$

$$\therefore \left. \begin{aligned} V_o &= -\frac{R_2}{R_1} V_1 \\ V_2 &= V_o + 2 \end{aligned} \right\} \Rightarrow \boxed{V_2 = -\frac{R_2}{R_1} V_1 + 2}$$

②

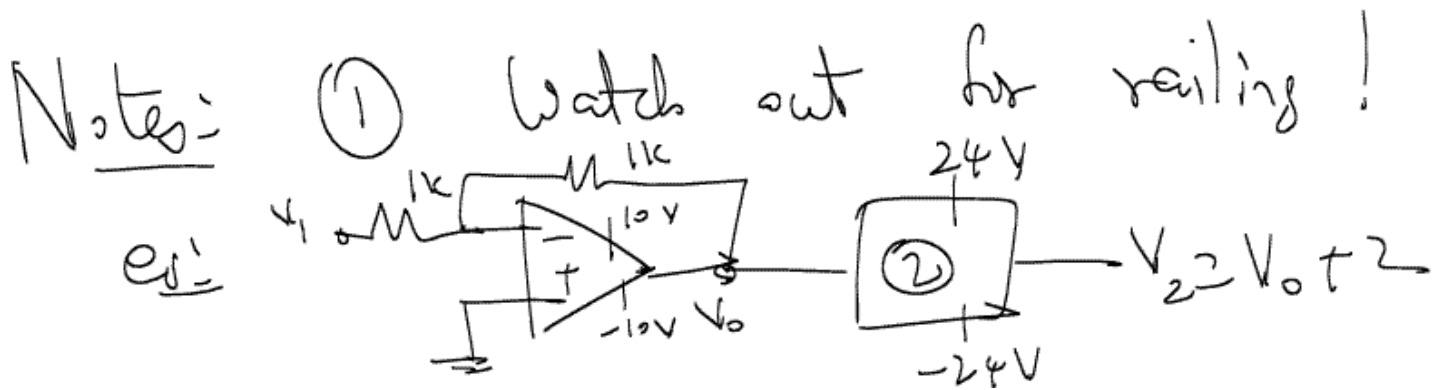

$$\Downarrow \quad V_1 = 20 \text{ V}, \quad V_2 \stackrel{?}{=} -\left(\frac{1\text{k}}{1\text{k}}\right)(20) + 2 \quad (\text{From eqn. (2)})$$

$$V_2 \stackrel{?}{=} -18 \text{ V} \quad \text{increased}$$

because  $V_o \neq -\left(\frac{1\text{k}}{1\text{k}}\right)20 = -20 \text{ V} \rightarrow$  op-amp ① rails!!!!

$\therefore V_o = -10 \text{ V}, \quad \boxed{V_2 = -8 \text{ V}}$

② Why do you need an offset "amplifier"?

