

Lecture 23 - Q/A session for MT II.

- Administrivia → Grade corrections will be addressed after MT II
- Justin's review session tonight (5-7) in 101 Morgan
- Review problem solutions up by tonight

Note: TBP Telebears advising sessions
(FREE FOOD!)

Tu Apr. 12 Mon. Apr. 18 Wed. Apr. 20th

6 pm - 8 pm
Wozniak
Lounge
4th floor
Soda hall

Midterm \rightarrow ① op-amps I (cascade ?) (25 pts)

(3 points
for filling
out front
page correctly)

② Dynamic route I (e.g. oscillators) (30 pts)

③ Dynamic route II (e.g. flip-flop) (30 pts)
Lecture 20

④ op-amp II (difficult ?) (12 pts)


Total: 100 pts

Important concepts:

Eg. point: $f'(t) = 0$

Dynamic route: Illustrate
($i(t), v(t)$)
on i-v graph

Op-amps \rightarrow linear $v_o = A(v_p - v_n)$ v_o 
 \rightarrow Saturation (i.e., railings)

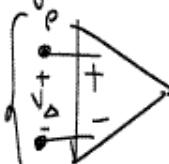$v_o > 0$  $v_o = +ve \text{ rail}$

$v_o < 0$  $v_o = -ve \text{ rail}$

$$V_{in} = 1 \text{ V}, V_o = \left(1 + \frac{1k}{1k}\right) 1 \text{ V}$$


$$= 2 \cdot 1 = 2 \text{ V}$$

Hence $2 \text{ V} < 12 \text{ V}$

\Rightarrow Op-amp does not rail

$$\Rightarrow v_p \approx v_n = 1 \text{ V}$$

E_o :

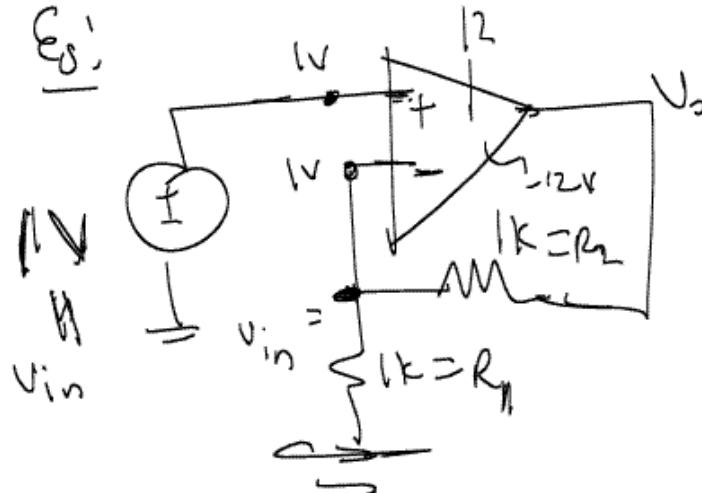


Non-inverting topology: $V_o = \left(1 + \frac{R_f}{R_1}\right) V_{in}$

Cheat sheet: inverting amplifier


noninverting amplifier

voltage follower

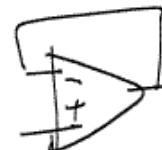inverting summing amplifier, differential amplifier




Note: Purpose of voltage follower:

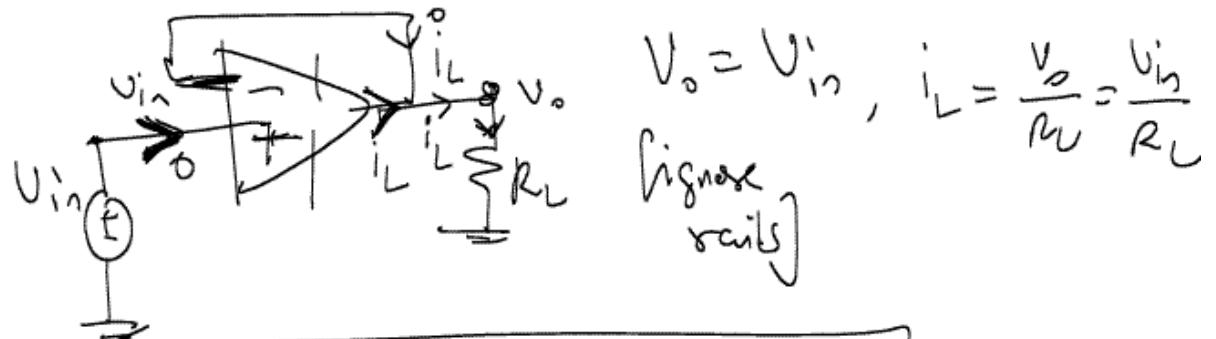


⇒ V_{in} does not put out any current,
op-amp does all the work!!!.

Eg 2:

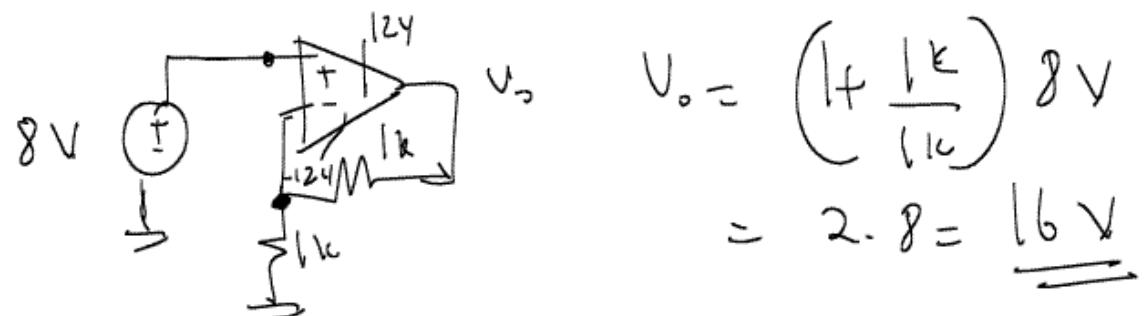

OpA, $V_o = 12V$ [op-amp reils]

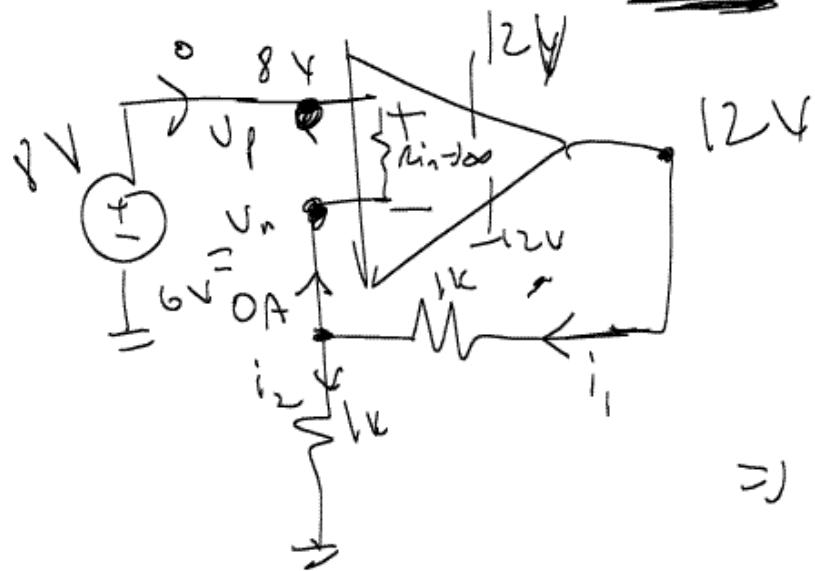
i.e., $V_o = \left(1 + \frac{R_2}{R_1}\right)V_{in}$ is invalid




$$i_1 = i_2 \text{ (kCL @ } V_n\text{)}$$

$$\Rightarrow \frac{12 - V_n}{1k} = \frac{V_o}{1k}$$
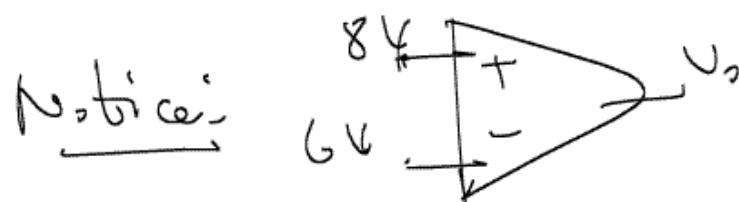
$$\Rightarrow 12 = 2V_n \Rightarrow \boxed{V_n = 6V}$$



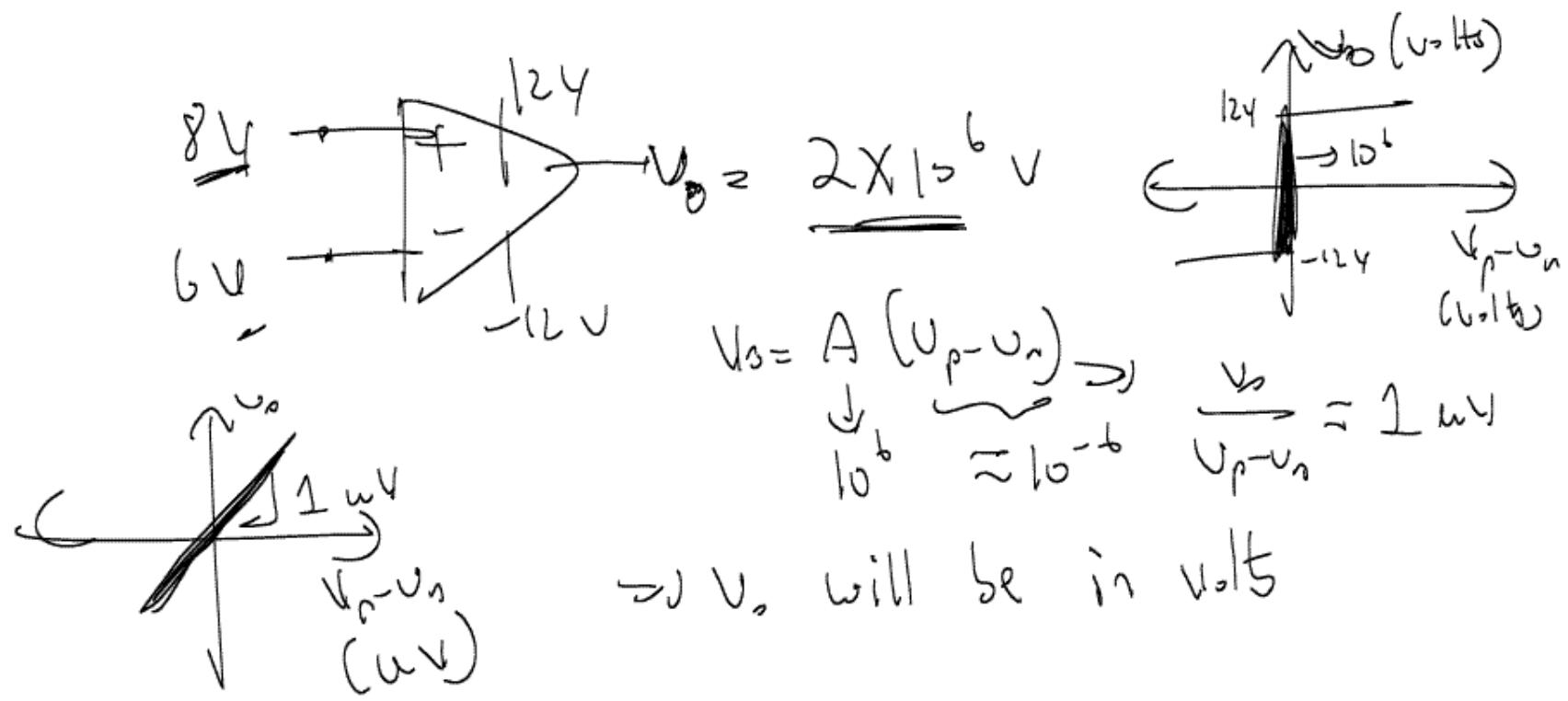
$$\boxed{V_o = A \left(\frac{V_p - V_n}{A} \right) + 6V} \approx 2 \times 10^5 V$$



Questions on Review Problems

2(b) : Prev. equivalent at AB :

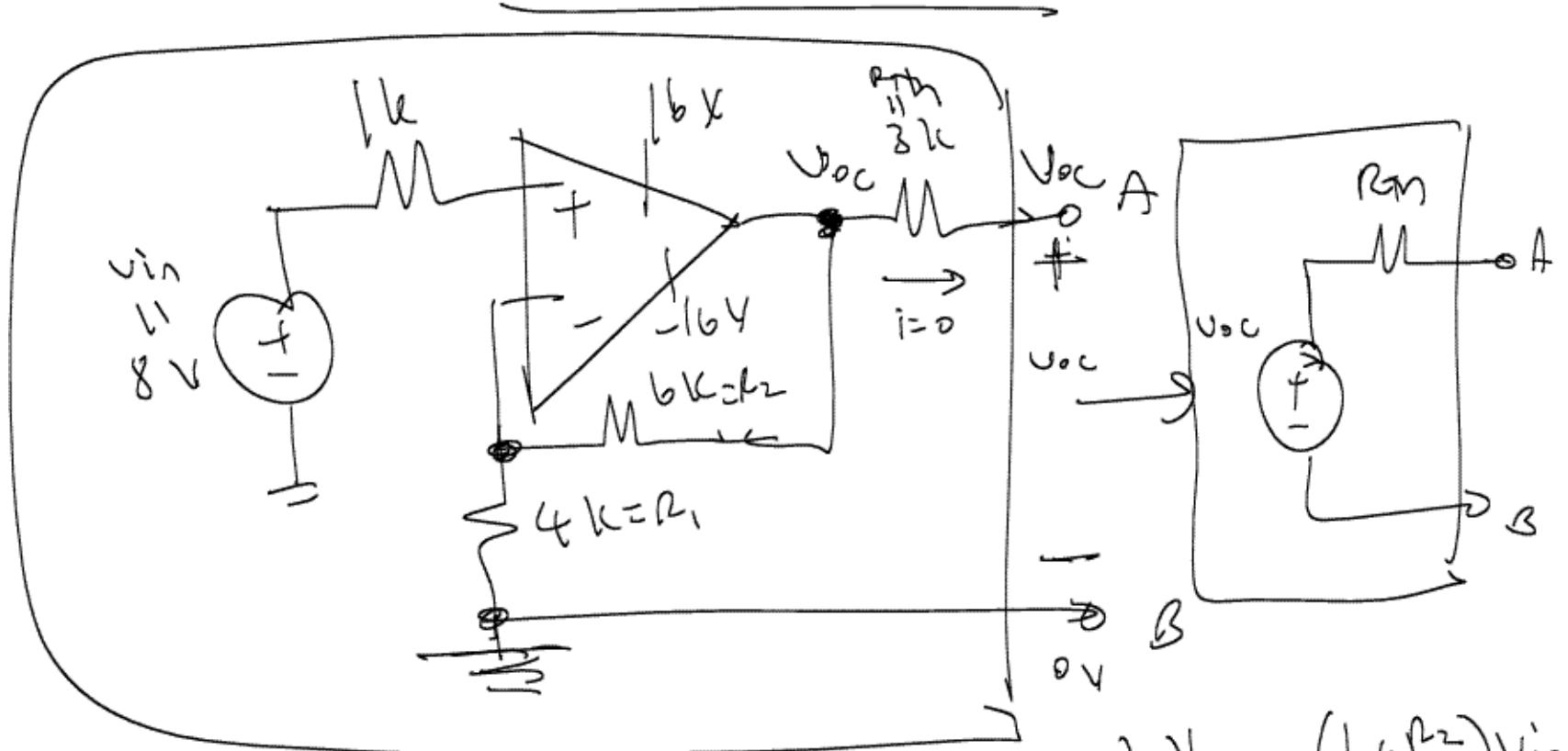

V_{oc} = Output voltage of the op-amp



$$V_{oc} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

Op-amp unity


$$V_{o.c} = 16 \text{ V}$$


$$= \left(1 + \frac{6k}{4k}\right) 8$$
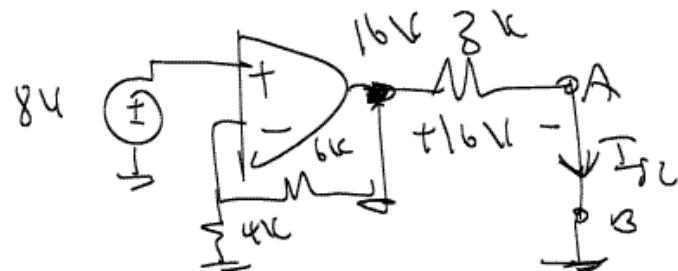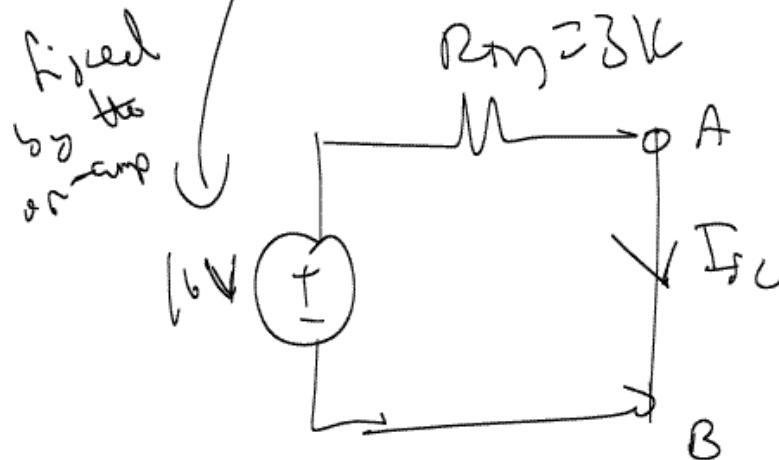
$$2.5 \cdot 8 \text{ V} = \underline{\underline{20 \text{ V}}}$$



$$I_{SC} = \frac{16 \text{ V}}{3 \text{ k}}$$

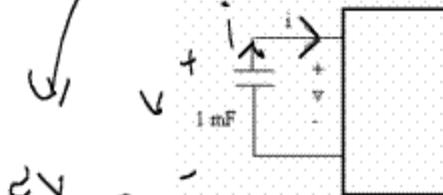
$i = -(\text{mF}) \frac{dv}{dt}$

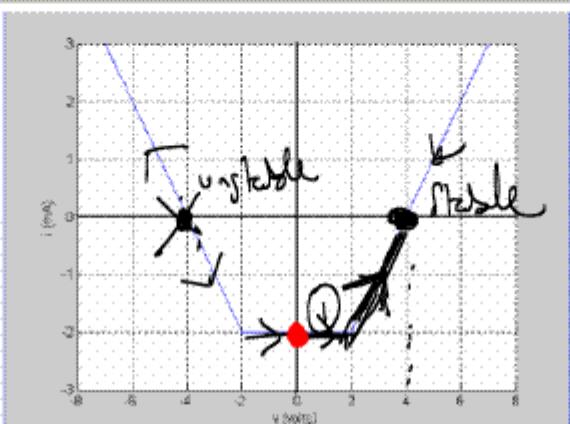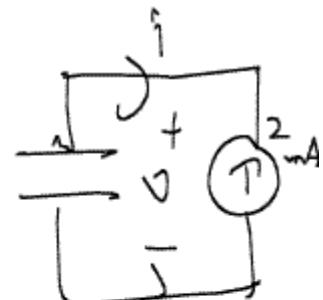
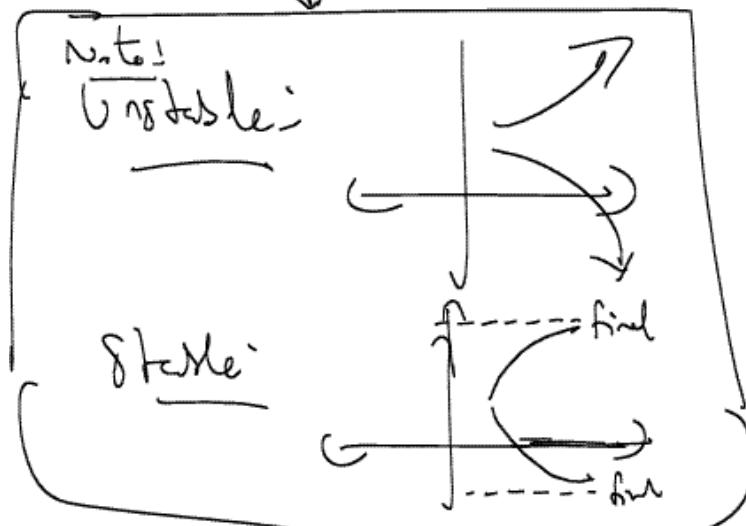
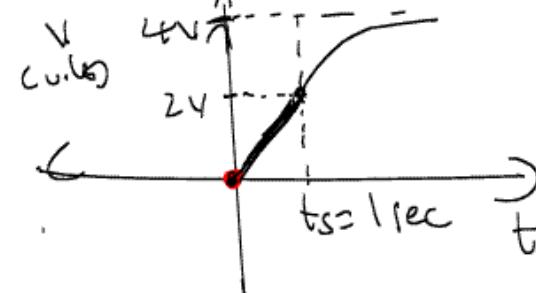
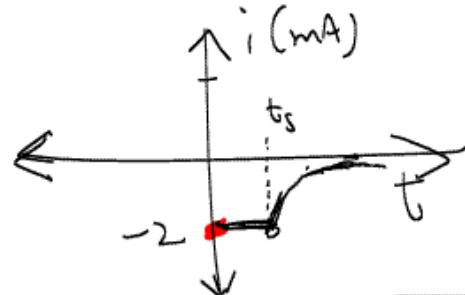


The i - v graph of the nonlinear circuit element is shown in the figure above. Assuming $v(0) = 0$ V:
 $\Rightarrow i = 0$

(a) Find the equilibrium points and sketch the dynamic route.
 (b) Sketch $i(t)$ and $v(t)$, make sure to mark the switching times on the graph(s).

$i > 0, v' < 0$
 $i < 0, v' > 0$





$$i(t) = \begin{cases} -2 \text{ mA} & \text{if } t < t_s \\ -2 e^{-\frac{(t-t_s)}{\tau}} \text{ mA} & \text{if } t > t_s \end{cases}$$

$$i(t) = -2 \text{ mA} \quad \text{for } t < t_s$$

$$\Rightarrow -(\text{1 mF}) \frac{dy}{dt} = -2 \text{ mA}$$

$$\Rightarrow \frac{dy}{dt} = 2 \Rightarrow v(t) = 2t + v_{\text{initial}}$$

$$v_{\text{initial}} = v(0) = 0 \text{ V}$$

$$v(t) = 2t \text{ Volts}$$

$$v(t_s) = 2V \Rightarrow t_s = 1 \text{ second}$$

Problem]

(a)

$$i = (-1 \text{ mF}) \frac{dy}{dt}$$

$$\frac{dy}{dt} = 0 \Rightarrow i = 0$$

The $i-v$ graph of the nonlinear circuit element is shown in the figure above. Assuming $i(0) = 0.5 \text{ mA}$: $v(0) = 1.5 \text{ V}$

(c) Find the equilibrium points and sketch the dynamic route.


(d) Sketch $i(t)$ and $v(t)$, make sure to mark the switching times on the graph(s).
(Hint: for the unstable part, think carefully about the final values of i and v).

You should look over the flip-flop example from Lecture 20 on the EE100 homepage.
MAKE SURE YOU UNDERSTAND THIS PROBLEM FOR THE MIDTERM! Of course, you could surf <http://hkn.eecs.berkeley.edu/student/onlineexams.shtml> for online exams from EE10 and EE100, but many of these problems are way too difficult and

Done

start Lecture23 http://inst.eecs.berk... http://inst/~ee100/e... Lecture23 - Windows ... 3:21 PM

(d)

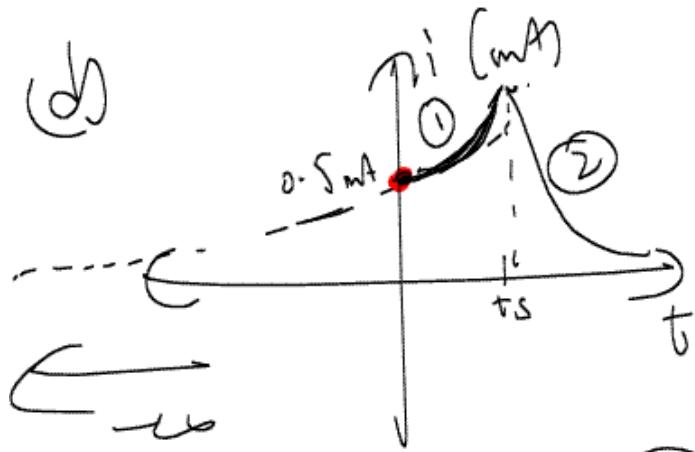

$$i_{(1)}(t) = i_f + (i_i - i_f) e^{-t/\tau_1}$$

$$i_{(2)}(t) = i_f + (i_i - i_f) e^{-t/\tau_2}$$

