


Lecture 24 - Diodes (contd.)

Administrivia → PROJECT LECTURE ON
THURSDAY (04/21)

→ Jaleh's Friday 2-5 section

[If you are NOT enrolled in the
section and want to attend it:

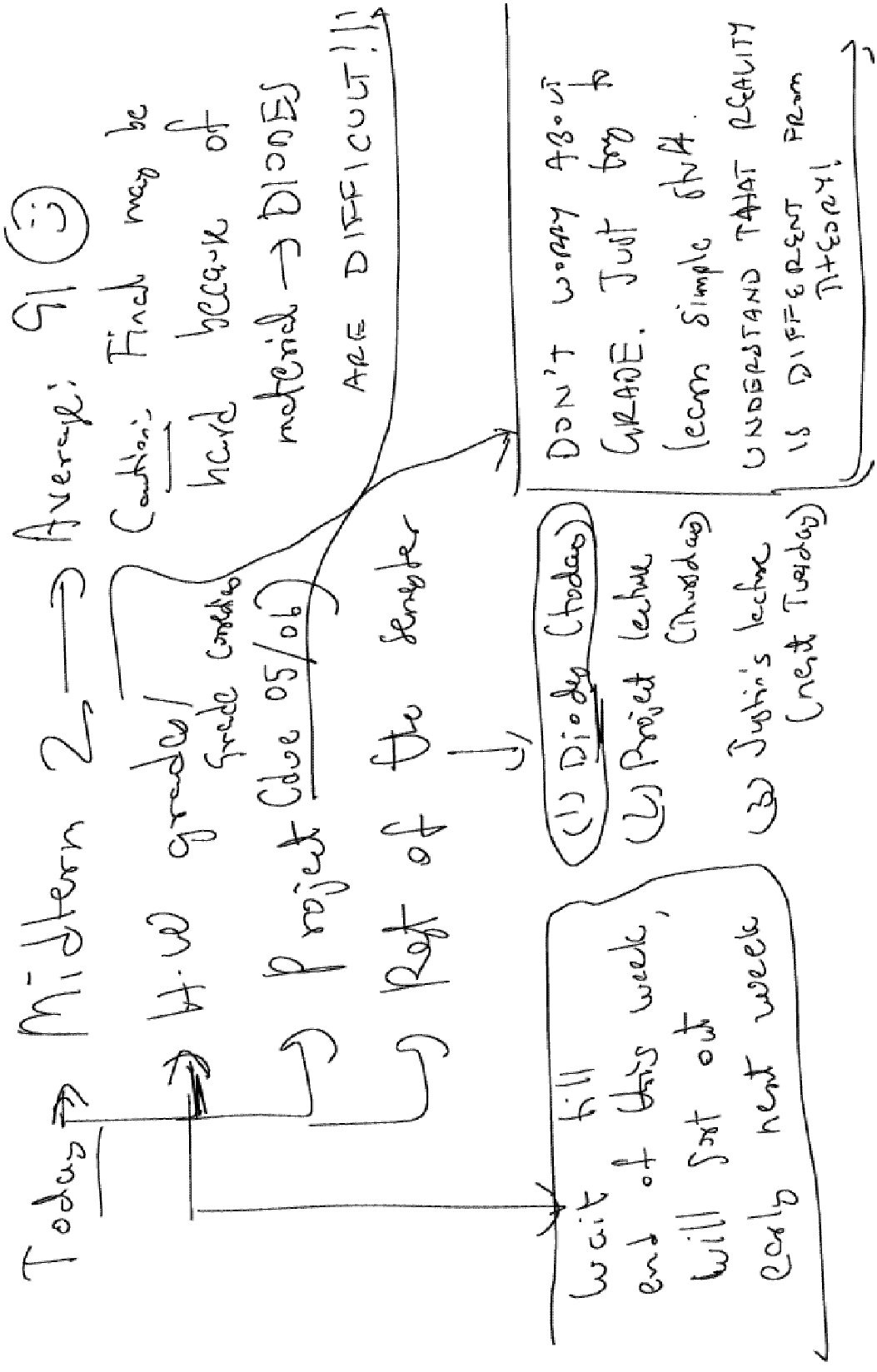email Jaleh (jaleh@berkeley.edu)
by Wednesday, 5:00pm]



Today → Midterm 2 → Average: 91 😊

Cautions: Finish may be hard because of material → DIONES ARE DIFFICULT!!

H.W grade / grade coming

Project due 05/06

Rest of the semester

- (1) Diodo (today)
- (2) Project lecture (Thursday)
- (3) Justin's lecture (next Tuesday)

wait till end of this week, will sort out early next week

DON'T WORRY ABOUT GRADE. Just try to learn simple stuff. UNDERSTAND THAT REALITY IS DIFFERENT FROM THEORY!

Diodes

→ (1) How do LEDs work?


↳ Refer to reader, p. 326

→ (2) Do you have to check if

every diode in the circuit is
in a valid operating range?

↳ YES!!!

Oh, total aside, midterm 2 comment!

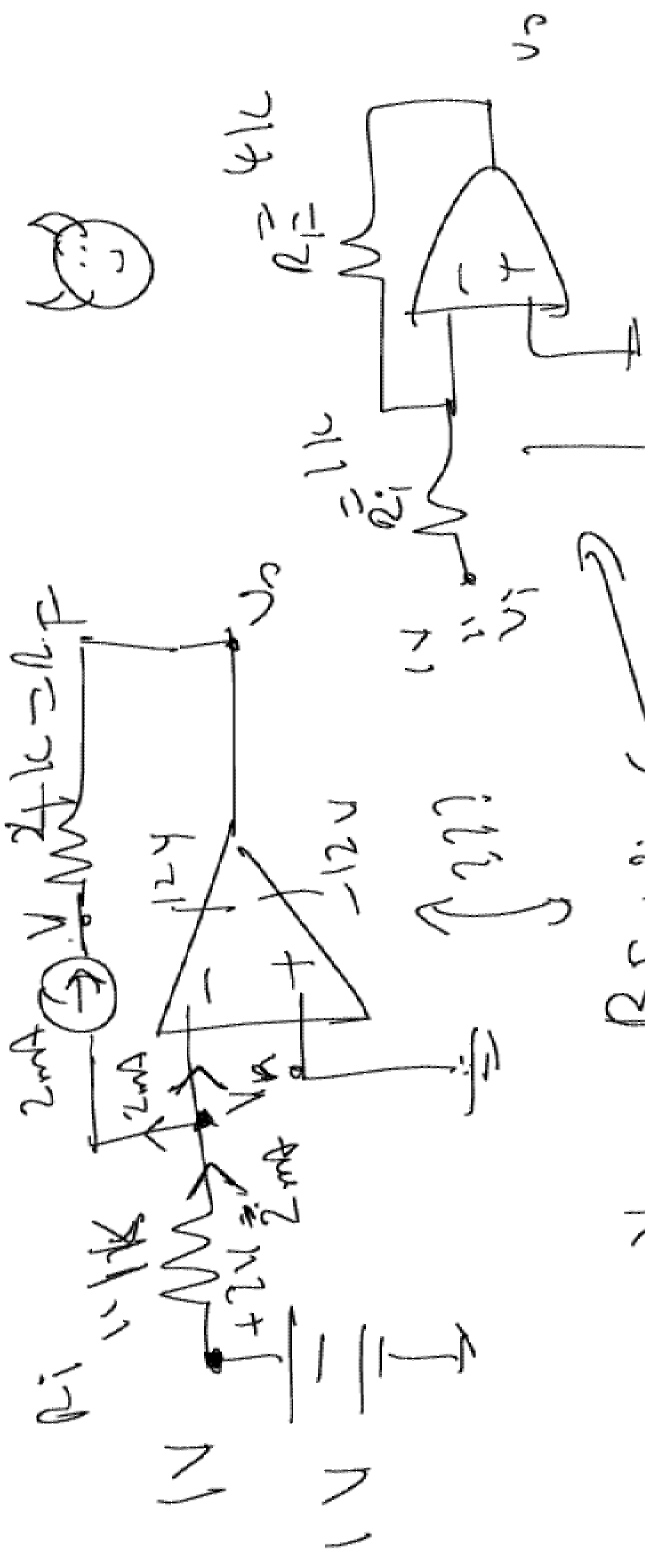

$$V_o = -\frac{R_f}{R_i} V_i$$

$$V_n = -1V \quad \text{Trials: } V_o = A(V_p - V_n)$$


$$V_o = +12V \quad \downarrow = A(0 - (-1))$$

$10^6 \div A \cdot 1 \rightarrow 10^6$ (Op-amp open loop gain)

$$V_o = +12V$$




$$V_o = 12V$$

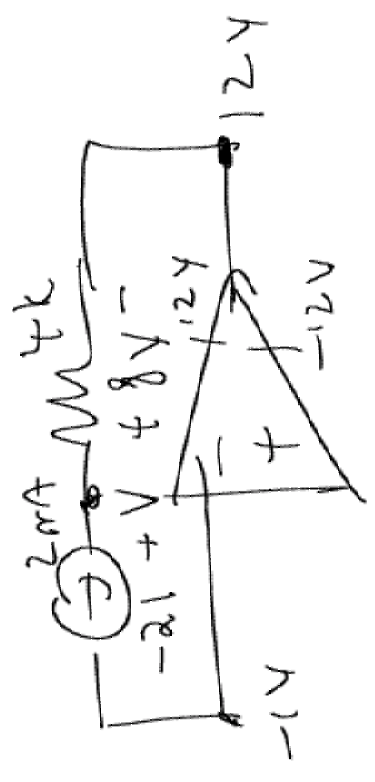

$$V = 20V$$

Finish up Eg 2




lecture 211:

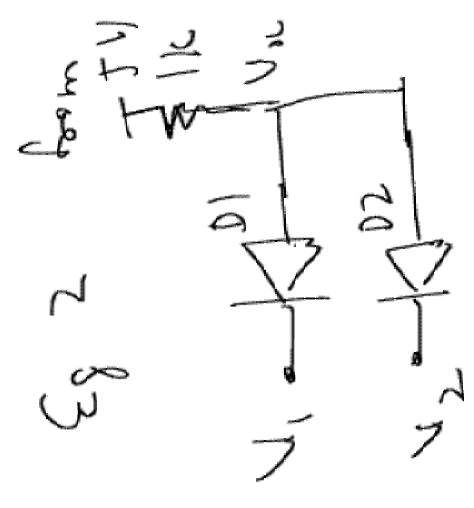

V_1	V_2	V_{DL}
0	0	0
0	5	0
5	0	0
5	5	5

symmetry


Case (w): $V_1 = 0, V_2 = 0$

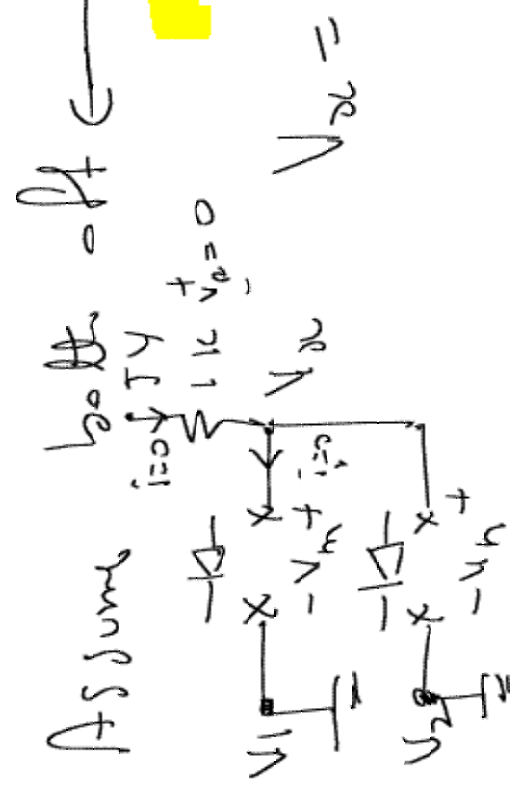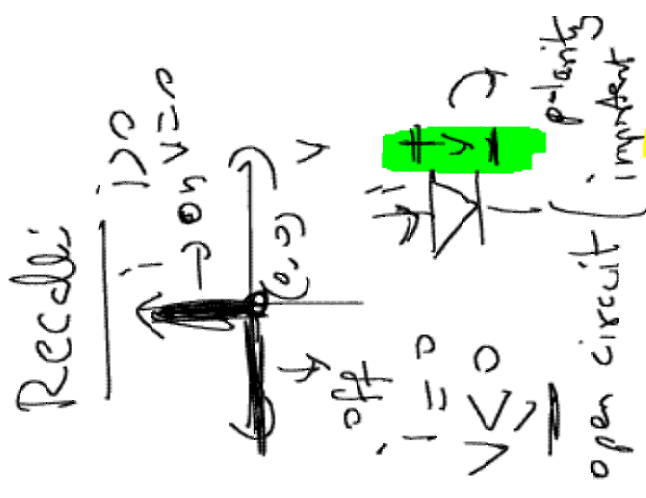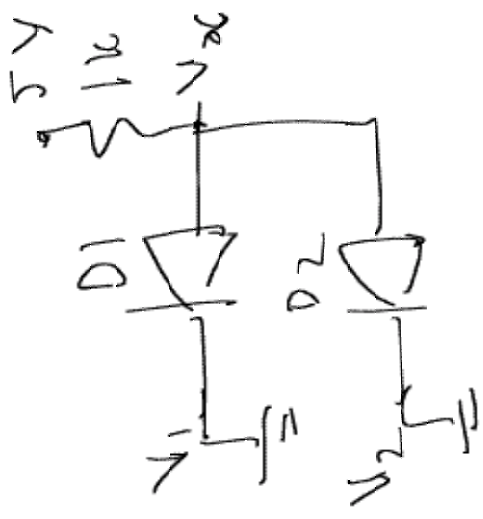

easy to solve circuit


if diode is off!

possible if diodes are off!

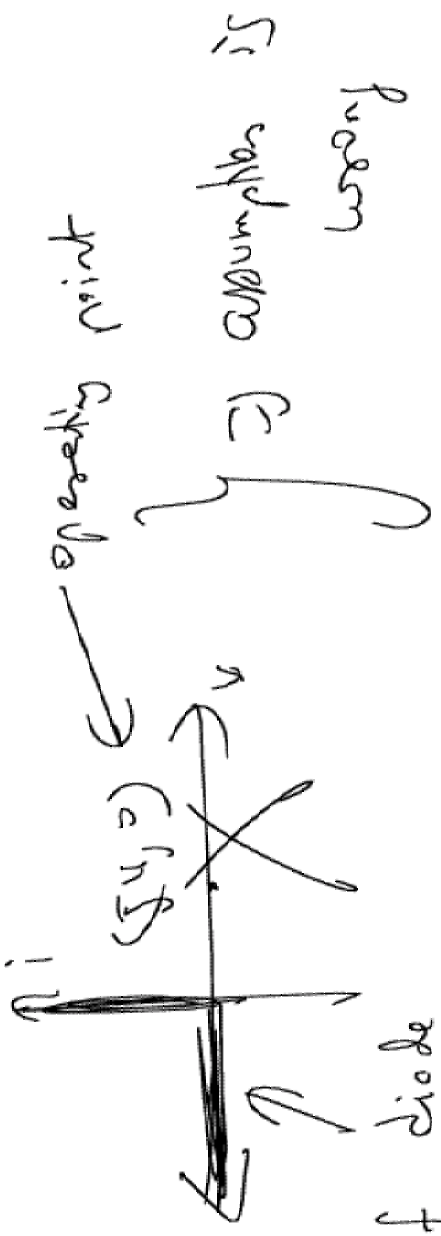


if diode is off, your here!

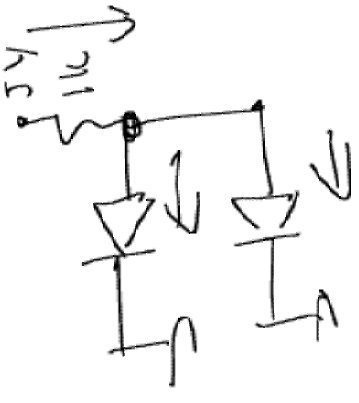Diode (1) are on \rightarrow but which one???



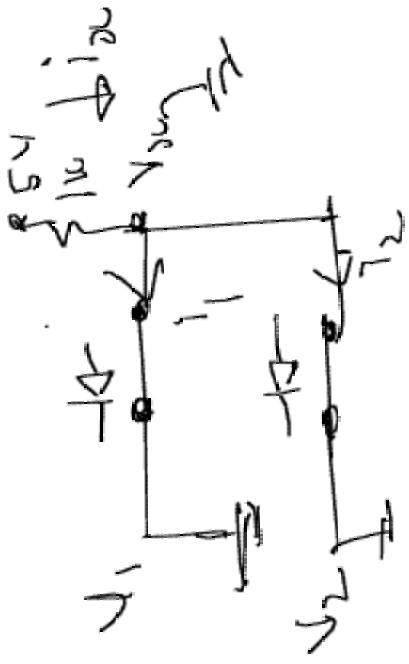Tip (2): look at direction of current flow in the circuit



$$i_2 = \frac{5 - V_{D2}}{1k} = 5 \text{ mA}$$

$$i_1 + i_2 = 5 \text{ mA (KCL)} \quad \text{--- (1)}$$


If diodes are on, $i_1 > 0$
 ~~$i_2 > 0$~~

But, there exists an (i_1, i_2) that satisfies (1)

Such that $i_1 > 0, i_2 > 0$ eg $i_1 = 2 \text{ mA}, i_2 = 3 \text{ mA}$

No. 61

Let's assume D_1 on, D_2 off

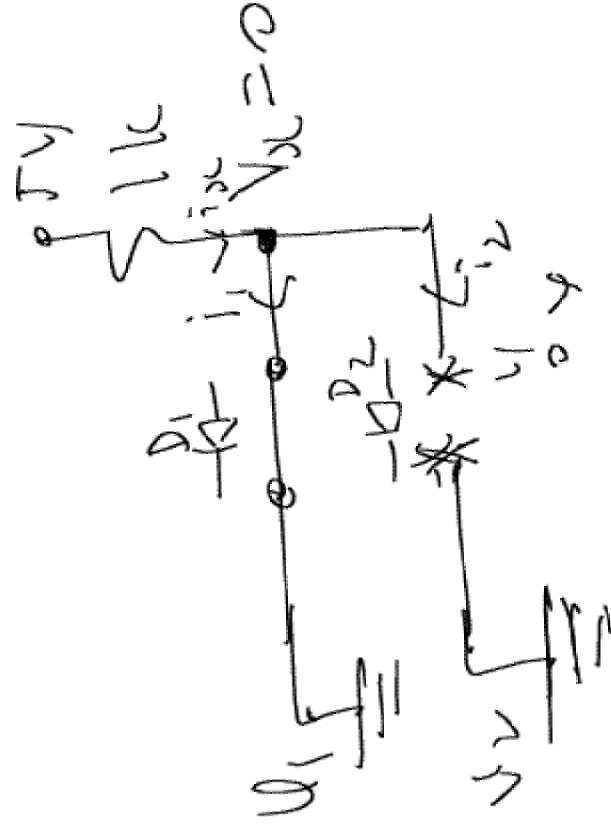


$$V_x = 0V$$

$$i_x = 5mA$$

$$i_2 = 0mA$$

$$i_1 = 5mA$$

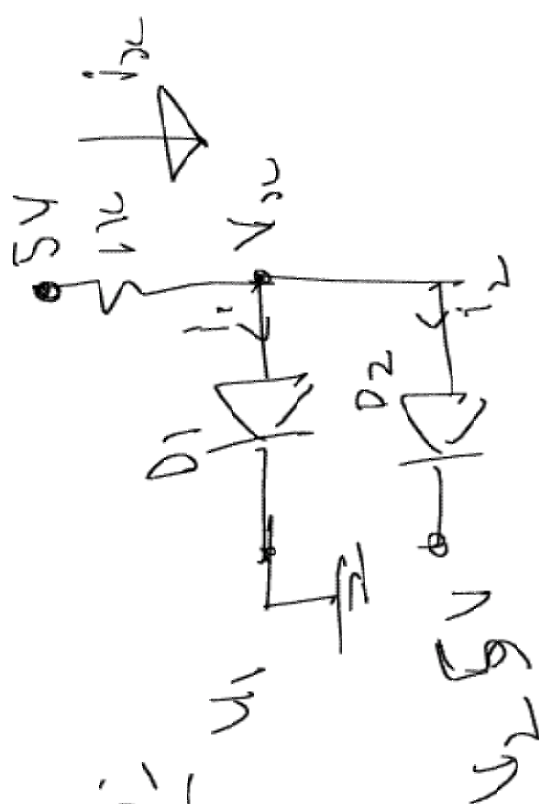

Case (20):


Tip (30): Try to find range of


Unknown node

Volts

e.g. $V_{2c} \in [0, 5]$

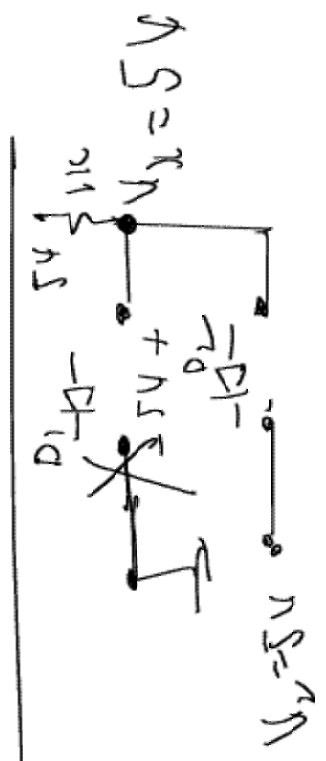Assume diodes off: \rightarrow assumption is wrong






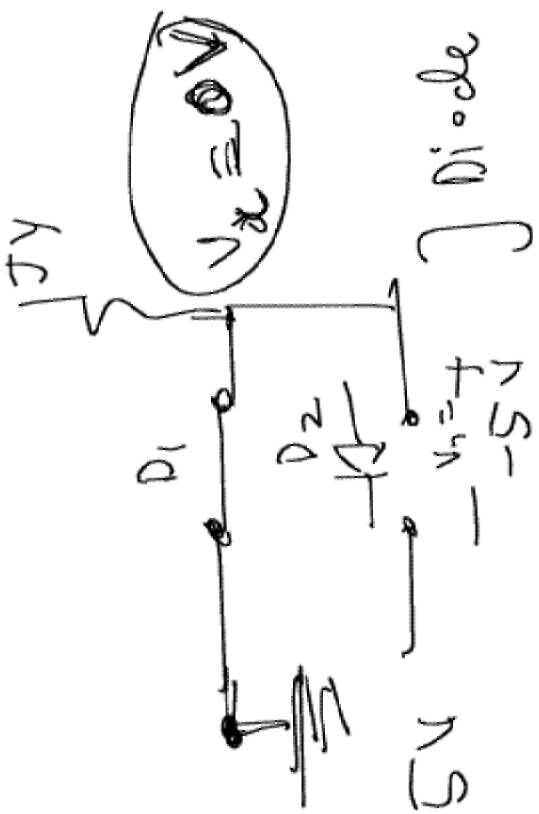

Diode is off ($V_n > 0$)

Case (3): $V_1 = 5, V_2 = 0$ } Same as Case (2)
by symmetry

Case (4): $V_1 = 5, V_2 = 5$

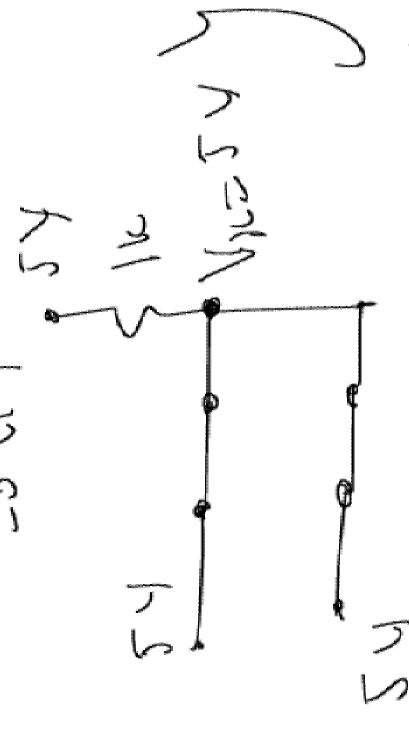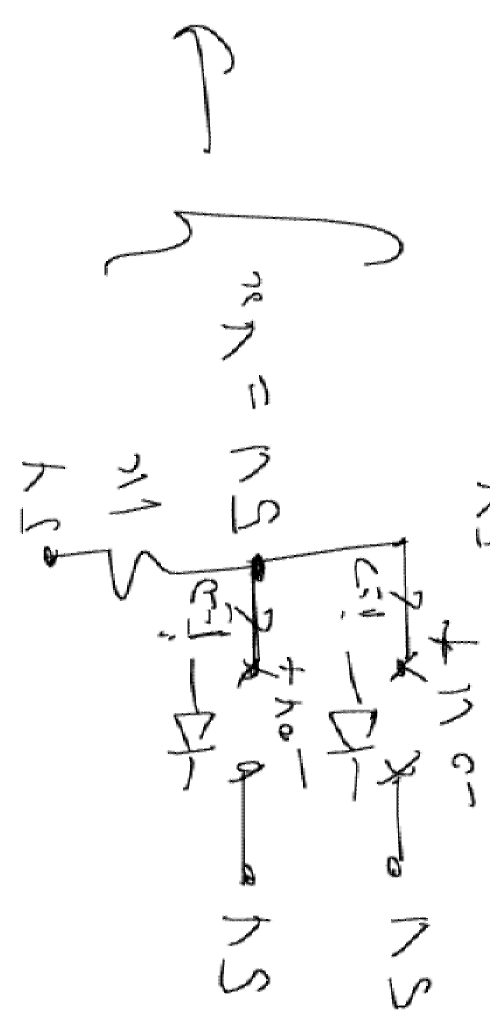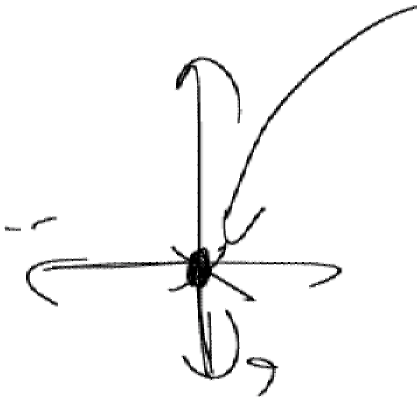

Diode circuit implements AND

A	B	A · B
0	0	0
0	1	0
1	0	0
1	1	1

Mathematically:

$$V_{out} = V_1 \cdot V_2$$

Diode study is in Reader.

CHANGE: IMPLEMENT XOR BOOLEAN FUNCTION

USING 2-INPUTS & RESISTOR

i.e.:

V_1	V_2	$V_1 \oplus V_2$
0	0	0
0	1	1
1	0	1
1	1	0

$$V_1 \oplus V_2 = V_1 \cdot \overline{V_2} + \overline{V_1} \cdot V_2$$