

Lecture 25 - Project Lecture

Today's → Talk about the project.

→ Bart: some details about your project


→ John: overall view of
(audio guy) audio stuff.

Your project:

(Q:) What is it?

A: Tone Controller / Treble-Bass amplifier.
(stereo)

Block diagram:

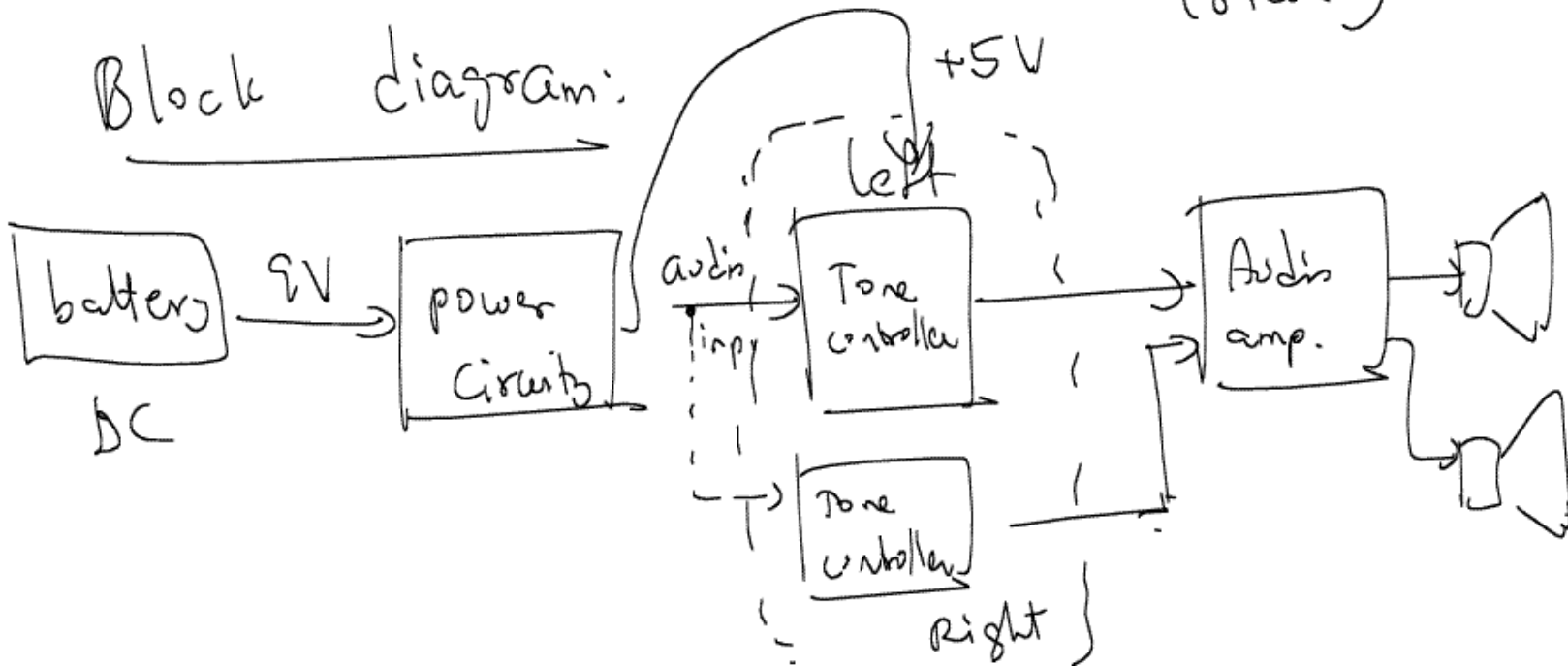

(Q) Why ????


(1) one of the first projects which EE people build

(2) Easy to build, easy to understand qualitatively.

(3) ^{Very} good project to understand the limitations of theory.


(4) Cheap!

Component of your project

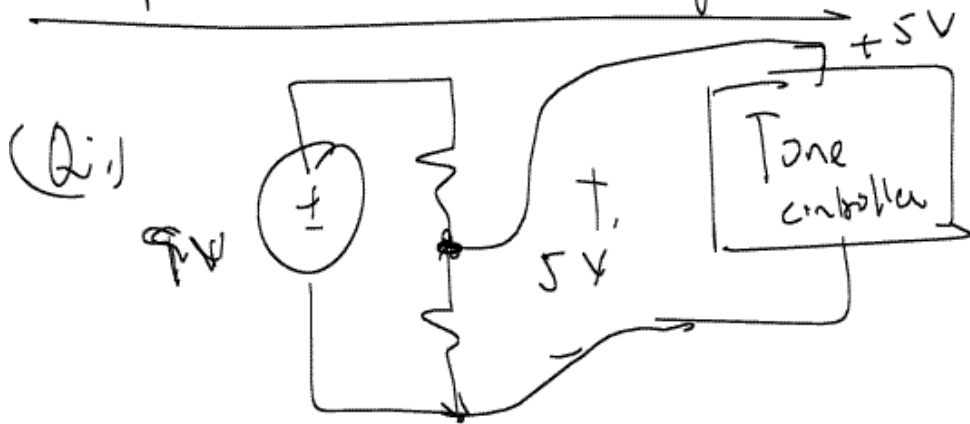

bad, because
a real battery
cannot put out
steady 9V

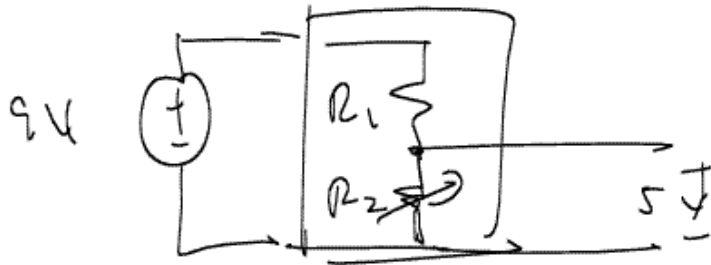Solution: "Linear low drop out regulator."
also "Smart voltage divider"



R_2 will be adjusted
to provide 5V
"as long as it can"


"as long as it can" means Δ between V_{in} (9V)
& V_{out} (5V) should be at least 1.2V

(Q:) How do you choose a regulator?

(A:) Look at datasheets from companies
(eg: Motorola, National Semiconductor ...)



eg: LM2940, LM1086 - - -


In reality, regulators look like:

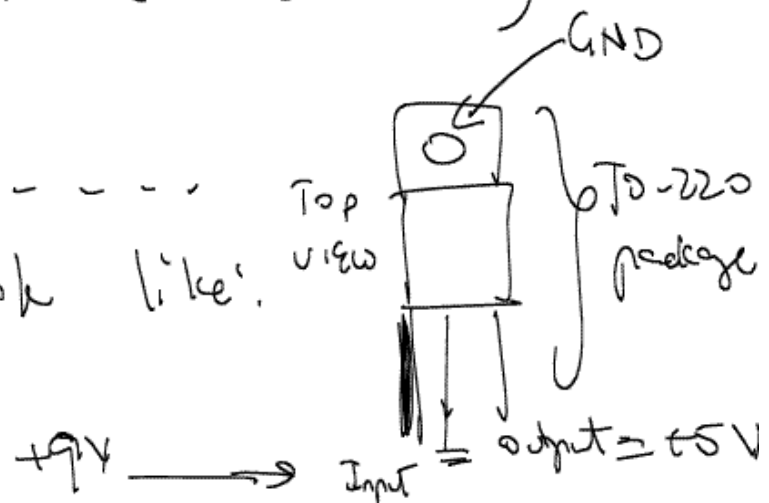


Note: You need filter capacitors at the input & output.

Caps. help filter out noise.

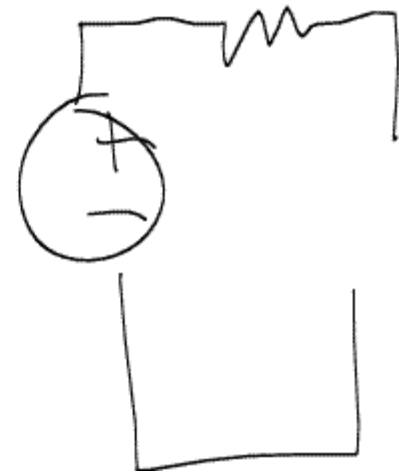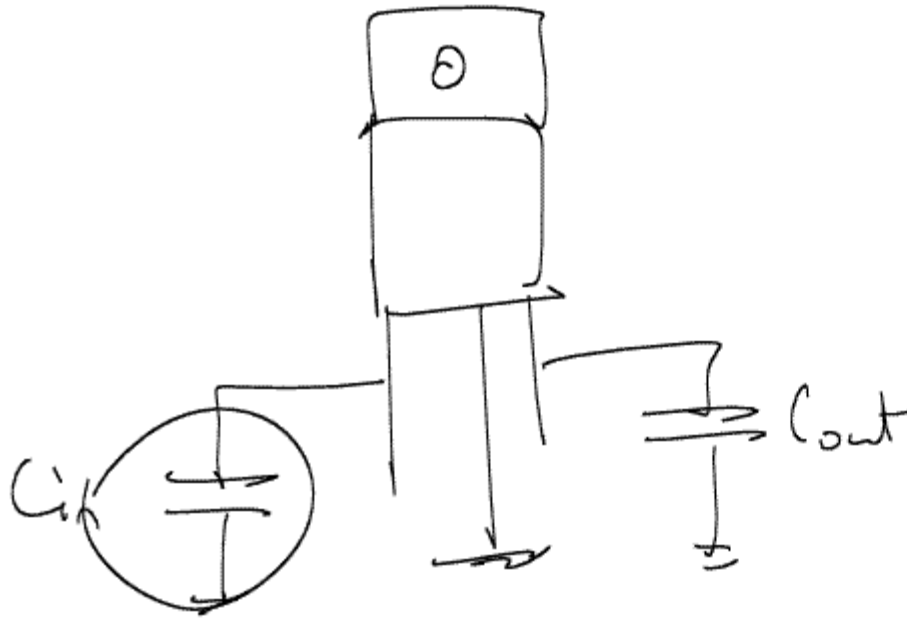


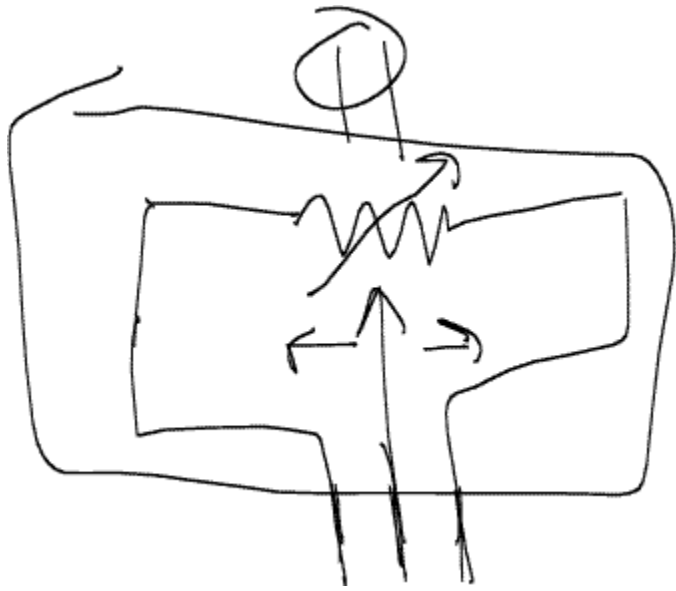




← Potentiometer

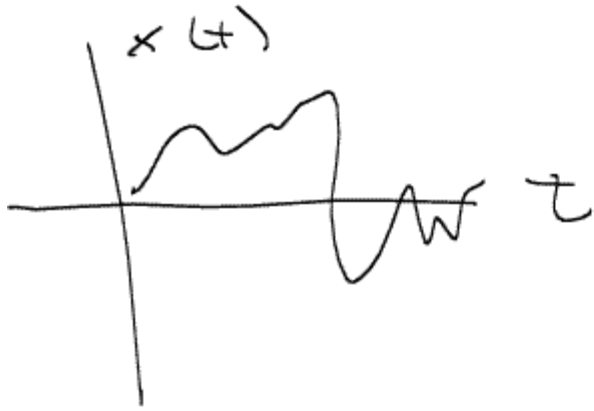

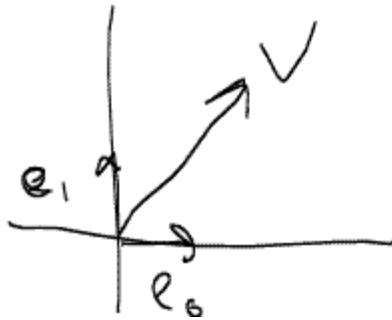
$$x(t) = a_0 + a_1 \cos(t) + b_1 \sin(t) + a_2 \cos(2t)$$



$$v = c_0 e_0 + c_1 e_1$$

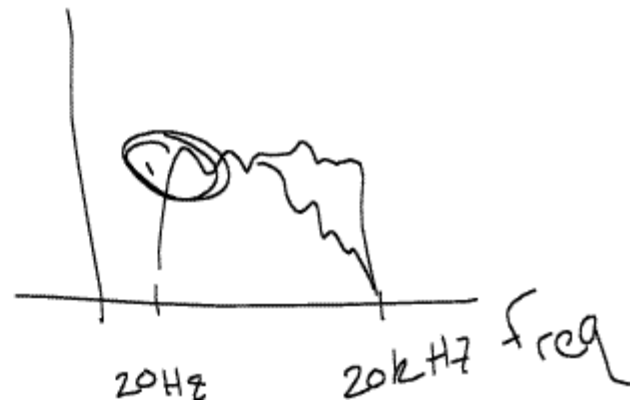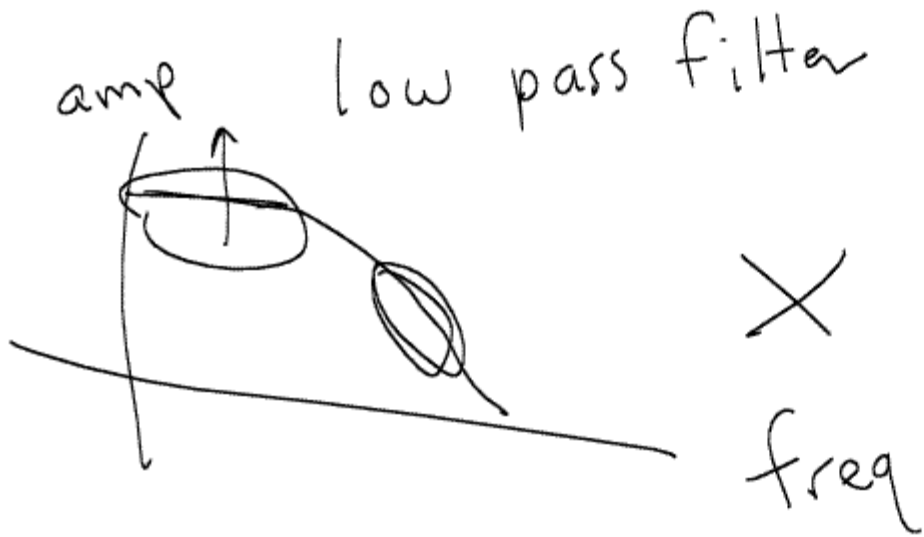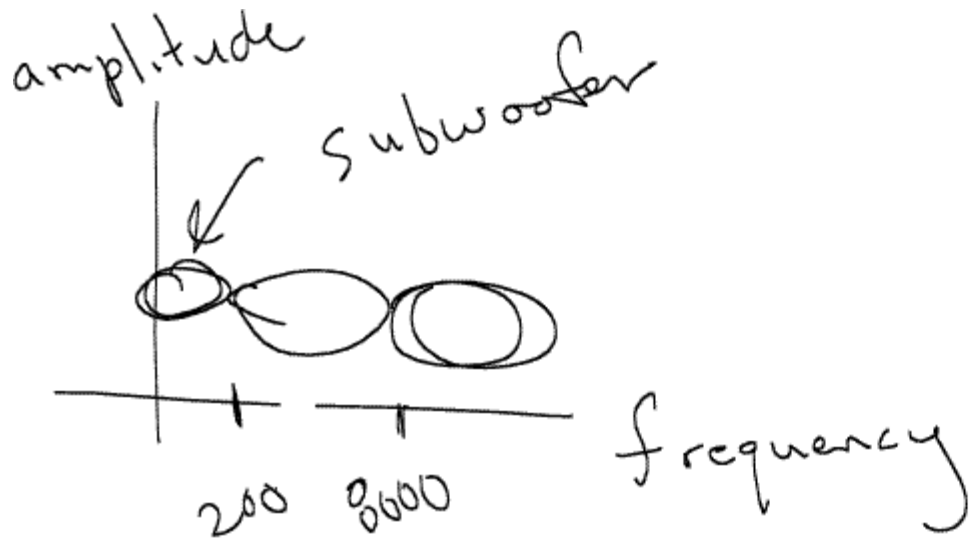

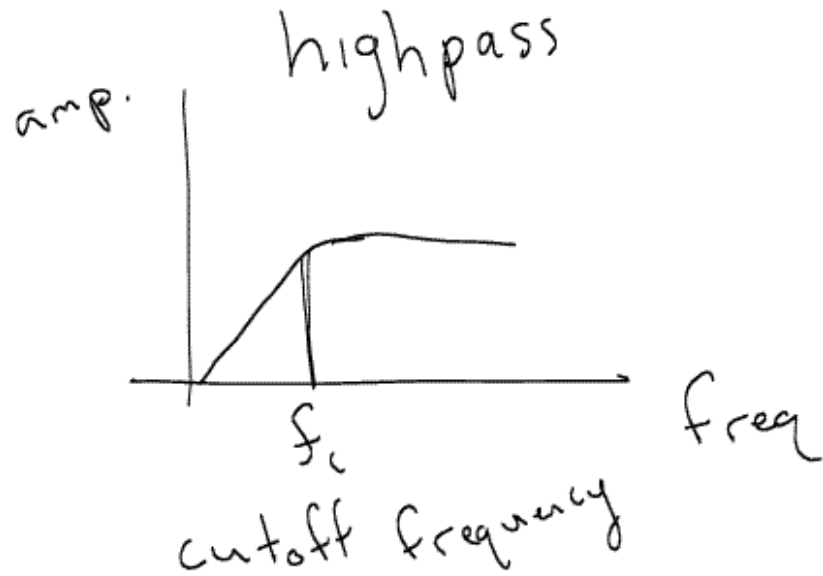

Speakers

Standard $8\ \Omega$


$$(20\text{mA})^2 R$$

$$(.02)^2 8$$

$$(.0004) 8$$

$$.0032\text{W}$$

$$3.2\text{mW}$$

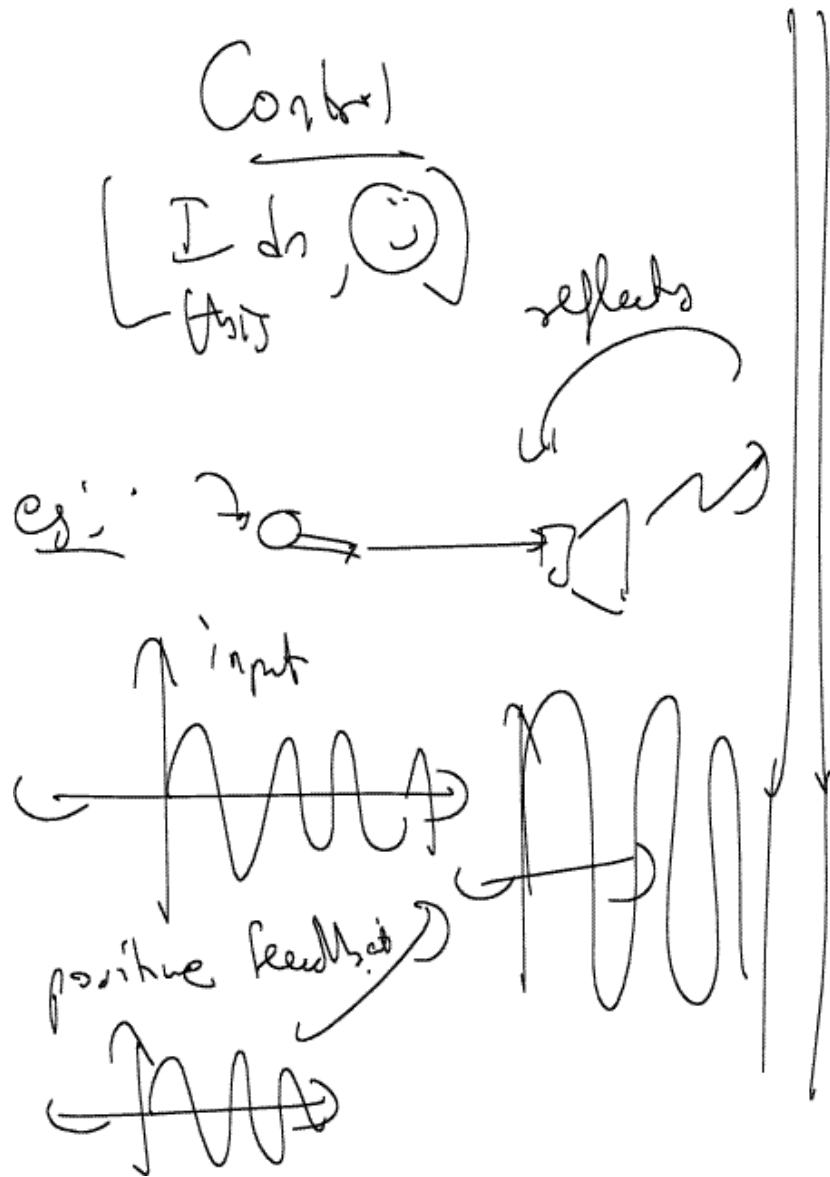

Audis

phase difference is
not important because
as humans, we can't
"hear" phase differences.

John's comment: phase
difference in audio means
time delay

