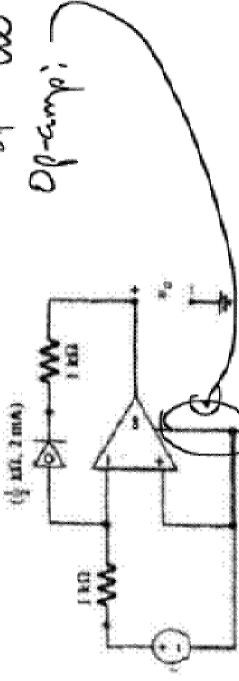


# Lecture 26 - GRAPHICAL METHODS

Administrivia → Last H.W set due on Friday 04/29 @ 1:00 pm

→ Corrections → Problem 2, ignore the -ve rail of the



Assume op-amp never fails

→ Semester is almost over!

→ Only one more lecture 😞

→ Your responsibility

→ Start checking your scores online, I will update them by Thursday morning. Error: POST ON GOOGLE GROUPS, DO NOT EMAIL ME! WE WILL NOT ACCEPT CONNECTIONS AFTER 5:00 pm, 08/06/05!

↳ FINISH PROJECT. Although project report is due on 05/06/05 @ 5:00pm, all I need in the report (max. 2 pages).

- ↳ how to improve the project
- ↳ Difficulties encountered
- ↳ Qualitative explanation of how your circuit works.

Turn it into how box. (one / gear)


Project is graded on neat wiring & how well your circuit works. Do


TURN IN A REPORT, IF NOT I WILL ASSUME YOU DIDN'T DO THE PROJECT.  
!!! TRY TO FINISH PROJECT BY THIS WEEK!!!

Note : Since final exam (Friday the 13<sup>th</sup> ☹️) is  
cumulative, **PR & ARE**!!!! Do NOT  
Slack off! → Tallo next week

---

Load-line method:

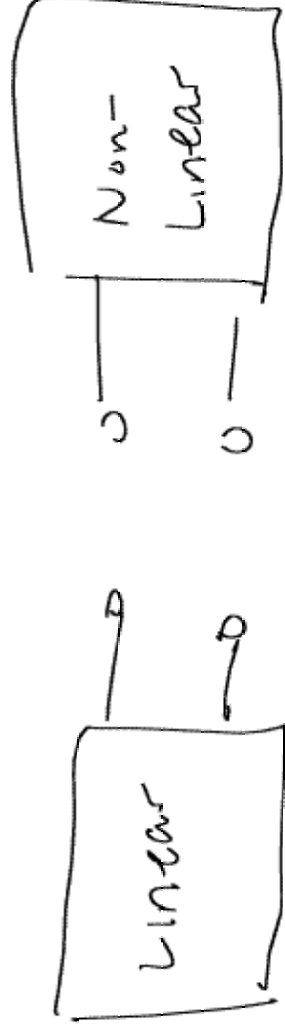


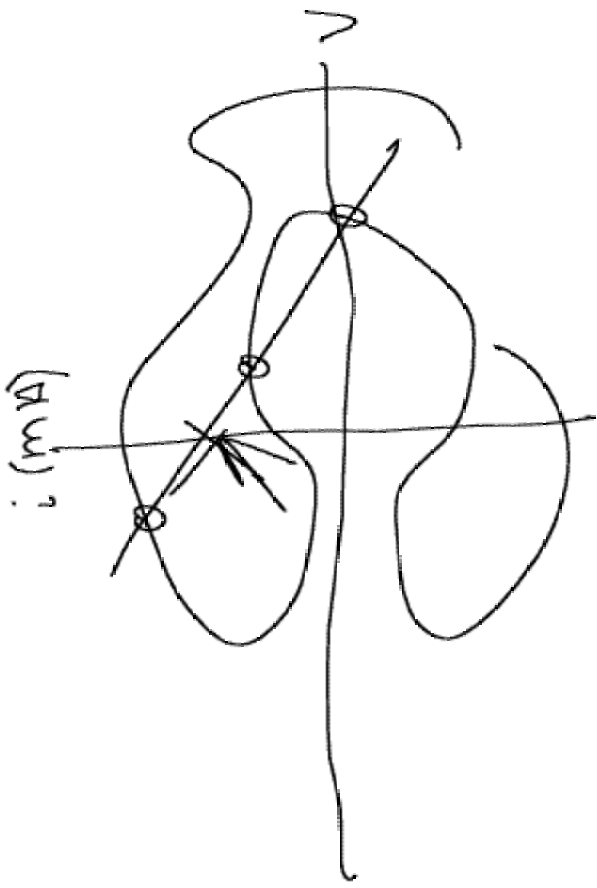



$$E - iR = V$$

$$E - V = iR$$




$$i = \frac{1}{R}(E - V)$$

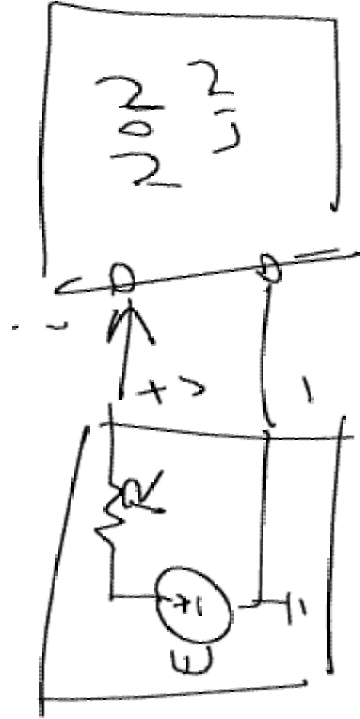

Graphical Method:

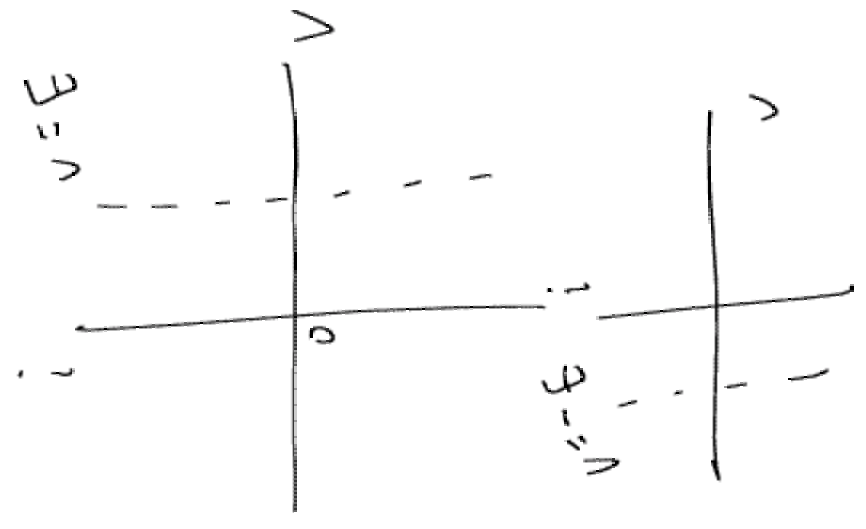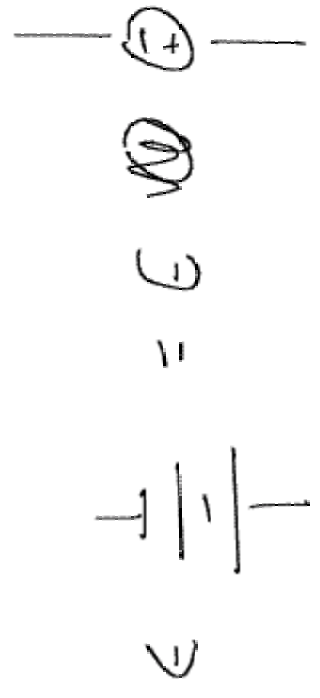


Current Sources:

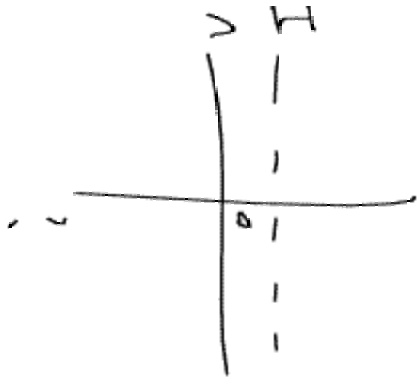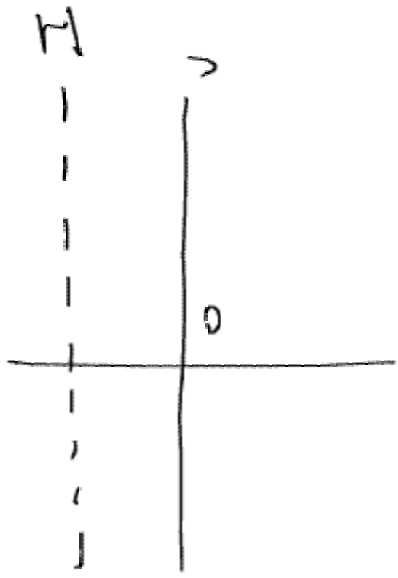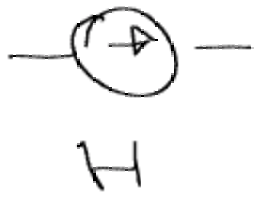


Resistors

$$i = \frac{V}{R}$$



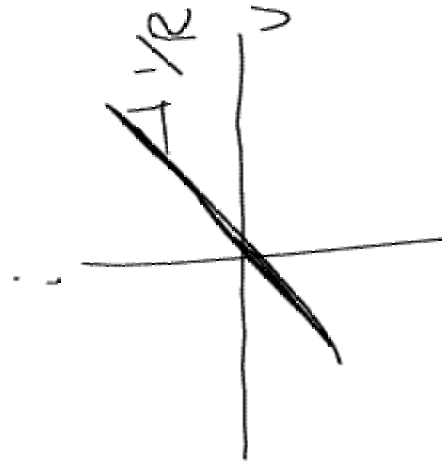


$i = R < 0$

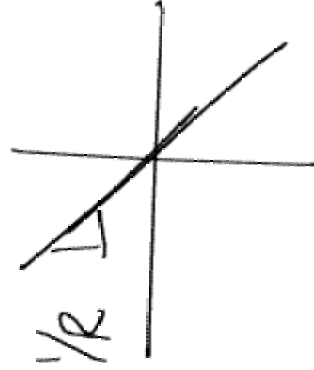






Diodes

Always ideal

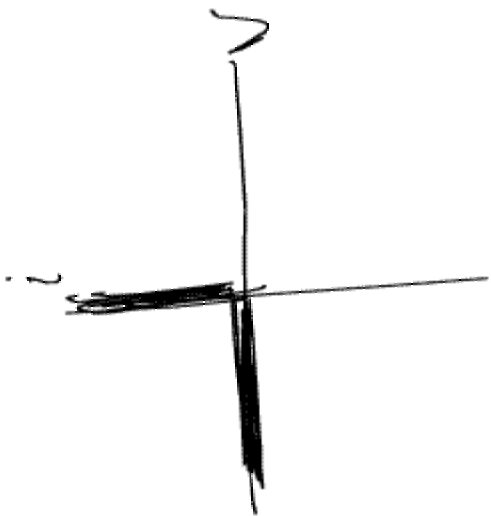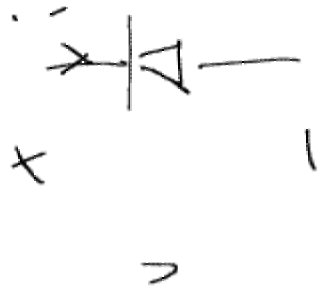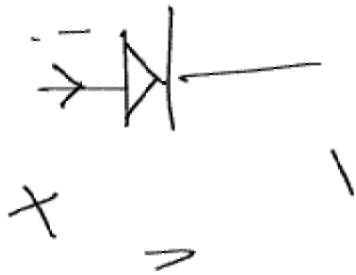

HW

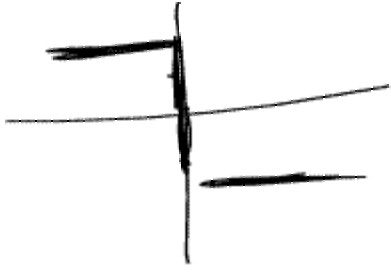


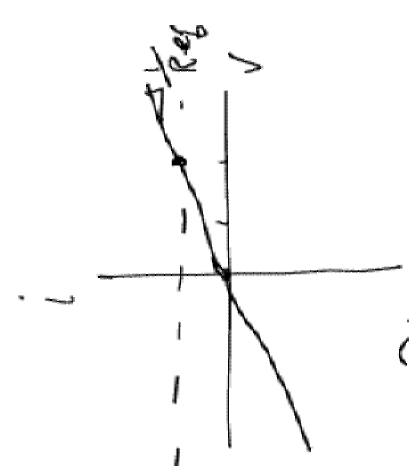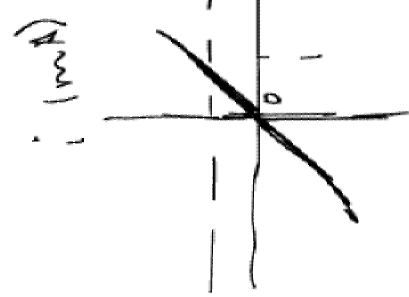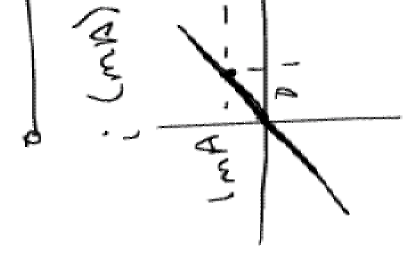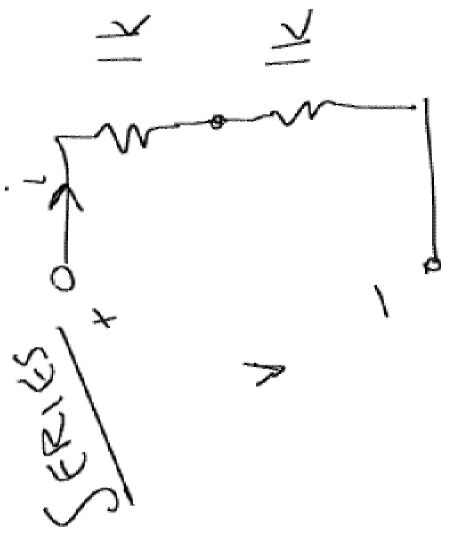




$R_{eq} = 2k$



Parallel

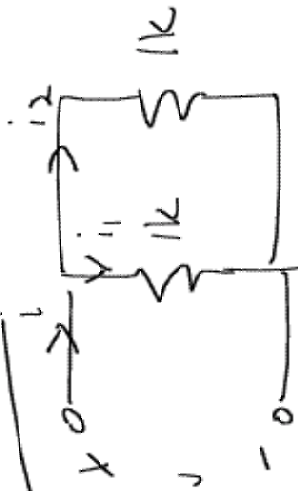

$$i = i_1 + i_2$$

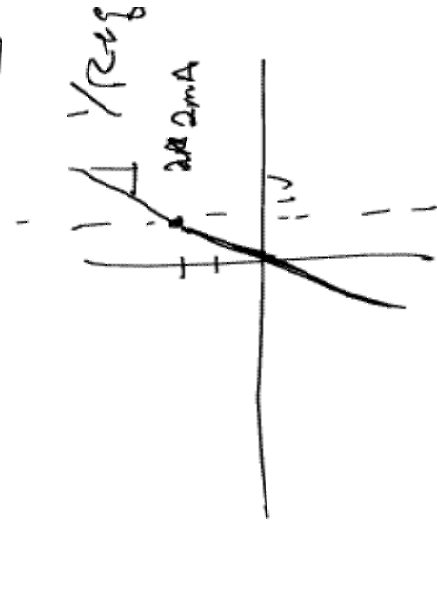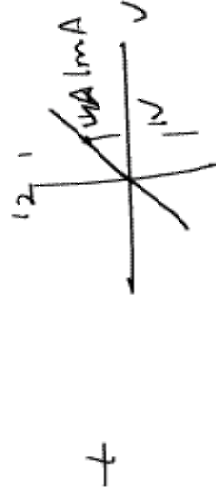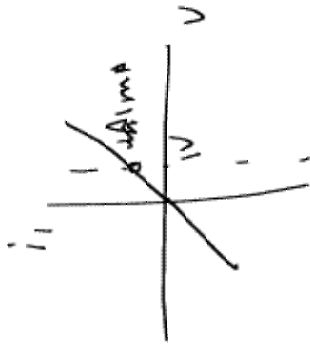



$$R_{eq} = 5\text{ k}\Omega$$

Conclusion:

Series: Add horizontally



Parallel: Add vertically



Ex. 1

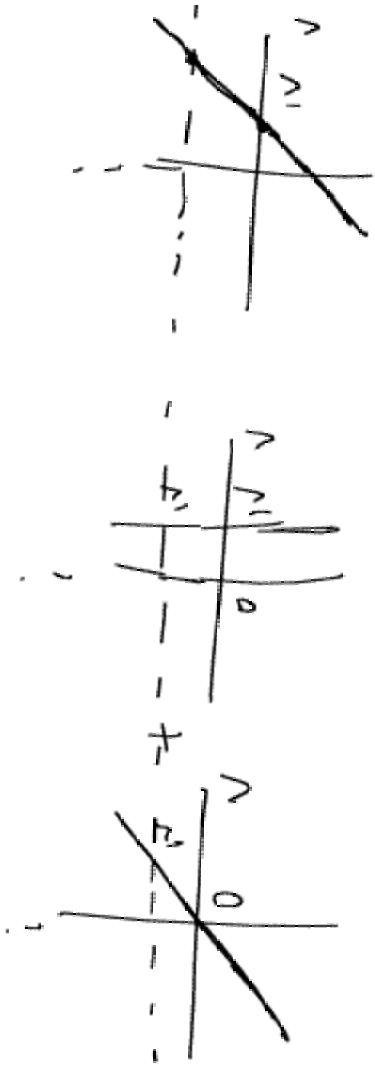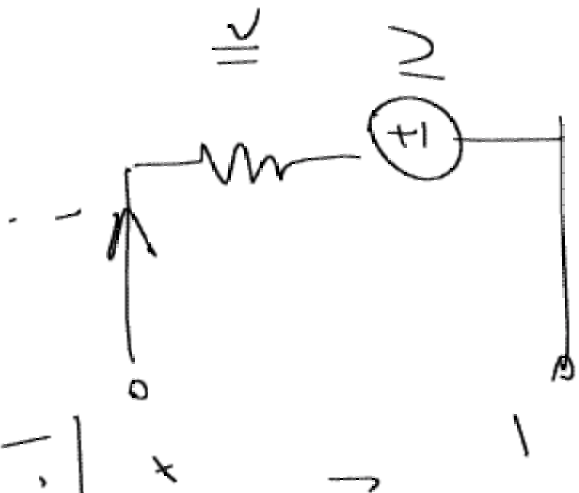


Slope = 1

Ex. 2

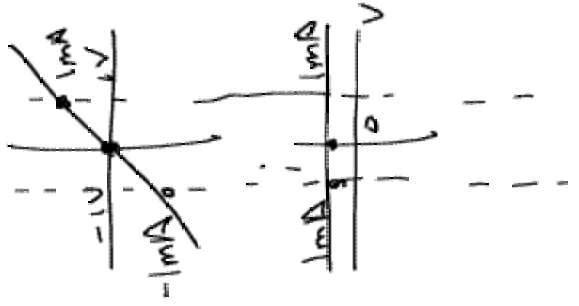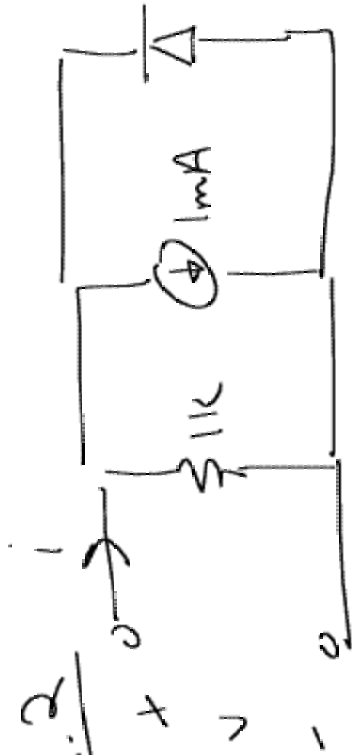


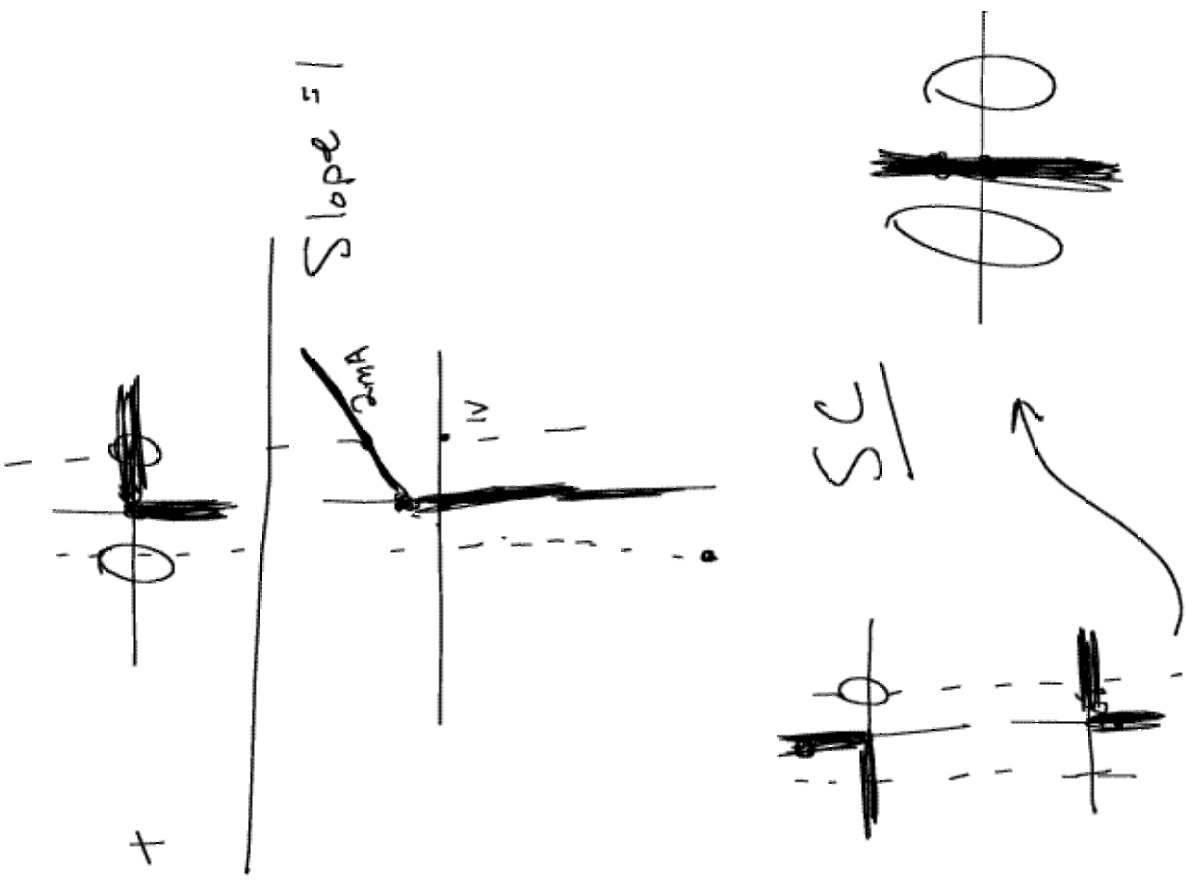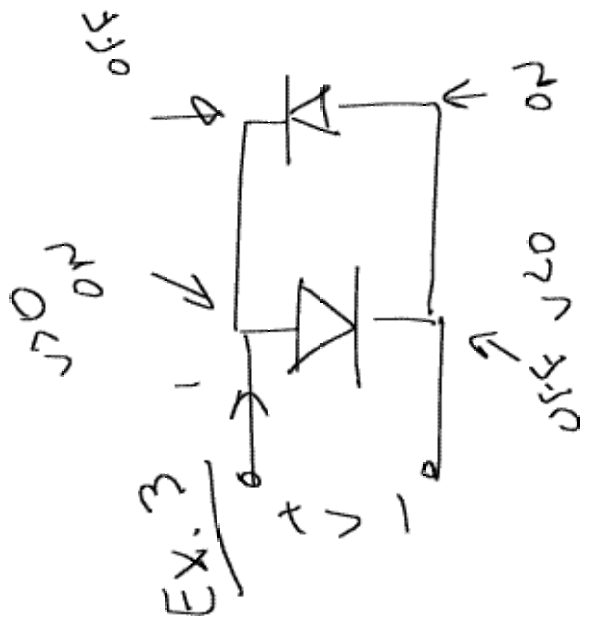



Ex. 4

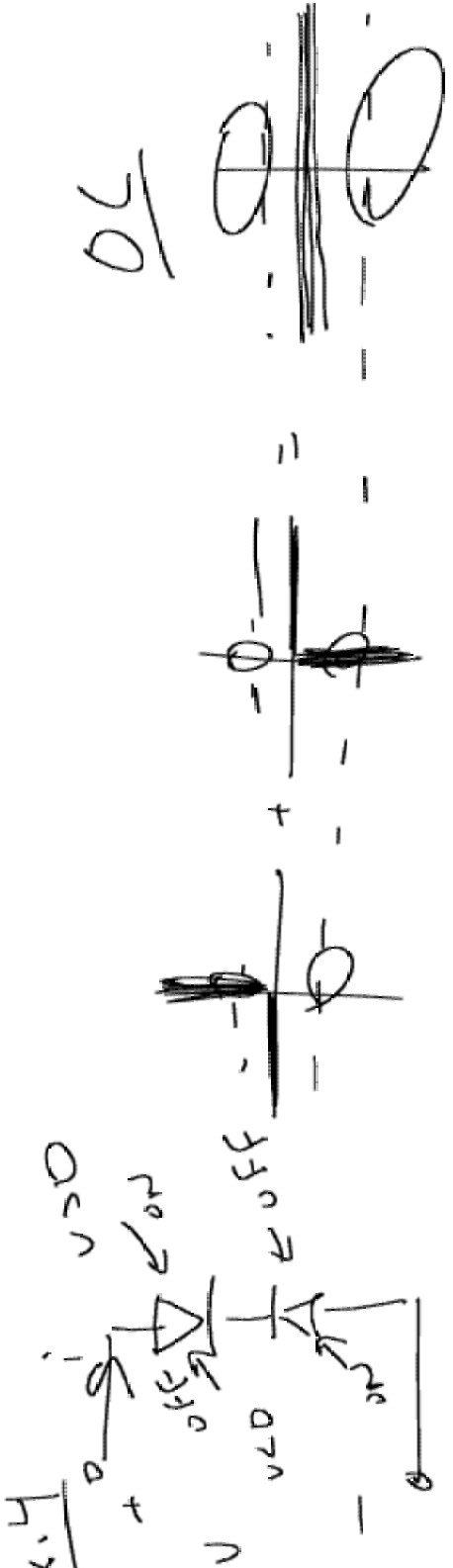


Ex. 5

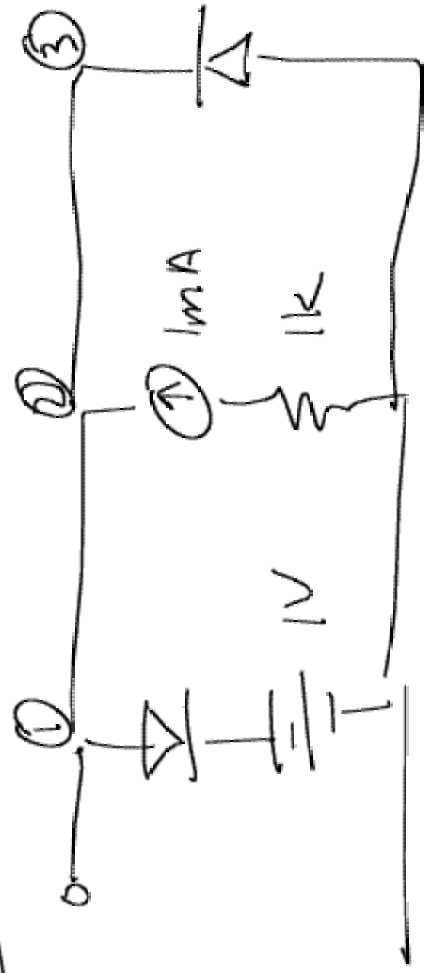



①

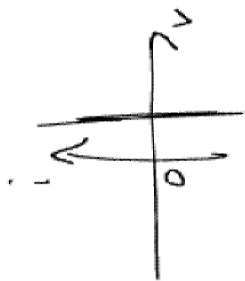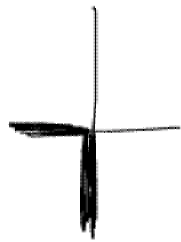


=

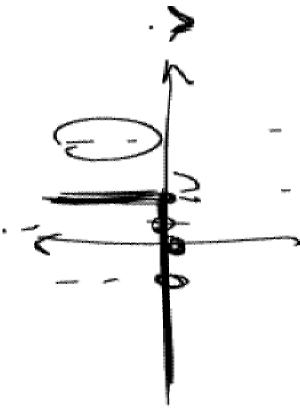


②

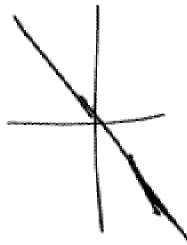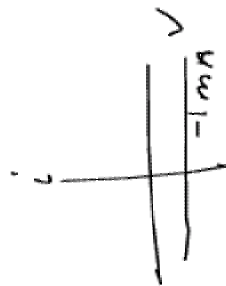


=

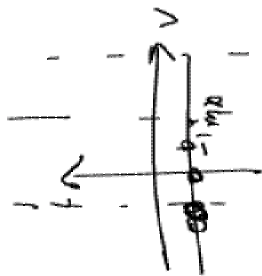

③

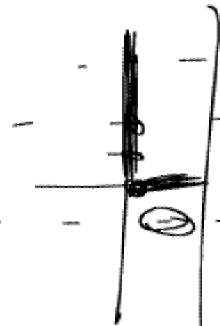

=

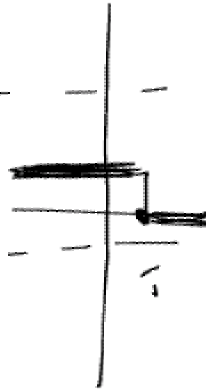

TOTAL

Ex. 4

