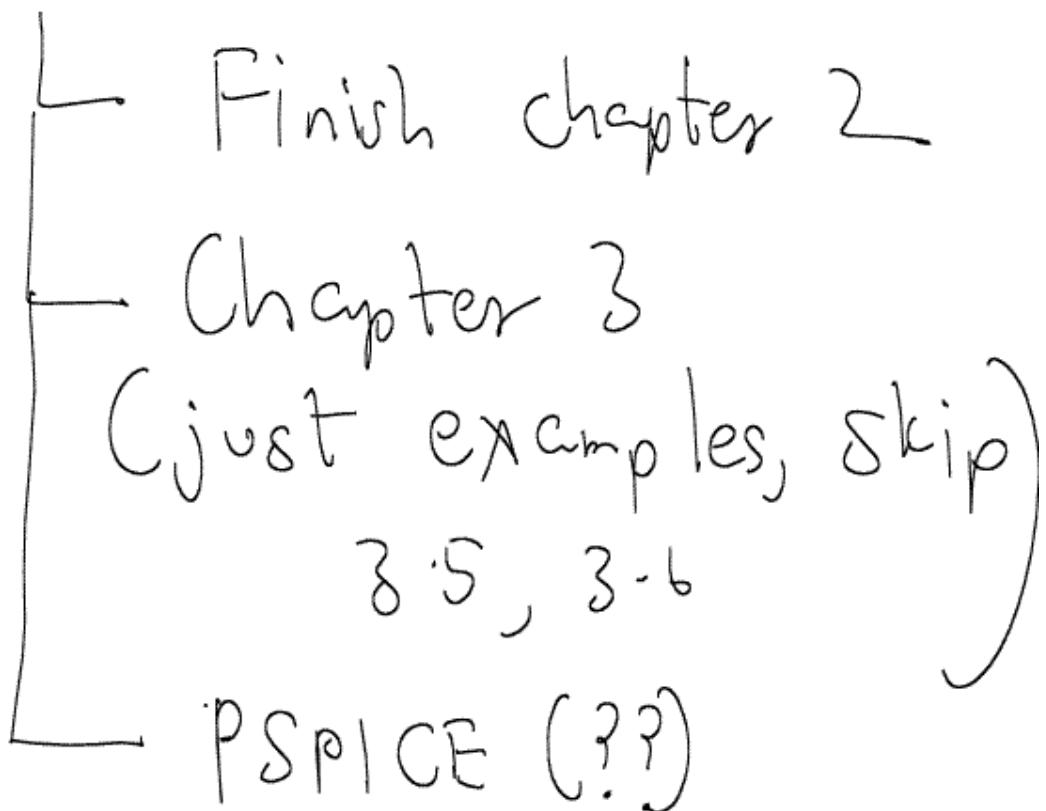


# EE100 - Lecture 3

## (b) Administrivia

- (i) Readers - Copy central  
printed more copies!
- (ii) Office hours in 197 Copy
- (iii) Homework
  - in course notes!
  - "P" symbol does not  
means you should do  
the problem in PSpice
  - Scan in Hw problems
  - No!


② Today:



TODAY  $\rightarrow$  KCL  
(Kirchhoff's Current law)

Mechanical Analogy:



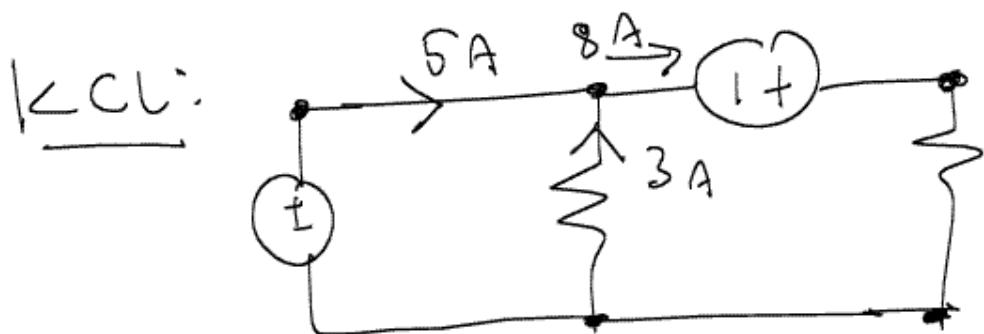

Algebraic sum of currents at a node is zero.

→ i.e. assign a sign to indicate direction of current

Current entering  $\triangleq$  positive


Current leaving  $\triangleq$  negative

$$( +5 ) + ( +3 ) + ( -8 ) = 0$$


---

KVL: "Duck of KCL"

[Kirchhoff's voltage law]

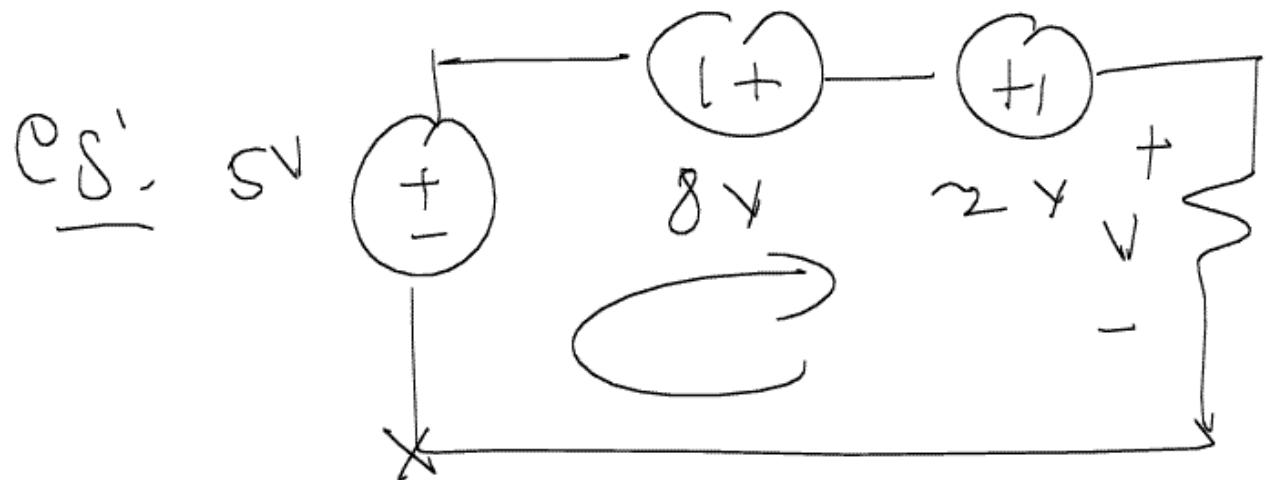

KVL:  $(5V) + (8V) + (-2V)$


$$+ (-V) = 0$$

$\Rightarrow \boxed{V = 11V}$

---

EXAMPLES


(2.7) [over  $\rightarrow$ ]

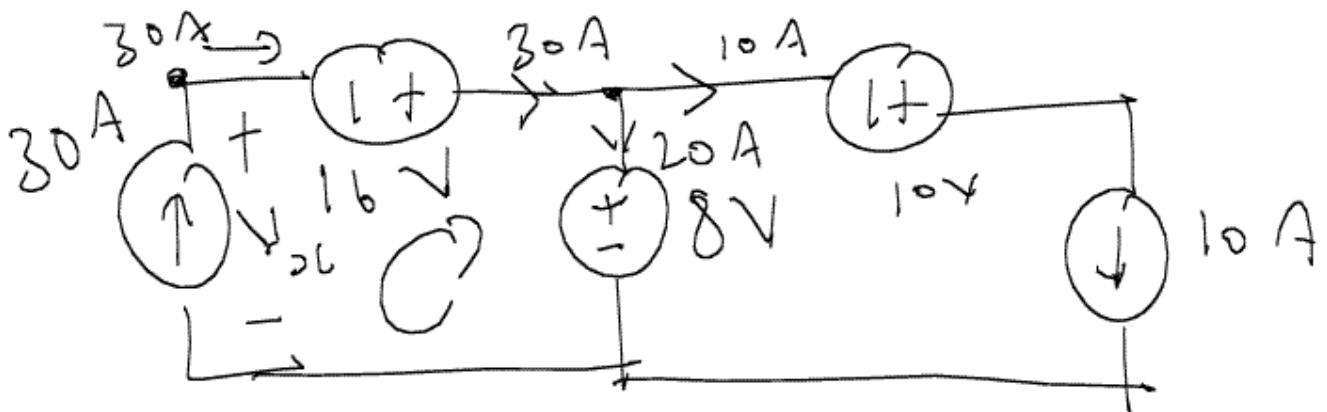

(Q:) Check if the circuit above is valid?

↙ means  
are KCL, KVL, power law  
satisfied

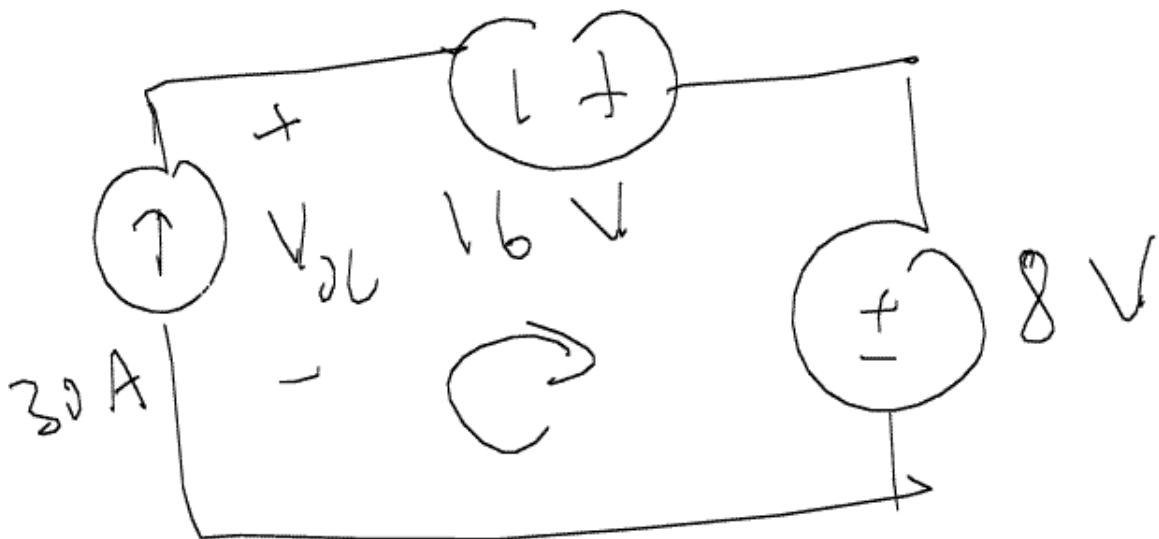↙  
is power delivered  
= power absorbed





Note:

KVL:

$$V_{DC} + 16 - 8 = 0$$

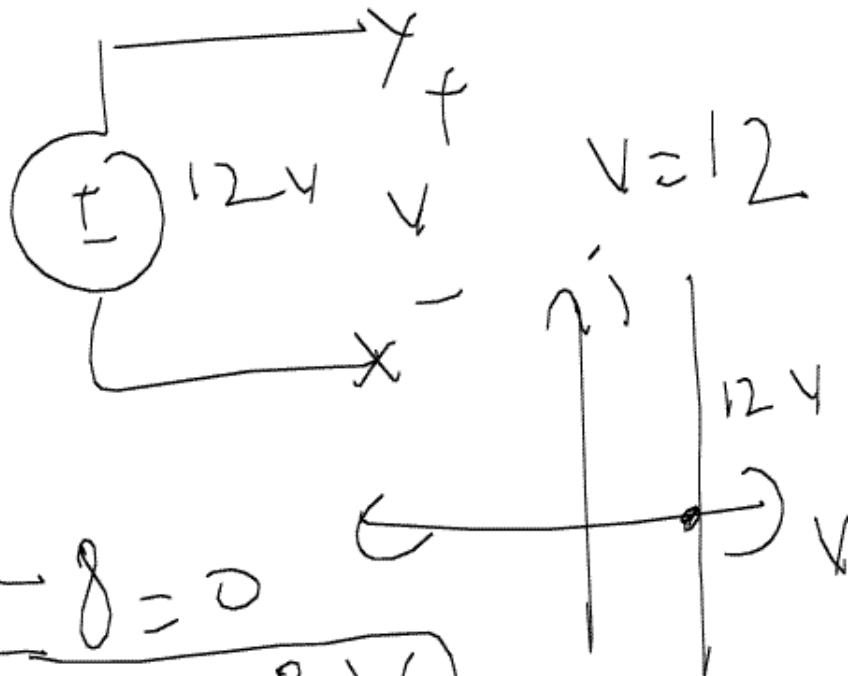
$$\Rightarrow \boxed{V_{DC} = -8 \text{ V}}$$




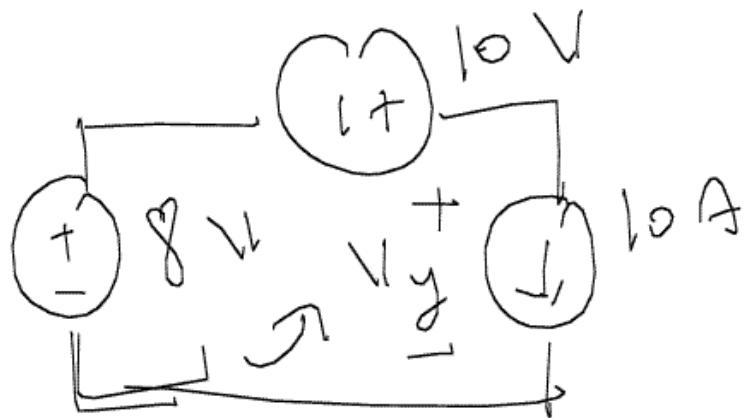


KVL:  $V_y - 10 - 8 = 0$


$$\Rightarrow V_y = 18 \text{ V}$$

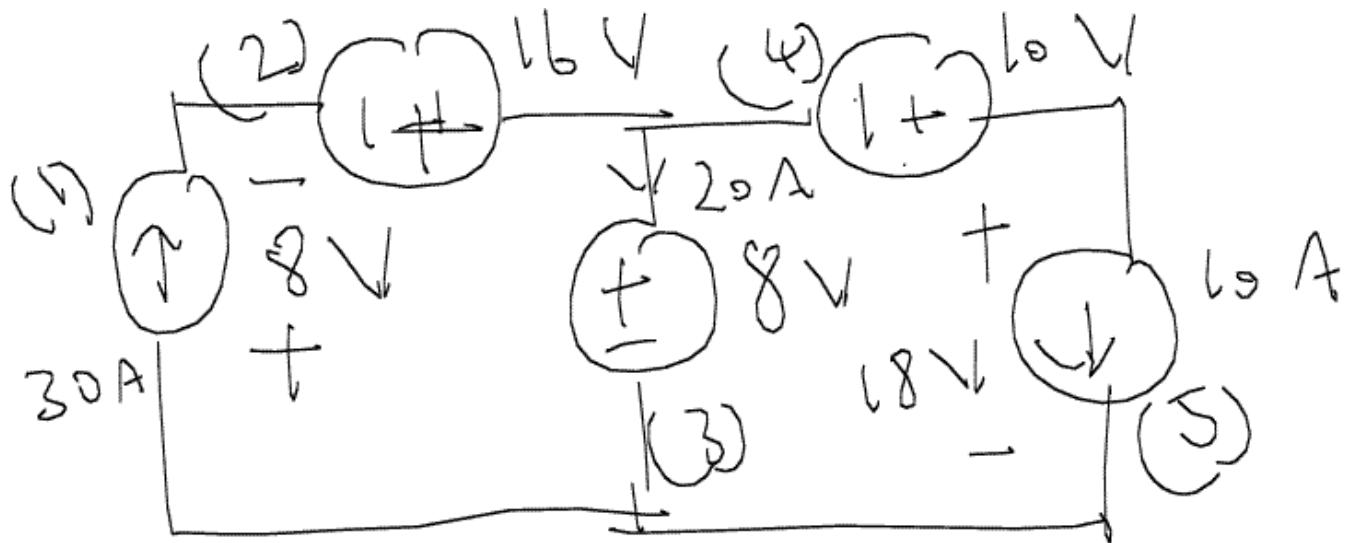

<u>Delivered</u>	<u>Absorbed</u>
$(2): (16V)(30A)$ $= 480W$	$(1): (30A)(8V)$ $= 240W$
$(4): (10A)(10V)$ $= 100W$	$(3): (20A)(8V)$ $= 160W$
<hr/>	<hr/>
$\underline{580W}$	$\underline{\frac{180W}{580W}}$

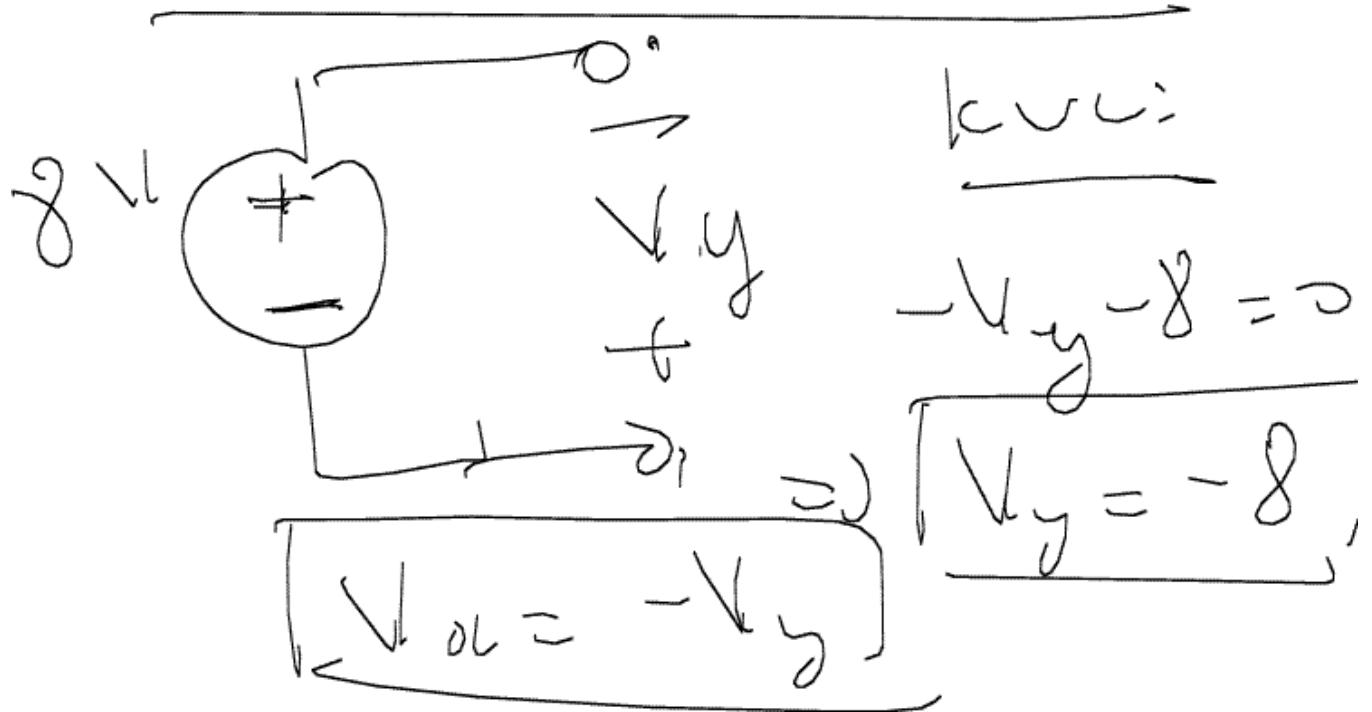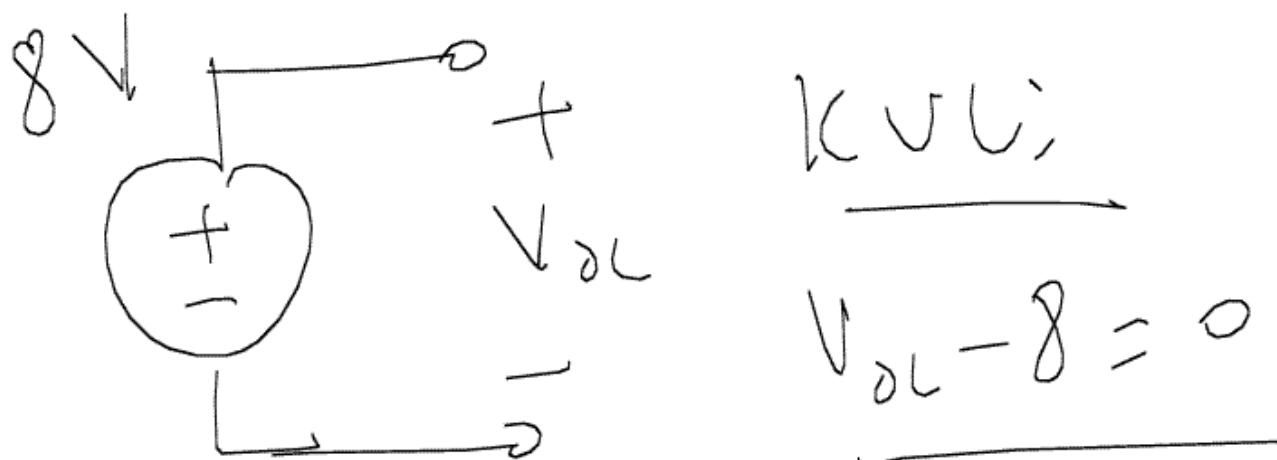


Example p. 2-12

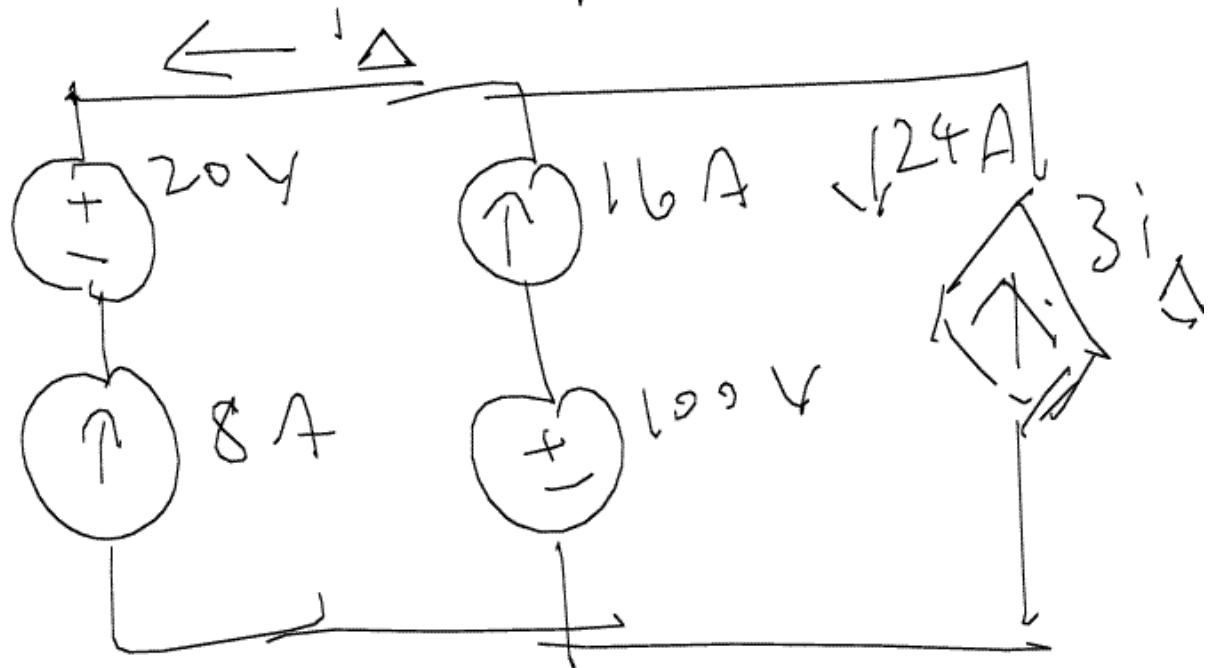

(Q:) Is circuit valid?

$$I_A = -8 \text{ A}$$

$$\therefore 3i_A = -24A$$

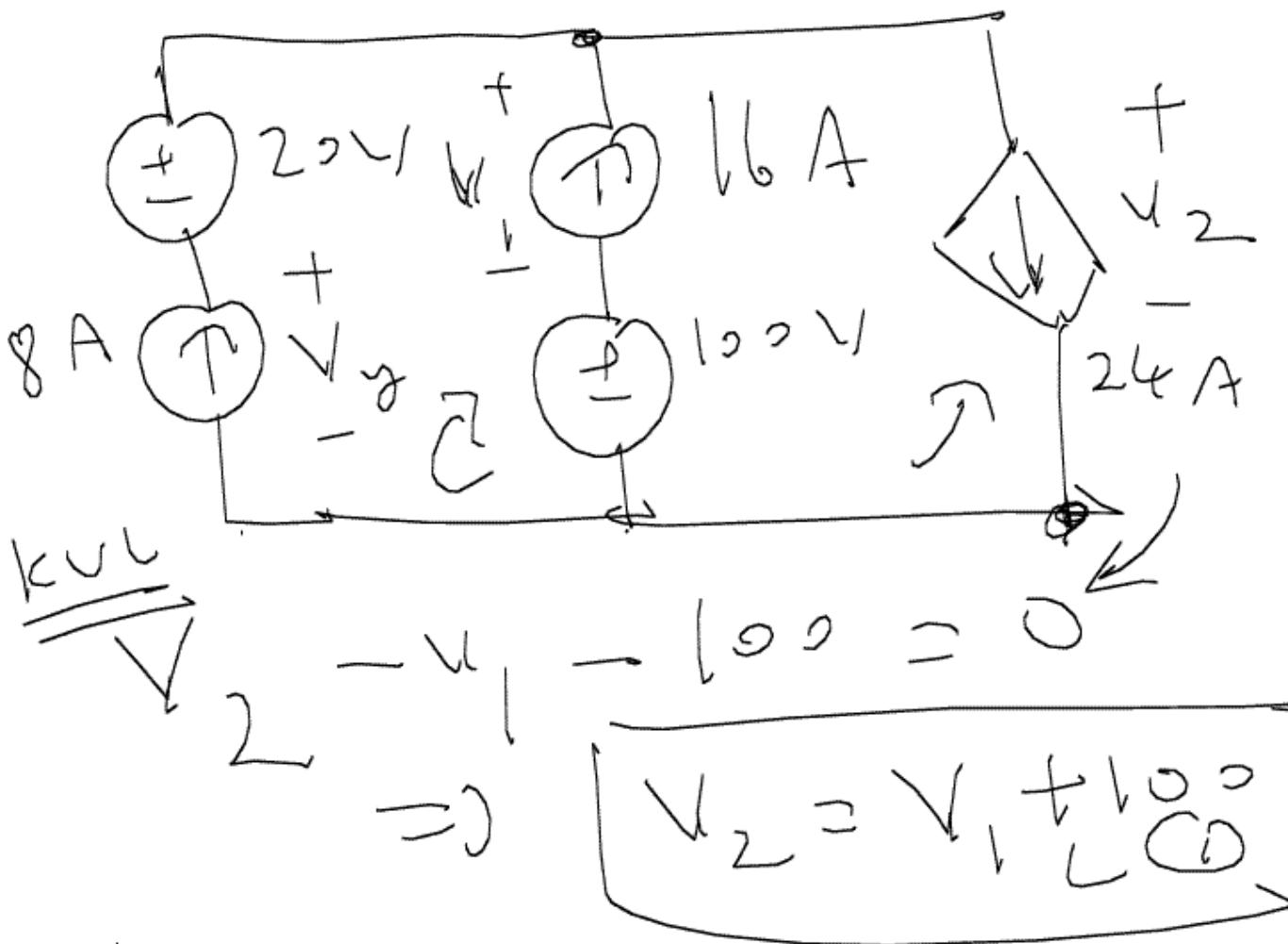

$$\underline{V_y} + 2\Omega - \underline{V_1} - 10\Omega = 0$$

$$\Rightarrow \boxed{\underline{V_y} - \underline{V_1} = 8\Omega} \quad (2)$$

"outside loop"



$$V_y + 2^{\circ} - V_2 = 0$$

$$\Rightarrow \boxed{V_y - V_2 = -2^{\circ} \text{ eq. 3}}$$

But, (2) - (1)

$$\Rightarrow V_y - \cancel{V_1} - V_2$$

$$= 80 - \cancel{V_1} - 10^{\circ}$$

$\Rightarrow$  eq. 3

So, is System valid?

Now, we have a linear circuit. Going back to linear algebra, this system has ~~only~~ many solutions. ~~may~~ have

$$\underline{\text{Ex:}} \quad V_1 = 20 \text{ V}$$
$$V_2 = 120 \text{ V} \text{ [ex. (1)]}$$
$$V_y = 100 \text{ V} \text{ [ex (2)]}$$

---

~~BUT~~ Power absorbed  
=  $P_{\text{delivered}}$

We still have to do this!


Delivered	Absorbed
$(1) (8A)(V_2)$	$(V_2) (24A)$
$(2) (8A) (20V)$ = 160V	
$(3) (6A)(V_1)$	
$(4) (16A) (100A)$	
$\therefore 8V_2 + 160 + 16V_1 + 1600 = 24V_2$	

$$\Rightarrow 8v_2 + 16v_1 + 1760 = 24v_2$$

$$\Rightarrow v_2 + 2v_1 + 220 = 3v_2$$

$$\Rightarrow \boxed{v_2 + 2v_1 - 3v_2 = 220}$$


# Chapter 3 - Simple

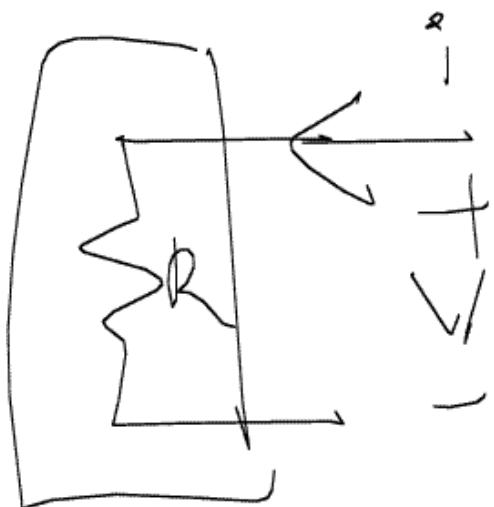

Resistive

circuits


$$V = iR$$

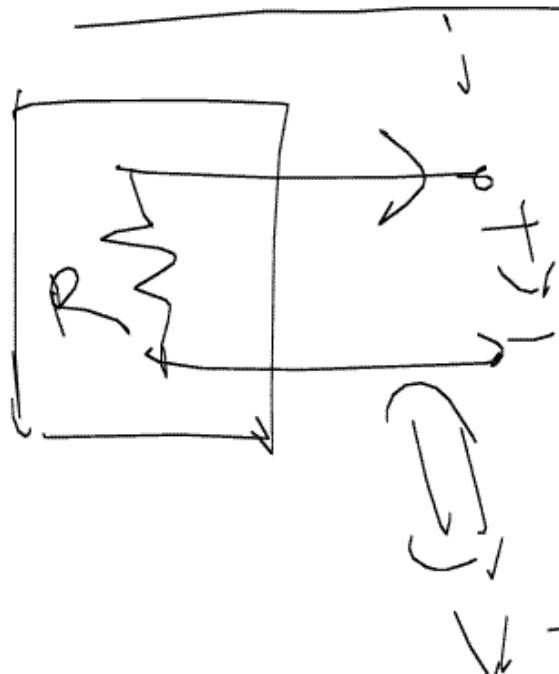

Resistors  
don't  
do this!

$$V = -iR$$

# Resistors in Series

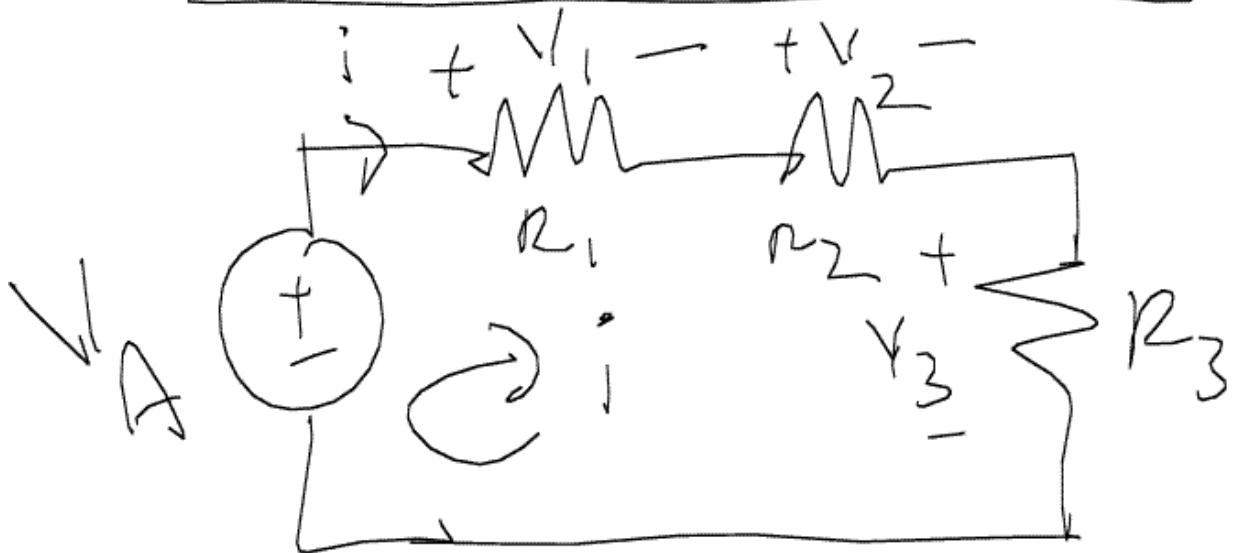

Series: Same Current  
flows through the  
elements

Goal: Find  $V_1$ ,  $V_2$  &  $V_3$

$$\text{Ohm's Law: } V_1 = iR_1$$

$\overbrace{\quad\quad\quad}$

$$V_3 = iR_3 \quad V_2 = iR_2$$

$$\text{KVL: } V_A - V_1 - V_2$$

$\overbrace{\quad\quad\quad}$


$$-V_3 = 0$$

$$\Rightarrow V_A = V_1 + V_2 + V_3$$

$$\Rightarrow V_A = iR_1 + iR_2 + iR_3$$

$$V_A = i(R_1 + R_2 + R_3)$$


$\underbrace{\quad\quad\quad}_{R}$

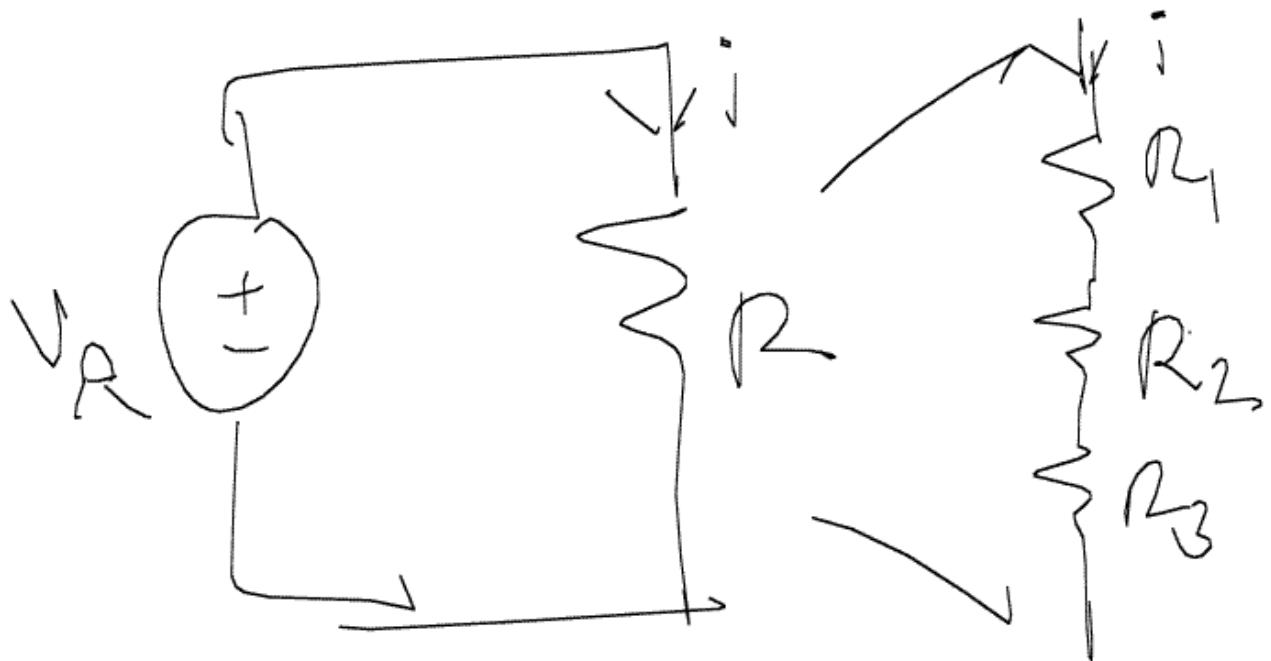

"Series Combinations  
of resistors")

Sign Convention:

Note:

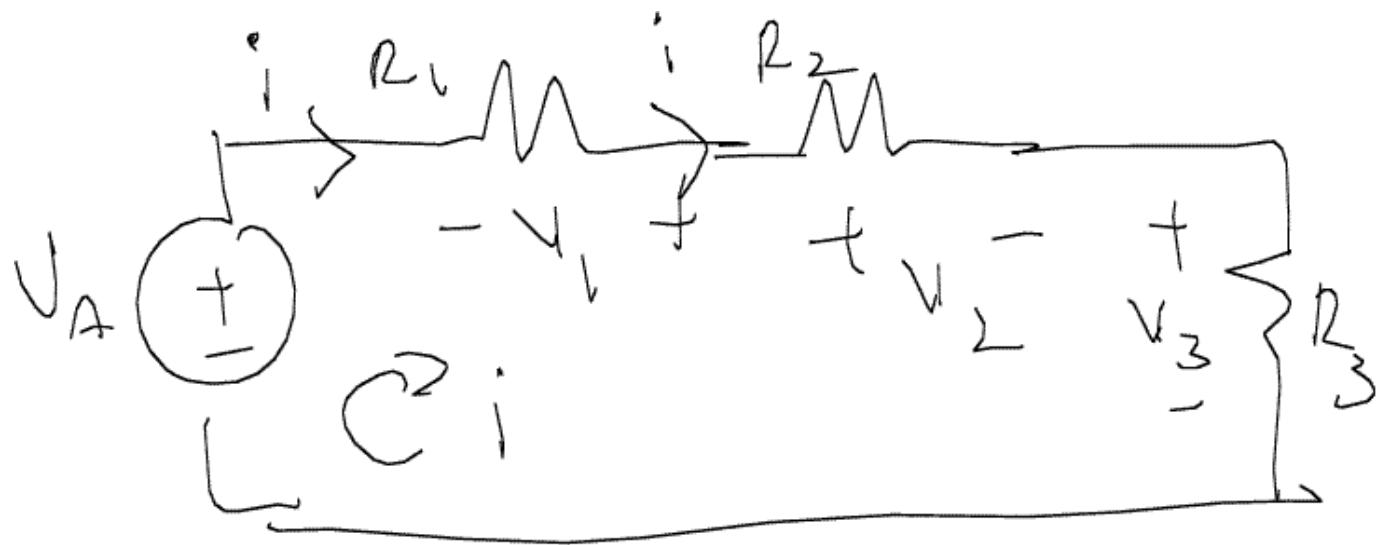

$$\text{KVL: } V_A + V_1 - V_2 - V_3 = 0$$

$$\Rightarrow V_A = -V_1 + V_2 + V_3$$

Ohm's law:  $V_1 = -iR_1$

$$\therefore V_A = iR_1 + iR_2 + iR_3$$

Bottomline: You can pick the direction of unknown voltages and currents in a circuit arbitrarily, you just have to apply the correct sign convention.

Next time → Finish chapter 3

- Voltage divider
- Parallel Circuits
- $\Delta$ -Y transforms
- Ex. 2.28

→ PSpice example

→ Chapter 4