

Lecture 4 - Chapter 3,  
Chapter 4 intro.

Administrivia: (1) I have office  
hours on Sunday!  
→ Check celoo website

---

To day : → Finish Chapter 3  
[skip 3.5, 3.6 & 3.7 😊]

skip  $\Downarrow$  problem 3-30 in HW#2

$\rightarrow$  Example 2.28

$\rightarrow$  Chapter 4: Introduction


$\rightarrow$  PSpice example

---

Recall: Elements in Series

Characteristic: Same currents flowing

through elements:

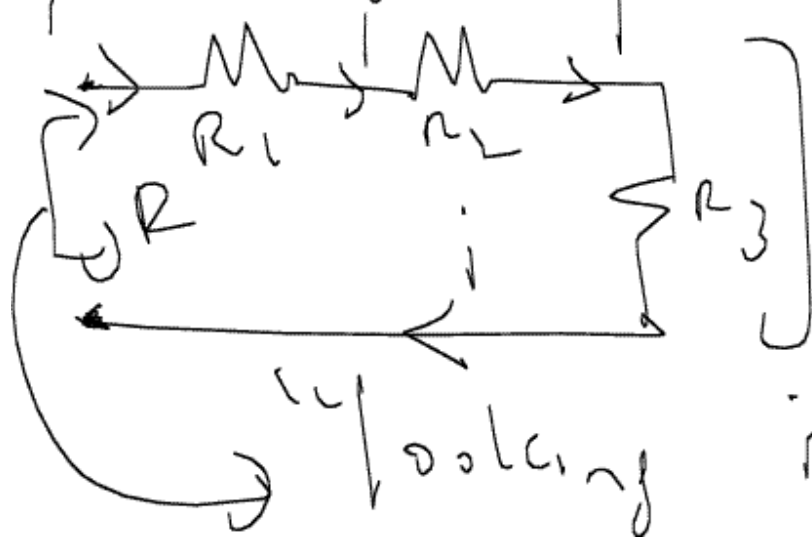


elements in series

$$R = R_1 + R_2 + R_3$$

# Voltage divider

Circuit which is used to obtain different voltage values from a single supply voltage

Important: output voltage  $<$  supply

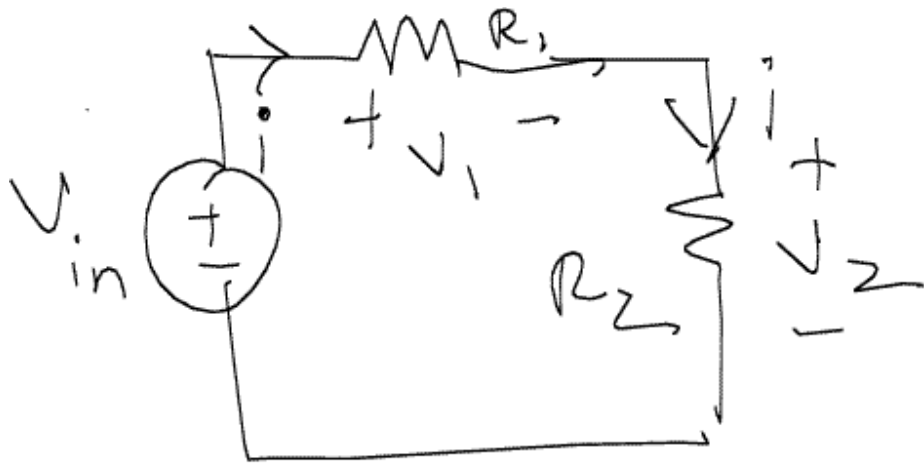

Goal: Find  $V_2$

$$V_2 = i R_2 \quad (\text{ohm's law})$$


$$V_2 = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

KVL:  $V_{in} = V_1 + V_2$

$$V_{in} = i R_1 + i R_2$$
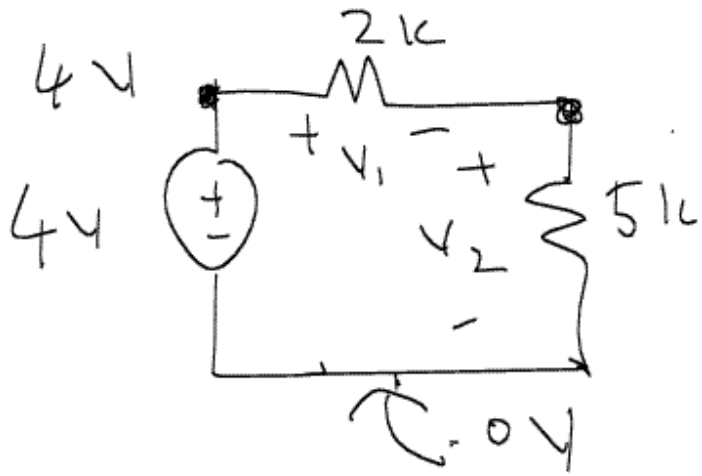
$$\Rightarrow i = \frac{V_{in}}{R_1 + R_2}$$






$$V_2 = (4V) \left[ \frac{5k}{2k+5k} \right] \quad (\text{Voltage divider})$$

$$= 4 \cdot \frac{5}{7} = \frac{20}{7} \approx 2.86V$$

---


Current divider: → Not very practical,  
 good thing to know!

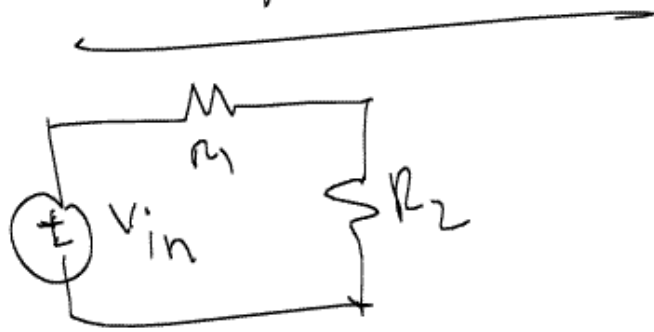This is the "deal" of voltage divider  
Voltage divider



Series

Current divider

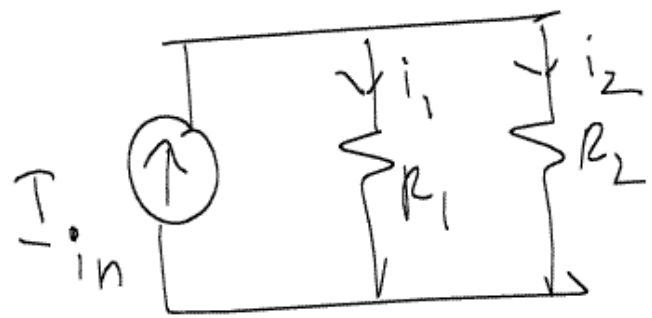


parallel

(Q:) Give an example of a circuit with at least one voltage source in which all the elements are in series

2 parallel at the same time can  
prove a circuit like that cannot exist.


ex:

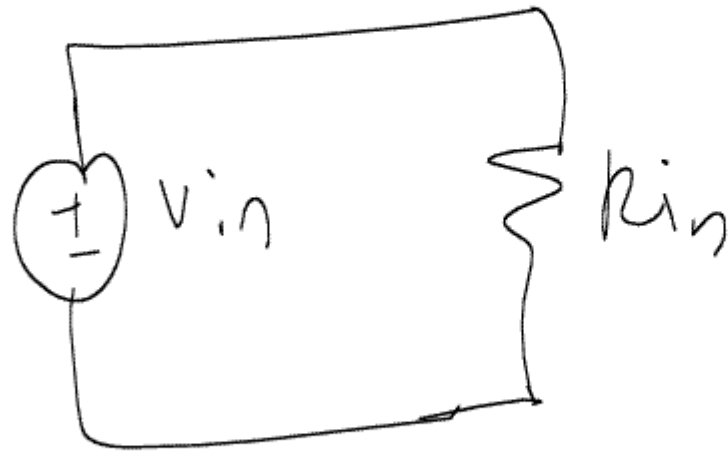

← I think  
this is the  
only type of  
circuits ???


---




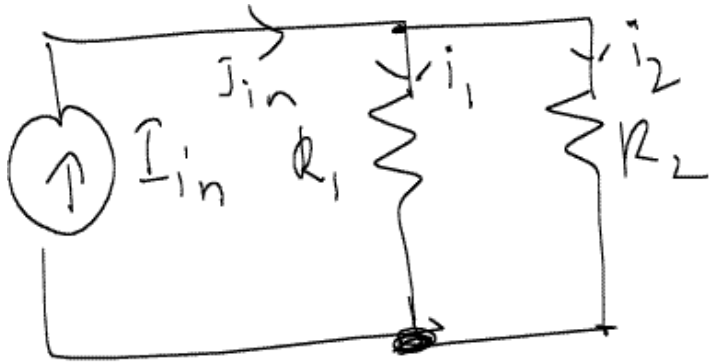

Parallel: voltages across every element is the same.

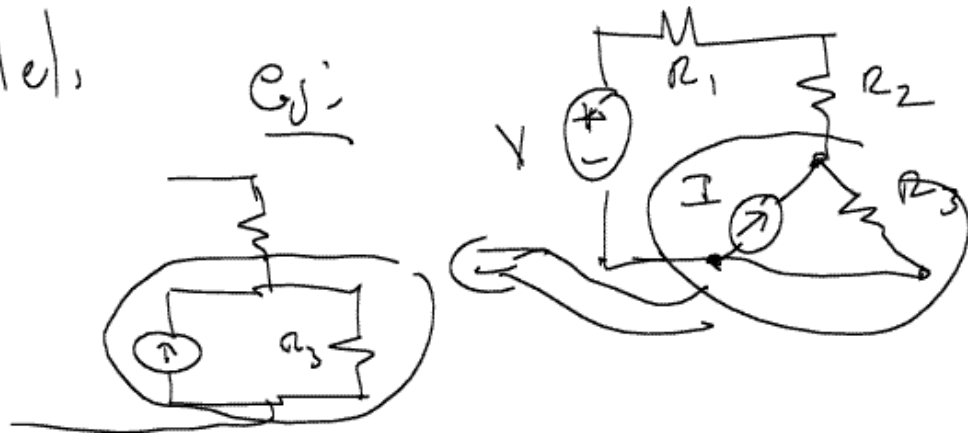Tricks: If you go around a loop once, you hit two elements, they are in parallel.



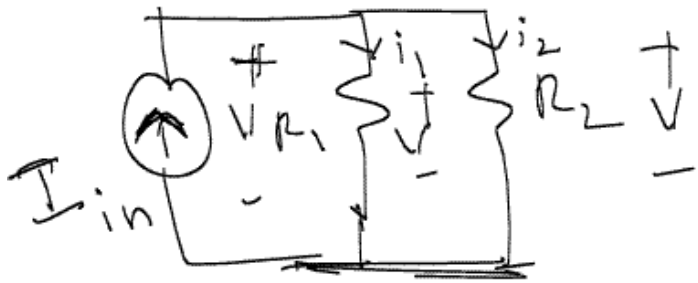

$$i_1 = \frac{V}{R_1}, \quad i_2 = \frac{V}{R_2} \quad \left( \begin{array}{l} \text{Ohm's} \\ \text{Law} \end{array} \right)$$

$$I_{in} = i_1 + i_2 \quad (\text{KCL})$$


$$I_{in} = \frac{V}{R_1} + \frac{V}{R_2}$$

parallel  
resistors  
↓  
formula


$$\Rightarrow \frac{I_{in}}{V} = \frac{1}{R_1} + \frac{1}{R_2}$$

$\Rightarrow$   
 $\frac{1}{R_{eq}}$
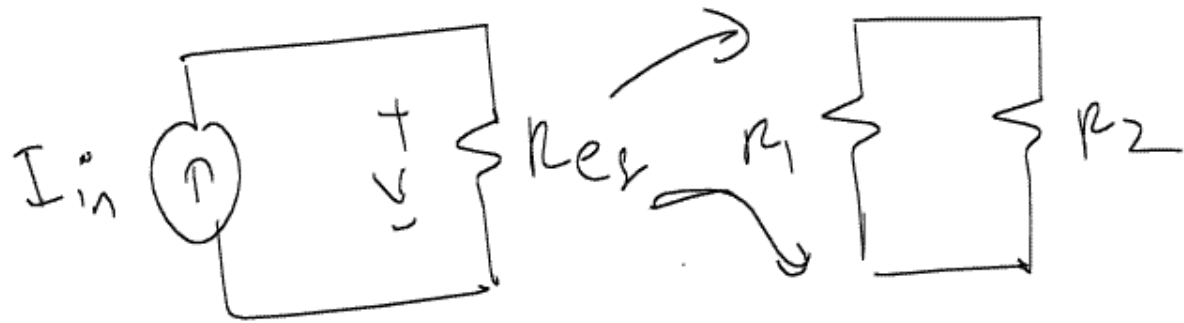
$$\boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}}$$




Tip: Intuitively understanding formula

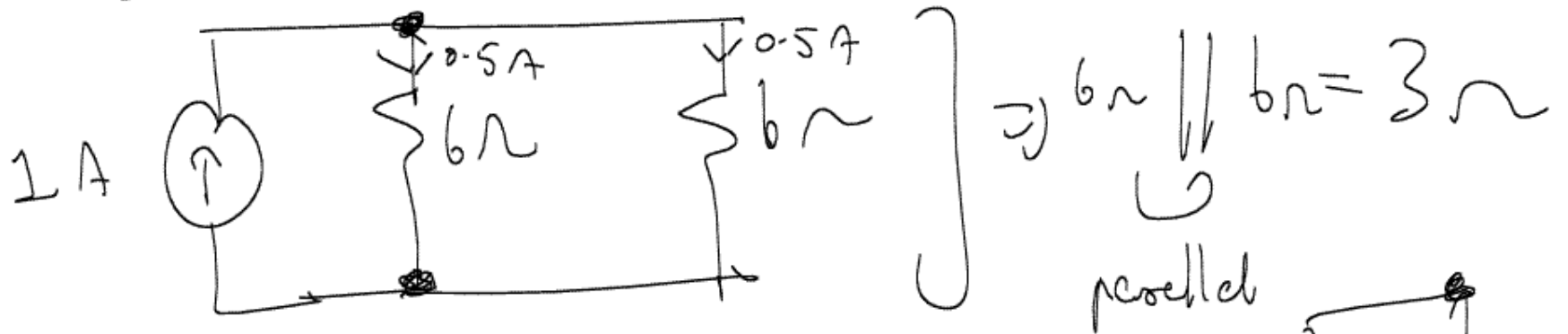

$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{6} = \frac{1}{3} \Rightarrow R_{eq} = 3\Omega \Rightarrow$$

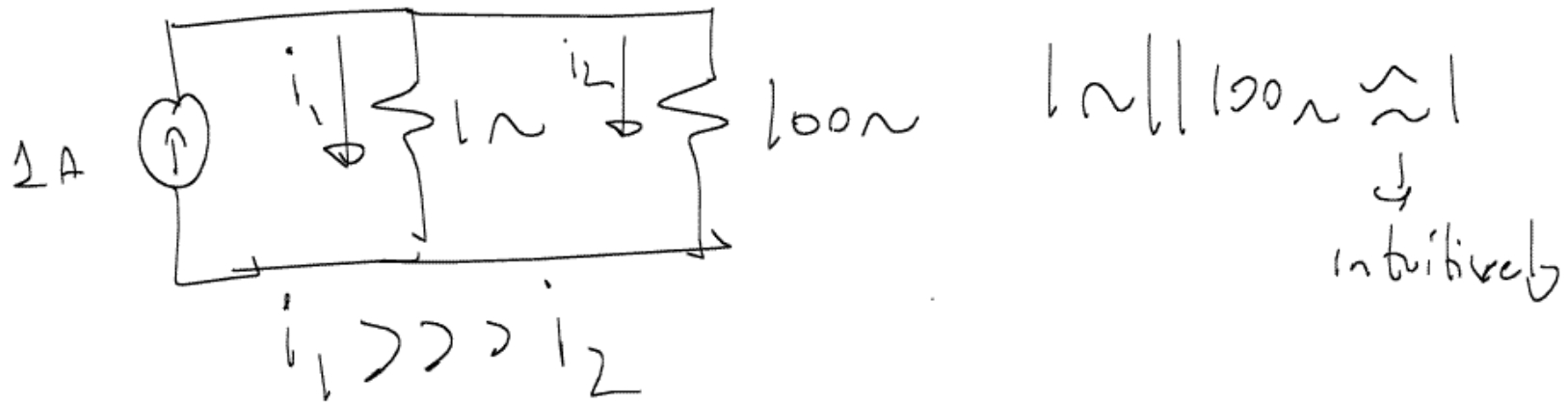A simplified circuit diagram showing a  $2A$  current source in parallel with a  $3\Omega$  resistor.




$$\frac{1}{R_{eq}} = \frac{1}{1} + \frac{1}{100} \Rightarrow R_{eq} = \frac{1}{1.01} \approx \underline{\underline{0.99\Omega}}$$

Notice  $0.99 < 1 \leftarrow$  Smallest resistor,

In other words, equivalent resistance better be smaller than the smallest resistance in parallel combination

Finish deriving current divider

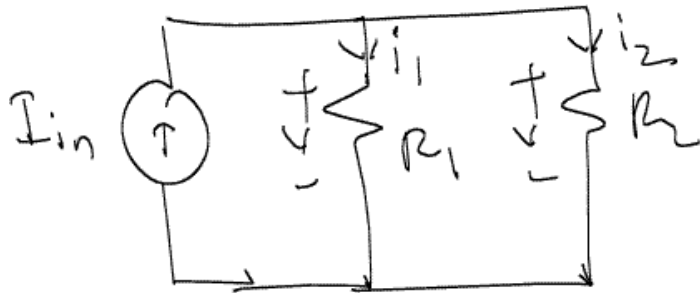

$$i_1 = \frac{V}{R_1}$$

$$i_2 = \frac{V}{R_2}$$

$$I_{in} = i_1 + i_2 \Rightarrow I_{in} = \left( \frac{V}{R_1} + \frac{V}{R_2} \right)$$

$$\Rightarrow I_{in} = V \left[ \frac{R_1 + R_2}{R_1 R_2} \right]$$


$$\Rightarrow V = \frac{R_1 R_2}{R_1 + R_2} I_{in}$$

$$\therefore i_1 = \frac{\cancel{R_1} R_2}{R_1 + R_2} I_{in} \xrightarrow{\cancel{R_1}} i_1 = \frac{R_2}{R_1 + R_2} I_{in}$$

Similarly,

$$i_2 = \frac{R_1}{R_1 + R_2} I_{in}$$

Example: Problem 2-28 (p. 61)

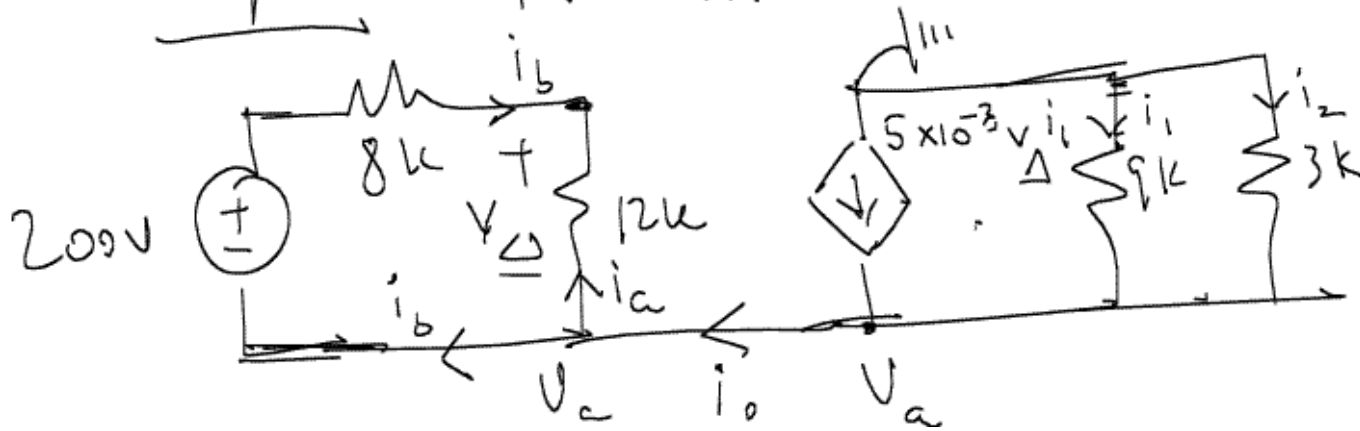


(Q:) Find  $i_o, i_1, i_2$ .


(a)  $i_o = 0 A$ . Why? (1)  $V_a \rightarrow V_a = 0$   
[no voltage drop]



(2) KCL:  $i_o = i_a + i_b$   
 $i_b + i_a = 0 \Rightarrow i_b = -i_a$

(3)

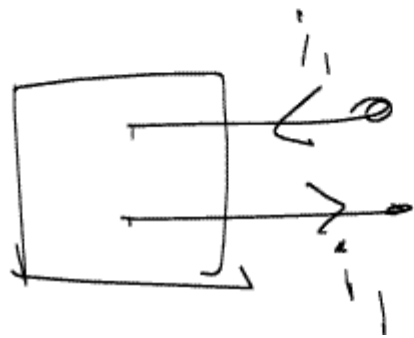

} KCL

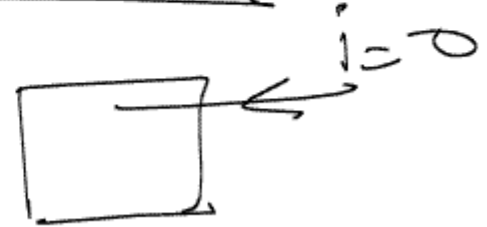


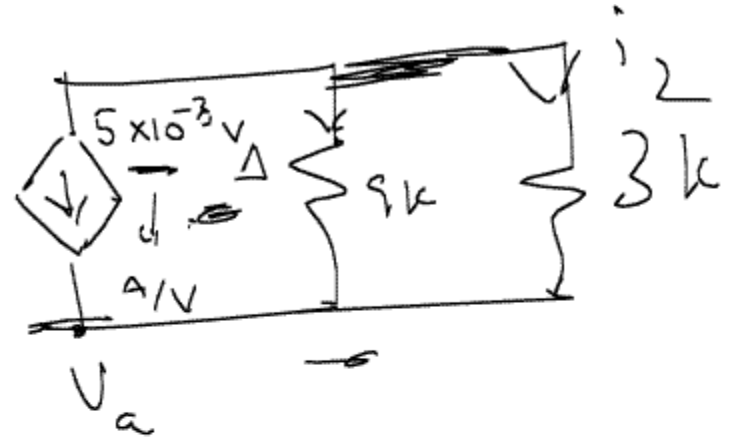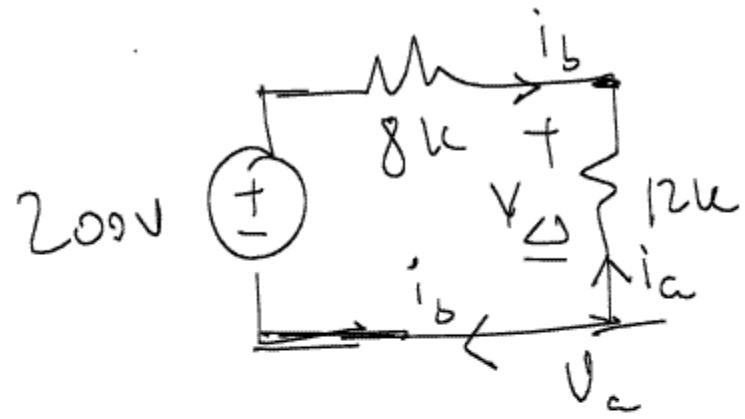

$$V_{\Delta} = 200 \cdot \left( \frac{12k}{8k + 12k} \right) \quad \left[ \text{Voltage divider} \right]$$

$$V_a = 120 V$$



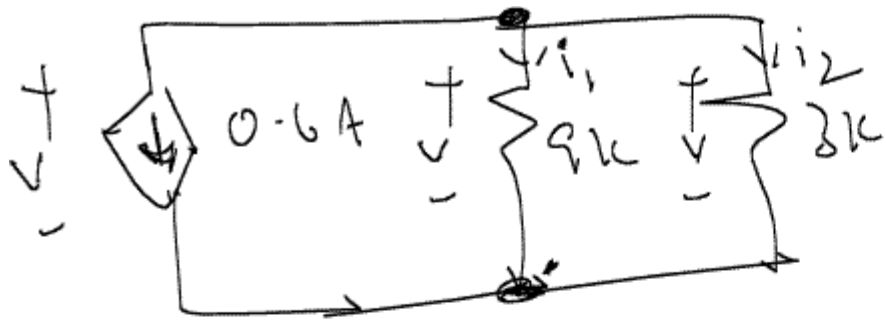


KCL:  $0.6 + i_1 + i_2 = 0$

$$i_1 = \frac{V}{9k}, \quad i_2 = \frac{V}{3k}$$


$$\therefore 0.6 + \frac{V}{9k} + \frac{V}{3k} = 0$$

$$\Rightarrow V = -\alpha \text{ volts}$$

This means!

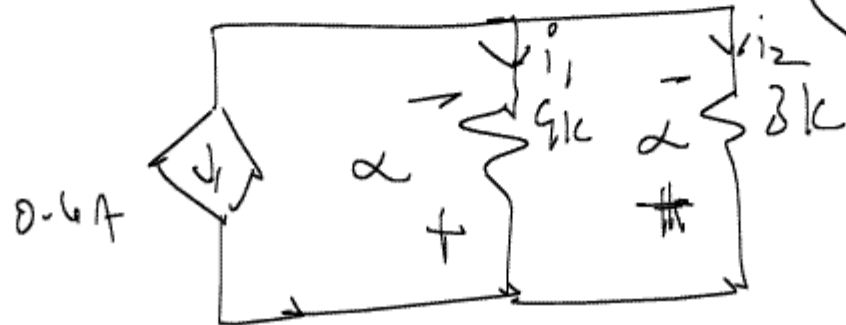

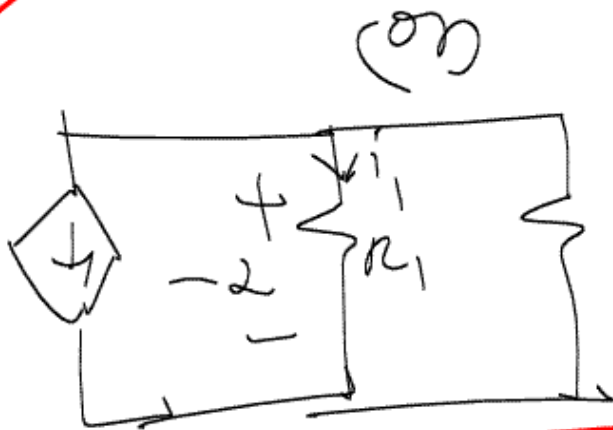Ohm's law:  $i_1 = \frac{-\alpha}{R_1}$  Because  $i_1$  enters negative terminal.



Ohm's law:  $i_1 = + \left( \frac{-\alpha}{R_1} \right)$

Most common mistake:  ~~$i_1 = \frac{\alpha}{R_1}$~~

Tip: Don't carry negative sign around

---

# Chapter 4 - Techniques of Circuit Analysis

---

Section 4.1  $\Rightarrow$  Read. Don't need to  
know all circuit terminology.

Important: node, branch, ground or  
reference node.

---

Next time: Nodal Analysis (oo)  
Node Voltage method.