

# Lecture 9 - Finish chapter 4

Administrivia - (1) No labs this week (02/14) <sup>& next week (02/21)</sup>, but TAs will be in lab to answer questions\*

Don't do part (b) in 4-58 in Hw#4

(2) Grades online now arranged by increasing SID nos.

Today: Thevenin/Norton

Maximum power transfer

Finish chapter 4

Not responsible for mesh analysis

& Superposition


← Taleh does not have lab tonight

Theremin's theorem: Statement unimportant,



French dude

Concept: EQUIVALENT CIRCUIT


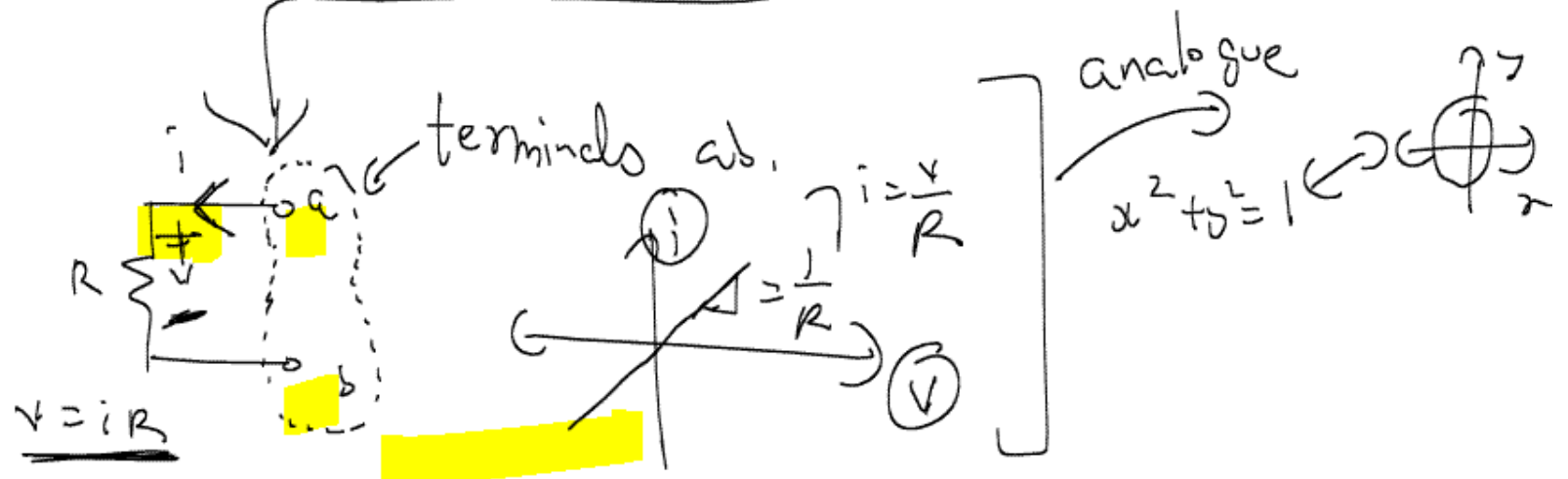


Theremin noticed something very interesting: If you have a linear circuit, then the i-v graph

will be a straight line. Now, you need two points to plot a straight line. KEY CONCEPT:



**TWO DIFFERENT LINEAR CIRCUITS CAN GIVE RISE TO THE SAME I-V GRAPH!**

eg  $i$  vs  $v$

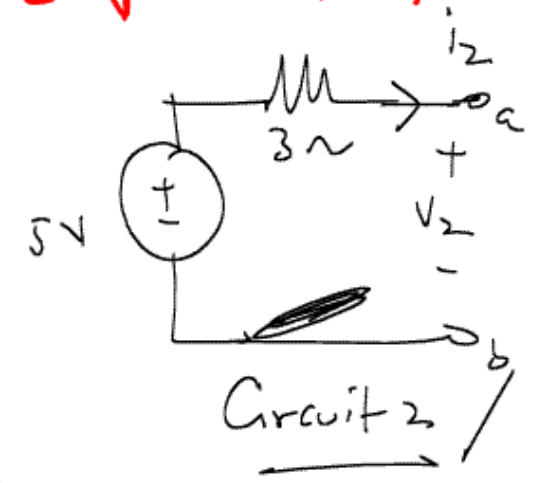
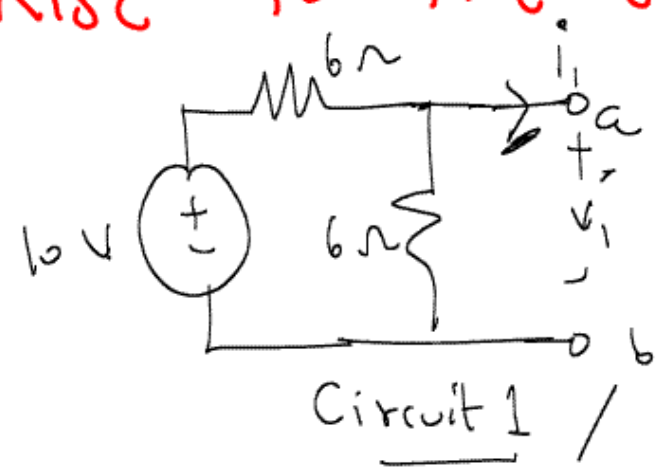


Turns out  $i$  vs  $v$  graph for both circuits at terminals ab are the same!

Matter mechanically

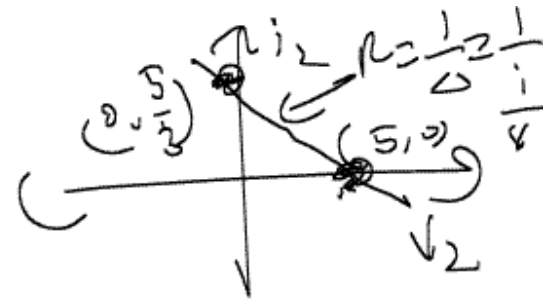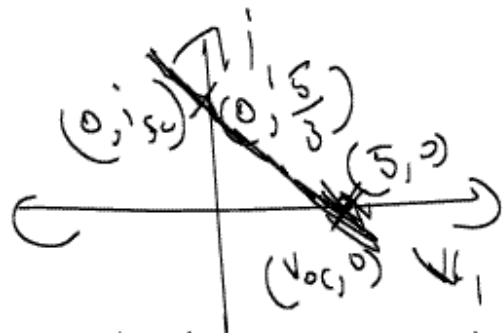

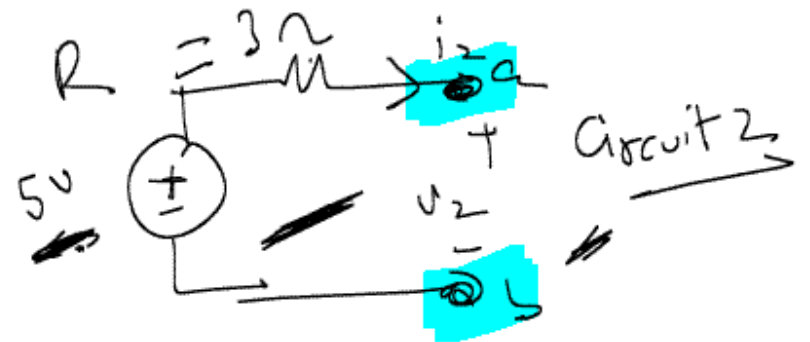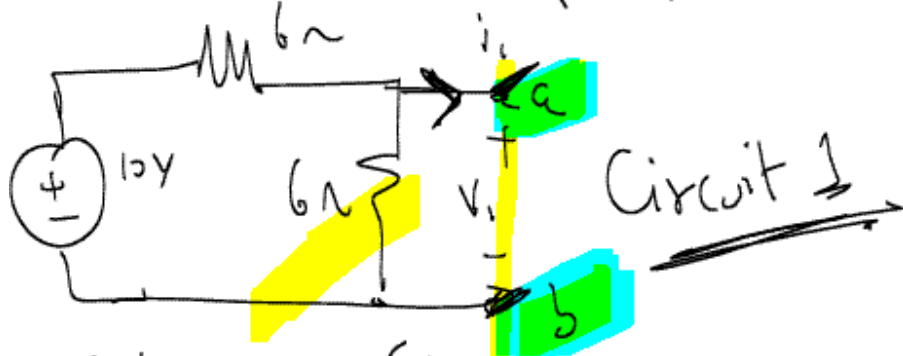
intercepts help plot straight line(s) easily!



x-intercept:  $(V_{oc}, 0) \rightarrow$  open circuit



y-intercept:  $(0, I_{sc}) \rightarrow$  short circuit

$$V_{oc} = 5 \text{ V}$$

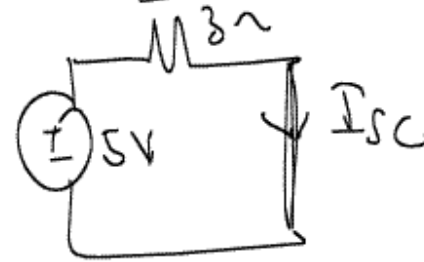

$$I_{sc} = \frac{5}{3} \text{ A}$$

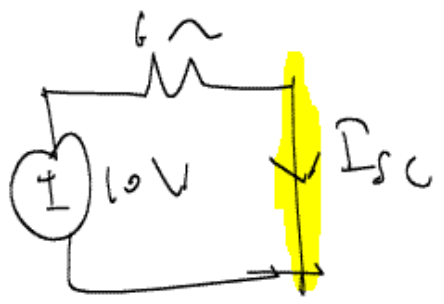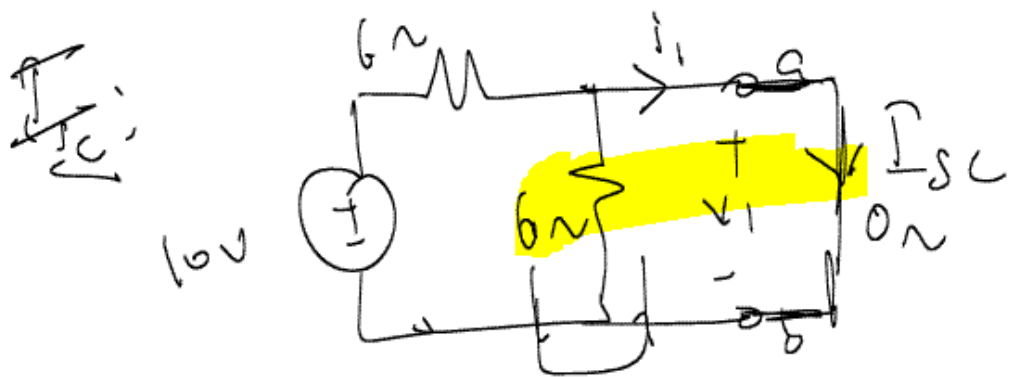V<sub>oc</sub>:  $V_{oc} = \left( \frac{6}{6+6} \right) 10$  (voltage divider)  
 $\approx 5 \text{ V}$




ignore (0Ω || 6Ω) = 0Ω

$$I_{sc} = \frac{10}{6} = \frac{5}{3} \text{ A}$$


Note:  $V_2 = V_{oc}$

How is R related to  $V_{oc}$  &  $I_{sc}$ ?

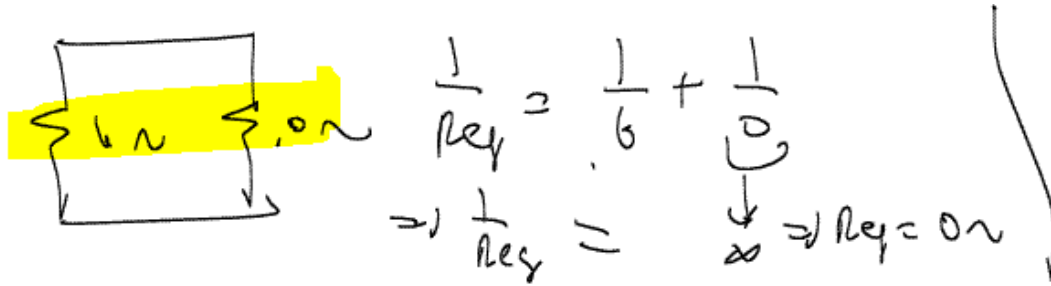
$$R = \frac{V_{oc}}{I_{sc}} = \frac{5}{\frac{5}{3}} = 3\Omega$$




Point of Thevenin's

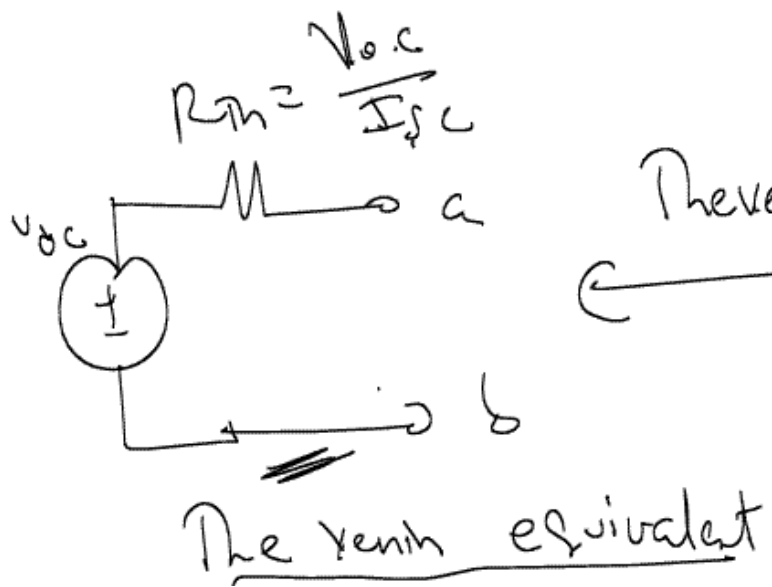


Thevenin's

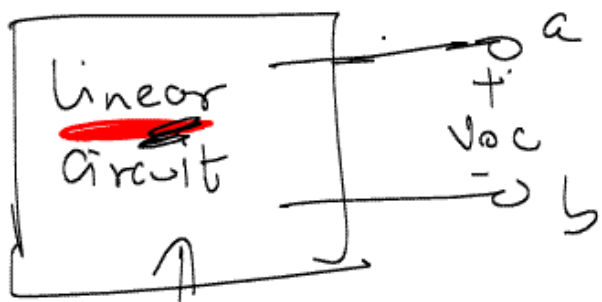


Same

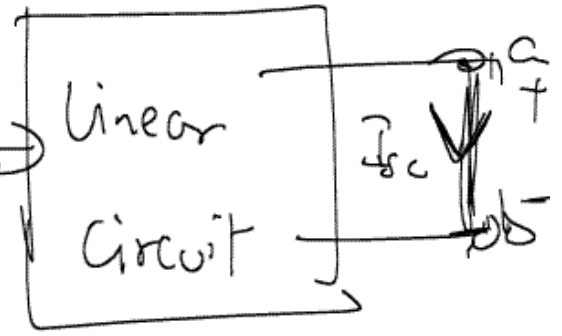


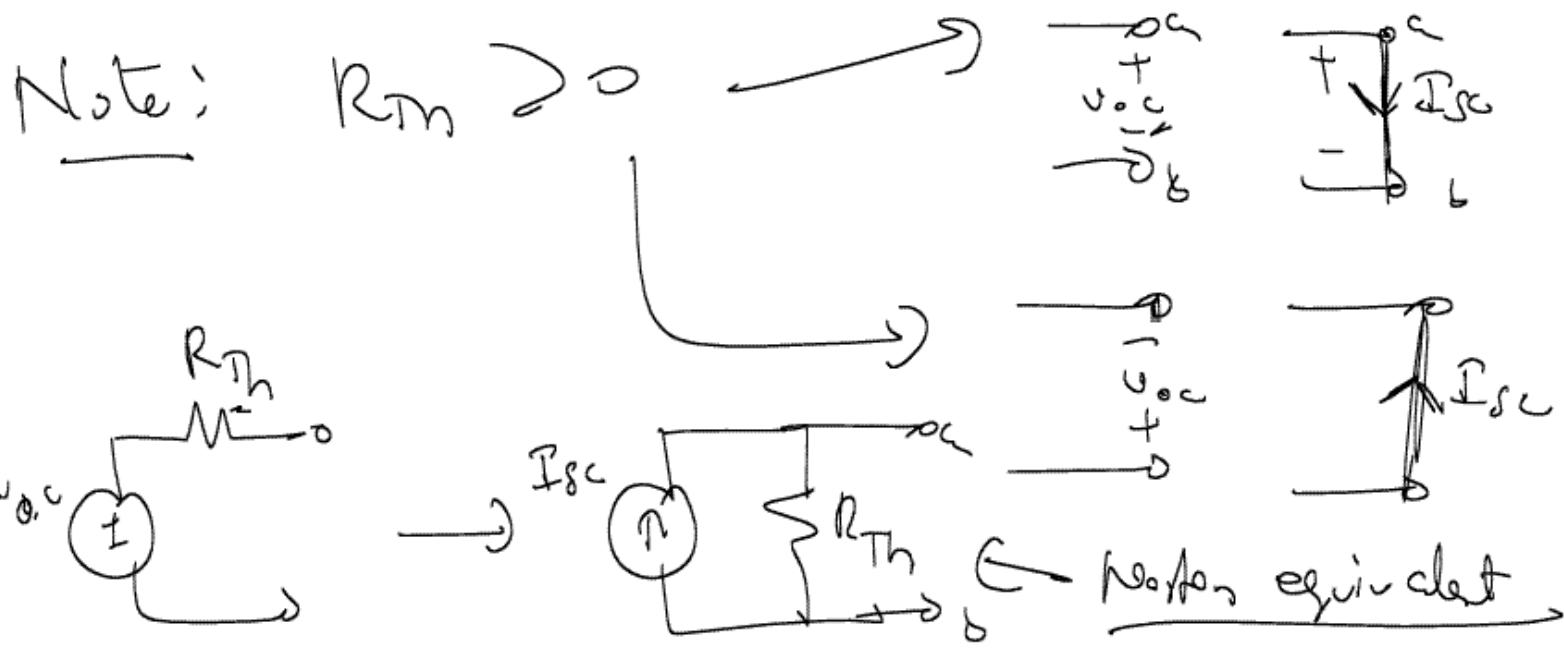

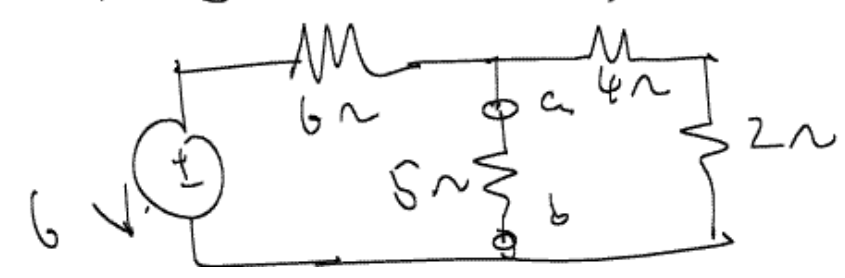Eg: Find the <sup>Norton</sup> equivalent at ab





Solution:

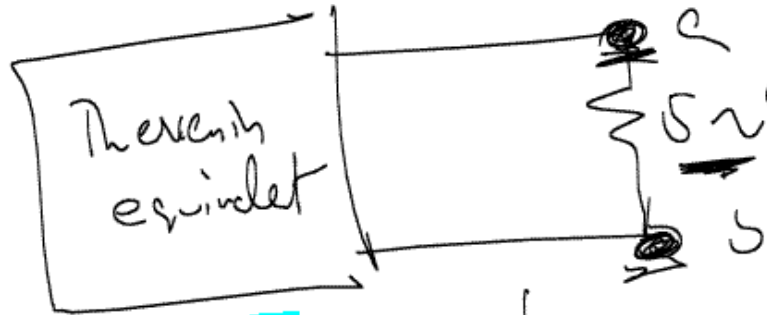


Don't include resistance in calculation

Voc:

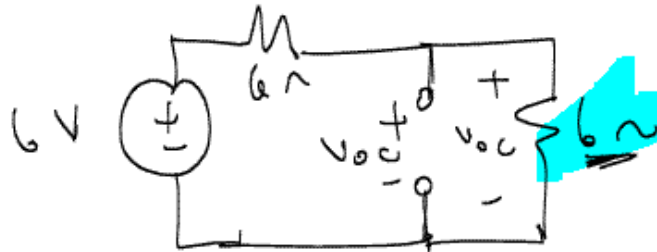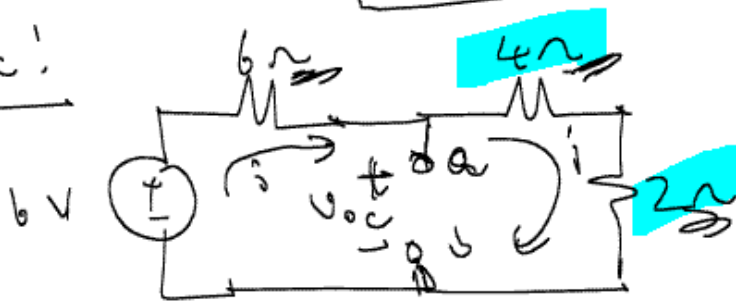

$$V_{oc} = \left( \frac{6\Omega}{6\Omega + 6\Omega} \right) 6V = 3V$$


Isc:

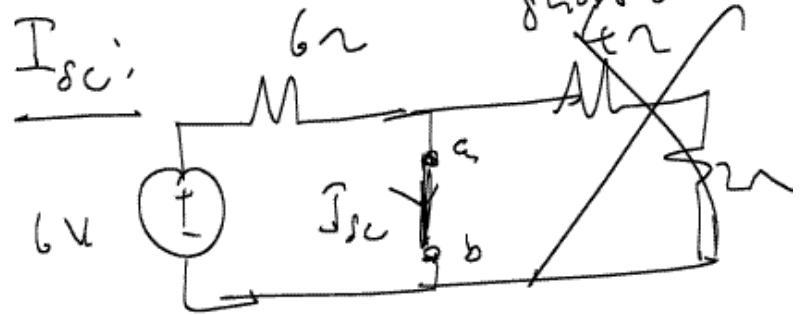


$$I_{sc} = 1A$$
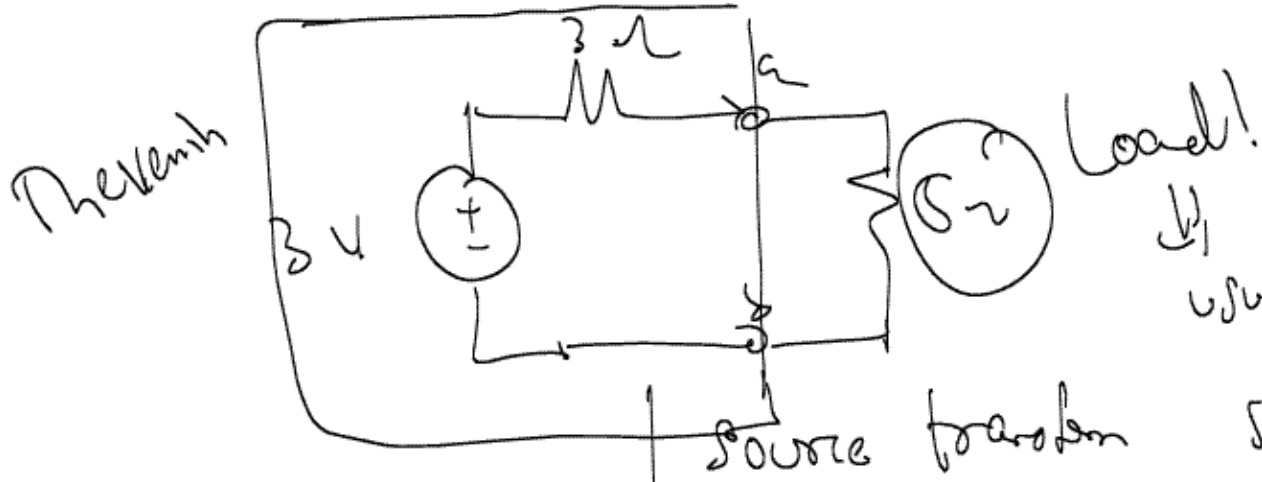
$$R_{th} = \frac{V_{oc}}{I_{sc}} = 3\Omega$$





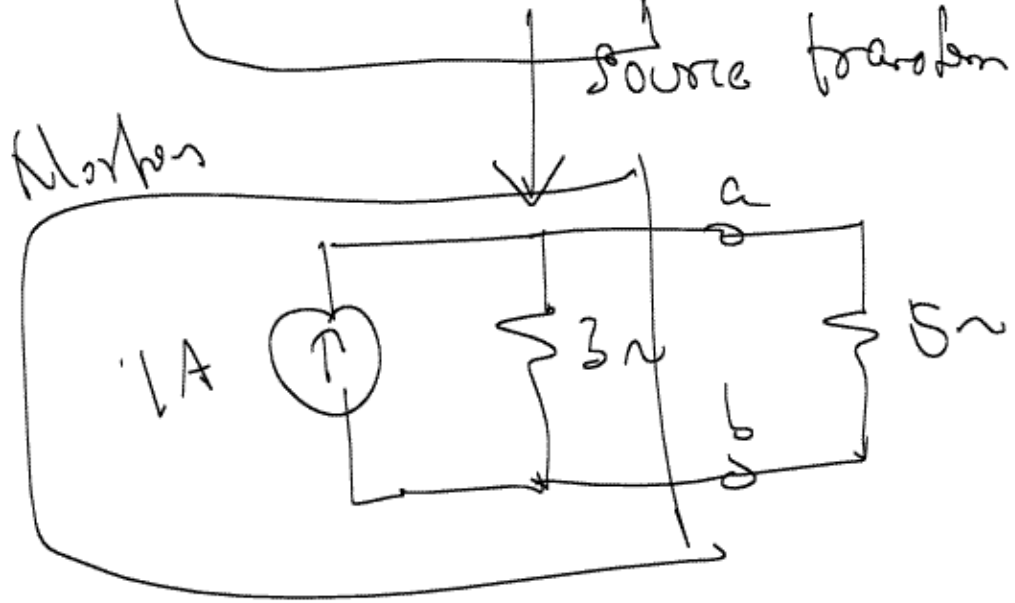usually nonlinear  
 ↓  
 so you don't  
 include in  
 Thévenin





Note: Two shortcuts to Thévenin!

Shortcut 2: If a circuit has only independent sources & resistors (i.e. no dependent source)

Shortcut: Easily compute  $R_{in}$


Previous example:

idea

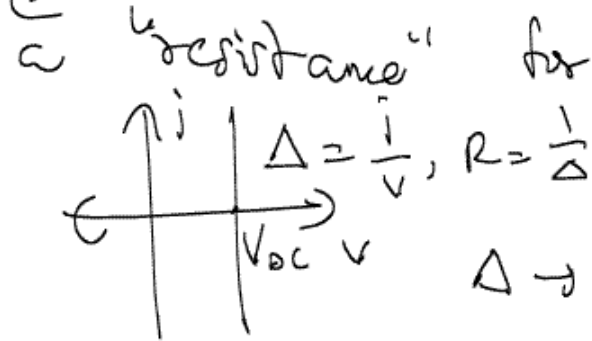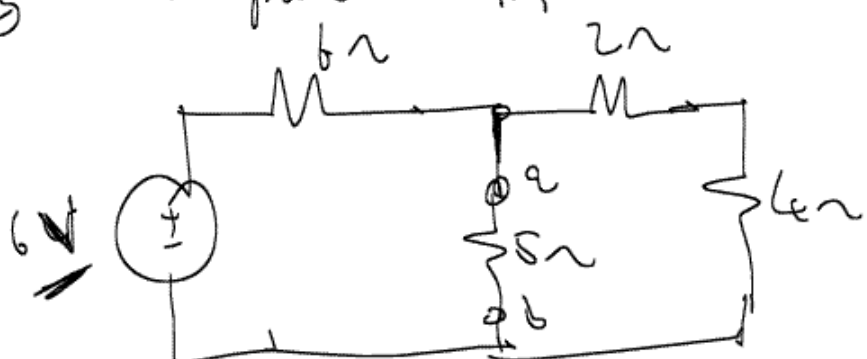


replace voltage source with short circuit!

Similarly

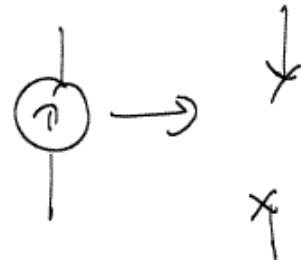


Note! This will not work for dependent sources!


Therefore:

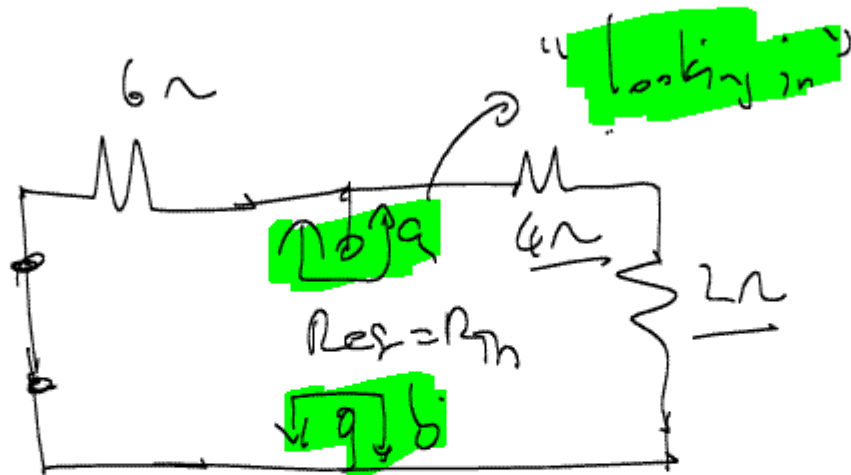
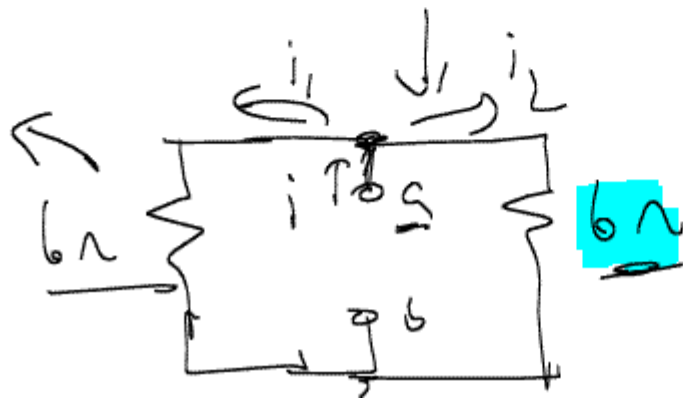
$$R_{th} = 6\Omega \parallel 6\Omega = 3\Omega$$



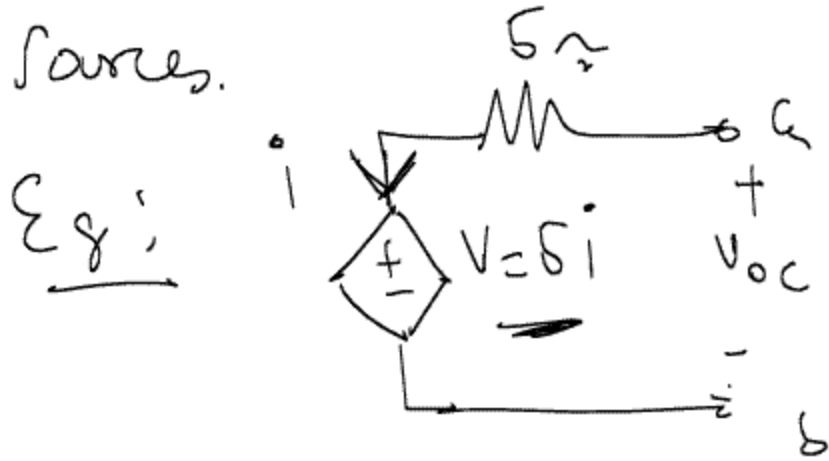Short cut 2: A circuit with only dependent sources.



Find thevenin equivalent at ab


Voc?  $i = 0$  (open circuit)

$$\boxed{V_{oc} = 0 \text{ V}}$$

$$I_{sc} = i = 0 \text{ A}$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} \rightarrow \text{undefined}$$

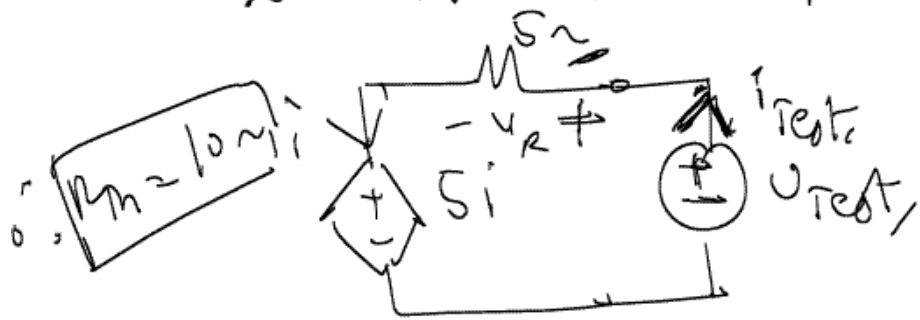Therefore, we have to apply a test voltage & use it to compute  $R_{Th}$ .



$$R_{Th} = \frac{V_{test}}{i_{test}}$$

$$V_R = S_i R_{Th}$$

$$V_{test} = V_R + S_i R_{Th}$$

[kV]


---

$\therefore V_{test} = 10 i_{test}$        $\because i = i_{test}$


Note: (1) Direction of  $i_{test}$ . (2) polarity of positive terminal because  $V_{test}$  is power in the circuit!

(2) You can use  $V_{test} = 10 V$  (or) any other number, except 0 V!


Thevenin equivalent:

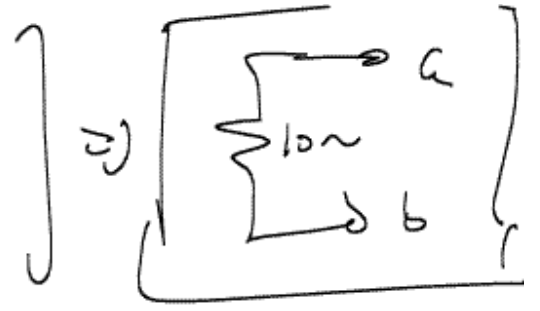


Note (2):

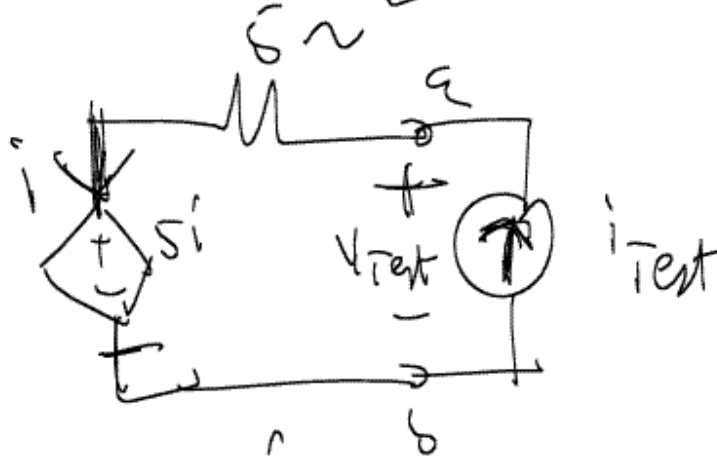

Note:

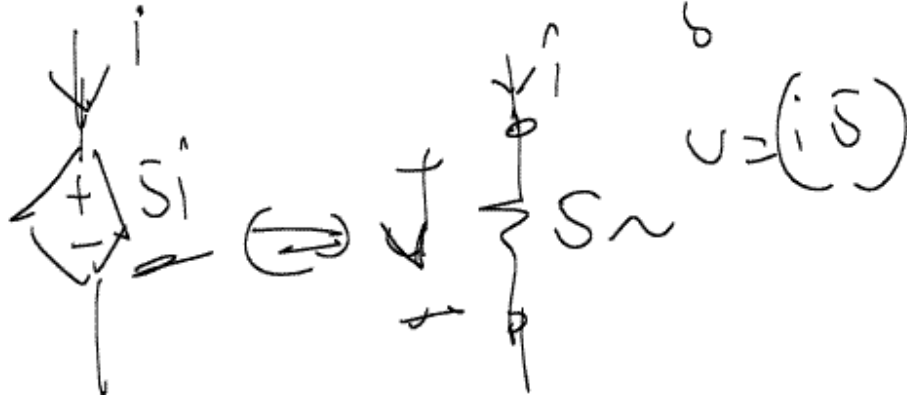

Last topic is chapter 4: Maximum power

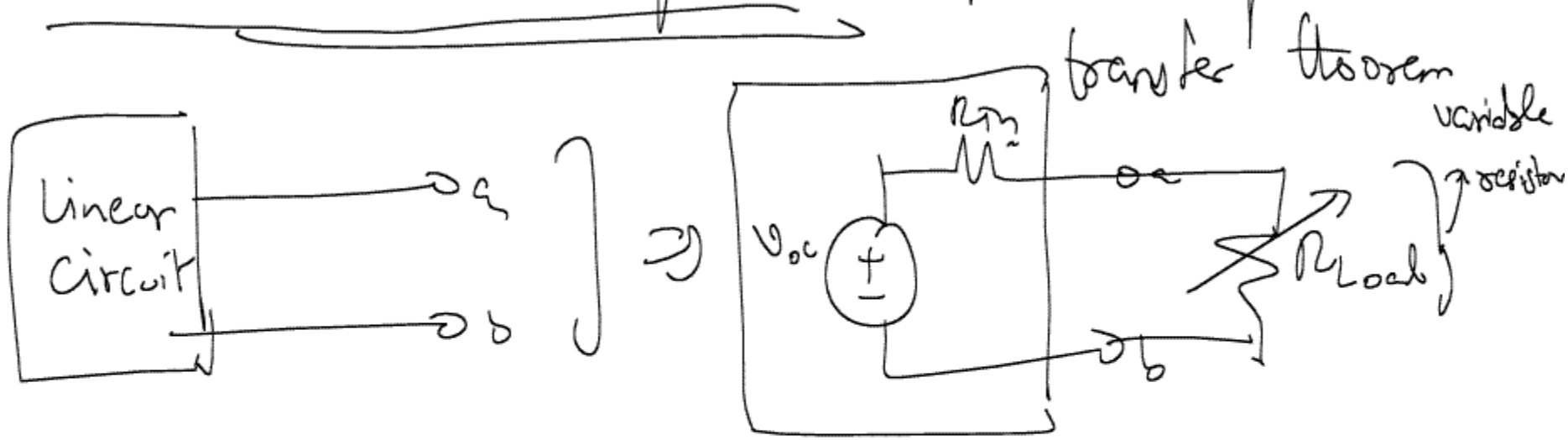

(Q:) What value of  $R_{load}$  (in terms of  $R_m$ )  
so maximum power is dissipated in  $R_{load}$ ?

Let's think for a little!

$$P = V_i i$$

load  $R_{load} = 0 \Rightarrow$  short-circuit  
doesn't make



Sense practically, no device with 0 resistance

(2)  $R_{load} \rightarrow \infty \Rightarrow$  open circuit

Turns out  $R_{load} = R_m$

← MAXIMUM POWER TRANSFER THEOREM

Proof: Calculates:

$$P = V_i i = \left[ \frac{R_{load}}{R_{load} + R_m} \right] V_{oc} i$$



We also know:  $P(R_{load}) = \left( \frac{R_{load}}{R_{load} + R_{in}} \right) V_{oc} \cdot \frac{V_{oc}}{R_{load}}$

$$P(R_{load}) = \left( \frac{R_{load}}{R_{load} + R_{in}} \right) V_{oc} \cdot \frac{V_{oc}}{R_{load}}$$

Notice:  $R_{th}$ ,  $V_{oc}$  are known, so

$\frac{dP}{dR_{load}} = 0$  simplify  $(R_{in} = R_{load})$

↳ Refer to chapter 4 for details on maths!

Note! Problem 4-86 (Hw #5) <sup>next week</sup> is good

Next time: Applications of circuits  
↓  
AC Circuits