

EE 100/42 Spring 2009 Solutions to Homework 2

P 2.9 Combining the resistances shown in Figure P 2.9b, we have

$$\begin{aligned}R_{\text{eq}} &= 1 + \frac{1}{1 + \frac{1}{R_{\text{eq}}}} + 1 = 2 + \frac{R_{\text{eq}}}{1 + R_{\text{eq}}} \\R_{\text{eq}}(1 + R_{\text{eq}}) &= 2(1 + R_{\text{eq}}) + R_{\text{eq}} \\(R_{\text{eq}})^2 &= 2R_{\text{eq}} - 2 = 0 \\R_{\text{eq}} &= 2.732 \Omega\end{aligned}$$

($R_{\text{eq}} = -0.732 \Omega$ is another root, but is not physically reasonable)

P 2.10 The 12Ω and 6Ω resistors are in parallel having an equivalent resistance of 4Ω . Similarly, the 18Ω and 9Ω resistors are in parallel and have an equivalent resistance of 6Ω . Finally, the two parallel combinations are in series and we have:

$$R_{\text{ab}} = 4 + 6 = 10 \Omega$$

P 2.16 The 20Ω and 30Ω resistors are in parallel and have an equivalent resistance of $R_{\text{eq1}} = 12 \Omega$. The 40Ω and 60Ω are in parallel and have an equivalent resistance of $R_{\text{eq2}} = 24 \Omega$. Next we see that R_{eq1} and the 4Ω resistor are in series and have equivalent resistance of $R_{\text{eq3}} = R_{\text{eq1}} + 4 = 16 \Omega$. Finally, R_{eq2} and R_{eq3} are in parallel and the overall equivalent resistance is

$$R_{\text{ab}} = \frac{1}{\frac{1}{R_{\text{eq2}}} + \frac{1}{R_{\text{eq3}}}} = 9.6 \Omega$$

P 2.47 At node 1 we have: $\frac{V_1}{20} + \frac{V_1 - V_2}{10} = 1$

At node 2 we have: $\frac{V_2}{5} + \frac{V_2 - V_1}{10} = 2$

The equations can be rewritten as

$$\begin{aligned}0.15V_1 - 0.1V_2 &= 1 \\-0.1V_1 + 0.3V_2 &= 2\end{aligned}$$

Solving simultaneously we get $V_1 = 14.29$ and $V_2 = 11.43$
Then we have $i_1 = \frac{V_1 - V_2}{10} = 0.2857A$

P 2.49 Writing KCL equations at nodes 1, 2, and 3 we have

$$\begin{aligned}\frac{V_1}{5} + \frac{V_1 - V_2}{15} + \frac{V_1 - V_3}{15} &= 0 \\ \frac{V_2 - V_1}{15} + \frac{V_2 - V_3}{15} &= 4 \\ \frac{V_3}{25} + \frac{V_3 - V_2}{15} + \frac{V_3 - V_1}{15} &= 0\end{aligned}$$

These equations can be rewritten as

$$\begin{aligned}.333V_1 - 0.06667V_2 - 0.06667V_3 &= 0 \\ -0.06667V_1 + 0.1333V_2 - 0.06667V_3 &= 4 \\ -0.06667V_1 - 0.06667V_2 + 0.1733V_3 &= 0\end{aligned}$$

Solving simultaneously we get $V_1 = 15$, $V_2 = 50$, and $V_3 = 25$

P 2.51 Writing KCL equations at nodes 1 and 2, we have

$$\begin{aligned}\frac{V_1}{21} + \frac{V_1}{28} + \frac{V_1 - V_2}{9} &= 3 \\ \frac{V_2 - V_1}{9} + \frac{V_2}{6} &= -3\end{aligned}$$

which can be rewritten as

$$\begin{aligned}0.194V_1 - 0.111V_2 &= 3 \\ -0.111V_1 + 0.278V_2 &= -3\end{aligned}$$

Solving simultaneously we find $V_1 = 12$ and $V_2 = -6$.

If the source is reversed, the algebraic signs of the node voltages are reversed.

P 2.54 Once a 1 Amp source is connected to a and b, three nodal equations can be written

$$\begin{aligned}\frac{V_1 - V_2}{10} + \frac{V_1 - V_3}{20} &= 1 \\ \frac{V_2}{10} + \frac{V_2 - V_1}{10} + \frac{V_2 - V_3}{10} &= 0 \\ \frac{V_3}{20} + \frac{V_3 - V_1}{20} + \frac{V_3 - V_2}{10} &= 0\end{aligned}$$

Solving simultaneously, we find $R_{eq} = V_1 = 13.33 \Omega$

P 2.62 Writing KVL equations around each mesh, we have

$$\begin{aligned}5i_1 + 7(i_1 - i_3) + 100 &= 0 \\ 11(i_2 - i_3) + 13i_2 - 100 &= 0 \\ 9i_3 + 11(i_3 - i_2) + 7(i_3 - i_1) &= 0\end{aligned}$$

which can be rewritten as

$$\begin{aligned}12i_1 - 7i_3 &= -100 \\24i_2 - 11i_3 &= 100 \\-7i_1 - 11i_2 + 27i_3 &= 0\end{aligned}$$

Solving, we obtain $i_1 = -8.741$ A, $i_2 = 3.846$ A, and $i_3 = -0.6993$ A. Then, the power delivered by the source is $P = 100(i_1 - i_2) = 1259$ W.