

EECS 100, Spring 2009

Homework #4

$$\text{P 3.25 (a) } C_{eq} = 3 + \left(\frac{1}{10} + \frac{1}{15} \right)^{-1} + \left(\frac{1}{12} + \frac{1}{(5+1)} \right)^{-1} = 13\mu F$$

$$\text{(b) } C_{eq} = \left(\frac{1}{10+8} + \frac{1}{4+5} \right)^{-1} = 6\mu F$$

P.3.28


$$I=C(dv/dt) \quad q=CV \quad C_{eq}=1/C_1+1/C_2=6\mu F$$


$$Q=CV= C_{eq} \cdot V=60\mu C$$

$$V_1=Q/ C_1=4V \quad V_2=Q/ C_2=6V$$

P.3.45
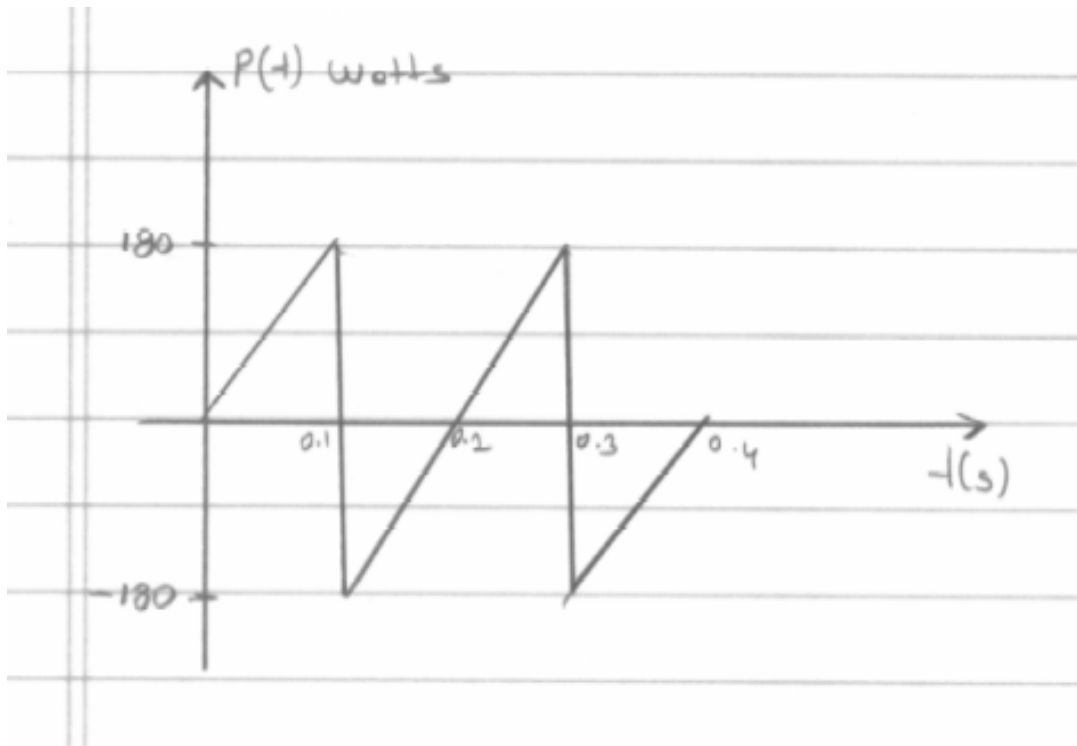
$$V_t = L(di/dt) \quad w(t) = 1/2 Li(t)^2 \quad p(t) = i(t)v(t)$$



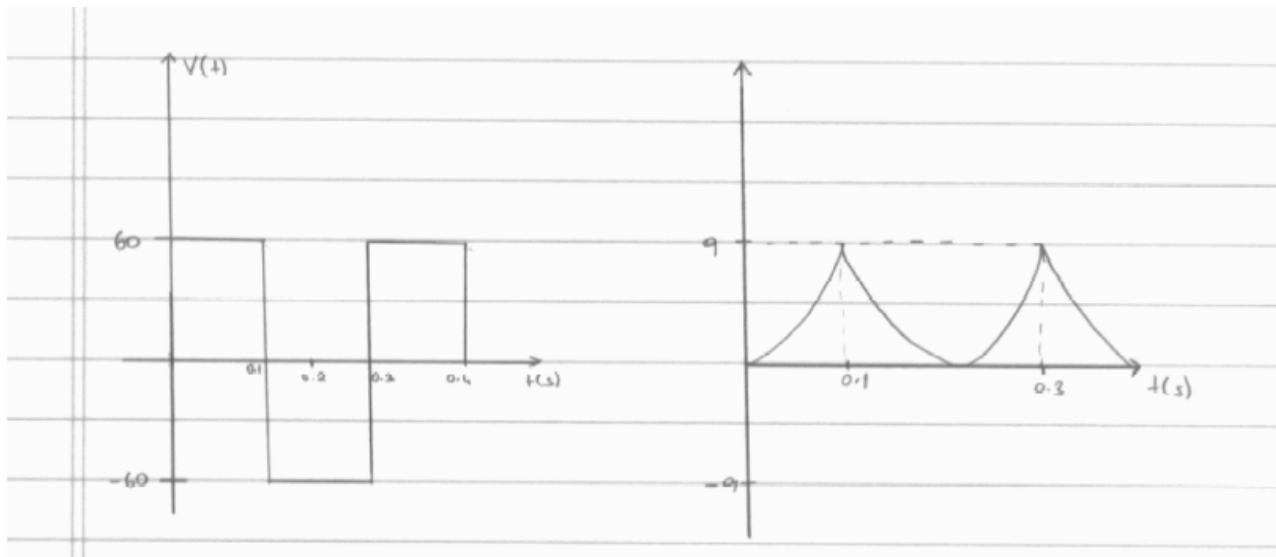

3.62

a) $L1=1H+2H=3H$
 $L2=1/3+1/6=2H$ $L_{equ}=2H+1H=3H$

b) $L1=1/20+1/5=4H$
 $L2=1/18+1/9=6H$ $L1+L2=10H$

$L_{final}=1/10+1/15=6$

3.68

$$c(t)=0.1\cos(10^5t) \quad V_L=L(di/dt)=-100\sin(10^5t)$$

$$V_R=i(t)R_s=0.1\cos(10^5t)$$

$$V_L + V_R=0.1\cos(10^5t) -100\sin(10^5t)$$

***%1 accuracy Ignore Resistance.


$$b) i(t)=0.1\cos(10t) \quad V_R=i(t)R_s=0.1\cos(10t)$$

$$V_L=L(di/dt)=-0.01\sin(10t)$$

*** Resistance cannot be ignored

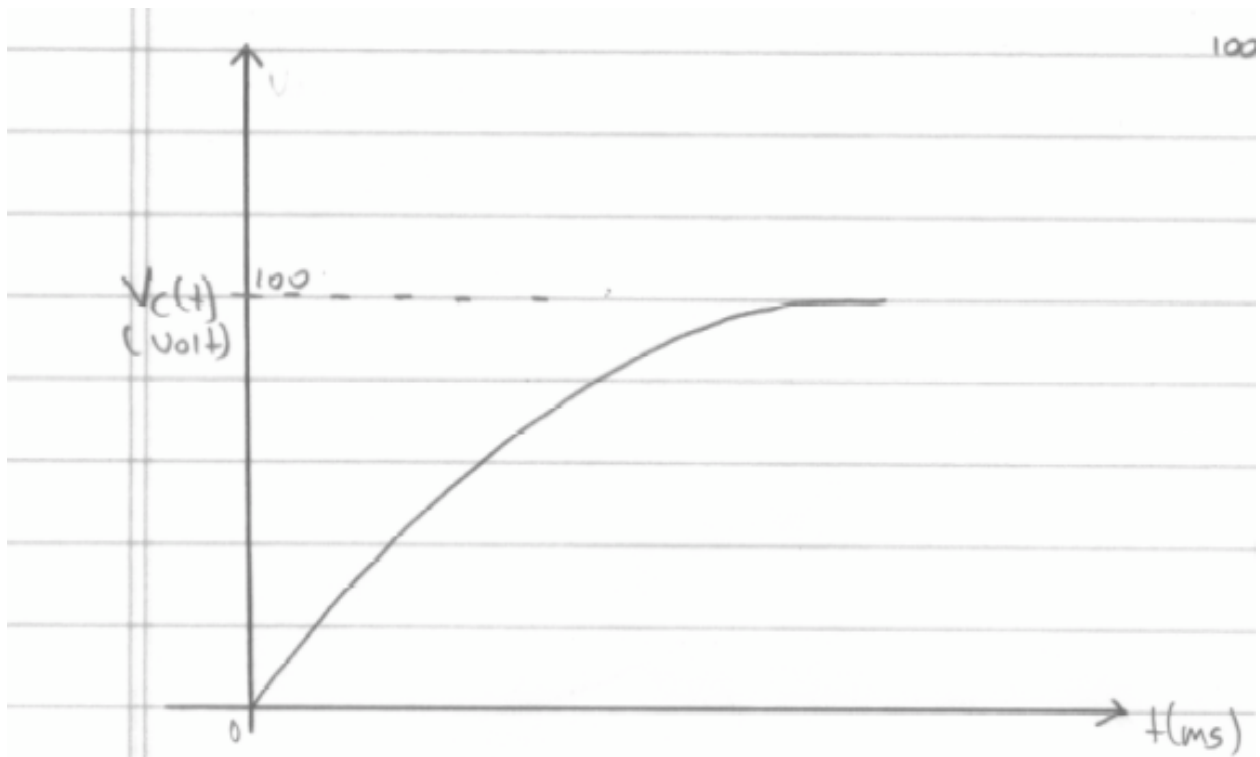4.3

$$V_c(t) = V_s - V_s \cdot e^{-t/R_c} = 100 - 100 e^{-1000t} \quad R_c = 1/1000 = 1\text{ms}$$



4.7

$$a) \quad V_c(t) = V_i e^{-t/Rc} = 50 e^{-50t} \quad V_c(t) = 50 e^{-50t} \quad t > 0$$

$$V_c(t) = 50 \quad t < 0$$

$$V_r(t) = V_c(t) \quad t > 0 \quad V_c(t) = 0 \quad t < 0$$

$$P(t) = i(t)V(t) = V(t)^2 / R = 2500 e^{-100t} \text{ MW}$$


$$W_r = \int P_R dt = 25 \text{ MJ}$$

$$W_c = 1/2 CV^2 = 1/2 (0.02 \cdot 10^{-6} \cdot 50^2) = 25 \text{ MJ}$$

4.20

$$i_1=0 \quad i_2=2A \quad i_3=2A$$

Equivalent circuit for Steady-state:

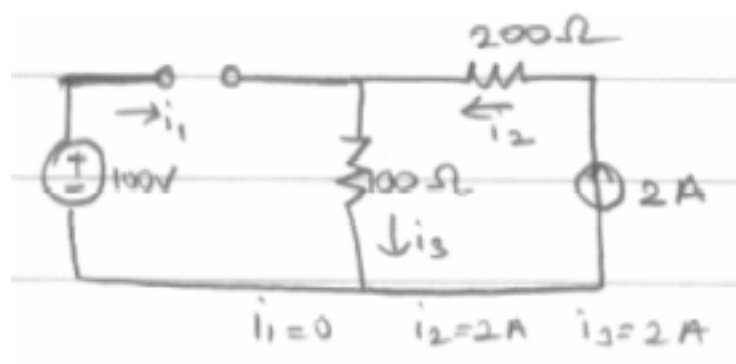

4.27

$$i_R=2mA \quad V_R=L_R R=20V \quad V_C=V_R+15V=35V$$

4.33

$$i_L(t=0)=0$$

$$i_L(t)=K_1+K_2e^{-Rt/L} \quad V(t)=di(t)/dt$$

At $t=0$; $i_L(t)=K_1+K_2=0$

At $t=\infty$; $i_L(t)=K_1=0.1$ $K_2=-K_1=-0.1$

$i_L(t)=0$ $t=0$
 $i_L(t)=0.1-0.1e^{-E6t}$ $t>0$

$V_t = L(di/dt)$

$V(t)=0$ $t<0$
 $V(t)=100 e^{-E6t}$ $t>0$

